

▷ **10: Digital Filter Structures**

Direct Forms

Transposition

State Space +

Precision Issues

Coefficient Sensitivity

Cascaded Biquads

Pole-zero

Pairing/Ordering

Linear Phase

Hardware

Implementation

Allpass Filters

Lattice Stage +

Example

$A(z) \leftrightarrow D(z)$

Allpass Lattice

Lattice Filter

Lattice Example

Lattice Example

Numerator

Summary

MATLAB routines

10: Digital Filter Structures

Direct Forms

10: Digital Filter Structures

▷ Direct Forms

Transposition

State Space +

Precision Issues

Coefficient Sensitivity

Cascaded Biquads

Pole-zero

Pairing/Ordering

Linear Phase

Hardware

Implementation

Allpass Filters

Lattice Stage +

Example

$A(z) \leftrightarrow D(z)$

Allpass Lattice

Lattice Filter

Lattice Example

Lattice Example

Numerator

Summary

MATLAB routines

Filter: $H(z) = \frac{B(z)}{A(z)}$ with input $x[n]$ and output $y[n]$

$$y[n] = \sum_{k=0}^M b[k]x[n-k] - \sum_{k=1}^N a[k]y[n-k]$$



Direct forms use coefficients $a[k]$ and $b[k]$ directly

Direct Form 1:

- Direct implementation of difference equation
- Can view as $B(z)$ followed by $\frac{1}{A(z)}$

Direct Form II:

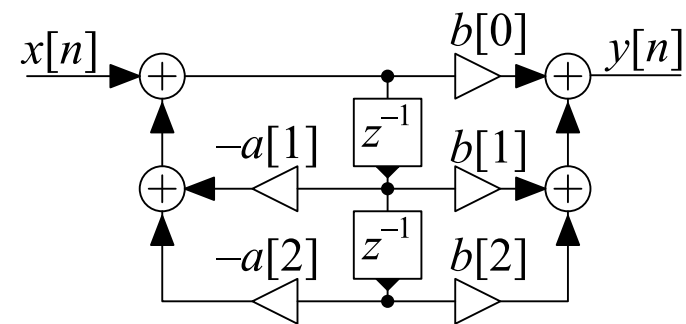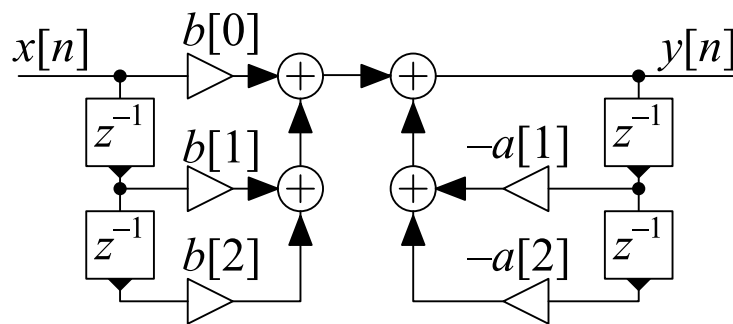- Implements $\frac{1}{A(z)}$ followed by $B(z)$
- Saves on delays (= storage)



Transposition

10: Digital Filter Structures

Direct Forms

▷ Transposition

State Space +

Precision Issues

Coefficient Sensitivity

Cascaded Biquads

Pole-zero

Pairing/Ordering

Linear Phase

Hardware

Implementation

Allpass Filters

Lattice Stage +

Example

$A(z) \leftrightarrow D(z)$

Allpass Lattice

Lattice Filter

Lattice Example

Lattice Example

Numerator

Summary

MATLAB routines

Can convert any block diagram into an equivalent **transposed form**:



- Reverse direction of each interconnection
- Reverse direction of each multiplier
- Change junctions to adders and vice-versa
- Interchange the input and output signals

Example:

Direct form II \rightarrow Direct Form II_t

Would normally be drawn with input on the left

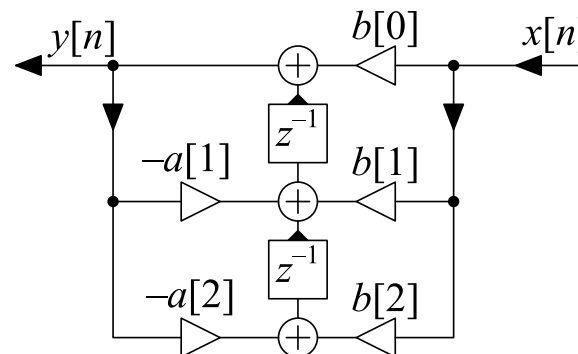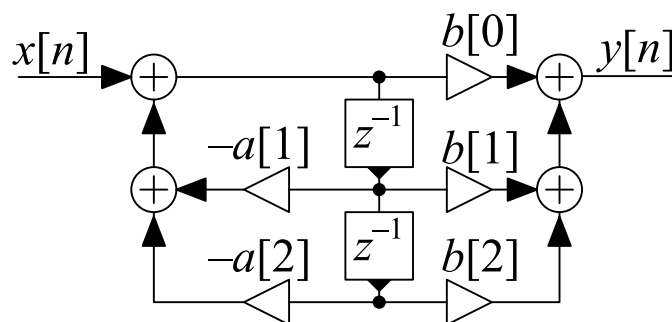Note: A valid block diagram must never have any feedback loops that don't go through a delay (z^{-1} block).



$\mathbf{v}[n]$ is a vector of **delay element outputs**

Can write: $\mathbf{v}[n + 1] = \mathbf{P}\mathbf{v}[n] + \mathbf{q}x[n]$

$$y[n] = \mathbf{r}^T \mathbf{v}[n] + sx[n]$$

$\{\mathbf{P}, \mathbf{q}, \mathbf{r}^T, s\}$ is the **state-space representation** of the filter structure.

The transfer function is given by:

$$H(z) = \frac{B(z)}{A(z)} = \frac{\det(z\mathbf{I} - \mathbf{P} + \mathbf{q}\mathbf{r}^T)}{\det(z\mathbf{I} - \mathbf{P})} + s - 1$$


The transposed form has $\mathbf{P} \rightarrow \mathbf{P}^T$ and $\mathbf{q} \leftrightarrow \mathbf{r} \Rightarrow$ same $H(z)$

Example: Direct Form II_t

$$\mathbf{P} = \begin{pmatrix} -a[1] & 1 \\ -a[2] & 0 \end{pmatrix} \quad \mathbf{q} = \begin{pmatrix} b[1] - b[0]a[1] \\ b[2] - b[0]a[2] \end{pmatrix}$$

$$\mathbf{r}^T = \begin{pmatrix} 1 & 0 \end{pmatrix} \quad s = b[0]$$
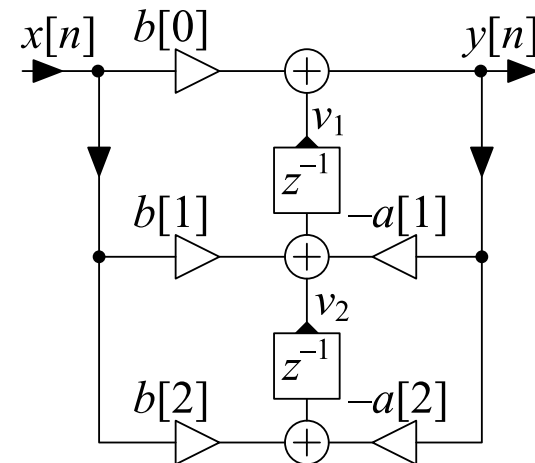
$$\text{From which } H(z) = \frac{b[0]z^2 + b[1]z + b[2]}{z^2 + a[1]z + a[2]}$$



[State-Space \rightarrow Transfer Function]

[This is not examinable]

We start by proving a useful formula which shows how the determinant of a matrix, \mathbf{A} , changes when you add a rank-1 matrix, $\mathbf{q}\mathbf{r}^T$, onto it. The formula is known as the Matrix Determinant Lemma. For any nonsingular matrix \mathbf{A} and column vectors \mathbf{q} and \mathbf{r} , we can write

$$\begin{pmatrix} 1 & \mathbf{r}^T \\ \mathbf{0} & \mathbf{A} \end{pmatrix} \begin{pmatrix} 1 + \mathbf{r}^T \mathbf{A}^{-1} \mathbf{q} & \mathbf{0}^T \\ -\mathbf{A}^{-1} \mathbf{q} & \mathbf{I} \end{pmatrix} = \begin{pmatrix} 1 & \mathbf{0}^T \\ -\mathbf{q} & \mathbf{I} \end{pmatrix} \begin{pmatrix} 1 & \mathbf{r}^T \\ \mathbf{0} & \mathbf{A} + \mathbf{q}\mathbf{r}^T \end{pmatrix}.$$

It is easy to verify this by multiplying out the matrices. We now take the determinant of both sides making use of the result that the determinant of a block triangular matrix is the product of the determinants of the blocks along the diagonal (assuming they are all square). This gives:

$$\det(\mathbf{A}) \times (1 + \mathbf{r}^T \mathbf{A}^{-1} \mathbf{q}) = \det(\mathbf{A} + \mathbf{q}\mathbf{r}^T) \quad \Rightarrow \quad \mathbf{r}^T \mathbf{A}^{-1} \mathbf{q} = \frac{\det(\mathbf{A} + \mathbf{q}\mathbf{r}^T)}{\det(\mathbf{A})} - 1$$

Now we take the z -transform of the state space equations

$$\begin{aligned} \mathbf{v}[n+1] &= \mathbf{P}\mathbf{v}[n] + \mathbf{q}x[n] && \xrightarrow{z\text{-transform}} && z\mathbf{V} = \mathbf{P}\mathbf{V} + \mathbf{q}X \\ y[n] &= \mathbf{r}^T \mathbf{v}[n] + sx[n] && && Y = \mathbf{r}^T \mathbf{V} + sX \end{aligned}$$

The upper equation gives $(z\mathbf{I} - \mathbf{P})\mathbf{V} = \mathbf{q}X$ from which $\mathbf{V} = (z\mathbf{I} - \mathbf{P})^{-1} \mathbf{q}X$ and by substituting this in the lower equation, we get $\frac{Y}{X} = \mathbf{r}^T (z\mathbf{I} - \mathbf{P})^{-1} \mathbf{q} + s = \frac{\det(z\mathbf{I} - \mathbf{P} + \mathbf{q}\mathbf{r}^T)}{\det(z\mathbf{I} - \mathbf{P})} + s - 1$.

Precision Issues

10: Digital Filter Structures

Direct Forms

Transposition

State Space +

▷ Precision Issues

Coefficient Sensitivity

Cascaded Biquads

Pole-zero

Pairing/Ordering

Linear Phase

Hardware

Implementation

Allpass Filters

Lattice Stage +

Example

$A(z) \leftrightarrow D(z)$

Allpass Lattice

Lattice Filter

Lattice Example

Lattice Example

Numerator

Summary

MATLAB routines

If all computations were exact, it would not make any difference which of the equivalent structures was used. However ...

- **Coefficient precision**

Coefficients are stored to finite precision and so are not exact. The filter actually implemented is therefore incorrect.

- **Arithmetic precision**

Arithmetic calculations are not exact.

- Worst case for arithmetic errors is when calculating the difference between two similar values:

$$1.23456789 - 1.23455678 = 0.00001111: 9 \text{ s.f.} \rightarrow 4 \text{ s.f.}$$

Arithmetic errors introduce noise that is then filtered by the transfer function between the point of noise creation and the output.

Coefficient Sensitivity

10: Digital Filter Structures

Direct Forms

Transposition

State Space

+

Precision Issues

 Coefficient

▷ Sensitivity

Cascaded Biquads

Pole-zero

Pairing/Ordering

Linear Phase

Hardware

Implementation

Allpass Filters

Lattice Stage

+

Example

$A(z) \leftrightarrow D(z)$

Allpass Lattice

Lattice Filter

Lattice Example

Lattice Example

Numerator

Summary

MATLAB routines

The roots of high order polynomials can be very sensitive to small changes in coefficient values.



Wilkinson's polynomial: (famous example)

$$f(x) = \prod_{n=1}^{20} (x - n) = x^{20} - 210x^{19} + 20615x^{18} - \dots$$

has roots well separated on the real axis.

Multiplying the coefficient of x^{19} by 1.000001 moves the roots a lot.

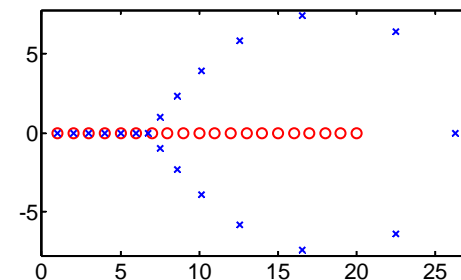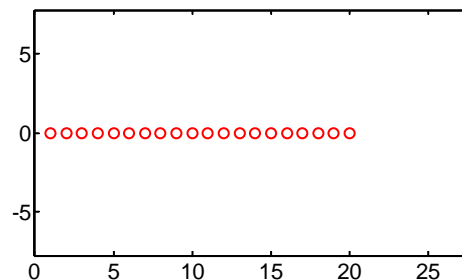“Speaking for myself I regard it as the most traumatic experience in my career as a numerical analyst”, James Wilkinson 1984



Moral: Avoid using direct form for filters orders over about 10.

Cascaded Biquads

Avoid high order polynomials by **factorizing into quadratic terms**:


$$\frac{B(z)}{A(z)} = g \frac{\prod (1 + b_{k,1}z^{-1} + b_{k,2}z^{-2})}{\prod (1 + a_{k,1}z^{-1} + a_{k,2}z^{-2})} = g \prod_{k=1}^K \frac{1 + b_{k,1}z^{-1} + b_{k,2}z^{-2}}{1 + a_{k,1}z^{-1} + a_{k,2}z^{-2}}$$

where $K = \max \left(\lceil \frac{M}{2} \rceil, \lceil \frac{N}{2} \rceil \right)$.

The term $\frac{1 + b_{k,1}z^{-1} + b_{k,2}z^{-2}}{1 + a_{k,1}z^{-1} + a_{k,2}z^{-2}}$ is a **biquad** (bi-quadratic section).

We need to choose:

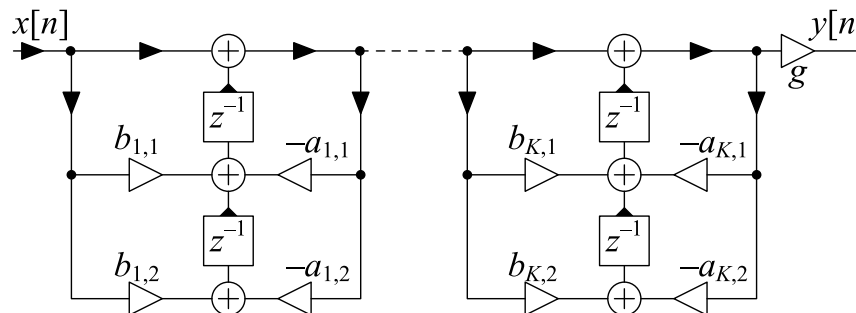- (a) which poles to **pair** with which zeros in each biquad
- (b) how to **order** the biquads



Direct Form II
Transposed

10: Digital Filter Structures

Direct Forms

Transposition

State Space +

Precision Issues

Coefficient Sensitivity

▷ Cascaded Biquads

Pole-zero

Pairing/Ordering

Linear Phase

Hardware

Implementation

Allpass Filters

Lattice Stage +

Example

$A(z) \leftrightarrow D(z)$

Allpass Lattice

Lattice Filter

Lattice Example

Lattice Example

Numerator

Summary

MATLAB routines

Pole-zero Pairing/Ordering

10: Digital Filter Structures

Direct Forms

Transposition

State Space +

Precision Issues

Coefficient Sensitivity

Cascaded Biquads

▷ Pole-zero Pairing/Ordering

Linear Phase

Hardware

Implementation

Allpass Filters

Lattice Stage +

Example

$A(z) \leftrightarrow D(z)$

Allpass Lattice

Lattice Filter

Lattice Example

Lattice Example

Numerator

Summary




MATLAB routines

Example: Elliptic lowpass filter

2 pole pairs and 2 zero pairs
need 2 biquads

Noise introduced in one biquad is amplified
by all the subsequent ones:

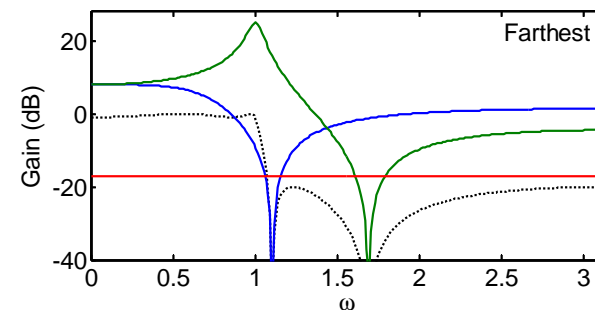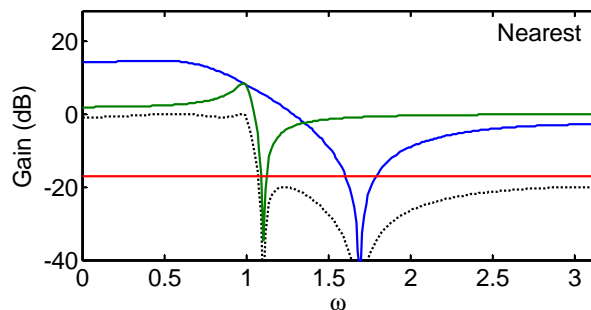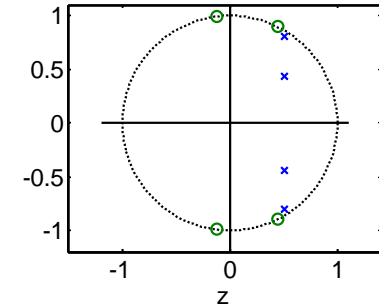- Make the peak gain of each biquad as small as possible
 - **Pair poles with nearest zeros** to get lowest peak gain
begin with the pole nearest the unit circle
 - Pairing with farthest zeros gives higher peak biquad gain
- Poles near the unit circle have the highest peaks and introduce most noise so **place them last in the chain**



Linear Phase


- 10: Digital Filter Structures
- Direct Forms
- Transposition
- State Space +
- Precision Issues
- Coefficient Sensitivity
- Cascaded Biquads
- Pole-zero
- Pairing/Ordering
- ▷ Linear Phase
- Hardware Implementation
- Allpass Filters
- Lattice Stage +
- Example
- $A(z) \leftrightarrow D(z)$
- Allpass Lattice
- Lattice Filter
- Lattice Example
- Lattice Example
- Numerator
- Summary
- MATLAB routines

Implementation can take advantage of any symmetry in the coefficients.

Linear phase filters are always FIR and have **symmetric** (or, more rarely, **antisymmetric**) coefficients.

$$\begin{aligned}
 H(z) &= \sum_{m=0}^M h[m]z^{-m} & h[M - m] &= h[m] \\
 &= h \left[\frac{M}{2} \right] z^{-\frac{M}{2}} + \sum_{m=0}^{\frac{M}{2}-1} h[m] (z^{-m} + z^{m-M}) & [m \text{ even}]
 \end{aligned}$$

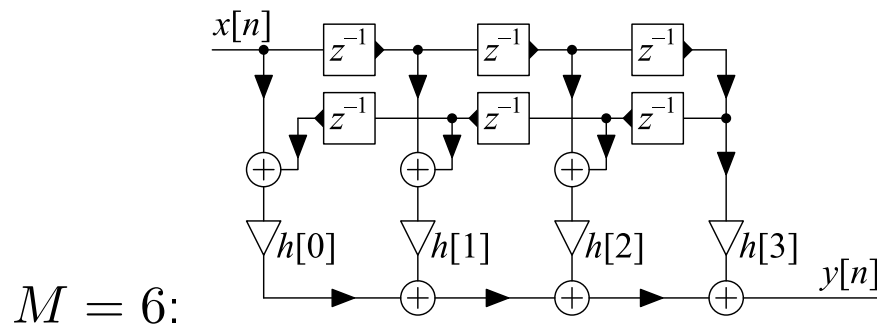For M even, we only need $\frac{M}{2} + 1$ multiplies instead of $M + 1$. We still need M additions and M delays.



For M odd (no central coefficient), we only need $\frac{M+1}{2}$ multiplies.

Hardware Implementation

10: Digital Filter Structures

Direct Forms

Transposition

State Space +

Precision Issues

Coefficient Sensitivity

Cascaded Biquads

Pole-zero

Pairing/Ordering

Linear Phase

Hardware

▷ Implementation

Allpass Filters

Lattice Stage +

Example

$A(z) \leftrightarrow D(z)$

Allpass Lattice

Lattice Filter

Lattice Example

Lattice Example

Numerator

Summary

MATLAB routines

Software Implementation:

All that matters is the total number of multiplies and adds

Hardware Implementation:

Delay elements (z^{-1}) represent storage registers



The maximum clock speed is limited by the number of sequential operations between registers

Example: Symmetric Linear Phase Filter

Direct form: Maximum sequential delay = $4a + m$

Transpose form: Maximum sequential delay = $a + m$ ☺

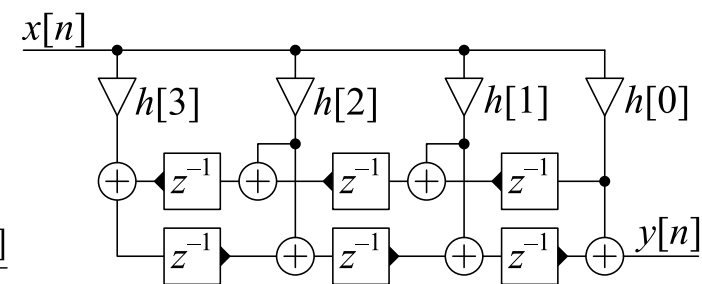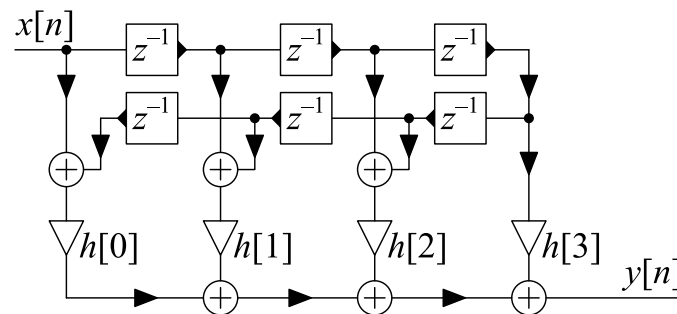a and *m* are the delays of adder and multiplier respectively



Allpass Filters

- 10: Digital Filter Structures
- Direct Forms
- Transposition
- State Space +
- Precision Issues
- Coefficient Sensitivity
- Cascaded Biquads
- Pole-zero Pairing/Ordering
- Linear Phase
- Hardware Implementation
- ▷ Allpass Filters
- Lattice Stage +
- Example
- $A(z) \leftrightarrow D(z)$
- Allpass Lattice
- Lattice Filter
- Lattice Example
- Lattice Example Numerator
- Summary
- MATLAB routines



Allpass filters have **mirror image** numerator and denominator coefficients:

$$b[n] = a[N - n] \quad \Leftrightarrow \quad B(z) = z^{-N} A(z^{-1})$$

$$\Rightarrow |H(e^{j\omega})| \equiv 1 \forall \omega$$

There are several efficient structures, e.g.

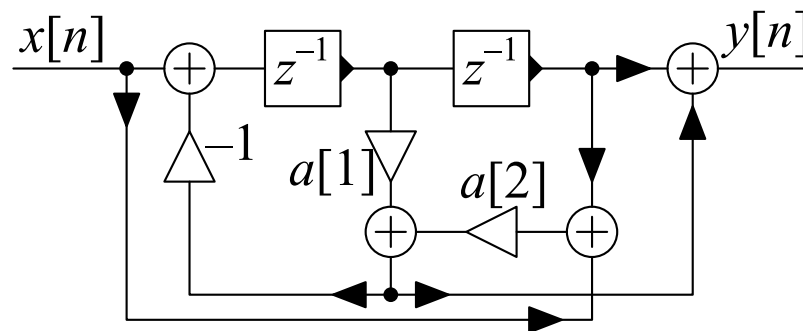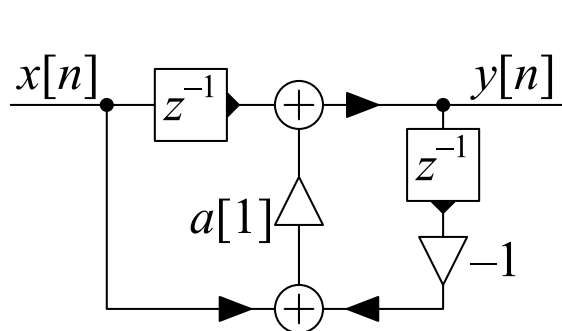- **First Order:** $H(z) = \frac{a[1] + z^{-1}}{1 + a[1]z^{-1}}$
- **Second Order:** $H(z) = \frac{a[2] + a[1]z^{-1} + z^{-2}}{1 + a[1]z^{-1} + a[2]z^{-2}}$



Allpass filters have a gain magnitude of 1 even with coefficient errors.


Suppose G is allpass: $G(z) = \frac{z^{-N} A(z^{-1})}{A(z)}$

$$V(z) = X(z) - kGz^{-1}V(z)$$

$$\Rightarrow V(z) = \frac{1}{1+kGz^{-1}} X(z)$$

$$Y(z) = kV(z) + Gz^{-1}V(z) = \frac{k+z^{-1}G}{1+kGz^{-1}} X(z)$$
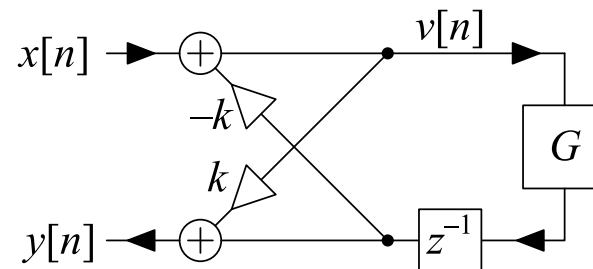
$$\frac{Y(z)}{X(z)} = \frac{kA(z)+z^{-N-1}A(z^{-1})}{A(z)+kz^{-N-1}A(z^{-1})} \triangleq \frac{z^{-(N+1)}D(z^{-1})}{D(z)}$$



Obtaining $\{d[n]\}$ from $\{a[n]\}$:

$$d[n] = \begin{cases} 1 & n = 0 \\ a[n] + ka[N+1-n] & 1 \leq n \leq N \\ k & n = N+1 \end{cases}$$

Obtaining $\{a[n]\}$ from $\{d[n]\}$:

$$k = d[N+1] \quad a[n] = \frac{d[n] - kd[N+1-n]}{1-k^2}$$

If $G(z)$ is stable then $\frac{Y(z)}{X(z)}$ is stable if and only if $|k| < 1$ (see note)

[Proof of Stability Criterion]

We want to show that if $G(z)$ is a stable allpass filter then $\frac{Y(z)}{X(z)} = \frac{k+z^{-1}G(z)}{1+kz^{-1}G(z)}$ is stable if and only if $|k| < 1$.

We make use of a property of allpass filters (proved in a note in lecture 5) that if $G(z)$ is a stable allpass filter, then $|G(z)| \begin{matrix} \geq \\ \leq \end{matrix} 1$ according to whether $|z| \begin{matrix} \leq \\ \geq \end{matrix} 1$.


If z is a root of the denominator $1 + kz^{-1}G(z)$, then

$$\begin{aligned} kz^{-1}G(z) &= -1 \\ \Rightarrow |k| \times |z^{-1}| \times |G(z)| &= 1 \\ \Rightarrow |k| &= \frac{|z|}{|G(z)|} \end{aligned}$$

It follows from the previously stated property of $G(z)$ that $|z| \begin{matrix} \leq \\ \geq \end{matrix} 1 \Leftrightarrow \frac{|z|}{|G(z)|} \begin{matrix} \leq \\ \geq \end{matrix} 1 \Leftrightarrow |k| \begin{matrix} \leq \\ \geq \end{matrix} 1$.

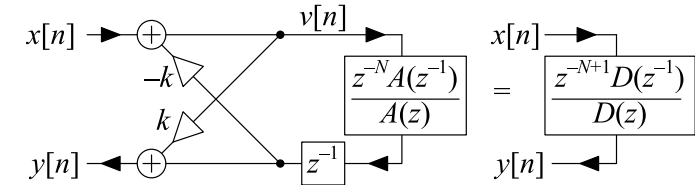Example $A(z) \leftrightarrow D(z)$

Suppose $N = 3$, $k = 0.5$ and
 $A(z) = 1 + 4z^{-1} - 6z^{-2} + 10z^{-3}$



$A(z) \rightarrow D(z)$

	z^0	z^{-1}	z^{-2}	z^{-3}	z^{-4}
$A(z)$	1	4	-6	10	
$z^{-4}A(z^{-1})$		10	-6	4	1
$D(z) = A(z) + kz^{-4}A(z^{-1})$	1	9	-9	12	0.5

$D(z) \rightarrow A(z)$

	z^0	z^{-1}	z^{-2}	z^{-3}	z^{-4}
$D(z)$	1	9	-9	12	0.5
$k = d[N + 1]$					0.5
$z^{-4}D(z^{-1})$	0.5	12	-9	9	1
$D(z) - kz^{-4}D(z^{-1})$	0.75	3	-4.5	7.5	0
$A(z) = \frac{D(z) - kz^{-4}D(z^{-1})}{1 - k^2}$	1	4	-6	10	0

- 10: Digital Filter Structures
- Direct Forms
- Transposition
- State Space +
- Precision Issues
- Coefficient Sensitivity
- Cascaded Biquads
- Pole-zero Pairing/Ordering
- Linear Phase
- Hardware Implementation
- Allpass Filters
- Lattice Stage +
- Example
- ▷ $A(z) \leftrightarrow D(z)$
- Allpass Lattice
- Lattice Filter
- Lattice Example
- Lattice Example Numerator
- Summary
- MATLAB routines

Allpass Lattice

10: Digital Filter Structures

Direct Forms

Transposition

State Space +

Precision Issues

Coefficient Sensitivity

Cascaded Biquads

Pole-zero

Pairing/Ordering

Linear Phase

Hardware

Implementation

Allpass Filters

Lattice Stage +

Example

$A(z) \leftrightarrow D(z)$

▷ Allpass Lattice

Lattice Filter

Lattice Example

Lattice Example

Numerator

Summary


MATLAB routines

We can implement **any allpass filter** $H(z) = \frac{z^{-M} A(z^{-1})}{A(z)}$ as a lattice filter with M stages:


- Initialize $A_M(z) = A(z)$
- Repeat for $m = M : -1 : 1$
 - $k[m] = a_m[m]$
 - $a_{m-1}[n] = \frac{a_m[n] - k[m]a_m[m-n]}{1 - k^2[m]}$ for $0 \leq n \leq m - 1$

equivalently $A_{m-1}(z) = \frac{A_m(z) - k[m]z^{-m}A_m(z^{-1})}{1 - k^2[m]}$

$A(z)$ is stable iff $|k[m]| < 1$ for all m (good stability test)

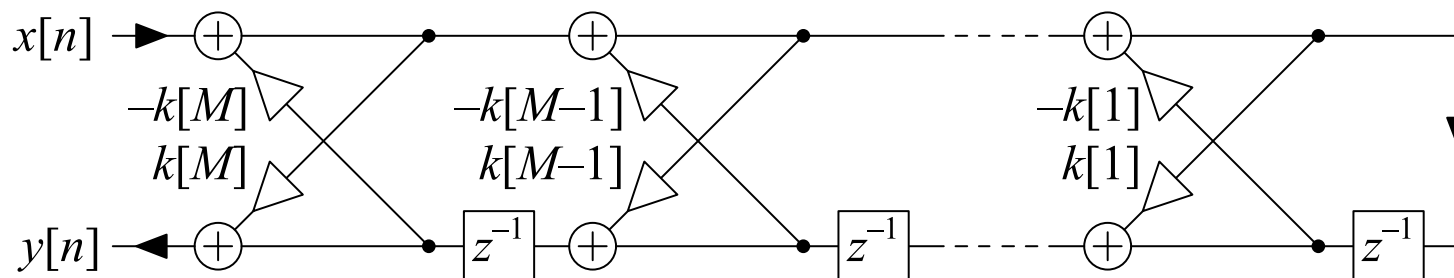

Lattice Filter

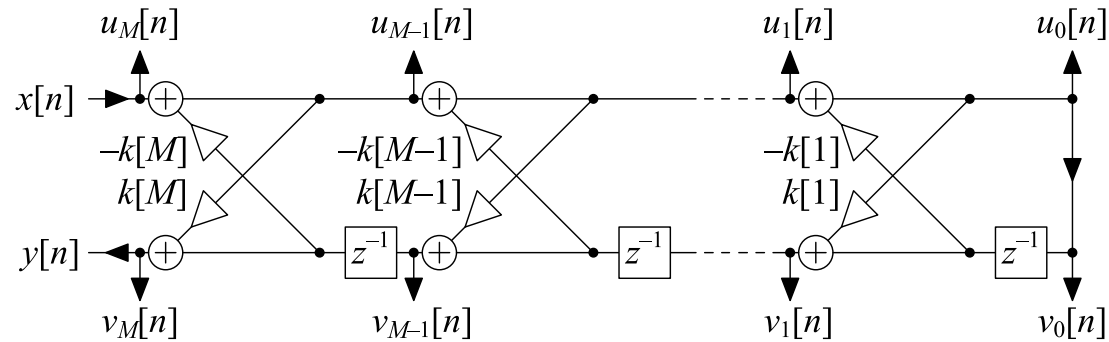

Label outputs $u_m[n]$ and $v_m[n]$ and define $H_m(z) = \frac{V_m(z)}{U_m(z)} = \frac{z^{-m} A_m(z^{-1})}{A_m(z)}$

From earlier slide (slide 12):

$$\frac{U_{m-1}(z)}{U_m(z)} = \frac{1}{1+k[m]z^{-1}H_{m-1}(z)} = \frac{A_{m-1}(z)}{A_{m-1}(z)+k[m]z^{-m}A_{m-1}(z^{-1})} = \frac{A_{m-1}(z)}{A_m(z)}$$


Hence:

$$\frac{U_m(z)}{X(z)} = \frac{A_m(z)}{A(z)} \quad \text{and} \quad \frac{V_m(z)}{X(z)} = \frac{U_m(z)}{X(z)} \times \frac{V_m(z)}{U_m(z)} = \frac{z^{-m} A_m(z^{-1})}{A(z)}$$

The numerator of $\frac{V_m(z)}{X(z)}$ is of order m so you can create **any numerator of order M** by summing appropriate multiples of $V_m(z)$:

$$w[n] = \sum_{m=0}^M c_m v_m[n] \quad \Rightarrow \quad W(z) = \frac{\sum_{m=0}^M c_m z^{-m} A_m(z^{-1})}{A(z)}$$

Lattice Example

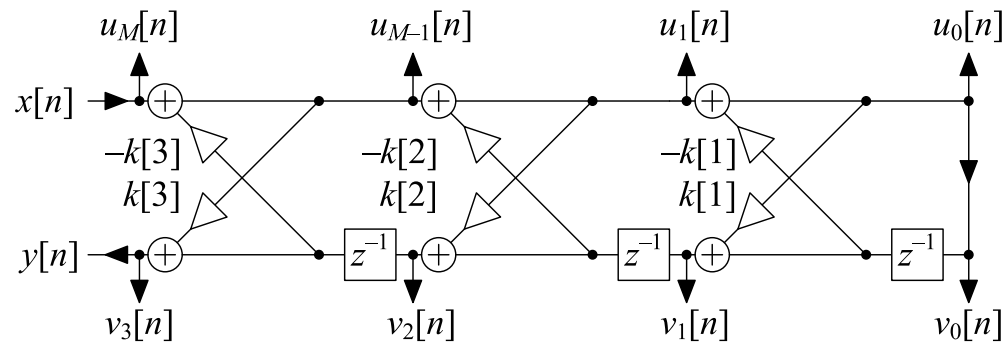

$$A(z) = A_3(z) = 1 + 0.2z^{-1} - 0.23z^{-2} + 0.2z^{-3}$$

- $k[3] = 0.2 \Rightarrow a_2[\] = \frac{[1, 0.2, -0.23] - 0.2[0.2, -0.23, 0.2]}{1 - 0.2^2} = [1, 0.256, -0.281]$
- $k[2] = -0.281 \Rightarrow a_1[\] = \frac{[1, 0.256] + 0.281[-0.281, 0.256]}{1 - 0.281^2} = [1, 0.357]$
- $k[1] = 0.357 \Rightarrow a_0[\] = 1$

$$\frac{V_0(z)}{X(z)} = \frac{1}{1 + 0.2z^{-1} - 0.23z^{-2} + 0.2z^{-3}}$$

$$\frac{V_1(z)}{X(z)} = \frac{0.357 + z^{-1}}{1 + 0.2z^{-1} - 0.23z^{-2} + 0.2z^{-3}}$$

$$\frac{V_2(z)}{X(z)} = \frac{-0.281 + 0.256z^{-1} + z^{-2}}{1 + 0.2z^{-1} - 0.23z^{-2} + 0.2z^{-3}}$$


$$\frac{V_3(z)}{X(z)} = \frac{0.2 - 0.23z^{-1} + 0.2z^{-2} + z^{-3}}{1 + 0.2z^{-1} - 0.23z^{-2} + 0.2z^{-3}}$$

Add together multiples of $\frac{V_m(z)}{X(z)}$ to create an arbitrary $\frac{B(z)}{1 + 0.2z^{-1} - 0.23z^{-2} + 0.2z^{-3}}$

Lattice Example Numerator

Form a new output signal as $w[n] = \sum_{m=0}^M c_m v_m[n]$
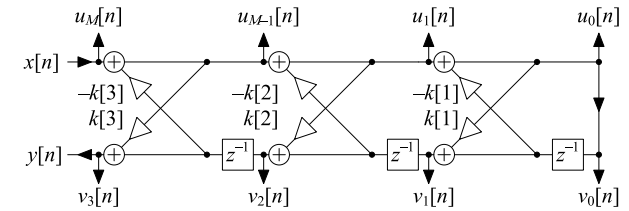
$$W(z) = \sum_{m=0}^M c_m V_m(z) = \frac{B(z)}{1+0.2z^{-1}-0.23z^{-2}+0.2z^{-3}} X(z)$$



$$\frac{V_0(z)}{X(z)} = \frac{1}{1+0.2z^{-1}-0.23z^{-2}+0.2z^{-3}} \quad \frac{V_1(z)}{X(z)} = \frac{0.357+z^{-1}}{1+0.2z^{-1}-0.23z^{-2}+0.2z^{-3}}$$

$$\frac{V_2(z)}{X(z)} = \frac{-0.281+0.256z^{-1}+z^{-2}}{1+0.2z^{-1}-0.23z^{-2}+0.2z^{-3}} \quad \frac{V_3(z)}{X(z)} = \frac{0.2-0.23z^{-1}+0.2z^{-2}+z^{-3}}{1+0.2z^{-1}-0.23z^{-2}+0.2z^{-3}}$$

We have
$$\begin{pmatrix} b[0] \\ b[1] \\ b[2] \\ b[3] \end{pmatrix} = \begin{pmatrix} 1 & 0.357 & -0.281 & 0.2 \\ 0 & 1 & 0.256 & -0.23 \\ 0 & 0 & 1 & 0.2 \\ 0 & 0 & 0 & 1 \end{pmatrix} \begin{pmatrix} c_0 \\ c_1 \\ c_2 \\ c_3 \end{pmatrix}$$

Hence choose c_m as
$$\begin{pmatrix} c_0 \\ c_1 \\ c_2 \\ c_3 \end{pmatrix} = \begin{pmatrix} 1 & 0.357 & -0.281 & 0.2 \\ 0 & 1 & 0.256 & -0.23 \\ 0 & 0 & 1 & 0.2 \\ 0 & 0 & 0 & 1 \end{pmatrix}^{-1} \begin{pmatrix} b[0] \\ b[1] \\ b[2] \\ b[3] \end{pmatrix}$$

Summary

10: Digital Filter Structures

Direct Forms

Transposition

State Space +

Precision Issues

Coefficient Sensitivity

Cascaded Biquads

Pole-zero

Pairing/Ordering

Linear Phase

Hardware

Implementation

Allpass Filters

Lattice Stage +

Example

$A(z) \leftrightarrow D(z)$

Allpass Lattice

Lattice Filter

Lattice Example

Lattice Example

Numerator

▷ Summary

MATLAB routines

- Filter block diagrams
 - Direct forms
 - Transposition
 - State space representation
- Precision issues: coefficient error, arithmetic error
 - cascaded biquads
- Allpass filters
 - first and second order sections
- Lattice filters
 - Arbitrary allpass response
 - Arbitrary IIR response by summing intermediate outputs

For further details see Mitra: 8.

MATLAB routines

10: Digital Filter Structures

Direct Forms

Transposition

State Space +

Precision Issues

Coefficient Sensitivity

Cascaded Biquads

Pole-zero

Pairing/Ordering

Linear Phase

Hardware

Implementation

Allpass Filters

Lattice Stage +

Example

$A(z) \leftrightarrow D(z)$

Allpass Lattice

Lattice Filter

Lattice Example

Lattice Example

Numerator

Summary

▷ MATLAB routines

residuez	$\frac{b(z^{-1})}{a(z^{-1})} \rightarrow \sum_k \frac{r_k}{1-p_k z^{-1}}$
tf2sos,sos2tf	$\frac{b(z^{-1})}{a(z^{-1})} \leftrightarrow \prod_l \frac{b_{0,l}+b_{1,l}z^{-1}+b_{2,l}z^{-2}}{1+a_{1,l}z^{-1}+a_{2,l}z^{-2}}$
zp2sos,sos2zp	$\{z_m, p_k, g\} \leftrightarrow \prod_l \frac{b_{0,l}+b_{1,l}z^{-1}+b_{2,l}z^{-2}}{1+a_{\in 1,l}z^{-1}+a_{2,l}z^{-2}}$
zp2ss,ss2zp	$\{z_m, p_k, g\} \leftrightarrow \begin{cases} x' = Ax + Bu \\ y = Cx + Du \end{cases}$
tf2ss,ss2tf	$\frac{b(z^{-1})}{a(z^{-1})} \leftrightarrow \begin{cases} x' = Ax + Bu \\ y = Cx + Du \end{cases}$
poly	$\text{poly}(\mathbf{A}) = \det(z\mathbf{I}-\mathbf{A})$