

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1:
Label Nodes
- Nodal Analysis Stage 2:
KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog
Converter
- Dependent Sources
- Dependent Voltage
Sources
- Universal Nodal Analysis
Algorithm
- Summary

3: Nodal Analysis

Aim of Nodal Analysis

3: Nodal Analysis

- **Aim of Nodal Analysis**
- Nodal Analysis Stage 1:
Label Nodes
- Nodal Analysis Stage 2:
KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog
Converter
- Dependent Sources
- Dependent Voltage
Sources
- Universal Nodal Analysis
Algorithm
- Summary

The aim of nodal analysis is to determine the voltage at each node relative to the reference node (or ground). Once you have done this you can easily work out anything else you need.

Aim of Nodal Analysis

3: Nodal Analysis

- **Aim of Nodal Analysis**
- Nodal Analysis Stage 1:
Label Nodes
- Nodal Analysis Stage 2:
KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog
Converter
- Dependent Sources
- Dependent Voltage
Sources
- Universal Nodal Analysis
Algorithm
- Summary

The aim of nodal analysis is to determine the voltage at each node relative to the reference node (or ground). Once you have done this you can easily work out anything else you need.

There are two ways to do this:

(1) **Nodal Analysis** - systematic; always works

(2) **Circuit Manipulation** - ad hoc; but can be less work and clearer

Aim of Nodal Analysis

3: Nodal Analysis

● Aim of Nodal Analysis

- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

The aim of nodal analysis is to determine the voltage at each node relative to the reference node (or ground). Once you have done this you can easily work out anything else you need.

There are two ways to do this:


(1) **Nodal Analysis** - systematic; always works

(2) **Circuit Manipulation** - ad hoc; but can be less work and clearer

Reminders:

A node is all the points in a circuit that are directly interconnected.

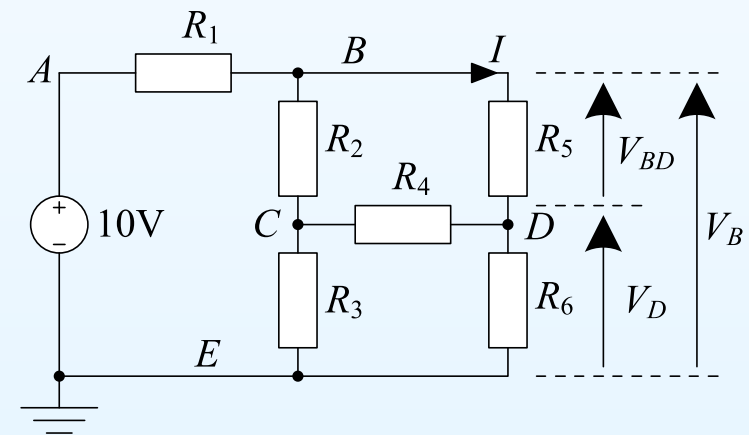We assume the interconnections have zero resistance so all points within a node have the same voltage. Five nodes: A, \dots, E .



Aim of Nodal Analysis

3: Nodal Analysis

- **Aim of Nodal Analysis**
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

The aim of nodal analysis is to determine the voltage at each node relative to the reference node (or ground). Once you have done this you can easily work out anything else you need.

There are two ways to do this:

(1) **Nodal Analysis** - systematic; always works


(2) **Circuit Manipulation** - ad hoc; but can be less work and clearer

Reminders:

A node is all the points in a circuit that are directly interconnected.

We assume the interconnections have zero resistance so all points within a node have the same voltage. Five nodes: A, \dots, E .

Ohm's Law: $V_{BD} = IR_5$

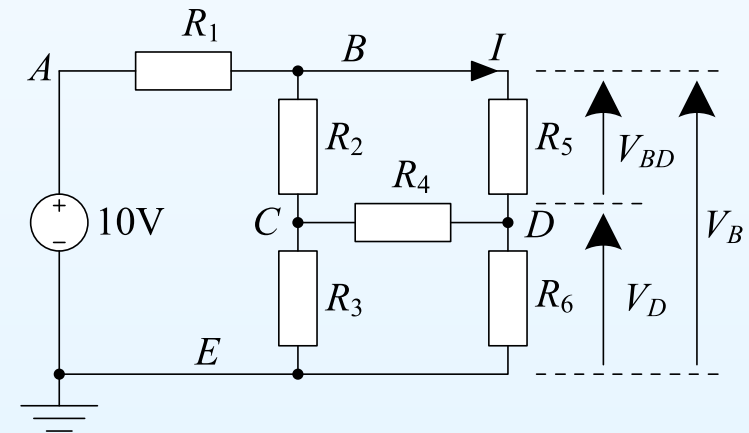

Aim of Nodal Analysis

3: Nodal Analysis

● Aim of Nodal Analysis

- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

The aim of nodal analysis is to determine the voltage at each node relative to the reference node (or ground). Once you have done this you can easily work out anything else you need.

There are two ways to do this:

(1) **Nodal Analysis** - systematic; always works

(2) **Circuit Manipulation** - ad hoc; but can be less work and clearer


Reminders:

A node is all the points in a circuit that are directly interconnected.

We assume the interconnections have zero resistance so all points within a node have the same voltage. Five nodes: A, \dots, E .

Ohm's Law: $V_{BD} = IR_5$

KVL: $V_{BD} = V_B - V_D$

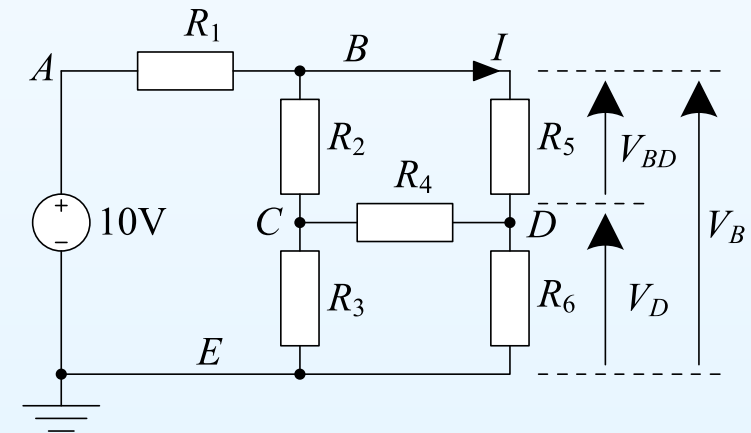

Aim of Nodal Analysis

3: Nodal Analysis

- **Aim of Nodal Analysis**
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

The aim of nodal analysis is to determine the voltage at each node relative to the reference node (or ground). Once you have done this you can easily work out anything else you need.

There are two ways to do this:

- (1) **Nodal Analysis** - systematic; always works
- (2) **Circuit Manipulation** - ad hoc; but can be less work and clearer

Reminders:


A node is all the points in a circuit that are directly interconnected.

We assume the interconnections have zero resistance so all points within a node have the same voltage. Five nodes: A, \dots, E .

Ohm's Law: $V_{BD} = IR_5$

KVL: $V_{BD} = V_B - V_D$

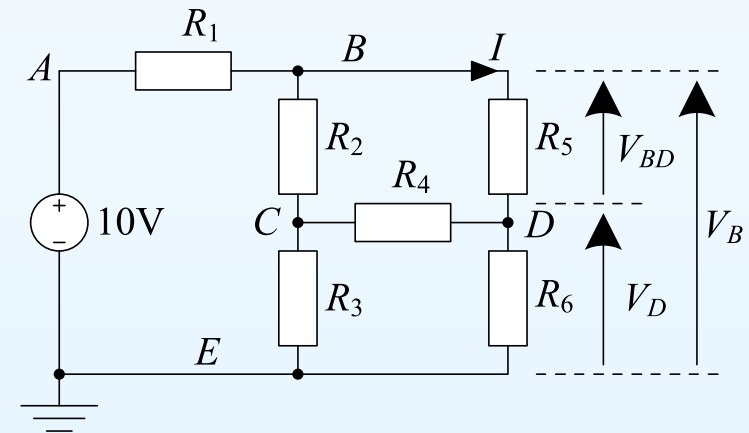KCL: Total current exiting any closed region is zero.




Nodal Analysis Stage 1: Label Nodes

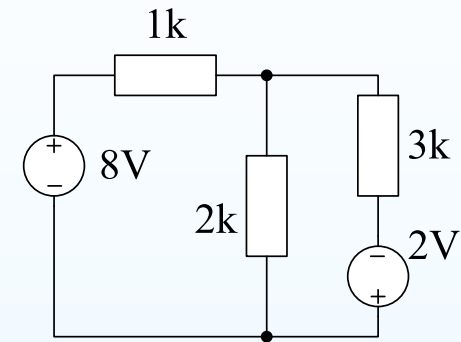3: Nodal Analysis

- Aim of Nodal Analysis
- **Nodal Analysis Stage 1: Label Nodes**
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

To find the voltage at each node, the first step is to label each node with its voltage as follows




- (1) Pick any node as the voltage reference. Label its voltage as 0 V .
- (2) If any fixed voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with X , Y , \dots , then go back to step (2) until all nodes are labelled.

Nodal Analysis Stage 1: Label Nodes

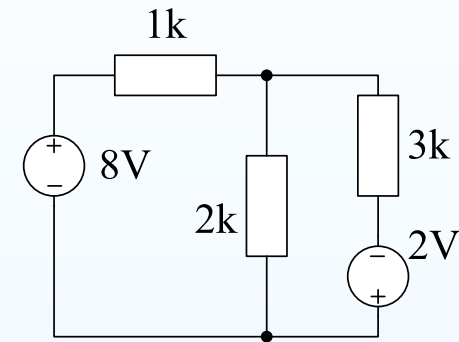3: Nodal Analysis

- Aim of Nodal Analysis
- **Nodal Analysis Stage 1: Label Nodes**
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

To find the voltage at each node, the first step is to label each node with its voltage as follows




- (1) Pick any node as the voltage reference. Label its voltage as 0 V .
- (2) If any fixed voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with X , Y , \dots , then go back to step (2) until all nodes are labelled.

Nodal Analysis Stage 1: Label Nodes

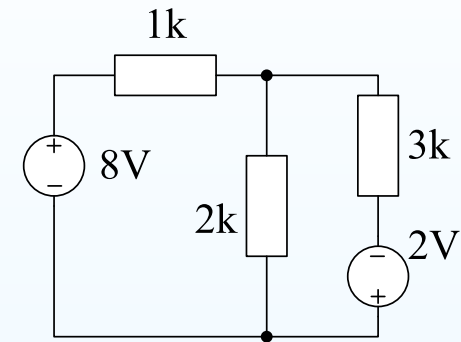3: Nodal Analysis

- Aim of Nodal Analysis
- **Nodal Analysis Stage 1: Label Nodes**
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary


To find the voltage at each node, the first step is to label each node with its voltage as follows



(1) Pick any node as the voltage reference. Label its voltage as 0 V .

(2) If any fixed voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.

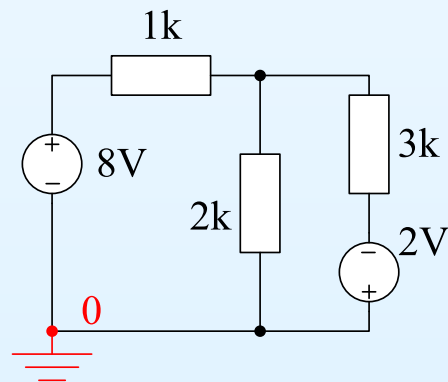(3) Pick an unlabelled node and label it with X , Y , \dots , then go back to step (2) until all nodes are labelled.




Nodal Analysis Stage 1: Label Nodes

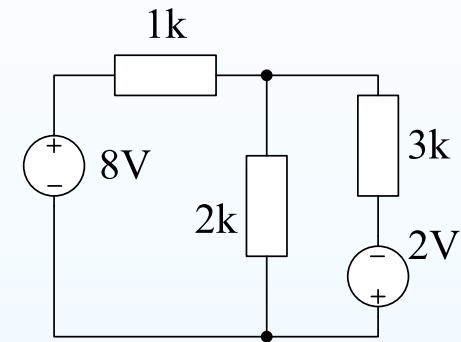
3: Nodal Analysis

- Aim of Nodal Analysis
- **Nodal Analysis Stage 1: Label Nodes**
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

To find the voltage at each node, the first step is to label each node with its voltage as follows



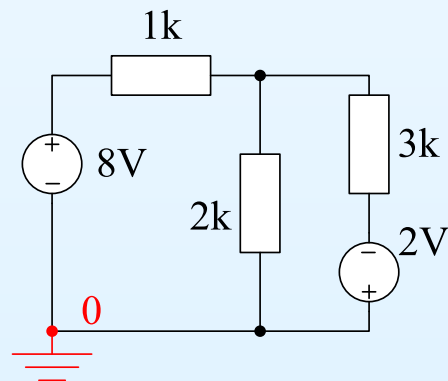- (1) Pick any node as the voltage reference. Label its voltage as 0 V .
- (2) If any fixed voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with X , Y , \dots , then go back to step (2) until all nodes are labelled.




Nodal Analysis Stage 1: Label Nodes

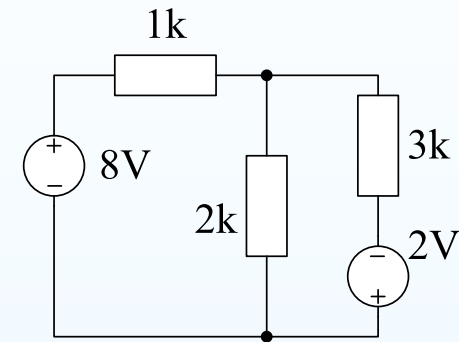
3: Nodal Analysis

- Aim of Nodal Analysis
- **Nodal Analysis Stage 1: Label Nodes**
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

To find the voltage at each node, the first step is to label each node with its voltage as follows



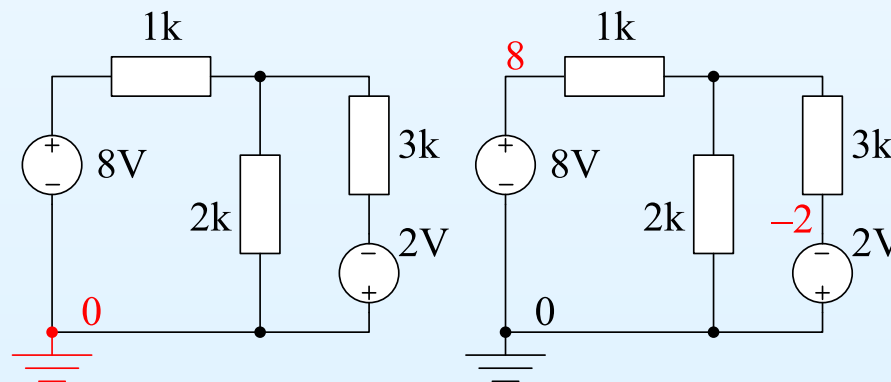- (1) Pick any node as the voltage reference. Label its voltage as 0 V .
- (2) If any fixed voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with X , Y , \dots , then go back to step (2) until all nodes are labelled.




Nodal Analysis Stage 1: Label Nodes

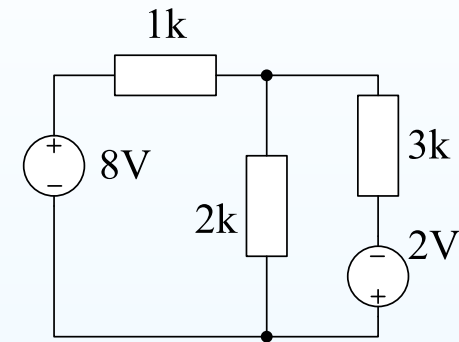
3: Nodal Analysis

- Aim of Nodal Analysis
- **Nodal Analysis Stage 1: Label Nodes**
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

To find the voltage at each node, the first step is to label each node with its voltage as follows



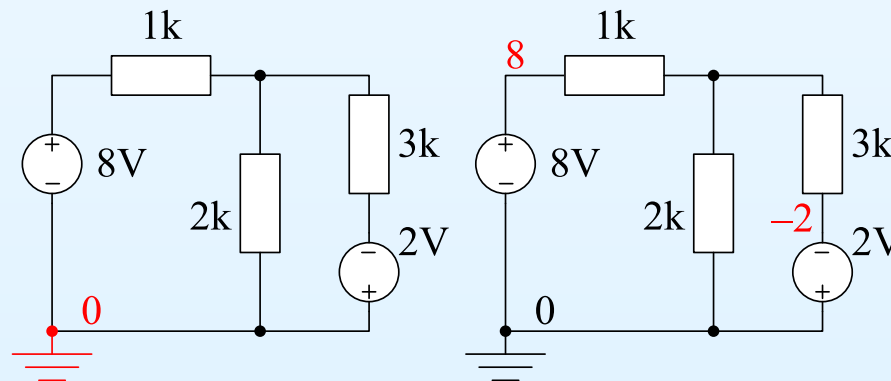- (1) Pick any node as the voltage reference. Label its voltage as 0 V .
- (2) If any fixed voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with X , Y , \dots , then go back to step (2) until all nodes are labelled.




Nodal Analysis Stage 1: Label Nodes



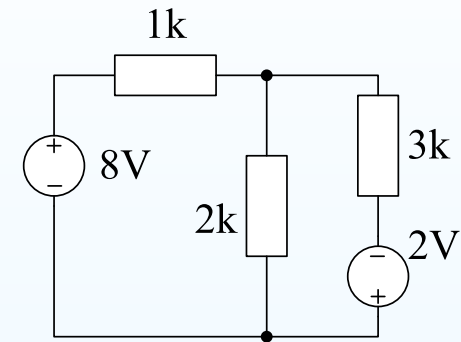
3: Nodal Analysis

- Aim of Nodal Analysis
- **Nodal Analysis Stage 1: Label Nodes**
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

To find the voltage at each node, the first step is to label each node with its voltage as follows



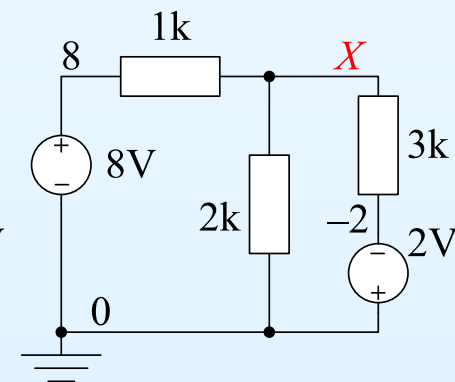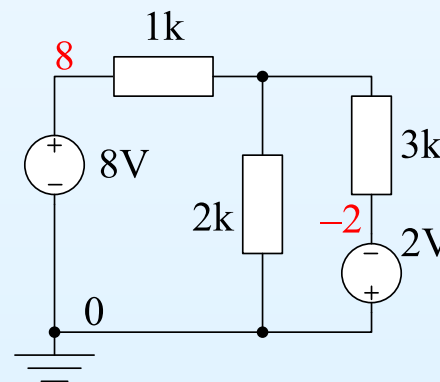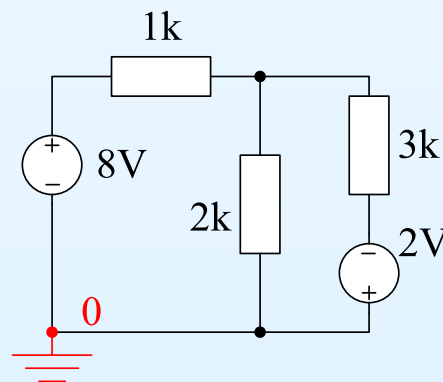- (1) Pick any node as the voltage reference. Label its voltage as 0 V .
- (2) If any fixed voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with X , Y , \dots , then go back to step (2) until all nodes are labelled.




Nodal Analysis Stage 2: KCL Equations

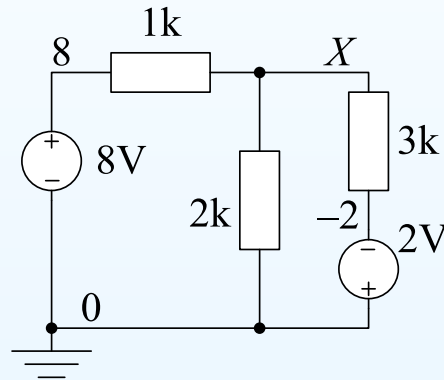3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- **Nodal Analysis Stage 2: KCL Equations**
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

The second step is to write down a KCL equation for each node labelled with a variable by setting the total current flowing out of the node to zero. For a circuit with N nodes and S voltage sources you will have $N - S - 1$ simultaneous equations to solve.





Nodal Analysis Stage 2: KCL Equations

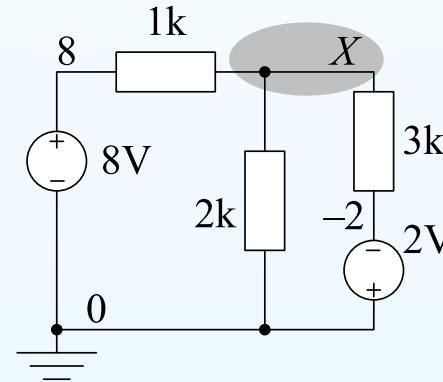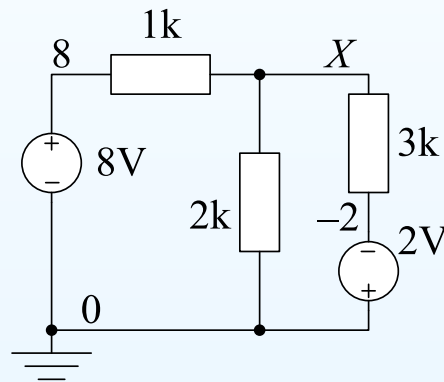3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- **Nodal Analysis Stage 2: KCL Equations**
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

The second step is to write down a KCL equation for each node labelled with a variable by setting the total current flowing out of the node to zero. For a circuit with N nodes and S voltage sources you will have $N - S - 1$ simultaneous equations to solve.



We only have one variable:



$$\frac{X-8}{1\text{ k}} + \frac{X-0}{2\text{ k}} + \frac{X-(-2)}{3\text{ k}} = 0$$

Nodal Analysis Stage 2: KCL Equations

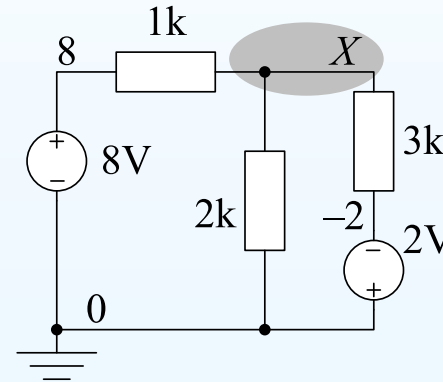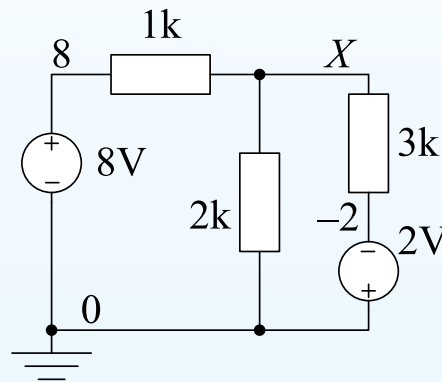3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- **Nodal Analysis Stage 2: KCL Equations**
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

The second step is to write down a KCL equation for each node labelled with a variable by setting the total current flowing out of the node to zero. For a circuit with N nodes and S voltage sources you will have $N - S - 1$ simultaneous equations to solve.



We only have one variable:

$$\frac{X-8}{1\text{ k}} + \frac{X-0}{2\text{ k}} + \frac{X-(-2)}{3\text{ k}} = 0$$



Numerator for a resistor is always of the form $X - V_N$ where V_N is the voltage on the other side of the resistor.

Nodal Analysis Stage 2: KCL Equations

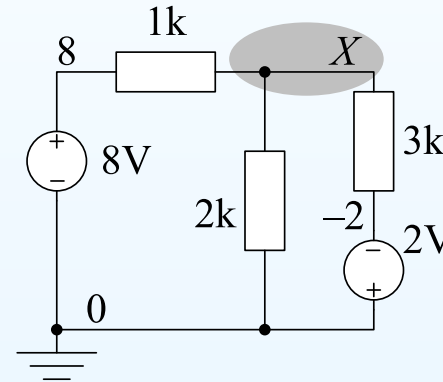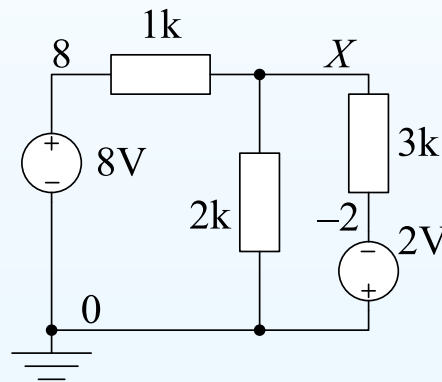3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- **Nodal Analysis Stage 2: KCL Equations**
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

The second step is to write down a KCL equation for each node labelled with a variable by setting the total current flowing out of the node to zero. For a circuit with N nodes and S voltage sources you will have $N - S - 1$ simultaneous equations to solve.



We only have one variable:

$$\frac{X-8}{1\text{ k}} + \frac{X-0}{2\text{ k}} + \frac{X-(-2)}{3\text{ k}} = 0 \Rightarrow (6X - 48) + 3X + (2X + 4) = 0$$



Numerator for a resistor is always of the form $X - V_N$ where V_N is the voltage on the other side of the resistor.

Nodal Analysis Stage 2: KCL Equations

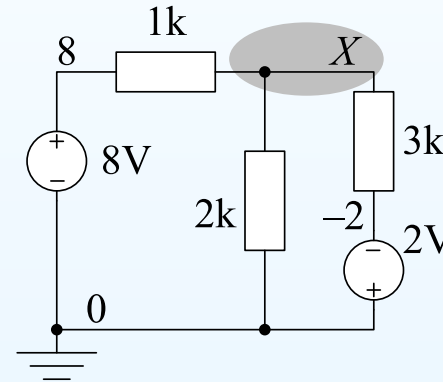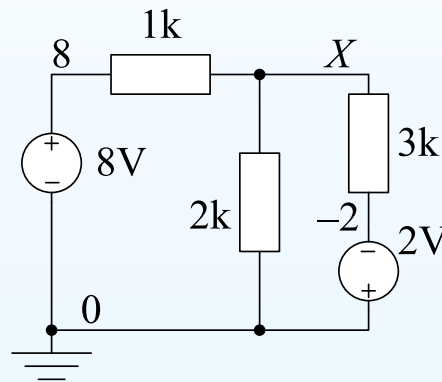3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- **Nodal Analysis Stage 2: KCL Equations**
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

The second step is to write down a KCL equation for each node labelled with a variable by setting the total current flowing out of the node to zero. For a circuit with N nodes and S voltage sources you will have $N - S - 1$ simultaneous equations to solve.



We only have one variable:

$$\frac{X-8}{1\text{ k}} + \frac{X-0}{2\text{ k}} + \frac{X-(-2)}{3\text{ k}} = 0 \Rightarrow (6X - 48) + 3X + (2X + 4) = 0$$

$$11X = 44 \Rightarrow X = 4$$


Numerator for a resistor is always of the form $X - V_N$ where V_N is the voltage on the other side of the resistor.

Current Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- **Current Sources**
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Current sources cause no problems.

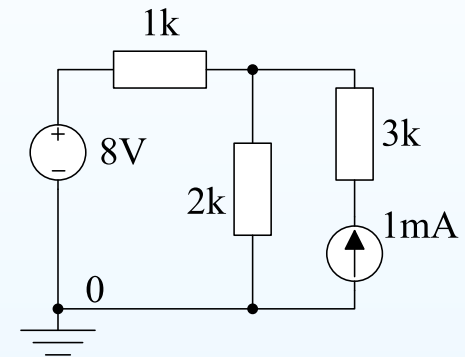


Current Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- **Current Sources**
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Current sources cause no problems.

(1) Pick reference node.

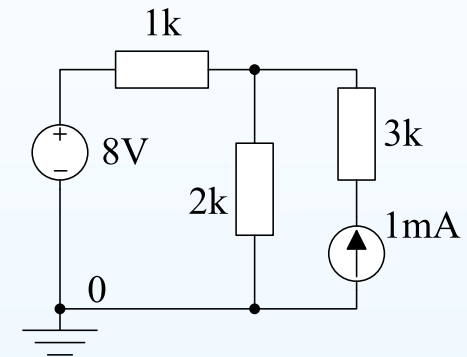

Current Sources


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- **Current Sources**
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Current sources cause no problems.

(1) Pick reference node.

(2) Label nodes: 8

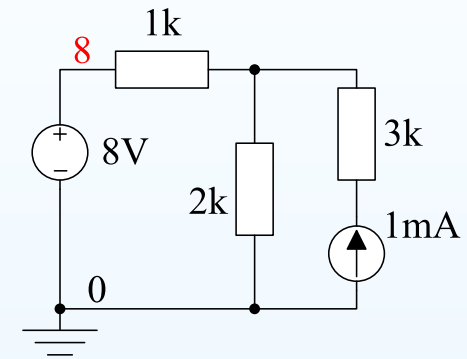

Current Sources


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- **Current Sources**
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Current sources cause no problems.

(1) Pick reference node.

(2) Label nodes: δ , X

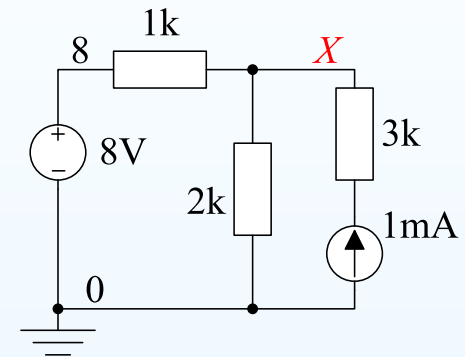

Current Sources


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- **Current Sources**
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Current sources cause no problems.

(1) Pick reference node.

(2) Label nodes: δ , X and Y .

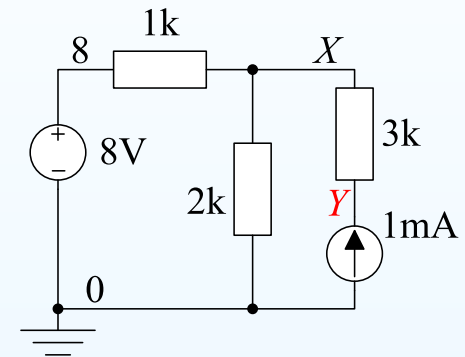

Current Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- **Current Sources**
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary



Current sources cause no problems.

(1) Pick reference node.

(2) Label nodes: 8, X and Y .

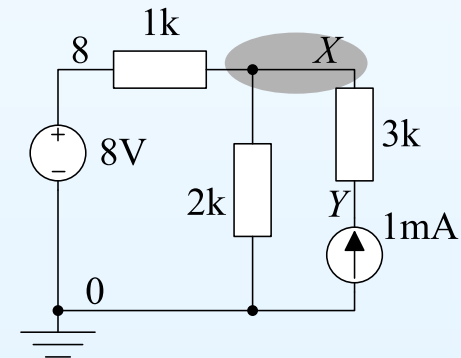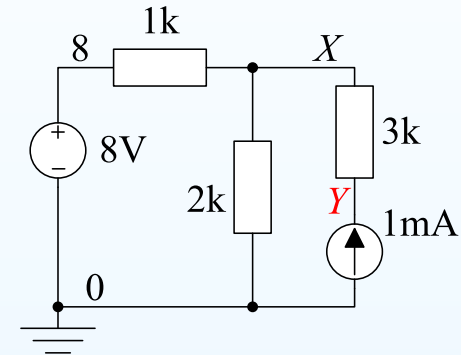(3) Write equations

$$\frac{X-8}{1} + \frac{X}{2} + \frac{X-Y}{3} = 0$$



Current Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- **Current Sources**
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Current sources cause no problems.



(1) Pick reference node.

(2) Label nodes: 8, X and Y .

(3) Write equations

$$\frac{X-8}{1} + \frac{X}{2} + \frac{X-Y}{3} = 0$$

$$\frac{Y-X}{3} + (-1) = 0$$

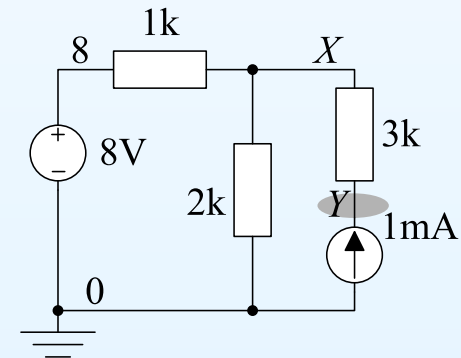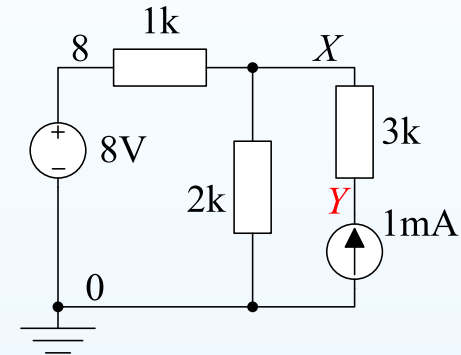

Current Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- **Current Sources**
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Current sources cause no problems.



(1) Pick reference node.

(2) Label nodes: 8, X and Y .

(3) Write equations

$$\frac{X-8}{1} + \frac{X}{2} + \frac{X-Y}{3} = 0$$

$$\frac{Y-X}{3} + (-1) = 0$$

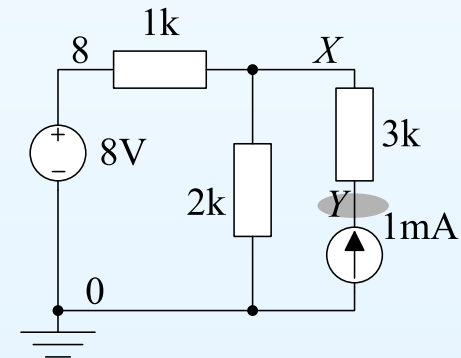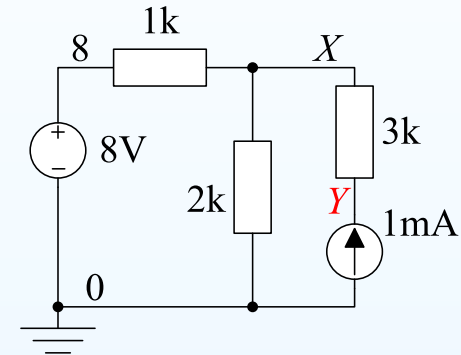

Ohm's law works OK if **all resistors** are in $k\Omega$ and **all currents** in mA .

Current Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- **Current Sources**
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Current sources cause no problems.

- (1) Pick reference node.
- (2) Label nodes: 8, X and Y .



- (3) Write equations

$$\frac{X-8}{1} + \frac{X}{2} + \frac{X-Y}{3} = 0$$

$$\frac{Y-X}{3} + (-1) = 0$$

Ohm's law works OK if **all resistors** are in $k\Omega$ and **all currents** in mA .

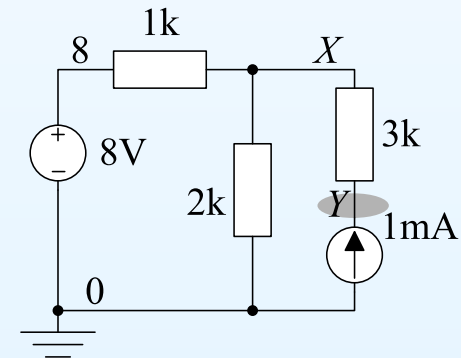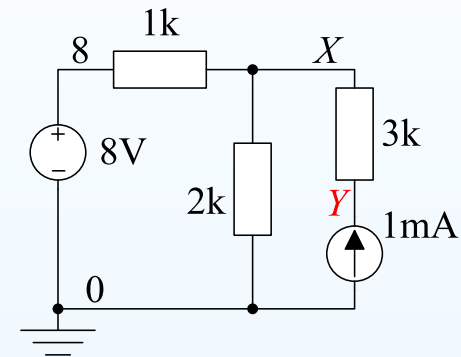- (4) Solve the equations: $X = 6$, $Y = 9$




Floating Voltage Sources

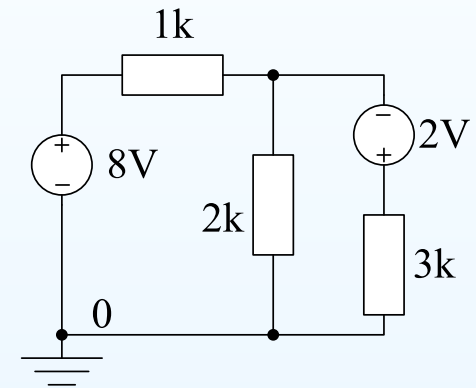3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- **Floating Voltage Sources**
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Floating voltage sources have neither end connected to a known fixed voltage. We have to change how we form the KCL equations slightly.




Floating Voltage Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- **Floating Voltage Sources**
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Floating voltage sources have neither end connected to a known fixed voltage. We have to change how we form the KCL equations slightly.

(1) Pick reference node.

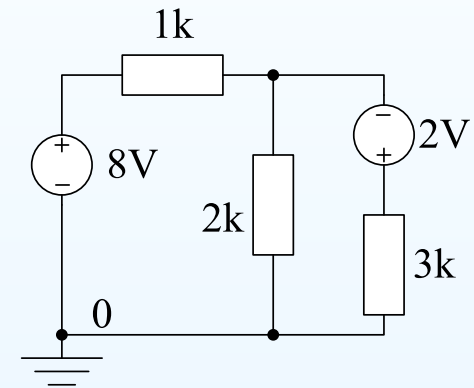

Floating Voltage Sources


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Floating voltage sources have neither end connected to a known fixed voltage. We have to change how we form the KCL equations slightly.

(1) Pick reference node.

(2) Label nodes: 8

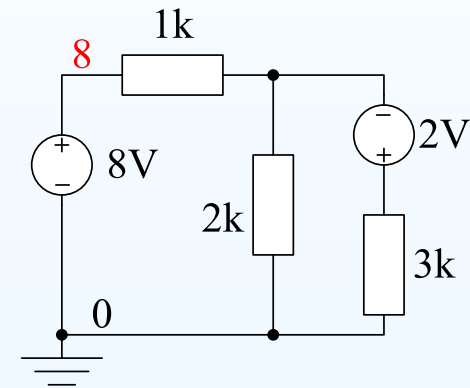

Floating Voltage Sources


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Floating voltage sources have neither end connected to a known fixed voltage. We have to change how we form the KCL equations slightly.

(1) Pick reference node.

(2) Label nodes: δ , X

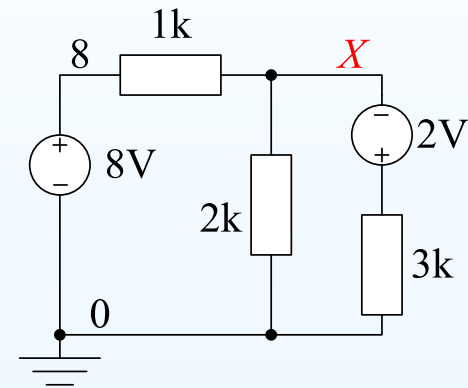

Floating Voltage Sources


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Floating voltage sources have neither end connected to a known fixed voltage. We have to change how we form the KCL equations slightly.

(1) Pick reference node.

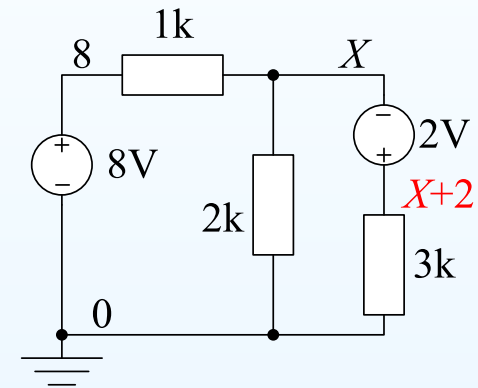(2) Label nodes: 8 , X and $X + 2$ since it is joined to X via a voltage source.



Floating Voltage Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary



Floating voltage sources have neither end connected to a known fixed voltage. We have to change how we form the KCL equations slightly.

(1) Pick reference node.

(2) Label nodes: 8, X and $X + 2$ since it is joined to X via a voltage source.

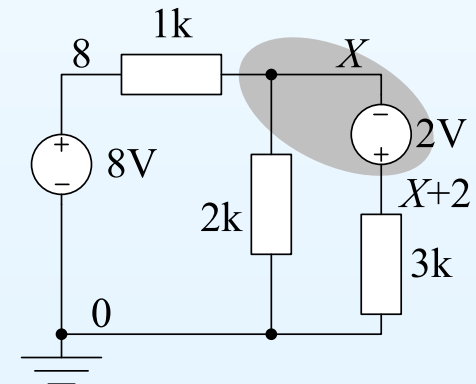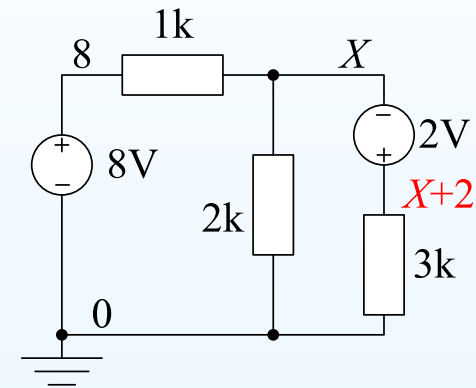(3) Write KCL equations but count all the nodes connected via floating voltage sources as a single “super-node” giving one equation

$$\frac{X-8}{1} + \frac{X}{2} + \frac{(X+2)-0}{3} = 0$$



Floating Voltage Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Floating voltage sources have neither end connected to a known fixed voltage. We have to change how we form the KCL equations slightly.


(1) Pick reference node.

(2) Label nodes: 8, X and $X + 2$ since it is joined to X via a voltage source.

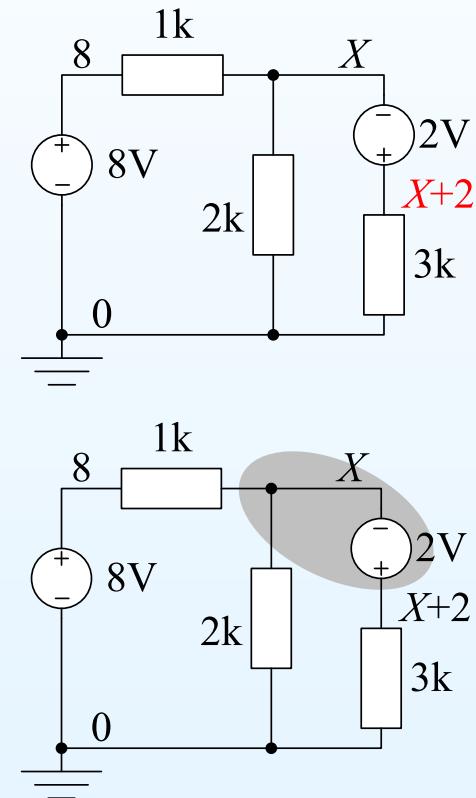(3) Write KCL equations but count all the nodes connected via floating voltage sources as a single “super-node” giving one equation

$$\frac{X-8}{1} + \frac{X}{2} + \frac{(X+2)-0}{3} = 0$$

Ohm's law always involves the difference between the voltages at **either end of a resistor**. (Obvious but easily forgotten)



Floating Voltage Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

Floating voltage sources have neither end connected to a known fixed voltage. We have to change how we form the KCL equations slightly.

(1) Pick reference node.



(2) Label nodes: 8, X and $X + 2$ since it is joined to X via a voltage source.

(3) Write KCL equations but count all the nodes connected via floating voltage sources as a single “super-node” giving one equation

$$\frac{X-8}{1} + \frac{X}{2} + \frac{(X+2)-0}{3} = 0$$

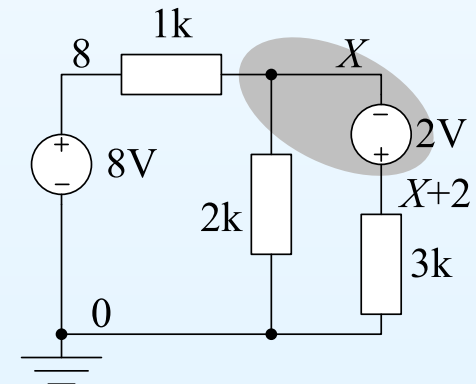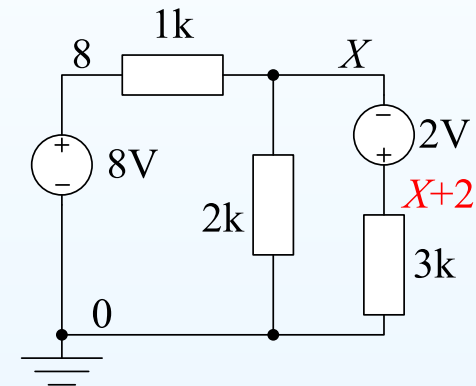(4) Solve the equations: $X = 4$

Ohm's law always involves the difference between the voltages at **either end of a resistor**. (Obvious but easily forgotten)




Weighted Average Circuit

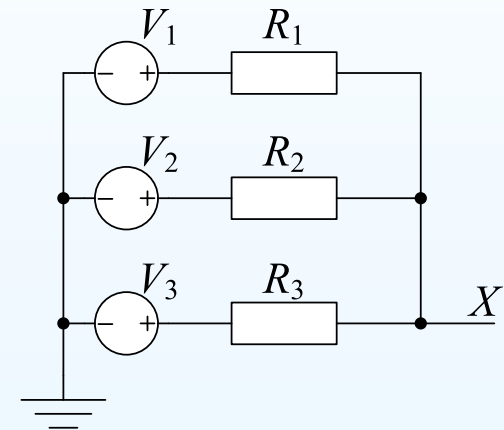3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- **Weighted Average Circuit**
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A very useful sub-circuit that calculates the weighted average of any number of voltages.



Weighted Average Circuit


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- **Weighted Average Circuit**
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A very useful sub-circuit that calculates the weighted average of any number of voltages.

KCL equation for node X :
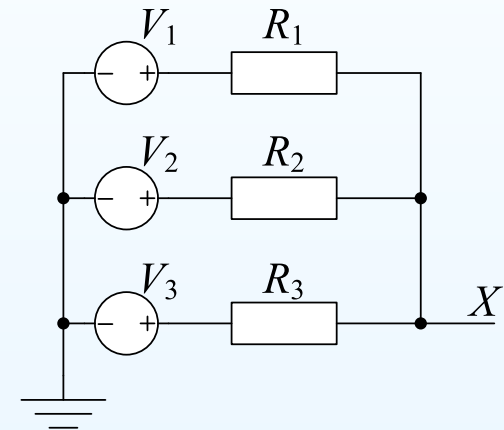
$$\frac{X - V_1}{R_1} + \frac{X - V_2}{R_2} + \frac{X - V_3}{R_3} = 0$$



Weighted Average Circuit


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A very useful sub-circuit that calculates the weighted average of any number of voltages.

KCL equation for node X :
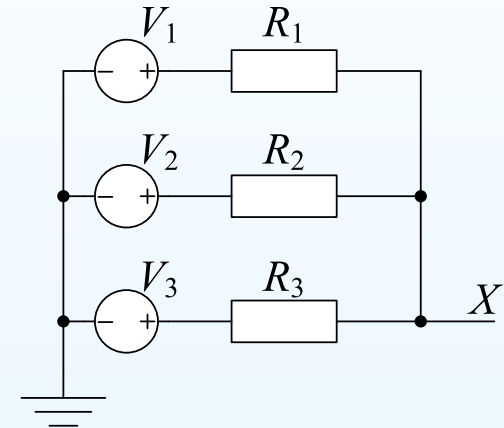
$$\frac{X - V_1}{R_1} + \frac{X - V_2}{R_2} + \frac{X - V_3}{R_3} = 0$$



Or using conductances:

$$(X - V_1)G_1 + (X - V_2)G_2 + (X - V_3)G_3 = 0$$

Weighted Average Circuit


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A very useful sub-circuit that calculates the weighted average of any number of voltages.

KCL equation for node X :
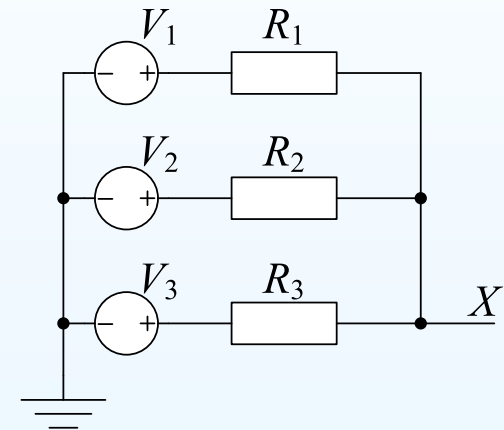
$$\frac{X - V_1}{R_1} + \frac{X - V_2}{R_2} + \frac{X - V_3}{R_3} = 0$$



Or using conductances:

$$(X - V_1)G_1 + (X - V_2)G_2 + (X - V_3)G_3 = 0$$

$$X(G_1 + G_2 + G_3) = V_1G_1 + V_2G_2 + V_3G_3$$

Weighted Average Circuit


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A very useful sub-circuit that calculates the weighted average of any number of voltages.

KCL equation for node X :
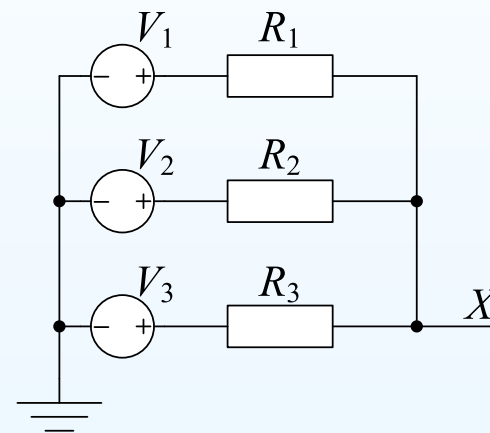
$$\frac{X - V_1}{R_1} + \frac{X - V_2}{R_2} + \frac{X - V_3}{R_3} = 0$$



Or using conductances:

$$(X - V_1)G_1 + (X - V_2)G_2 + (X - V_3)G_3 = 0$$

$$X(G_1 + G_2 + G_3) = V_1G_1 + V_2G_2 + V_3G_3$$

$$X = \frac{V_1G_1 + V_2G_2 + V_3G_3}{G_1 + G_2 + G_3} = \frac{\sum_{i=1}^3 V_i G_i}{\sum_{i=1}^3 G_i}$$

Weighted Average Circuit


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A very useful sub-circuit that calculates the weighted average of any number of voltages.

KCL equation for node X :
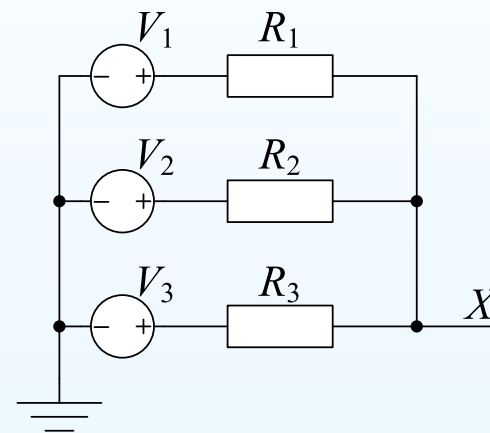
$$\frac{X - V_1}{R_1} + \frac{X - V_2}{R_2} + \frac{X - V_3}{R_3} = 0$$



Or using conductances:

$$(X - V_1)G_1 + (X - V_2)G_2 + (X - V_3)G_3 = 0$$

$$X(G_1 + G_2 + G_3) = V_1G_1 + V_2G_2 + V_3G_3$$

$$X = \frac{V_1G_1 + V_2G_2 + V_3G_3}{G_1 + G_2 + G_3} = \frac{\sum_{i=1}^3 V_i G_i}{\sum_{i=1}^3 G_i}$$

Voltage X is the average of V_1 , V_2 , V_3 weighted by the conductances.

Weighted Average Circuit

3: Nodal Analysis


- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- **Weighted Average Circuit**
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A very useful sub-circuit that calculates the weighted average of any number of voltages.

KCL equation for node X :

$$\frac{X-V_1}{R_1} + \frac{X-V_2}{R_2} + \frac{X-V_3}{R_3} = 0$$

Still works if $V_3 = 0$.

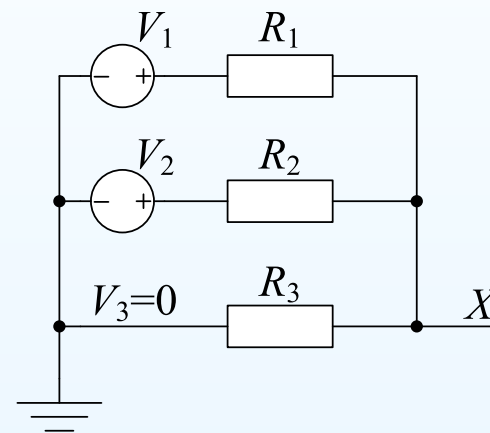

Or using conductances:

$$(X - V_1)G_1 + (X - V_2)G_2 + (X - V_3)G_3 = 0$$

$$X(G_1 + G_2 + G_3) = V_1G_1 + V_2G_2 + V_3G_3$$

$$X = \frac{V_1G_1 + V_2G_2 + V_3G_3}{G_1 + G_2 + G_3} = \frac{\sum_{i=1}^3 V_i G_i}{\sum_{i=1}^3 G_i}$$

Voltage X is the average of V_1 , V_2 , V_3 weighted by the conductances.

Digital-to-Analog Converter

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1:
Label Nodes
- Nodal Analysis Stage 2:
KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog
Converter
- Dependent Sources
- Dependent Voltage
Sources
- Universal Nodal Analysis
Algorithm
- Summary

A 3-bit binary number, b , has bit-weights of 4, 2 and 1. Thus 110 has a value 6 in decimal.

Digital-to-Analog Converter

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1:
Label Nodes
- Nodal Analysis Stage 2:
KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog
Converter
- Dependent Sources
- Dependent Voltage
Sources
- Universal Nodal Analysis
Algorithm
- Summary

A 3-bit binary number, b , has bit-weights of 4, 2 and 1. Thus 110 has a value 6 in decimal. If we label the bits $b_2b_1b_0$, then $b = 4b_2 + 2b_1 + b_0$.


Digital-to-Analog Converter

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A 3-bit binary number, b , has bit-weights of 4, 2 and 1. Thus 110 has a value 6 in decimal. If we label the bits $b_2b_1b_0$, then $b = 4b_2 + 2b_1 + b_0$.

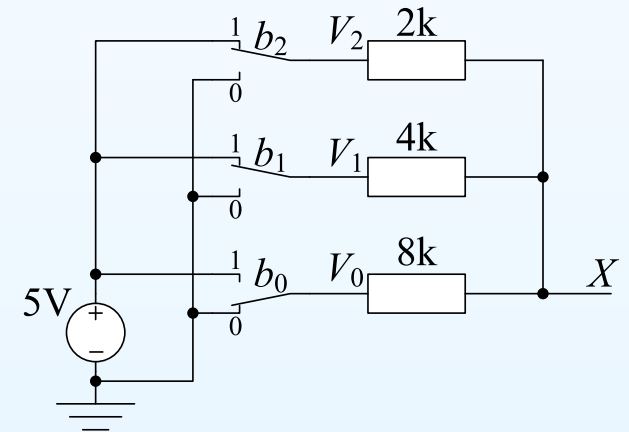We use $b_2b_1b_0$ to control the switches which determine whether $V_i = 5\text{ V}$ or $V_i = 0\text{ V}$. Thus $V_i = 5b_i$. Switches shown for $b = 6$.



Digital-to-Analog Converter


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A 3-bit binary number, b , has bit-weights of 4, 2 and 1. Thus 110 has a value 6 in decimal. If we label the bits $b_2b_1b_0$, then $b = 4b_2 + 2b_1 + b_0$.

We use $b_2b_1b_0$ to control the switches which determine whether $V_i = 5\text{ V}$ or $V_i = 0\text{ V}$. Thus $V_i = 5b_i$. Switches shown for $b = 6$.
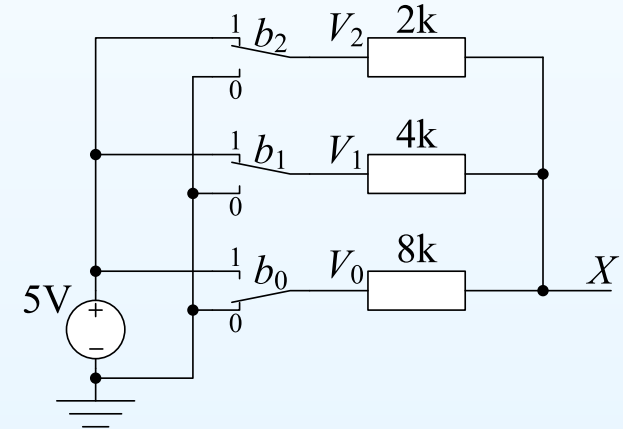
$$X = \frac{\frac{1}{2}V_2 + \frac{1}{4}V_1 + \frac{1}{8}V_0}{\frac{1}{2} + \frac{1}{4} + \frac{1}{8}}$$



$$G_2 = \frac{1}{R_2} = \frac{1}{2} \text{ mS}, \dots$$

Digital-to-Analog Converter


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A 3-bit binary number, b , has bit-weights of 4, 2 and 1. Thus 110 has a value 6 in decimal. If we label the bits $b_2b_1b_0$, then $b = 4b_2 + 2b_1 + b_0$.

We use $b_2b_1b_0$ to control the switches which determine whether $V_i = 5\text{ V}$ or $V_i = 0\text{ V}$. Thus $V_i = 5b_i$. Switches shown for $b = 6$.
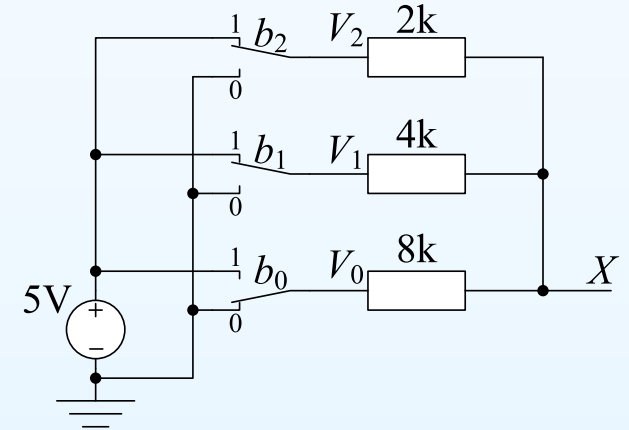
$$X = \frac{\frac{1}{2}V_2 + \frac{1}{4}V_1 + \frac{1}{8}V_0}{\frac{1}{2} + \frac{1}{4} + \frac{1}{8}}$$
$$= \frac{1}{7} (4V_2 + 2V_1 + V_0)$$



$$G_2 = \frac{1}{R_2} = \frac{1}{2} \text{ mS}, \dots$$

Digital-to-Analog Converter

3: Nodal Analysis


- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A 3-bit binary number, b , has bit-weights of 4, 2 and 1. Thus 110 has a value 6 in decimal. If we label the bits $b_2b_1b_0$, then $b = 4b_2 + 2b_1 + b_0$.

We use $b_2b_1b_0$ to control the switches which determine whether $V_i = 5\text{ V}$ or $V_i = 0\text{ V}$. Thus $V_i = 5b_i$. Switches shown for $b = 6$.

$$X = \frac{\frac{1}{2}V_2 + \frac{1}{4}V_1 + \frac{1}{8}V_0}{\frac{1}{2} + \frac{1}{4} + \frac{1}{8}}$$
$$= \frac{1}{7} (4V_2 + 2V_1 + V_0)$$

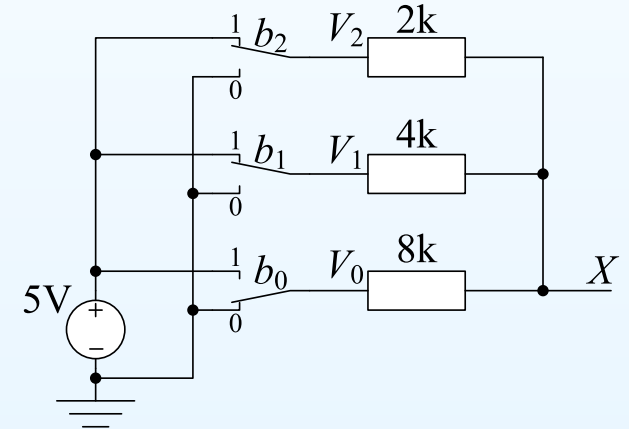but $V_i = 5 \times b_i$ since it connects to either 0 V or 5 V



$$G_2 = \frac{1}{R_2} = \frac{1}{2} \text{ mS}, \dots$$

Digital-to-Analog Converter

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary


A 3-bit binary number, b , has bit-weights of 4, 2 and 1. Thus 110 has a value 6 in decimal. If we label the bits $b_2b_1b_0$, then $b = 4b_2 + 2b_1 + b_0$.

We use $b_2b_1b_0$ to control the switches which determine whether $V_i = 5\text{ V}$ or $V_i = 0\text{ V}$. Thus $V_i = 5b_i$. Switches shown for $b = 6$.

$$X = \frac{\frac{1}{2}V_2 + \frac{1}{4}V_1 + \frac{1}{8}V_0}{\frac{1}{2} + \frac{1}{4} + \frac{1}{8}}$$
$$= \frac{1}{7} (4V_2 + 2V_1 + V_0)$$

but $V_i = 5 \times b_i$ since it connects to either 0 V or 5 V
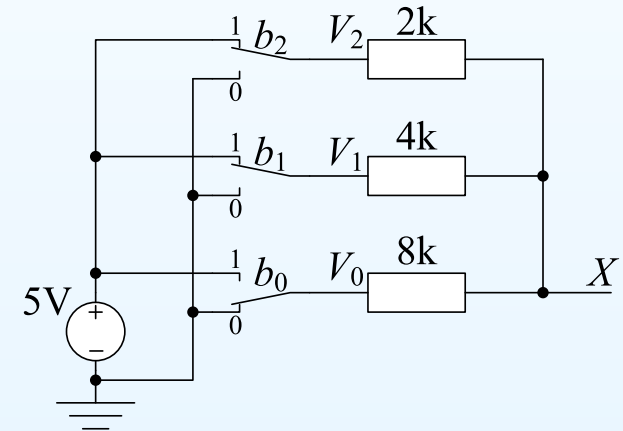
$$= \frac{5}{7} (4b_2 + 2b_1 + b_0) = \frac{5}{7}b$$



$$G_2 = \frac{1}{R_2} = \frac{1}{2} \text{ mS}, \dots$$

Digital-to-Analog Converter

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A 3-bit binary number, b , has bit-weights of 4, 2 and 1. Thus 110 has a value 6 in decimal. If we label the bits $b_2b_1b_0$, then $b = 4b_2 + 2b_1 + b_0$.


We use $b_2b_1b_0$ to control the switches which determine whether $V_i = 5\text{ V}$ or $V_i = 0\text{ V}$. Thus $V_i = 5b_i$. Switches shown for $b = 6$.

$$X = \frac{\frac{1}{2}V_2 + \frac{1}{4}V_1 + \frac{1}{8}V_0}{\frac{1}{2} + \frac{1}{4} + \frac{1}{8}}$$
$$= \frac{1}{7} (4V_2 + 2V_1 + V_0)$$

but $V_i = 5 \times b_i$ since it connects to either 0 V or 5 V

$$= \frac{5}{7} (4b_2 + 2b_1 + b_0) = \frac{5}{7}b$$

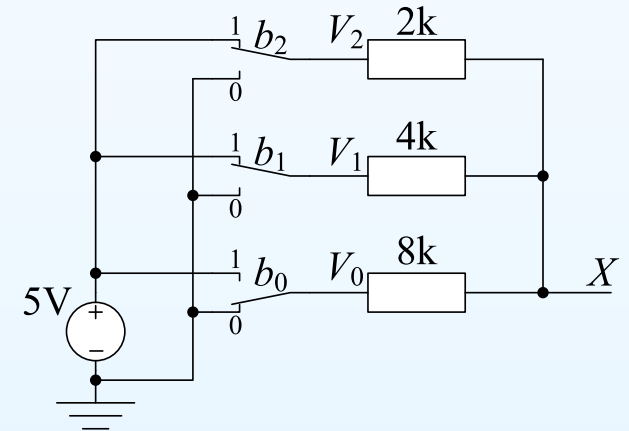So we have made a circuit in which X is proportional to a binary number b .



$$G_2 = \frac{1}{R_2} = \frac{1}{2} \text{ mS}, \dots$$


Dependent Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- **Dependent Sources**
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A *dependent* voltage or current source is one whose value is determined by voltages or currents elsewhere in the circuit. These are most commonly used when modelling the behaviour of transistors or op-amps. Each dependent source has a **defining equation**.

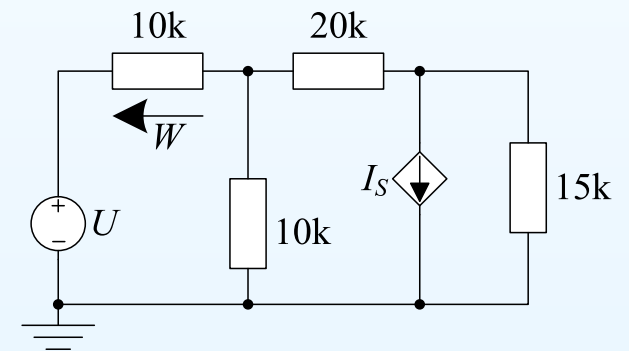In this circuit: $I_S = 0.2W$ mA where W is in volts.



Dependent Sources


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- **Dependent Sources**
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A *dependent* voltage or current source is one whose value is determined by voltages or currents elsewhere in the circuit. These are most commonly used when modelling the behaviour of transistors or op-amps. Each dependent source has a **defining equation**.

In this circuit: $I_S = 0.2W$ mA where W is in volts.

(1) Pick reference node.

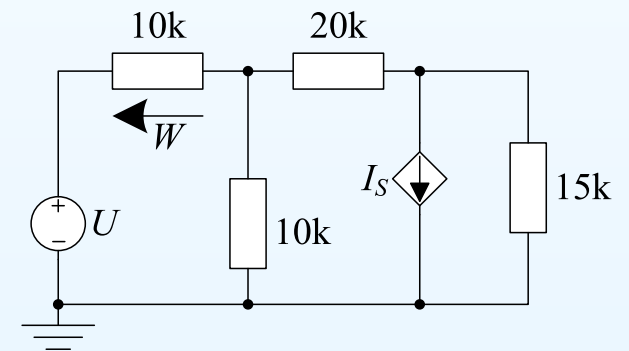

Dependent Sources

3: Nodal Analysis


- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- **Dependent Sources**
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A *dependent* voltage or current source is one whose value is determined by voltages or currents elsewhere in the circuit. These are most commonly used when modelling the behaviour of transistors or op-amps. Each dependent source has a **defining equation**.

In this circuit: $I_S = 0.2W$ mA where W is in volts.

(1) Pick reference node.

(2) Label nodes: 0, U

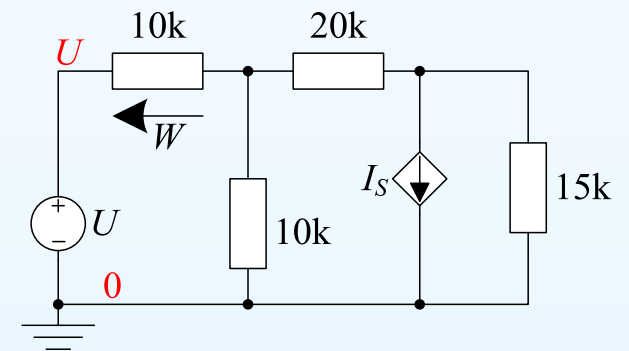

Dependent Sources

3: Nodal Analysis


- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- **Dependent Sources**
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A *dependent* voltage or current source is one whose value is determined by voltages or currents elsewhere in the circuit. These are most commonly used when modelling the behaviour of transistors or op-amps. Each dependent source has a **defining equation**.

In this circuit: $I_S = 0.2W$ mA where W is in volts.

(1) Pick reference node.

(2) Label nodes: 0, U , X and Y .

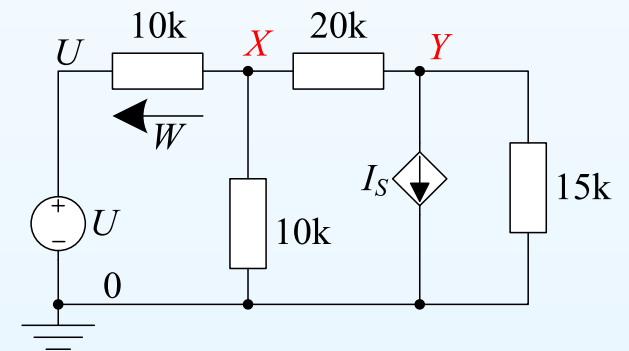

Dependent Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- **Dependent Sources**
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A *dependent* voltage or current source is one whose value is determined by voltages or currents elsewhere in the circuit. These are most commonly used when modelling the behaviour of transistors or op-amps. Each dependent source has a **defining equation**.


In this circuit: $I_S = 0.2W$ mA where W is in volts.

(1) Pick reference node.

(2) Label nodes: 0 , U , X and Y .

(3) Write equation for the dependent source, I_S , in terms of node voltages:

$$I_S = 0.2(U - X)$$

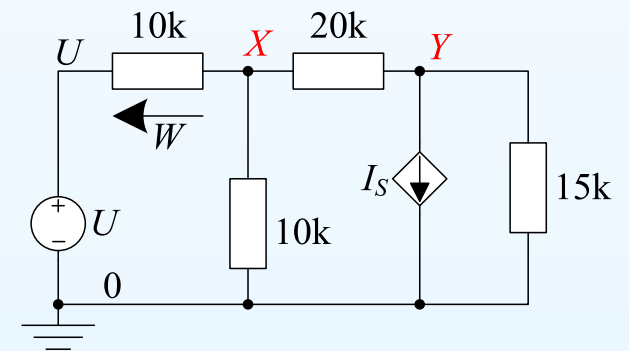

Dependent Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- **Dependent Sources**
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A *dependent* voltage or current source is one whose value is determined by voltages or currents elsewhere in the circuit. These are most commonly used when modelling the behaviour of transistors or op-amps. Each dependent source has a **defining equation**.

In this circuit: $I_S = 0.2W$ mA where W is in volts.

(1) Pick reference node.


(2) Label nodes: 0 , U , X and Y .

(3) Write equation for the dependent source, I_S , in terms of node voltages:

$$I_S = 0.2(U - X)$$

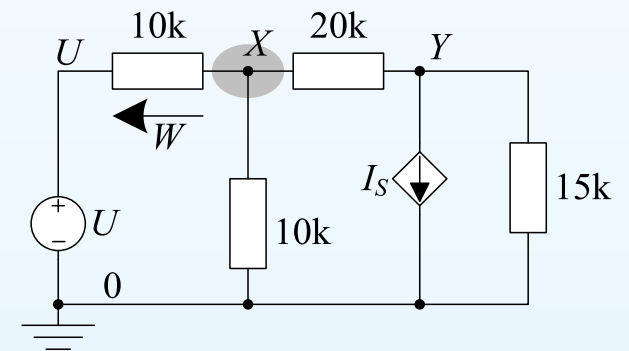(4) Write KCL equations:

$$\frac{X-U}{10} + \frac{X}{10} + \frac{X-Y}{20} = 0$$



Dependent Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- **Dependent Sources**
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A *dependent* voltage or current source is one whose value is determined by voltages or currents elsewhere in the circuit. These are most commonly used when modelling the behaviour of transistors or op-amps. Each dependent source has a **defining equation**.

In this circuit: $I_S = 0.2W$ mA where W is in volts.

(1) Pick reference node.

(2) Label nodes: 0 , U , X and Y .


(3) Write equation for the dependent source, I_S , in terms of node voltages:

$$I_S = 0.2(U - X)$$

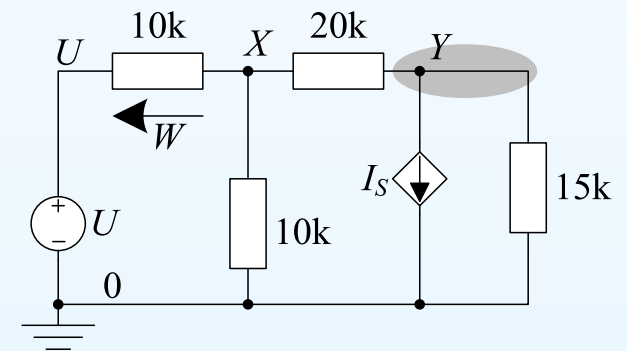(4) Write KCL equations:

$$\frac{X-U}{10} + \frac{X}{10} + \frac{X-Y}{20} = 0$$

$$\frac{Y-X}{20} + I_S + \frac{Y}{15} = 0$$



Dependent Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- **Dependent Sources**
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A *dependent* voltage or current source is one whose value is determined by voltages or currents elsewhere in the circuit. These are most commonly used when modelling the behaviour of transistors or op-amps. Each dependent source has a **defining equation**.

In this circuit: $I_S = 0.2W$ mA where W is in volts.

(1) Pick reference node.

(2) Label nodes: 0, U , X and Y .


(3) Write equation for the dependent source, I_S , in terms of node voltages:

$$I_S = 0.2 (U - X)$$

(4) Write KCL equations:

$$\frac{X-U}{10} + \frac{X}{10} + \frac{X-Y}{20} = 0 \qquad \frac{Y-X}{20} + I_S + \frac{Y}{15} = 0$$

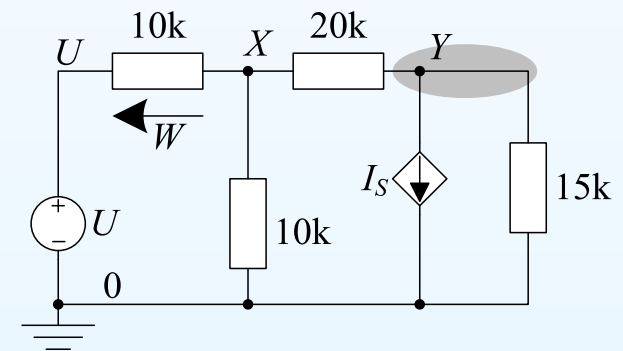(5) Solve all three equations to find X , Y and I_S in terms of U :



Dependent Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- **Dependent Sources**
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A *dependent* voltage or current source is one whose value is determined by voltages or currents elsewhere in the circuit. These are most commonly used when modelling the behaviour of transistors or op-amps. Each dependent source has a **defining equation**.

In this circuit: $I_S = 0.2W$ mA where W is in volts.

(1) Pick reference node.

(2) Label nodes: 0, U , X and Y .

(3) Write equation for the dependent source, I_S , in terms of node voltages:


$$I_S = 0.2(U - X)$$

(4) Write KCL equations:

$$\frac{X-U}{10} + \frac{X}{10} + \frac{X-Y}{20} = 0 \qquad \frac{Y-X}{20} + I_S + \frac{Y}{15} = 0$$

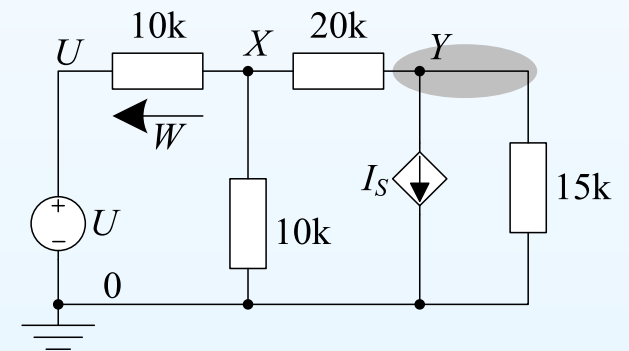(5) Solve all three equations to find X , Y and I_S in terms of U :

$$X = 0.1U, \quad Y = -1.5U, \quad I_S = 0.18U$$



Dependent Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- **Dependent Sources**
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

A *dependent* voltage or current source is one whose value is determined by voltages or currents elsewhere in the circuit. These are most commonly used when modelling the behaviour of transistors or op-amps. Each dependent source has a **defining equation**.

In this circuit: $I_S = 0.2W$ mA where W is in volts.

(1) Pick reference node.

(2) Label nodes: 0, U , X and Y .

(3) Write equation for the dependent source, I_S , in terms of node voltages:

$$I_S = 0.2(U - X)$$


(4) Write KCL equations:

$$\frac{X-U}{10} + \frac{X}{10} + \frac{X-Y}{20} = 0 \qquad \frac{Y-X}{20} + I_S + \frac{Y}{15} = 0$$

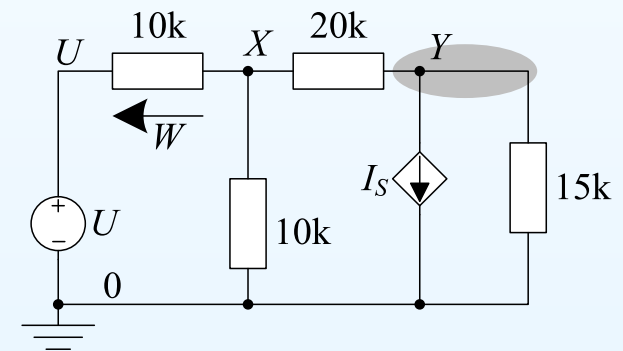(5) Solve all three equations to find X , Y and I_S in terms of U :

$$X = 0.1U, \quad Y = -1.5U, \quad I_S = 0.18U$$

Note that the value of U is assumed to be known.




Dependent Voltage Sources

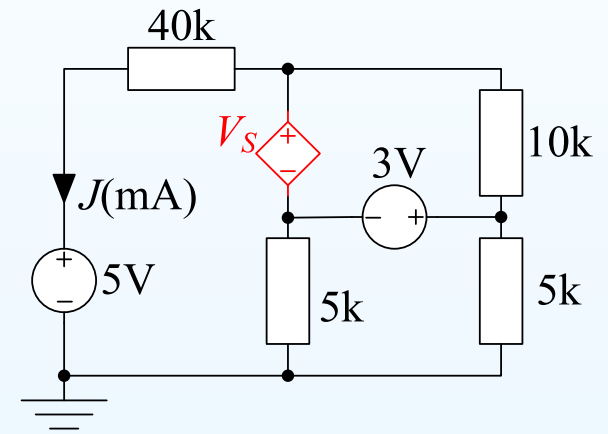3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- **Dependent Voltage Sources**
- Universal Nodal Analysis Algorithm
- Summary

The value of the highlighted dependent voltage source is $V_S = 10J$ Volts where J is the indicated current in mA.




Dependent Voltage Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- **Dependent Voltage Sources**
- Universal Nodal Analysis Algorithm
- Summary

The value of the highlighted dependent voltage source is $V_S = 10J$ Volts where J is the indicated current in mA.

(1) Pick reference node.

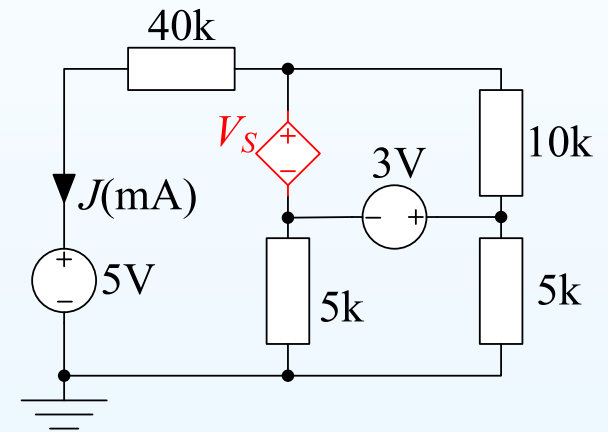

Dependent Voltage Sources


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- **Dependent Voltage Sources**
- Universal Nodal Analysis Algorithm
- Summary

The value of the highlighted dependent voltage source is $V_S = 10J$ Volts where J is the indicated current in mA.

(1) Pick reference node.

(2) Label nodes: 0, 5

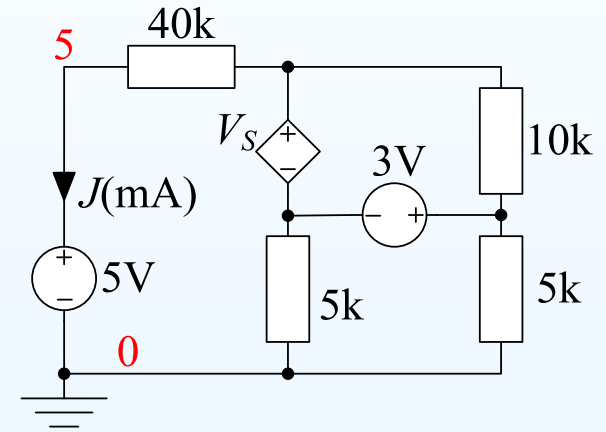

Dependent Voltage Sources


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- **Dependent Voltage Sources**
- Universal Nodal Analysis Algorithm
- Summary

The value of the highlighted dependent voltage source is $V_S = 10J$ Volts where J is the indicated current in mA.

(1) Pick reference node.

(2) Label nodes: 0, 5, X , $X + 3$

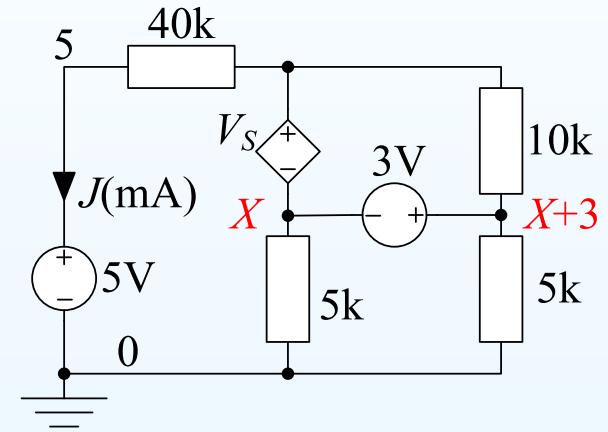

Dependent Voltage Sources


3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- **Dependent Voltage Sources**
- Universal Nodal Analysis Algorithm
- Summary

The value of the highlighted dependent voltage source is $V_S = 10J$ Volts where J is the indicated current in mA.

(1) Pick reference node.

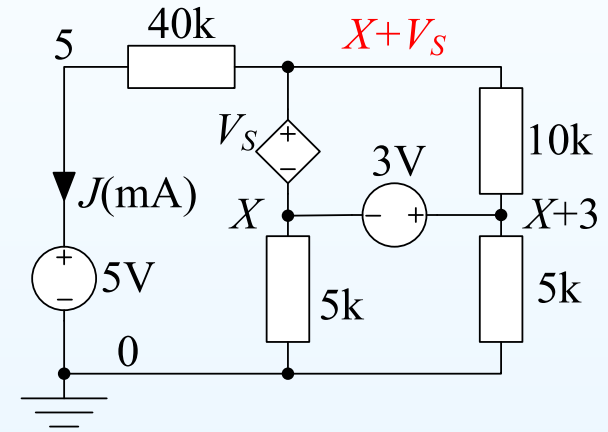(2) Label nodes: 0, 5, X , $X + 3$ and $X + V_S$.



Dependent Voltage Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit Converter
- Dependent Sources
- **Dependent Voltage Sources**
- Universal Nodal Analysis Algorithm
- Summary


The value of the highlighted dependent voltage source is $V_S = 10J$ Volts where J is the indicated current in mA.

(1) Pick reference node.

(2) Label nodes: 0, 5, X , $X + 3$ and $X + V_S$.

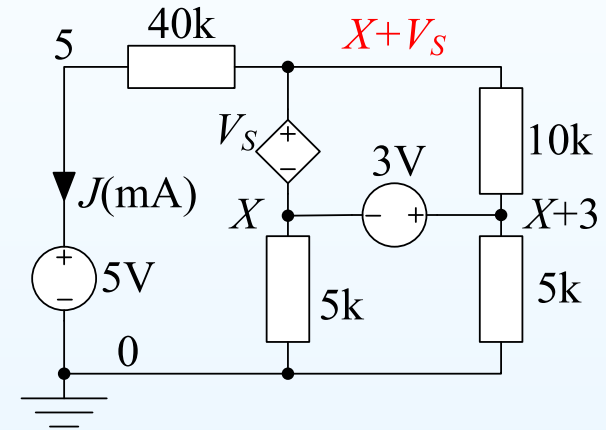(3) Write equation for the dependent source, V_S , in terms of node voltages:

$$V_S = 10J = 10 \times \frac{X + V_S - 5}{40} \Rightarrow 3V_S = X - 5$$



Dependent Voltage Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- **Dependent Voltage Sources**
- Universal Nodal Analysis Algorithm
- Summary

The value of the highlighted dependent voltage source is $V_S = 10J$ Volts where J is the indicated current in mA.

(1) Pick reference node.


(2) Label nodes: 0, 5, X , $X + 3$ and $X + V_S$.

(3) Write equation for the dependent source, V_S , in terms of node voltages:

$$V_S = 10J = 10 \times \frac{X + V_S - 5}{40} \Rightarrow 3V_S = X - 5$$

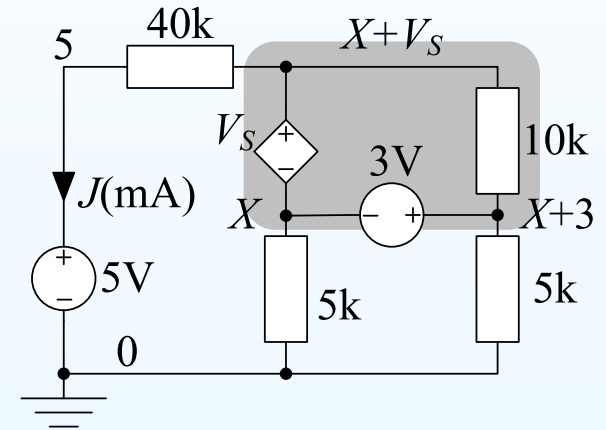(4) Write KCL equations: all nodes connected by floating voltage sources and all components connecting these nodes are in the same “super-node”

$$\frac{X + V_S - 5}{40} + \frac{X}{5} + \frac{X + 3}{5} = 0$$



Dependent Voltage Sources

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- **Dependent Voltage Sources**
- Universal Nodal Analysis Algorithm
- Summary

The value of the highlighted dependent voltage source is $V_S = 10J$ Volts where J is the indicated current in mA.

(1) Pick reference node.

(2) Label nodes: 0, 5, X , $X + 3$ and $X + V_S$.


(3) Write equation for the dependent source, V_S , in terms of node voltages:

$$V_S = 10J = 10 \times \frac{X + V_S - 5}{40} \Rightarrow 3V_S = X - 5$$

(4) Write KCL equations: all nodes connected by floating voltage sources and all components connecting these nodes are in the same “super-node”

$$\frac{X + V_S - 5}{40} + \frac{X}{5} + \frac{X + 3}{5} = 0$$

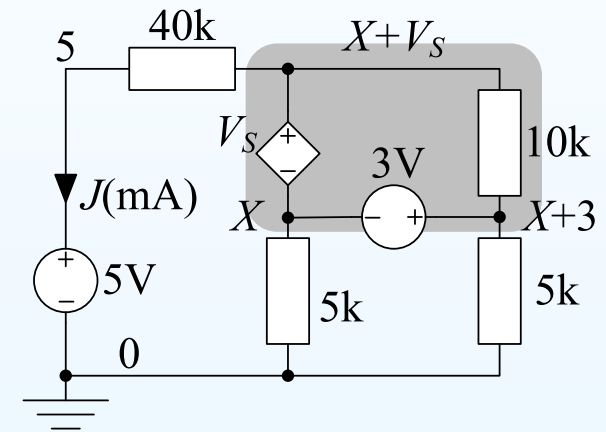(5) Solve the two equations: $X = -1$ and $V_S = -2$



Universal Nodal Analysis Algorithm

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

(1) Pick any node as the voltage reference. Label its voltage as 0 V . Label any dependent sources with V_S, I_S, \dots

(2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end. Repeat as many times as possible.

(3) Pick an unlabelled node and label it with X, Y, \dots , then loop back to step (2) until all nodes are labelled.

(4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.

(5) Write down a KCL equation for each “normal” node (i.e. one that is not connected to a floating voltage source).

(6) Write down a KCL equation for each “super-node”. A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components joining these nodes.

(7) Solve the set of simultaneous equations that you have written down.

Universal Nodal Analysis Algorithm

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

- (1) Pick any node as the voltage reference. Label its voltage as 0 V . Label any dependent sources with V_S, I_S, \dots
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end. Repeat as many times as possible.
- (3) Pick an unlabelled node and label it with X, Y, \dots , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each “normal” node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each “super-node”. A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components joining these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

Universal Nodal Analysis Algorithm

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

- (1) Pick any node as the voltage reference. Label its voltage as 0 V . Label any dependent sources with V_S, I_S, \dots
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end. Repeat as many times as possible.
- (3) Pick an unlabelled node and label it with X, Y, \dots , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each “normal” node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each “super-node”. A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components joining these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

Universal Nodal Analysis Algorithm

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

- (1) Pick any node as the voltage reference. Label its voltage as 0 V . Label any dependent sources with V_S, I_S, \dots
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end. Repeat as many times as possible.
- (3) Pick an unlabelled node and label it with X, Y, \dots , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each “normal” node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each “super-node”. A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components joining these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

Universal Nodal Analysis Algorithm

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1:
Label Nodes
- Nodal Analysis Stage 2:
KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog
Converter
- Dependent Sources
- Dependent Voltage
Sources
- Universal Nodal Analysis
Algorithm
- Summary

- (1) Pick any node as the voltage reference. Label its voltage as 0 V . Label any dependent sources with V_S, I_S, \dots
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end. Repeat as many times as possible.
- (3) Pick an unlabelled node and label it with X, Y, \dots , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each “normal” node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each “super-node”. A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components joining these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

Universal Nodal Analysis Algorithm

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

- (1) Pick any node as the voltage reference. Label its voltage as 0 V . Label any dependent sources with V_S, I_S, \dots
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end. Repeat as many times as possible.
- (3) Pick an unlabelled node and label it with X, Y, \dots , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each “normal” node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each “super-node”. A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components joining these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

Universal Nodal Analysis Algorithm

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1: Label Nodes
- Nodal Analysis Stage 2: KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog Converter
- Dependent Sources
- Dependent Voltage Sources
- Universal Nodal Analysis Algorithm
- Summary

- (1) Pick any node as the voltage reference. Label its voltage as 0 V . Label any dependent sources with V_S, I_S, \dots
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end. Repeat as many times as possible.
- (3) Pick an unlabelled node and label it with X, Y, \dots , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each “normal” node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each “super-node”. A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components joining these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

Summary

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1:
Label Nodes
- Nodal Analysis Stage 2:
KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog
Converter
- Dependent Sources
- Dependent Voltage
Sources
- Universal Nodal Analysis
Algorithm
- **Summary**

- **Nodal Analysis**
 - Simple Circuits (no floating or dependent voltage sources)

Summary

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1:
Label Nodes
- Nodal Analysis Stage 2:
KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog
Converter
- Dependent Sources
- Dependent Voltage
Sources
- Universal Nodal Analysis
Algorithm
- **Summary**

- **Nodal Analysis**
 - Simple Circuits (no floating or dependent voltage sources)
 - Floating Voltage Sources
 - ▷ use supernodes: all the nodes connected by floating voltage sources (independent or dependent)

Summary

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1:
Label Nodes
- Nodal Analysis Stage 2:
KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog
Converter
- Dependent Sources
- Dependent Voltage
Sources
- Universal Nodal Analysis
Algorithm
- Summary

- Nodal Analysis
 - Simple Circuits (no floating or dependent voltage sources)
 - Floating Voltage Sources
 - ▷ use supernodes: all the nodes connected by floating voltage sources (independent or dependent)
 - Dependent Voltage and Current Sources
 - ▷ Label each source with a variable
 - ▷ Write extra equations expressing the source values in terms of node voltages
 - ▷ Write down the KCL equations as before

Summary

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1:
Label Nodes
- Nodal Analysis Stage 2:
KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog
Converter
- Dependent Sources
- Dependent Voltage
Sources
- Universal Nodal Analysis
Algorithm
- Summary

- Nodal Analysis
 - Simple Circuits (no floating or dependent voltage sources)
 - Floating Voltage Sources
 - ▷ use supernodes: all the nodes connected by floating voltage sources (independent or dependent)
 - Dependent Voltage and Current Sources
 - ▷ Label each source with a variable
 - ▷ Write extra equations expressing the source values in terms of node voltages
 - ▷ Write down the KCL equations as before
- Mesh Analysis (in most textbooks)
 - Alternative to nodal analysis but doesn't work for all circuits
 - No significant benefits \Rightarrow ignore it

Summary

3: Nodal Analysis

- Aim of Nodal Analysis
- Nodal Analysis Stage 1:
Label Nodes
- Nodal Analysis Stage 2:
KCL Equations
- Current Sources
- Floating Voltage Sources
- Weighted Average Circuit
- Digital-to-Analog
Converter
- Dependent Sources
- Dependent Voltage
Sources
- Universal Nodal Analysis
Algorithm
- Summary

- Nodal Analysis
 - Simple Circuits (no floating or dependent voltage sources)
 - Floating Voltage Sources
 - ▷ use supernodes: all the nodes connected by floating voltage sources (independent or dependent)
 - Dependent Voltage and Current Sources
 - ▷ Label each source with a variable
 - ▷ Write extra equations expressing the source values in terms of node voltages
 - ▷ Write down the KCL equations as before
- Mesh Analysis (in most textbooks)
 - Alternative to nodal analysis but doesn't work for all circuits
 - No significant benefits \Rightarrow ignore it

For further details see Hayt Ch 4 or Irwin Ch 3.