

#### 4: Linearity and Superposition

---

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

# 4: Linearity and Superposition


# Linearity Theorem

## 4: Linearity and Superposition

- Linearity Theorem

- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

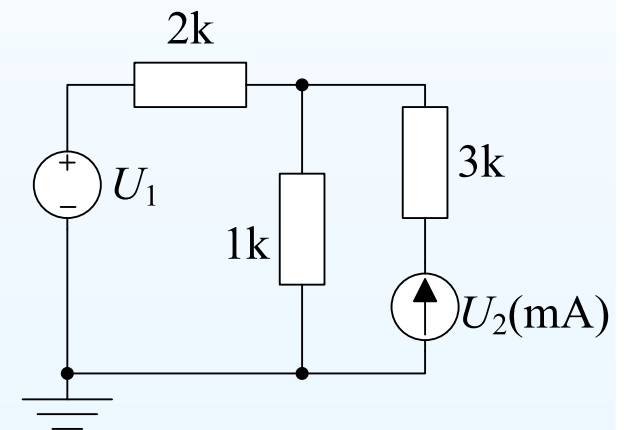Suppose we use variables instead of fixed values for all of the *independent* voltage and current sources. We can then use nodal analysis to find all node voltages in terms of the source values.



# Linearity Theorem


## 4: Linearity and Superposition

### ● Linearity Theorem

- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

Suppose we use variables instead of fixed values for all of the *independent* voltage and current sources. We can then use nodal analysis to find all node voltages in terms of the source values.

(1) Label all the nodes

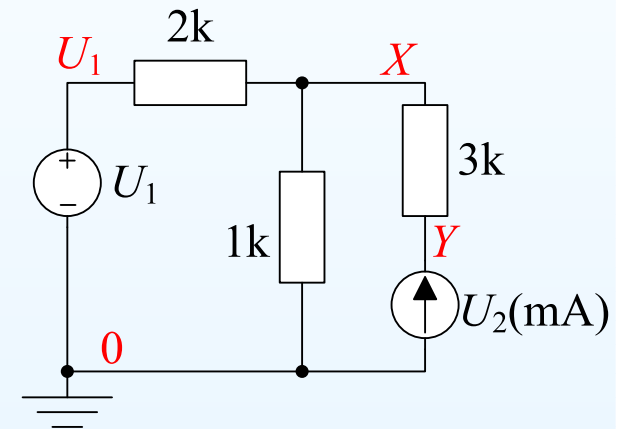

# Linearity Theorem

## 4: Linearity and Superposition

### ● Linearity Theorem

- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary


Suppose we use variables instead of fixed values for all of the *independent* voltage and current sources. We can then use nodal analysis to find all node voltages in terms of the source values.

(1) Label all the nodes

(2) KCL equations

$$\frac{X-U_1}{2} + \frac{X}{1} + \frac{X-Y}{3} = 0$$

$$\frac{Y-X}{3} + (-U_2) = 0$$

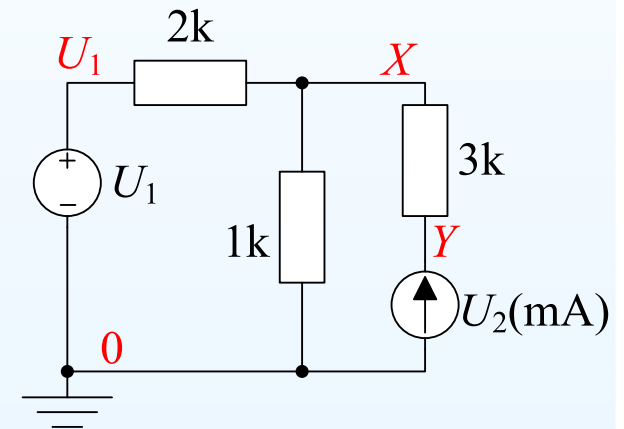

# Linearity Theorem

## 4: Linearity and Superposition

### ● Linearity Theorem

- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

Suppose we use variables instead of fixed values for all of the *independent* voltage and current sources. We can then use nodal analysis to find all node voltages in terms of the source values.

(1) Label all the nodes


(2) KCL equations

$$\frac{X-U_1}{2} + \frac{X}{1} + \frac{X-Y}{3} = 0$$

$$\frac{Y-X}{3} + (-U_2) = 0$$

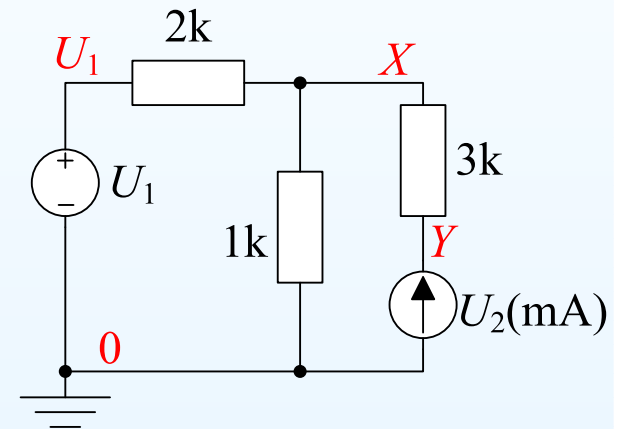(3) Solve for the node voltages

$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2, \quad Y = \frac{1}{3}U_1 + \frac{11}{3}U_2$$



# Linearity Theorem

## 4: Linearity and Superposition

### ● Linearity Theorem

- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

Suppose we use variables instead of fixed values for all of the *independent* voltage and current sources. We can then use nodal analysis to find all node voltages in terms of the source values.

(1) Label all the nodes


(2) KCL equations

$$\frac{X-U_1}{2} + \frac{X}{1} + \frac{X-Y}{3} = 0$$

$$\frac{Y-X}{3} + (-U_2) = 0$$

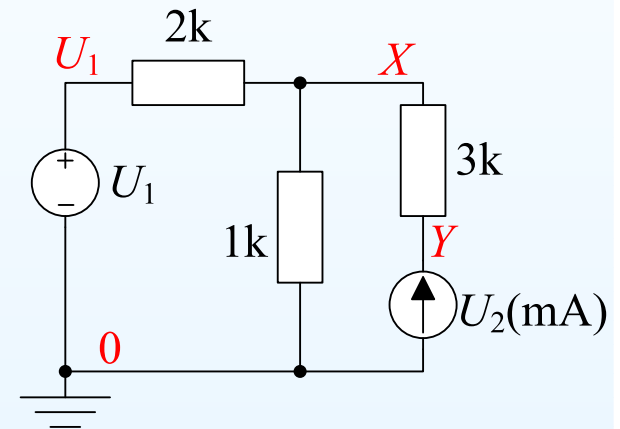(3) Solve for the node voltages

$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2, \quad Y = \frac{1}{3}U_1 + \frac{11}{3}U_2$$



Steps (2) and (3) never involve multiplying two source values together, so:

# Linearity Theorem

## 4: Linearity and Superposition

### ● Linearity Theorem

- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

Suppose we use variables instead of fixed values for all of the *independent* voltage and current sources. We can then use nodal analysis to find all node voltages in terms of the source values.

(1) Label all the nodes


(2) KCL equations

$$\frac{X-U_1}{2} + \frac{X}{1} + \frac{X-Y}{3} = 0$$

$$\frac{Y-X}{3} + (-U_2) = 0$$

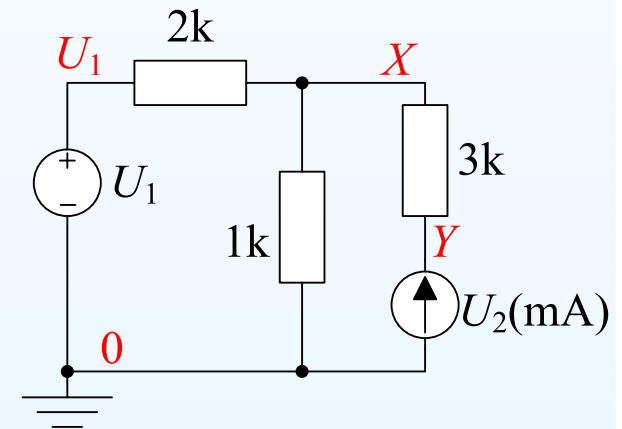(3) Solve for the node voltages

$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2, \quad Y = \frac{1}{3}U_1 + \frac{11}{3}U_2$$



Steps (2) and (3) never involve multiplying two source values together, so:

**Linearity Theorem:** For any circuit containing resistors and independent voltage and current sources, every node voltage and branch current is a linear function of the source values and has the form  $\sum a_i U_i$  where the  $U_i$  are the source values and the  $a_i$  are suitably dimensioned constants.

# Linearity Theorem

## 4: Linearity and Superposition

### • Linearity Theorem

- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

Suppose we use variables instead of fixed values for all of the *independent* voltage and current sources. We can then use nodal analysis to find all node voltages in terms of the source values.

(1) Label all the nodes


(2) KCL equations

$$\frac{X-U_1}{2} + \frac{X}{1} + \frac{X-Y}{3} = 0$$

$$\frac{Y-X}{3} + (-U_2) = 0$$

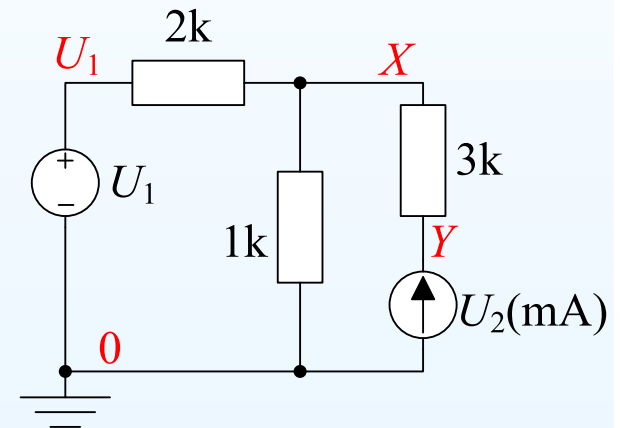(3) Solve for the node voltages

$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2, \quad Y = \frac{1}{3}U_1 + \frac{11}{3}U_2$$



Steps (2) and (3) never involve multiplying two source values together, so:

**Linearity Theorem:** For any circuit containing resistors and independent voltage and current sources, every node voltage and branch current is a linear function of the source values and has the form  $\sum a_i U_i$  where the  $U_i$  are the source values and the  $a_i$  are suitably dimensioned constants.

Also true for a circuit containing *dependent* sources whose values are proportional to voltages or currents elsewhere in the circuit.



## Zero-value sources

### 4: Linearity and Superposition

- Linearity Theorem
- **Zero-value sources**
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary


A **zero-valued** voltage source has zero volts between its terminals for any current. It is equivalent to a *short-circuit* or piece of wire or resistor of  $0 \Omega$  (or  $\infty S$ ).

## Zero-value sources
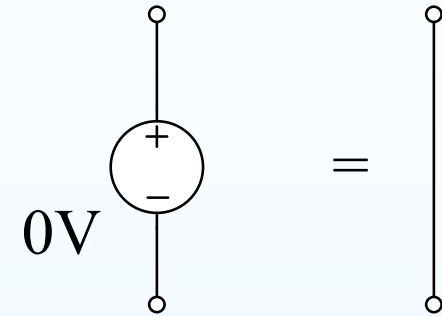
### 4: Linearity and Superposition

- Linearity Theorem
- **Zero-value sources**
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A **zero-valued** voltage source has zero volts between its terminals for any current. It is equivalent to a *short-circuit* or piece of wire or resistor of  $0 \Omega$  (or  $\infty S$ ).




#### 4: Linearity and Superposition

- Linearity Theorem
- **Zero-value sources**
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary
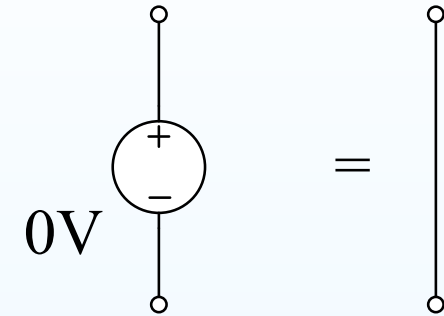
## Zero-value sources

A **zero-valued** voltage source has zero volts between its terminals for any current. It is equivalent to a *short-circuit* or piece of wire or resistor of  $0 \Omega$  (or  $\infty S$ ).




A **zero-valued** current source has no current flowing between its terminals. It is equivalent to an *open-circuit* or a broken wire or a resistor of  $\infty \Omega$  (or  $0 S$ ).

## Zero-value sources

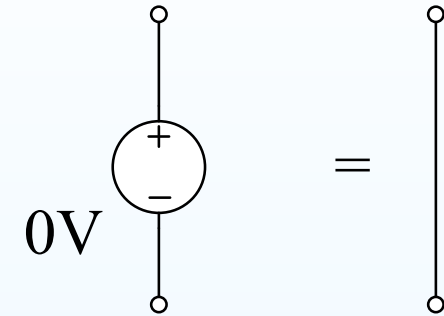
### 4: Linearity and Superposition

- Linearity Theorem
- **Zero-value sources**
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A **zero-valued** voltage source has zero volts between its terminals for any current. It is equivalent to a *short-circuit* or piece of wire or resistor of  $0 \Omega$  (or  $\infty S$ ).



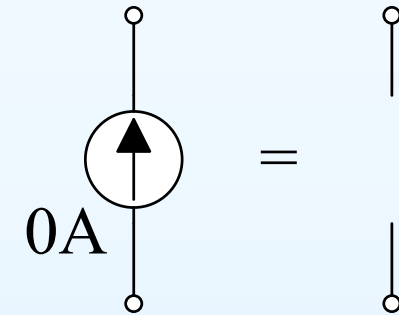A **zero-valued** current source has no current flowing between its terminals. It is equivalent to an *open-circuit* or a broken wire or a resistor of  $\infty \Omega$  (or  $0 S$ ).




# Superposition
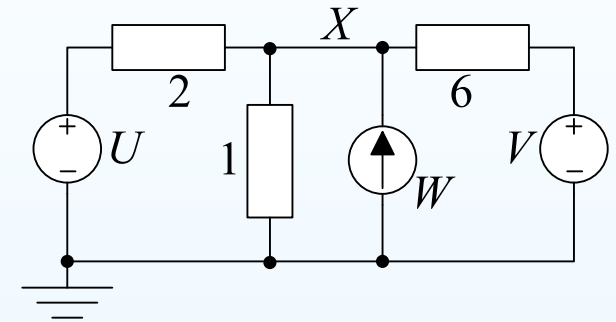
## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

We can use nodal analysis to find  $X$  in terms of  $U$ ,  $V$  and  $W$ .




# Superposition

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- **Superposition**
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

We can use nodal analysis to find  $X$  in terms of  $U$ ,  $V$  and  $W$ .
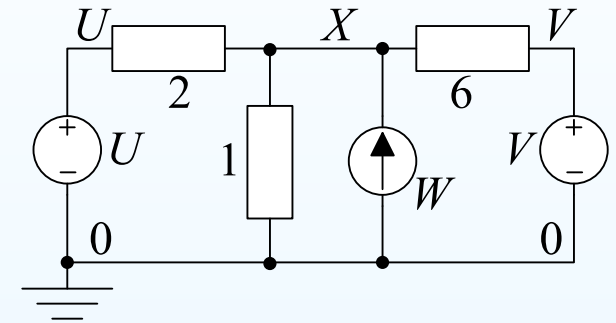
$$\text{KCL: } \frac{X-U}{2} + \frac{X-V}{6} + \frac{X}{1} - W = 0$$



# Superposition


## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- **Superposition**
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

We can use nodal analysis to find  $X$  in terms of  $U$ ,  $V$  and  $W$ .

$$\text{KCL: } \frac{X-U}{2} + \frac{X-V}{6} + \frac{X}{1} - W = 0$$

$$10X - 3U - V - 6W = 0$$

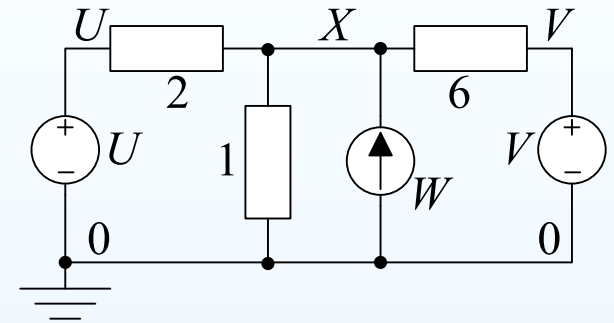

# Superposition

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- **Superposition**
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

We can use nodal analysis to find  $X$  in terms of  $U$ ,  $V$  and  $W$ .

$$\text{KCL: } \frac{X-U}{2} + \frac{X-V}{6} + \frac{X}{1} - W = 0$$

$$10X - 3U - V - 6W = 0$$

$$X = 0.3U + 0.1V + 0.6W$$

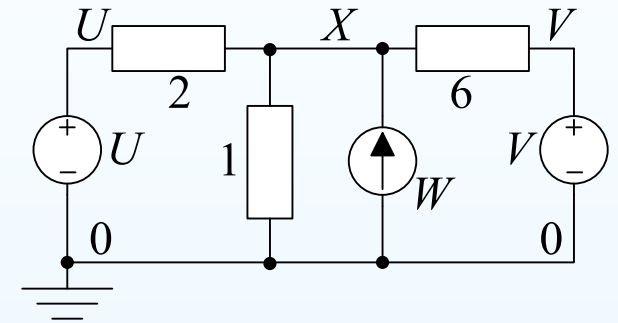



# Superposition

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- **Superposition**
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

We can use nodal analysis to find  $X$  in terms of  $U$ ,  $V$  and  $W$ .

$$\text{KCL: } \frac{X-U}{2} + \frac{X-V}{6} + \frac{X}{1} - W = 0$$

$$10X - 3U - V - 6W = 0$$

$$X = 0.3U + 0.1V + 0.6W$$

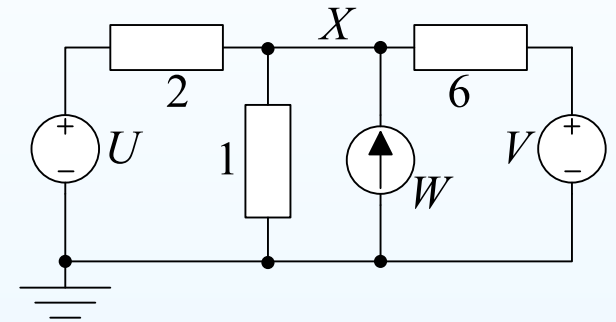

From the linearity theorem, we know anyway that  $X = aU + bV + cW$  so all we need to do is find the values of  $a$ ,  $b$  and  $c$ .

# Superposition

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- **Superposition**
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

We can use nodal analysis to find  $X$  in terms of  $U$ ,  $V$  and  $W$ .


$$\text{KCL: } \frac{X-U}{2} + \frac{X-V}{6} + \frac{X}{1} - W = 0$$

$$10X - 3U - V - 6W = 0$$

$$X = 0.3U + 0.1V + 0.6W$$

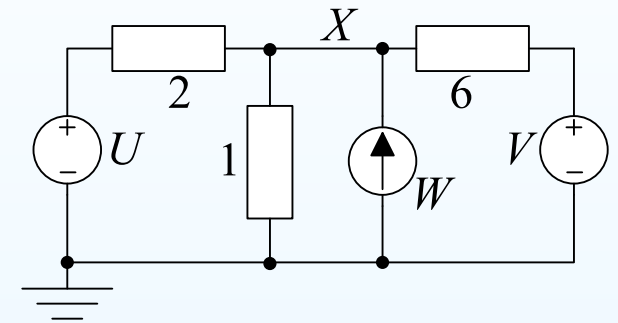

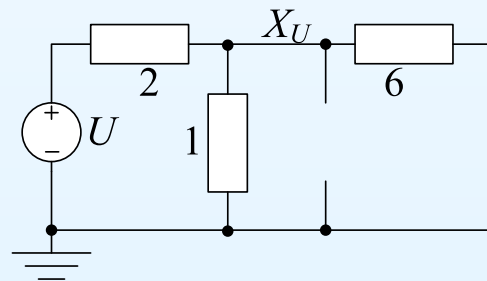From the linearity theorem, we know anyway that  $X = aU + bV + cW$  so all we need to do is find the values of  $a$ ,  $b$  and  $c$ . We find each coefficient in turn by setting all the other sources to zero:



# Superposition

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- **Superposition**
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

We can use nodal analysis to find  $X$  in terms of  $U$ ,  $V$  and  $W$ .


$$\text{KCL: } \frac{X-U}{2} + \frac{X-V}{6} + \frac{X}{1} - W = 0$$

$$10X - 3U - V - 6W = 0$$

$$X = 0.3U + 0.1V + 0.6W$$

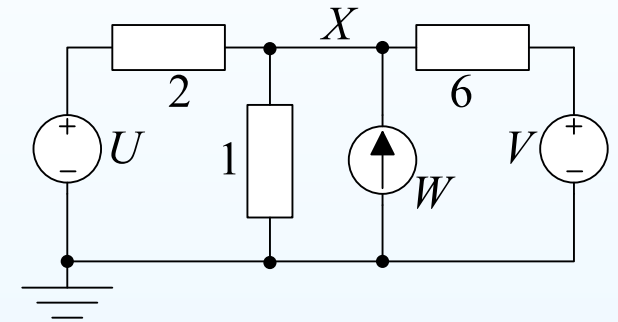

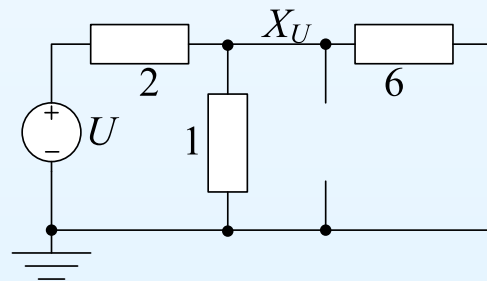From the linearity theorem, we know anyway that  $X = aU + bV + cW$  so all we need to do is find the values of  $a$ ,  $b$  and  $c$ . We find each coefficient in turn by setting all the other sources to zero:



We have  $X_U = aU + b \times 0 + c \times 0 = aU$ .

# Superposition

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- **Superposition**
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

We can use nodal analysis to find  $X$  in terms of  $U$ ,  $V$  and  $W$ .


$$\text{KCL: } \frac{X-U}{2} + \frac{X-V}{6} + \frac{X}{1} - W = 0$$

$$10X - 3U - V - 6W = 0$$

$$X = 0.3U + 0.1V + 0.6W$$

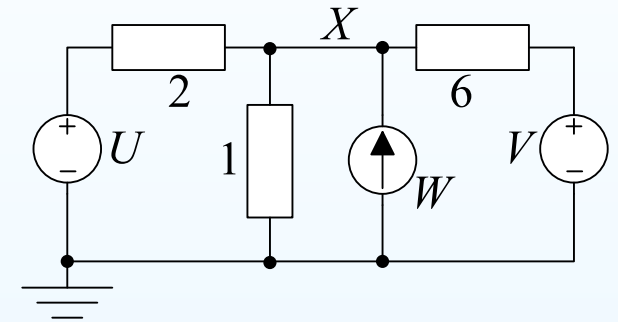

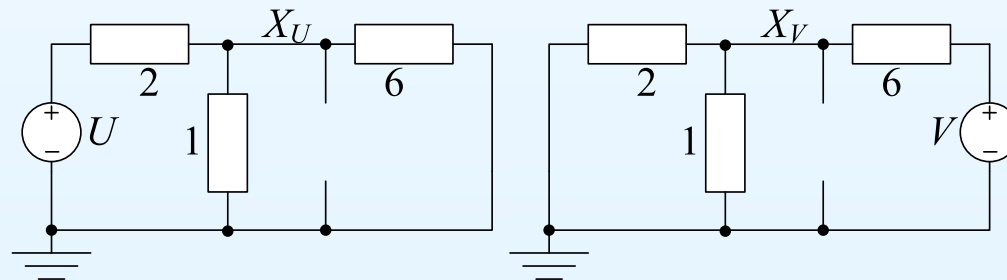From the linearity theorem, we know anyway that  $X = aU + bV + cW$  so all we need to do is find the values of  $a$ ,  $b$  and  $c$ . We find each coefficient in turn by setting all the other sources to zero:



We have  $X_U = aU + b \times 0 + c \times 0 = aU$ .

# Superposition

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- **Superposition**
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

We can use nodal analysis to find  $X$  in terms of  $U$ ,  $V$  and  $W$ .


$$\text{KCL: } \frac{X-U}{2} + \frac{X-V}{6} + \frac{X}{1} - W = 0$$

$$10X - 3U - V - 6W = 0$$

$$X = 0.3U + 0.1V + 0.6W$$

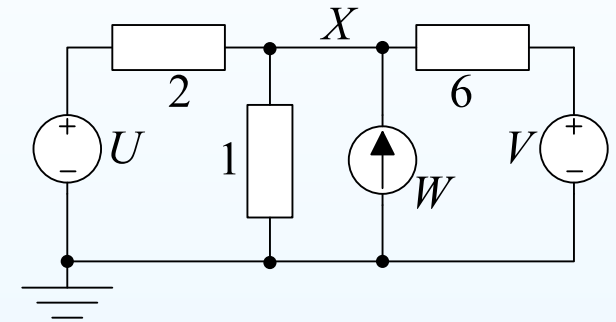

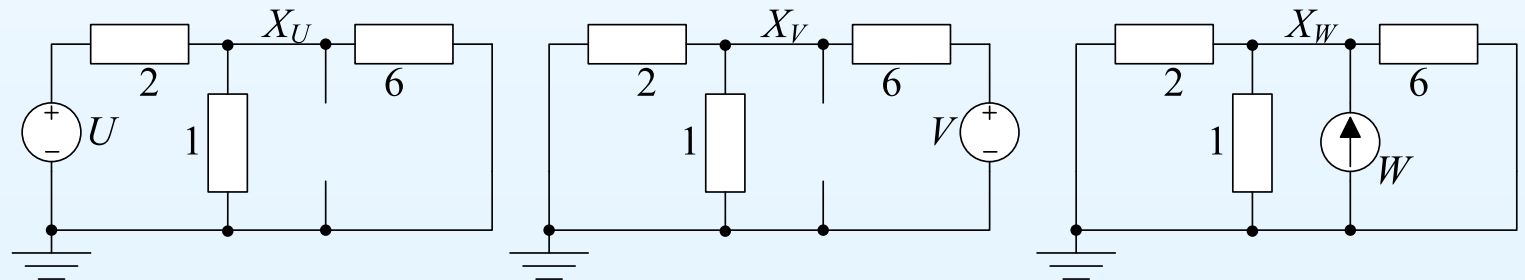From the linearity theorem, we know anyway that  $X = aU + bV + cW$  so all we need to do is find the values of  $a$ ,  $b$  and  $c$ . We find each coefficient in turn by setting all the other sources to zero:



We have  $X_U = aU + b \times 0 + c \times 0 = aU$ .

# Superposition

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- **Superposition**
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

We can use nodal analysis to find  $X$  in terms of  $U$ ,  $V$  and  $W$ .


$$\text{KCL: } \frac{X-U}{2} + \frac{X-V}{6} + \frac{X}{1} - W = 0$$

$$10X - 3U - V - 6W = 0$$

$$X = 0.3U + 0.1V + 0.6W$$

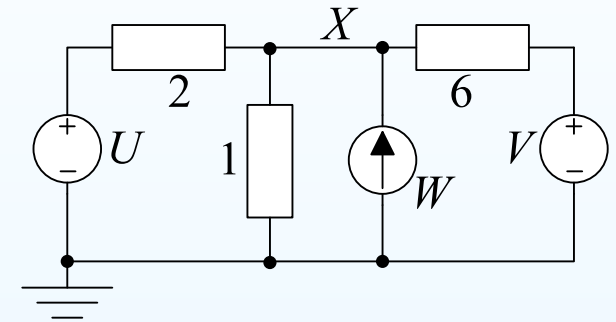

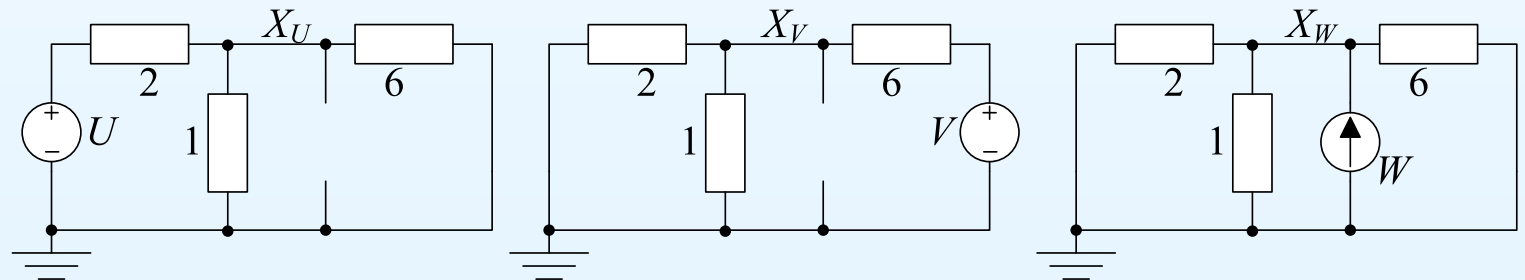From the linearity theorem, we know anyway that  $X = aU + bV + cW$  so all we need to do is find the values of  $a$ ,  $b$  and  $c$ . We find each coefficient in turn by setting all the other sources to zero:



We have  $X_U = aU + b \times 0 + c \times 0 = aU$ .

Similarly,  $X_V = bV$  and  $X_W = cW \Rightarrow X = X_U + X_V + X_W$ .


# Superposition Calculation

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- **Superposition Calculation**
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary
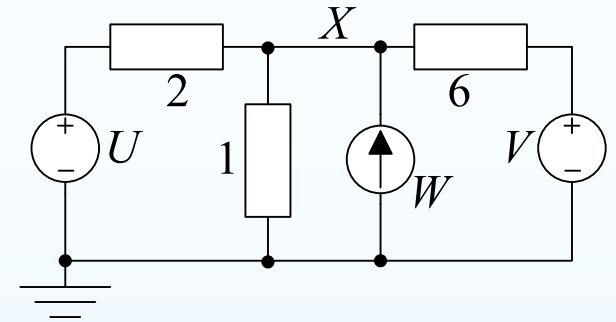
## Superposition:

Find the effect of each source on its own by setting all other sources to zero. Then add up the results.




# Superposition Calculation

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- **Superposition Calculation**
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary
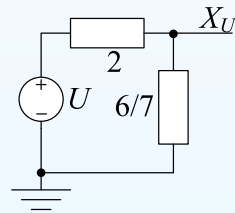
## Superposition:

Find the effect of each source on its own by setting all other sources to zero. Then add up the results.


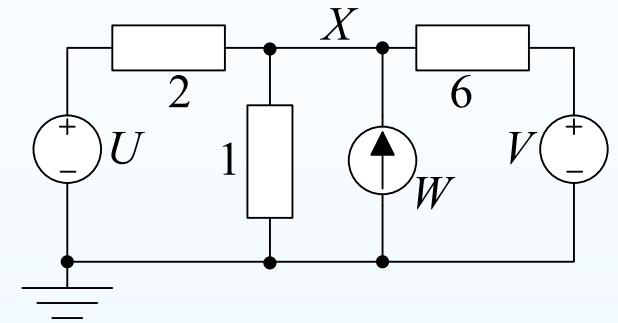
$$X_U = \frac{\frac{6}{7}}{2 + \frac{6}{7}} U = \frac{6}{20} U = 0.3U$$







# Superposition Calculation

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- **Superposition Calculation**
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary
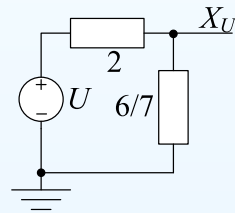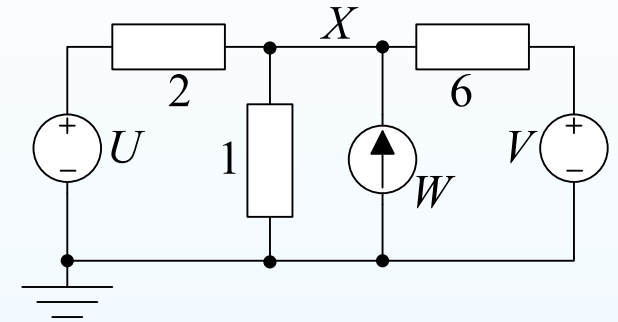
## Superposition:

Find the effect of each source on its own by setting all other sources to zero. Then add up the results.


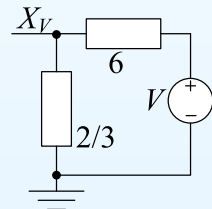
$$X_U = \frac{\frac{6}{7}}{2 + \frac{6}{7}} U = \frac{6}{20} U = 0.3U$$



$$X_V = \frac{\frac{2}{3}}{6 + \frac{2}{3}} V = \frac{2}{20} V = 0.1V$$



# Superposition Calculation

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- **Superposition Calculation**
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary
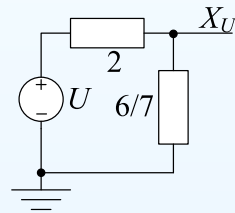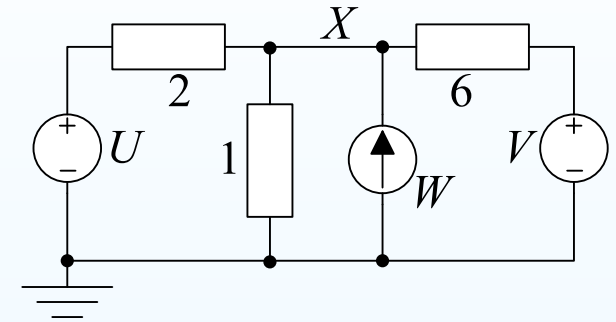
## Superposition:


Find the effect of each source on its own by setting all other sources to zero. Then add up the results.


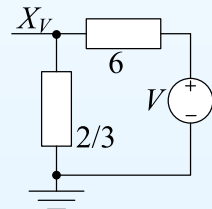
$$X_U = \frac{\frac{6}{7}}{2 + \frac{6}{7}} U = \frac{6}{20} U = 0.3U$$


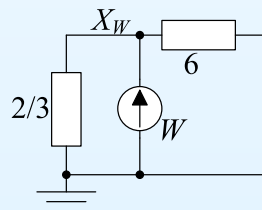
$$X_V = \frac{\frac{2}{3}}{6 + \frac{2}{3}} V = \frac{2}{20} V = 0.1V$$



$$X_W = \frac{6}{6 + \frac{2}{3}} W \times \frac{2}{3} = \frac{12}{20} W = 0.6W$$



# Superposition Calculation

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- **Superposition Calculation**
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary
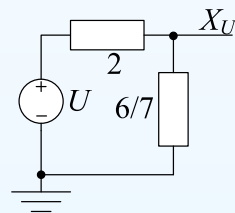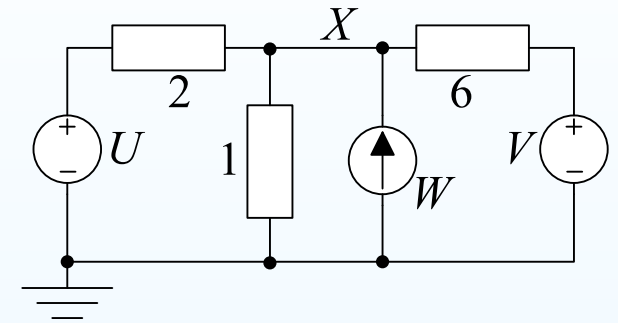
## Superposition:


Find the effect of each source on its own by setting all other sources to zero. Then add up the results.


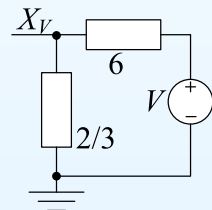
$$X_U = \frac{\frac{6}{7}}{2 + \frac{6}{7}} U = \frac{6}{20} U = 0.3U$$


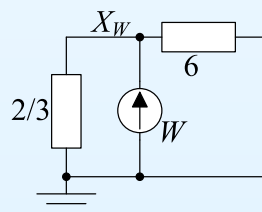
$$X_V = \frac{\frac{2}{3}}{6 + \frac{2}{3}} V = \frac{2}{20} V = 0.1V$$



$$X_W = \frac{6}{6 + \frac{2}{3}} W \times \frac{2}{3} = \frac{12}{20} W = 0.6W$$

Adding them up:  $X = X_U + X_V + X_W$



# Superposition Calculation

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- **Superposition Calculation**
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary
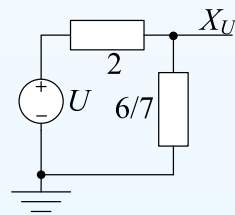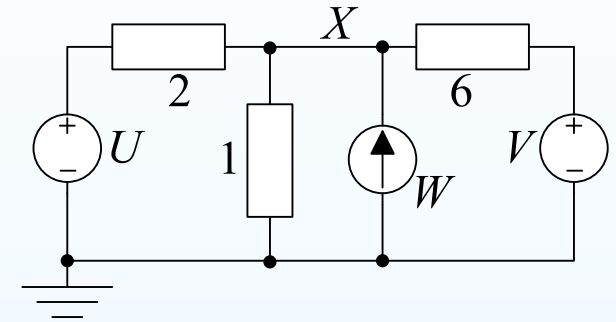
## Superposition:


Find the effect of each source on its own by setting all other sources to zero. Then add up the results.


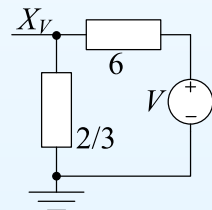
$$X_U = \frac{\frac{6}{7}}{2 + \frac{6}{7}} U = \frac{6}{20} U = 0.3U$$


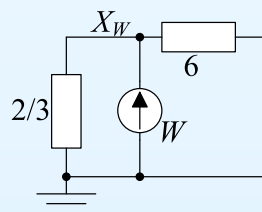
$$X_V = \frac{\frac{3}{2}}{6 + \frac{2}{3}} V = \frac{2}{20} V = 0.1V$$



$$X_W = \frac{6}{6 + \frac{2}{3}} W \times \frac{2}{3} = \frac{12}{20} W = 0.6W$$


Adding them up:  $X = X_U + X_V + X_W = 0.3U + 0.1V + 0.6W$

# Superposition and dependent sources
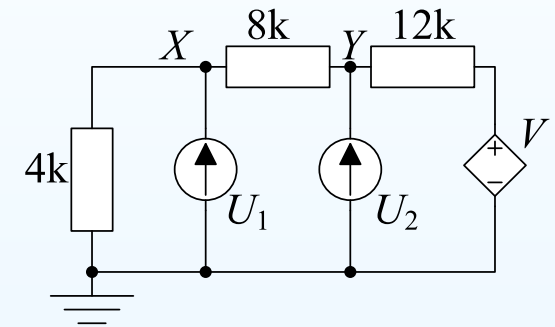
## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here  $V \triangleq Y - X$ .




# Superposition and dependent sources

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- **Superposition and dependent sources**
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here  $V \triangleq Y - X$ .

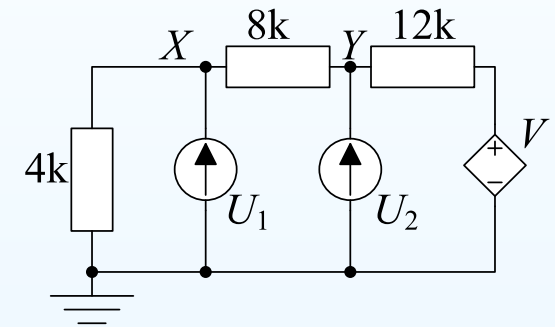**Step 1:** Pretend all sources are independent and use superposition to find expressions for the node voltages:



# Superposition and dependent sources

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- **Superposition and dependent sources**
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here  $V \triangleq Y - X$ .

**Step 1:** Pretend all sources are independent and use superposition to find expressions for the node voltages:

$$X = \frac{10}{3}U_1$$

$$Y = 2U_1$$

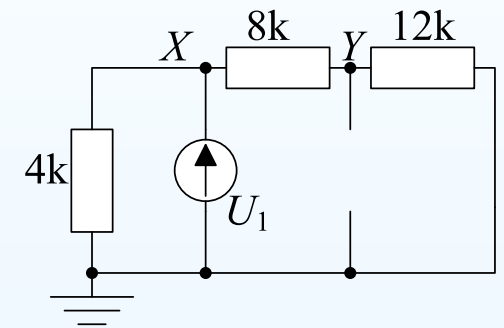

# Superposition and dependent sources

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- **Superposition and dependent sources**
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here  $V \triangleq Y - X$ .

**Step 1:** Pretend all sources are independent and use superposition to find expressions for the node voltages:

$$X = \frac{10}{3}U_1 + 2U_2$$

$$Y = 2U_1 + 6U_2$$

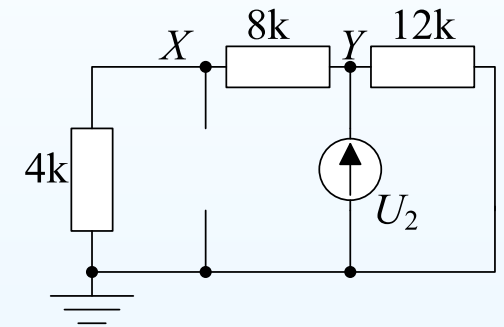



# Superposition and dependent sources

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- **Superposition and dependent sources**
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here  $V \triangleq Y - X$ .

**Step 1:** Pretend all sources are independent and use superposition to find expressions for the node voltages:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}V$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}V$$

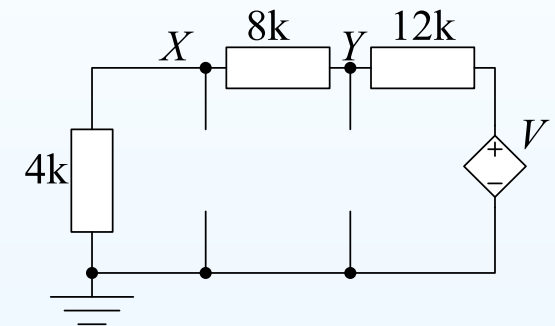

# Superposition and dependent sources

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- **Superposition and dependent sources**
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here  $V \triangleq Y - X$ .


**Step 1:** Pretend all sources are independent and use superposition to find expressions for the node voltages:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}V$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}V$$

**Step 2:** Express the dependent source values in terms of node voltages:

$$V = Y - X$$

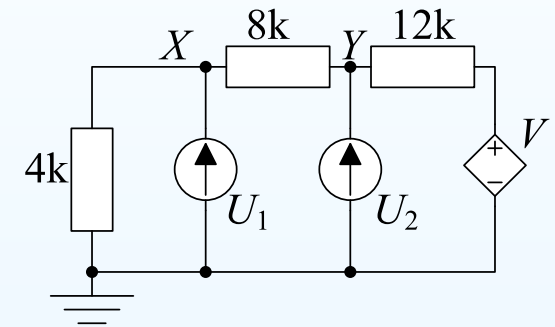

# Superposition and dependent sources

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- **Superposition and dependent sources**
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here  $V \triangleq Y - X$ .

**Step 1:** Pretend all sources are independent and use superposition to find expressions for the node voltages:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}V$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}V$$


**Step 2:** Express the dependent source values in terms of node voltages:

$$V = Y - X$$

**Step 3:** Eliminate the dependent source values from the node voltage equations:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}(Y - X)$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}(Y - X)$$

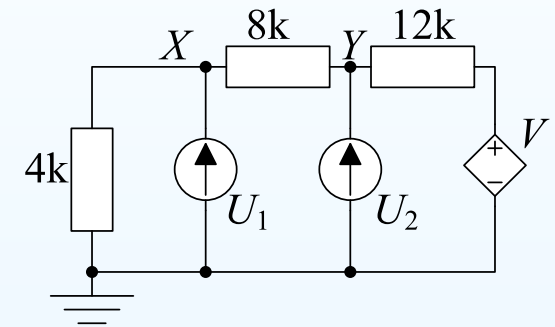

# Superposition and dependent sources

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- **Superposition and dependent sources**
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here  $V \triangleq Y - X$ .

**Step 1:** Pretend all sources are independent and use superposition to find expressions for the node voltages:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}V$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}V$$

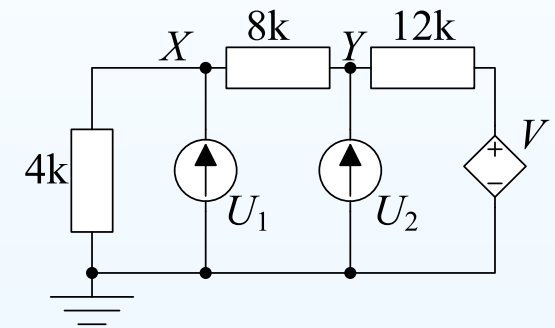

**Step 2:** Express the dependent source values in terms of node voltages:

$$V = Y - X$$

**Step 3:** Eliminate the dependent source values from the node voltage equations:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}(Y - X) \Rightarrow \frac{7}{6}X - \frac{1}{6}Y = \frac{10}{3}U_1 + 2U_2$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}(Y - X)$$

# Superposition and dependent sources

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- **Superposition and dependent sources**
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here  $V \triangleq Y - X$ .

**Step 1:** Pretend all sources are independent and use superposition to find expressions for the node voltages:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}V$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}V$$

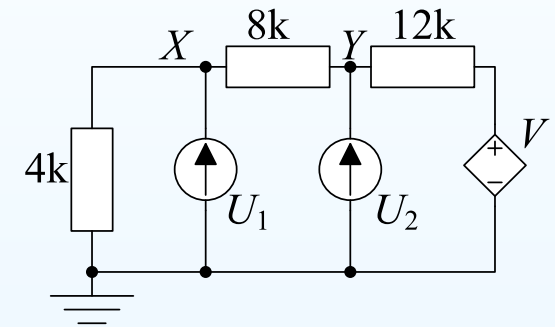

**Step 2:** Express the dependent source values in terms of node voltages:

$$V = Y - X$$

**Step 3:** Eliminate the dependent source values from the node voltage equations:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}(Y - X) \Rightarrow \frac{7}{6}X - \frac{1}{6}Y = \frac{10}{3}U_1 + 2U_2$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}(Y - X) \Rightarrow \frac{1}{2}X + \frac{1}{2}Y = 2U_1 + 6U_2$$

# Superposition and dependent sources

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- **Superposition and dependent sources**
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here  $V \triangleq Y - X$ .

**Step 1:** Pretend all sources are independent and use superposition to find expressions for the node voltages:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}V$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}V$$

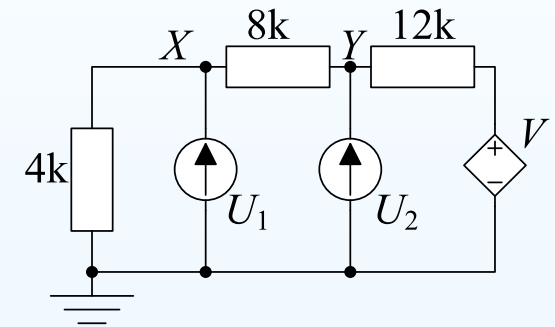

**Step 2:** Express the dependent source values in terms of node voltages:

$$V = Y - X$$

**Step 3:** Eliminate the dependent source values from the node voltage equations:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}(Y - X) \Rightarrow \frac{7}{6}X - \frac{1}{6}Y = \frac{10}{3}U_1 + 2U_2$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}(Y - X) \Rightarrow \frac{1}{2}X + \frac{1}{2}Y = 2U_1 + 6U_2$$

$$X = 3U_1 + 3U_2$$

$$Y = U_1 + 9U_2$$

# Superposition and dependent sources

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- **Superposition and dependent sources**
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

A *dependent source* is one that is determined by the voltage and/or current elsewhere in the circuit via a known equation. Here  $V \triangleq Y - X$ .

**Step 1:** Pretend all sources are independent and use superposition to find expressions for the node voltages:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}V$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}V$$

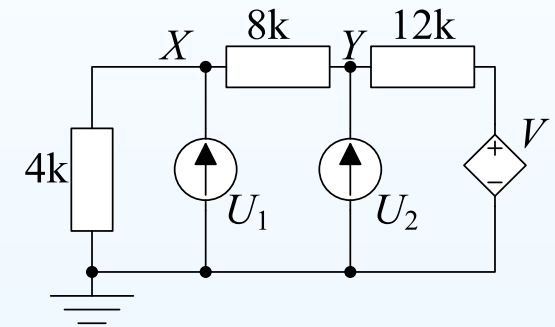

**Step 2:** Express the dependent source values in terms of node voltages:

$$V = Y - X$$

**Step 3:** Eliminate the dependent source values from the node voltage equations:

$$X = \frac{10}{3}U_1 + 2U_2 + \frac{1}{6}(Y - X) \Rightarrow \frac{7}{6}X - \frac{1}{6}Y = \frac{10}{3}U_1 + 2U_2$$

$$Y = 2U_1 + 6U_2 + \frac{1}{2}(Y - X) \Rightarrow \frac{1}{2}X + \frac{1}{2}Y = 2U_1 + 6U_2$$

$$X = 3U_1 + 3U_2$$

$$Y = U_1 + 9U_2$$


**Note:** This is an **alternative** to nodal analysis: you get the same answer.

# Single Variable Source
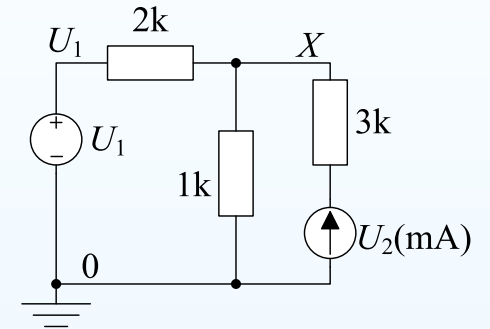
## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- **Single Variable Source**
- Superposition and Power
- Proportionality
- Summary

Any current or voltage can be written  $X = a_1U_1 + a_2U_2 + a_3U_3 + \dots$





# Single Variable Source


## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- **Single Variable Source**
- Superposition and Power
- Proportionality
- Summary

Any current or voltage can be written  $X = a_1U_1 + a_2U_2 + a_3U_3 + \dots$

Using nodal analysis (slide 4-2) or else superposition:

$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2.$$

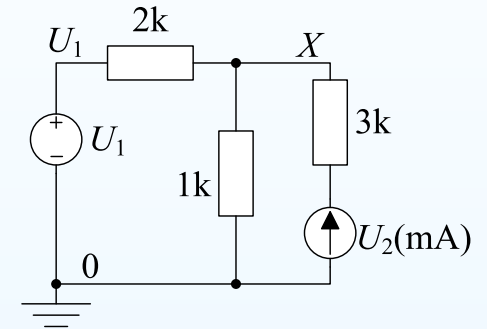

# Single Variable Source

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- **Single Variable Source**
- Superposition and Power
- Proportionality
- Summary

Any current or voltage can be written  $X = a_1U_1 + a_2U_2 + a_3U_3 + \dots$

Using nodal analysis (slide 4-2) or else superposition:

$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2.$$

Suppose we know  $U_2 = 6 \text{ mA}$

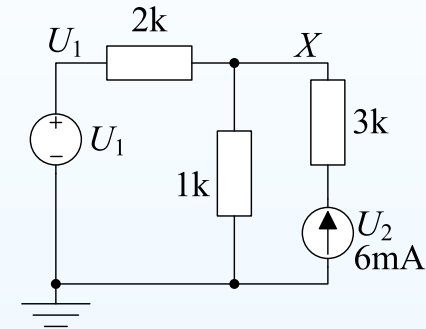

# Single Variable Source

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- **Single Variable Source**
- Superposition and Power
- Proportionality
- Summary


Any current or voltage can be written  $X = a_1U_1 + a_2U_2 + a_3U_3 + \dots$

Using nodal analysis (slide 4-2) or else superposition:

$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2.$$

Suppose we know  $U_2 = 6 \text{ mA}$ , then
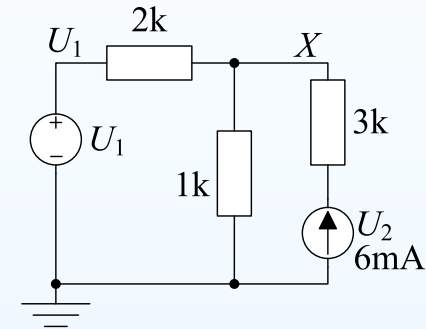
$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2 = \frac{1}{3}U_1 + 4.$$



# Single Variable Source

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- **Single Variable Source**
- Superposition and Power
- Proportionality
- Summary

Any current or voltage can be written  $X = a_1U_1 + a_2U_2 + a_3U_3 + \dots$

Using nodal analysis (slide 4-2) or else superposition:

$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2.$$


Suppose we know  $U_2 = 6 \text{ mA}$ , then

$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2 = \frac{1}{3}U_1 + 4.$$

If all the independent sources except for  $U_1$  have known fixed values, then

$$X = a_1U_1 + b$$

where  $b = a_2U_2 + a_3U_3 + \dots$

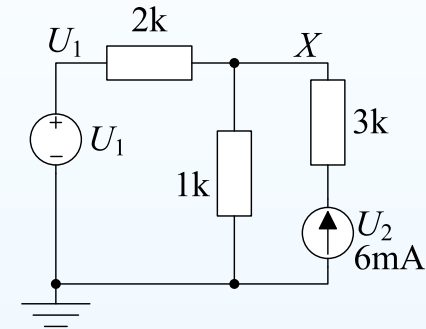

# Single Variable Source

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- **Single Variable Source**
- Superposition and Power
- Proportionality
- Summary

Any current or voltage can be written  $X = a_1U_1 + a_2U_2 + a_3U_3 + \dots$

Using nodal analysis (slide 4-2) or else superposition:

$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2.$$

Suppose we know  $U_2 = 6 \text{ mA}$ , then



$$X = \frac{1}{3}U_1 + \frac{2}{3}U_2 = \frac{1}{3}U_1 + 4.$$

If all the independent sources except for  $U_1$  have known fixed values, then

$$X = a_1U_1 + b$$

where  $b = a_2U_2 + a_3U_3 + \dots$

This has a straight line graph.

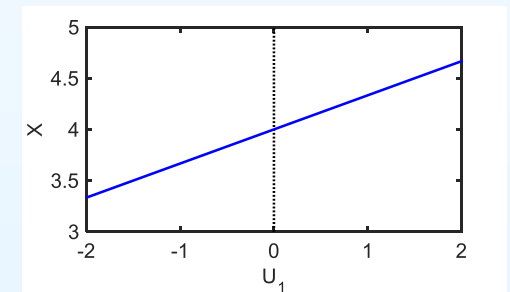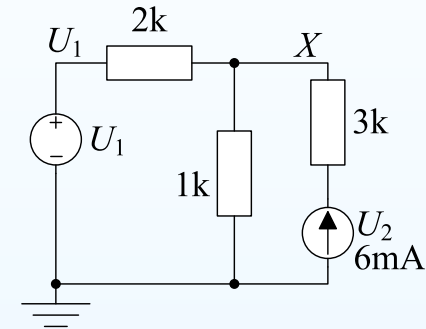

# Superposition and Power

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- **Superposition and Power**
- Proportionality
- Summary

The power absorbed (or *dissipated*) by a component always equals  $VI$  where the measurement directions of  $V$  and  $I$  follow the passive sign convention.

For a resistor  $VI = \frac{V^2}{R} = I^2 R$ .

# Superposition and Power


## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

The power absorbed (or *dissipated*) by a component always equals  $VI$  where the measurement directions of  $V$  and  $I$  follow the passive sign convention.

For a resistor  $VI = \frac{V^2}{R} = I^2 R$ .

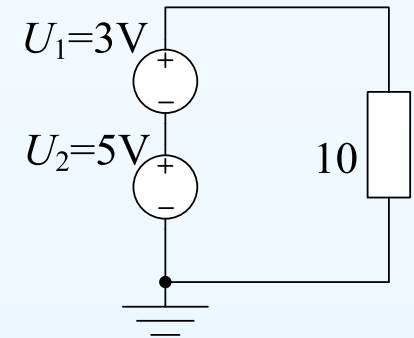Power in resistor is  $P = \frac{(U_1 + U_2)^2}{10} = 6.4 \text{ W}$



# Superposition and Power

## 4: Linearity and Superposition


- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- Summary

The power absorbed (or *dissipated*) by a component always equals  $VI$  where the measurement directions of  $V$  and  $I$  follow the passive sign convention.

For a resistor  $VI = \frac{V^2}{R} = I^2 R$ .

$$\text{Power in resistor is } P = \frac{(U_1 + U_2)^2}{10} = 6.4 \text{ W}$$
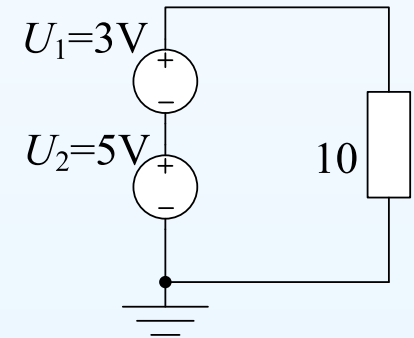
$$\text{Power due to } U_1 \text{ alone is } P_1 = \frac{U_1^2}{10} = 0.9 \text{ W}$$





# Superposition and Power

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- **Superposition and Power**
- Proportionality
- Summary


The power absorbed (or *dissipated*) by a component always equals  $VI$  where the measurement directions of  $V$  and  $I$  follow the passive sign convention.

For a resistor  $VI = \frac{V^2}{R} = I^2 R$ .

$$\text{Power in resistor is } P = \frac{(U_1 + U_2)^2}{10} = 6.4 \text{ W}$$

$$\text{Power due to } U_1 \text{ alone is } P_1 = \frac{U_1^2}{10} = 0.9 \text{ W}$$
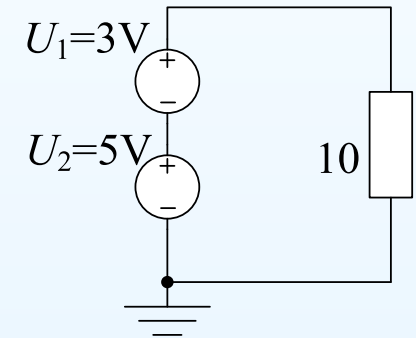
$$\text{Power due to } U_2 \text{ alone is } P_2 = \frac{U_2^2}{10} = 2.5 \text{ W}$$



# Superposition and Power

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- **Superposition and Power**
- Proportionality
- Summary

The power absorbed (or *dissipated*) by a component always equals  $VI$  where the measurement directions of  $V$  and  $I$  follow the passive sign convention.


For a resistor  $VI = \frac{V^2}{R} = I^2 R$ .

$$\text{Power in resistor is } P = \frac{(U_1 + U_2)^2}{10} = 6.4 \text{ W}$$

$$\text{Power due to } U_1 \text{ alone is } P_1 = \frac{U_1^2}{10} = 0.9 \text{ W}$$

$$\text{Power due to } U_2 \text{ alone is } P_2 = \frac{U_2^2}{10} = 2.5 \text{ W}$$

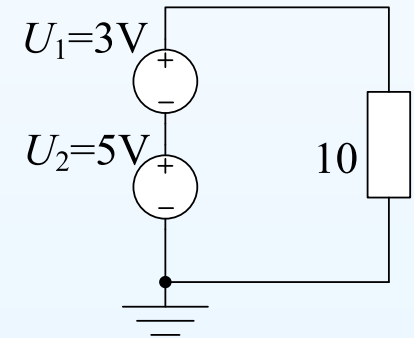$P \neq P_1 + P_2 \Rightarrow$  **Power does not obey superposition.**



# Superposition and Power

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- **Superposition and Power**
- Proportionality
- Summary

The power absorbed (or *dissipated*) by a component always equals  $VI$  where the measurement directions of  $V$  and  $I$  follow the passive sign convention.

For a resistor  $VI = \frac{V^2}{R} = I^2 R$ .


$$\text{Power in resistor is } P = \frac{(U_1 + U_2)^2}{10} = 6.4 \text{ W}$$

$$\text{Power due to } U_1 \text{ alone is } P_1 = \frac{U_1^2}{10} = 0.9 \text{ W}$$

$$\text{Power due to } U_2 \text{ alone is } P_2 = \frac{U_2^2}{10} = 2.5 \text{ W}$$

$P \neq P_1 + P_2 \Rightarrow$  **Power does not obey superposition.**

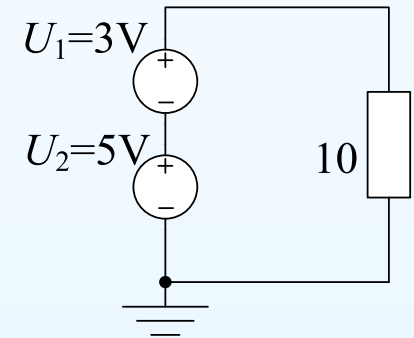You must use superposition to calculate the total  $V$  and/or the total  $I$  and then calculate the power.



# Proportionality

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- **Proportionality**
- Summary

From the linearity theorem, all voltages and currents have the form  $\sum a_i U_i$  where the  $U_i$  are the values of the independent sources.

If you multiply *all* the independent sources by the same factor,  $k$ , then all voltages and currents in the circuit will be multiplied by  $k$ .

The power dissipated in any component will be multiplied by  $k^2$ .

# Proportionality

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- **Proportionality**
- Summary

From the linearity theorem, all voltages and currents have the form  $\sum a_i U_i$  where the  $U_i$  are the values of the independent sources.

If you multiply *all* the independent sources by the same factor,  $k$ , then all voltages and currents in the circuit will be multiplied by  $k$ .

The power dissipated in any component will be multiplied by  $k^2$ .

### Special Case:

If there is only one independent source,  $U$ , then all voltages and currents are proportional to  $U$  and all power dissipations are proportional to  $U^2$ .

# Summary

## 4: Linearity and Superposition

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- **Summary**

- **Linearity Theorem:**  $X = \sum_i a_i U_i$  over all independent sources  $U_i$

- Linearity Theorem
- Zero-value sources
- Superposition
- Superposition Calculation
- Superposition and dependent sources
- Single Variable Source
- Superposition and Power
- Proportionality
- **Summary**

## Summary

- **Linearity Theorem:**  $X = \sum_i a_i U_i$  over all independent sources  $U_i$
- **Superposition:** sometimes simpler than nodal analysis, often more insight.
  - Zero-value voltage and current sources
  - Dependent sources - treat as independent and add dependency as an extra equation

## Summary

- **Linearity Theorem:**  $X = \sum_i a_i U_i$  over all independent sources  $U_i$
- **Superposition:** sometimes simpler than nodal analysis, often more insight.
  - Zero-value voltage and current sources
  - Dependent sources - treat as independent and add dependency as an extra equation
- If all sources are fixed except for  $U_1$  then all voltages and currents in the circuit have the form  $aU_1 + b$ .



## Summary

- **Linearity Theorem:**  $X = \sum_i a_i U_i$  over all independent sources  $U_i$
- **Superposition:** sometimes simpler than nodal analysis, often more insight.
  - Zero-value voltage and current sources
  - Dependent sources - treat as independent and add dependency as an extra equation
- If all sources are fixed except for  $U_1$  then all voltages and currents in the circuit have the form  $aU_1 + b$ .
- Power **does not obey** superposition.

## Summary

- **Linearity Theorem:**  $X = \sum_i a_i U_i$  over all independent sources  $U_i$
- **Superposition:** sometimes simpler than nodal analysis, often more insight.
  - Zero-value voltage and current sources
  - Dependent sources - treat as independent and add dependency as an extra equation
- If all sources are fixed except for  $U_1$  then all voltages and currents in the circuit have the form  $aU_1 + b$ .
- Power **does not obey** superposition.
- **Proportionality:** multiplying all sources by  $k$  multiplies all voltages and currents by  $k$  and all powers by  $k^2$ .

## Summary

- **Linearity Theorem:**  $X = \sum_i a_i U_i$  over all independent sources  $U_i$
- **Superposition:** sometimes simpler than nodal analysis, often more insight.
  - Zero-value voltage and current sources
  - Dependent sources - treat as independent and add dependency as an extra equation
- If all sources are fixed except for  $U_1$  then all voltages and currents in the circuit have the form  $aU_1 + b$ .
- Power **does not obey** superposition.
- **Proportionality:** multiplying all sources by  $k$  multiplies all voltages and currents by  $k$  and all powers by  $k^2$ .

For further details see Hayt Ch 5 or Irwin Ch 5.