

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

7: Negative Feedback is Wonderful

Block Diagram

7: Negative Feedback is Wonderful


- **Block Diagram**

- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

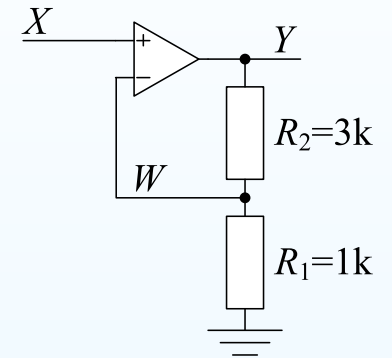Examples

- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

In the non-inverting op amp circuit we take a fraction of the output signal, Y , and subtract it from the input signal, X .



Block Diagram

7: Negative Feedback is Wonderful

- **Block Diagram**

- Solving Block Diagrams

- Inverting Amplifier

- Negative Feedback

Examples

- Benefits of Negative

Feedback

- Gain Stabilization

- Distortion Reduction +

- Interference Rejection

- Cause/Effect Inversion

- Instability

- Summary



In the non-inverting op amp circuit we take a fraction of the output signal, Y , and subtract it from the input signal, X .

We can represent this using a block diagram:

$$A = \frac{Y}{E}: \text{the gain of the op amp}$$

$$B = \frac{W}{Y} = \frac{1}{4}: \text{gain of the feedback path}$$

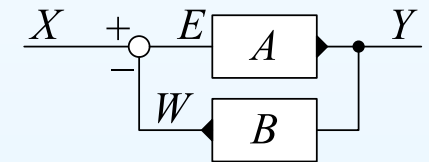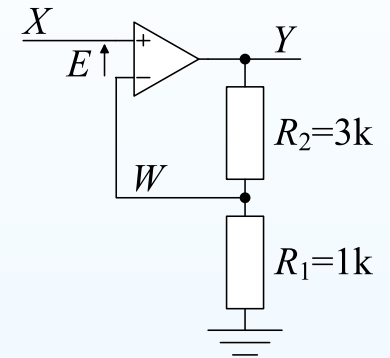The “+” and “-” signs indicate that the feedback is subtracted from X to give an “error” signal, E .



Block Diagram

7: Negative Feedback is Wonderful

- **Block Diagram**

- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- Benefits of Negative Feedback

- Gain Stabilization

- Distortion Reduction +

- Interference Rejection

- Cause/Effect Inversion

- Instability

- Summary

In the non-inverting op amp circuit we take a fraction of the output signal, Y , and subtract it from the input signal, X .




We can represent this using a block diagram:

$$A = \frac{Y}{E}: \text{the gain of the op amp}$$

$$B = \frac{W}{Y} = \frac{1}{4}: \text{gain of the feedback path}$$

The “+” and “-” signs indicate that the feedback is subtracted from X to give an “error” signal, E .

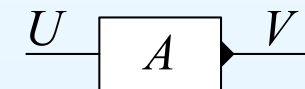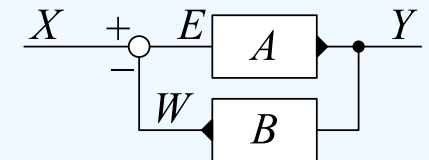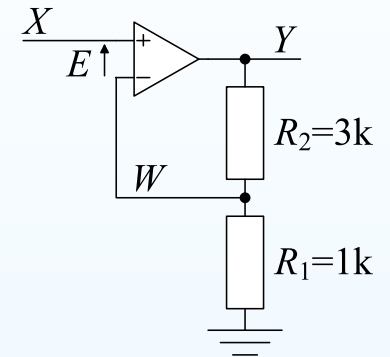A *gain block* has one input and one output (indicated here by an arrow): $V = A \times U$



Block Diagram

7: Negative Feedback is Wonderful

- **Block Diagram**

- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- Benefits of Negative Feedback

- Gain Stabilization

- Distortion Reduction

- Interference Rejection

- Cause/Effect Inversion

- Instability

- Summary

In the non-inverting op amp circuit we take a fraction of the output signal, Y , and subtract it from the input signal, X .

We can represent this using a block diagram:





$$A = \frac{Y}{E}: \text{the gain of the op amp}$$

$$B = \frac{W}{Y} = \frac{1}{4}: \text{gain of the feedback path}$$

The “+” and “-” signs indicate that the feedback is subtracted from X to give an “error” signal, E .

A *gain block* has one input and one output (indicated here by an arrow): $V = A \times U$

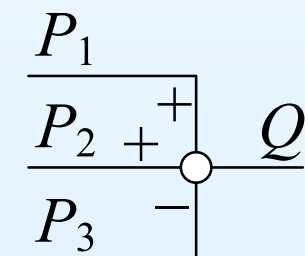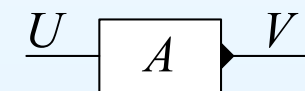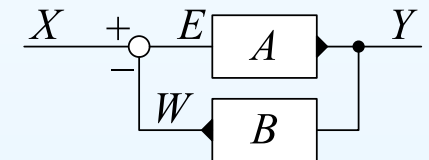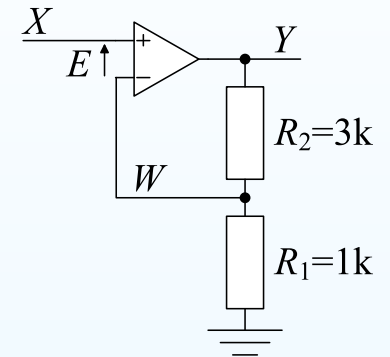An *adder block* many inputs and one output. The signs indicate whether each input is added or subtracted: $Q = P_1 + P_2 - P_3$



Block Diagram

7: Negative Feedback is Wonderful

- **Block Diagram**

- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- Benefits of Negative Feedback

- Gain Stabilization

- Distortion Reduction +

- Interference Rejection

- Cause/Effect Inversion

- Instability

- Summary

In the non-inverting op amp circuit we take a fraction of the output signal, Y , and subtract it from the input signal, X .

We can represent this using a block diagram:





$$A = \frac{Y}{E}: \text{the gain of the op amp}$$

$$B = \frac{W}{Y} = \frac{1}{4}: \text{gain of the feedback path}$$

The “+” and “-” signs indicate that the feedback is subtracted from X to give an “error” signal, E .

A *gain block* has one input and one output (indicated here by an arrow): $V = A \times U$

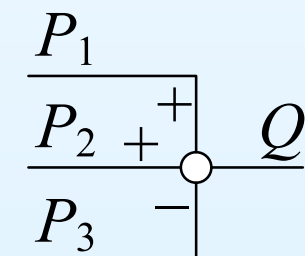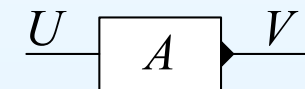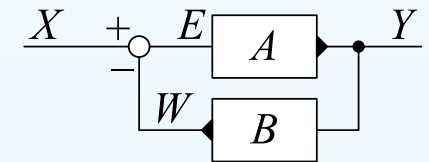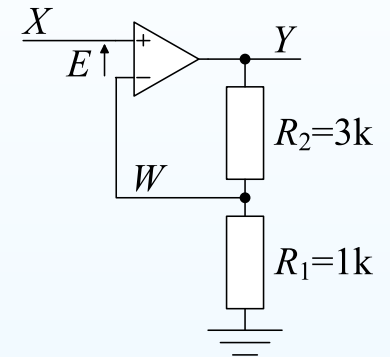An *adder block* many inputs and one output. The signs indicate whether each input is added or subtracted: $Q = P_1 + P_2 - P_3$




Normally, **inputs are on the left** and **outputs are on the right**.

Solving Block Diagrams

7: Negative Feedback is Wonderful

- Block Diagram
 - Solving Block Diagrams
 - Inverting Amplifier
 - Negative Feedback
- Examples
- Benefits of Negative Feedback
- Feedback
- Gain Stabilization
 - Distortion Reduction +
 - Interference Rejection
 - Cause/Effect Inversion
 - Instability
 - Summary

- Label inputs, output and adder outputs

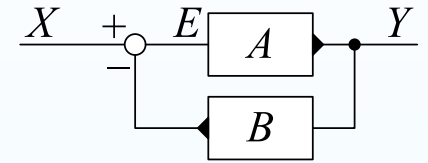


Solving Block Diagrams

7: Negative Feedback is Wonderful

- Block Diagram
 - Solving Block Diagrams
 - Inverting Amplifier
 - Negative Feedback
- Examples
- Benefits of Negative Feedback
 - Gain Stabilization
 - Distortion Reduction
 - Interference Rejection
 - Cause/Effect Inversion
 - Instability
 - Summary

- Label inputs, output and adder outputs

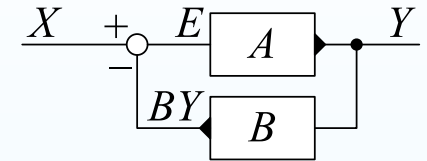

- Write down equations for the output and all adder outputs

$$Y = AE$$


$$E = X - BY$$

Solving Block Diagrams

7: Negative Feedback is Wonderful

- Block Diagram
 - Solving Block Diagrams
 - Inverting Amplifier
 - Negative Feedback
- Examples
- Benefits of Negative Feedback
 - Gain Stabilization
 - Distortion Reduction
 - Interference Rejection
 - Cause/Effect Inversion
 - Instability
 - Summary

- Label inputs, output and adder outputs

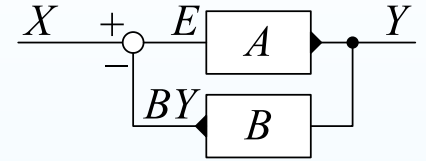

- Write down equations for the output and all adder outputs

$$Y = AE$$

$$E = X - BY$$

Never use Kichoff's current law in block diagrams.

Solving Block Diagrams

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams

- Inverting Amplifier
- Negative Feedback

Examples

- Benefits of Negative Feedback

- Gain Stabilization

- Distortion Reduction +


- Interference Rejection

- Cause/Effect Inversion

- Instability

- Summary

- Label inputs, output and adder outputs

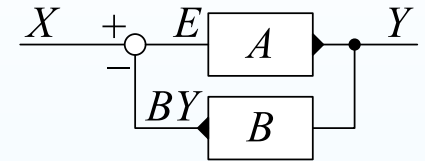

- Write down equations for the output and all adder outputs

$$Y = AE$$

$$E = X - BY$$

Never use Kichoff's current law in block diagrams.

- Solve the equations by eliminating unwanted variables

Solving Block Diagrams

7: Negative Feedback is Wonderful

- Block Diagram

- Solving Block Diagrams

- Inverting Amplifier

- Negative Feedback

Examples

- Benefits of Negative Feedback

- Gain Stabilization

- Distortion Reduction


- Interference Rejection

- Cause/Effect Inversion

- Instability

- Summary

- Label inputs, output and adder outputs

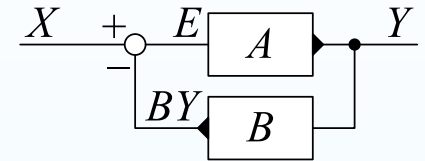

- Write down equations for the output and all adder outputs

$$Y = AE$$

$$E = X - BY$$

Never use Kichoff's current law in block diagrams.

- Solve the equations by eliminating unwanted variables

$$Y = AE$$

Solving Block Diagrams

7: Negative Feedback is Wonderful


- Block Diagram
- Solving Block Diagrams

- Inverting Amplifier
- Negative Feedback

Examples

- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

- Label inputs, output and adder outputs

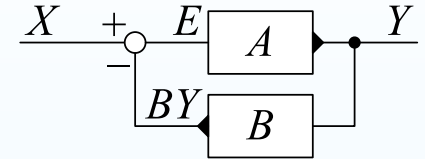

- Write down equations for the output and all adder outputs

$$Y = AE$$

$$E = X - BY$$

Never use Kichoff's current law in block diagrams.

- Solve the equations by eliminating unwanted variables

$$Y = AE = A(X - BY)$$

Solving Block Diagrams

7: Negative Feedback is Wonderful

- Block Diagram

- Solving Block Diagrams

- Inverting Amplifier

- Negative Feedback

Examples

- Benefits of Negative

Feedback

- Gain Stabilization

- Distortion Reduction


- Interference Rejection

- Cause/Effect Inversion

- Instability

- Summary

- Label inputs, output and adder outputs

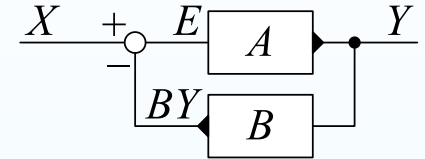

- Write down equations for the output and all adder outputs

$$Y = AE$$

$$E = X - BY$$

Never use Kichoff's current law in block diagrams.

- Solve the equations by eliminating unwanted variables

$$Y = AE = A(X - BY) = AX - ABY$$

Solving Block Diagrams

7: Negative Feedback is Wonderful

- Block Diagram

- Solving Block Diagrams

- Inverting Amplifier

- Negative Feedback

Examples

- Benefits of Negative Feedback

Feedback

- Gain Stabilization

- Distortion Reduction


- Interference Rejection

- Cause/Effect Inversion

- Instability

- Summary

- Label inputs, output and adder outputs

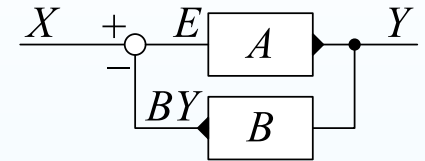

- Write down equations for the output and all adder outputs

$$Y = AE$$

$$E = X - BY$$

Never use Kichoff's current law in block diagrams.

- Solve the equations by eliminating unwanted variables

$$Y = AE = A(X - BY) = AX - ABY$$


$$\Rightarrow Y(1 + AB) = AX$$

Solving Block Diagrams

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

- Label inputs, output and adder outputs

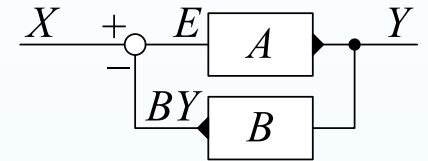

- Write down equations for the output and all adder outputs

$$Y = AE$$

$$E = X - BY$$

Never use Kichoff's current law in block diagrams.

- Solve the equations by eliminating unwanted variables

$$Y = AE = A(X - BY) = AX - ABY$$

$$\Rightarrow Y(1 + AB) = AX \Rightarrow \frac{Y}{X} = \frac{A}{1 + AB}$$

Solving Block Diagrams

7: Negative Feedback is Wonderful

- Block Diagram

- Solving Block Diagrams

- Inverting Amplifier

- Negative Feedback

Examples

- Benefits of Negative Feedback

Feedback

- Gain Stabilization

- Distortion Reduction


- Interference Rejection

- Cause/Effect Inversion

- Instability

- Summary

- Label inputs, output and adder outputs

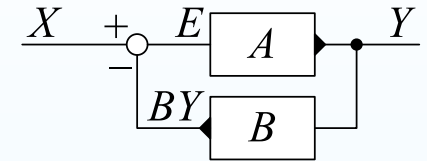

- Write down equations for the output and all adder outputs

$$Y = AE$$

$$E = X - BY$$


Never use Kichoff's current law in block diagrams.

- Solve the equations by eliminating unwanted variables

$$Y = AE = A(X - BY) = AX - ABY$$

$$\Rightarrow Y(1 + AB) = AX \Rightarrow \frac{Y}{X} = \frac{A}{1 + AB}$$

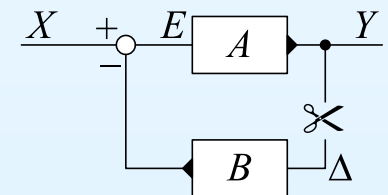AB is called the *loop gain* of the circuit. If you break the loop at any point and inject a signal Δ after the break, this will cause the other side of the break to change by $-\Delta \times AB$.




Inverting Amplifier

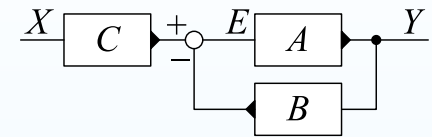7: Negative Feedback is Wonderful

- Block Diagram
 - Solving Block Diagrams
 - **Inverting Amplifier**
 - Negative Feedback
- Examples
- Benefits of Negative Feedback
- Feedback
- Gain Stabilization
 - Distortion Reduction +
 - Interference Rejection
 - Cause/Effect Inversion
 - Instability
 - Summary

Sometimes we have an additional block at the input shown here as C .




Inverting Amplifier

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- **Inverting Amplifier**
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Sometimes we have an additional block at the input shown here as C .

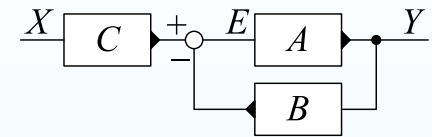We see that $E = CX - BY$ and, as before,
 $Y = AE$



Inverting Amplifier

7: Negative Feedback is Wonderful


- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Sometimes we have an additional block at the input shown here as C .

We see that $E = CX - BY$ and, as before,

$$Y = AE$$
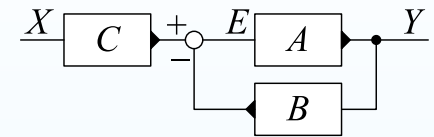
$$\text{Eliminating } E : \frac{Y}{X} = \frac{CA}{1+AB} = \frac{C}{A^{-1}+B}$$



Inverting Amplifier

7: Negative Feedback is Wonderful


- Block Diagram
- Solving Block Diagrams
- **Inverting Amplifier**
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Sometimes we have an additional block at the input shown here as C .

We see that $E = CX - BY$ and, as before,

$$Y = AE$$
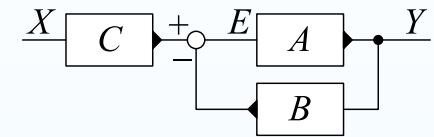
$$\text{Eliminating } E : \frac{Y}{X} = \frac{CA}{1+AB} = \frac{C}{A^{-1}+B} \approx \frac{C}{B}$$



provided $A^{-1} \ll B$.

Inverting Amplifier

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams

- **Inverting Amplifier**

- Negative Feedback

Examples

- Benefits of Negative Feedback

- Gain Stabilization

- Distortion Reduction

- Interference Rejection

- Cause/Effect Inversion

- Instability

- Summary


Sometimes we have an additional block at the input shown here as C .

We see that $E = CX - BY$ and, as before,

$$Y = AE$$

Eliminating E : $\frac{Y}{X} = \frac{CA}{1+AB} = \frac{C}{A^{-1}+B} \approx \frac{C}{B}$ provided $A^{-1} \ll B$.

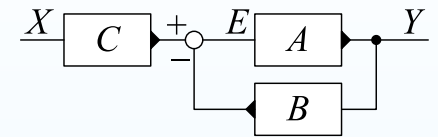$\frac{Y}{X}$ equals the forward gain, CA , divided by the loop gain plus one.



Inverting Amplifier

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams

- **Inverting Amplifier**

- Negative Feedback Examples

- Benefits of Negative Feedback

- Gain Stabilization

- Distortion Reduction

- Interference Rejection

- Cause/Effect Inversion

- Instability

- Summary


Sometimes we have an additional block at the input shown here as C .

We see that $E = CX - BY$ and, as before,


$$Y = AE$$

Eliminating E : $\frac{Y}{X} = \frac{CA}{1+AB} = \frac{C}{A^{-1}+B} \approx \frac{C}{B}$ provided $A^{-1} \ll B$.

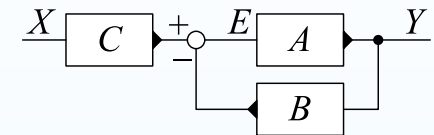$\frac{Y}{X}$ equals the forward gain, CA , divided by the loop gain plus one.



Inverting Amplifier

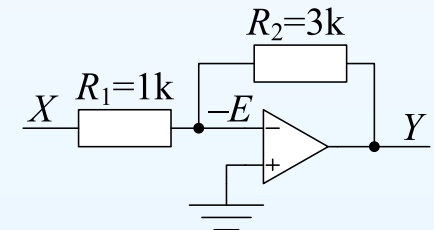

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- **Inverting Amplifier**
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Inverting Amplifier


Sometimes we have an additional block at the input shown here as C .

We see that $E = CX - BY$ and, as before,

$$Y = AE$$

Eliminating E : $\frac{Y}{X} = \frac{CA}{1+AB} = \frac{C}{A^{-1}+B} \approx \frac{C}{B}$ provided $A^{-1} \ll B$.

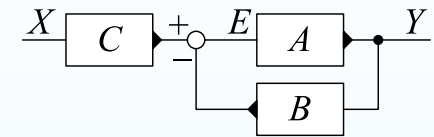$\frac{Y}{X}$ equals the forward gain, CA , divided by the loop gain plus one.




Inverting Amplifier

Error signal is $E \triangleq V_+ - V_-$

$$\text{Hence } V_+ = 0 \Rightarrow V_- = -E$$

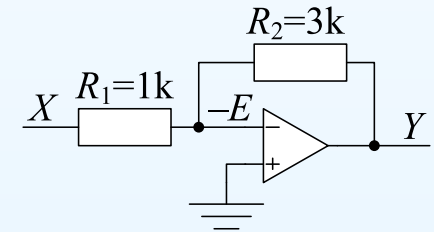Op-amp output is $Y = AE$ where $A \approx 10^5$ is the op-amp gain.



7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- **Inverting Amplifier**
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Inverting Amplifier


Sometimes we have an additional block at the input shown here as C .

We see that $E = CX - BY$ and, as before,

$$Y = AE$$

Eliminating E : $\frac{Y}{X} = \frac{CA}{1+AB} = \frac{C}{A^{-1}+B} \approx \frac{C}{B}$ provided $A^{-1} \ll B$.

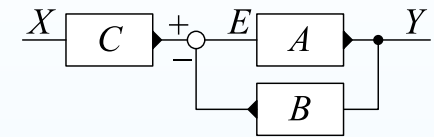$\frac{Y}{X}$ equals the forward gain, CA , divided by the loop gain plus one.




Inverting Amplifier

Error signal is $E \triangleq V_+ - V_-$

$$\text{Hence } V_+ = 0 \Rightarrow V_- = -E$$

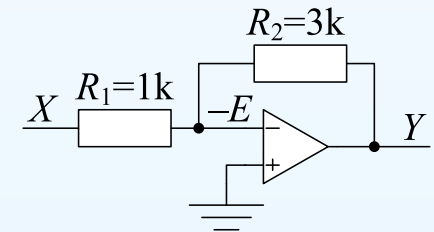Op-amp output is $Y = AE$ where $A \approx 10^5$ is the op-amp gain.



Use superposition, nodal analysis or weighted average formula to find an expression for $-E$ in terms of X and Y :

$$-E = \frac{\frac{1}{1}X + \frac{1}{3}Y}{\frac{1}{1} + \frac{1}{3}} = \frac{3}{4}X + \frac{1}{4}Y$$

Inverting Amplifier

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- **Inverting Amplifier**
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary


Sometimes we have an additional block at the input shown here as C .

We see that $E = CX - BY$ and, as before,

$$Y = AE$$

Eliminating E : $\frac{Y}{X} = \frac{CA}{1+AB} = \frac{C}{A^{-1}+B} \approx \frac{C}{B}$ provided $A^{-1} \ll B$.

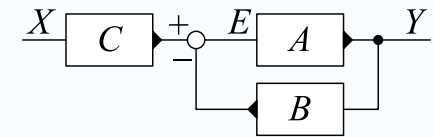$\frac{Y}{X}$ equals the forward gain, CA , divided by the loop gain plus one.



Inverting Amplifier


Error signal is $E \triangleq V_+ - V_-$

$$\text{Hence } V_+ = 0 \Rightarrow V_- = -E$$

Op-amp output is $Y = AE$ where $A \approx 10^5$ is the op-amp gain.

Use superposition, nodal analysis or weighted average formula to find an expression for $-E$ in terms of X and Y :
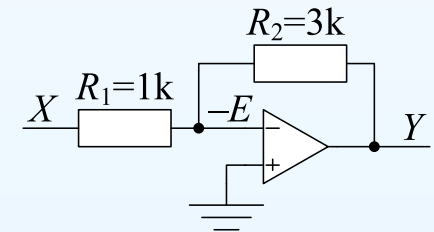
$$-E = \frac{\frac{1}{1}X + \frac{1}{3}Y}{\frac{1}{1} + \frac{1}{3}} = \frac{3}{4}X + \frac{1}{4}Y = -(CX - BY)$$



Inverting Amplifier

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- **Inverting Amplifier**
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary


Sometimes we have an additional block at the input shown here as C .

We see that $E = CX - BY$ and, as before,

$$Y = AE$$

Eliminating E : $\frac{Y}{X} = \frac{CA}{1+AB} = \frac{C}{A^{-1}+B} \approx \frac{C}{B}$ provided $A^{-1} \ll B$.

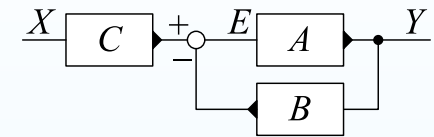$\frac{Y}{X}$ equals the forward gain, CA , divided by the loop gain plus one.



Inverting Amplifier

Error signal is $E \triangleq V_+ - V_-$


$$\text{Hence } V_+ = 0 \Rightarrow V_- = -E$$

Op-amp output is $Y = AE$ where $A \approx 10^5$ is the op-amp gain.

Use superposition, nodal analysis or weighted average formula to find an expression for $-E$ in terms of X and Y :

$$-E = \frac{\frac{1}{1}X + \frac{1}{3}Y}{\frac{1}{1} + \frac{1}{3}} = \frac{3}{4}X + \frac{1}{4}Y = -(CX - BY)$$

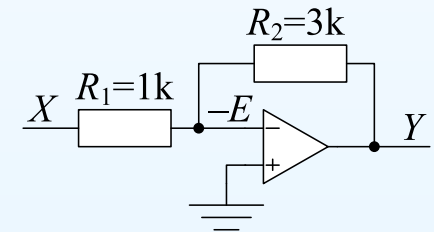Hence $C = -\frac{3}{4}$ and $B = +\frac{1}{4}$ and $\frac{Y}{X} \approx \frac{C}{B} = -3$



Negative Feedback Examples

7: Negative Feedback is Wonderful


- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Central Heating:

X : Desired temperature

Y : Actual room temperature

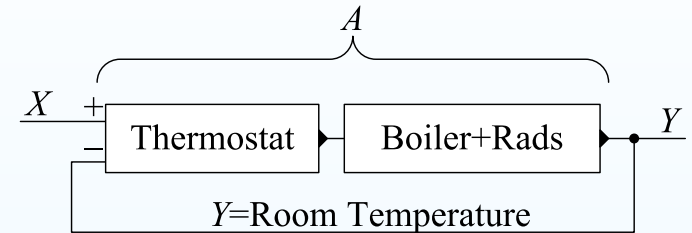A : Rather complicated system of boiler and radiators



Negative Feedback Examples

7: Negative Feedback is Wonderful


- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Central Heating:

X : Desired temperature

Y : Actual room temperature

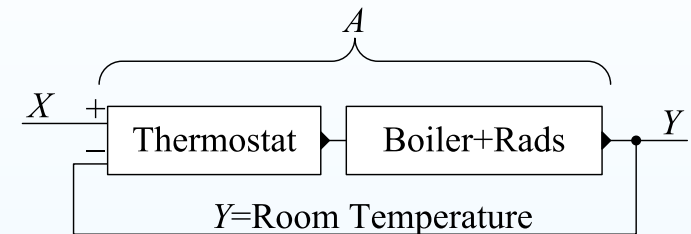A : Rather complicated system of boiler and radiators




Steam Engine Governor:

X : Desired Speed

Y : Actual Speed

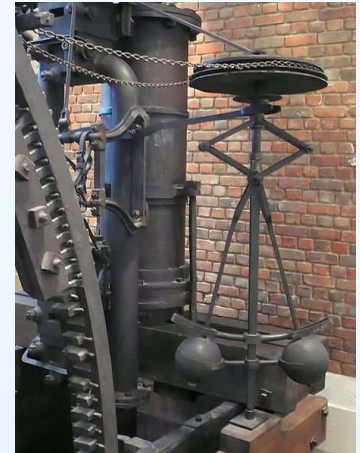A : Rotational speed causes weights to fly apart (centrifugal force) which adjusts the steam supply via a throttle valve.



Negative Feedback Examples

7: Negative Feedback is Wonderful


- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Central Heating:

X : Desired temperature

Y : Actual room temperature

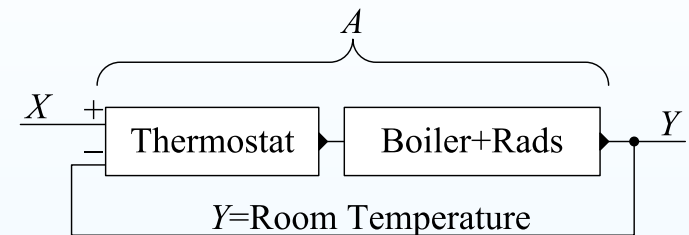A : Rather complicated system of boiler and radiators




Steam Engine Governor:

X : Desired Speed

Y : Actual Speed

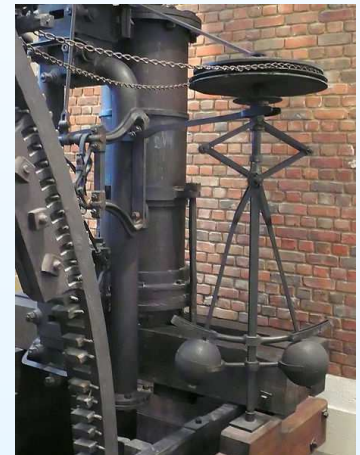A : Rotational speed causes weights to fly apart (centrifugal force) which adjusts the steam supply via a throttle valve.



Many Other Examples:

Economics: Demand \uparrow \Rightarrow Price \uparrow \Rightarrow Supply \uparrow \Rightarrow Supply=Demand

Negative Feedback Examples

7: Negative Feedback is Wonderful


- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Central Heating:

X : Desired temperature

Y : Actual room temperature

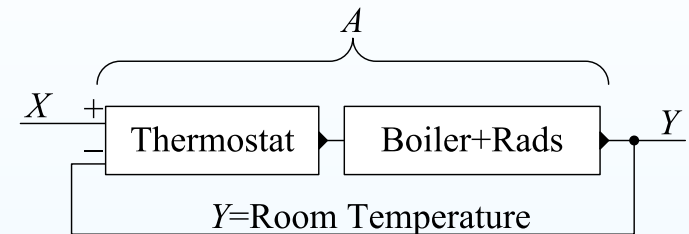A : Rather complicated system of boiler and radiators




Steam Engine Governor:

X : Desired Speed

Y : Actual Speed

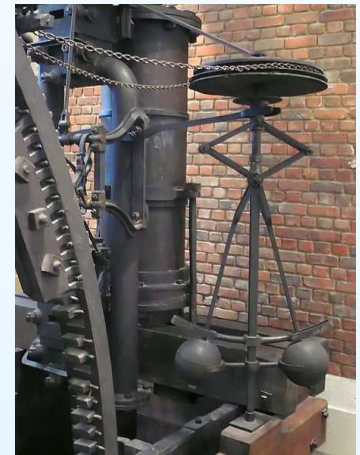A : Rotational speed causes weights to fly apart (centrifugal force) which adjusts the steam supply via a throttle valve.



Many Other Examples:

Economics: Demand \uparrow \Rightarrow Price \uparrow \Rightarrow Supply \uparrow \Rightarrow Supply=Demand

Biology: More rabbits \Rightarrow Not enough food \Rightarrow Less rabbits \Rightarrow Enough food

Benefits of Negative Feedback

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- **Benefits of Negative Feedback**

- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

1) Gain Stabilization

The gain of a feedback system is almost entirely determined by the feedback path and not by the gain of the amplification path. This means that you can get predictable gains even when the gain of the amplification path is unknown or time-varying.

Benefits of Negative Feedback

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- **Benefits of Negative Feedback**

- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

1) Gain Stabilization

The gain of a feedback system is almost entirely determined by the feedback path and not by the gain of the amplification path. This means that you can get predictable gains even when the gain of the amplification path is unknown or time-varying.

2) Distortion Reduction

High power amplifiers are often non-linear, e.g. their gain decreases at high signal amplitudes. Since the gain of a feedback system does not depend much on the gain of the amplification path, the non-linearity has little effect.

Benefits of Negative Feedback

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- **Benefits of Negative Feedback**

- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

1) Gain Stabilization

The gain of a feedback system is almost entirely determined by the feedback path and not by the gain of the amplification path. This means that you can get predictable gains even when the gain of the amplification path is unknown or time-varying.

2) Distortion Reduction

High power amplifiers are often non-linear, e.g. their gain decreases at high signal amplitudes. Since the gain of a feedback system does not depend much on the gain of the amplification path, the non-linearity has little effect.

3) Interference Rejection

External disturbances have little effect on the output of a feedback system because the feedback adjusts to compensate for them.

Gain Stabilization

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback


Examples

- Benefits of Negative Feedback

- **Gain Stabilization**

- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary
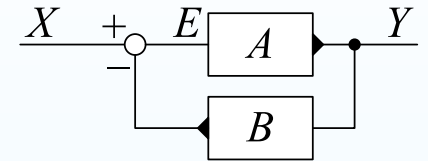
$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB}$$



Gain Stabilization

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback


Examples

- Benefits of Negative Feedback

- **Gain Stabilization**

- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary
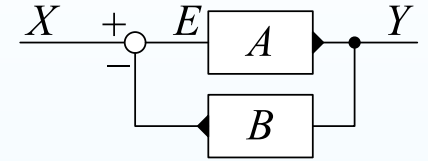
$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B}$$




Gain Stabilization

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- **Gain Stabilization**
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B}$$

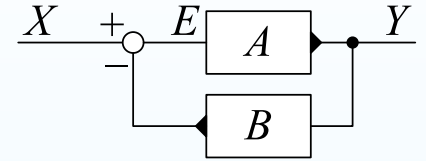If A is very large then $\frac{Y}{X} \approx \frac{1}{B}$ and the precise value of A makes no difference.



Gain Stabilization


7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- **Gain Stabilization**
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B}$$

If A is very large then $\frac{Y}{X} \approx \frac{1}{B}$ and the precise value of A makes no difference.

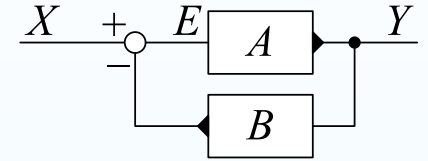“very large” means $A^{-1} \ll B \Leftrightarrow A \gg \frac{1}{B}$.



Gain Stabilization


7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- **Gain Stabilization**
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B}$$

If A is very large then $\frac{Y}{X} \approx \frac{1}{B}$ and the precise value of A makes no difference.

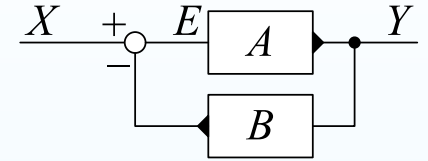“very large” means $A^{-1} \ll B \Leftrightarrow A \gg \frac{1}{B}$. So as long as A is much larger than the desired gain, its actual value does not matter.



Gain Stabilization

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- Benefits of Negative Feedback

- **Gain Stabilization**


- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B}$$

If A is very large then $\frac{Y}{X} \approx \frac{1}{B}$ and the precise value of A makes no difference.

“very large” means $A^{-1} \ll B \Leftrightarrow A \gg \frac{1}{B}$. So as long as A is much larger than the desired gain, its actual value does not matter.

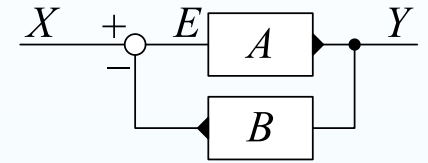For an op amp $A \approx 10^5$ at low frequencies but less at high frequencies.



Gain Stabilization

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- **Gain Stabilization**
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B}$$



If A is very large then $\frac{Y}{X} \approx \frac{1}{B}$ and the precise value of A makes no difference.

“very large” means $A^{-1} \ll B \Leftrightarrow A \gg \frac{1}{B}$. So as long as A is much larger than the desired gain, its actual value does not matter.

For an op amp $A \approx 10^5$ at low frequencies but less at high frequencies.

Motor Speed Control:

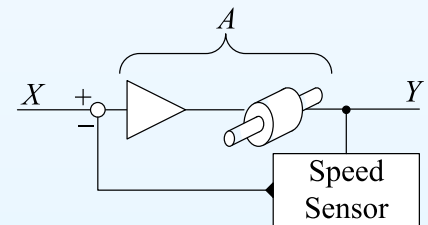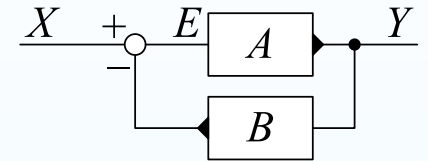A is the “gain” of the amplifier and motor (units = rotation speed per volt = $\text{rad}\cdot\text{s}^{-1}\text{V}^{-1}$).



Gain Stabilization

7: Negative Feedback is Wonderful


- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- **Gain Stabilization**
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B}$$

If A is very large then $\frac{Y}{X} \approx \frac{1}{B}$ and the precise value of A makes no difference.

“very large” means $A^{-1} \ll B \Leftrightarrow A \gg \frac{1}{B}$. So as long as A is much larger than the desired gain, its actual value does not matter.

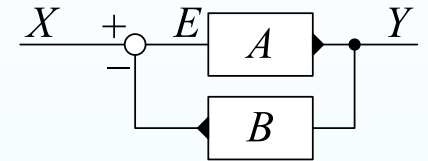For an op amp $A \approx 10^5$ at low frequencies but less at high frequencies.




Motor Speed Control:

A is the “gain” of the amplifier and motor
(units = rotation speed per volt = $\text{rad}\cdot\text{s}^{-1}\text{V}^{-1}$).

A cannot be precisely known: it depends on mechanical load and friction.

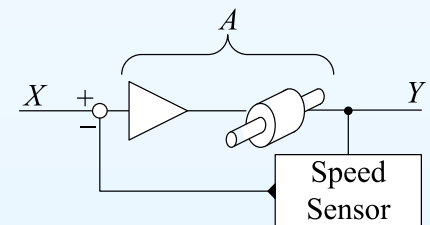However this is OK so long as it is large enough.



Gain Stabilization

7: Negative Feedback is Wonderful


- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- **Gain Stabilization**
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B}$$

If A is very large then $\frac{Y}{X} \approx \frac{1}{B}$ and the precise value of A makes no difference.

“very large” means $A^{-1} \ll B \Leftrightarrow A \gg \frac{1}{B}$. So as long as A is much larger than the desired gain, its actual value does not matter.

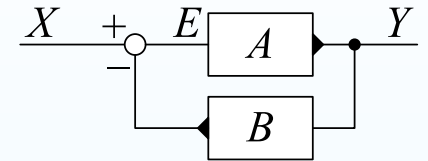For an op amp $A \approx 10^5$ at low frequencies but less at high frequencies.





Motor Speed Control:

A is the “gain” of the amplifier and motor (units = rotation speed per volt = $\text{rad}\cdot\text{s}^{-1}\text{V}^{-1}$).

A cannot be precisely known: it depends on mechanical load and friction.

However this is OK so long as it is large enough.

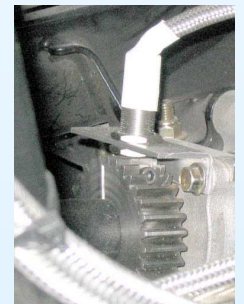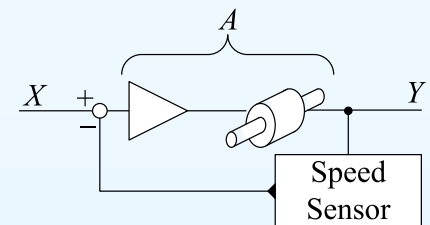We can sense the motor speed using gear-teeth and a magnetic (Hall effect) sensor together with a circuit that converts frequency to voltage.




Distortion Reduction

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- **Distortion Reduction** +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

If A includes a high-power amplifier and/or a mechanical system (e.g. a motor) it is almost always non-linear.

$$y = 15x - 2x^3$$

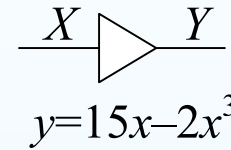



Distortion Reduction

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- **Distortion Reduction** +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

If A includes a high-power amplifier and/or a mechanical system (e.g. a motor) it is almost always non-linear.

$y = 15x - 2x^3$: gain decreases at high $|x|$

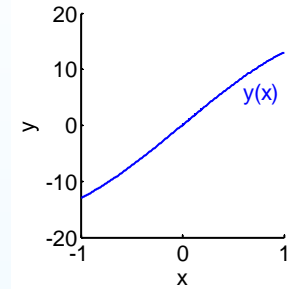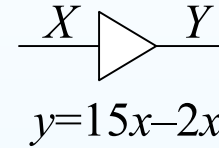

Distortion Reduction



7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- **Distortion Reduction** +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

If A includes a high-power amplifier and/or a mechanical system (e.g. a motor) it is almost always non-linear.

$y = 15x - 2x^3$: gain decreases at high $|x|$
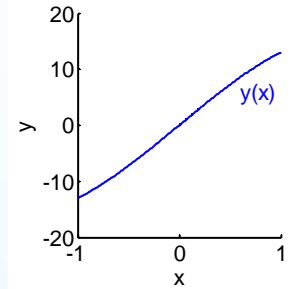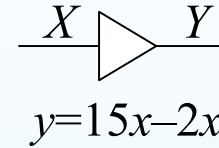
$$x = \sin t \Rightarrow y = 15 \sin t - 2 \sin^3 t$$



Distortion Reduction



7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- **Distortion Reduction** +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

If A includes a high-power amplifier and/or a mechanical system (e.g. a motor) it is almost always non-linear.

$y = 15x - 2x^3$: gain decreases at high $|x|$
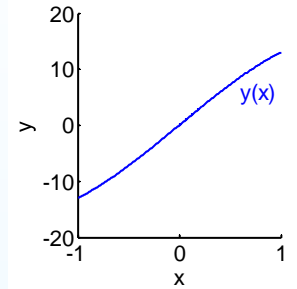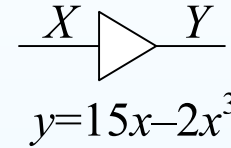
$$x = \sin t \Rightarrow y = 15 \sin t - 2 \sin^3 t$$
$$\Rightarrow y = 13.5 \sin t + 0.5 \sin 3t$$



Distortion Reduction

7: Negative Feedback is Wonderful




- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- **Distortion Reduction** +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

If A includes a high-power amplifier and/or a mechanical system (e.g. a motor) it is almost always non-linear.

$$y = 15x - 2x^3: \text{ gain decreases at high } |x|$$

$$x = \sin t \Rightarrow y = 15 \sin t - 2 \sin^3 t \\ \Rightarrow y = 13.5 \sin t + 0.5 \sin 3t$$

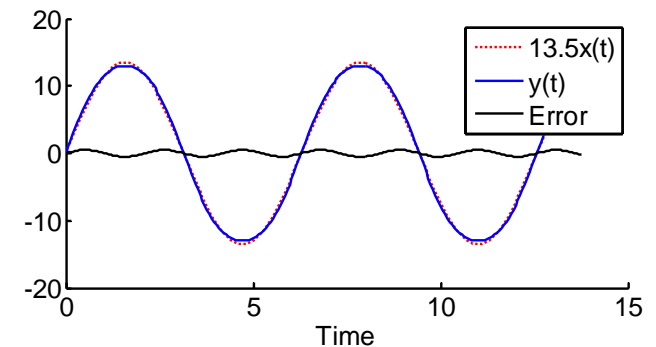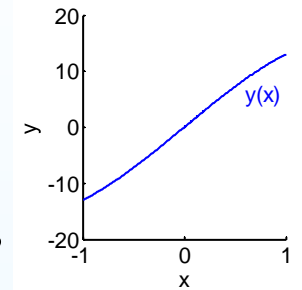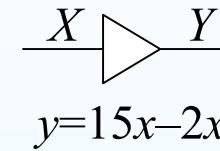The gain is only 13.5 instead of 15 and *harmonic distortion* is added at a multiple of the original frequency.



Distortion Reduction

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- **Distortion Reduction** +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary




If A includes a high-power amplifier and/or a mechanical system (e.g. a motor) it is almost always non-linear.

$y = 15x - 2x^3$: gain decreases at high $|x|$

$$x = \sin t \Rightarrow y = 15 \sin t - 2 \sin^3 t$$
$$\Rightarrow y = 13.5 \sin t + 0.5 \sin 3t$$

The gain is only 13.5 instead of 15 and *harmonic distortion* is added at a multiple of the original frequency.

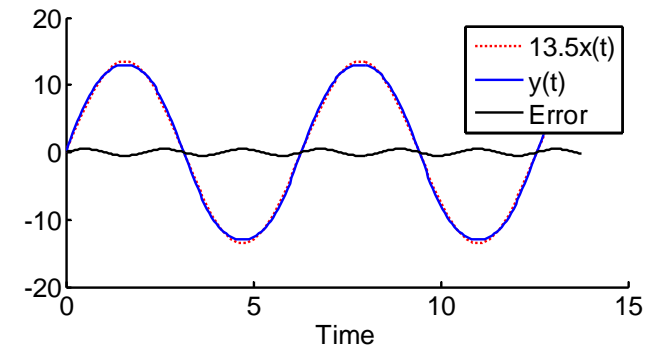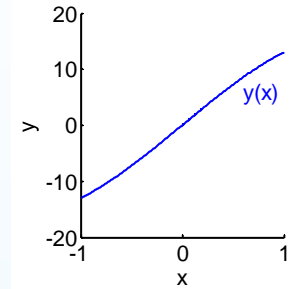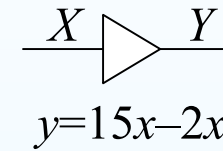The total harmonic distortion (THD) is equal to $\frac{0.5^2}{13.5^2} = 0.14\%$.



Distortion Reduction

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- **Distortion Reduction**
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

If A includes a high-power amplifier and/or a mechanical system (e.g. a motor) it is almost always non-linear.

$$y = 15x - 2x^3: \text{ gain decreases at high } |x|$$

$$x = \sin t \Rightarrow y = 15 \sin t - 2 \sin^3 t$$




$$\Rightarrow y = 13.5 \sin t + 0.5 \sin 3t$$

The gain is only 13.5 instead of 15 and *harmonic distortion* is added at a multiple of the original frequency.

The total harmonic distortion (THD) is equal to $\frac{0.5^2}{13.5^2} = 0.14\%$.

Use feedback to reduce distortion

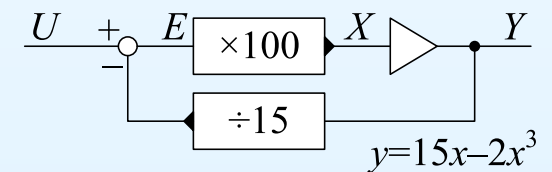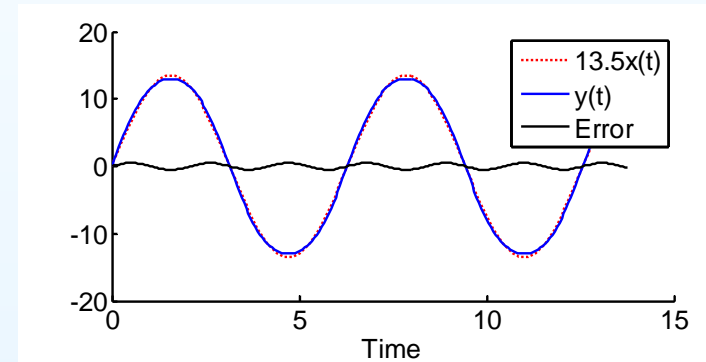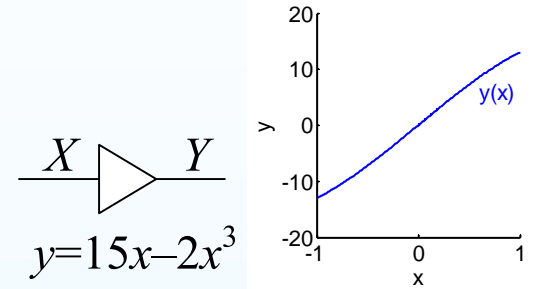Put in feedback loop with $\times 100$ gain,
 $A = \frac{Y}{E} = 100 \frac{Y}{X}$ and $B = \frac{1}{15}$



Distortion Reduction

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- **Distortion Reduction** +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

If A includes a high-power amplifier and/or a mechanical system (e.g. a motor) it is almost always non-linear.

$$y = 15x - 2x^3: \text{ gain decreases at high } |x|$$

$$x = \sin t \Rightarrow y = 15 \sin t - 2 \sin^3 t$$

$$\Rightarrow y = 13.5 \sin t + 0.5 \sin 3t$$




The gain is only 13.5 instead of 15 and *harmonic distortion* is added at a multiple of the original frequency.

The total harmonic distortion (THD) is equal to $\frac{0.5^2}{13.5^2} = 0.14\%$.

Use feedback to reduce distortion

Put in feedback loop with $\times 100$ gain,
 $A = \frac{Y}{E} = 100 \frac{Y}{X}$ and $B = \frac{1}{15}$

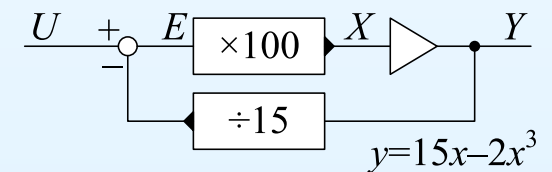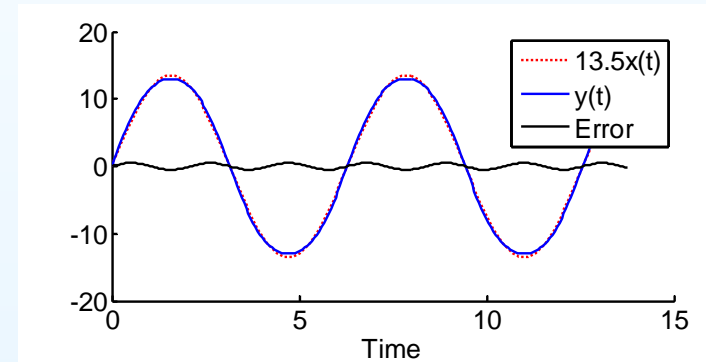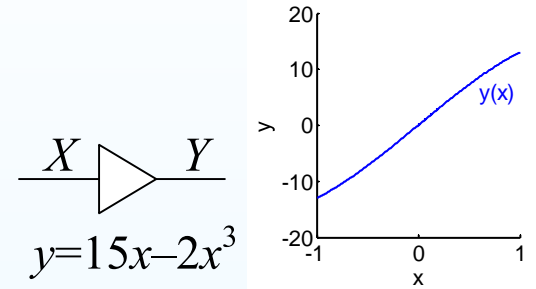Even though A depends on the signal amplitude, the gain is $\frac{Y}{U} \approx \frac{1}{B} = 15$.



Distortion Reduction

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- **Distortion Reduction**
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

If A includes a high-power amplifier and/or a mechanical system (e.g. a motor) it is almost always non-linear.

$$y = 15x - 2x^3: \text{ gain decreases at high } |x|$$

$$x = \sin t \Rightarrow y = 15 \sin t - 2 \sin^3 t$$

$$\Rightarrow y = 13.5 \sin t + 0.5 \sin 3t$$




The gain is only 13.5 instead of 15 and *harmonic distortion* is added at a multiple of the original frequency.

The total harmonic distortion (THD) is equal to $\frac{0.5^2}{13.5^2} = 0.14\%$.

Use feedback to reduce distortion

Put in feedback loop with $\times 100$ gain,
 $A = \frac{Y}{E} = 100 \frac{Y}{X}$ and $B = \frac{1}{15}$

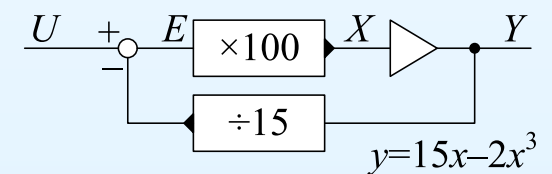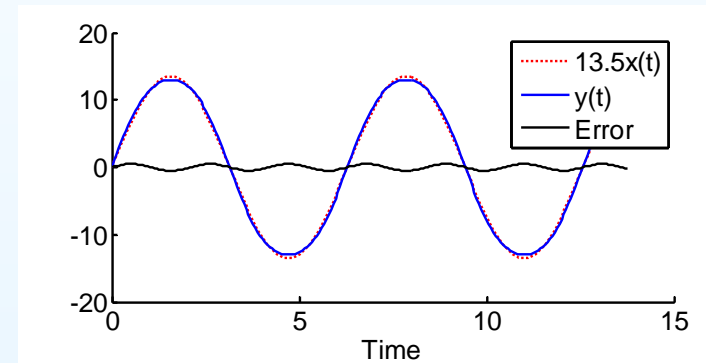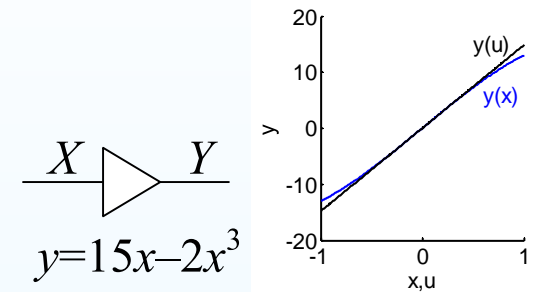Even though A depends on the signal amplitude, the gain is $\frac{Y}{U} \approx \frac{1}{B} = 15$.



Interference Rejection


7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

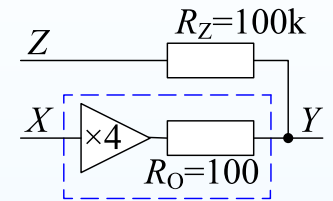Examples

- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

The amplifier output, Y , is affected by interference, Z .



Interference Rejection


7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- **Interference Rejection**
- Cause/Effect Inversion
- Instability
- Summary

The amplifier output, Y , is affected by interference, Z .

$Y =$ average of $4X$ and Z weighted by conductances:
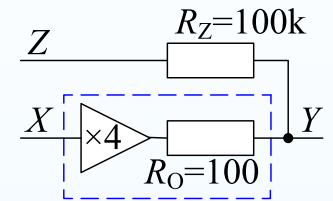
$$Y = \frac{\frac{1}{R_O} 4X + \frac{1}{R_Z} Z}{\frac{1}{R_O} + \frac{1}{R_Z}} = 3.996X + \frac{1}{1001} Z$$



Interference Rejection

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- **Interference Rejection**
- Cause/Effect Inversion
- Instability
- Summary


The amplifier output, Y , is affected by interference, Z .

Y = average of $4X$ and Z weighted by conductances:

$$Y = \frac{\frac{1}{R_O} 4X + \frac{1}{R_Z} Z}{\frac{1}{R_O} + \frac{1}{R_Z}} = 3.996X + \frac{1}{1001} Z$$

Z is often much bigger than X (e.g. mains @ 230V).

R_O is amplifier *output resistance*.

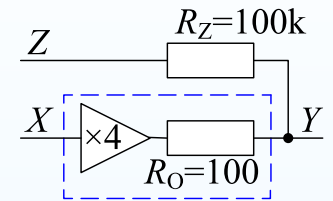

Interference Rejection

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

The amplifier output, Y , is affected by interference, Z .

$Y =$ average of $4X$ and Z weighted by conductances:



$$Y = \frac{\frac{1}{R_O} 4X + \frac{1}{R_Z} Z}{\frac{1}{R_O} + \frac{1}{R_Z}} = 3.996X + \frac{1}{1001} Z$$

Z is often much bigger than X (e.g. mains @ 230V).

R_O is amplifier *output resistance*.

Use feedback to reject interference
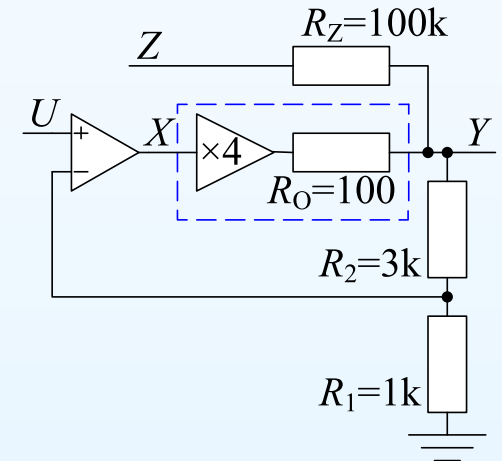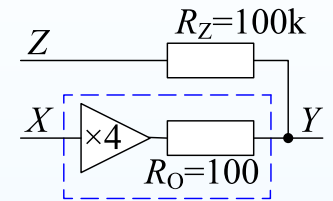
$$\text{Opamp gain} = A \approx 10^5 \Rightarrow X = A \left(U - \frac{Y}{4} \right)$$



Interference Rejection

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

The amplifier output, Y , is affected by interference, Z .

$Y =$ average of $4X$ and Z weighted by conductances:

$$Y = \frac{\frac{1}{R_O} 4X + \frac{1}{R_Z} Z}{\frac{1}{R_O} + \frac{1}{R_Z}} = 3.996X + \frac{1}{1001} Z$$



Z is often much bigger than X (e.g. mains @ 230V).

R_O is amplifier *output resistance*.

Use feedback to reject interference

Opamp gain = $A \approx 10^5 \Rightarrow X = A \left(U - \frac{Y}{4} \right)$
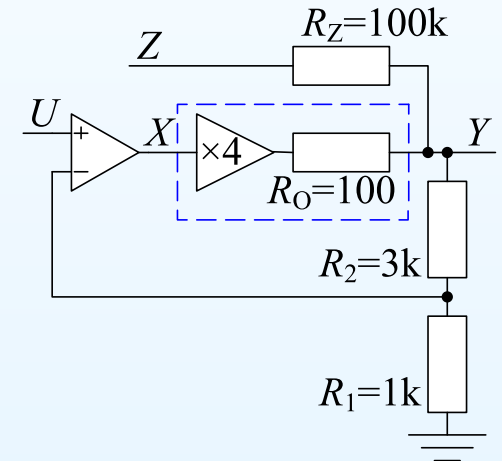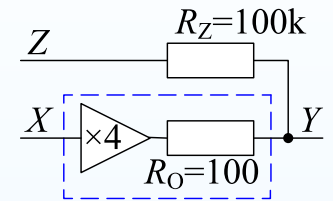
$$Y = \frac{\frac{1}{R_O} 4X + \frac{1}{R_Z} Z + \frac{1}{4k} 0}{\frac{1}{R_O} + \frac{1}{R_Z} + \frac{1}{4k}} = 3.899X + \frac{1}{1026} Z$$



Interference Rejection

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary


The amplifier output, Y , is affected by interference, Z .

$Y =$ average of $4X$ and Z weighted by conductances:

$$Y = \frac{\frac{1}{R_O} 4X + \frac{1}{R_Z} Z}{\frac{1}{R_O} + \frac{1}{R_Z}} = 3.996X + \frac{1}{1001} Z$$

Z is often much bigger than X (e.g. mains @ 230V).

R_O is amplifier *output resistance*.

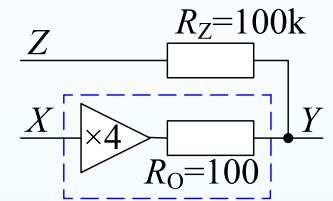


Use feedback to reject interference

Opamp gain = $A \approx 10^5 \Rightarrow X = A \left(U - \frac{Y}{4} \right)$

$$Y = \frac{\frac{1}{R_O} 4X + \frac{1}{R_Z} Z + \frac{1}{4k} 0}{\frac{1}{R_O} + \frac{1}{R_Z} + \frac{1}{4k}} = 3.899X + \frac{1}{1026} Z$$

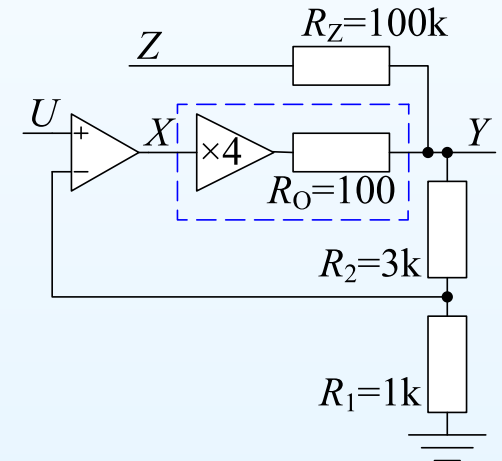Eliminate X : $Y = 4U + \frac{1}{10001026} Z$



Interference Rejection

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- **Interference Rejection**
- Cause/Effect Inversion
- Instability
- Summary


The amplifier output, Y , is affected by interference, Z .

$Y =$ average of $4X$ and Z weighted by conductances:

$$Y = \frac{\frac{1}{R_O} 4X + \frac{1}{R_Z} Z}{\frac{1}{R_O} + \frac{1}{R_Z}} = 3.996X + \frac{1}{1001} Z$$

Z is often much bigger than X (e.g. mains @ 230V).

R_O is amplifier *output resistance*.

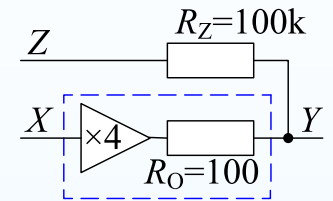


Use feedback to reject interference

Opamp gain = $A \approx 10^5 \Rightarrow X = A \left(U - \frac{Y}{4} \right)$

$$Y = \frac{\frac{1}{R_O} 4X + \frac{1}{R_Z} Z + \frac{1}{4k} 0}{\frac{1}{R_O} + \frac{1}{R_Z} + \frac{1}{4k}} = 3.899X + \frac{1}{1026} Z$$

Eliminate X : $Y = 4U + \frac{1}{100001026} Z$

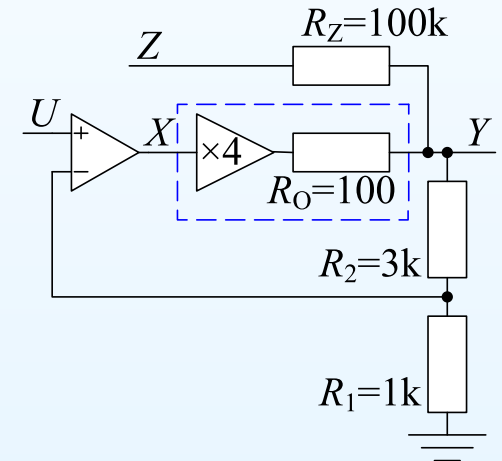Interference reduced by the loop gain $\approx 10^5$.



Interference Rejection


7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- **Interference Rejection**
- Cause/Effect Inversion
- Instability
- Summary

The amplifier output, Y , is affected by interference, Z .
 $Y =$ average of $4X$ and Z weighted by conductances:

$$Y = \frac{\frac{1}{R_O} 4X + \frac{1}{R_Z} Z}{\frac{1}{R_O} + \frac{1}{R_Z}} = 3.996X + \frac{1}{1001} Z$$

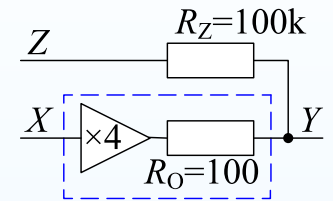Z is often much bigger than X (e.g. mains @ 230V).
 R_O is amplifier *output resistance*.




Use feedback to reject interference

Opamp gain = $A \approx 10^5 \Rightarrow X = A(U - \frac{Y}{4})$

$$Y = \frac{\frac{1}{R_O} 4X + \frac{1}{R_Z} Z + \frac{1}{4k} 0}{\frac{1}{R_O} + \frac{1}{R_Z} + \frac{1}{4k}} = 3.899X + \frac{1}{1026} Z$$


Eliminate X : $Y = 4U + \frac{1}{100001026} Z$

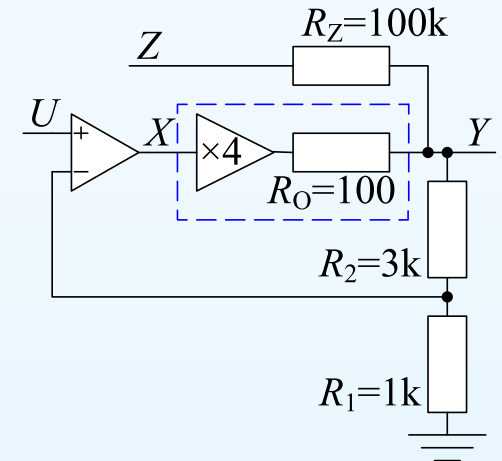Interference reduced by the loop gain $\approx 10^5$.



“Interference” includes any external influence that may affect the output.

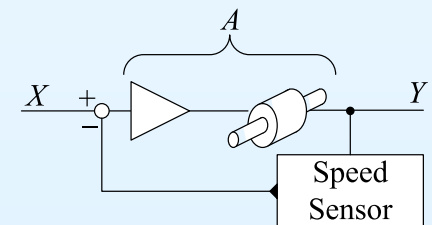E.g. the mechanical load changing on a motor or an opened window in a heating system.




Cause/Effect Inversion

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B} \approx \frac{1}{B}$$

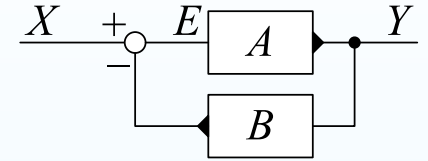If multiplying by B is easier than dividing by B , use feedback to multiply by $\frac{1}{B}$.



7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary



Cause/Effect Inversion

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B} \approx \frac{1}{B}$$

If multiplying by B is easier than dividing by B , use feedback to multiply by $\frac{1}{B}$.

Division Circuit

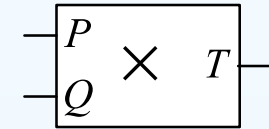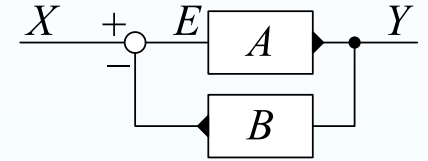Multiplier circuit is quite easy to make: $T = P \times Q$



7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Cause/Effect Inversion



$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B} \approx \frac{1}{B}$$

If multiplying by B is easier than dividing by B , use feedback to multiply by $\frac{1}{B}$.

Division Circuit

Multiplier circuit is quite easy to make: $T = P \times Q$

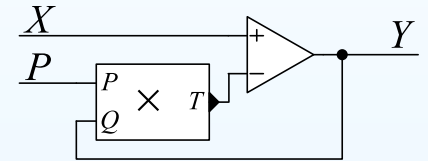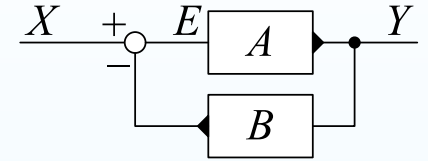Use in feedback loop to give $Y = \frac{X}{P}$



7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Cause/Effect Inversion

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B} \approx \frac{1}{B}$$



If multiplying by B is easier than dividing by B , use feedback to multiply by $\frac{1}{B}$.

Division Circuit

Multiplier circuit is quite easy to make: $T = P \times Q$

Use in feedback loop to give $Y = \frac{X}{P}$

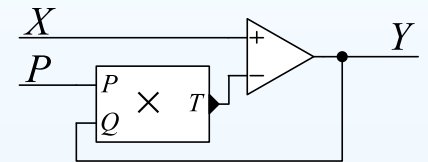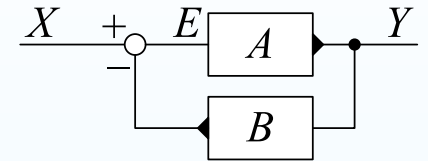P must be +ve to ensure negative feedback.




Cause/Effect Inversion

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Gain is $\frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B} \approx \frac{1}{B}$

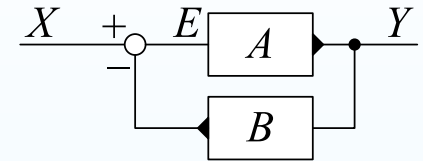
If multiplying by B is easier than dividing by B , use feedback to multiply by $\frac{1}{B}$.



Division Circuit


Multiplier circuit is quite easy to make: $T = P \times Q$

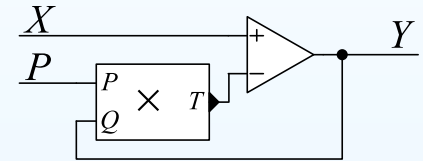Use in feedback loop to give $Y = \frac{X}{P}$
 P must be +ve to ensure negative feedback.



Phase Lock Loop

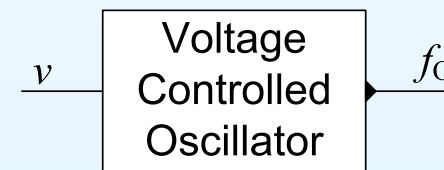Easy to make a voltage controlled oscillator with $f_o = k \times v$



Cause/Effect Inversion

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B} \approx \frac{1}{B}$$

If multiplying by B is easier than dividing by B , use feedback to multiply by $\frac{1}{B}$.

Division Circuit

Multiplier circuit is quite easy to make: $T = P \times Q$




Use in feedback loop to give $Y = \frac{X}{P}$

P must be +ve to ensure negative feedback.

Phase Lock Loop

Easy to make a voltage controlled oscillator with $f_O = k \times v$

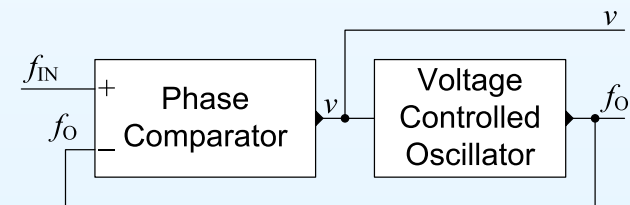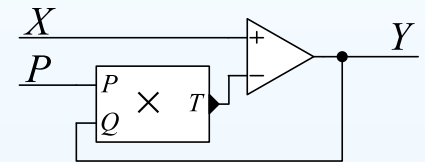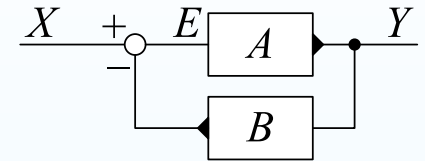Phase comparator output is $v \propto \int (f_{IN} - f_O) dt$ so v increases whenever $f_O < f_{IN}$ and decreases when $f_O > f_{IN}$.




Cause/Effect Inversion

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B} \approx \frac{1}{B}$$

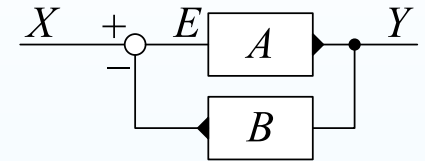If multiplying by B is easier than dividing by B , use feedback to multiply by $\frac{1}{B}$.




Division Circuit

Multiplier circuit is quite easy to make: $T = P \times Q$


Use in feedback loop to give $Y = \frac{X}{P}$

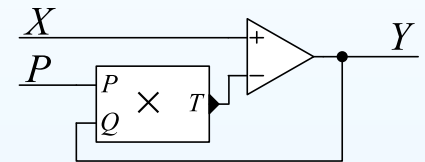P must be +ve to ensure negative feedback.



Phase Lock Loop

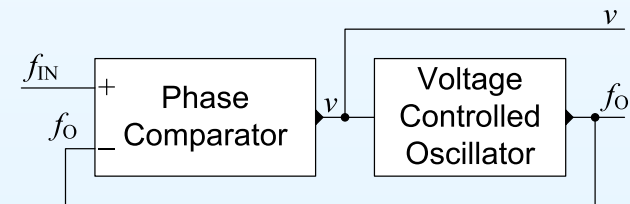Easy to make a voltage controlled oscillator with $f_O = k \times v$



Phase comparator output is $v \propto \int (f_{IN} - f_O) dt$ so v increases whenever $f_O < f_{IN}$ and decreases when $f_O > f_{IN}$. When v reaches equilibrium, we must have $f_O = f_{IN}$ so $v = \frac{1}{k} \times f_{IN}$.


Cause/Effect Inversion

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Gain is $\frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B} \approx \frac{1}{B}$

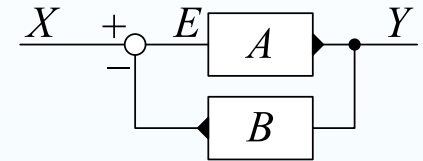
If multiplying by B is easier than dividing by B , use feedback to multiply by $\frac{1}{B}$.



Division Circuit


Multiplier circuit is quite easy to make: $T = P \times Q$

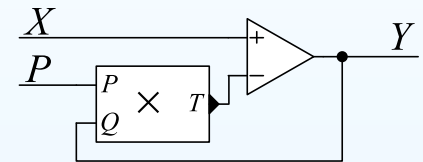Use in feedback loop to give $Y = \frac{X}{P}$
 P must be +ve to ensure negative feedback.



Phase Lock Loop

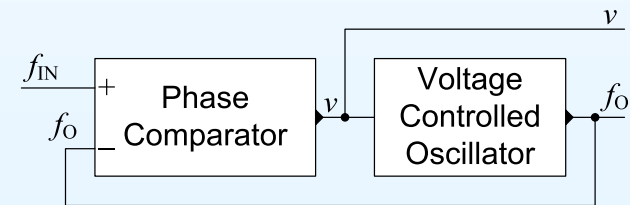Easy to make a voltage controlled oscillator with $f_O = k \times v$



Phase comparator output is $v \propto \int (f_{IN} - f_O) dt$ so v increases whenever $f_O < f_{IN}$ and decreases when $f_O > f_{IN}$. When v reaches equilibrium, we must have $f_O = f_{IN}$ so $v = \frac{1}{k} \times f_{IN}$.

We have generated a voltage proportional to the input frequency.


Cause/Effect Inversion

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB} = \frac{1}{A^{-1}+B} \approx \frac{1}{B}$$

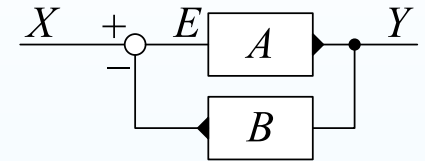If multiplying by B is easier than dividing by B , use feedback to multiply by $\frac{1}{B}$.




Division Circuit

Multiplier circuit is quite easy to make: $T = P \times Q$


Use in feedback loop to give $Y = \frac{X}{P}$

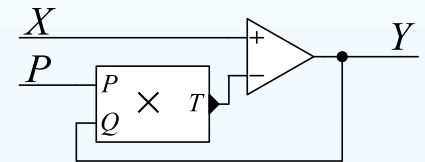P must be +ve to ensure negative feedback.



Phase Lock Loop

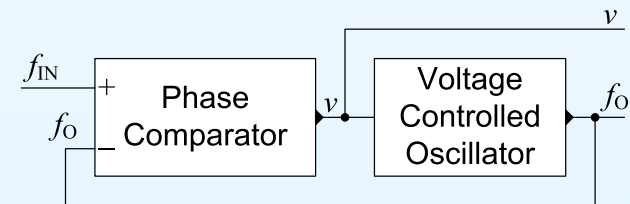Easy to make a voltage controlled oscillator with $f_O = k \times v$



Phase comparator output is $v \propto \int (f_{IN} - f_O) dt$ so v increases whenever $f_O < f_{IN}$ and decreases when $f_O > f_{IN}$. When v reaches equilibrium, we must have $f_O = f_{IN}$ so $v = \frac{1}{k} \times f_{IN}$.

We have generated a voltage proportional to the input frequency.

Used in FM radios and in many other circuits.


Instability

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
 - Benefits of Negative Feedback
 - Gain Stabilization
 - Distortion Reduction +
 - Interference Rejection
 - Cause/Effect Inversion
 - **Instability**
 - Summary

The biggest problem of feedback systems is the possibility of instability.
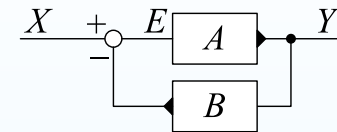
$$\text{Gain is } \frac{Y}{X} = \frac{A}{1+AB}$$



Instability


7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- **Instability**
- Summary

The biggest problem of feedback systems is the possibility of instability.

Gain is $\frac{Y}{X} = \frac{A}{1+AB}$. We have four cases:
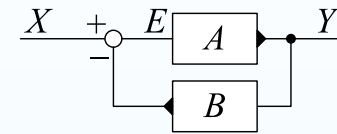
$$AB > 0 \quad \text{Normal: } \frac{Y}{X} \approx \frac{1}{B} < A$$



Instability


7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- **Instability**
- Summary

The biggest problem of feedback systems is the possibility of instability.

Gain is $\frac{Y}{X} = \frac{A}{1+AB}$. We have four cases:
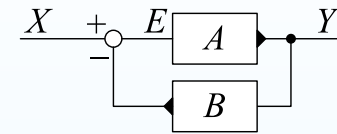
$$\begin{array}{ll} AB > 0 & \text{Normal: } \frac{Y}{X} \approx \frac{1}{B} < A \\ -1 < AB < 0 & \text{Increased Gain: } \frac{Y}{X} > A \end{array}$$



Instability

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion


● **Instability**

● Summary

The biggest problem of feedback systems is the possibility of instability.

Gain is $\frac{Y}{X} = \frac{A}{1+AB}$. We have four cases:
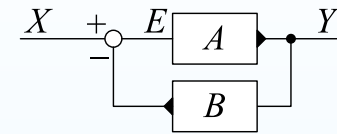
$$\begin{array}{ll} AB > 0 & \text{Normal: } \frac{Y}{X} \approx \frac{1}{B} < A \\ -1 < AB < 0 & \text{Increased Gain: } \frac{Y}{X} > A \\ AB = -1 & \frac{Y}{X} = \infty \end{array}$$



Instability

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion

● **Instability**


● Summary

The biggest problem of feedback systems is the possibility of instability.

Gain is $\frac{Y}{X} = \frac{A}{1+AB}$. We have four cases:

$AB > 0$	Normal: $\frac{Y}{X} \approx \frac{1}{B} < A$
$-1 < AB < 0$	Increased Gain: $\frac{Y}{X} > A$
$AB = -1$	$\frac{Y}{X} = \infty$

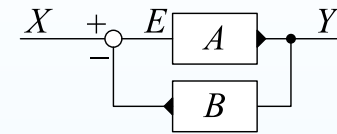$AB < -1$ Usually saturates or oscillates if $AB > 0$ at DC



Instability

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion

- **Instability**



- Summary

The biggest problem of feedback systems is the possibility of instability.

Gain is $\frac{Y}{X} = \frac{A}{1+AB}$. We have four cases:

$AB > 0$	Normal: $\frac{Y}{X} \approx \frac{1}{B} < A$
$-1 < AB < 0$	Increased Gain: $\frac{Y}{X} > A$
$AB = -1$	$\frac{Y}{X} = \infty$

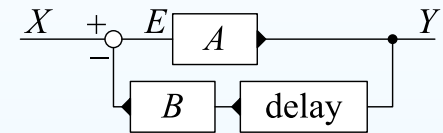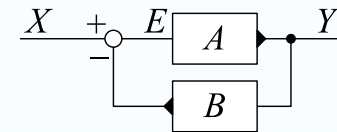$AB < -1$ Usually saturates or oscillates if $AB > 0$ at DC



Delays are Death

For a sine wave, a delay anywhere within the loop of half a period (e.g. 0.5 ms for 1 kHz) is the same as multiplying by -1 .

Instability

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion

- **Instability**



- Summary

The biggest problem of feedback systems is the possibility of instability.

Gain is $\frac{Y}{X} = \frac{A}{1+AB}$. We have four cases:

$AB > 0$	Normal: $\frac{Y}{X} \approx \frac{1}{B} < A$
$-1 < AB < 0$	Increased Gain: $\frac{Y}{X} > A$
$AB = -1$	$\frac{Y}{X} = \infty$

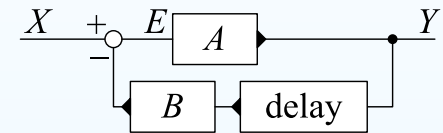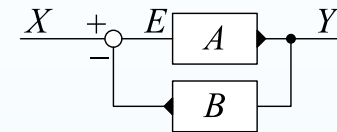$AB < -1$ Usually saturates or oscillates if $AB > 0$ at DC



Delays are Death

For a sine wave, a delay anywhere within the loop of half a period (e.g. 0.5 ms for 1 kHz) is the same as multiplying by -1 . At this frequency the loop gain, AB , is large and negative so the system becomes unstable and oscillates.

Instability



7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction
- Interference Rejection
- Cause/Effect Inversion
- **Instability**
- Summary

The biggest problem of feedback systems is the possibility of instability.

Gain is $\frac{Y}{X} = \frac{A}{1+AB}$. We have four cases:


$AB > 0$	Normal: $\frac{Y}{X} \approx \frac{1}{B} < A$
$-1 < AB < 0$	Increased Gain: $\frac{Y}{X} > A$
$AB = -1$	$\frac{Y}{X} = \infty$
$AB < -1$	Usually saturates or oscillates if $AB > 0$ at DC

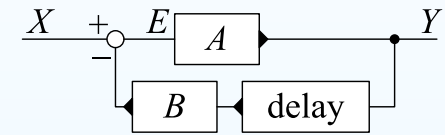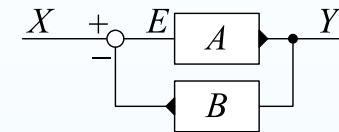

Delays are Death

For a sine wave, a delay anywhere within the loop of half a period (e.g. 0.5 ms for 1 kHz) is the same as multiplying by -1 . At this frequency the loop gain, AB , is large and negative so the system becomes unstable and oscillates.

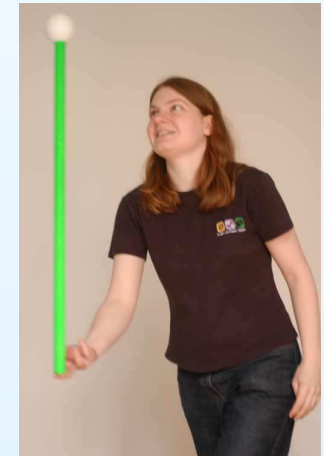Quite a common problem: steering a boat, walking when drunk, balancing a stick.



© Science made simple

Summary

7: Negative Feedback is Wonderful

- Block Diagram
 - Solving Block Diagrams
 - Inverting Amplifier
 - Negative Feedback
- Examples
- Benefits of Negative Feedback
 - Gain Stabilization
 - Distortion Reduction +
 - Interference Rejection
 - Cause/Effect Inversion
 - Instability
 - **Summary**

Why negative feedback is wonderful:

Summary

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback

Examples

- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Why negative feedback is wonderful:

- The precise value of A does not matter as long as it is big enough because the gain is determined by the feedback, B .

Summary

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Why negative feedback is wonderful:

- The precise value of A does not matter as long as it is big enough because the gain is determined by the feedback, B .
- It makes no difference if A varies with time or with signal amplitude (i.e. A is non-linear).

Summary

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback
- Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Why negative feedback is wonderful:

- The precise value of A does not matter as long as it is big enough because the gain is determined by the feedback, B .
- It makes no difference if A varies with time or with signal amplitude (i.e. A is non-linear).
- The effect of external interference at the output is reduced by the loop gain, AB .

Summary

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Why negative feedback is wonderful:

- The precise value of A does not matter as long as it is big enough because the gain is determined by the feedback, B .
- It makes no difference if A varies with time or with signal amplitude (i.e. A is non-linear).
- The effect of external interference at the output is reduced by the loop gain, AB .
- If making a gain B is easy, you can use feedback to make B^{-1} .

Summary

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Why negative feedback is wonderful:

- The precise value of A does not matter as long as it is big enough because the gain is determined by the feedback, B .
- It makes no difference if A varies with time or with signal amplitude (i.e. A is non-linear).
- The effect of external interference at the output is reduced by the loop gain, AB .
- If making a gain B is easy, you can use feedback to make B^{-1} .

The one thing that can go wrong:

- Phase lags or delays can make a feedback system unstable (oscillate).

Summary

7: Negative Feedback is Wonderful

- Block Diagram
- Solving Block Diagrams
- Inverting Amplifier
- Negative Feedback Examples
- Benefits of Negative Feedback
- Gain Stabilization
- Distortion Reduction +
- Interference Rejection
- Cause/Effect Inversion
- Instability
- Summary

Why negative feedback is wonderful:

- The precise value of A does not matter as long as it is big enough because the gain is determined by the feedback, B .
- It makes no difference if A varies with time or with signal amplitude (i.e. A is non-linear).
- The effect of external interference at the output is reduced by the loop gain, AB .
- If making a gain B is easy, you can use feedback to make B^{-1} .

The one thing that can go wrong:

- Phase lags or delays can make a feedback system unstable (oscillate).
- Must make sure that as frequency increases, the loop gain falls below 1 before the phase shift reaches -180° .