

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

8: Nonlinear Components


8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Ideal Diode

The *characteristic* of a component is a plot of I against V using the passive sign convention.

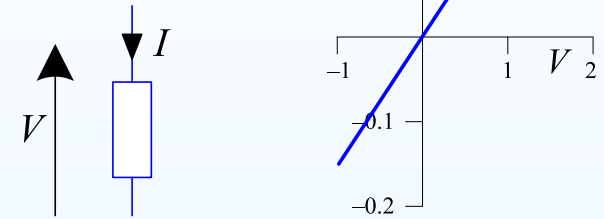All our components have had straight-line characteristics.




Ideal Diode

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

The *characteristic* of a component is a plot of I against V using the passive sign convention.

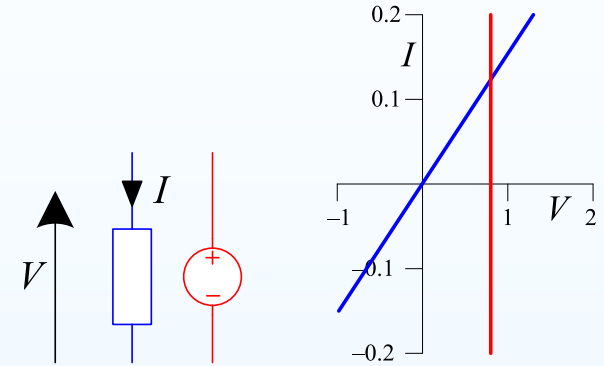All our components have had straight-line characteristics.




Ideal Diode

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

The *characteristic* of a component is a plot of I against V using the passive sign convention.

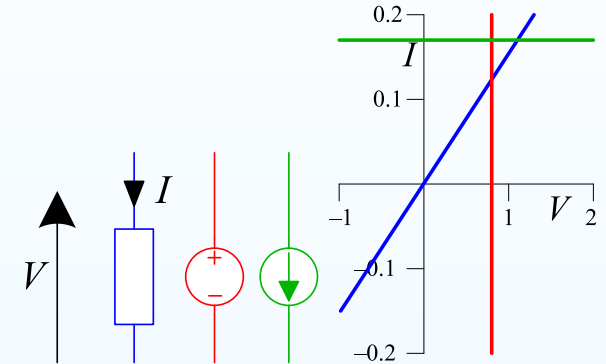All our components have had straight-line characteristics.



Ideal Diode



8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

The *characteristic* of a component is a plot of I against V using the passive sign convention.

All our components have had straight-line characteristics.

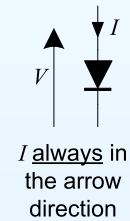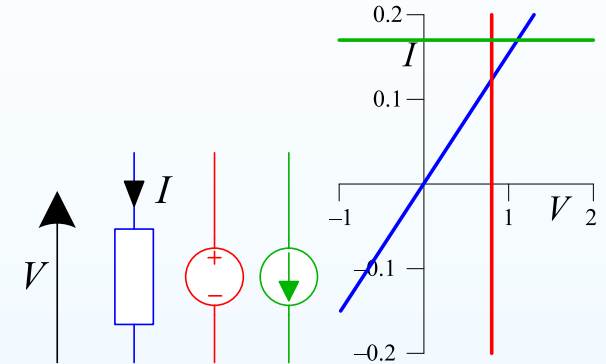An ideal *diode* allows current to flow in one direction only.



Ideal Diode

8: Nonlinear Components



- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

The *characteristic* of a component is a plot of I against V using the passive sign convention.

All our components have had straight-line characteristics.

An ideal *diode* allows current to flow in one direction only.

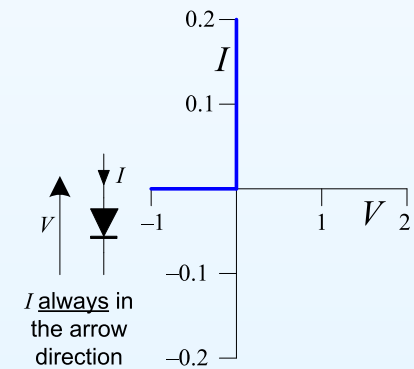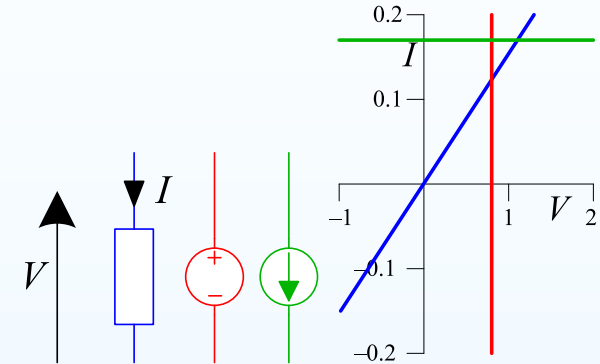Its characteristic is not a straight line, but is made from two straight line segments: *piecewise-linear*.



Ideal Diode

8: Nonlinear Components



- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

The *characteristic* of a component is a plot of I against V using the passive sign convention.

All our components have had straight-line characteristics.

An ideal *diode* allows current to flow in one direction only.

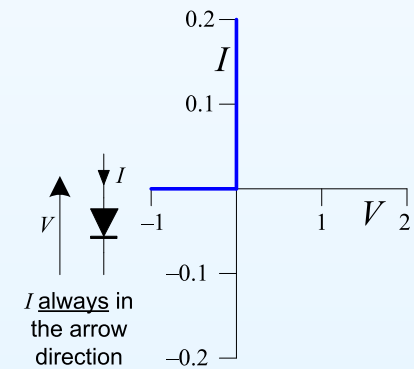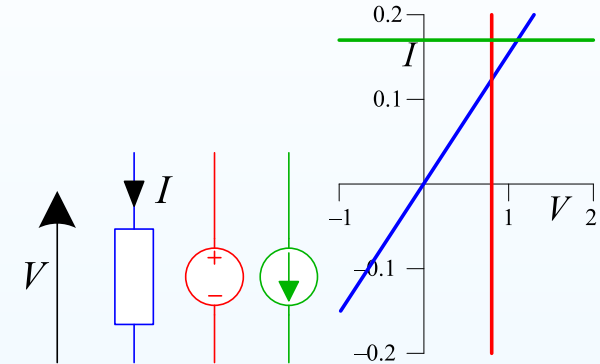Its characteristic is not a straight line, but is made from two straight line segments: *piecewise-linear*. Each segment is a *mode of operation*.



- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Ideal Diode

The *characteristic* of a component is a plot of I against V using the passive sign convention.



All our components have had straight-line characteristics.

An ideal *diode* allows current to flow in one direction only.

Its characteristic is not a straight line, but is made from two straight line segments: *piecewise-linear*. Each segment is a *mode of operation*.

Each mode applies only when a particular condition is true:

Mode	Condition	Equation
Conducting (or “forward bias” or “on”)	$I > 0$	$V = 0$
Non-conducting (or “reverse bias” or “off”)	$V < 0$	$I = 0$

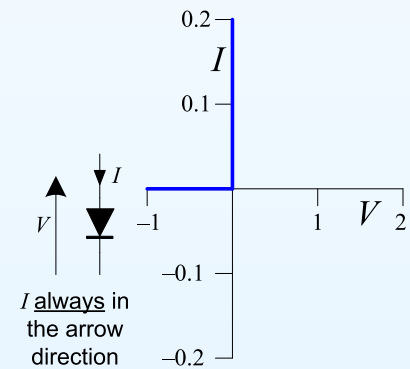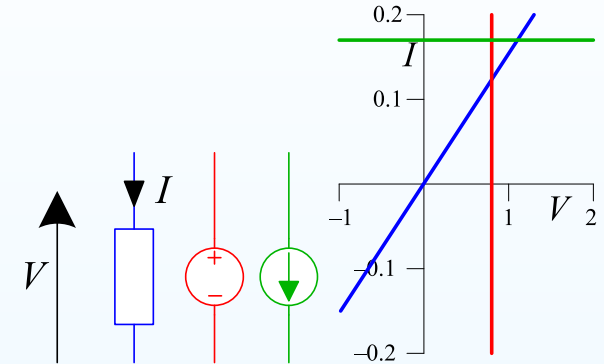

Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.
If you guessed wrongly, the condition will not be met.

Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary


To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.

If you guessed wrongly, the condition will not be met.

Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Voltage across diode is $V_D = U - X$.

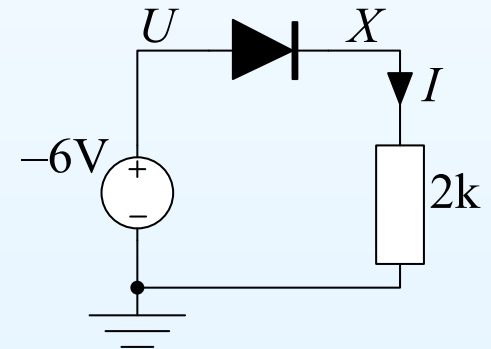Current through diode is $I = \frac{X}{2} \text{ mA}$.



Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary


To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.
If you guessed wrongly, the condition will not be met.

Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Voltage across diode is $V_D = U - X$.

Current through diode is $I = \frac{X}{2} \text{ mA}$.

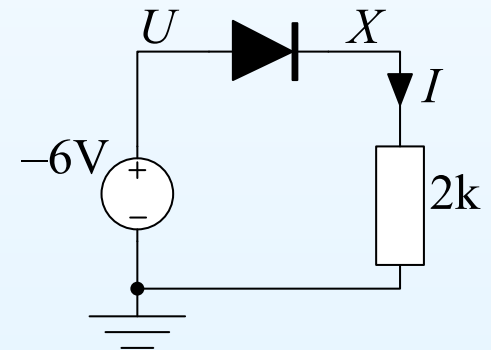Assume Conducting Mode $\Rightarrow V_D = 0$



Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.

If you guessed wrongly, the condition will not be met.


Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Voltage across diode is $V_D = U - X$.

Current through diode is $I = \frac{X}{2} \text{ mA}$.

Assume Conducting Mode $\Rightarrow V_D = 0$

$$V_D = 0$$

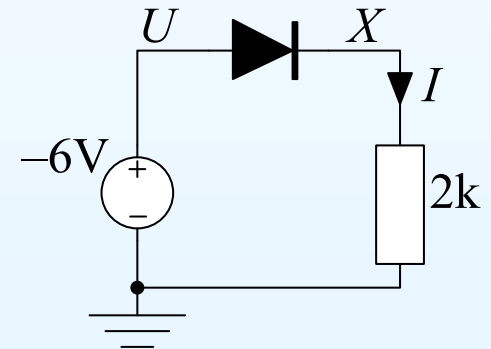

Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.

If you guessed wrongly, the condition will not be met.


Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Voltage across diode is $V_D = U - X$.

Current through diode is $I = \frac{X}{2} \text{ mA}$.

Assume Conducting Mode $\Rightarrow V_D = 0$

$$V_D = 0 \Rightarrow X = U = -6$$

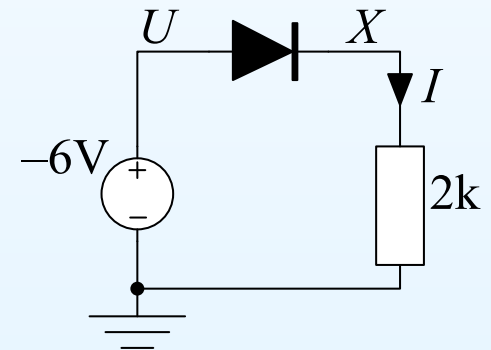

Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.
If you guessed wrongly, the condition will not be met.


Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Voltage across diode is $V_D = U - X$.

Current through diode is $I = \frac{X}{2} \text{ mA}$.

Assume Conducting Mode $\Rightarrow V_D = 0$
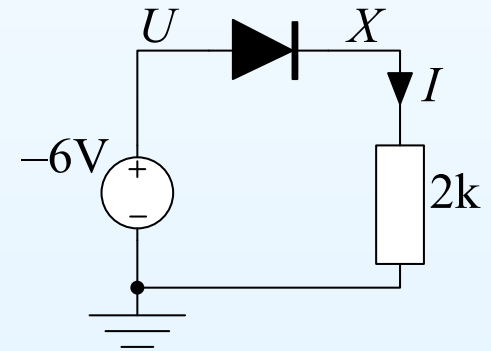
$$V_D = 0 \Rightarrow X = U = -6 \Rightarrow I = -3$$



Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.
If you guessed wrongly, the condition will not be met.

Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$


Voltage across diode is $V_D = U - X$.

Current through diode is $I = \frac{X}{2} \text{ mA}$.

Assume Conducting Mode $\Rightarrow V_D = 0$

$$V_D = 0 \Rightarrow X = U = -6 \Rightarrow I = -3$$

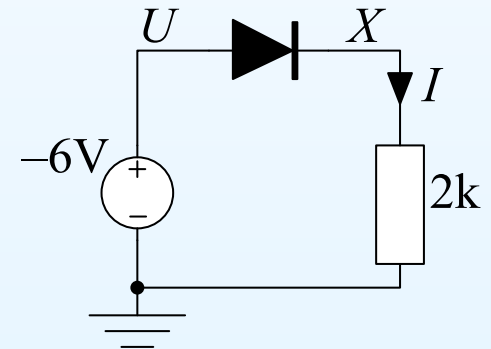but condition is $I > 0$ so **bad guess**



Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.
If you guessed wrongly, the condition will not be met.

Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Voltage across diode is $V_D = U - X$.


Current through diode is $I = \frac{X}{2} \text{ mA}$.

Assume Conducting Mode $\Rightarrow V_D = 0$

$$V_D = 0 \Rightarrow X = U = -6 \Rightarrow I = -3$$

but condition is $I > 0$ so **bad guess**

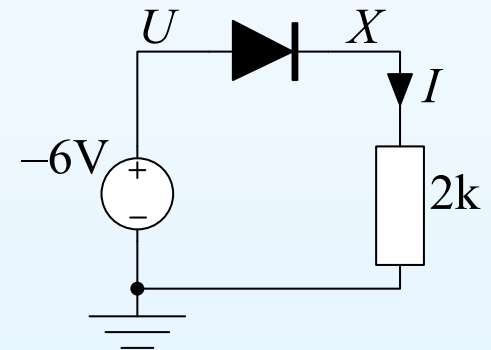Assume Non-conducting Mode $\Rightarrow I = 0$



Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary


To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.
If you guessed wrongly, the condition will not be met.

Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Voltage across diode is $V_D = U - X$.
Current through diode is $I = \frac{X}{2}$ mA.

Assume Conducting Mode $\Rightarrow V_D = 0$
 $V_D = 0 \Rightarrow X = U = -6 \Rightarrow I = -3$
but condition is $I > 0$ so **bad guess**

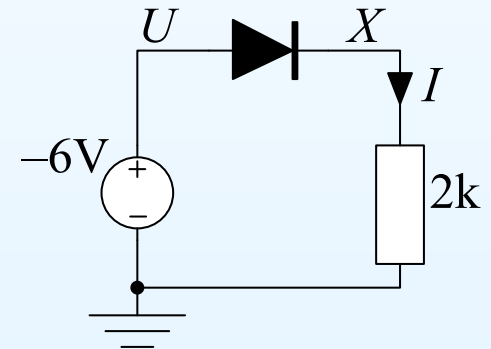Assume Non-conducting Mode $\Rightarrow I = 0$
 $I = 0$



Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.
If you guessed wrongly, the condition will not be met.

Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Voltage across diode is $V_D = U - X$.

Current through diode is $I = \frac{X}{2}$ mA.


Assume Conducting Mode $\Rightarrow V_D = 0$

$$V_D = 0 \Rightarrow X = U = -6 \Rightarrow I = -3$$

but condition is $I > 0$ so **bad guess**

Assume Non-conducting Mode $\Rightarrow I = 0$

$$I = 0 \Rightarrow X = 2I = 0$$

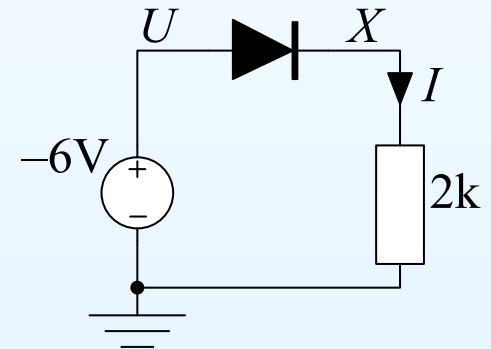

Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary


To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.
If you guessed wrongly, the condition will not be met.

Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Voltage across diode is $V_D = U - X$.
Current through diode is $I = \frac{X}{2}$ mA.

Assume Conducting Mode $\Rightarrow V_D = 0$
 $V_D = 0 \Rightarrow X = U = -6 \Rightarrow I = -3$
but condition is $I > 0$ so **bad guess**

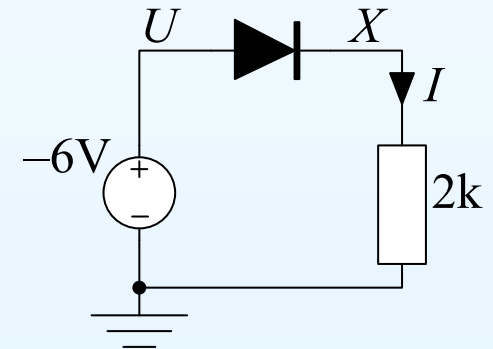Assume Non-conducting Mode $\Rightarrow I = 0$
 $I = 0 \Rightarrow X = 2I = 0 \Rightarrow V_D = U - X = -6$



Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary


To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.
If you guessed wrongly, the condition will not be met.

Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Voltage across diode is $V_D = U - X$.
Current through diode is $I = \frac{X}{2}$ mA.

Assume Conducting Mode $\Rightarrow V_D = 0$
 $V_D = 0 \Rightarrow X = U = -6 \Rightarrow I = -3$
but condition is $I > 0$ so **bad guess**

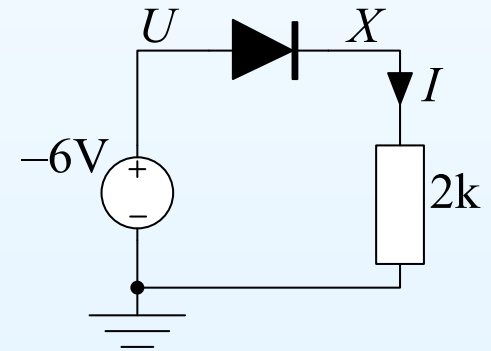Assume Non-conducting Mode $\Rightarrow I = 0$
 $I = 0 \Rightarrow X = 2I = 0 \Rightarrow V_D = U - X = -6$
condition is $V_D < 0$ so **good guess**



Operating modes

8: Nonlinear Components

- Ideal Diode
- **Operating modes**
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

To analyse a circuit with a diode in it, you first guess which mode it is operating in, solve the circuit and then check the condition.
If you guessed wrongly, the condition will not be met.


Mode	Condition	Equation
Conducting	$I > 0$	$V_D = 0$
Non-conducting	$V_D < 0$	$I = 0$

Voltage across diode is $V_D = U - X$.
Current through diode is $I = \frac{X}{2}$ mA.

Assume Conducting Mode $\Rightarrow V_D = 0$
 $V_D = 0 \Rightarrow X = U = -6 \Rightarrow I = -3$
but condition is $I > 0$ so **bad guess**

Assume Non-conducting Mode $\Rightarrow I = 0$
 $I = 0 \Rightarrow X = 2I = 0 \Rightarrow V_D = U - X = -6$
condition is $V_D < 0$ so **good guess**

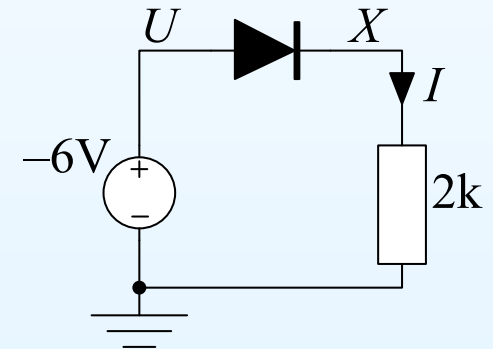Current flows from **anode** to **cathode**.




Switching Point

8: Nonlinear Components

- Ideal Diode
- Operating modes
- **Switching Point**
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

How does X change with U ?

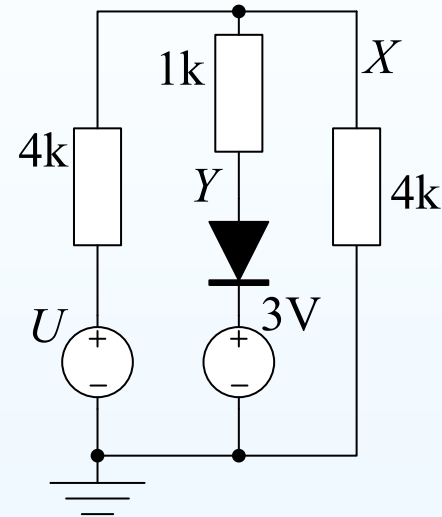

Switching Point


8: Nonlinear Components

- Ideal Diode
- Operating modes
- **Switching Point**
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

How does X change with U ?

Voltage across diode is $V_D = Y - 3$.

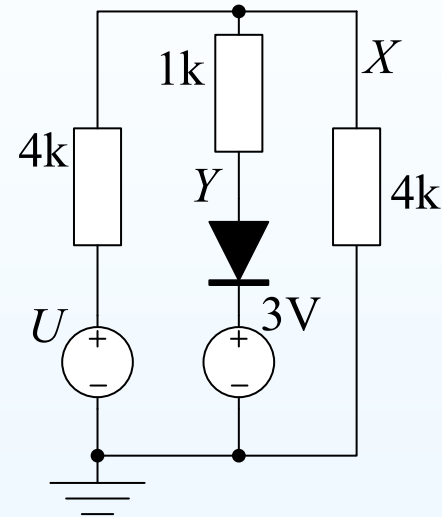Current through diode is $I_D = \frac{X - Y}{1} \text{ mA}$.



Switching Point

8: Nonlinear Components


- Ideal Diode
- Operating modes
- **Switching Point**
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

How does X change with U ?

Voltage across diode is $V_D = Y - 3$.

Current through diode is $I_D = \frac{X - Y}{1} \text{ mA}$.

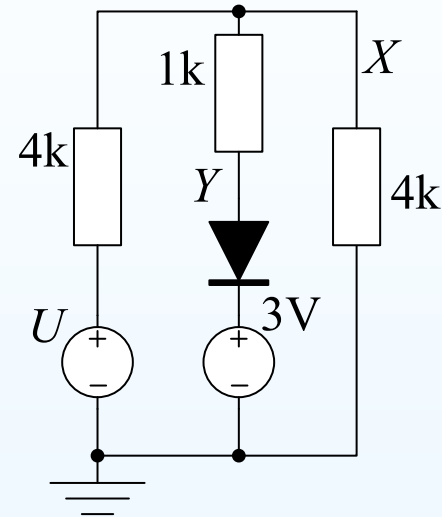Assume Conducting Mode $\Rightarrow Y = 3$



Switching Point

8: Nonlinear Components

- Ideal Diode
- Operating modes
- **Switching Point**
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary



How does X change with U ?

Voltage across diode is $V_D = Y - 3$.

Current through diode is $I_D = \frac{X-Y}{1} \text{ mA}$.

Assume Conducting Mode $\Rightarrow Y = 3$
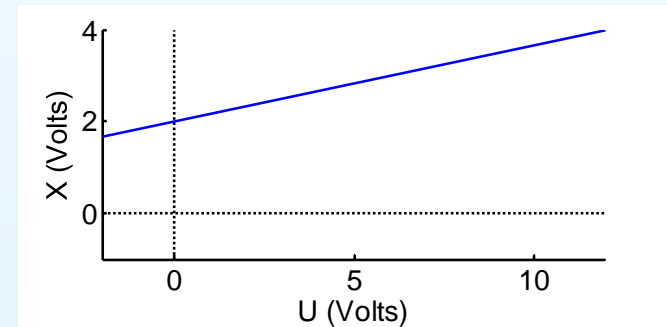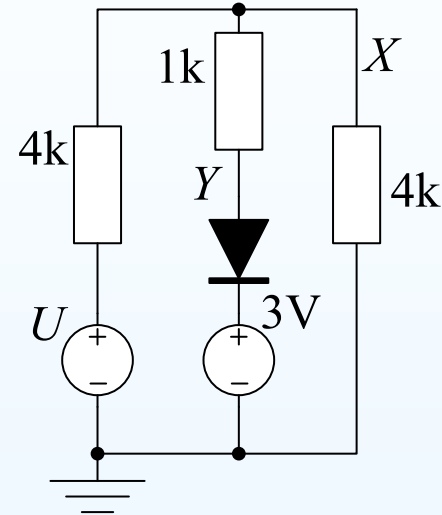
$$\begin{aligned} \text{KCL: } \frac{X-U}{4} + \frac{X-3}{1} + \frac{X}{4} &= 0 \\ \Rightarrow X &= \frac{1}{6}U + 2 \end{aligned}$$



Switching Point

8: Nonlinear Components

- Ideal Diode
- Operating modes
- **Switching Point**
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

How does X change with U ?



Voltage across diode is $V_D = Y - 3$.

Current through diode is $I_D = \frac{X-Y}{1}$ mA.

Assume Conducting Mode $\Rightarrow Y = 3$

$$\text{KCL: } \frac{X-U}{4} + \frac{X-3}{1} + \frac{X}{4} = 0$$
$$\Rightarrow X = \frac{1}{6}U + 2$$
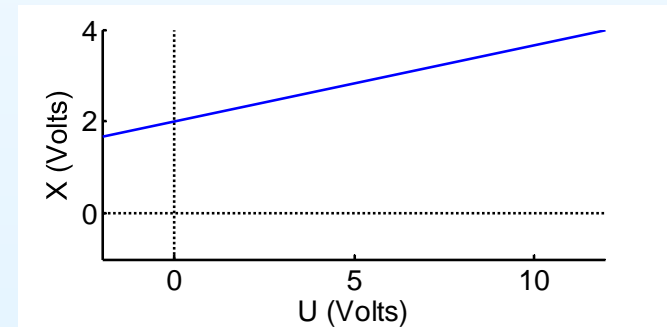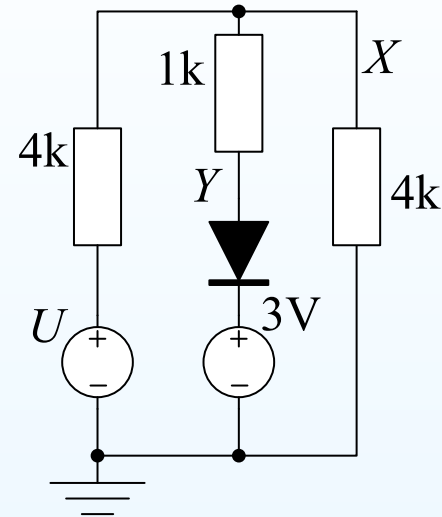
$$I_D = \frac{X-3}{1} = \frac{1}{6}U - 1$$



Switching Point

8: Nonlinear Components

- Ideal Diode
- Operating modes
- **Switching Point**
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

How does X change with U ?

Voltage across diode is $V_D = Y - 3$.



Current through diode is $I_D = \frac{X-Y}{1}$ mA.

Assume Conducting Mode $\Rightarrow Y = 3$

$$\text{KCL: } \frac{X-U}{4} + \frac{X-3}{1} + \frac{X}{4} = 0$$
$$\Rightarrow X = \frac{1}{6}U + 2$$

$$I_D = \frac{X-3}{1} = \frac{1}{6}U - 1$$

$$I_D > 0 \Leftrightarrow U > 6$$

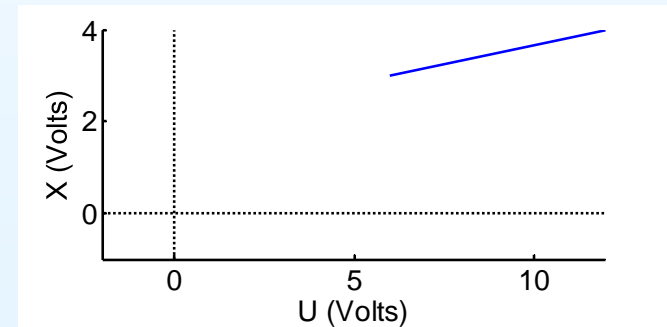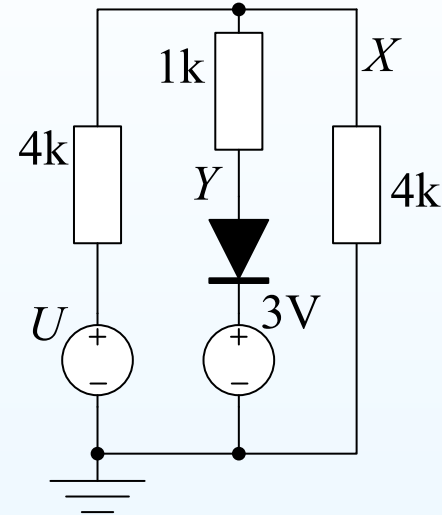

Switching Point

8: Nonlinear Components

- Ideal Diode
- Operating modes
- **Switching Point**
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

How does X change with U ?

Voltage across diode is $V_D = Y - 3$.

Current through diode is $I_D = \frac{X-Y}{1}$ mA.

Assume Conducting Mode $\Rightarrow Y = 3$



$$\text{KCL: } \frac{X-U}{4} + \frac{X-3}{1} + \frac{X}{4} = 0$$
$$\Rightarrow X = \frac{1}{6}U + 2$$

$$I_D = \frac{X-3}{1} = \frac{1}{6}U - 1$$

$$I_D > 0 \Leftrightarrow U > 6$$

Assume Non-conducting Mode

$$\Rightarrow I_D = 0$$

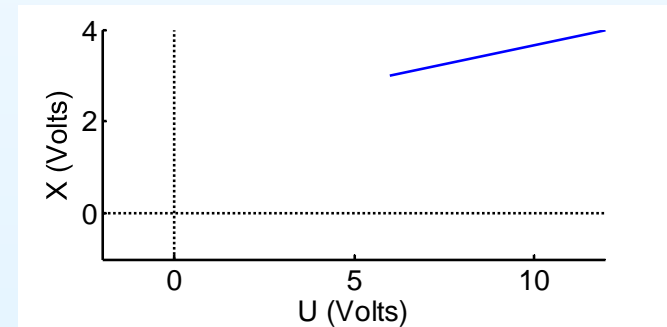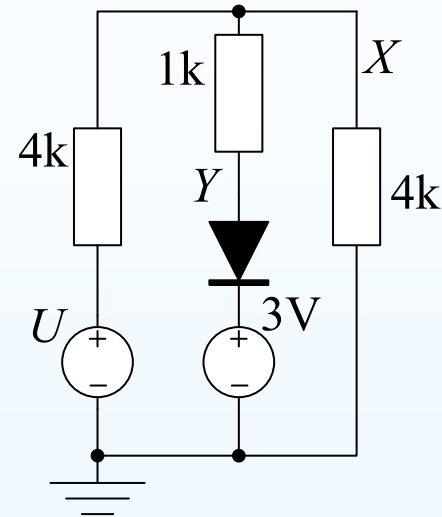

Switching Point

8: Nonlinear Components

- Ideal Diode
- Operating modes
- **Switching Point**
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

How does X change with U ?

Voltage across diode is $V_D = Y - 3$.

Current through diode is $I_D = \frac{X-Y}{1}$ mA.

Assume Conducting Mode $\Rightarrow Y = 3$

$$\text{KCL: } \frac{X-U}{4} + \frac{X-3}{1} + \frac{X}{4} = 0$$

$$\Rightarrow X = \frac{1}{6}U + 2$$



$$I_D = \frac{X-3}{1} = \frac{1}{6}U - 1$$

$$I_D > 0 \Leftrightarrow U > 6$$

Assume Non-conducting Mode

$$\Rightarrow I_D = 0$$
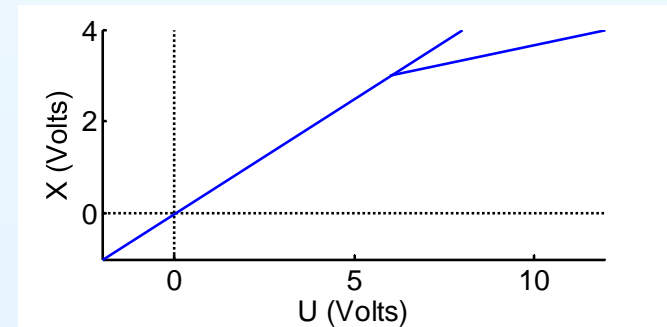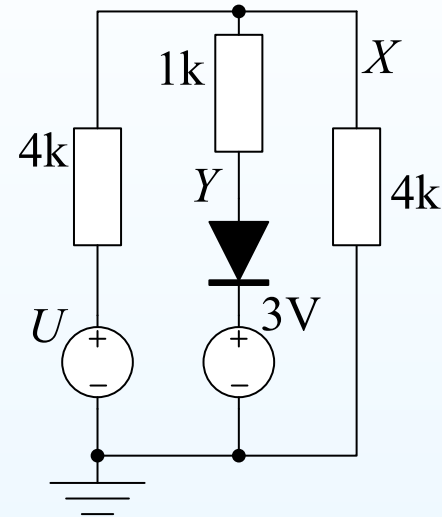
$$\text{Potential Div: } X = Y = \frac{1}{2}U$$



Switching Point

8: Nonlinear Components

- Ideal Diode
- Operating modes
- **Switching Point**
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

How does X change with U ?

Voltage across diode is $V_D = Y - 3$.

Current through diode is $I_D = \frac{X-Y}{1}$ mA.

Assume Conducting Mode $\Rightarrow Y = 3$

$$\text{KCL: } \frac{X-U}{4} + \frac{X-3}{1} + \frac{X}{4} = 0$$

$$\Rightarrow X = \frac{1}{6}U + 2$$

$$I_D = \frac{X-3}{1} = \frac{1}{6}U - 1$$



$$I_D > 0 \Leftrightarrow U > 6$$

Assume Non-conducting Mode

$$\Rightarrow I_D = 0$$

$$\text{Potential Div: } X = Y = \frac{1}{2}U$$

$$V_D = Y - 3 = \frac{1}{2}U - 3$$

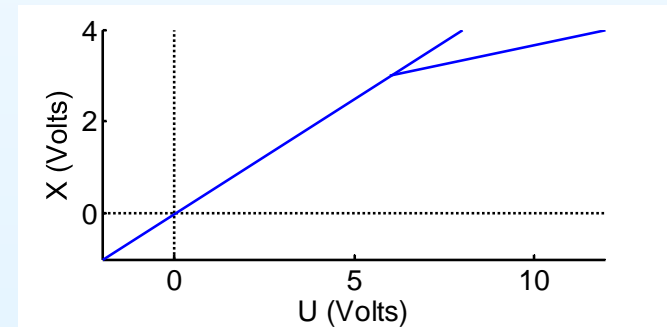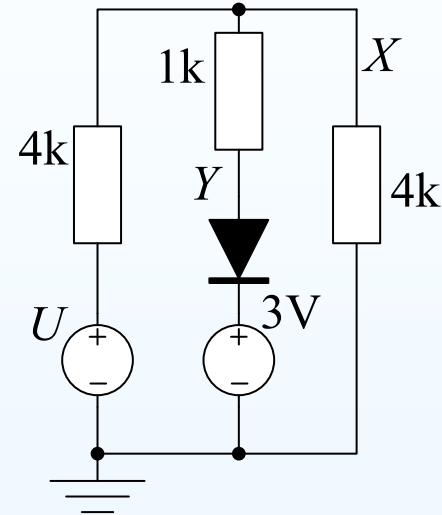

Switching Point

8: Nonlinear Components

- Ideal Diode
- Operating modes
- **Switching Point**
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

How does X change with U ?

Voltage across diode is $V_D = Y - 3$.

Current through diode is $I_D = \frac{X-Y}{1}$ mA.

Assume Conducting Mode $\Rightarrow Y = 3$

$$\text{KCL: } \frac{X-U}{4} + \frac{X-3}{1} + \frac{X}{4} = 0$$
$$\Rightarrow X = \frac{1}{6}U + 2$$

$$I_D = \frac{X-3}{1} = \frac{1}{6}U - 1$$

$$I_D > 0 \Leftrightarrow U > 6$$



Assume Non-conducting Mode

$$\Rightarrow I_D = 0$$

$$\text{Potential Div: } X = Y = \frac{1}{2}U$$

$$V_D = Y - 3 = \frac{1}{2}U - 3$$

$$V_D < 0 \Leftrightarrow U < 6$$

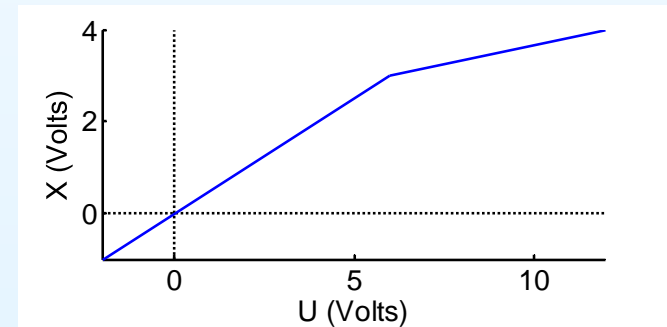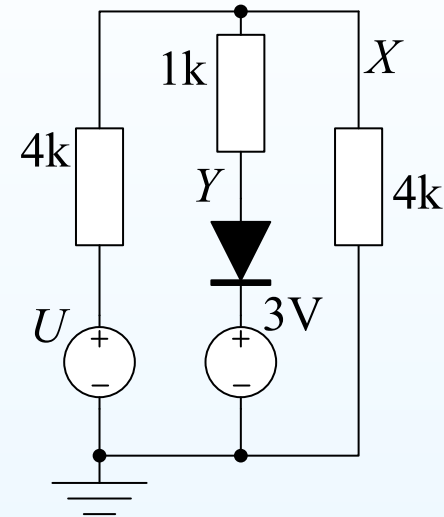

Switching Point

8: Nonlinear Components

- Ideal Diode
- Operating modes
- **Switching Point**
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

How does X change with U ?

Voltage across diode is $V_D = Y - 3$.

Current through diode is $I_D = \frac{X-Y}{1}$ mA.

Assume Conducting Mode $\Rightarrow Y = 3$

$$\text{KCL: } \frac{X-U}{4} + \frac{X-3}{1} + \frac{X}{4} = 0$$

$$\Rightarrow X = \frac{1}{6}U + 2$$

$$I_D = \frac{X-3}{1} = \frac{1}{6}U - 1$$

$$I_D > 0 \Leftrightarrow U > 6$$

Assume Non-conducting Mode

$$\Rightarrow I_D = 0$$



$$\text{Potential Div: } X = Y = \frac{1}{2}U$$

$$V_D = Y - 3 = \frac{1}{2}U - 3$$

$$V_D < 0 \Leftrightarrow U < 6$$

Diode switches between regions where the graphs intersect ($U = 6$).

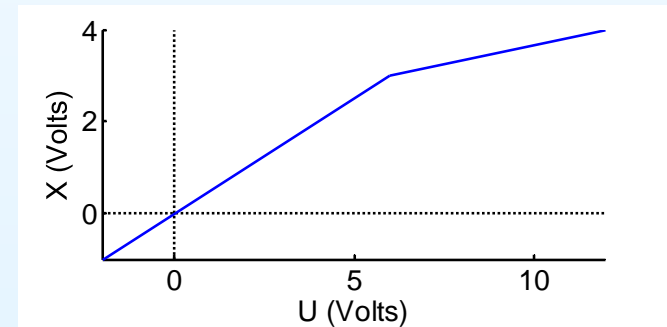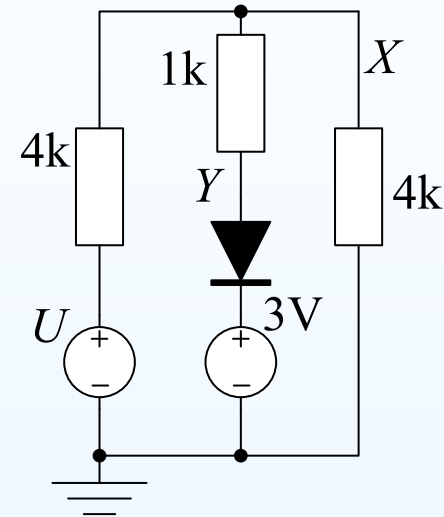At this point both the diode equations, $V_D = 0$ and $I_D = 0$, are true.



Bridge Rectifier

8: Nonlinear Components


- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.

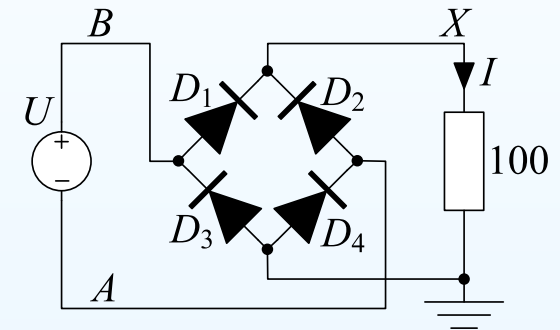

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary


Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.

Case 1: $U > 0$.

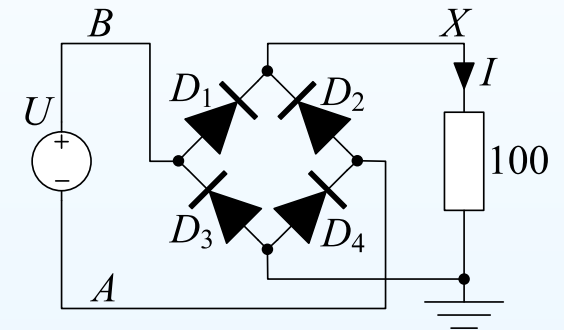

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary


Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.

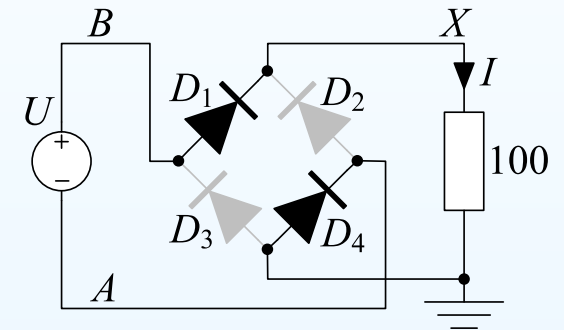Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$



Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:


D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.

Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$

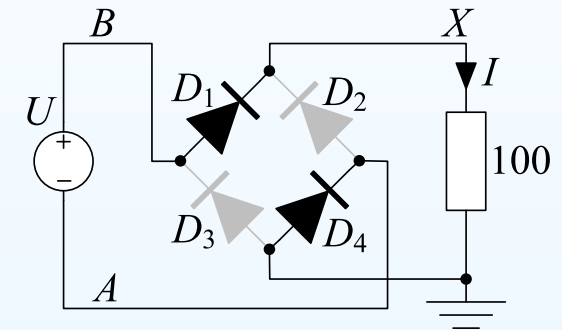Check D_1, D_4 : $I_1 = I_4 = I = \frac{U}{100} > 0$



Note: I_n, V_n apply to diode n

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .


D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.

Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$

Check D_1, D_4 : $I_1 = I_4 = I = \frac{U}{100} > 0$

Check D_2, D_3 : $V_2 = V_3 = -U < 0$

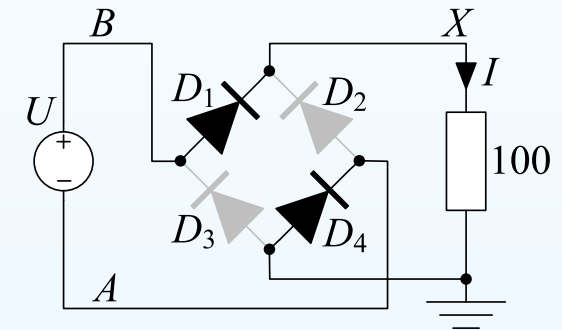

Note: I_n, V_n apply to diode n

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.


The input voltage is $U = B - A$.

Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$

Check D_1, D_4 : $I_1 = I_4 = I = \frac{U}{100} > 0$

Check D_2, D_3 : $V_2 = V_3 = -U < 0$

All diodes OK

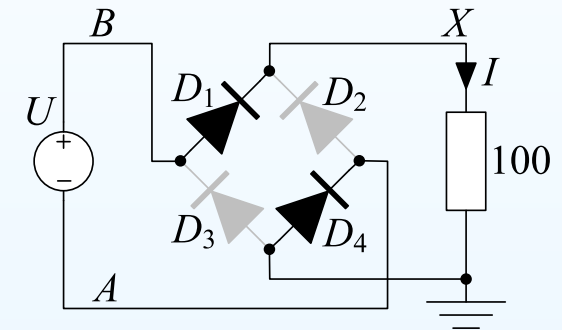

Note: I_n, V_n apply to diode n

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.


Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$

Check D_1, D_4 : $I_1 = I_4 = I = \frac{U}{100} > 0$

Check D_2, D_3 : $V_2 = V_3 = -U < 0$

All diodes OK

Case 2: $U < 0$.

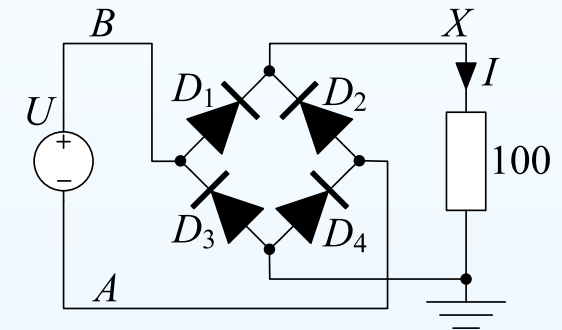

Note: I_n, V_n apply to diode n

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.


Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$

Check D_1, D_4 : $I_1 = I_4 = I = \frac{U}{100} > 0$

Check D_2, D_3 : $V_2 = V_3 = -U < 0$

All diodes OK

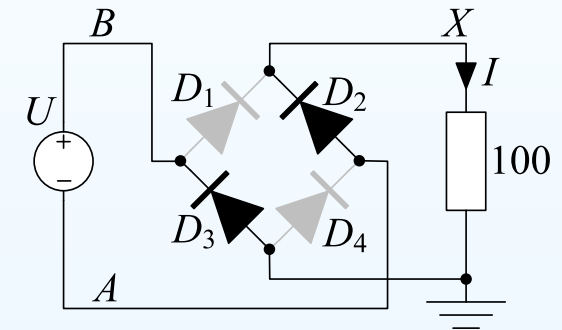Case 2: $U < 0$. D_2, D_3 on $\Rightarrow X = -U$



Note: I_n, V_n apply to diode n

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.

Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$


Check D_1, D_4 : $I_1 = I_4 = I = \frac{U}{100} > 0$

Check D_2, D_3 : $V_2 = V_3 = -U < 0$

All diodes OK

Case 2: $U < 0$. D_2, D_3 on $\Rightarrow X = -U$

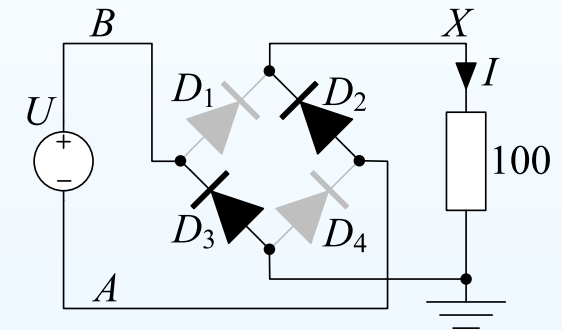Check D_2, D_3 : $I_{2,3} = I = \frac{-U}{100} > 0$



Note: I_n, V_n apply to diode n

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- **Bridge Rectifier**
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.

Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$

Check D_1, D_4 : $I_1 = I_4 = I = \frac{U}{100} > 0$


Check D_2, D_3 : $V_2 = V_3 = -U < 0$

All diodes OK

Case 2: $U < 0$. D_2, D_3 on $\Rightarrow X = -U$

Check D_2, D_3 : $I_{2,3} = I = \frac{-U}{100} > 0$

Check D_1, D_4 : $V_1 = V_4 = U < 0$

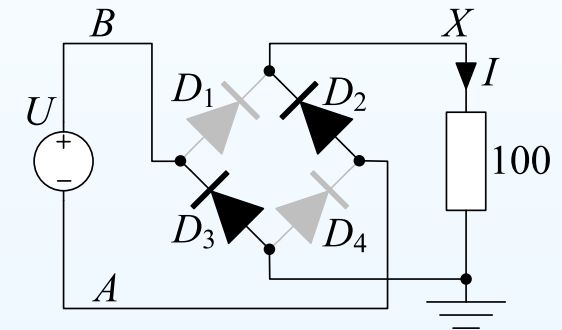

Note: I_n, V_n apply to diode n

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- **Bridge Rectifier**
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.

Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$

Check D_1, D_4 : $I_1 = I_4 = I = \frac{U}{100} > 0$

Check D_2, D_3 : $V_2 = V_3 = -U < 0$


All diodes OK

Case 2: $U < 0$. D_2, D_3 on $\Rightarrow X = -U$

Check D_2, D_3 : $I_{2,3} = I = \frac{-U}{100} > 0$

Check D_1, D_4 : $V_1 = V_4 = U < 0$

All diodes OK

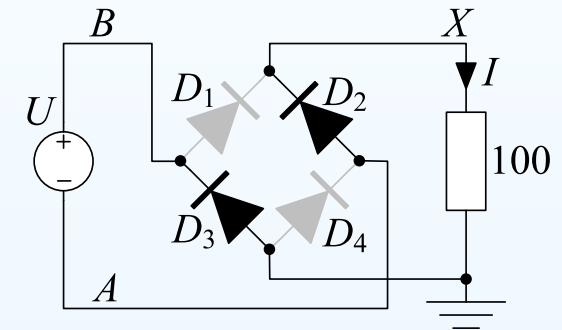

Note: I_n, V_n apply to diode n

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- **Bridge Rectifier**
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.

Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$

Check D_1, D_4 : $I_1 = I_4 = I = \frac{U}{100} > 0$

Check D_2, D_3 : $V_2 = V_3 = -U < 0$

All diodes OK


Case 2: $U < 0$. D_2, D_3 on $\Rightarrow X = -U$

Check D_2, D_3 : $I_{2,3} = I = \frac{-U}{100} > 0$

Check D_1, D_4 : $V_1 = V_4 = U < 0$

All diodes OK

X is always equal to $|U|$: this is an **absolute value circuit**.

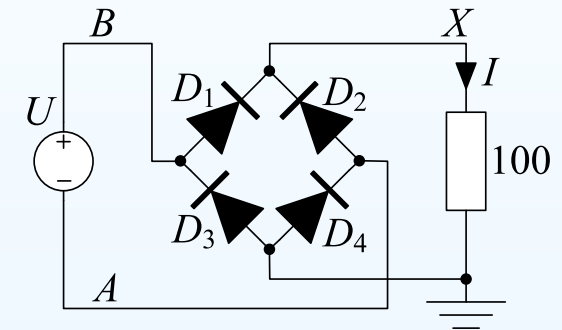

Note: I_n, V_n apply to diode n

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- **Bridge Rectifier**
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.

Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$

Check D_1, D_4 : $I_1 = I_4 = I = \frac{U}{100} > 0$

Check D_2, D_3 : $V_2 = V_3 = -U < 0$

All diodes OK

Case 2: $U < 0$. D_2, D_3 on $\Rightarrow X = -U$


Check D_2, D_3 : $I_{2,3} = I = \frac{-U}{100} > 0$

Check D_1, D_4 : $V_1 = V_4 = U < 0$


All diodes OK

X is always equal to $|U|$: this is an **absolute value** circuit.

If U is a sine wave,

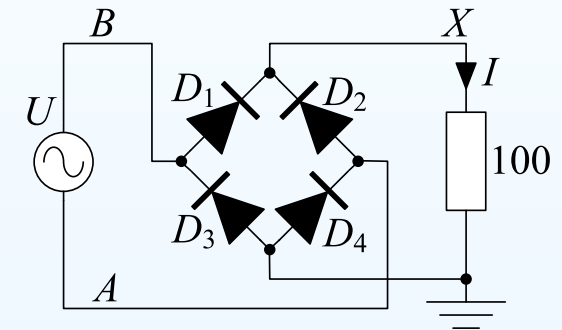

Note: I_n, V_n apply to diode n

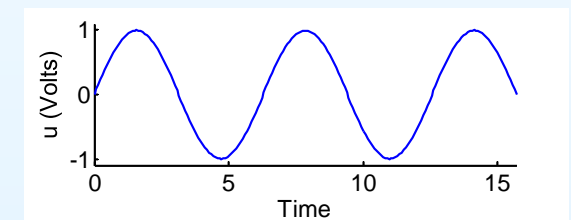

Bridge Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- **Bridge Rectifier**
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Bridge Rectifier: 4 diodes:

D_1 and D_2 both point towards node X .

D_3 and D_4 both point away from ground.

The input voltage is $U = B - A$.

Case 1: $U > 0$. D_1, D_4 on $\Rightarrow X = U$

Check D_1, D_4 : $I_1 = I_4 = I = \frac{U}{100} > 0$

Check D_2, D_3 : $V_2 = V_3 = -U < 0$

All diodes OK

Case 2: $U < 0$. D_2, D_3 on $\Rightarrow X = -U$


Check D_2, D_3 : $I_{2,3} = I = \frac{-U}{100} > 0$

Check D_1, D_4 : $V_1 = V_4 = U < 0$



All diodes OK

X is always equal to $|U|$: this is an **absolute value** circuit.

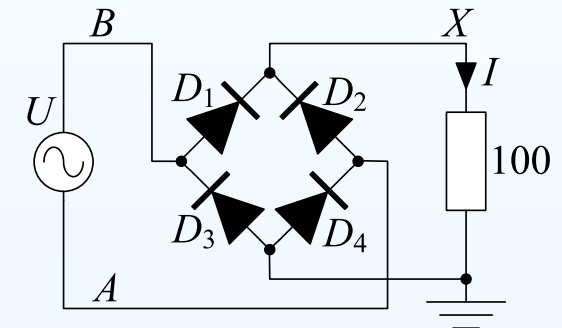If U is a sine wave, then X is a **full-wave rectified** sine wave with twice the frequency.



Note: I_n, V_n apply to diode n

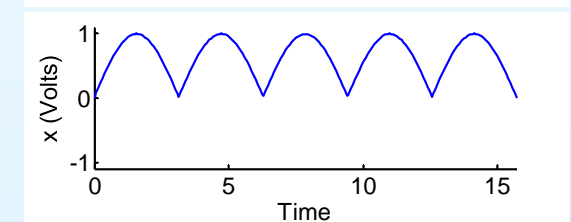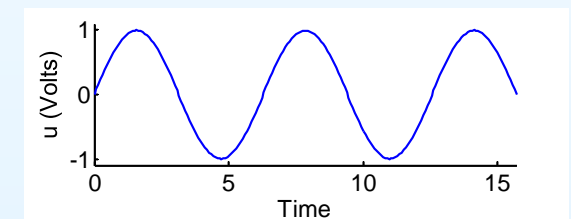


Non-Ideal Diode

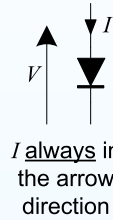8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- **Non-Ideal Diode**
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

An *ideal* diode allows has $V = 0$ whenever it is “on”.





Non-Ideal Diode

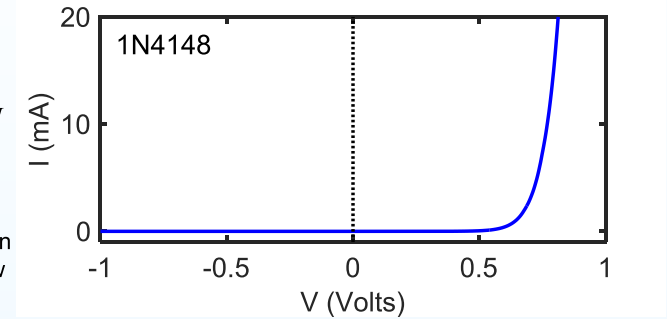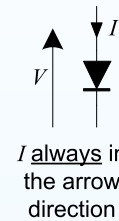8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

An *ideal* diode allows has $V = 0$ whenever it is “on”.




A *real* diode has a voltage drop that depends approximately logarithmically on the current: it increases by about 0.1 V for every 50-fold increase in current.

Non-Ideal Diode

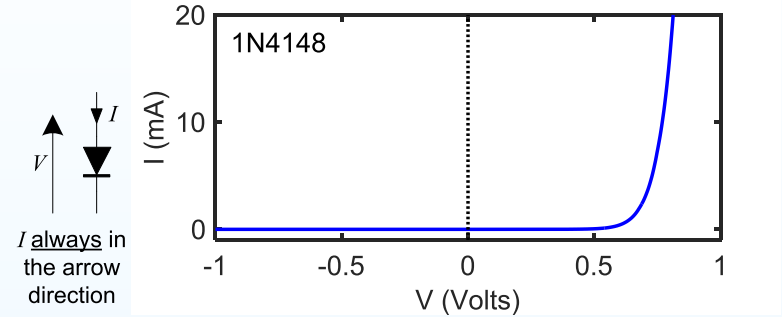8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

An *ideal* diode allows has $V = 0$ whenever it is “on”.



A *real* diode has a voltage drop that depends approximately logarithmically on the current: it increases by about 0.1 V for every 50-fold increase in current.


For a wide range of currents we can treat V as almost constant:

Non-Ideal Diode

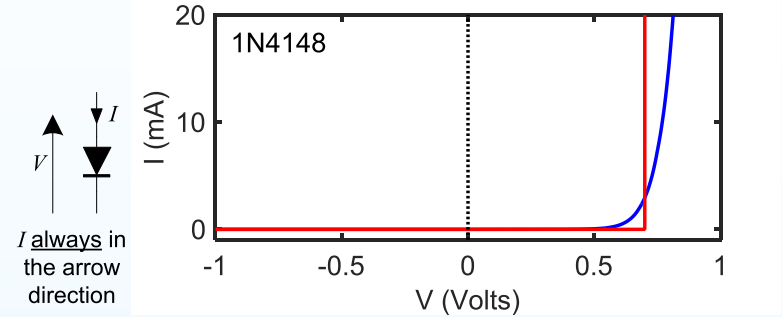8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

An *ideal* diode allows has $V = 0$ whenever it is “on”.



A *real* diode has a voltage drop that depends approximately logarithmically on the current: it increases by about 0.1 V for every 50-fold increase in current.

For a wide range of currents we can treat V as almost constant:


(a) For low-current circuits (e.g $I < 20$ mA): $V \simeq 0.7$ V.

Non-Ideal Diode

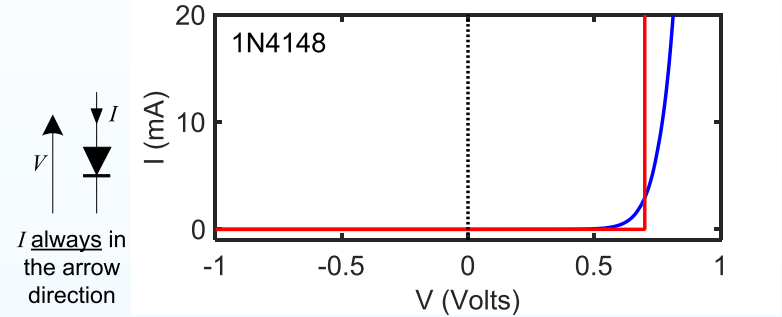8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

An *ideal* diode allows has $V = 0$ whenever it is “on”.



A *real* diode has a voltage drop that depends approximately logarithmically on the current: it increases by about 0.1 V for every 50-fold increase in current.

For a wide range of currents we can treat V as almost constant:


- For low-current circuits (e.g $I < 20$ mA): $V \simeq 0.7$ V.
- For high-current circuits: $V \simeq 1.0$ V.

Non-Ideal Diode

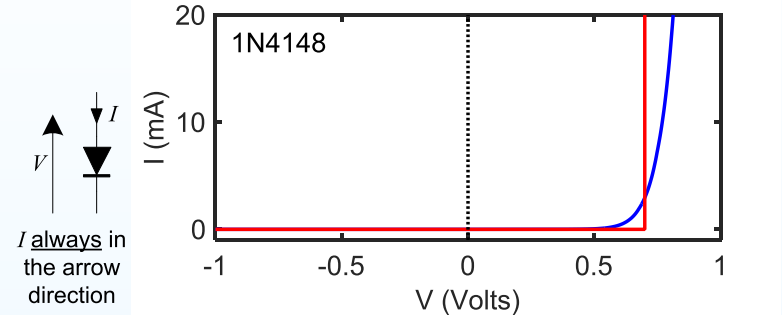8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

An *ideal* diode allows has $V = 0$ whenever it is “on”.



A *real* diode has a voltage drop that depends approximately logarithmically on the current: it increases by about 0.1 V for every 50-fold increase in current.

For a wide range of currents we can treat V as almost constant:

- For low-current circuits (e.g $I < 20$ mA): $V \simeq 0.7$ V.
- For high-current circuits: $V \simeq 1.0$ V.

The two regions of operation are now:


Region	Condition	Equation
Conducting Mode (“on”)	$I > 0$	$V = 0.7$
Non-conducting Mode (“off”)	$V < 0.7$	$I = 0$

Halfwave Rectifier

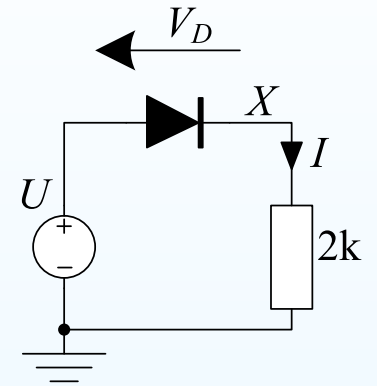8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- **Halfwave Rectifier**
- Precision Halfwave Rectifier
- Summary

A halfwave rectifier aims for $X = \max(U, 0)$



Halfwave Rectifier


8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- **Halfwave Rectifier**
- Precision Halfwave Rectifier
- Summary

A halfwave rectifier aims for $X = \max(U, 0)$

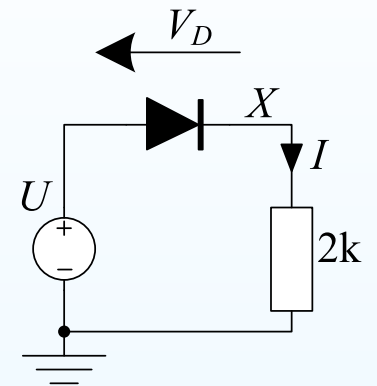(a) $U > 0.7$

Diode on, $X = U - 0.7$, $I = \frac{U - 0.7}{2k} > 0$



Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- **Halfwave Rectifier**
- Precision Halfwave Rectifier
- Summary


A halfwave rectifier aims for $X = \max(U, 0)$

(a) $U > 0.7$

Diode on, $X = U - 0.7$, $I = \frac{U - 0.7}{2k} > 0$

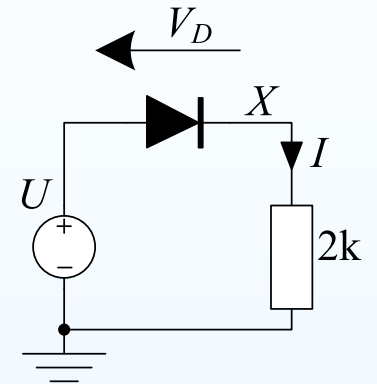(b) $U < 0.7$

Diode off, $I = 0$, $X = 0$, $V_D = U < 0.7$



Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- **Halfwave Rectifier**
- Precision Halfwave Rectifier
- Summary

A halfwave rectifier aims for $X = \max(U, 0)$


(a) $U > 0.7$

Diode on, $X = U - 0.7$, $I = \frac{U - 0.7}{2k} > 0$

(b) $U < 0.7$

Diode off, $I = 0$, $X = 0$, $V_D = U < 0.7$

We actually have $X = \max(U - 0.7, 0)$

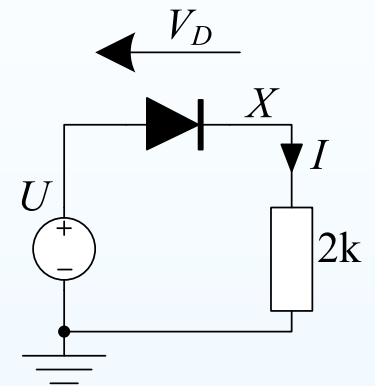

Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- **Halfwave Rectifier**
- Precision Halfwave Rectifier
- Summary

A halfwave rectifier aims for $X = \max(U, 0)$

(a) $U > 0.7$

Diode on, $X = U - 0.7$, $I = \frac{U - 0.7}{2k} > 0$



(b) $U < 0.7$

Diode off, $I = 0$, $X = 0$, $V_D = U < 0.7$

We actually have $X = \max(U - 0.7, 0)$

(1) $u(t) = 20 \sin \omega t$

The 0.7 V drop makes little difference.

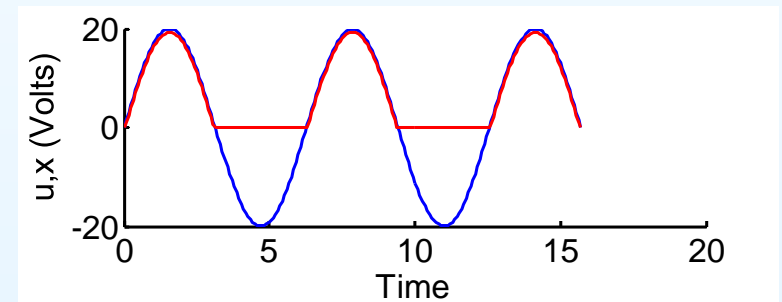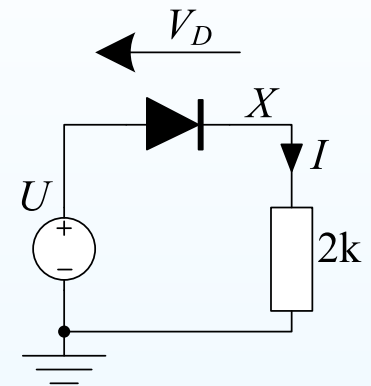

Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- **Halfwave Rectifier**
- Precision Halfwave Rectifier
- Summary

A halfwave rectifier aims for $X = \max(U, 0)$


(a) $U > 0.7$

Diode on, $X = U - 0.7$, $I = \frac{U - 0.7}{2k} > 0$

(b) $U < 0.7$

Diode off, $I = 0$, $X = 0$, $V_D = U < 0.7$

We actually have $X = \max(U - 0.7, 0)$

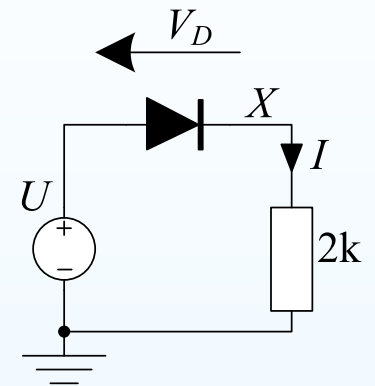


(1) $u(t) = 20 \sin \omega t$

The 0.7 V drop makes little difference.

(2) $u(t) = \sin \omega t$

The 0.7 V drop makes a big difference.

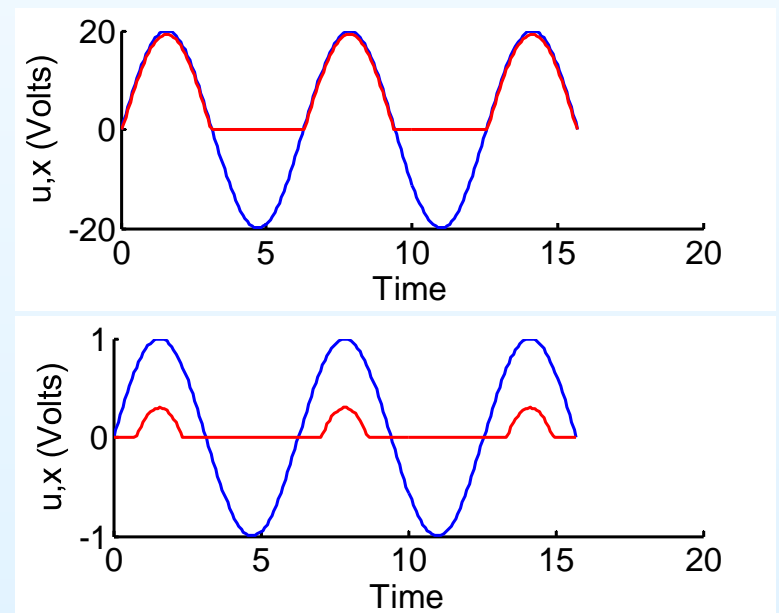


Precision Halfwave Rectifier

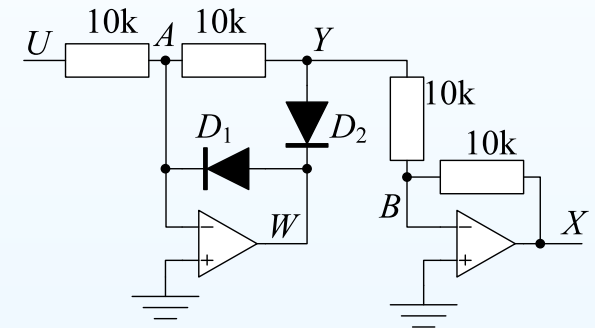8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
Second op-amp is an inverting amplifier so $X = -Y$.




Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$.

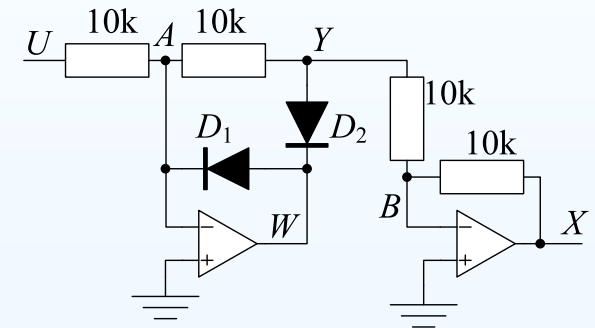


Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
Second op-amp is an inverting amplifier so $X = -Y$.

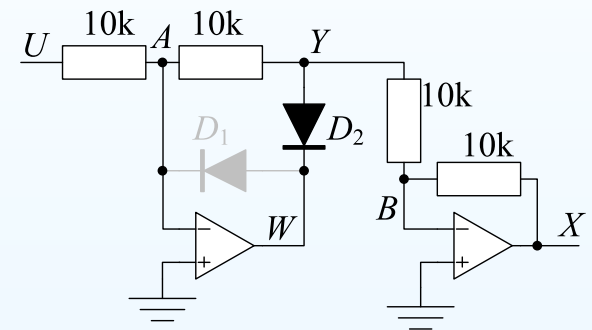Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$



Precision Halfwave Rectifier


8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$
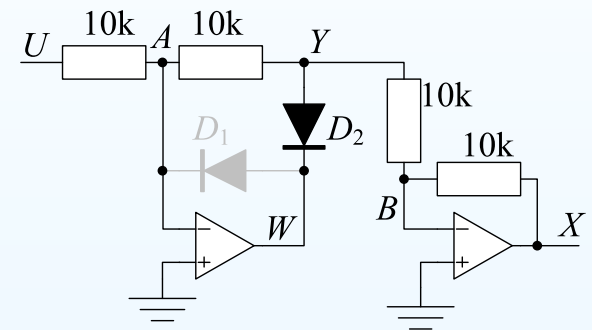
$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$
$$\Rightarrow Y = -U$$



Precision Halfwave Rectifier

8: Nonlinear Components


- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$
$$\Rightarrow Y = -U$$
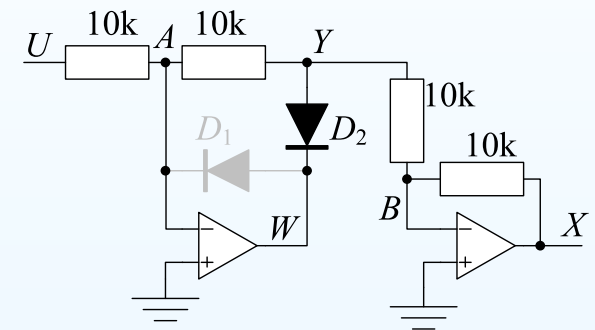
$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$
$$\Rightarrow I_2 = \frac{U}{5} > 0$$



Note: I_n, V_n apply to diode n

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary


Both op-amps have negative feedback, so $A = B = 0$.
Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$
$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$
$$\Rightarrow I_2 = \frac{U}{5} > 0$$

Check D_1 : $V_1 = -U - 0.7 < 0.7$

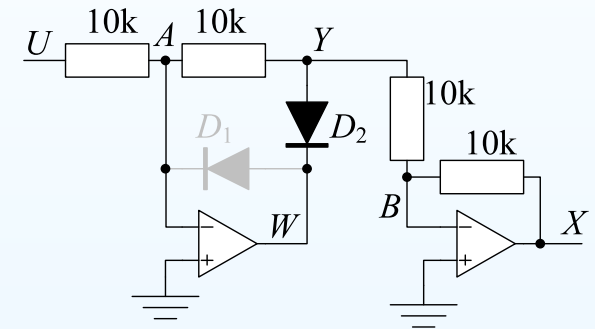

Note: I_n, V_n apply to diode n

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
Second op-amp is an inverting amplifier so $X = -Y$.


Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$
$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$
$$\Rightarrow I_2 = \frac{U}{5} > 0$$

$$\text{Check } D_1: V_1 = -U - 0.7 < 0.7$$

Both diodes OK

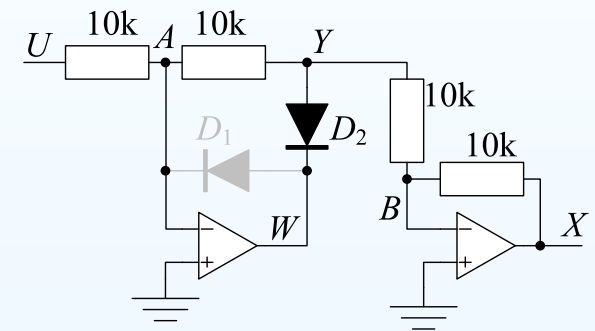

Note: I_n, V_n apply to diode n

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$


$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$
$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$
$$\Rightarrow I_2 = \frac{U}{5} > 0$$

$$\text{Check } D_1: V_1 = -U - 0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = U$$

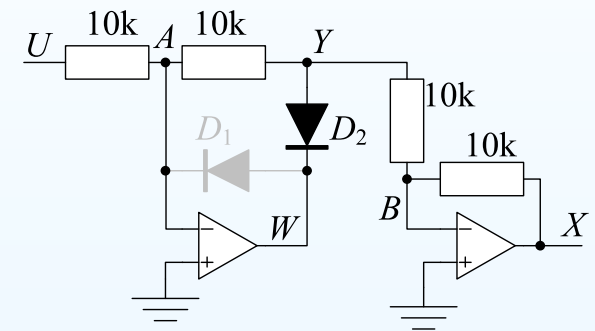

Note: I_n, V_n apply to diode n

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
 Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$

$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$


$$\Rightarrow I_2 = \frac{U}{5} > 0$$

$$\text{Check } D_1: V_1 = -U - 0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = U$$

Case 2: $U < 0$.

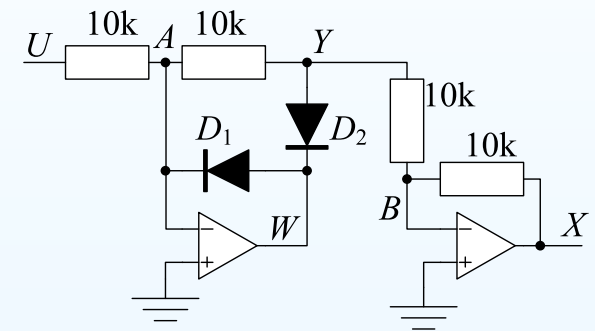

Note: I_n, V_n apply to diode n

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
 Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$

$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$


$$\Rightarrow I_2 = \frac{U}{5} > 0$$

$$\text{Check } D_1: V_1 = -U - 0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = U$$

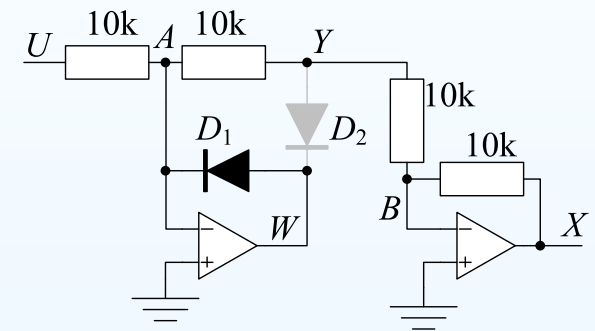Case 2: $U < 0$. D_1 on $\Rightarrow W = 0.7$



Note: I_n, V_n apply to diode n

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
 Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$

$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$

$$\Rightarrow I_2 = \frac{U}{5} > 0$$


$$\text{Check } D_1: V_1 = -U - 0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = U$$

Case 2: $U < 0$. D_1 on $\Rightarrow W = 0.7$
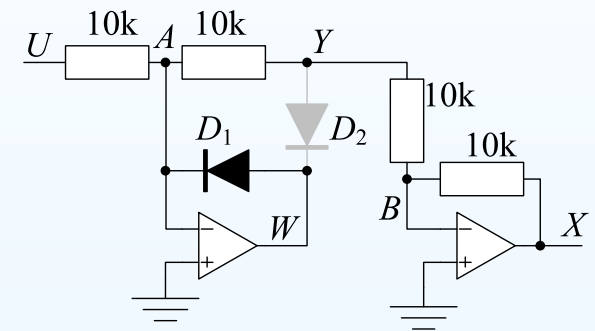
$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} = 0 \Rightarrow Y = 0$$



Note: I_n, V_n apply to diode n

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
 Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$

$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$

$$\Rightarrow I_2 = \frac{U}{5} > 0$$

$$\text{Check } D_1: V_1 = -U - 0.7 < 0.7$$

Both diodes OK


$$\text{Output: } X = -Y = U$$

Case 2: $U < 0$. D_1 on $\Rightarrow W = 0.7$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} = 0 \Rightarrow Y = 0$$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-0}{10} + -I_1 = 0$$

$$\Rightarrow I_1 = -\frac{U}{10} > 0$$

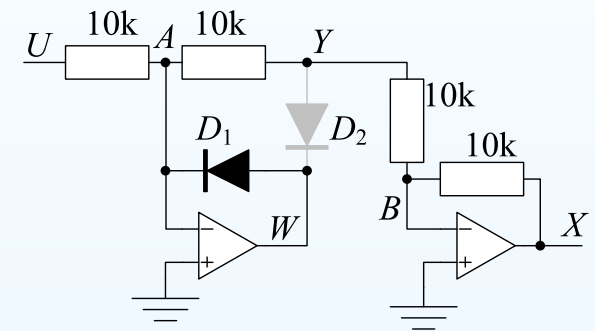

Note: I_n, V_n apply to diode n

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
 Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$

$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$

$$\Rightarrow I_2 = \frac{U}{5} > 0$$

$$\text{Check } D_1: V_1 = -U - 0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = U$$


Case 2: $U < 0$. D_1 on $\Rightarrow W = 0.7$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} = 0 \Rightarrow Y = 0$$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-0}{10} + -I_1 = 0$$

$$\Rightarrow I_1 = -\frac{U}{10} > 0$$
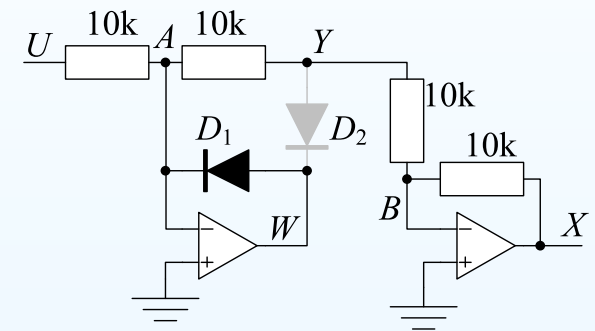
$$\text{Check } D_2: V_2 = Y - W = -0.7 < 0.7$$



Note: I_n, V_n apply to diode n

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
 Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$

$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$

$$\Rightarrow I_2 = \frac{U}{5} > 0$$

$$\text{Check } D_1: V_1 = -U - 0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = U$$

Case 2: $U < 0$. D_1 on $\Rightarrow W = 0.7$


$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} = 0 \Rightarrow Y = 0$$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-0}{10} + -I_1 = 0$$

$$\Rightarrow I_1 = -\frac{U}{10} > 0$$

$$\text{Check } D_2: V_2 = Y - W = -0.7 < 0.7$$

Both diodes OK

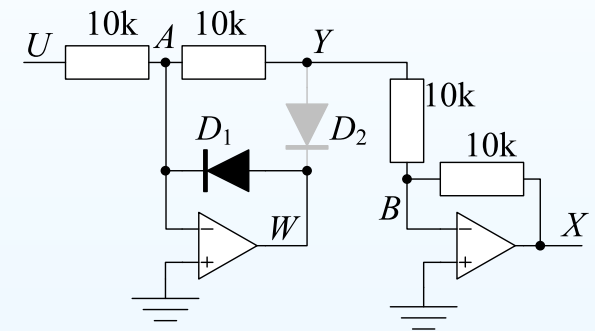

Note: I_n, V_n apply to diode n

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
 Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$

$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$

$$\Rightarrow I_2 = \frac{U}{5} > 0$$

$$\text{Check } D_1: V_1 = -U - 0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = U$$

Case 2: $U < 0$. D_1 on $\Rightarrow W = 0.7$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} = 0 \Rightarrow Y = 0$$


$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-0}{10} + -I_1 = 0$$

$$\Rightarrow I_1 = -\frac{U}{10} > 0$$

$$\text{Check } D_2: V_2 = Y - W = -0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = 0$$

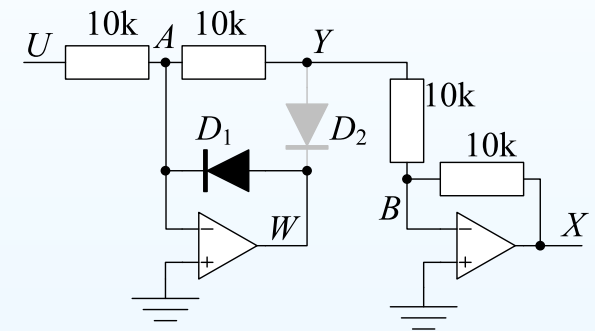

Note: I_n, V_n apply to diode n

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
 Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$

$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$

$$\Rightarrow I_2 = \frac{U}{5} > 0$$

$$\text{Check } D_1: V_1 = -U - 0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = U$$

Case 2: $U < 0$. D_1 on $\Rightarrow W = 0.7$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} = 0 \Rightarrow Y = 0$$


$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-0}{10} + -I_1 = 0$$

$$\Rightarrow I_1 = -\frac{U}{10} > 0$$

$$\text{Check } D_2: V_2 = Y - W = -0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = 0$$

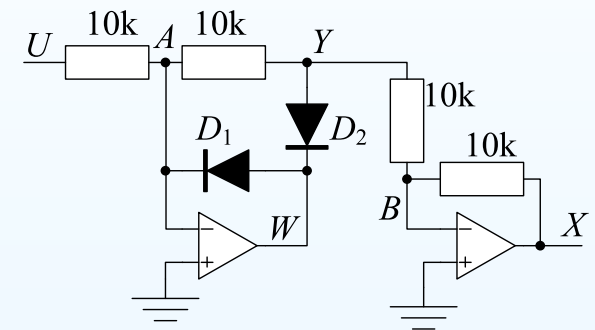

Note: I_n, V_n apply to diode n

$$\text{So } X = \max(U, 0)$$

Precision Halfwave Rectifier

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

Both op-amps have negative feedback, so $A = B = 0$.
 Second op-amp is an inverting amplifier so $X = -Y$.

Case 1: $U > 0$. D_2 on $\Rightarrow W = Y - 0.7$

$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-Y}{10} = 0$$

$$\Rightarrow Y = -U$$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} + I_2 = 0$$

$$\Rightarrow I_2 = \frac{U}{5} > 0$$

$$\text{Check } D_1: V_1 = -U - 0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = U$$

Case 2: $U < 0$. D_1 on $\Rightarrow W = 0.7$

$$\text{KCL @ Y: } \frac{Y-0}{10} + \frac{Y-0}{10} = 0 \Rightarrow Y = 0$$


$$\text{KCL @ A: } \frac{0-U}{10} + \frac{0-0}{10} + -I_1 = 0$$

$$\Rightarrow I_1 = -\frac{U}{10} > 0$$

$$\text{Check } D_2: V_2 = Y - W = -0.7 < 0.7$$

Both diodes OK

$$\text{Output: } X = -Y = 0$$

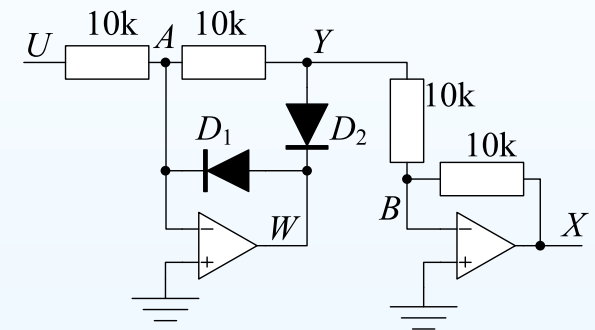

Note: I_n, V_n apply to diode n

$$\text{So } X = \max(U, 0)$$

Putting diodes in a feedback loop allows their voltage drops to be eliminated.

Summary

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- **Summary**

- **Beware: a nonlinear circuit does not obey superposition**

Summary

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- **Summary**

- **Beware: a nonlinear circuit does not obey superposition**
- **Ideal diode:**
 - Two regions of operation:
 - ▷ **Conducting Mode** (= “on”): $V = 0$ and $I > 0$

Summary

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

- Beware: a nonlinear circuit does not obey superposition
- Ideal diode:
 - Two regions of operation:
 - ▷ **Conducting Mode** (= “on”): $V = 0$ and $I > 0$
 - ▷ **Non-conducting Mode** (= “off”): $I = 0$ and $V < 0$

Summary

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

- **Beware: a nonlinear circuit does not obey superposition**
- **Ideal diode:**
 - Two regions of operation:
 - ▷ **Conducting Mode** (= “on”): $V = 0$ and $I > 0$
 - ▷ **Non-conducting Mode** (= “off”): $I = 0$ and $V < 0$
- **Solving a diode circuit:**
 - (a) Guess region
 - (b) Solve circuit: assuming $V = 0$ or $I = 0$
 - (c) Check condition: either $I > 0$ or $V < 0$

Summary

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

- **Beware: a nonlinear circuit does not obey superposition**
- **Ideal diode:**
 - Two regions of operation:
 - ▷ **Conducting Mode** (= “on”): $V = 0$ and $I > 0$
 - ▷ **Non-conducting Mode** (= “off”): $I = 0$ and $V < 0$
- **Solving a diode circuit:**
 - (a) Guess region
 - (b) Solve circuit: assuming $V = 0$ or $I = 0$
 - (c) Check condition: either $I > 0$ or $V < 0$
- **Real diode:** $V \simeq 0.7$ in Conducting Mode ($\simeq 1.0$ for high currents)

Summary

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

- **Beware: a nonlinear circuit does not obey superposition**
- **Ideal diode:**
 - Two regions of operation:
 - ▷ **Conducting Mode** (= “on”): $V = 0$ and $I > 0$
 - ▷ **Non-conducting Mode** (= “off”): $I = 0$ and $V < 0$
- **Solving a diode circuit:**
 - (a) Guess region
 - (b) Solve circuit: assuming $V = 0$ or $I = 0$
 - (c) Check condition: either $I > 0$ or $V < 0$
- **Real diode:** $V \simeq 0.7$ in Conducting Mode ($\simeq 1.0$ for high currents)
- Fullwave and halfwave rectifier circuits

Summary

- **Beware: a nonlinear circuit does not obey superposition**
- **Ideal diode:**
 - Two regions of operation:
 - ▷ **Conducting Mode** (= “on”): $V = 0$ and $I > 0$
 - ▷ **Non-conducting Mode** (= “off”): $I = 0$ and $V < 0$
- **Solving a diode circuit:**
 - (a) Guess region
 - (b) Solve circuit: assuming $V = 0$ or $I = 0$
 - (c) Check condition: either $I > 0$ or $V < 0$
- **Real diode:** $V \simeq 0.7$ in Conducting Mode ($\simeq 1.0$ for high currents)
- Fullwave and halfwave rectifier circuits
- Precision Rectifier Circuit
 - Use an opamp to eliminate the 0.7 V diode drop.

Summary

8: Nonlinear Components

- Ideal Diode
- Operating modes
- Switching Point
- Bridge Rectifier
- Non-Ideal Diode
- Halfwave Rectifier
- Precision Halfwave Rectifier
- Summary

- **Beware: a nonlinear circuit does not obey superposition**
- **Ideal diode:**
 - Two regions of operation:
 - ▷ **Conducting Mode** (= “on”): $V = 0$ and $I > 0$
 - ▷ **Non-conducting Mode** (= “off”): $I = 0$ and $V < 0$
- **Solving a diode circuit:**
 - (a) Guess region
 - (b) Solve circuit: assuming $V = 0$ or $I = 0$
 - (c) Check condition: either $I > 0$ or $V < 0$
- **Real diode:** $V \simeq 0.7$ in Conducting Mode ($\simeq 1.0$ for high currents)
- Fullwave and halfwave rectifier circuits
- Precision Rectifier Circuit
 - Use an opamp to eliminate the 0.7 V diode drop.

For further details see Irwin Ch 17.