#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

# **9: Capacitors and Inductors**

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

A capacitor is formed from two conducting plates separated by a thin insulating layer.

If a current i flows, positive change, q, will accumulate on the upper plate. To preserve charge neutrality, a balancing negative charge will be present on the lower plate.



#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

A capacitor is formed from two conducting plates separated by a thin insulating layer.

If a current i flows, positive change, q, will accumulate on the upper plate. To preserve charge neutrality, a balancing negative charge will be present on the lower plate.



There will be a potential energy difference (or voltage v) between the plates proportional to q.

 $v = \frac{d}{A\epsilon}q$  where A is the area of the plates, d is their separation and  $\epsilon$  is the permittivity of the insulating layer ( $\epsilon_0 = 8.85 \, pF/m$  for a vacuum).

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

A capacitor is formed from two conducting plates separated by a thin insulating layer.

If a current i flows, positive change, q, will accumulate on the upper plate. To preserve charge neutrality, a balancing negative charge will be present on the lower plate.



There will be a potential energy difference (or voltage v) between the plates proportional to q.

 $v = \frac{d}{A\epsilon}q$  where A is the area of the plates, d is their separation and  $\epsilon$  is the permittivity of the insulating layer ( $\epsilon_0 = 8.85 \, pF/m$  for a vacuum).

The quantity  $C = \frac{A\epsilon}{d}$  is the *capacitance* and is measured in Farads (F), hence q = Cv.

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

A capacitor is formed from two conducting plates separated by a thin insulating layer.

If a current i flows, positive change, q, will accumulate on the upper plate. To preserve charge neutrality, a balancing negative charge will be present on the lower plate.



There will be a potential energy difference (or voltage v) between the plates proportional to q.

 $v = \frac{d}{A\epsilon}q$  where A is the area of the plates, d is their separation and  $\epsilon$  is the permittivity of the insulating layer ( $\epsilon_0 = 8.85 \ pF/m$  for a vacuum).

The quantity  $C = \frac{A\epsilon}{d}$  is the *capacitance* and is measured in Farads (F), hence q = Cv.

The current, i, is the rate of charge on the plate, hence the

capacitor equation: 
$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Capacitor symbol represents the two separated plates. Capacitor types are distinguished by the material used as the insulator.

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Capacitor symbol represents the two separated plates. Capacitor types are distinguished by the material used as the insulator.

Polystyrene: Two sheets of foil separated by a thin plastic film and rolled up to save space. Values:  $10\,pF$  to  $1\,nF.$ 



#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Capacitor symbol represents the two separated plates. Capacitor types are distinguished by the material used as the insulator.

Polystyrene: Two sheets of foil separated by a thin plastic film and rolled up to save space. Values:  $10 \, pF$  to  $1 \, nF$ .

Ceramic: Alternate layers of metal and ceramic (a few  $\mu m$  thick). Values: 1 nF to  $1 \mu F$ .





#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Capacitor symbol represents the two separated plates. Capacitor types are distinguished by the material used as the insulator.

Polystyrene: Two sheets of foil separated by a thin plastic film and rolled up to save space. Values:  $10 \, pF$  to  $1 \, nF$ .

Ceramic: Alternate layers of metal and ceramic (a few  $\mu m$  thick). Values: 1 nF to  $1 \mu F$ .

Electrolytic: Two sheets of aluminium foil separated by paper soaked in conducting electrolyte. The insulator is a thin oxide layer on one of the foils. Values:  $1 \,\mu F$  to  $10 \,m F$ .







#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Capacitor symbol represents the two separated plates. Capacitor types are distinguished by the material used as the insulator.

Polystyrene: Two sheets of foil separated by a thin plastic film and rolled up to save space. Values:  $10\,pF$  to  $1\,nF.$ 

Ceramic: Alternate layers of metal and ceramic (a few  $\mu m$  thick). Values: 1 nF to  $1 \mu F$ .

Electrolytic: Two sheets of aluminium foil separated by paper soaked in conducting electrolyte. The insulator is a thin oxide layer on one of the foils. Values:  $1 \,\mu F$  to  $10 \,m F$ .







Electrolytic capacitors are **polarised**: the foil with the oxide layer must always be at a positive voltage relative to the other (else **explosion**). Negative terminal indicated by a curved plate in symbol

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Capacitor symbol represents the two separated plates. Capacitor types are distinguished by the material used as the insulator.

Polystyrene: Two sheets of foil separated by a thin plastic film and rolled up to save space. Values:  $10\,pF$  to  $1\,nF.$ 

Ceramic: Alternate layers of metal and ceramic (a few  $\mu m$  thick). Values: 1 nF to  $1 \mu F$ .

Electrolytic: Two sheets of aluminium foil separated by paper soaked in conducting electrolyte. The insulator is a thin oxide layer on one of the foils. Values:  $1 \,\mu F$  to  $10 \,m F$ .









Electrolytic capacitors are **polarised**: the foil with the oxide layer must always be at a positive voltage relative to the other (else **explosion**). Negative terminal indicated by a curved plate in symbol or "-".

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Inductors are formed from coils of wire, often around a steel or ferrite core.





#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Inductors are formed from coils of wire, often around a steel or ferrite core.





The magnetic flux within the coil is  $\Phi = \frac{\mu NA}{l}i$  where *N* is the number of turns, *A* is the cross-sectional area of the coil and *l* is the length of the coil (around the toroid).

 $\mu$  is a property of the material that the core is made from and is called its *permeability*. For free space (or air):  $\mu_0 = 4\pi \times 10^{-7} = 1.26 \,\mu$ /m, for steel,  $\mu \approx 4000 \mu_0 = 5 \, m$ /m.

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Inductors are formed from coils of wire, often around a steel or ferrite core.





The magnetic flux within the coil is  $\Phi = \frac{\mu NA}{l}i$  where *N* is the number of turns, *A* is the cross-sectional area of the coil and *l* is the length of the coil (around the toroid).

 $\mu$  is a property of the material that the core is made from and is called its *permeability*. For free space (or air):  $\mu_0 = 4\pi \times 10^{-7} = 1.26 \,\mu$ /m, for steel,  $\mu \approx 4000 \mu_0 = 5 \, m$ /m.

From Faraday's law:  $v = N \frac{d\Phi}{dt} = \frac{\mu N^2 A}{l} \frac{di}{dt} = L \frac{di}{dt}$ .

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Inductors are formed from coils of wire, often around a steel or ferrite core.





The magnetic flux within the coil is  $\Phi = \frac{\mu NA}{l}i$  where *N* is the number of turns, *A* is the cross-sectional area of the coil and *l* is the length of the coil (around the toroid).

 $\mu$  is a property of the material that the core is made from and is called its *permeability*. For free space (or air):  $\mu_0 = 4\pi \times 10^{-7} = 1.26 \,\mu H/m$ , for steel,  $\mu \approx 4000 \mu_0 = 5 \, m H/m$ .

From Faraday's law:  $v = N \frac{d\Phi}{dt} = \frac{\mu N^2 A}{l} \frac{di}{dt} = L \frac{di}{dt}$ .

We measure the *inductance*,  $L = \frac{\mu N^2 A}{l}$ , in Henrys (H).

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

We can describe all three types of passive component by the relationship between V and I using, in each case, the passive sign convention.

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

We can describe all three types of passive component by the relationship between V and I using, in each case, the passive sign convention.

Resistor: v = Ri



#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

We can describe all three types of passive component by the relationship between V and I using, in each case, the passive sign convention.

Resistor: v = Ri

Inductor:  $v = L \frac{di}{dt}$ 





#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

We can describe all three types of passive component by the relationship between V and I using, in each case, the passive sign convention.

Resistor: v = Ri

Inductor:  $v = L \frac{di}{dt}$ 







Capacitor:  $i = C \frac{dv}{dt}$ 

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

We can describe all three types of passive component by the relationship between V and I using, in each case, the passive sign convention.

Resistor: v = Ri

Inductor:  $v = L \frac{di}{dt}$ 

Capacitor:  $i = C \frac{dv}{dt}$ 







Notes: (1) There are **no minus signs anywhere** whatever you were taught at school.

(2) We use lower case, v, for time-varying voltages.

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary





- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary





- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

$$v = v_1 + v_2 = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} = (L_1 + L_2) \frac{di}{dt}$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

 $v = v_1 + v_2 = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$  $= (L_1 + L_2) \frac{di}{dt}$ 



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary









- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



Same equation as a single inductor of value  $L_1 + L_2$ 





- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary









- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

$$v = v_1 + v_2 = L_1 \frac{di}{dt} + L_2 \frac{di}{dt} = (L_1 + L_2) \frac{di}{dt}$$







- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



$$\frac{di}{dt} = \frac{d(i_1 + i_2)}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} \\ = \frac{v}{L_1} + \frac{v}{L_2} = v\left(\frac{1}{L_1} + \frac{1}{L_2}\right) \\ v = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} \frac{di}{dt}$$





Same as a single inductor of value 
$$\frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$$

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

 $v = v_1 + v_2 = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$  $= (L_1 + L_2) \frac{di}{dt}$ 





Same as a single inductor of value 
$$\frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} = \frac{L_1 L_2}{L_1 + L_2}$$

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



Same equation as a single inductor of value  $L_1 + L_2$ 





Same as a single inductor of value  $\frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} = \frac{L_1 L_2}{L_1 + L_2}$ 

Inductors combine just like resistors.

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

#### Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary





- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

#### Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

$$i = i_1 + i_2 = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt}$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

$$i = i_1 + i_2 = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt}$$
$$= (C_1 + C_2) \frac{dv}{dt}$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

 $i = i_1 + i_2 = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt}$  $= (C_1 + C_2) \frac{dv}{dt}$ 



Same equation as a single capacitor of value  $C_1 + C_2$ 

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

$$i = i_1 + i_2 = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt}$$
$$= (C_1 + C_2) \frac{dv}{dt}$$



#### Same equation as a single capacitor of value $C_1 + C_2$




- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

 $i = i_1 + i_2 = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt}$  $= (C_1 + C_2) \frac{dv}{dt}$ 



#### Same equation as a single capacitor of value $C_1 + C_2$

$$\frac{dv}{dt} = \frac{d(v_1 + v_2)}{dt} = \frac{dv_1}{dt} + \frac{dv_2}{dt}$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

 $i = i_1 + i_2 = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt}$  $= (C_1 + C_2) \frac{dv}{dt}$ 



#### Same equation as a single capacitor of value $C_1 + C_2$

$$\frac{dv}{dt} = \frac{d(v_1 + v_2)}{dt} = \frac{dv_1}{dt} + \frac{dv_2}{dt} = \frac{i}{C_1} + \frac{i}{C_2} = i\left(\frac{1}{C_1} + \frac{1}{C_2}\right)$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

$$i = i_1 + i_2 = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt}$$
$$= (C_1 + C_2) \frac{dv}{dt}$$



#### Same equation as a single capacitor of value $C_1 + C_2$

$$\frac{dv}{dt} = \frac{d(v_1 + v_2)}{dt} = \frac{dv_1}{dt} + \frac{dv_2}{dt}$$
$$= \frac{i}{C_1} + \frac{i}{C_2} = i\left(\frac{1}{C_1} + \frac{1}{C_2}\right)$$
$$i = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}\frac{dv}{dt}$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

 $i = i_1 + i_2 = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt}$  $= (C_1 + C_2) \frac{dv}{dt}$ 



#### Same equation as a single capacitor of value $C_1 + C_2$

$$\frac{dv}{dt} = \frac{d(v_1 + v_2)}{dt} = \frac{dv_1}{dt} + \frac{dv_2}{dt}$$
$$= \frac{i}{C_1} + \frac{i}{C_2} = i\left(\frac{1}{C_1} + \frac{1}{C_2}\right)$$
$$\vdots \qquad 1 \qquad dv$$

$$i = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \frac{dv}{dt}$$

Same as a single capacitor of value  $\frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$ 



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

 $i = i_1 + i_2 = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt}$  $= (C_1 + C_2) \frac{dv}{dt}$ 



#### Same equation as a single capacitor of value $C_1 + C_2$

$$\frac{dv}{dt} = \frac{d(v_1 + v_2)}{dt} = \frac{dv_1}{dt} + \frac{dv_2}{dt} = \frac{i}{C_1} + \frac{i}{C_2} = i\left(\frac{1}{C_1} + \frac{1}{C_2}\right)$$

$$i = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \frac{dv}{dt}$$

Same as a single capacitor of value  $\frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2}$ 



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary





#### Same equation as a single capacitor of value $C_1 + C_2$



Capacitors combine just like conductances (i.e. parallel capacitors add).

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary





- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



For the voltage to change abruptly

 $\frac{dv}{dt} = \infty \Rightarrow i = \infty.$ 



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors

  Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



For the voltage to change abruptly

 $\frac{dv}{dt} = \infty \Rightarrow i = \infty.$ 

#### This never happens so ...



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



For the voltage to change abruptly

 $\frac{dv}{dt} = \infty \Rightarrow i = \infty.$ 



The voltage across a capacitor never changes instantaneously.



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



For the voltage to change abruptly

 $\frac{dv}{dt} = \infty \Rightarrow i = \infty.$ 





The voltage across a capacitor never changes instantaneously. Informal version: A capacitor "tries" to keep its voltage constant.

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



For the voltage to change abruptly

 $\frac{dv}{dt} = \infty \Rightarrow i = \infty.$ 





The voltage across a capacitor never changes instantaneously. Informal version: A capacitor "tries" to keep its voltage constant.

Inductor: 
$$v = L \frac{di}{dt}$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Capacitor:  $i = C \frac{dv}{dt}$ 

For the voltage to change abruptly

 $\frac{dv}{dt} = \infty \Rightarrow i = \infty.$ 





The voltage across a capacitor never changes instantaneously. Informal version: A capacitor "tries" to keep its voltage constant.

Inductor:  $v = L \frac{di}{dt}$ 

For the current to change abruptly

$$\frac{di}{dt} = \infty \Rightarrow v = \infty.$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



For the voltage to change abruptly

 $\frac{dv}{dt} = \infty \Rightarrow i = \infty.$ 





The voltage across a capacitor never changes instantaneously. Informal version: A capacitor "tries" to keep its voltage constant.

Inductor:  $v = L \frac{di}{dt}$ 

For the current to change abruptly

$$\frac{di}{dt} = \infty \Rightarrow v = \infty$$

This never happens so ...



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



For the voltage to change abruptly

 $\frac{dv}{dt} = \infty \Rightarrow i = \infty.$ 





The voltage across a capacitor never changes instantaneously. Informal version: A capacitor "tries" to keep its voltage constant.

Inductor:  $v = L \frac{di}{dt}$ 

For the current to change abruptly

$$\frac{di}{dt} = \infty \Rightarrow v = \infty.$$

This never happens so ...

The current through an inductor never changes instantaneously.



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



For the voltage to change abruptly

 $\frac{dv}{dt} = \infty \Rightarrow i = \infty.$ 





The voltage across a capacitor never changes instantaneously. Informal version: A capacitor "tries" to keep its voltage constant.

Inductor:  $v = L \frac{di}{dt}$ 

For the current to change abruptly

$$\frac{di}{dt} = \infty \Rightarrow v = \infty.$$

This never happens so ...

The current through an inductor never changes instantaneously. Informal version: An inductor "tries" to keep its current constant.



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel Capacitors
- Current/Voltage ContinuityAverage Current/Voltage
- Buck Converter
- Power and Energy
- Summary





- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel

Inductors

Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

$$\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} i dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} C \frac{dv}{dt} dt$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel

Inductors

Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

$$\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} i dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} C \frac{dv}{dt} dt = \frac{C}{t_2 - t_1} \int_{v(t_1)}^{v(t_2)} dv$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel

Inductors

Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

$$\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} i dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} C \frac{dv}{dt} dt = \frac{C}{t_2 - t_1} \int_{v(t_1)}^{v(t_2)} dv$$

$$= \frac{C}{t_2 - t_1} \left[ v \right]_{v(t_1)}^{v(t_2)}$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel

Inductors

• Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

$$\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} i dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} C \frac{dv}{dt} dt = \frac{C}{t_2 - t_1} \int_{v(t_1)}^{v(t_2)} dv$$

$$= \frac{C}{t_2 - t_1} \left[ v \right]_{v(t_1)}^{v(t_2)} = \frac{C}{t_2 - t_1} \left( v(t_2) - v(t_1) \right)$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

For a capacitor  $i = C \frac{dv}{dt}$ . Take the average of both sides:

$$\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} i dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} C \frac{dv}{dt} dt = \frac{C}{t_2 - t_1} \int_{v(t_1)}^{v(t_2)} dv$$

$$= \frac{C}{t_2 - t_1} \left[ v \right]_{v(t_1)}^{v(t_2)} = \frac{C}{t_2 - t_1} \left( v(t_2) - v(t_1) \right)$$

(1) If  $v(t_1) = v(t_2)$  then the average current exactly equals zero.



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

$$\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} i dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} C \frac{dv}{dt} dt = \frac{C}{t_2 - t_1} \int_{v(t_1)}^{v(t_2)} dv$$

$$= \frac{C}{t_2 - t_1} \left[ v \right]_{v(t_1)}^{v(t_2)} = \frac{C}{t_2 - t_1} \left( v(t_2) - v(t_1) \right)$$

- (1) If  $v(t_1) = v(t_2)$  then the average current exactly equals zero.
- (2) If v is bounded then the average current  $\rightarrow 0$  as  $(t_2 t_1) \rightarrow \infty$ .



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

For a capacitor  $i = C \frac{dv}{dt}$ . Take the average of both sides:

$$\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} i dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} C \frac{dv}{dt} dt = \frac{C}{t_2 - t_1} \int_{v(t_1)}^{v(t_2)} dv$$

$$= \frac{C}{t_2 - t_1} \left[ v \right]_{v(t_1)}^{v(t_2)} = \frac{C}{t_2 - t_1} \left( v(t_2) - v(t_1) \right)$$

- (1) If  $v(t_1) = v(t_2)$  then the average current exactly equals zero.
- (2) If v is bounded then the average current  $\rightarrow 0$  as  $(t_2 t_1) \rightarrow \infty$ .



#### The average current through a capacitor is zero

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

For a capacitor  $i = C \frac{dv}{dt}$ . Take the average of both sides:

$$\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} i dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} C \frac{dv}{dt} dt = \frac{C}{t_2 - t_1} \int_{v(t_1)}^{v(t_2)} dv$$

$$= \frac{C}{t_2 - t_1} \left[ v \right]_{v(t_1)}^{v(t_2)} = \frac{C}{t_2 - t_1} \left( v(t_2) - v(t_1) \right)$$

(1) If v(t<sub>1</sub>) = v(t<sub>2</sub>) then the average current exactly equals zero.
(2) If v is bounded then the average current → 0 as (t<sub>2</sub> - t<sub>1</sub>) → ∞.



The average current through a capacitor is zero and, likewise, the average voltage across an inductor is zero.

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

For a capacitor  $i = C \frac{dv}{dt}$ . Take the average of both sides:

$$\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} i dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} C \frac{dv}{dt} dt = \frac{C}{t_2 - t_1} \int_{v(t_1)}^{v(t_2)} dv$$

$$= \frac{C}{t_2 - t_1} \left[ v \right]_{v(t_1)}^{v(t_2)} = \frac{C}{t_2 - t_1} \left( v(t_2) - v(t_1) \right)$$





The average current through a capacitor is zero and, likewise, the average voltage across an inductor is zero. The circuit symbols remind you of this.

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary



$$\frac{1}{t_2 - t_1} \int_{t_1}^{t_2} i dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} C \frac{dv}{dt} dt = \frac{C}{t_2 - t_1} \int_{v(t_1)}^{v(t_2)} dv$$

$$= \frac{C}{t_2 - t_1} \left[ v \right]_{v(t_1)}^{v(t_2)} = \frac{C}{t_2 - t_1} \left( v(t_2) - v(t_1) \right)$$



(1) If v(t<sub>1</sub>) = v(t<sub>2</sub>) then the average current exactly equals zero.
(2) If v is bounded then the average current → 0 as (t<sub>2</sub> - t<sub>1</sub>) → ∞.



The average current through a capacitor is zero and, likewise, the average voltage across an inductor is zero. The circuit symbols remind you of this.

"Average" can either be over an exact number of periods of a repetitive waveform or else the long-term average (provided v and i remain bounded).

"v is bounded" means |v| always stays less than a predefined maximum value.

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

A buck converter converts a high voltage, V, into a lower one, Y.

The switch, *S*, closes for a fraction *a* of the time. *a* is the *duty cycle* and is  $\frac{1}{3}$  in this example.





#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

A buck converter converts a high voltage, V, into a lower one, Y.

The switch, *S*, closes for a fraction *a* of the time. *a* is the *duty cycle* and is  $\frac{1}{3}$  in this example.

When S is closed, x = v, and a current  $i_L$  flows.





#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

A buck converter converts a high voltage, V, into a lower one, Y.

The switch, *S*, closes for a fraction *a* of the time. *a* is the *duty cycle* and is  $\frac{1}{3}$  in this example.

When S is closed, x = v, and a current  $i_L$  flows. When S opens, the current  $i_L$  cannot change instantly and so it must flow through the diode (we assume the diode is ideal).





#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

A buck converter converts a high voltage, V, into a lower one, Y.

The switch, *S*, closes for a fraction *a* of the time. *a* is the *duty cycle* and is  $\frac{1}{3}$  in this example.

When S is closed, x = v, and a current  $i_L$  flows. When S opens, the current  $i_L$  cannot change instantly and so it must flow through the diode (we assume the diode is ideal).

The average value of x is  $aV \Rightarrow$  the average value of y must also be aV.





#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

A buck converter converts a high voltage, V, into a lower one, Y.

The switch, *S*, closes for a fraction *a* of the time. *a* is the *duty cycle* and is  $\frac{1}{3}$  in this example.

When S is closed, x = v, and a current  $i_L$  flows. When S opens, the current  $i_L$  cannot change instantly and so it must flow through the diode (we assume the diode is ideal).





The average value of x is  $aV \Rightarrow$  the average value of y must also be aV.

The average current through R is  $\frac{aV}{R}$  so, since the average current through C must be zero, the average current  $i_L$  must also be  $\frac{aV}{R}$ .

#### 9: Capacitors and Inductors

- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

A buck converter converts a high voltage, V, into a lower one, Y.

The switch, *S*, closes for a fraction *a* of the time. *a* is the *duty cycle* and is  $\frac{1}{3}$  in this example.

When S is closed, x = v, and a current  $i_L$  flows. When S opens, the current  $i_L$  cannot change instantly and so it must flow through the diode (we assume the diode is ideal).





The average value of x is  $aV \Rightarrow$  the average value of y must also be aV.

The average current through R is  $\frac{aV}{R}$  so, since the average current through C must be zero, the average current  $i_L$  must also be  $\frac{aV}{R}$ .

 $C\frac{dy}{dt} = i_L - i_R \Rightarrow$  if C is large, then the variations in y will be very small.

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

#### [Do not memorize this circuit]

A buck converter converts a high voltage, V, into a lower one, Y.

The switch, *S*, closes for a fraction *a* of the time. *a* is the *duty cycle* and is  $\frac{1}{3}$  in this example.

When S is closed, x = v, and a current  $i_L$  flows. When S opens, the current  $i_L$  cannot change instantly and so it must flow through the diode (we assume the diode is ideal).





The average value of x is  $aV \Rightarrow$  the average value of y must also be aV.

The average current through R is  $\frac{aV}{R}$  so, since the average current through C must be zero, the average current  $i_L$  must also be  $\frac{aV}{R}$ .

 $C\frac{dy}{dt} = i_L - i_R \Rightarrow$  if C is large, then the variations in y will be very small.

# **Power and Energy**

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors

  Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Electrical power absorbed by any component at the instant t is  $v(t) \times i(t)$ .

# **Power and Energy**

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Electrical power absorbed by any component at the instant t is  $v(t) \times i(t)$ . So total energy absorbed between times  $t_1$  and  $t_2$  is  $W = \int_{t=t_1}^{t_2} vi \, dt$ .
- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

For a capacitor 
$$i=Crac{dv}{dt}$$
, so

$$V = C \int_{t=t_1}^{t_2} v \frac{dv}{dt} dt$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

For a capacitor 
$$i=Crac{dv}{dt}$$
, so

$$W = C \int_{t=t_1}^{t_2} v \frac{dv}{dt} dt = C \int_{v=v(t_1)}^{v(t_2)} v dv$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

For a capacitor 
$$i=Crac{dv}{dt}$$
, so

$$W = C \int_{t=t_1}^{t_2} v \frac{dv}{dt} dt = C \int_{v=v(t_1)}^{v(t_2)} v dv$$





- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

For a capacitor 
$$i=Crac{dv}{dt}$$
, so

$$V = C \int_{t=t_1}^{t_2} v \frac{dv}{dt} dt = C \int_{v=v(t_1)}^{v(t_2)} v dv$$

$$= C \left[\frac{1}{2}v^2\right]_{v(t_1)}^{v(t_2)} = \frac{1}{2}C \left(v^2(t_2) - v^2(t_1)\right)$$



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

So total energy absorbed between times  $t_1$  and  $t_2$  is  $W = \int_{t=t_1}^{t_2} vi dt$ . For a capacitor  $i = C \frac{dv}{dt}$ , so  $W = C \int_{t=t_1}^{t_2} v \frac{dv}{dt} dt = C \int_{v=v(t_1)}^{v(t_2)} v dv$  $= C \left[\frac{1}{2}v^2\right]_{v(t_1)}^{v(t_2)} = \frac{1}{2}C \left(v^2(t_2) - v^2(t_1)\right)$ 

Electrical power absorbed by any component at the instant t is  $v(t) \times i(t)$ .



If  $v(t_1) = v(t_2)$  then there has been no nett energy absorbed: all the energy absorbed when the voltage rises is returned to the circuit when it falls.



- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

So total energy absorbed between times  $t_1$  and  $t_2$  is  $W = \int_{t=t_1}^{t_2} vi \, dt$ . For a capacitor  $i = C \frac{dv}{dt}$ , so  $W = C \int_{t=t_1}^{t_2} v \frac{dv}{dt} dt = C \int_{v=v(t_1)}^{v(t_2)} v dv$ 

Electrical power absorbed by any component at the instant t is  $v(t) \times i(t)$ .



If  $v(t_1) = v(t_2)$  then there has been no nett energy absorbed: all the energy absorbed when the voltage rises is returned to the circuit when it falls.

v(t)

The energy stored in a capacitor is  $\frac{1}{2}Cv^2$ 



И

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Electrical power absorbed by any component at the instant t is  $v(t) \times i(t)$ . So total energy absorbed between times  $t_1$  and  $t_2$  is  $W = \int_{t=t_1}^{t_2} vi \, dt$ .

For a capacitor 
$$i = C \frac{dv}{dt}$$
, so

$$V = C \int_{t=t_1}^{t_2} v \frac{dv}{dt} dt = C \int_{v=v(t_1)}^{v(t_2)} v dv$$

$$= C \left[\frac{1}{2}v^2\right]_{v(t_1)}^{v(t_2)} = \frac{1}{2}C \left(v^2(t_2) - v^2(t_1)\right)$$

If  $v(t_1) = v(t_2)$  then there has been no nett energy absorbed: all the energy absorbed when the voltage rises is returned to the circuit when it falls.



The energy stored in a capacitor is  $\frac{1}{2}Cv^2$  and likewise in an inductor  $\frac{1}{2}Li^2$ .

И

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

Electrical power absorbed by any component at the instant t is  $v(t) \times i(t)$ . So total energy absorbed between times  $t_1$  and  $t_2$  is  $W = \int_{t=t_1}^{t_2} vi \, dt$ .

For a capacitor 
$$i = C \frac{dv}{dt}$$
, so

$$V = C \int_{t=t_1}^{t_2} v \frac{dv}{dt} dt = C \int_{v=v(t_1)}^{v(t_2)} v dv$$

$$= C \left[\frac{1}{2}v^2\right]_{v(t_1)}^{v(t_2)} = \frac{1}{2}C \left(v^2(t_2) - v^2(t_1)\right)$$

If  $v(t_1) = v(t_2)$  then there has been no nett energy absorbed: all the energy absorbed when the voltage rises is returned to the circuit when it falls.





The energy stored in a capacitor is  $\frac{1}{2}Cv^2$  and likewise in an inductor  $\frac{1}{2}Li^2$ .

If v and i remain bounded, then the average power absorbed by a capacitor or inductor is always zero.

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

• Capacitor:

$$\circ \quad i = C \frac{dv}{dt}$$

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

• Capacitor:

$$\circ \quad i = C \frac{dv}{dt}$$

parallel capacitors add in value

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel
- Inductors

  Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

- Capacitor:
  - $\circ \quad i = C \frac{dv}{dt}$
  - parallel capacitors add in value
  - $\circ$  average *i* is zero, *v* never changes instantaneously.

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

- Capacitor:
  - $\circ \quad i = C \frac{dv}{dt}$
  - parallel capacitors add in value
  - $\circ$  average *i* is zero, *v* never changes instantaneously.
  - average power absorbed is zero

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel

Capacitors

- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

• Capacitor:

$$\circ \quad i = C \frac{dv}{dt}$$

- parallel capacitors add in value
- $\circ$  average *i* is zero, *v* never changes instantaneously.
- average power absorbed is zero
- Inductor:

$$\circ \quad v = L \frac{di}{dt}$$

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

- Capacitor:
  - $\circ \quad i = C \frac{dv}{dt}$
  - parallel capacitors add in value
  - $\circ$  average *i* is zero, *v* never changes instantaneously.
  - average power absorbed is zero
- Inductor:
  - $\circ \quad v = L \frac{di}{dt}$
  - series inductors add in value (like resistors)

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

- Capacitor:
  - $\circ \quad i = C \frac{dv}{dt}$
  - parallel capacitors add in value
  - $\circ$  average *i* is zero, *v* never changes instantaneously.
  - average power absorbed is zero
- Inductor:
  - $\circ \quad v = L \frac{di}{dt}$
  - series inductors add in value (like resistors)
  - $\circ$  average v is zero, i never changes instantaneously.

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

- Capacitor:
  - $\circ \quad i = C \frac{dv}{dt}$
  - parallel capacitors add in value
  - $\circ$  average *i* is zero, *v* never changes instantaneously.
  - average power absorbed is zero
- Inductor:
  - $\circ \quad v = L \frac{di}{dt}$
  - series inductors add in value (like resistors)
  - $\circ$  average v is zero, i never changes instantaneously.
  - average power absorbed is zero

- 9: Capacitors and Inductors
- Capacitors
- Types of Capacitor
- Inductors
- Passive Components
- Series and Parallel Inductors
- Series and Parallel
- Capacitors
- Current/Voltage Continuity
- Average Current/Voltage
- Buck Converter
- Power and Energy
- Summary

- Capacitor:
  - $\circ \quad i = C \frac{dv}{dt}$
  - parallel capacitors add in value
  - $\circ$  average *i* is zero, *v* never changes instantaneously.
  - average power absorbed is zero
- Inductor:
  - $\circ \quad v = L \frac{di}{dt}$
  - series inductors add in value (like resistors)
  - $\circ$  average v is zero, i never changes instantaneously.
  - average power absorbed is zero

For further details see Hayt Ch 7 or Irwin Ch 6.