

▷ **10: Sine waves
and phasors**

Sine Waves

Rotating Rod

Phasors

Phasor Examples +

Phasor arithmetic

Complex Impedances

Phasor Analysis +

CIVIL

**Impedance and
Admittance**

Summary

10: Sine waves and phasors

Sine Waves

10: Sine waves and phasors

▷ Sine Waves

Rotating Rod

Phasors

Phasor Examples +

Phasor arithmetic

Complex Impedances

Phasor Analysis +

CIVIL

Impedance and Admittance

Summary

For inductors and capacitors $i = C \frac{dv}{dt}$ and $v = L \frac{di}{dt}$ so we need to differentiate $i(t)$ and $v(t)$ when analysing circuits containing them.

Usually differentiation changes the shape of a waveform.

For bounded waveforms there is only one exception:





$v(t) = \sin t \Rightarrow \frac{dv}{dt} = \cos t$
same shape but with a time shift.

$\sin t$ completes one full period every time t increases by 2π .

$\sin 2\pi ft$ makes f complete repetitions every time t increases by 1; this gives a **frequency** of f cycles per second, or f Hz.

We often use the **angular frequency**, $\omega = 2\pi f$ instead.

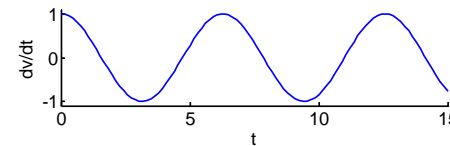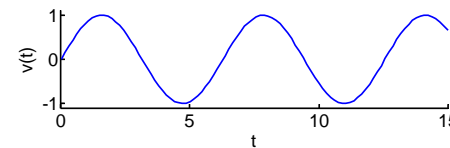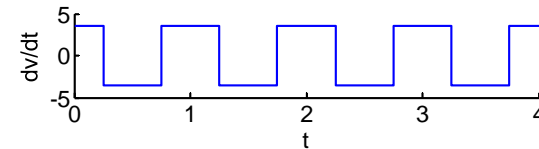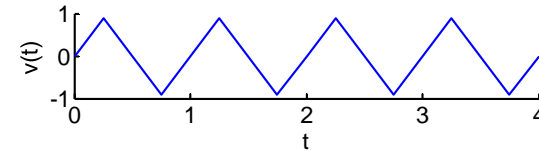ω is measured in **radians per second**. E.g. $50 \text{ Hz} \simeq 314 \text{ rad.s}^{-1}$.



Rotating Rod

10: Sine waves and phasors

Sine Waves

▷ Rotating Rod

Phasors

Phasor Examples +

Phasor arithmetic

Complex Impedances

Phasor Analysis +

CIVIL

Impedance and Admittance

Summary



A useful way to think of a cosine wave is as the projection of a rotating rod onto the horizontal axis.

For a unit-length rod, the projection has length $\cos \theta$.


If the rod is rotating at a speed of f revolutions per second, then θ increases uniformly with time:

$$\theta = 2\pi ft.$$

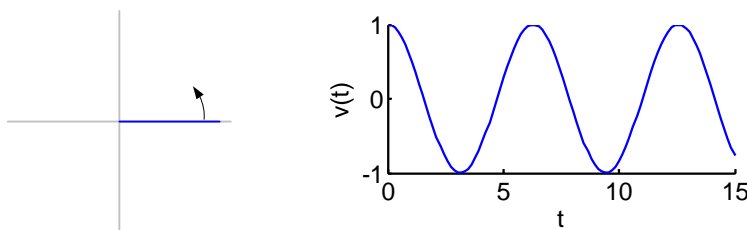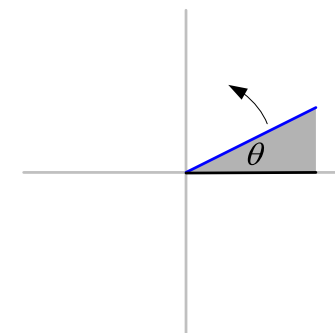The only difference between \cos and \sin is the starting position of the rod:



$$v = \cos 2\pi ft$$

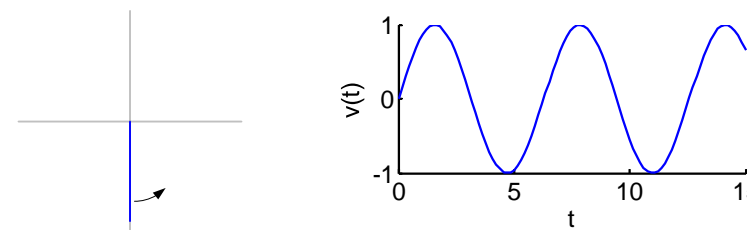

$$v = \sin 2\pi ft = \cos \left(2\pi ft - \frac{\pi}{2} \right)$$

$\sin 2\pi ft$ *lags* $\cos 2\pi ft$ by 90° (or $\frac{\pi}{2}$ radians) because its peaks occurs $\frac{1}{4}$ of a cycle later (equivalently \cos *leads* \sin).

Phasors

10: Sine waves and phasors

Sine Waves

Rotating Rod

▷ Phasors

Phasor Examples +

Phasor arithmetic

Complex Impedances

Phasor Analysis +

CIVIL


Impedance and Admittance

Summary

If the rod has length A and starts at an angle ϕ then the projection onto the horizontal axis is

$$\begin{aligned} & A \cos(2\pi ft + \phi) \\ &= A \cos \phi \cos 2\pi ft - A \sin \phi \sin 2\pi ft \\ &= X \cos 2\pi ft - Y \sin 2\pi ft \end{aligned}$$

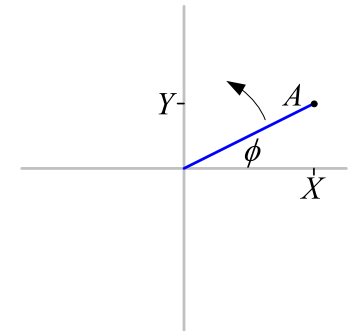At time $t = 0$, the tip of the rod has coordinates $(X, Y) = (A \cos \phi, A \sin \phi)$.



If we think of the plane as an Argand Diagram (or complex plane), then the complex number $X + jY$ corresponding to the tip of the rod at $t = 0$ is called a *phasor*.

The *magnitude* of the phasor, $A = \sqrt{X^2 + Y^2}$, gives the amplitude (peak value) of the sine wave.

The *argument* of the phasor, $\phi = \arctan \frac{Y}{X}$, gives the phase shift relative to $\cos 2\pi ft$.

If $\phi > 0$, it is *leading* and if $\phi < 0$, it is *lagging* relative to $\cos 2\pi ft$.

- 10: Sine waves and phasors
- Sine Waves
- Rotating Rod
- Phasors
- ▷ Phasor Examples +
- Phasor arithmetic
- Complex Impedances
- Phasor Analysis +
- CIVIL
- Impedance and Admittance
- Summary

$$V = 1, f = 50 \text{ Hz}$$

$$v(t) = \cos 2\pi ft$$

$$V = -j$$

$$v(t) = \sin 2\pi ft$$

$$V = -1 - 0.5j = 1.12 \angle -153^\circ$$


$$v(t) = -\cos 2\pi ft + 0.5 \sin 2\pi ft$$

$$= 1.12 \cos(2\pi ft - 2.68)$$

$$V = X + jY$$

$$v(t) = X \cos 2\pi ft - Y \sin 2\pi ft$$

Beware minus sign.

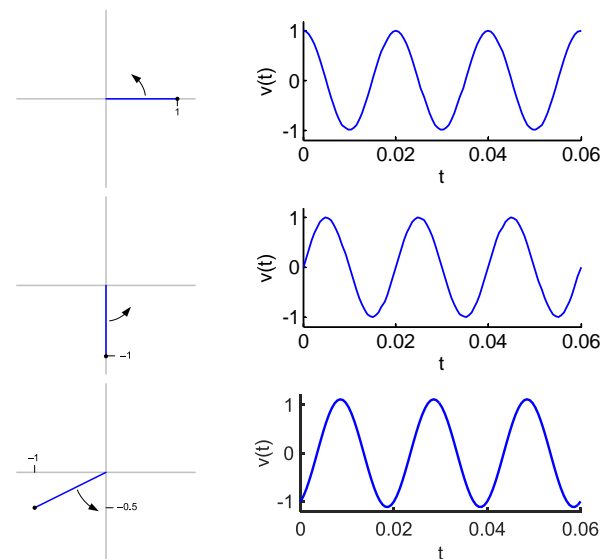

$$V = A \angle \phi = Ae^{j\phi}$$

$$v(t) = A \cos(2\pi ft + \phi)$$

A phasor represents an entire waveform (encompassing all time) as a single complex number. We assume the frequency, f , is known.

A phasor is not time-varying, so we use a capital letter: V .
 A waveform is time-varying, so we use a small letter: $v(t)$.

Casio: $\text{Pol}(X, Y) \rightarrow A, \phi$, $\text{Rec}(A, \phi) \rightarrow X, Y$. Saved $\rightarrow X$ & Y mems.

[Algebraic Phasor ↔ Waveform Mapping]

A phasor is a complex number, V , that uniquely defines a waveform, $v(t)$, via the mapping $V = Ae^{j\phi} \longleftrightarrow v(t) = A \cos(2\pi ft + \phi)$. It is sometimes convenient to give an algebraic formula for this.

For the direction $V \longrightarrow v(t)$ the mapping is easy:

$$v(t) = \Re(Ve^{j2\pi ft}) = \frac{1}{2}(V + V^*) \cos 2\pi ft + \frac{1}{2}j(V - V^*) \sin 2\pi ft.$$

The reverse mapping, $V \longleftarrow v(t)$ is a bit more complicated and we use a technique that you will also use in the Maths of Fourier transforms. The mapping is given by

$$V = 2f \int_0^{\frac{1}{f}} v(t)e^{-j2\pi ft} dt.$$

To confirm that this is true, we can substitute $v(t) = A \cos(2\pi ft + \phi)$ and do the integration:

$$\begin{aligned} 2f \int_0^{\frac{1}{f}} v(t)e^{-j2\pi ft} dt &= Af \int_0^{\frac{1}{f}} \left(e^{j(2\pi ft + \phi)} + e^{-j(2\pi ft + \phi)} \right) e^{-j2\pi ft} dt \\ &= Af \int_0^{\frac{1}{f}} \left(e^{j\phi} + e^{-j4\pi ft - j\phi} \right) dt = Ae^{j\phi} + Afe^{-j\phi} \int_0^{\frac{1}{f}} e^{-j4\pi ft} dt \\ &= Ae^{j\phi} + \frac{Afe^{-j\phi}}{-j4\pi f} \left[e^{-j4\pi ft} \right]_0^{\frac{1}{f}} = Ae^{j\phi} + \frac{Afe^{-j\phi}}{-j4\pi f} (e^{-j4\pi} - 1) = Ae^{j\phi} \end{aligned}$$

Phasor arithmetic

10: Sine waves and phasors

Sine Waves

Rotating Rod

Phasors

Phasor Examples +

▷ Phasor arithmetic

Complex Impedances

Phasor Analysis +

CIVIL

Impedance and Admittance

Summary

Phasors

$$V = P + jQ$$

$$aV$$

$$V_1 + V_2$$

Waveforms

$$v(t) = P \cos \omega t - Q \sin \omega t$$

where $\omega = 2\pi f$.

$$a \times v(t) = aP \cos \omega t - aQ \sin \omega t$$

$$v_1(t) + v_2(t)$$


Adding or scaling is the same for waveforms and phasors.

$$\begin{aligned}\dot{V} &= (-\omega Q) + j(\omega P) \\ &= j\omega(P + jQ) \\ &= j\omega V\end{aligned}$$

$$\begin{aligned}\frac{dv}{dt} &= -\omega P \sin \omega t - \omega Q \cos \omega t \\ &= (-\omega Q) \cos \omega t - (\omega P) \sin \omega t\end{aligned}$$

Differentiating waveforms corresponds to multiplying phasors by $j\omega$.

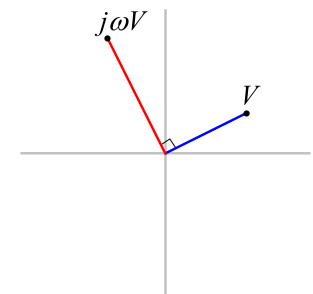Rotate anti-clockwise 90° and scale by $\omega = 2\pi f$.



Complex Impedances

10: Sine waves and phasors

Sine Waves

Rotating Rod

Phasors

Phasor Examples +

Phasor arithmetic

Complex

▷ Impedances

Phasor Analysis +


CIVIL

Impedance and Admittance

Summary


Resistor:
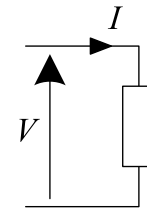
$$v(t) = Ri(t) \Rightarrow V = RI \quad \Rightarrow \frac{V}{I} = R$$




Inductor:
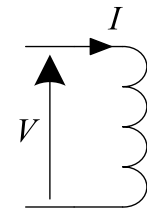
$$v(t) = L \frac{di}{dt} \Rightarrow V = j\omega LI \quad \Rightarrow \frac{V}{I} = j\omega L$$



Capacitor:
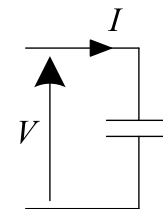
$$i(t) = C \frac{dv}{dt} \Rightarrow I = j\omega CV \quad \Rightarrow \frac{V}{I} = \frac{1}{j\omega C}$$



For all three components, phasors obey Ohm's law if we use the *complex impedances* $j\omega L$ and $\frac{1}{j\omega C}$ as the "resistance" of an inductor or capacitor.

If all sources in a circuit are sine waves having the same frequency, we can do circuit analysis exactly as before by using complex impedances.

- 10: Sine waves and phasors
- Sine Waves
- Rotating Rod
- Phasors
- Phasor Examples +
- Phasor arithmetic
- Complex Impedances
- ▷ Phasor Analysis +
- CIVIL
- Impedance and Admittance
- Summary

Given $v = 10 \sin \omega t$ where $\omega = 2\pi \times 1000$, find $v_C(t)$.

(1) Find capacitor complex impedance

$$Z = \frac{1}{j\omega C} = \frac{1}{6.28j \times 10^{-4}} = -1592j$$




(2) Solve circuit with phasors

$$\begin{aligned} V_C &= V \times \frac{Z}{R+Z} \\ &= -10j \times \frac{-1592j}{1000-1592j} \\ &= -4.5 - 7.2j = 8.47 \angle -122^\circ \\ v_C &= 8.47 \cos(\omega t - 122^\circ) \end{aligned}$$

(3) Draw a *phasor diagram* showing KVL:

$$\begin{aligned} V &= -10j \\ V_C &= -4.5 - 7.2j \\ V_R &= V - V_C = 4.5 - 2.8j = 5.3 \angle -32^\circ \end{aligned}$$

Phasors add like vectors

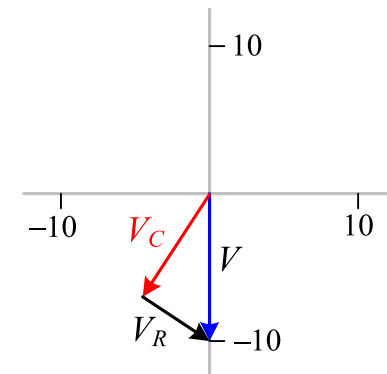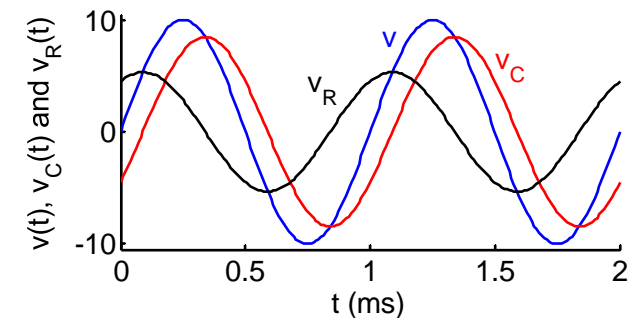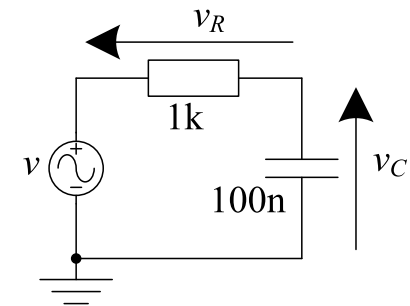

[Differential Equation Analysis]

To solve the problem from the previous slide without using phasors, we define i to be the current flowing clockwise and use the capacitor equation $i = C \frac{dv_C}{dt}$.

From KVL, we have $v = v_R + v_C = iR + v_C$.

Differentiating and applying the capacitor equation gives $\frac{dv}{dt} = 10\omega \cos \omega t = R \frac{di}{dt} + \frac{1}{C}i$.

We need to find the particular integral for the above equation. To do so, we guess that the answer will be of the form $i = A \cos \omega t + B \sin \omega t$ and substitute it into the equation (multiplied by C).

$$\begin{aligned} 10C\omega \cos \omega t &= RC(-A\omega \sin \omega t + B\omega \cos \omega t) + (A \cos \omega t + B \sin \omega t) \\ &= (A + RC B\omega) \cos \omega t + (B - RC A\omega) \sin \omega t \end{aligned}$$

which gives two simultaneous equations: $A + RC\omega B = 10C\omega$ and $-RC\omega A + B = 0$. Substituting values for R , C and ω gives $A + 0.628B = 0.00628$ and $-0.628A + B = 0$. Solving these simultaneous equations gives $A = 4.5 \text{ mA}$ and $B = 2.8 \text{ mA}$.

The resistor voltage is therefore $v_R = iR = 4.5 \cos \omega t + 2.8 \sin \omega t$ and therefore, from KVL, the capacitor voltage is $v_C = v - v_R = -4.5 \cos \omega t + 7.2 \sin \omega t$.

Thus we get the same answer as using phasors but with more work even for a simple circuit like this. For more complicated circuits the difference is much much bigger.

Capacitors: $i = C \frac{dv}{dt} \Rightarrow I \text{ leads } V$

Inductors: $v = L \frac{di}{dt} \Rightarrow V \text{ leads } I$

Mnemonic: **CIVIL** = "In a capacitor I lead V but V leads I in an inductor".

COMPLEX ARITHMETIC TRICKS:

(1) $j \times j = -j \times -j = -1$

(2) $\frac{1}{j} = -j$

(3) $a + jb = r \angle \theta = re^{j\theta}$

where $r = \sqrt{a^2 + b^2}$ and $\theta = \arctan \frac{b}{a}$ ($\pm 180^\circ$ if $a < 0$)

(4) $r \angle \theta = re^{j\theta} = (r \cos \theta) + j (r \sin \theta)$

(5) $a \angle \theta \times b \angle \phi = ab \angle (\theta + \phi)$ and $\frac{a \angle \theta}{b \angle \phi} = \frac{a}{b} \angle (\theta - \phi)$.

Multiplication and division are much easier in polar form.

(6) **All scientific calculators** will convert rectangular to/from polar form.

Casio fx-991 (available in all exams except Maths) will do complex arithmetic ($+$, $-$, \times , \div , x^2 , $\frac{1}{x}$, $|x|$, x^*) in CMPLX mode.

Learn how to use this: it will save lots of time and errors.

Impedance and Admittance

10: Sine waves and phasors

Sine Waves

Rotating Rod

Phasors

Phasor Examples +

Phasor arithmetic

Complex Impedances

Phasor Analysis +

CIVIL

Impedance and

▷ Admittance

Summary

For any network (resistors+capacitors+inductors):

(1) **Impedance** = **Resistance** + $j \times$ **Reactance**

$$Z = R + jX \ (\Omega)$$

$$|Z|^2 = R^2 + X^2 \quad \angle Z = \arctan \frac{X}{R}$$

(2) **Admittance** = $\frac{1}{\text{Impedance}}$ = **Conductance** + $j \times$ **Susceptance**

$$Y = \frac{1}{Z} = G + jB \text{ Siemens (S)}$$

$$|Y|^2 = \frac{1}{|Z|^2} = G^2 + B^2 \quad \angle Y = -\angle Z = \arctan \frac{B}{G}$$

Note:

$$Y = G + jB = \frac{1}{Z} = \frac{1}{R+jX} = \frac{R}{R^2+X^2} + j \frac{-X}{R^2+X^2}$$

$$\text{So } G = \frac{R}{R^2+X^2} = \frac{R}{|Z|^2}$$

$$B = \frac{-X}{R^2+X^2} = \frac{-X}{|Z|^2}$$

Beware: $G \neq \frac{1}{R}$ unless $X = 0$.

Summary

10: Sine waves and phasors

Sine Waves

Rotating Rod

Phasors

Phasor Examples +

Phasor arithmetic

Complex Impedances

Phasor Analysis +

CIVIL

Impedance and Admittance

▷ Summary

- Sine waves are the only bounded signals whose shape is unchanged by differentiation.
- Think of a sine wave as the projection of a rotating rod onto the horizontal (or real) axis.
 - A *phasor* is a complex number representing the length and position of the rod at time $t = 0$.
 - If $V = a + jb = r\angle\theta = re^{j\theta}$, then
$$v(t) = a \cos \omega t - b \sin \omega t = r \cos(\omega t + \theta) = \Re(Ve^{j\omega t})$$
 - The *angular frequency* $\omega = 2\pi f$ is assumed known.
- If **all sources in a linear circuit are sine waves having the same frequency**, we can use phasors for circuit analysis:
 - Use complex impedances: $j\omega L$ and $\frac{1}{j\omega C}$
 - **Mnemonic:** CIVIL tells you whether I leads V or vice versa (“leads” means “reaches its peak before”).
 - Phasors eliminate time from equations 😊, converts simultaneous **differential** equations into simultaneous **linear** equations 😊😊😊.
 - Needs complex numbers 😞 but worth it.

See Hayt Ch 10 or Irwin Ch 8