

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

11: Frequency Responses


Frequency Response

11: Frequency Responses

● Frequency Response

- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

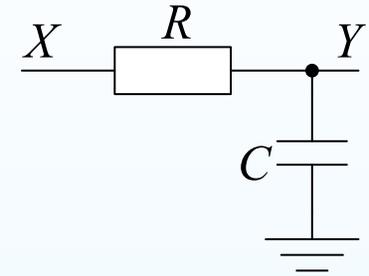If $x(t)$ is a sine wave, then $y(t)$ will also be a sine wave but with a different amplitude and phase shift. X is an input phasor and Y is the output phasor.



Frequency Response

11: Frequency Responses

● Frequency Response

● Sine Wave Response

● Logarithmic axes

● Logs of Powers +

● Straight Line

Approximations

● Plot Magnitude Response

● Low and High Frequency

Asymptotes

● Phase Approximation +


● Plot Phase Response +

● RCR Circuit

● Summary

If $x(t)$ is a sine wave, then $y(t)$ will also be a sine wave but with a different amplitude and phase shift. X is an input phasor and Y is the output phasor.

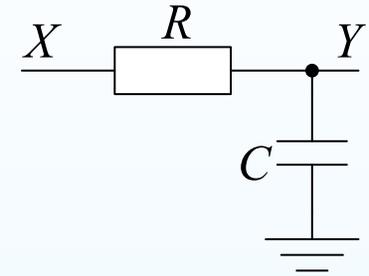The *gain* of the circuit is $\frac{Y}{X} = \frac{1/j\omega C}{R+1/j\omega C} = \frac{1}{j\omega RC+1}$



Frequency Response

11: Frequency Responses

● Frequency Response

● Sine Wave Response

● Logarithmic axes

● Logs of Powers +

● Straight Line

Approximations

● Plot Magnitude Response

● Low and High Frequency

Asymptotes

● Phase Approximation +

● Plot Phase Response +


● RCR Circuit

● Summary

If $x(t)$ is a sine wave, then $y(t)$ will also be a sine wave but with a different amplitude and phase shift. X is an input phasor and Y is the output phasor.

The *gain* of the circuit is $\frac{Y}{X} = \frac{1/j\omega C}{R+1/j\omega C} = \frac{1}{j\omega RC+1}$

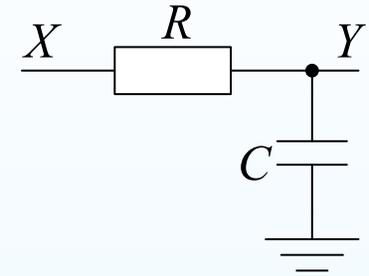This is a complex function of ω so we plot separate graphs for:



Frequency Response

11: Frequency Responses

● Frequency Response

● Sine Wave Response

● Logarithmic axes

● Logs of Powers +

● Straight Line

Approximations

● Plot Magnitude Response

● Low and High Frequency

Asymptotes


● Phase Approximation +

● Plot Phase Response +

● RCR Circuit

● Summary

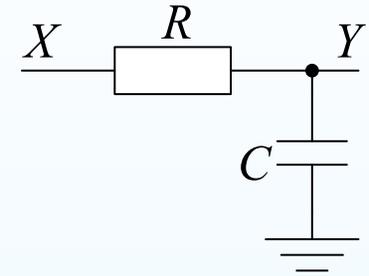If $x(t)$ is a sine wave, then $y(t)$ will also be a sine wave but with a different amplitude and phase shift. X is an input phasor and Y is the output phasor.



The *gain* of the circuit is $\frac{Y}{X} = \frac{1/j\omega C}{R+1/j\omega C} = \frac{1}{j\omega RC+1}$

This is a complex function of ω so we plot separate graphs for:

$$\text{Magnitude: } \left| \frac{Y}{X} \right| = \frac{1}{|j\omega RC+1|} = \frac{1}{\sqrt{1+(\omega RC)^2}}$$

Frequency Response

11: Frequency Responses

● Frequency Response

● Sine Wave Response

● Logarithmic axes

● Logs of Powers +

● Straight Line

Approximations

● Plot Magnitude Response

● Low and High Frequency

Asymptotes


● Phase Approximation +

● Plot Phase Response +

● RCR Circuit

● Summary

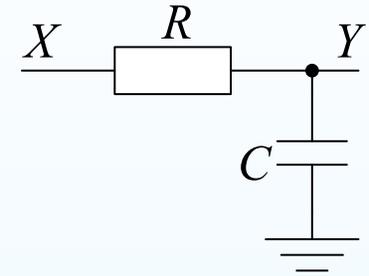
If $x(t)$ is a sine wave, then $y(t)$ will also be a sine wave but with a different amplitude and phase shift. X is an input phasor and Y is the output phasor.



The *gain* of the circuit is $\frac{Y}{X} = \frac{1/j\omega C}{R+1/j\omega C} = \frac{1}{j\omega RC+1}$

This is a complex function of ω so we plot separate graphs for:

$$\text{Magnitude: } \left| \frac{Y}{X} \right| = \frac{1}{|j\omega RC+1|} = \frac{1}{\sqrt{1+(\omega RC)^2}}$$

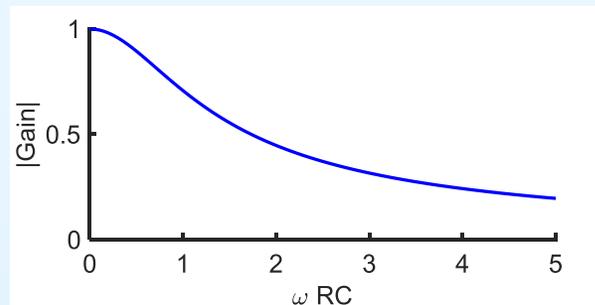

Magnitude Response

Frequency Response

11: Frequency Responses

● Frequency Response

● Sine Wave Response

● Logarithmic axes

● Logs of Powers +

● Straight Line

Approximations

● Plot Magnitude Response

● Low and High Frequency

Asymptotes


● Phase Approximation +

● Plot Phase Response +

● RCR Circuit

● Summary

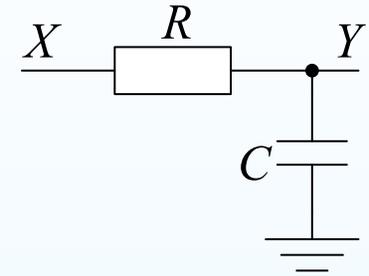If $x(t)$ is a sine wave, then $y(t)$ will also be a sine wave but with a different amplitude and phase shift. X is an input phasor and Y is the output phasor.




The *gain* of the circuit is $\frac{Y}{X} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{j\omega RC + 1}$

This is a complex function of ω so we plot separate graphs for:

$$\text{Magnitude: } \left| \frac{Y}{X} \right| = \frac{1}{|j\omega RC + 1|} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$
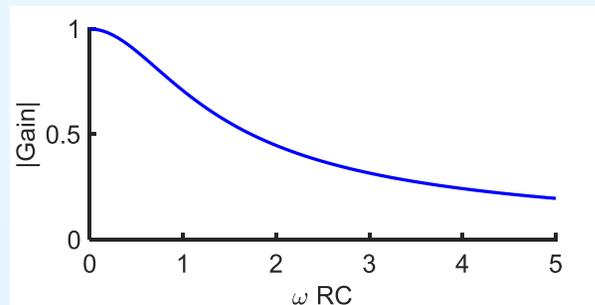
$$\text{Phase Shift: } \angle \left(\frac{Y}{X} \right) = -\angle (j\omega RC + 1) = -\arctan \left(\frac{\omega RC}{1} \right)$$



Magnitude Response

Frequency Response

11: Frequency Responses

● Frequency Response

● Sine Wave Response

● Logarithmic axes

● Logs of Powers

+

● Straight Line

Approximations

● Plot Magnitude Response

● Low and High Frequency

Asymptotes

● Phase Approximation

+


● Plot Phase Response

+

● RCR Circuit

● Summary

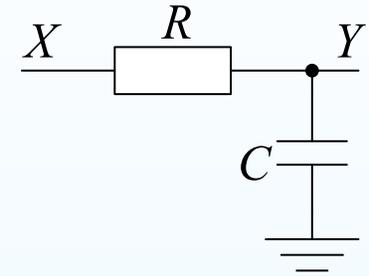If $x(t)$ is a sine wave, then $y(t)$ will also be a sine wave but with a different amplitude and phase shift. X is an input phasor and Y is the output phasor.




The *gain* of the circuit is $\frac{Y}{X} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{j\omega RC + 1}$


This is a complex function of ω so we plot separate graphs for:

$$\text{Magnitude: } \left| \frac{Y}{X} \right| = \frac{1}{|j\omega RC + 1|} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$
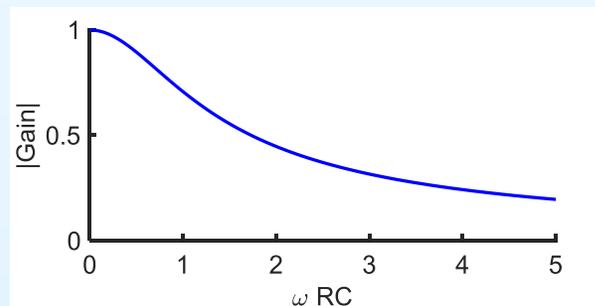
$$\text{Phase Shift: } \angle \left(\frac{Y}{X} \right) = -\angle (j\omega RC + 1) = -\arctan \left(\frac{\omega RC}{1} \right)$$



Magnitude Response

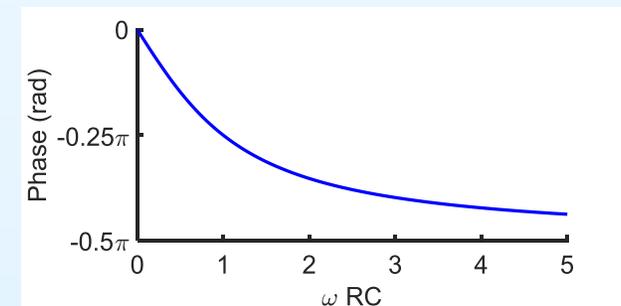

Phase Response


Sine Wave Response

11: Frequency Responses

- Frequency Response
- **Sine Wave Response**
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$RC = 10 \text{ ms}$$
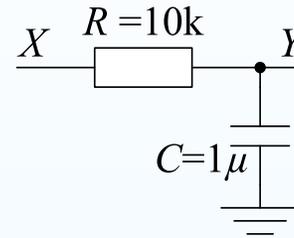
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = \frac{1}{0.01j\omega + 1}$$



$$\omega = 50 \Rightarrow \frac{Y}{X} = 0.89 \angle -27^\circ$$

$$\omega = 100 \Rightarrow \frac{Y}{X} = 0.71 \angle -45^\circ$$

$$\omega = 300 \Rightarrow \frac{Y}{X} = 0.32 \angle -72^\circ$$


Sine Wave Response

11: Frequency Responses

- Frequency Response
- **Sine Wave Response**
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$RC = 10 \text{ ms}$$


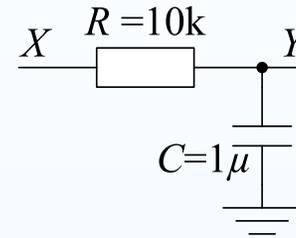
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = \frac{1}{0.01j\omega + 1}$$



$$\omega = 50 \Rightarrow \frac{Y}{X} = 0.89 \angle -27^\circ$$

$$\omega = 100 \Rightarrow \frac{Y}{X} = 0.71 \angle -45^\circ$$
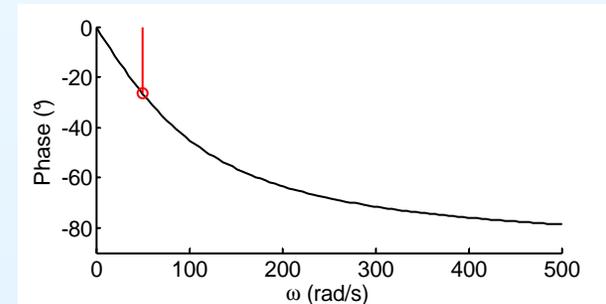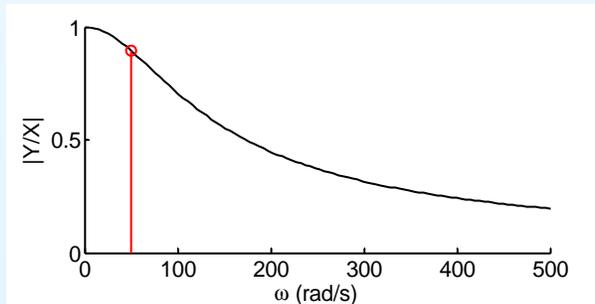
$$\omega = 300 \Rightarrow \frac{Y}{X} = 0.32 \angle -72^\circ$$





Sine Wave Response

11: Frequency Responses

- Frequency Response
- **Sine Wave Response**
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$RC = 10 \text{ ms}$$

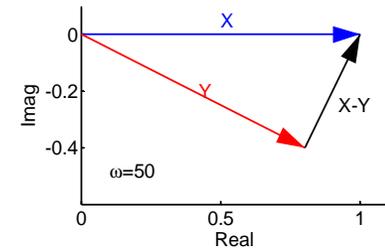
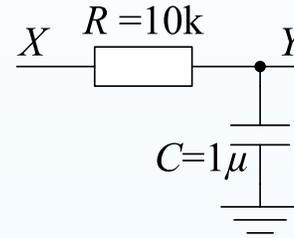
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = \frac{1}{0.01j\omega + 1}$$



$$\omega = 50 \Rightarrow \frac{Y}{X} = 0.89 \angle -27^\circ$$

$$\omega = 100 \Rightarrow \frac{Y}{X} = 0.71 \angle -45^\circ$$
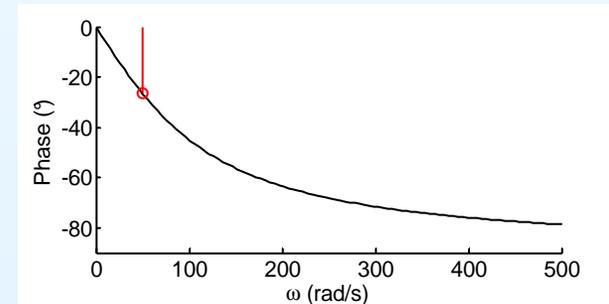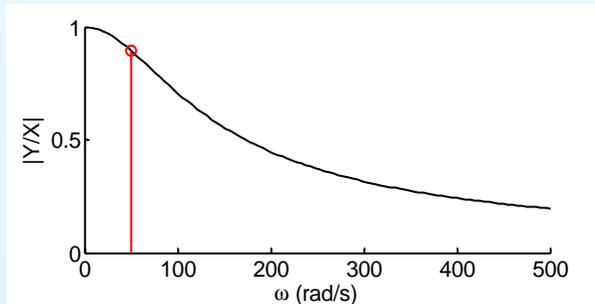
$$\omega = 300 \Rightarrow \frac{Y}{X} = 0.32 \angle -72^\circ$$





Sine Wave Response

11: Frequency Responses

- Frequency Response
- **Sine Wave Response**
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$RC = 10 \text{ ms}$$


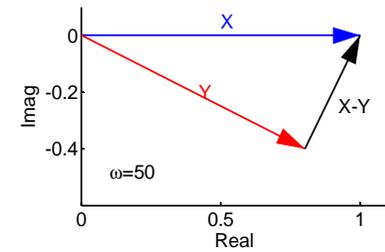
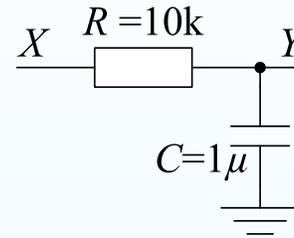
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = \frac{1}{0.01j\omega + 1}$$



$$\omega = 50 \Rightarrow \frac{Y}{X} = 0.89 \angle -27^\circ$$

$$\omega = 100 \Rightarrow \frac{Y}{X} = 0.71 \angle -45^\circ$$
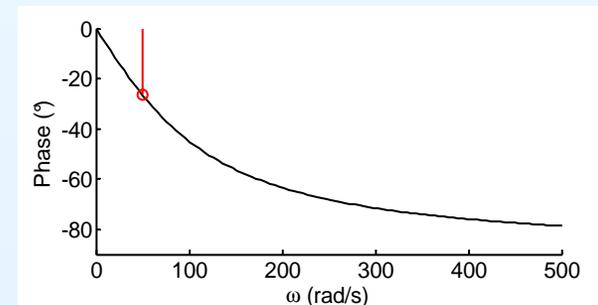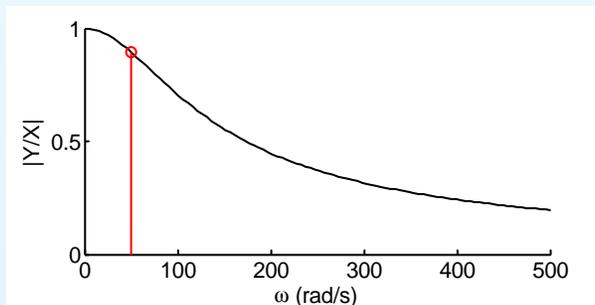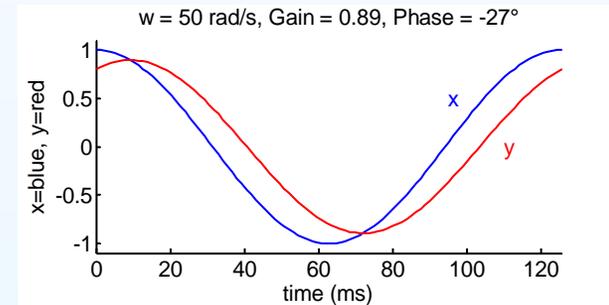
$$\omega = 300 \Rightarrow \frac{Y}{X} = 0.32 \angle -72^\circ$$




Sine Wave Response

11: Frequency Responses

- Frequency Response
- **Sine Wave Response**
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$RC = 10 \text{ ms}$$


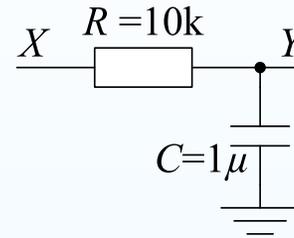
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = \frac{1}{0.01j\omega + 1}$$



$$\omega = 50 \Rightarrow \frac{Y}{X} = 0.89 \angle -27^\circ$$

$$\omega = 100 \Rightarrow \frac{Y}{X} = 0.71 \angle -45^\circ$$
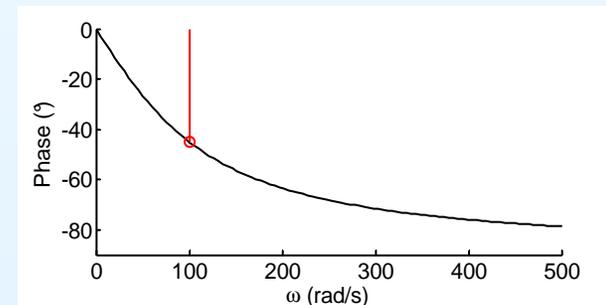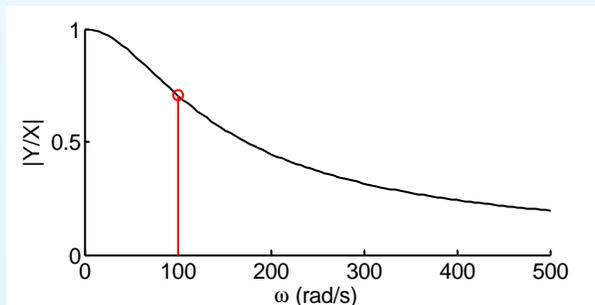
$$\omega = 300 \Rightarrow \frac{Y}{X} = 0.32 \angle -72^\circ$$





Sine Wave Response

11: Frequency Responses

- Frequency Response
- **Sine Wave Response**
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$RC = 10 \text{ ms}$$

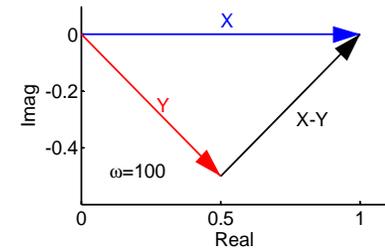
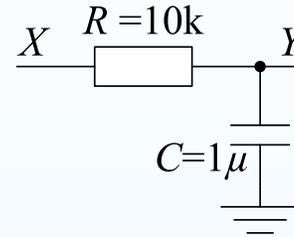
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = \frac{1}{0.01j\omega + 1}$$



$$\omega = 50 \Rightarrow \frac{Y}{X} = 0.89 \angle -27^\circ$$

$$\omega = 100 \Rightarrow \frac{Y}{X} = 0.71 \angle -45^\circ$$
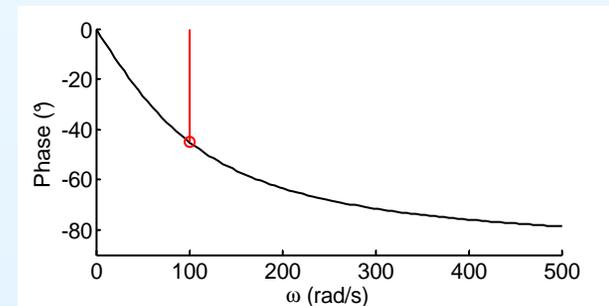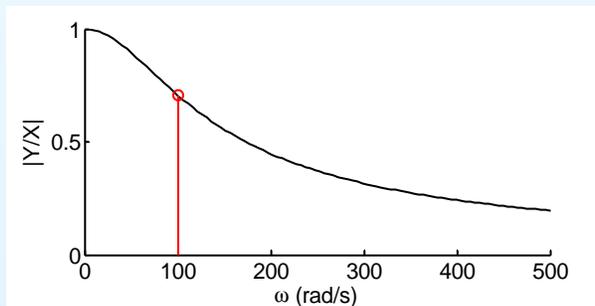
$$\omega = 300 \Rightarrow \frac{Y}{X} = 0.32 \angle -72^\circ$$





Sine Wave Response

11: Frequency Responses

- Frequency Response
- **Sine Wave Response**
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$RC = 10 \text{ ms}$$


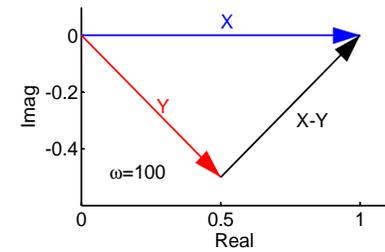
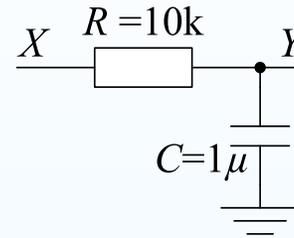
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = \frac{1}{0.01j\omega + 1}$$



$$\omega = 50 \Rightarrow \frac{Y}{X} = 0.89 \angle -27^\circ$$

$$\omega = 100 \Rightarrow \frac{Y}{X} = 0.71 \angle -45^\circ$$
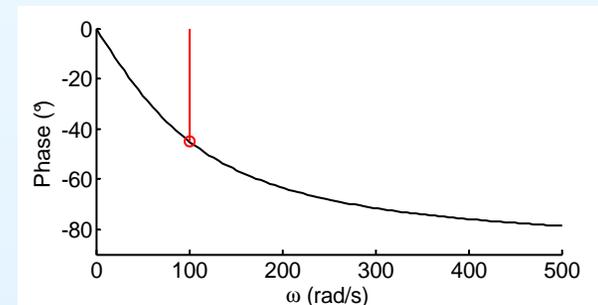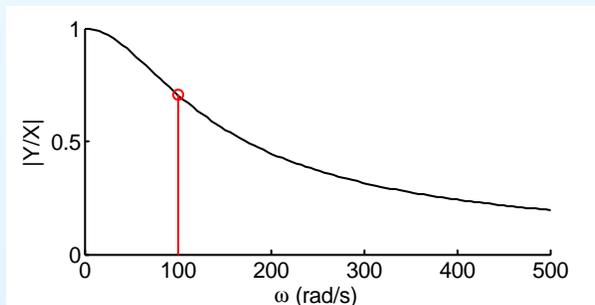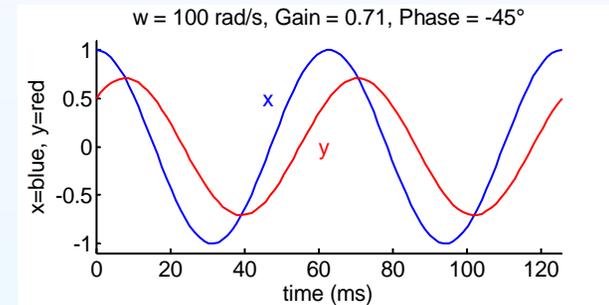
$$\omega = 300 \Rightarrow \frac{Y}{X} = 0.32 \angle -72^\circ$$




Sine Wave Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$RC = 10 \text{ ms}$$


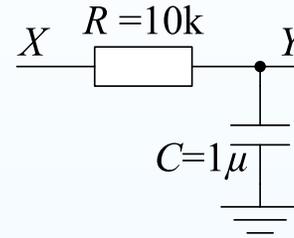
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = \frac{1}{0.01j\omega + 1}$$



$$\omega = 50 \Rightarrow \frac{Y}{X} = 0.89 \angle -27^\circ$$

$$\omega = 100 \Rightarrow \frac{Y}{X} = 0.71 \angle -45^\circ$$
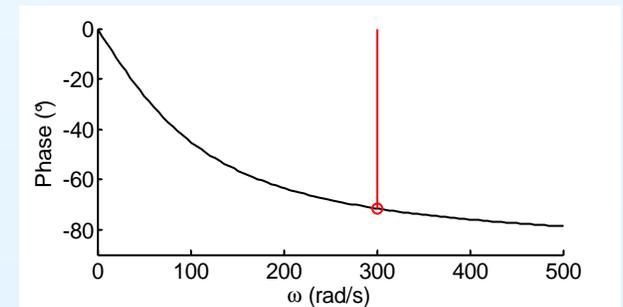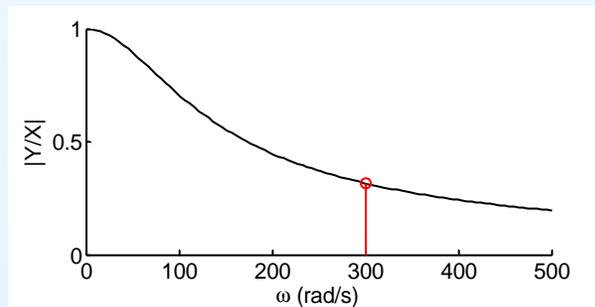
$$\omega = 300 \Rightarrow \frac{Y}{X} = 0.32 \angle -72^\circ$$





Sine Wave Response

11: Frequency Responses

- Frequency Response
- **Sine Wave Response**
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$RC = 10 \text{ ms}$$

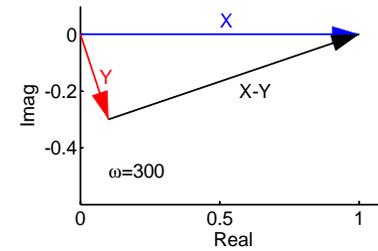
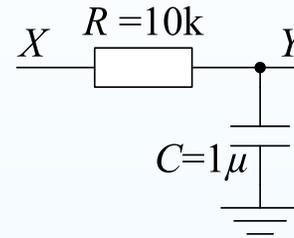
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = \frac{1}{0.01j\omega + 1}$$



$$\omega = 50 \Rightarrow \frac{Y}{X} = 0.89 \angle -27^\circ$$

$$\omega = 100 \Rightarrow \frac{Y}{X} = 0.71 \angle -45^\circ$$
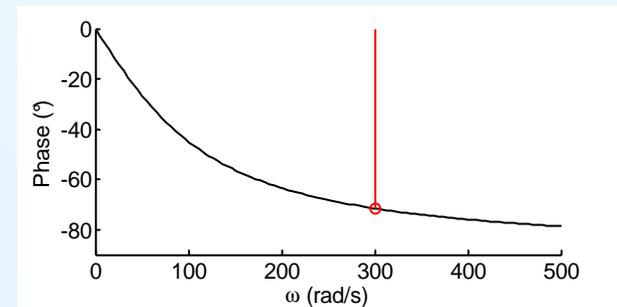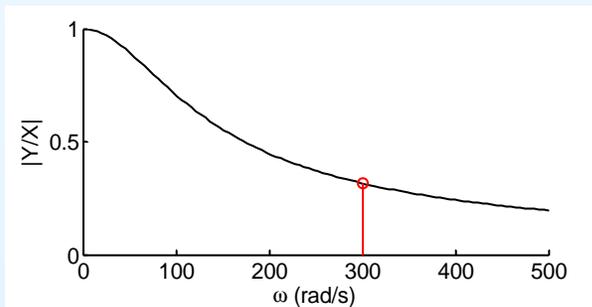
$$\omega = 300 \Rightarrow \frac{Y}{X} = 0.32 \angle -72^\circ$$





Sine Wave Response

11: Frequency Responses

- Frequency Response
- **Sine Wave Response**
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$RC = 10 \text{ ms}$$


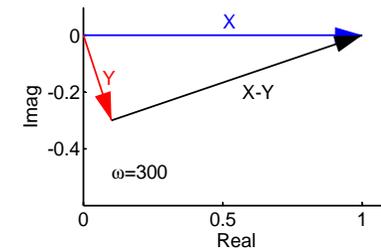
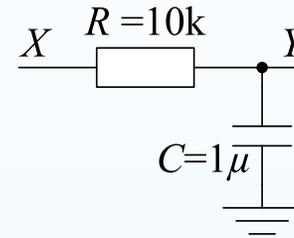
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = \frac{1}{0.01j\omega + 1}$$



$$\omega = 50 \Rightarrow \frac{Y}{X} = 0.89 \angle -27^\circ$$

$$\omega = 100 \Rightarrow \frac{Y}{X} = 0.71 \angle -45^\circ$$
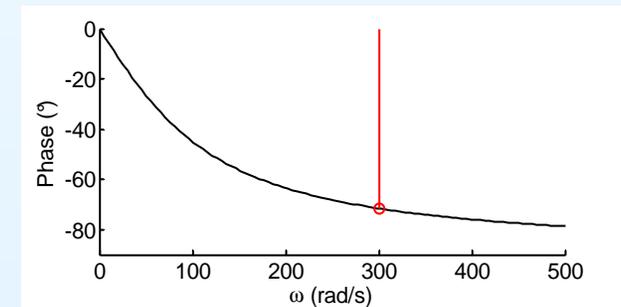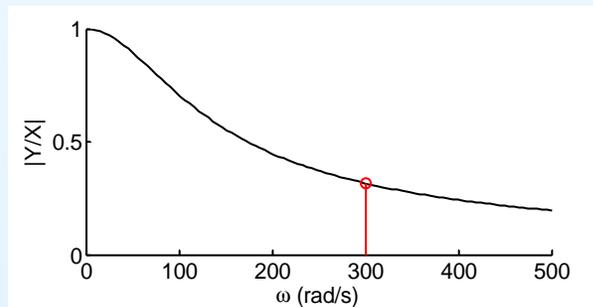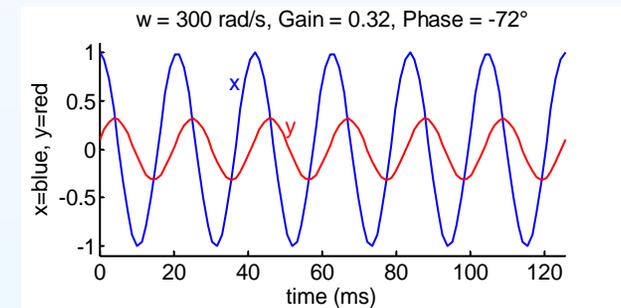
$$\omega = 300 \Rightarrow \frac{Y}{X} = 0.32 \angle -72^\circ$$





Sine Wave Response

11: Frequency Responses

- Frequency Response
- **Sine Wave Response**
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$RC = 10 \text{ ms}$$


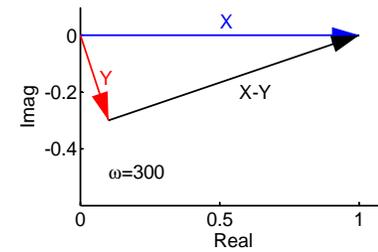
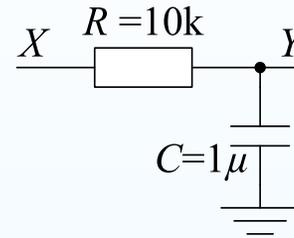
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = \frac{1}{0.01j\omega + 1}$$



$$\omega = 50 \Rightarrow \frac{Y}{X} = 0.89 \angle -27^\circ$$

$$\omega = 100 \Rightarrow \frac{Y}{X} = 0.71 \angle -45^\circ$$
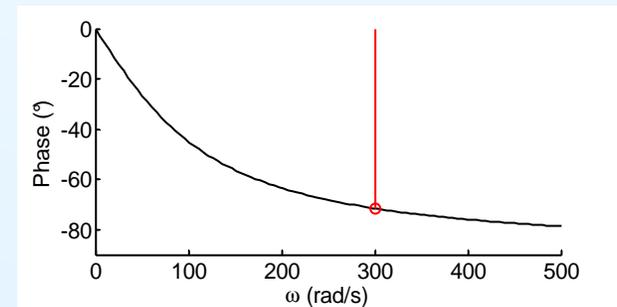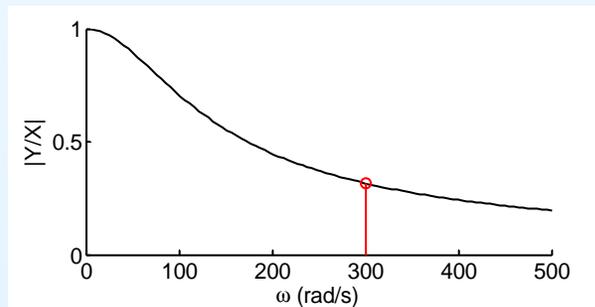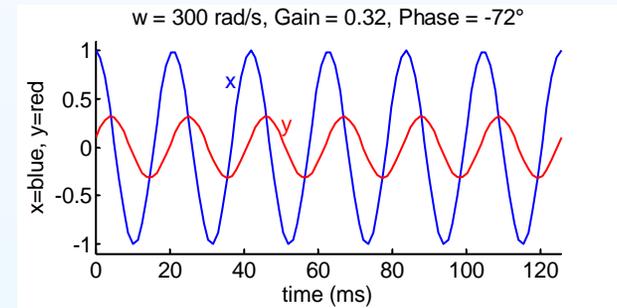
$$\omega = 300 \Rightarrow \frac{Y}{X} = 0.32 \angle -72^\circ$$




The output, $y(t)$, *lags* the input, $x(t)$, by up to 90° .

Logarithmic axes

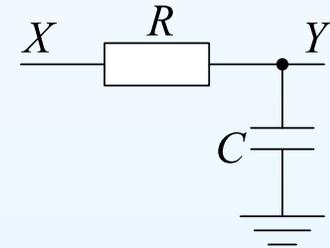11: Frequency Responses

- Frequency Response
- Sine Wave Response
- **Logarithmic axes**
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

We usually use logarithmic axes for frequency and gain (**but not phase**) because % differences are more significant than absolute differences. E.g. 5 kHz versus 5.005 kHz is less significant than 10 Hz versus 15 Hz even though both differences equal 5 Hz.





Logarithmic axes

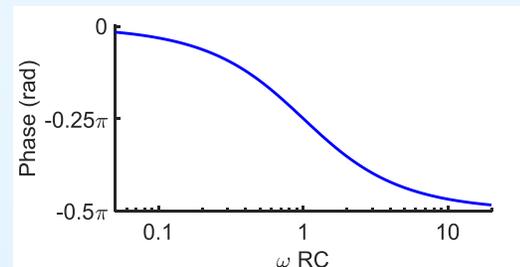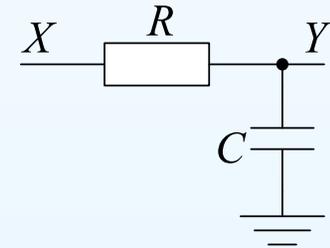11: Frequency Responses

- Frequency Response
- Sine Wave Response
- **Logarithmic axes**
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

We usually use logarithmic axes for frequency and gain (**but not phase**) because % differences are more significant than absolute differences. E.g. 5 kHz versus 5.005 kHz is less significant than 10 Hz versus 15 Hz even though both differences equal 5 Hz.






Logarithmic axes

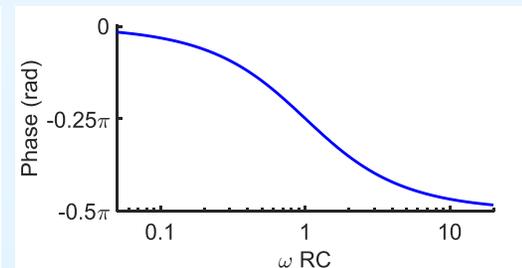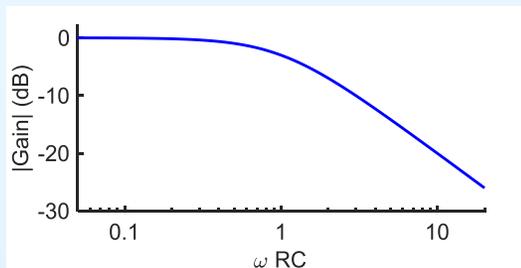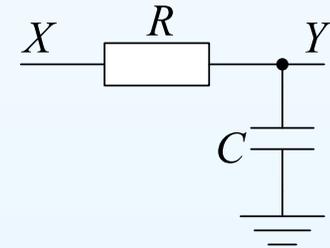11: Frequency Responses

- Frequency Response
- Sine Wave Response
- **Logarithmic axes**
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

We usually use logarithmic axes for frequency and gain (**but not phase**) because % differences are more significant than absolute differences. E.g. 5 kHz versus 5.005 kHz is less significant than 10 Hz versus 15 Hz even though both differences equal 5 Hz.






Logarithmic axes

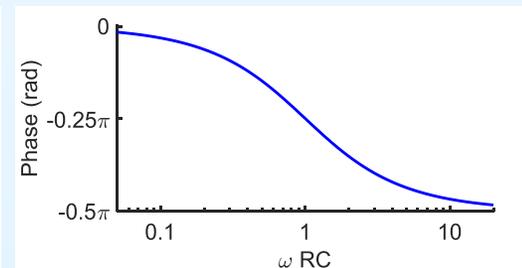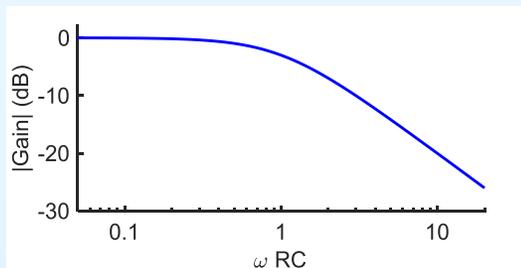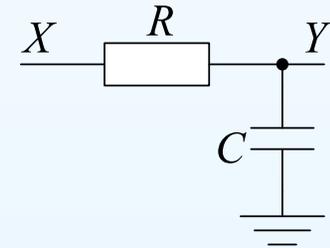11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

We usually use logarithmic axes for frequency and gain (**but not phase**) because % differences are more significant than absolute differences. E.g. 5 kHz versus 5.005 kHz is less significant than 10 Hz versus 15 Hz even though both differences equal 5 Hz.



Note that 0 does not exist on a log axis and so the starting point of the axis is arbitrary.




Logarithmic axes

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- **Logarithmic axes**
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

We usually use logarithmic axes for frequency and gain (**but not phase**) because % differences are more significant than absolute differences. E.g. 5 kHz versus 5.005 kHz is less significant than 10 Hz versus 15 Hz even though both differences equal 5 Hz.

Logarithmic voltage ratios are specified in *decibels* (dB) = $20 \log_{10} \frac{|V_2|}{|V_1|}$.

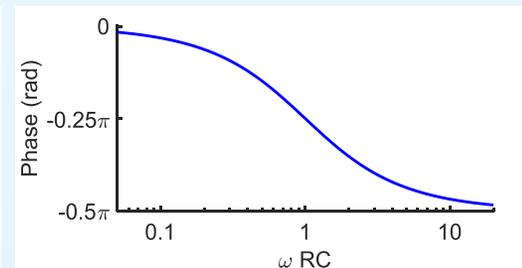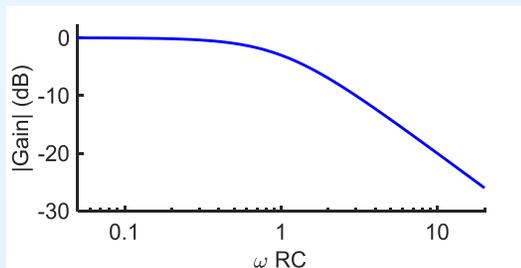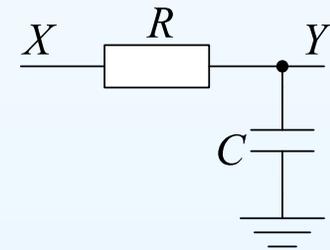

Note that 0 does not exist on a log axis and so the starting point of the axis is arbitrary.

Logarithmic axes




11: Frequency Responses

- Frequency Response
- Sine Wave Response
- **Logarithmic axes**
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

We usually use logarithmic axes for frequency and gain (**but not phase**) because % differences are more significant than absolute differences. E.g. 5 kHz versus 5.005 kHz is less significant than 10 Hz versus 15 Hz even though both differences equal 5 Hz.

Logarithmic voltage ratios are specified in *decibels (dB)* = $20 \log_{10} \frac{|V_2|}{|V_1|}$.

Common voltage ratios:

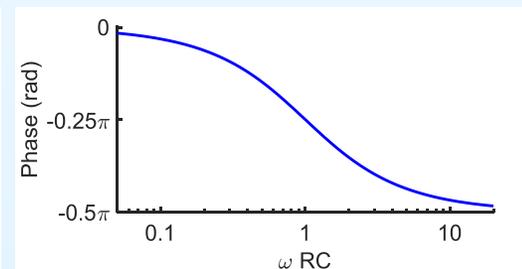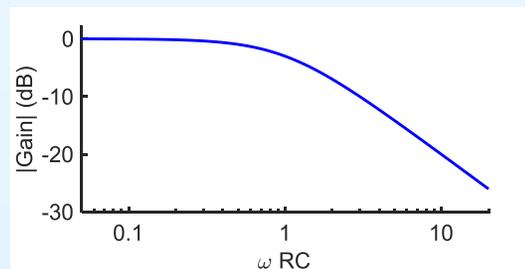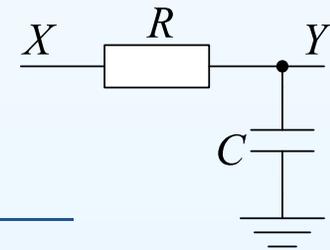

Note that 0 does not exist on a log axis and so the starting point of the axis is arbitrary.

Logarithmic axes

11: Frequency Responses




- Frequency Response
- Sine Wave Response
- **Logarithmic axes**
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

We usually use logarithmic axes for frequency and gain (**but not phase**) because % differences are more significant than absolute differences. E.g. 5 kHz versus 5.005 kHz is less significant than 10 Hz versus 15 Hz even though both differences equal 5 Hz.

Logarithmic voltage ratios are specified in *decibels* (dB) = $20 \log_{10} \left| \frac{V_2}{V_1} \right|$.

Common voltage ratios:

$\left \frac{V_2}{V_1} \right $	0.1			1			10	100
dB	-20			0			20	40

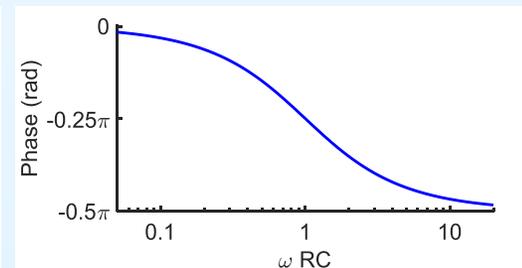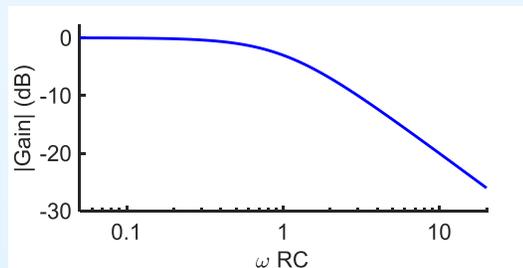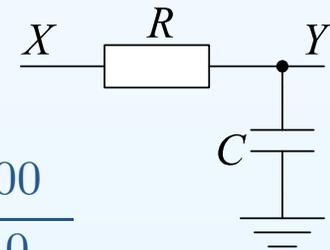

Note that 0 does not exist on a log axis and so the starting point of the axis is arbitrary.

Logarithmic axes

11: Frequency Responses




- Frequency Response
- Sine Wave Response
- **Logarithmic axes**
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

We usually use logarithmic axes for frequency and gain (**but not phase**) because % differences are more significant than absolute differences. E.g. 5 kHz versus 5.005 kHz is less significant than 10 Hz versus 15 Hz even though both differences equal 5 Hz.

Logarithmic voltage ratios are specified in *decibels* (dB) = $20 \log_{10} \frac{|V_2|}{|V_1|}$.

Common voltage ratios:

$\frac{ V_2 }{ V_1 }$	0.1	0.5	1	2	10	100
dB	-20	-6	0	6	20	40

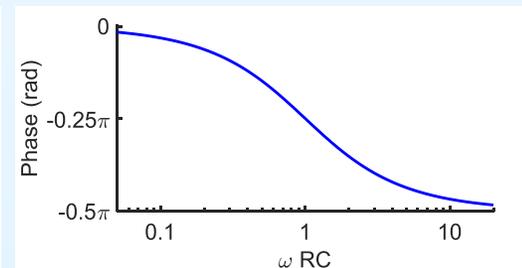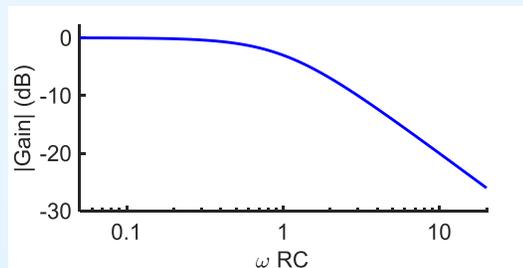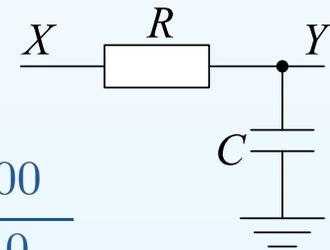

Note that 0 does not exist on a log axis and so the starting point of the axis is arbitrary.

Logarithmic axes

11: Frequency Responses




- Frequency Response
- Sine Wave Response
- **Logarithmic axes**
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

We usually use logarithmic axes for frequency and gain (**but not phase**) because % differences are more significant than absolute differences. E.g. 5 kHz versus 5.005 kHz is less significant than 10 Hz versus 15 Hz even though both differences equal 5 Hz.

Logarithmic voltage ratios are specified in *decibels (dB)* = $20 \log_{10} \frac{|V_2|}{|V_1|}$.

Common voltage ratios:

$\frac{ V_2 }{ V_1 }$	0.1	0.5	$\sqrt{0.5}$	1	$\sqrt{2}$	2	10	100
dB	-20	-6	-3	0	3	6	20	40

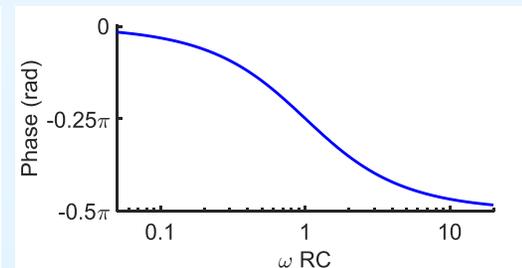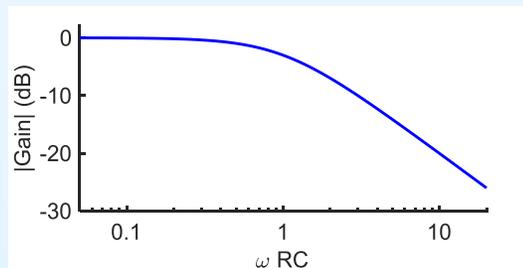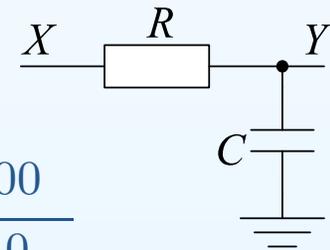

Note that 0 does not exist on a log axis and so the starting point of the axis is arbitrary.

Logarithmic axes

11: Frequency Responses




- Frequency Response
- Sine Wave Response
- **Logarithmic axes**
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

We usually use logarithmic axes for frequency and gain (**but not phase**) because % differences are more significant than absolute differences. E.g. 5 kHz versus 5.005 kHz is less significant than 10 Hz versus 15 Hz even though both differences equal 5 Hz.

Logarithmic voltage ratios are specified in *decibels* (dB) = $20 \log_{10} \frac{|V_2|}{|V_1|}$.

Common voltage ratios:

$\frac{ V_2 }{ V_1 }$	0.1	0.5	$\sqrt{0.5}$	1	$\sqrt{2}$	2	10	100
dB	-20	-6	-3	0	3	6	20	40

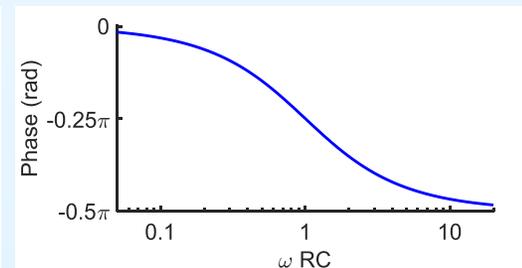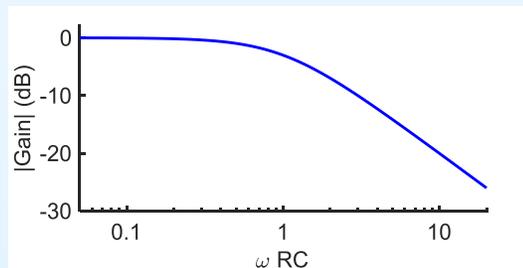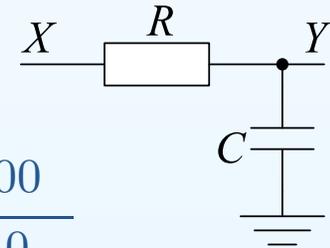

Note that 0 does not exist on a log axis and so the starting point of the axis is arbitrary.

Note: $P \propto V^2 \Rightarrow$ decibel power ratios are given by $10 \log_{10} \frac{P_2}{P_1}$

Logs of Powers



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- **Logs of Powers** +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Logs of Powers



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- **Logs of Powers** +
- Straight Line
- Approximations
 - Plot Magnitude Response
 - Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

Logs of Powers


11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- **Logs of Powers** +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

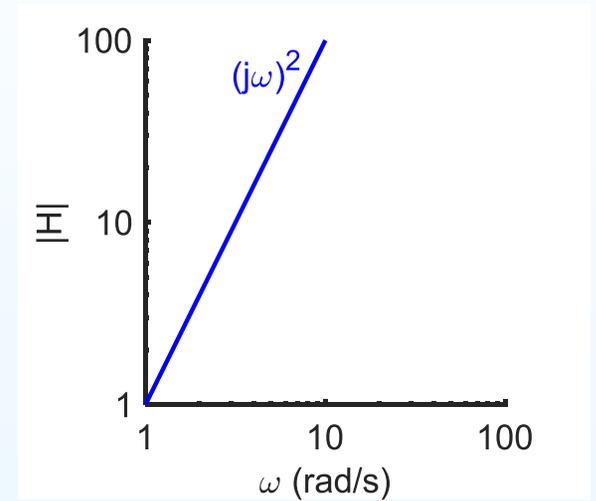

Logs of Powers



11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- **Logs of Powers** +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

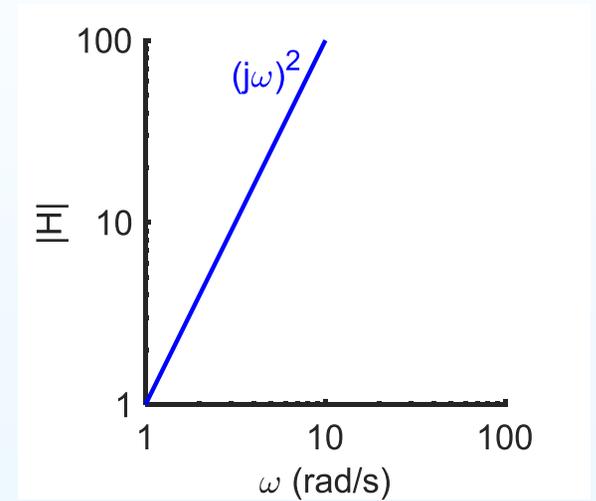This is a straight line with a slope of r .



Logs of Powers



11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

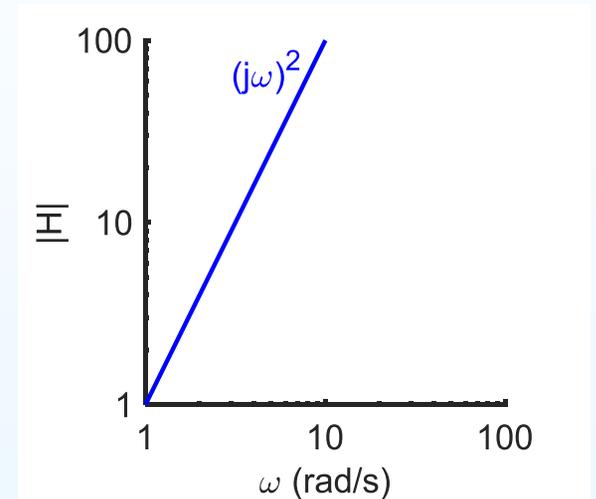This is a straight line with a slope of r .



Phase (log-lin graph):

$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$

Logs of Powers



11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Magnitude (log-log graph):


$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

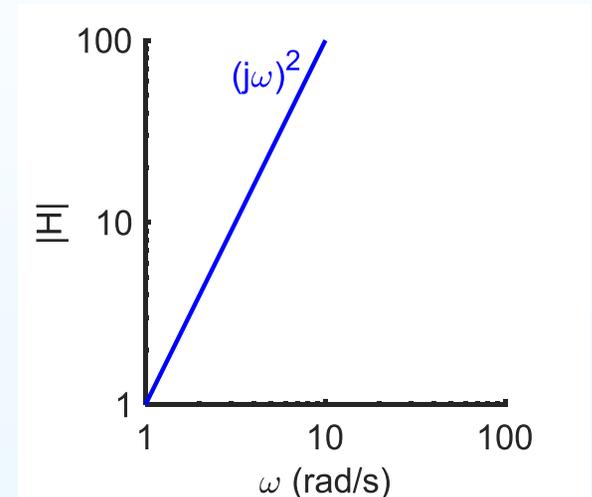This is a straight line with a slope of r .



Phase (log-lin graph):
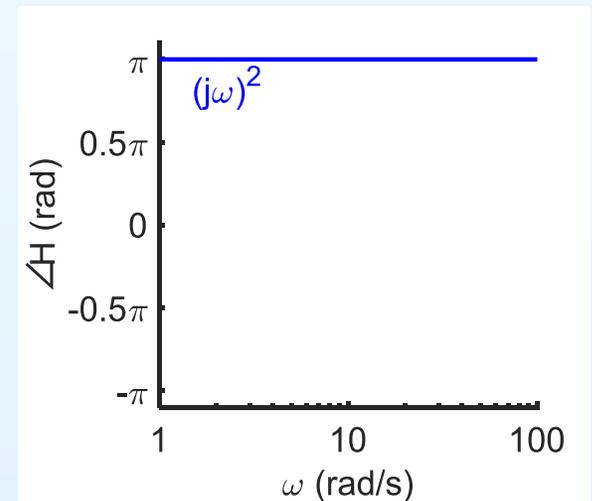
$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$



Logs of Powers



11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

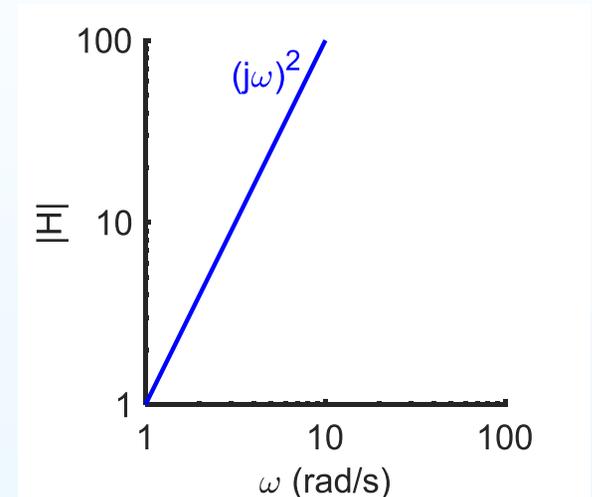
This is a straight line with a slope of r .



Phase (log-lin graph):

$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$

The phase is constant $\forall \omega$.

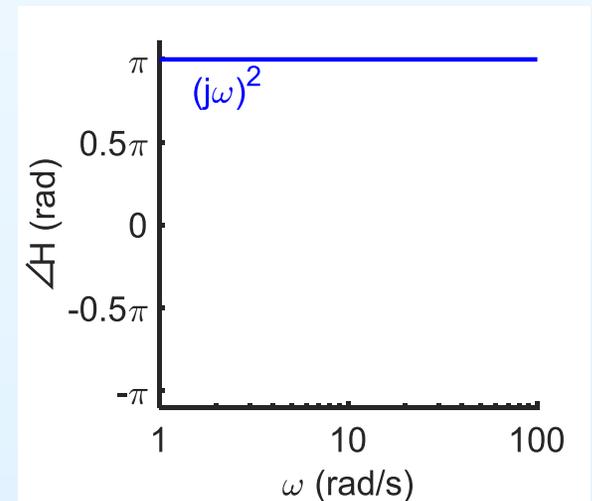

Logs of Powers



11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

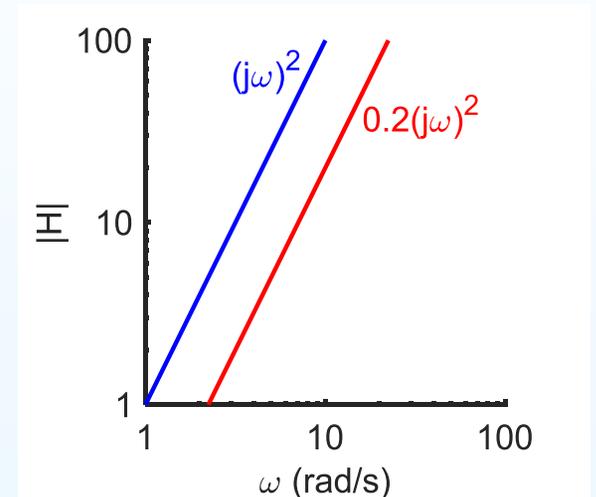
This is a straight line with a slope of r .



Phase (log-lin graph):

$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$

The phase is constant $\forall \omega$.

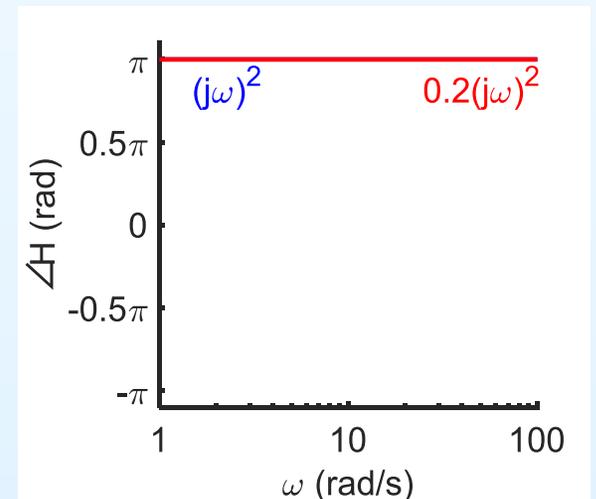

Logs of Powers



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary


Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

This is a straight line with a slope of r .

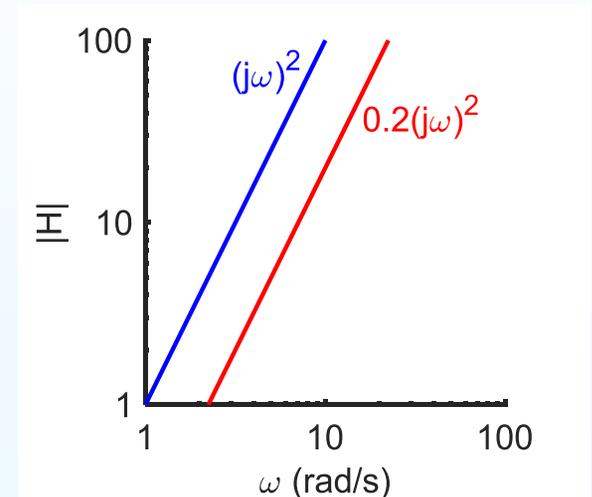
c only affects the line's vertical position.



Phase (log-lin graph):

$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$

The phase is constant $\forall \omega$.

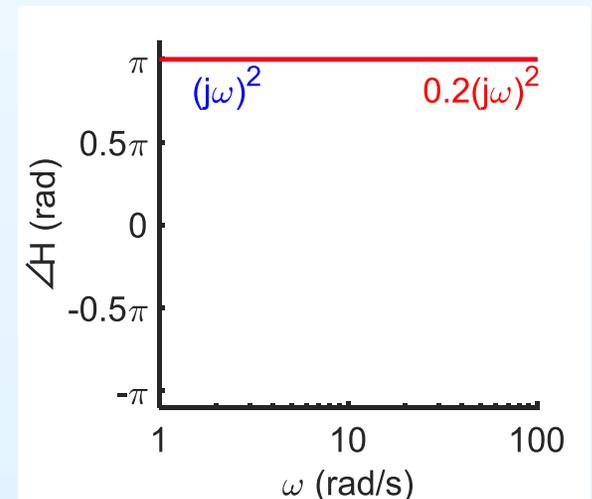

Logs of Powers



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary


Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

This is a straight line with a slope of r .

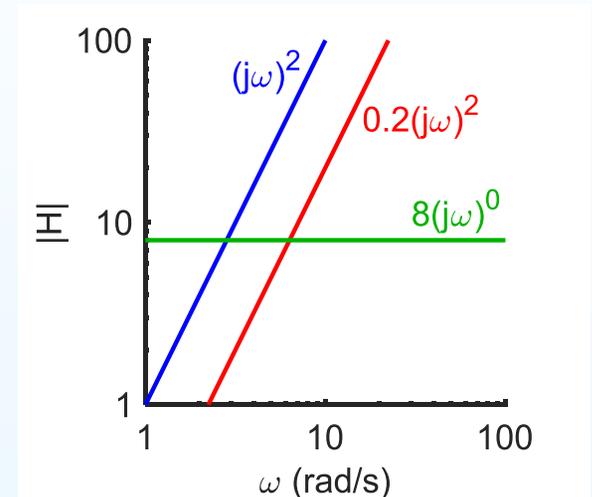
c only affects the line's vertical position.



Phase (log-lin graph):

$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$

The phase is constant $\forall \omega$.

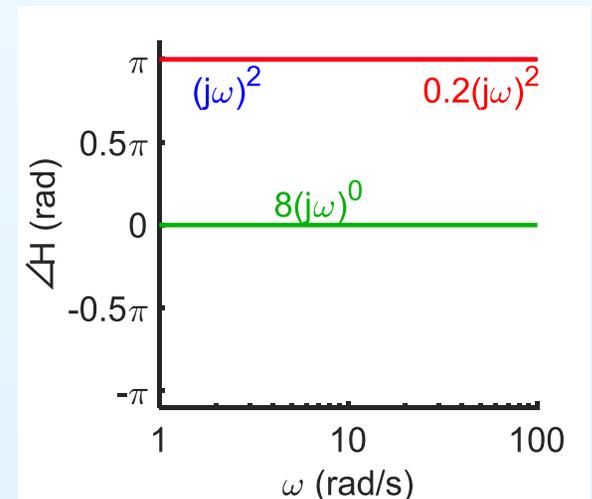

Logs of Powers



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- **Logs of Powers** +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary


Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

This is a straight line with a slope of r .

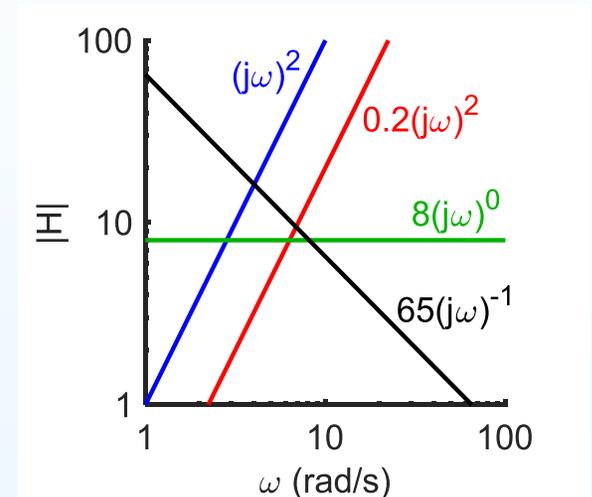
c only affects the line's vertical position.



Phase (log-lin graph):

$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$

The phase is constant $\forall \omega$.

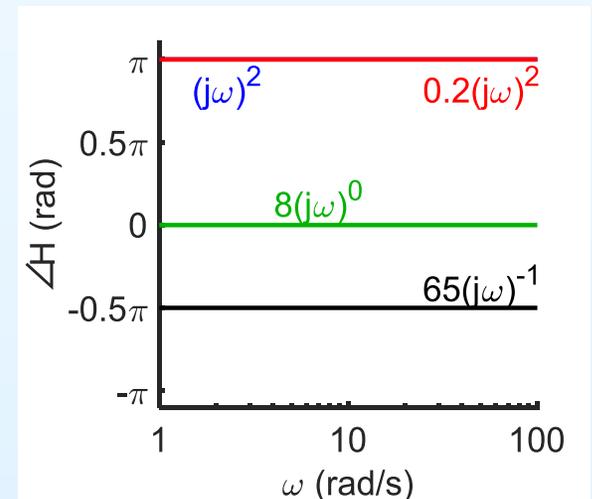

Logs of Powers



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary


Suppose we plot the magnitude and phase of $H = c(j\omega)^r$

Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

This is a straight line with a slope of r .

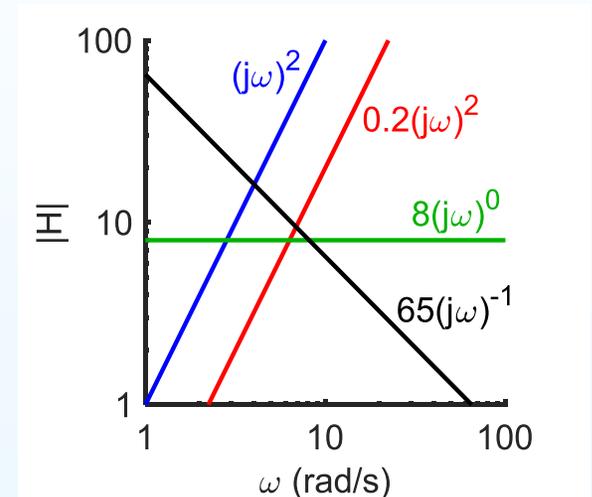c only affects the line's vertical position.




Phase (log-lin graph):

$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$

The phase is constant $\forall \omega$.

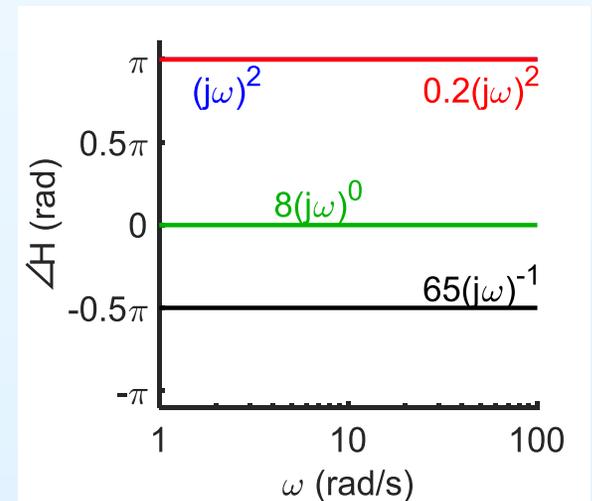If $c > 0$, phase = $90^\circ \times$ magnitude slope.



Logs of Powers



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Suppose we plot the magnitude and phase of $H = c(j\omega)^r$


Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

This is a straight line with a slope of r .

c only affects the line's vertical position.

If $|H|$ is measured in decibels, a slope of r is called $6r$ dB/octave or $20r$ dB/decade.

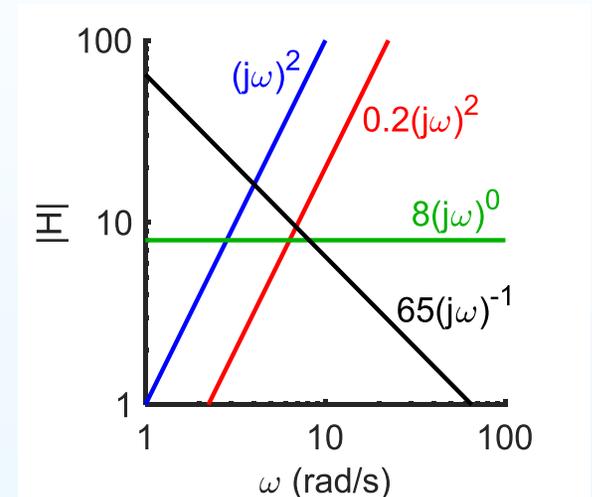


Phase (log-lin graph):

$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$

The phase is constant $\forall \omega$.

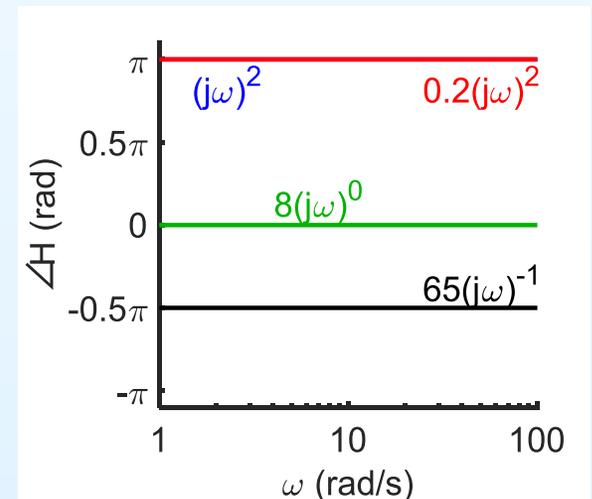If $c > 0$, phase = $90^\circ \times$ magnitude slope.



Logs of Powers



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- **Logs of Powers** +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Suppose we plot the magnitude and phase of $H = c(j\omega)^r$


Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

This is a straight line with a slope of r .

c only affects the line's vertical position.

If $|H|$ is measured in decibels, a slope of r is called $6r$ dB/octave or $20r$ dB/decade.

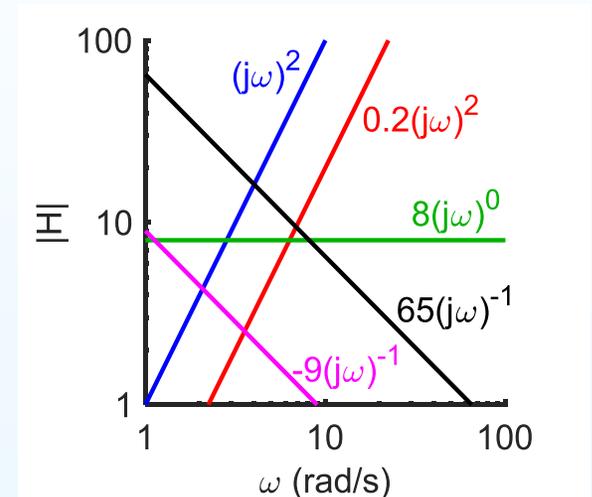


Phase (log-lin graph):

$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$

The phase is constant $\forall \omega$.

If $c > 0$, phase = $90^\circ \times$ magnitude slope.

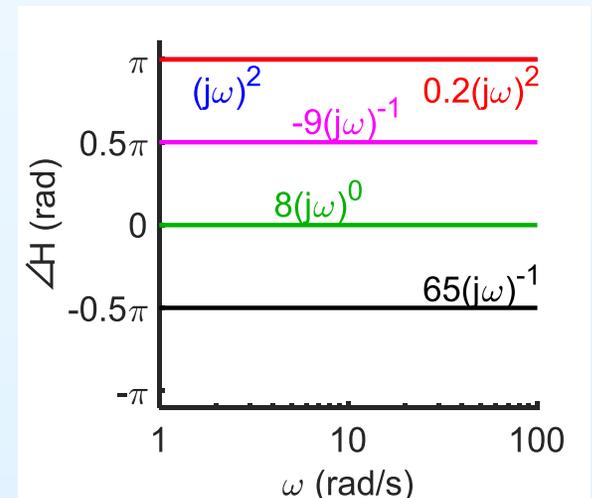Negative c adds $\pm 180^\circ$ to the phase.



Logs of Powers



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Suppose we plot the magnitude and phase of $H = c(j\omega)^r$


Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

This is a straight line with a slope of r .

c only affects the line's vertical position.

If $|H|$ is measured in decibels, a slope of r is called $6r$ dB/octave or $20r$ dB/decade.

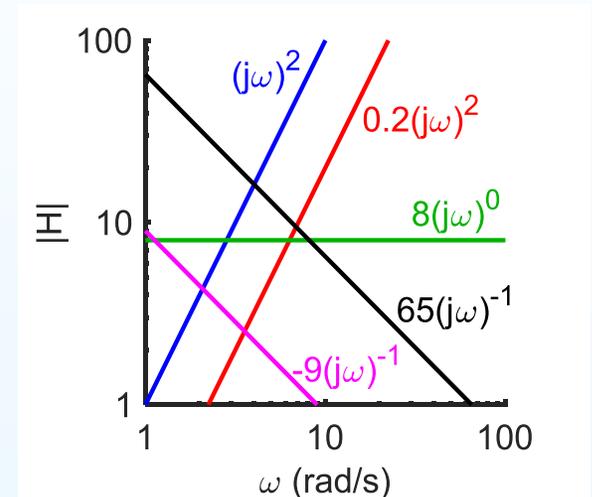

Phase (log-lin graph):


$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$

The phase is constant $\forall \omega$.

If $c > 0$, phase = $90^\circ \times$ magnitude slope.

Negative c adds $\pm 180^\circ$ to the phase.

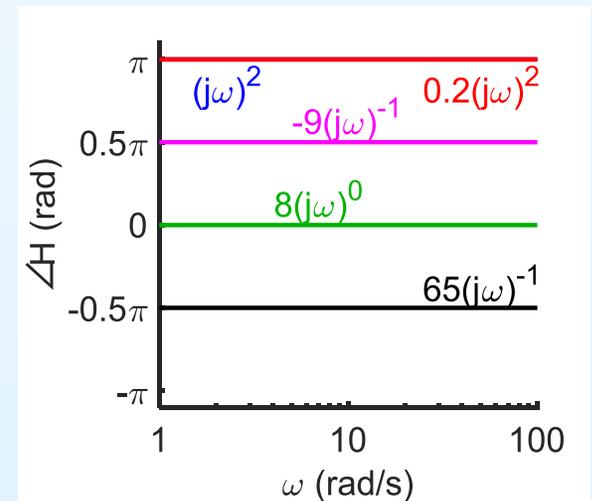Note: Phase angles are modulo 360° , i.e. $+180^\circ \equiv -180^\circ$ and $450^\circ \equiv 90^\circ$.



Logs of Powers



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- **Logs of Powers** +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$H = c(j\omega)^r$ has a straight-line magnitude graph and a constant phase.


Magnitude (log-log graph):

$$|H| = c\omega^r \Rightarrow \log |H| = \log |c| + r \log \omega$$

This is a straight line with a slope of r .

c only affects the line's vertical position.

If $|H|$ is measured in decibels, a slope of r is called $6r$ dB/octave or $20r$ dB/decade.

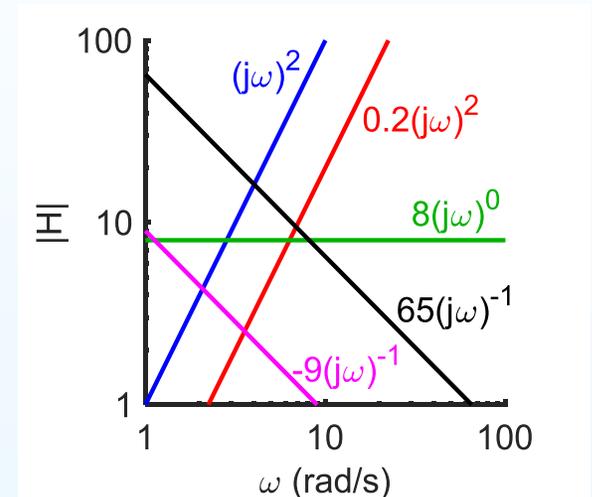

Phase (log-lin graph):


$$\angle H = \angle j^r + \angle c = r \times \frac{\pi}{2} \quad (+\pi \text{ if } c < 0)$$

The phase is constant $\forall \omega$.

If $c > 0$, phase = $90^\circ \times$ magnitude slope.

Negative c adds $\pm 180^\circ$ to the phase.

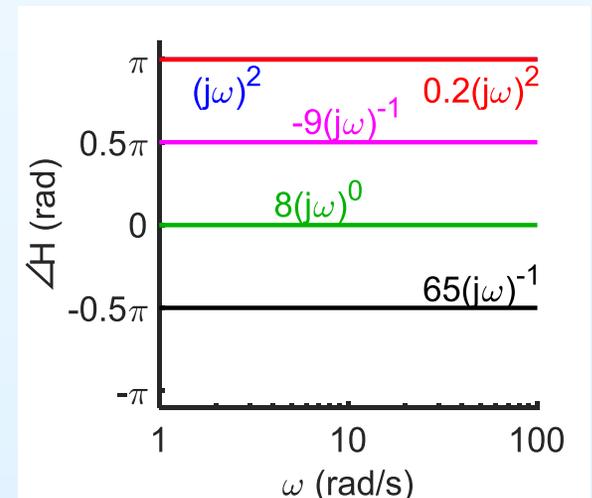Note: Phase angles are modulo 360° , i.e. $+180^\circ \equiv -180^\circ$ and $450^\circ \equiv 90^\circ$.



Straight Line Approximations

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\text{Key idea: } (aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$$



Straight Line Approximations

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Key idea: $(aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$
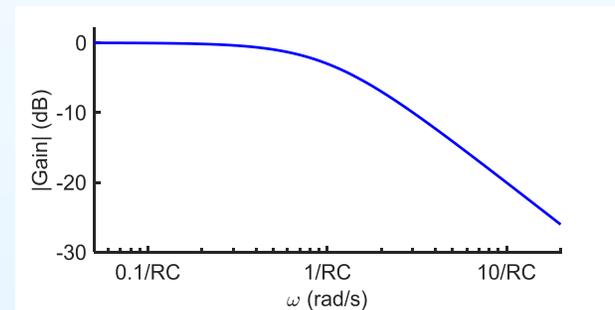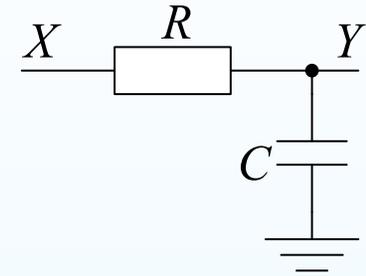
$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$



Straight Line Approximations



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Key idea: $(aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$

$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

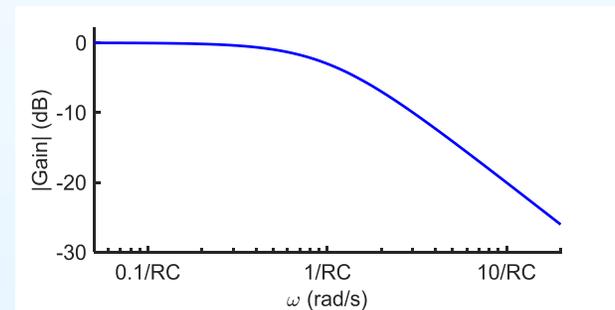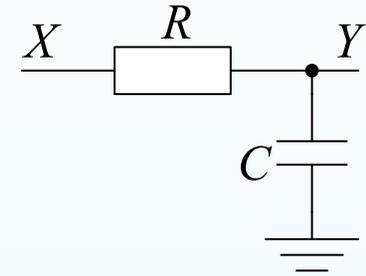Low frequencies ($\omega \ll \frac{1}{RC}$): $H(j\omega) \approx 1$



Straight Line Approximations

11: Frequency Responses



- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Key idea: $(aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$

$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

Low frequencies ($\omega \ll \frac{1}{RC}$): $H(j\omega) \approx 1$

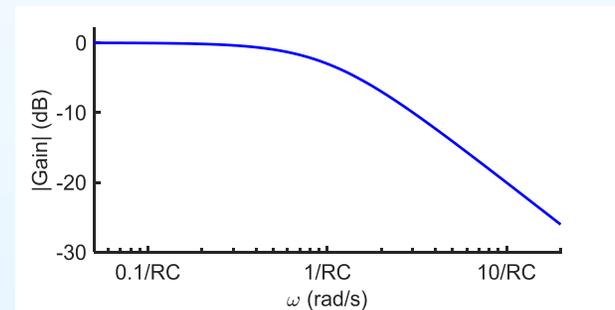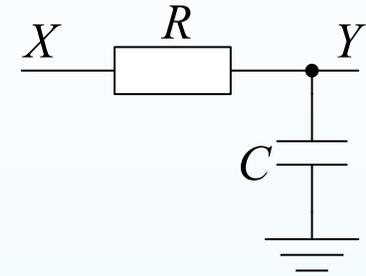High frequencies ($\omega \gg \frac{1}{RC}$): $H(j\omega) \approx \frac{1}{j\omega RC}$



Straight Line Approximations

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary



$$\text{Key idea: } (aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$$

$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

$$\text{Low frequencies } (\omega \ll \frac{1}{RC}): H(j\omega) \approx 1$$

$$\text{High frequencies } (\omega \gg \frac{1}{RC}): H(j\omega) \approx \frac{1}{j\omega RC}$$

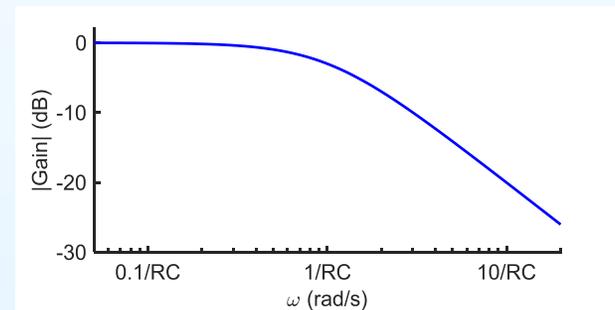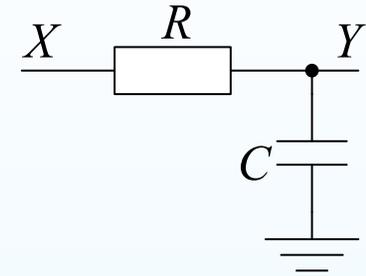Approximate the magnitude response as two straight lines



Straight Line Approximations

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary



$$\text{Key idea: } (aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$$

$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

Low frequencies ($\omega \ll \frac{1}{RC}$): $H(j\omega) \approx 1 \Rightarrow |H(j\omega)| \approx 1$

High frequencies ($\omega \gg \frac{1}{RC}$): $H(j\omega) \approx \frac{1}{j\omega RC}$

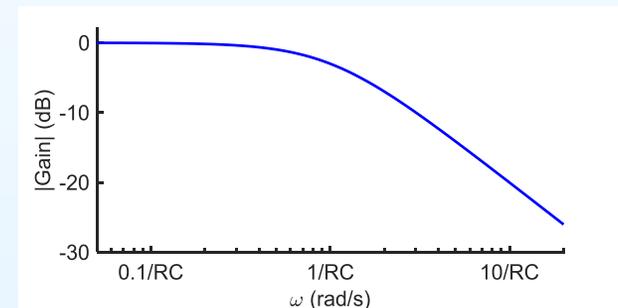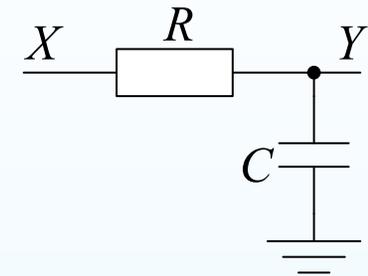Approximate the magnitude response as two straight lines



Straight Line Approximations

11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\text{Key idea: } (aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$$


$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

$$\text{Low frequencies } (\omega \ll \frac{1}{RC}): H(j\omega) \approx 1 \Rightarrow |H(j\omega)| \approx 1$$

$$\text{High frequencies } (\omega \gg \frac{1}{RC}): H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow |H(j\omega)| \approx \frac{1}{RC} \omega^{-1}$$

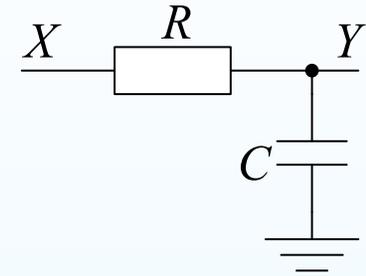

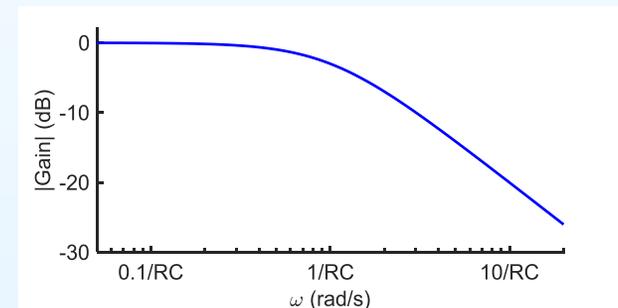Approximate the magnitude response as two straight lines



Straight Line Approximations

11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\text{Key idea: } (aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$$


$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

$$\text{Low frequencies } (\omega \ll \frac{1}{RC}): H(j\omega) \approx 1 \Rightarrow |H(j\omega)| \approx 1$$

$$\text{High frequencies } (\omega \gg \frac{1}{RC}): H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow |H(j\omega)| \approx \frac{1}{RC} \omega^{-1}$$

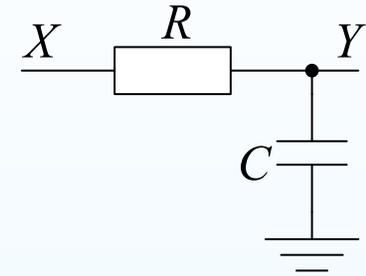

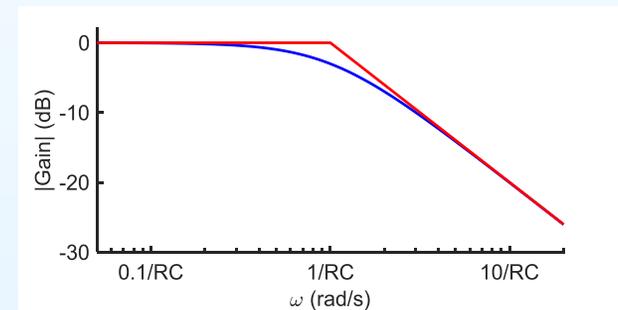Approximate the magnitude response as two straight lines



Straight Line Approximations

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary



$$\text{Key idea: } (aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$$

$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

$$\text{Low frequencies } (\omega \ll \frac{1}{RC}): H(j\omega) \approx 1 \Rightarrow |H(j\omega)| \approx 1$$

$$\text{High frequencies } (\omega \gg \frac{1}{RC}): H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow |H(j\omega)| \approx \frac{1}{RC} \omega^{-1}$$

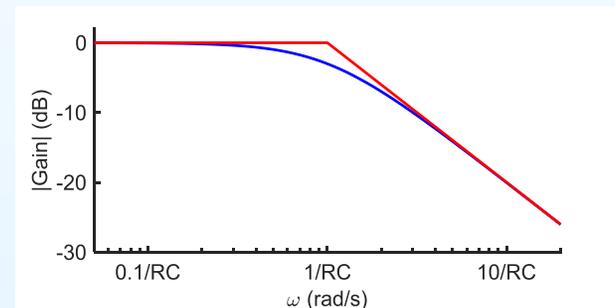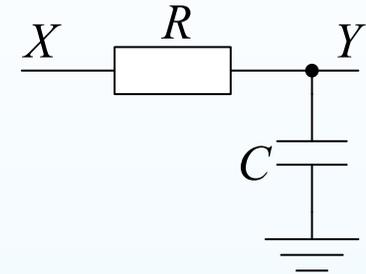Approximate the magnitude response as two straight lines intersecting at the corner frequency, $\omega_c = \frac{1}{RC}$.




Straight Line Approximations

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\text{Key idea: } (aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$$
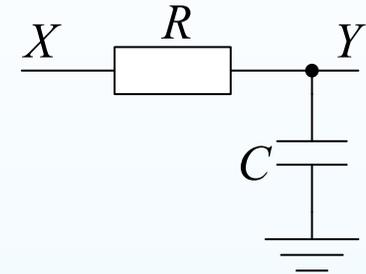
$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$




$$\text{Low frequencies } (\omega \ll \frac{1}{RC}): H(j\omega) \approx 1 \Rightarrow |H(j\omega)| \approx 1$$

$$\text{High frequencies } (\omega \gg \frac{1}{RC}): H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow |H(j\omega)| \approx \frac{1}{RC} \omega^{-1}$$

Approximate the magnitude response as two straight lines intersecting at the corner frequency, $\omega_c = \frac{1}{RC}$.

At the corner frequency:

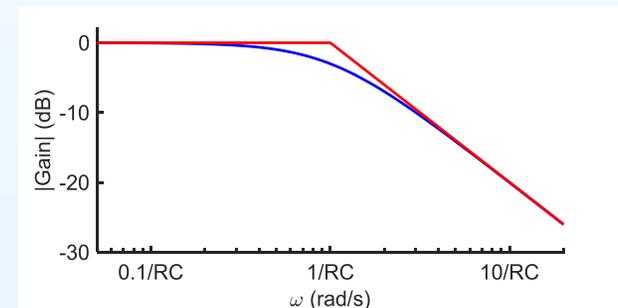(a) the gradient changes by -1 ($= -6 \text{ dB/octave} = -20 \text{ dB/decade}$).




Straight Line Approximations

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Key idea: $(aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$

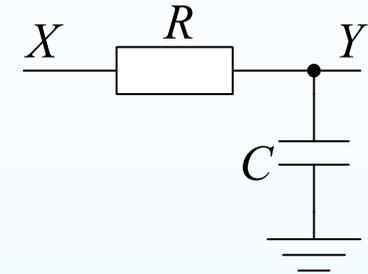


Gain: $H(j\omega) = \frac{1}{j\omega RC + 1}$

Low frequencies ($\omega \ll \frac{1}{RC}$): $H(j\omega) \approx 1 \Rightarrow |H(j\omega)| \approx 1$

High frequencies ($\omega \gg \frac{1}{RC}$): $H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow |H(j\omega)| \approx \frac{1}{RC} \omega^{-1}$

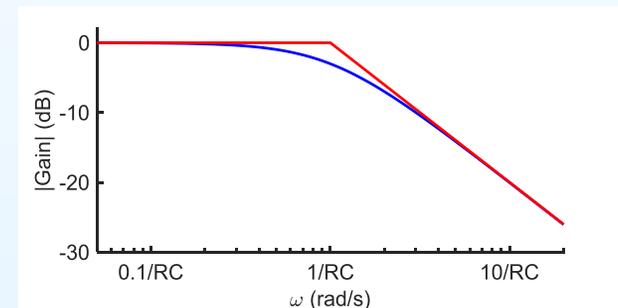Approximate the magnitude response as two straight lines intersecting at the corner frequency, $\omega_c = \frac{1}{RC}$.



At the corner frequency:

(a) the gradient changes by -1 ($= -6$ dB/octave $= -20$ dB/decade).


(b) $|H(j\omega_c)| = \left| \frac{1}{1+j} \right| = \frac{1}{\sqrt{2}} = -3$ dB (worst-case error).

Straight Line Approximations

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- **Straight Line Approximations**
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Key idea: $(aj\omega + b) \approx \begin{cases} aj\omega & \text{for } |a\omega| \gg |b| \\ b & \text{for } |a\omega| \ll |b| \end{cases}$

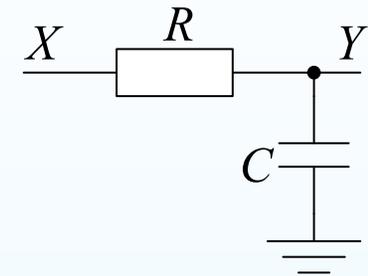


Gain: $H(j\omega) = \frac{1}{j\omega RC + 1}$

Low frequencies ($\omega \ll \frac{1}{RC}$): $H(j\omega) \approx 1 \Rightarrow |H(j\omega)| \approx 1$

High frequencies ($\omega \gg \frac{1}{RC}$): $H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow |H(j\omega)| \approx \frac{1}{RC} \omega^{-1}$

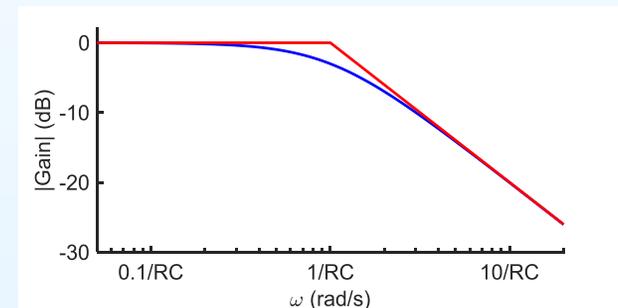Approximate the magnitude response as two straight lines intersecting at the corner frequency, $\omega_c = \frac{1}{RC}$.



At the corner frequency:

(a) the gradient changes by -1 ($= -6$ dB/octave $= -20$ dB/decade).

(b) $|H(j\omega_c)| = \left| \frac{1}{1+j} \right| = \frac{1}{\sqrt{2}} = -3$ dB (worst-case error).

A linear factor $(aj\omega + b)$ has a corner frequency of $\omega_c = \left| \frac{b}{a} \right|$.


Plot Magnitude Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- **Plot Magnitude Response**
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

The gain of a linear circuit is always a *rational polynomial* in $j\omega$ and is called the *transfer function* of the circuit. For example:
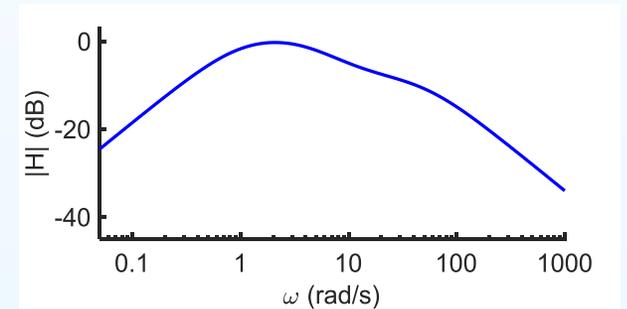
$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600}$$



Plot Magnitude Response


11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

The gain of a linear circuit is always a *rational polynomial* in $j\omega$ and is called the *transfer function* of the circuit. For example:

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

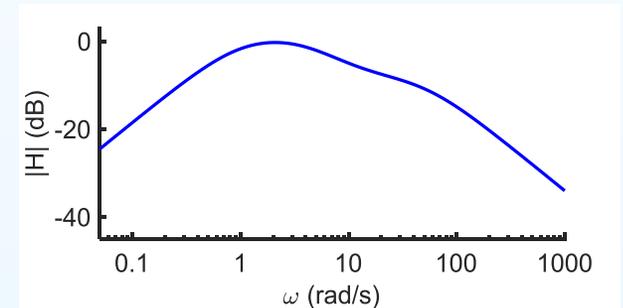

Plot Magnitude Response

11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

The gain of a linear circuit is always a *rational polynomial* in $j\omega$ and is called the *transfer function* of the circuit. For example:

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: Sort corner freqs: 1, 4, 12, 50

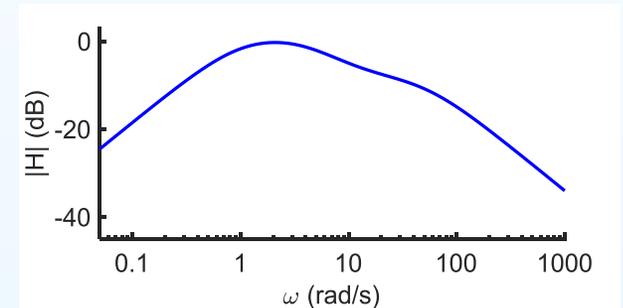

Plot Magnitude Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

The gain of a linear circuit is always a *rational polynomial* in $j\omega$ and is called the *transfer function* of the circuit. For example:


$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: Sort corner freqs: 1, 4, 12, 50

Step 3: For $\omega < 1$ all linear factors equal their constant terms:

$$|H| \approx \frac{20\omega \times 12}{1 \times 4 \times 50} = 1.2\omega^1.$$

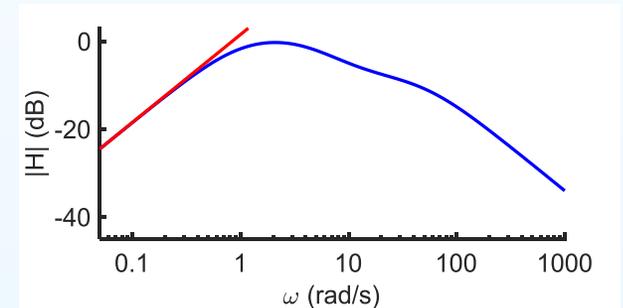

Plot Magnitude Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

The gain of a linear circuit is always a *rational polynomial* in $j\omega$ and is called the *transfer function* of the circuit. For example:

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials


Step 2: Sort corner freqs: 1, 4, 12, 50

Step 3: For $\omega < 1$ all linear factors equal their constant terms:

$$|H| \approx \frac{20\omega \times 12}{1 \times 4 \times 50} = 1.2\omega^1.$$

Step 4: For $1 < \omega < 4$, the factor $(j\omega + 1) \approx j\omega$ so

$$|H| \approx \frac{20\omega \times 12}{\omega \times 4 \times 50} = 1.2\omega^0$$

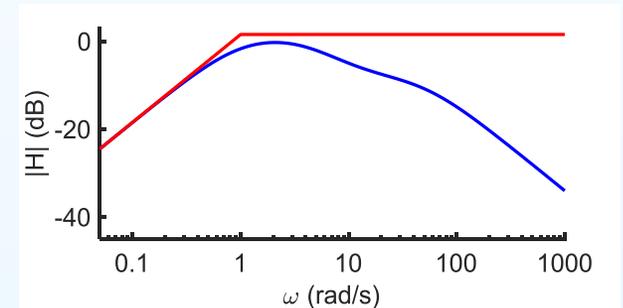

Plot Magnitude Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

The gain of a linear circuit is always a *rational polynomial* in $j\omega$ and is called the *transfer function* of the circuit. For example:

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials


Step 2: Sort corner freqs: 1, 4, 12, 50

Step 3: For $\omega < 1$ all linear factors equal their constant terms:

$$|H| \approx \frac{20\omega \times 12}{1 \times 4 \times 50} = 1.2\omega^1.$$

Step 4: For $1 < \omega < 4$, the factor $(j\omega + 1) \approx j\omega$ so

$$|H| \approx \frac{20\omega \times 12}{\omega \times 4 \times 50} = 1.2\omega^0 = +1.58 \text{ dB}.$$

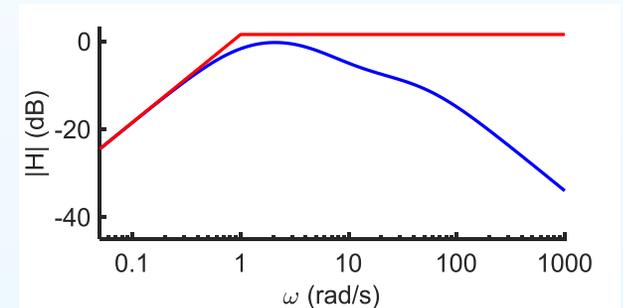

Plot Magnitude Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

The gain of a linear circuit is always a *rational polynomial* in $j\omega$ and is called the *transfer function* of the circuit. For example:

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: Sort corner freqs: 1, 4, 12, 50


Step 3: For $\omega < 1$ all linear factors equal their constant terms:

$$|H| \approx \frac{20\omega \times 12}{1 \times 4 \times 50} = 1.2\omega^1.$$

Step 4: For $1 < \omega < 4$, the factor $(j\omega + 1) \approx j\omega$ so

$$|H| \approx \frac{20\omega \times 12}{\omega \times 4 \times 50} = 1.2\omega^0 = +1.58 \text{ dB.}$$

Step 5: For $4 < \omega < 12$, $|H| \approx \frac{20\omega \times 12}{\omega \times \omega \times 50} = 4.8\omega^{-1}.$

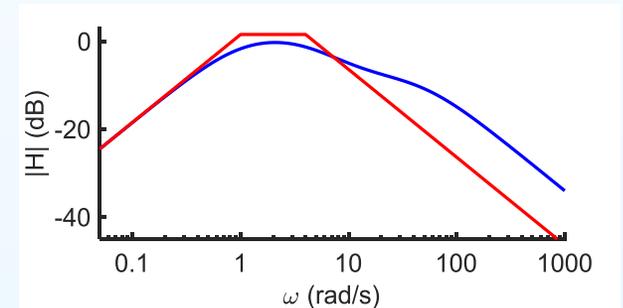

Plot Magnitude Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

The gain of a linear circuit is always a *rational polynomial* in $j\omega$ and is called the *transfer function* of the circuit. For example:

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: Sort corner freqs: 1, 4, 12, 50

Step 3: For $\omega < 1$ all linear factors equal their constant terms:


$$|H| \approx \frac{20\omega \times 12}{1 \times 4 \times 50} = 1.2\omega^1.$$

Step 4: For $1 < \omega < 4$, the factor $(j\omega + 1) \approx j\omega$ so

$$|H| \approx \frac{20\omega \times 12}{\omega \times 4 \times 50} = 1.2\omega^0 = +1.58 \text{ dB.}$$

Step 5: For $4 < \omega < 12$, $|H| \approx \frac{20\omega \times 12}{\omega \times \omega \times 50} = 4.8\omega^{-1}$.

Step 6: For $12 < \omega < 50$, $|H| \approx \frac{20\omega \times \omega}{\omega \times \omega \times 50} = 0.4\omega^0 = -7.96 \text{ dB.}$

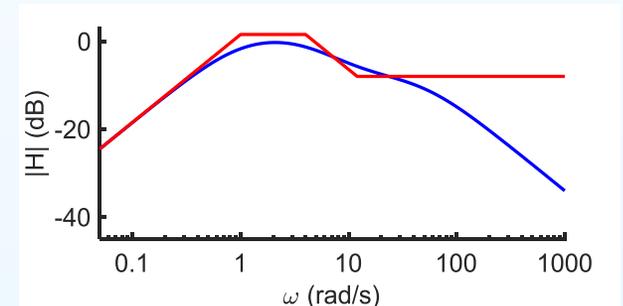

Plot Magnitude Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

The gain of a linear circuit is always a *rational polynomial* in $j\omega$ and is called the *transfer function* of the circuit. For example:

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: Sort corner freqs: 1, 4, 12, 50

Step 3: For $\omega < 1$ all linear factors equal their constant terms:

$$|H| \approx \frac{20\omega \times 12}{1 \times 4 \times 50} = 1.2\omega^1.$$


Step 4: For $1 < \omega < 4$, the factor $(j\omega + 1) \approx j\omega$ so

$$|H| \approx \frac{20\omega \times 12}{\omega \times 4 \times 50} = 1.2\omega^0 = +1.58 \text{ dB}.$$

Step 5: For $4 < \omega < 12$, $|H| \approx \frac{20\omega \times 12}{\omega \times \omega \times 50} = 4.8\omega^{-1}$.

Step 6: For $12 < \omega < 50$, $|H| \approx \frac{20\omega \times \omega}{\omega \times \omega \times 50} = 0.4\omega^0 = -7.96 \text{ dB}.$

Step 7: For $\omega > 50$, $|H| \approx \frac{20\omega \times \omega}{\omega \times \omega \times \omega} = 20\omega^{-1}$.

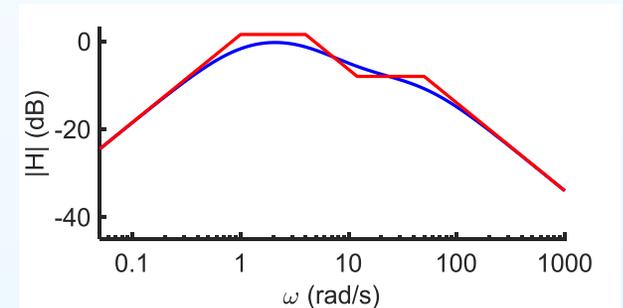

Plot Magnitude Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

The gain of a linear circuit is always a *rational polynomial* in $j\omega$ and is called the *transfer function* of the circuit. For example:

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: Sort corner freqs: 1, 4, 12, 50

Step 3: For $\omega < 1$ all linear factors equal their constant terms:

$$|H| \approx \frac{20\omega \times 12}{1 \times 4 \times 50} = 1.2\omega^1.$$

Step 4: For $1 < \omega < 4$, the factor $(j\omega + 1) \approx j\omega$ so


$$|H| \approx \frac{20\omega \times 12}{\omega \times 4 \times 50} = 1.2\omega^0 = +1.58 \text{ dB.}$$

Step 5: For $4 < \omega < 12$, $|H| \approx \frac{20\omega \times 12}{\omega \times \omega \times 50} = 4.8\omega^{-1}$.

Step 6: For $12 < \omega < 50$, $|H| \approx \frac{20\omega \times \omega}{\omega \times \omega \times 50} = 0.4\omega^0 = -7.96 \text{ dB.}$

Step 7: For $\omega > 50$, $|H| \approx \frac{20\omega \times \omega}{\omega \times \omega \times \omega} = 20\omega^{-1}$.

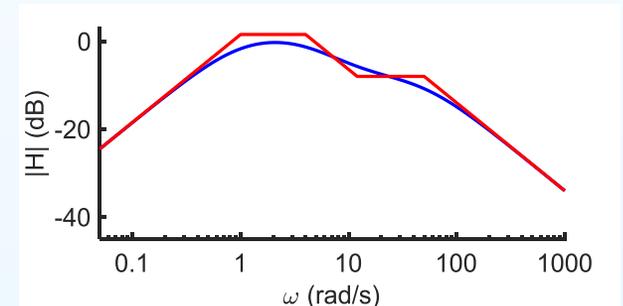At each corner frequency, the graph is continuous but its gradient changes abruptly by $+1$ (numerator factor) or -1 (denominator factor).



Low and High Frequency Asymptotes

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- **Low and High Frequency Asymptotes**
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

You can find the low and high frequency asymptotes without factorizing:

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$



Low and High Frequency Asymptotes

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- **Low and High Frequency Asymptotes**
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

You can find the low and high frequency asymptotes without factorizing:
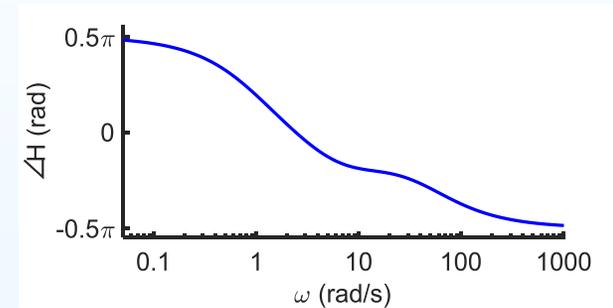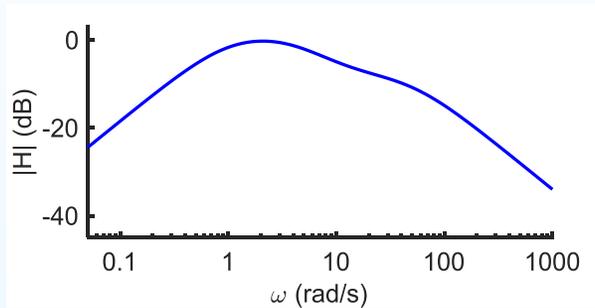
$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$





Low and High Frequency Asymptotes

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- **Low and High Frequency Asymptotes**
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

You can find the low and high frequency asymptotes without factorizing:
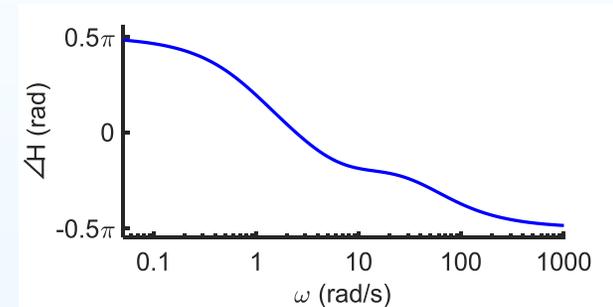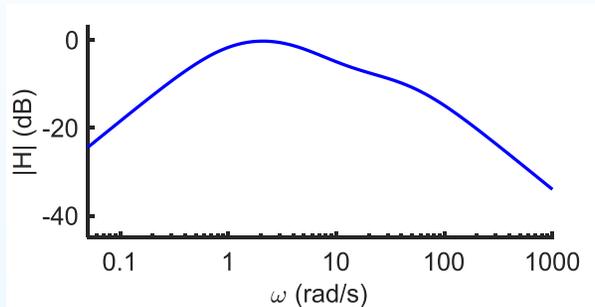
$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$



Low Frequency Asymptote:



Low and High Frequency Asymptotes

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- **Low and High Frequency Asymptotes**
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

You can find the low and high frequency asymptotes without factorizing:
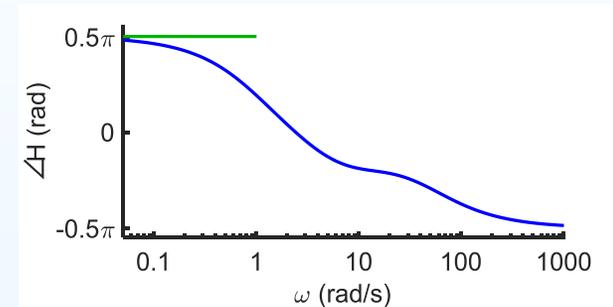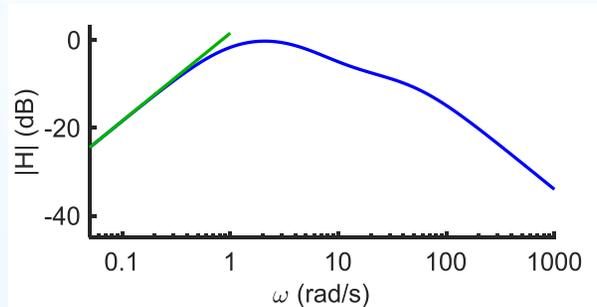
$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$



Low Frequency Asymptote:

$$\text{From factors: } H_{LF}(j\omega) = \frac{20j\omega(12)}{(1)(4)(50)} = 1.2j\omega$$



Low and High Frequency Asymptotes

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- **Low and High Frequency Asymptotes**
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

You can find the low and high frequency asymptotes without factorizing:
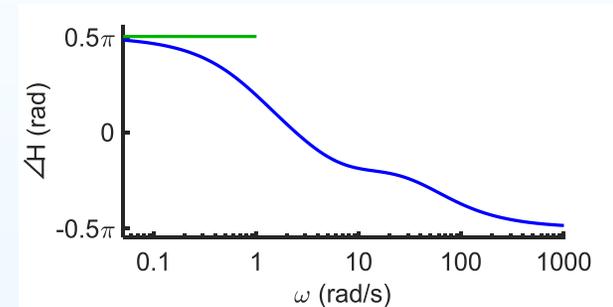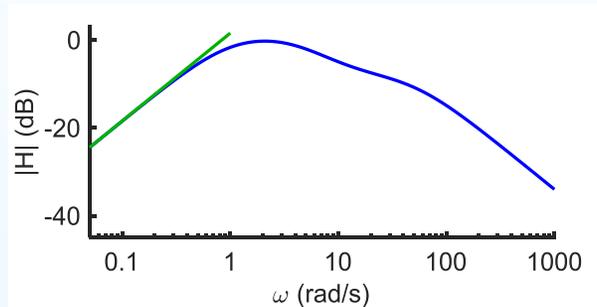
$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$



Low Frequency Asymptote:

From factors: $H_{LF}(j\omega) = \frac{20j\omega(12)}{(1)(4)(50)} = 1.2j\omega$

Lowest power of $j\omega$ on top and bottom: $H(j\omega) \simeq \frac{720(j\omega)}{600} = 1.2j\omega$



Low and High Frequency Asymptotes

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- **Low and High Frequency Asymptotes**
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

You can find the low and high frequency asymptotes without factorizing:
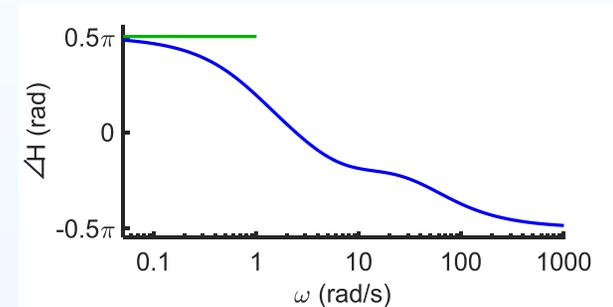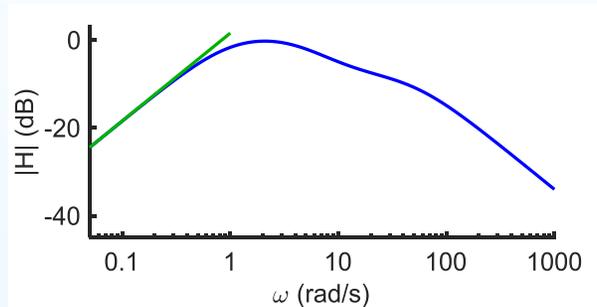
$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$



Low Frequency Asymptote:

From factors: $H_{LF}(j\omega) = \frac{20j\omega(12)}{(1)(4)(50)} = 1.2j\omega$

Lowest power of $j\omega$ on top and bottom: $H(j\omega) \simeq \frac{720(j\omega)}{600} = 1.2j\omega$

High Frequency Asymptote:



Low and High Frequency Asymptotes

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- **Low and High Frequency Asymptotes**
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

You can find the low and high frequency asymptotes without factorizing:
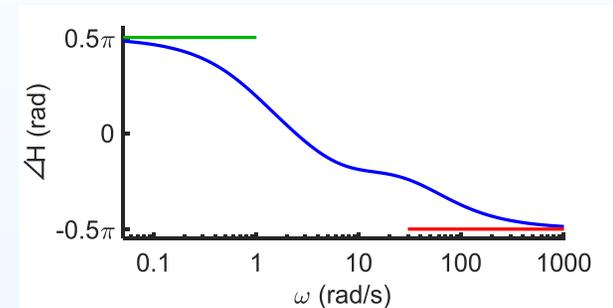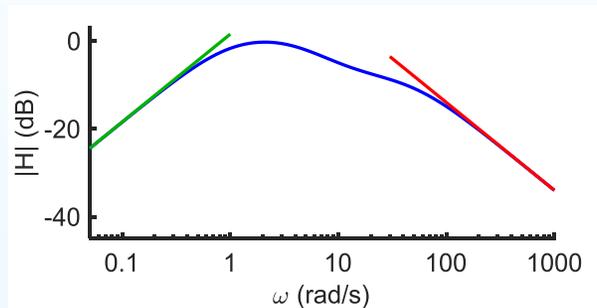
$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$



Low Frequency Asymptote:

From factors: $H_{LF}(j\omega) = \frac{20j\omega(12)}{(1)(4)(50)} = 1.2j\omega$

Lowest power of $j\omega$ on top and bottom: $H(j\omega) \simeq \frac{720(j\omega)}{600} = 1.2j\omega$

High Frequency Asymptote:

From factors: $H_{HF}(j\omega) = \frac{20j\omega(j\omega)}{(j\omega)(j\omega)(j\omega)} = 20(j\omega)^{-1}$



Low and High Frequency Asymptotes

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- **Low and High Frequency Asymptotes**
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

You can find the low and high frequency asymptotes without factorizing:
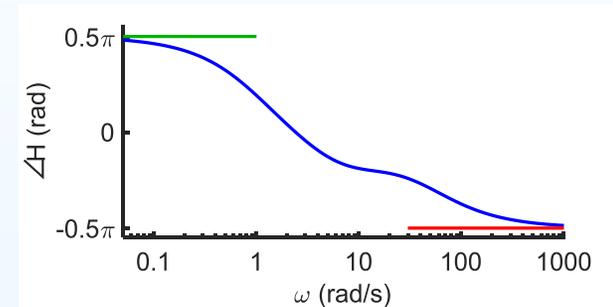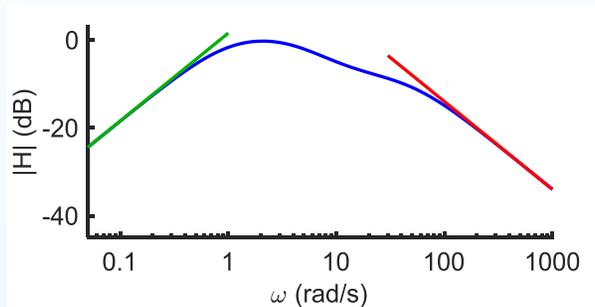
$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$



Low Frequency Asymptote:

From factors: $H_{LF}(j\omega) = \frac{20j\omega(12)}{(1)(4)(50)} = 1.2j\omega$

Lowest power of $j\omega$ on top and bottom: $H(j\omega) \simeq \frac{720(j\omega)}{600} = 1.2j\omega$

High Frequency Asymptote:

From factors: $H_{HF}(j\omega) = \frac{20j\omega(j\omega)}{(j\omega)(j\omega)(j\omega)} = 20(j\omega)^{-1}$


Highest power of $j\omega$ on top and bottom: $H(j\omega) \simeq \frac{60(j\omega)^2}{3(j\omega)^3} = 20(j\omega)^{-1}$

Phase Approximation

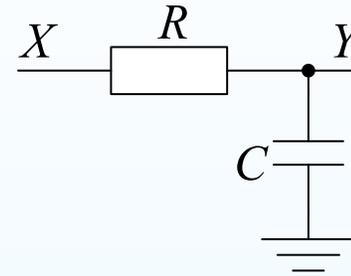11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- **Phase Approximation** +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$



Phase Approximation



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- **Phase Approximation** +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

Low frequencies ($\omega \ll \frac{1}{RC}$):

$$H(j\omega) \approx 1$$

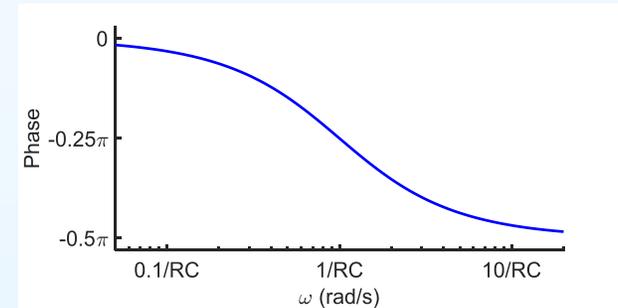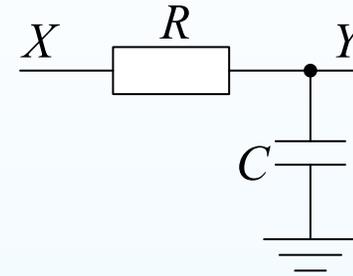

Phase Approximation



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- **Phase Approximation** +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

Low frequencies ($\omega \ll \frac{1}{RC}$):
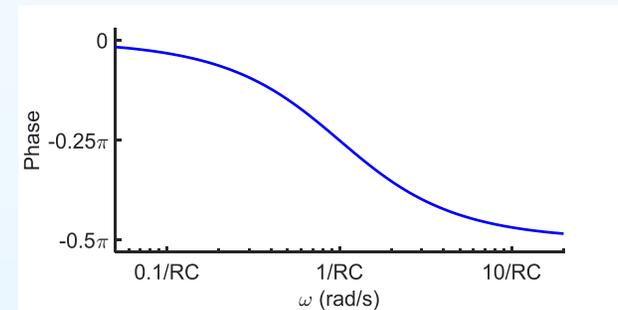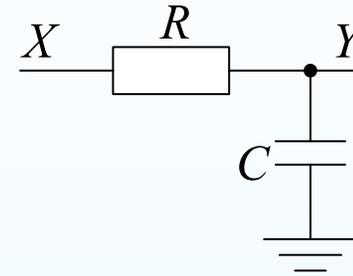
$$H(j\omega) \approx 1 \Rightarrow \angle 1 = 0$$



Phase Approximation

11: Frequency Responses



- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- **Phase Approximation** +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

Low frequencies ($\omega \ll \frac{1}{RC}$):

$$H(j\omega) \approx 1 \Rightarrow \angle 1 = 0$$

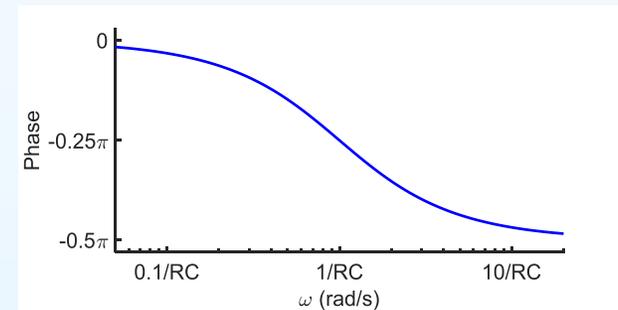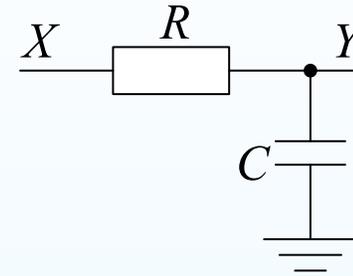High frequencies ($\omega \gg \frac{1}{RC}$): $H(j\omega) \approx \frac{1}{j\omega RC}$



Phase Approximation

11: Frequency Responses



- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- **Phase Approximation** +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

Low frequencies ($\omega \ll \frac{1}{RC}$):

$$H(j\omega) \approx 1 \Rightarrow \angle 1 = 0$$

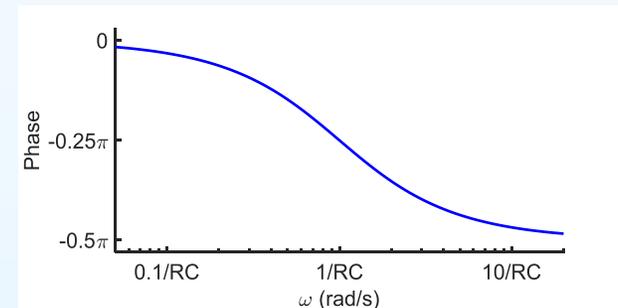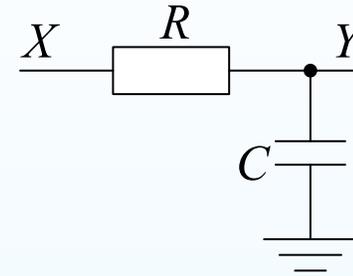High frequencies ($\omega \gg \frac{1}{RC}$): $H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow \angle j^{-1} = -\frac{\pi}{2}$



Phase Approximation

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary



Gain: $H(j\omega) = \frac{1}{j\omega RC + 1}$

Low frequencies ($\omega \ll \frac{1}{RC}$):

$$H(j\omega) \approx 1 \Rightarrow \angle 1 = 0$$

High frequencies ($\omega \gg \frac{1}{RC}$): $H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow \angle j^{-1} = -\frac{\pi}{2}$

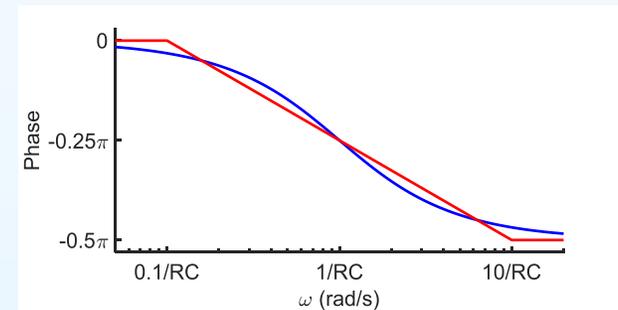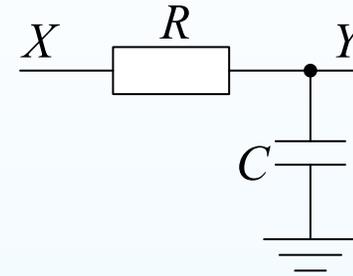Approximate the phase response as three straight lines.



Phase Approximation

11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- **Phase Approximation** +
- Plot Phase Response +
- RCR Circuit
- Summary

Gain: $H(j\omega) = \frac{1}{j\omega RC + 1}$

Low frequencies ($\omega \ll \frac{1}{RC}$):


$$H(j\omega) \approx 1 \Rightarrow \angle 1 = 0$$

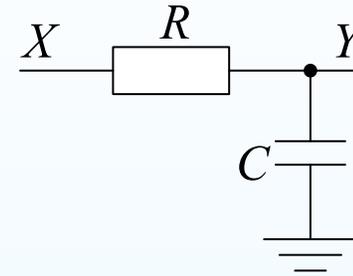High frequencies ($\omega \gg \frac{1}{RC}$): $H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow \angle j^{-1} = -\frac{\pi}{2}$



Approximate the phase response as three straight lines.

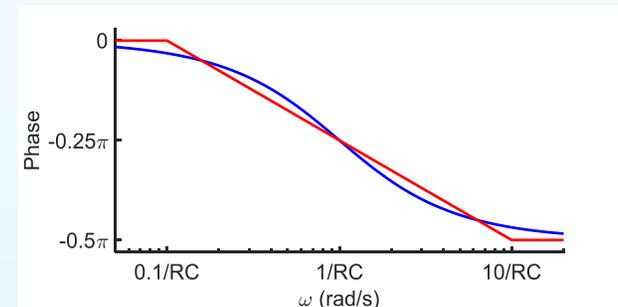By chance, they intersect close to $0.1\omega_c$ and $10\omega_c$ where $\omega_c = \frac{1}{RC}$.



Phase Approximation

11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\text{Gain: } H(j\omega) = \frac{1}{j\omega RC + 1}$$

Low frequencies ($\omega \ll \frac{1}{RC}$):


$$H(j\omega) \approx 1 \Rightarrow \angle 1 = 0$$

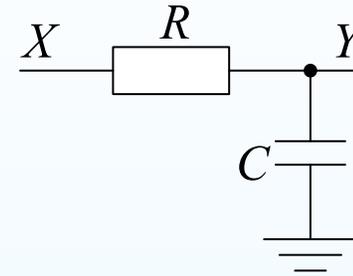High frequencies ($\omega \gg \frac{1}{RC}$): $H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow \angle j^{-1} = -\frac{\pi}{2}$



Approximate the phase response as three straight lines.

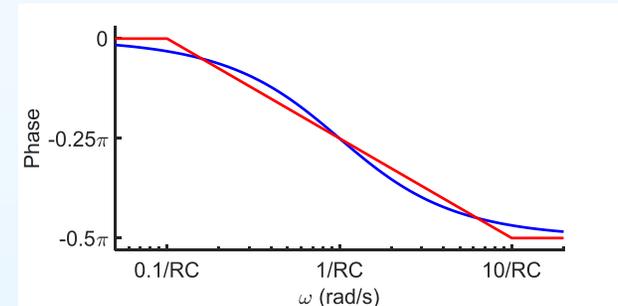By chance, they intersect close to $0.1\omega_c$ and $10\omega_c$ where $\omega_c = \frac{1}{RC}$.



Between $0.1\omega_c$ and $10\omega_c$ the phase changes by $-\frac{\pi}{2}$ over two decades. This gives a gradient = $-\frac{\pi}{4}$ radians/decade.

Phase Approximation

11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

Gain: $H(j\omega) = \frac{1}{j\omega RC + 1}$

Low frequencies ($\omega \ll \frac{1}{RC}$):


$$H(j\omega) \approx 1 \Rightarrow \angle 1 = 0$$

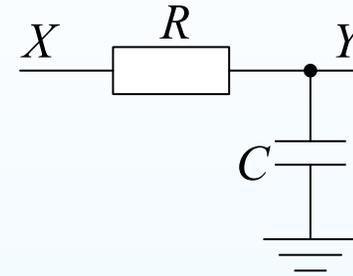High frequencies ($\omega \gg \frac{1}{RC}$): $H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow \angle j^{-1} = -\frac{\pi}{2}$



Approximate the phase response as three straight lines.

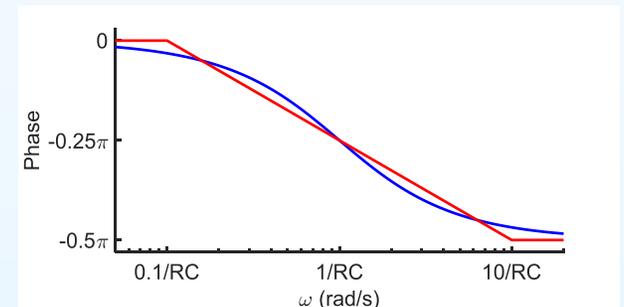By chance, they intersect close to $0.1\omega_c$ and $10\omega_c$ where $\omega_c = \frac{1}{RC}$.



Between $0.1\omega_c$ and $10\omega_c$ the phase changes by $-\frac{\pi}{2}$ over two decades. This gives a gradient = $-\frac{\pi}{4}$ radians/decade.

$(aj\omega + b)$ in denominator

$$\Rightarrow \Delta\text{gradient} = \mp \frac{\pi}{4} / \text{decade at } \omega = 10^{\mp 1} \left| \frac{b}{a} \right|.$$

Phase Approximation

11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- **Phase Approximation** +
- Plot Phase Response +
- RCR Circuit
- Summary

Gain: $H(j\omega) = \frac{1}{j\omega RC + 1}$

Low frequencies ($\omega \ll \frac{1}{RC}$):


$$H(j\omega) \approx 1 \Rightarrow \angle 1 = 0$$

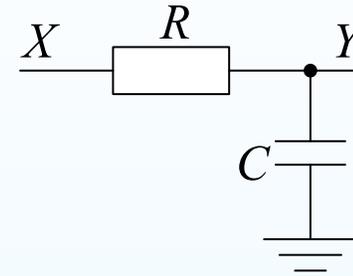High frequencies ($\omega \gg \frac{1}{RC}$): $H(j\omega) \approx \frac{1}{j\omega RC} \Rightarrow \angle j^{-1} = -\frac{\pi}{2}$



Approximate the phase response as three straight lines.

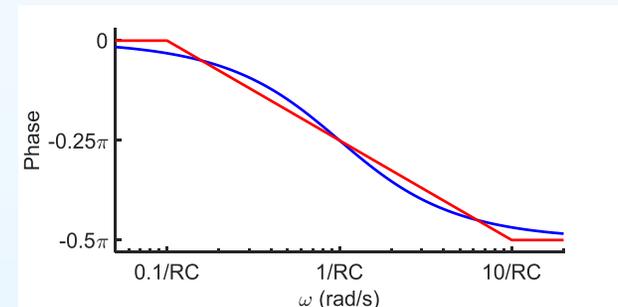By chance, they intersect close to $0.1\omega_c$ and $10\omega_c$ where $\omega_c = \frac{1}{RC}$.



Between $0.1\omega_c$ and $10\omega_c$ the phase changes by $-\frac{\pi}{2}$ over two decades. This gives a gradient = $-\frac{\pi}{4}$ radians/decade.

$(aj\omega + b)$ in denominator

$$\Rightarrow \Delta\text{gradient} = \mp \frac{\pi}{4} / \text{decade at } \omega = 10^{\mp 1} \left| \frac{b}{a} \right|.$$


The sign of $\Delta\text{gradient}$ is reversed for (a) numerator factors and (b) $\frac{b}{a} < 0$.

Plot Phase Response

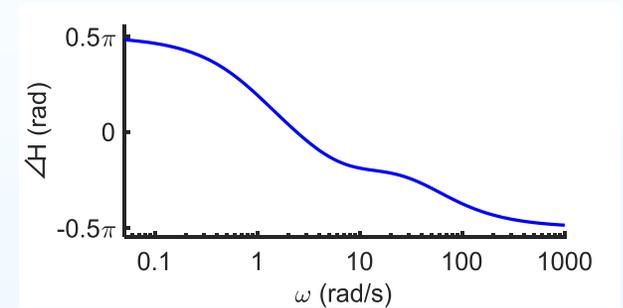11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- **Plot Phase Response** +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600}$$



Plot Phase Response

11: Frequency Responses


- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- **Plot Phase Response** +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

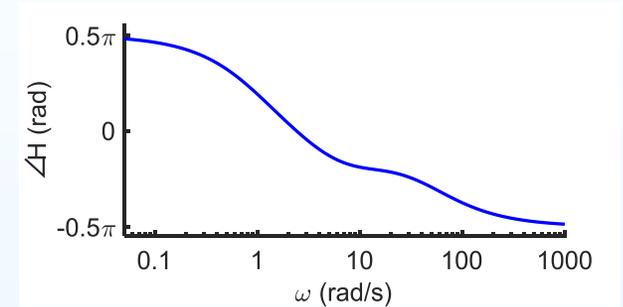

Plot Phase Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- **Plot Phase Response** +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials


Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.

Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:
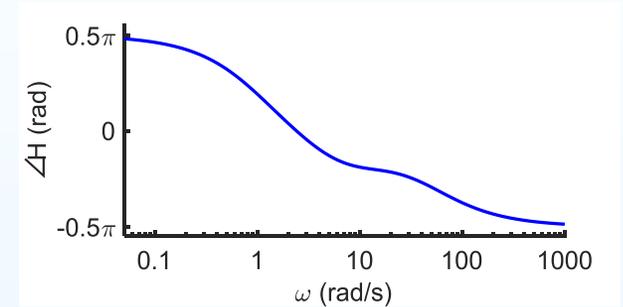
$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$



Plot Phase Response



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$


Step 3: Gradient changes at $10^{\mp 1} \omega_c$.

Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:

$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$

Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:
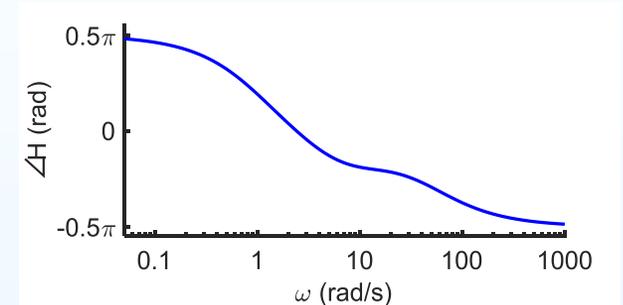
$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$



Plot Phase Response



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.


Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:

$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$

Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:

$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$

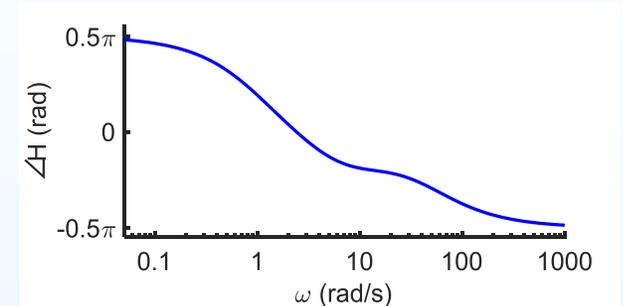Step 5: Find phase of LF asymptote: $\angle 1.2j\omega = +\frac{\pi}{2}$.



Plot Phase Response



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.


Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:

$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$

Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:

$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$

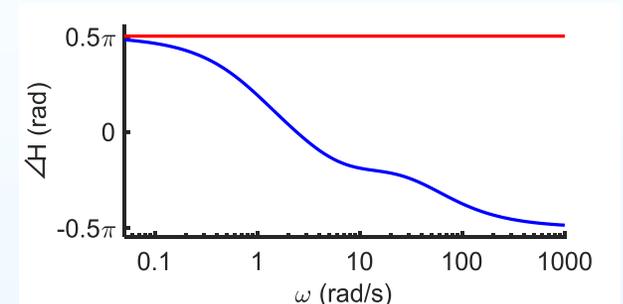Step 5: Find phase of LF asymptote: $\angle 1.2j\omega = +\frac{\pi}{2}$.



Plot Phase Response



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- **Plot Phase Response** +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.

Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:


$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$

Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:

$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$

Step 5: Find phase of LF asymptote: $\angle 1.2j\omega = +\frac{\pi}{2}$.

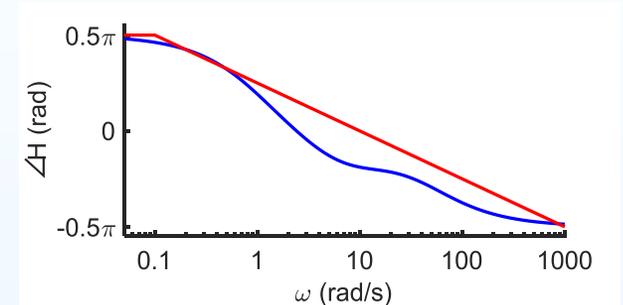Step 6: At $\omega = 0.1$ gradient becomes $-\frac{\pi}{4}$ rad/decade. ϕ is still $\frac{\pi}{2}$.



Plot Phase Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.

Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:

$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$


Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:

$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$

Step 5: Find phase of LF asymptote: $\angle 1.2j\omega = +\frac{\pi}{2}$.

Step 6: At $\omega = 0.1$ gradient becomes $-\frac{\pi}{4}$ rad/decade. ϕ is still $\frac{\pi}{2}$.

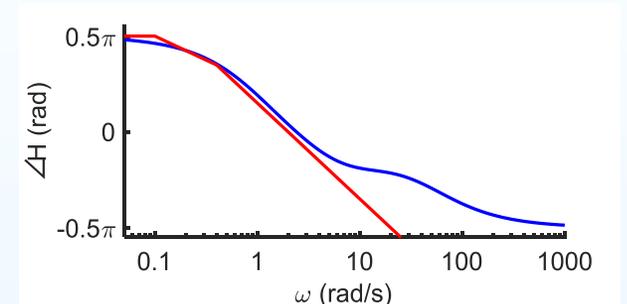Step 7: At $\omega = 0.4$, $\phi = \frac{\pi}{2} - 0.6\frac{\pi}{4} = 0.35\pi$. New gradient is $-\frac{\pi}{2}$.



Plot Phase Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.

Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:

$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$

Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:


$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$

Step 5: Find phase of LF asymptote: $\angle 1.2j\omega = +\frac{\pi}{2}$.

Step 6: At $\omega = 0.1$ gradient becomes $-\frac{\pi}{4}$ rad/decade. ϕ is still $\frac{\pi}{2}$.

Step 7: At $\omega = 0.4$, $\phi = \frac{\pi}{2} - 0.6\frac{\pi}{4} = 0.35\pi$. New gradient is $-\frac{\pi}{2}$.

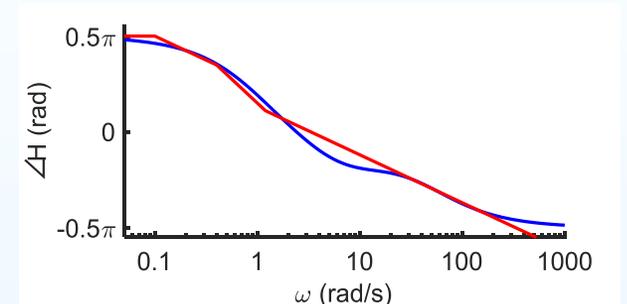Step 8: At $\omega = 1.2$, $\phi = 0.35\pi - 0.48\frac{\pi}{2} = 0.11\pi$. New gradient is $-\frac{\pi}{4}$.



Plot Phase Response



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- **Plot Phase Response** +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.

Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:

$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$

Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:

$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$


Step 5: Find phase of LF asymptote: $\angle 1.2j\omega = +\frac{\pi}{2}$.

Step 6: At $\omega = 0.1$ gradient becomes $-\frac{\pi}{4}$ rad/decade. ϕ is still $\frac{\pi}{2}$.

Step 7: At $\omega = 0.4$, $\phi = \frac{\pi}{2} - 0.6\frac{\pi}{4} = 0.35\pi$. New gradient is $-\frac{\pi}{2}$.

Step 8: At $\omega = 1.2$, $\phi = 0.35\pi - 0.48\frac{\pi}{2} = 0.11\pi$. New gradient is $-\frac{\pi}{4}$.

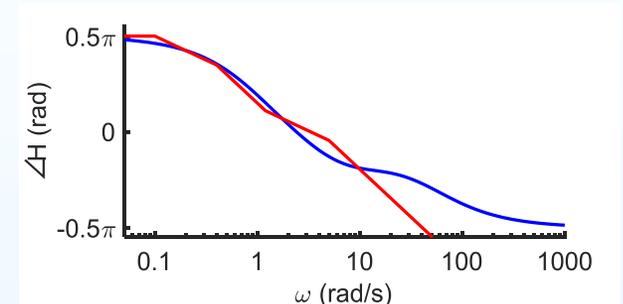Steps 9-13: Repeat for each gradient change.



Plot Phase Response



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.

Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:

$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$

Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:

$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$


Step 5: Find phase of LF asymptote: $\angle 1.2j\omega = +\frac{\pi}{2}$.

Step 6: At $\omega = 0.1$ gradient becomes $-\frac{\pi}{4}$ rad/decade. ϕ is still $\frac{\pi}{2}$.

Step 7: At $\omega = 0.4$, $\phi = \frac{\pi}{2} - 0.6\frac{\pi}{4} = 0.35\pi$. New gradient is $-\frac{\pi}{2}$.

Step 8: At $\omega = 1.2$, $\phi = 0.35\pi - 0.48\frac{\pi}{2} = 0.11\pi$. New gradient is $-\frac{\pi}{4}$.

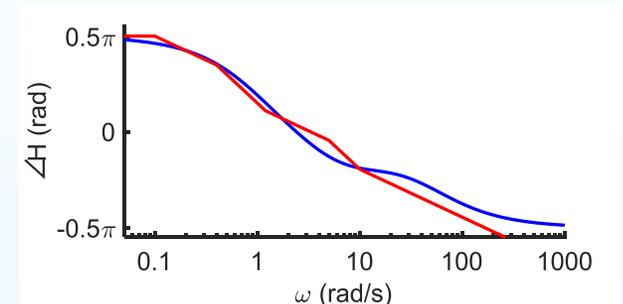Steps 9-13: Repeat for each gradient change.



Plot Phase Response

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.

Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:

$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$

Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:

$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$


Step 5: Find phase of LF asymptote: $\angle 1.2j\omega = +\frac{\pi}{2}$.

Step 6: At $\omega = 0.1$ gradient becomes $-\frac{\pi}{4}$ rad/decade. ϕ is still $\frac{\pi}{2}$.

Step 7: At $\omega = 0.4$, $\phi = \frac{\pi}{2} - 0.6\frac{\pi}{4} = 0.35\pi$. New gradient is $-\frac{\pi}{2}$.

Step 8: At $\omega = 1.2$, $\phi = 0.35\pi - 0.48\frac{\pi}{2} = 0.11\pi$. New gradient is $-\frac{\pi}{4}$.

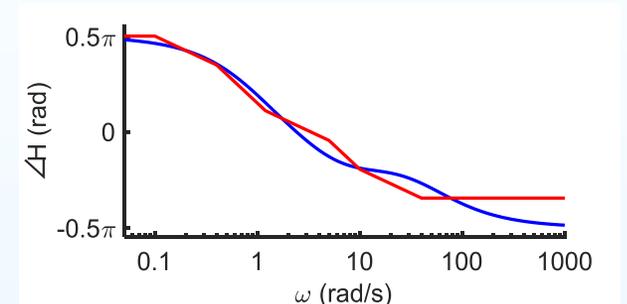Steps 9-13: Repeat for each gradient change.



Plot Phase Response



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.

Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:

$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$

Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:

$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$


Step 5: Find phase of LF asymptote: $\angle 1.2j\omega = +\frac{\pi}{2}$.

Step 6: At $\omega = 0.1$ gradient becomes $-\frac{\pi}{4}$ rad/decade. ϕ is still $\frac{\pi}{2}$.

Step 7: At $\omega = 0.4$, $\phi = \frac{\pi}{2} - 0.6\frac{\pi}{4} = 0.35\pi$. New gradient is $-\frac{\pi}{2}$.

Step 8: At $\omega = 1.2$, $\phi = 0.35\pi - 0.48\frac{\pi}{2} = 0.11\pi$. New gradient is $-\frac{\pi}{4}$.

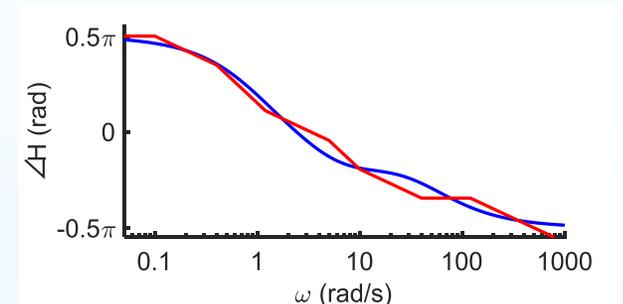Steps 9-13: Repeat for each gradient change.



Plot Phase Response



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.

Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:

$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$

Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:

$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$


Step 5: Find phase of LF asymptote: $\angle 1.2j\omega = +\frac{\pi}{2}$.

Step 6: At $\omega = 0.1$ gradient becomes $-\frac{\pi}{4}$ rad/decade. ϕ is still $\frac{\pi}{2}$.

Step 7: At $\omega = 0.4$, $\phi = \frac{\pi}{2} - 0.6\frac{\pi}{4} = 0.35\pi$. New gradient is $-\frac{\pi}{2}$.

Step 8: At $\omega = 1.2$, $\phi = 0.35\pi - 0.48\frac{\pi}{2} = 0.11\pi$. New gradient is $-\frac{\pi}{4}$.

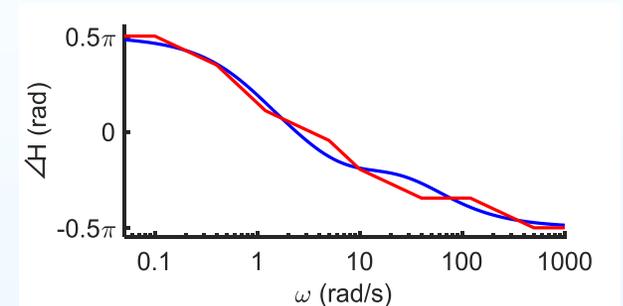Steps 9-13: Repeat for each gradient change. Final gradient is always 0.



Plot Phase Response



11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600} = \frac{20j\omega(j\omega + 12)}{(j\omega + 1)(j\omega + 4)(j\omega + 50)}$$

Step 1: Factorize the polynomials

Step 2: List corner freqs: $\pm = \text{num/den}$

$$\omega_c = \{1^-, 4^-, 12^+, 50^-\}$$

Step 3: Gradient changes at $10^{\mp 1} \omega_c$.

Sign depends on num/den and $\text{sgn}\left(\frac{b}{a}\right)$:

$$.1^-, 10^+; .4^-, 40^+; 1.2^+, 120^-; 5^-, 500^+$$

Step 4: Put in ascending order and calculate gaps as $\log_{10} \frac{\omega_2}{\omega_1}$ decades:

$$.1^- (.6) .4^- (.48) 1.2^+ (.62) 5^- (.3) 10^+ (.6) 40^+ (.48) 120^- (.62) 500^+.$$

Step 5: Find phase of LF asymptote: $\angle 1.2j\omega = +\frac{\pi}{2}$.


Step 6: At $\omega = 0.1$ gradient becomes $-\frac{\pi}{4}$ rad/decade. ϕ is still $\frac{\pi}{2}$.

Step 7: At $\omega = 0.4$, $\phi = \frac{\pi}{2} - 0.6\frac{\pi}{4} = 0.35\pi$. New gradient is $-\frac{\pi}{2}$.

Step 8: At $\omega = 1.2$, $\phi = 0.35\pi - 0.48\frac{\pi}{2} = 0.11\pi$. New gradient is $-\frac{\pi}{4}$.

Steps 9-13: Repeat for each gradient change. Final gradient is always 0.

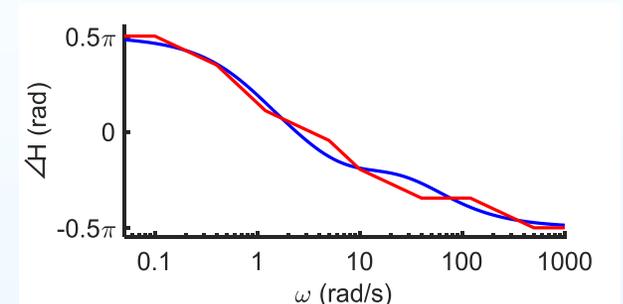
At 0.1 and 10 times each corner frequency, the graph is continuous but its gradient changes abruptly by $\pm \frac{\pi}{4}$ rad/decade.



RCR Circuit

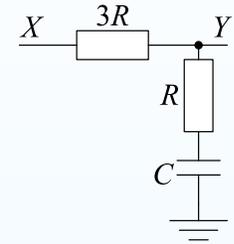11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- **RCR Circuit**
- Summary




RCR Circuit

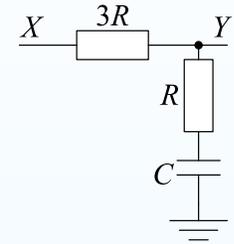11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- **RCR Circuit**
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}}$$






RCR Circuit

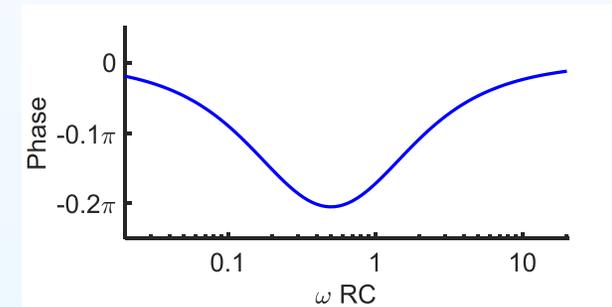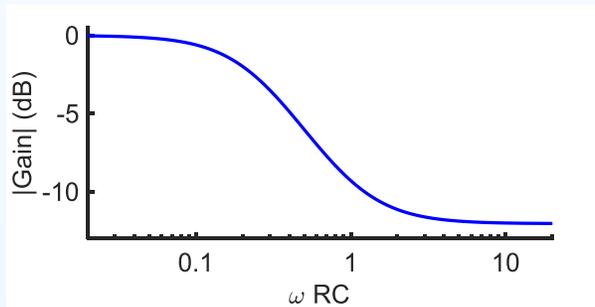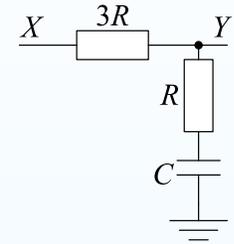11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}} = \frac{j\omega RC + 1}{4j\omega RC + 1}$$






RCR Circuit

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}} = \frac{j\omega RC + 1}{4j\omega RC + 1}$$

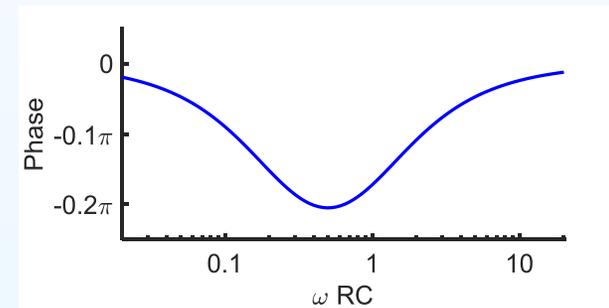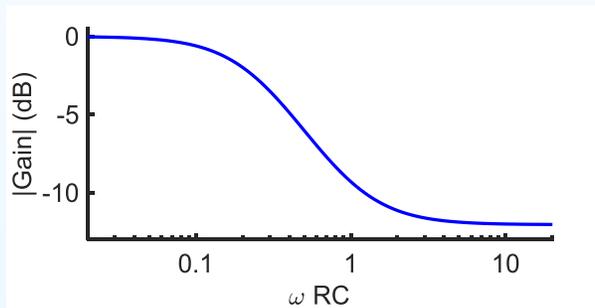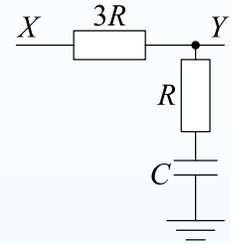Corner freqs: $\frac{0.25}{RC}^-$, $\frac{1}{RC}^+$






RCR Circuit

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}} = \frac{j\omega RC + 1}{4j\omega RC + 1}$$

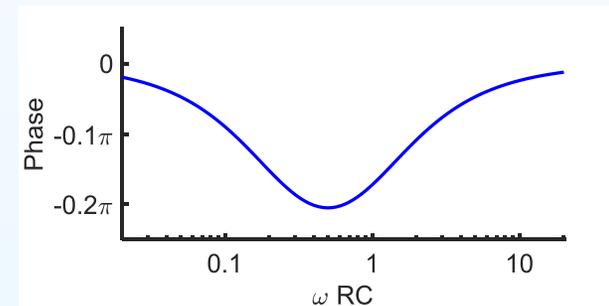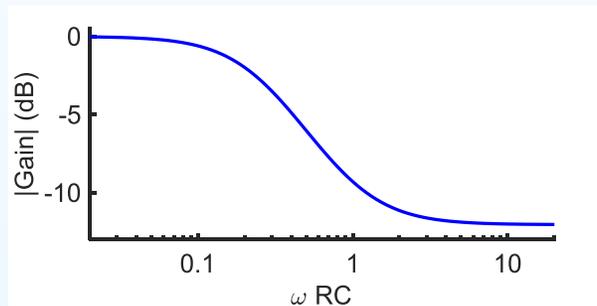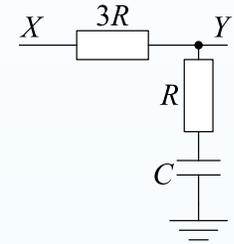Corner freqs: $\frac{0.25}{RC}^-$, $\frac{1}{RC}^+$ LF Asymptote: $H(j\omega) = 1$






RCR Circuit

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}} = \frac{j\omega RC + 1}{4j\omega RC + 1}$$

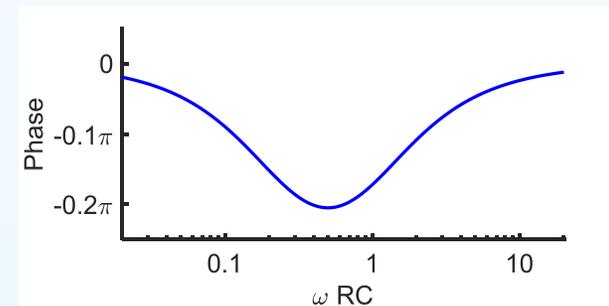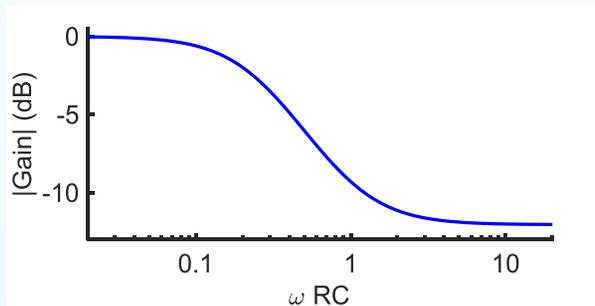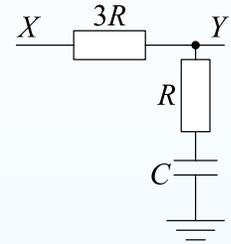Corner freqs: $\frac{0.25}{RC}^-$, $\frac{1}{RC}^+$ LF Asymptote: $H(j\omega) = 1$



Magnitude Response:




RCR Circuit

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}} = \frac{j\omega RC + 1}{4j\omega RC + 1}$$

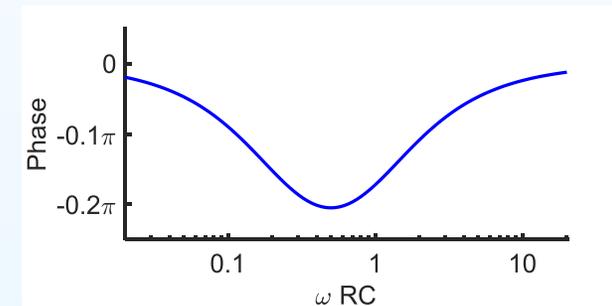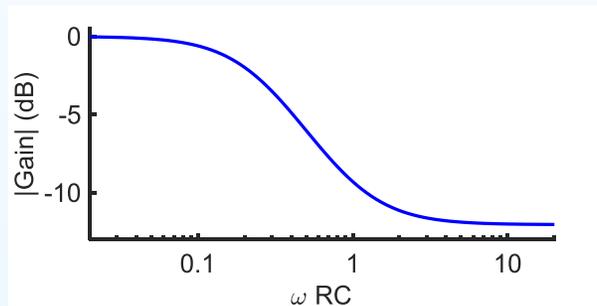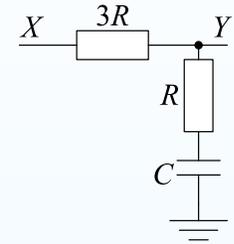Corner freqs: $\frac{0.25}{RC}^-$, $\frac{1}{RC}^+$ LF Asymptote: $H(j\omega) = 1$



Magnitude Response:

Gradient Changes: -20 dB/dec at $\omega = \frac{0.25}{RC}$ and $+20$ at $\omega = \frac{1}{RC}$




RCR Circuit

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- **RCR Circuit**
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}} = \frac{j\omega RC + 1}{4j\omega RC + 1}$$

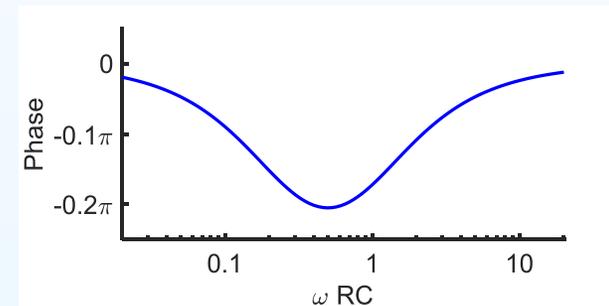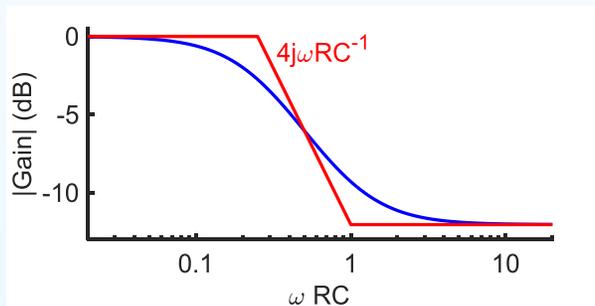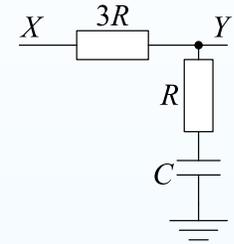Corner freqs: $\frac{0.25}{RC}^-$, $\frac{1}{RC}^+$ LF Asymptote: $H(j\omega) = 1$



Magnitude Response:

Gradient Changes: -20 dB/dec at $\omega = \frac{0.25}{RC}$ and $+20$ at $\omega = \frac{1}{RC}$




RCR Circuit

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}} = \frac{j\omega RC + 1}{4j\omega RC + 1}$$

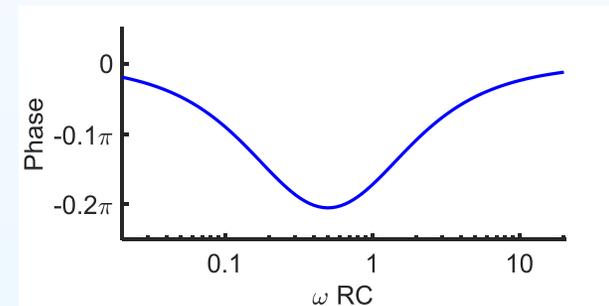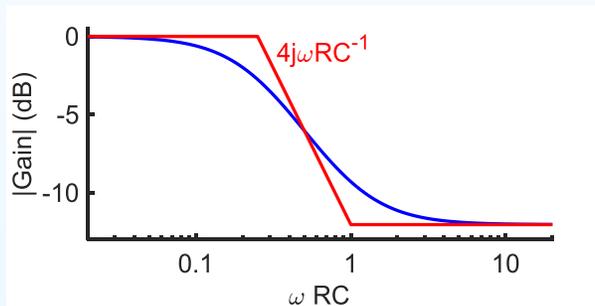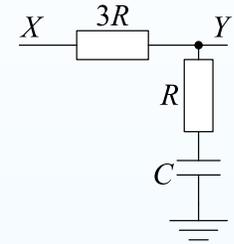Corner freqs: $\frac{0.25}{RC}^-$, $\frac{1}{RC}^+$ LF Asymptote: $H(j\omega) = 1$



Magnitude Response:

Gradient Changes: -20 dB/dec at $\omega = \frac{0.25}{RC}$ and $+20$ at $\omega = \frac{1}{RC}$

Line equations: $H(j\omega) =$ (a) 1 , (b) $\frac{1}{4j\omega RC}$, (c) $\frac{j\omega RC}{4j\omega RC} = 0.25$




RCR Circuit

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- **RCR Circuit**
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}} = \frac{j\omega RC + 1}{4j\omega RC + 1}$$

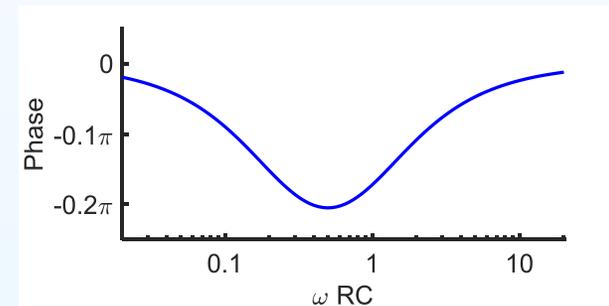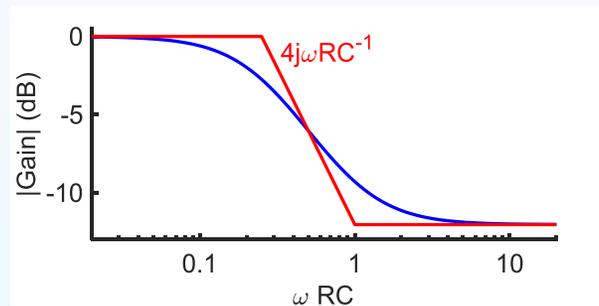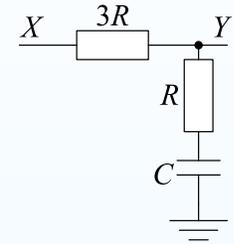Corner freqs: $\frac{0.25}{RC}^-$, $\frac{1}{RC}^+$ LF Asymptote: $H(j\omega) = 1$



Magnitude Response:

Gradient Changes: -20 dB/dec at $\omega = \frac{0.25}{RC}$ and $+20$ at $\omega = \frac{1}{RC}$

Line equations: $H(j\omega) =$ (a) 1, (b) $\frac{1}{4j\omega RC}$, (c) $\frac{j\omega RC}{4j\omega RC} = 0.25$

Phase Response:




RCR Circuit

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- **RCR Circuit**
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}} = \frac{j\omega RC + 1}{4j\omega RC + 1}$$

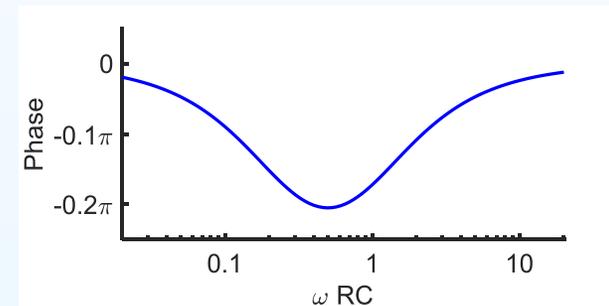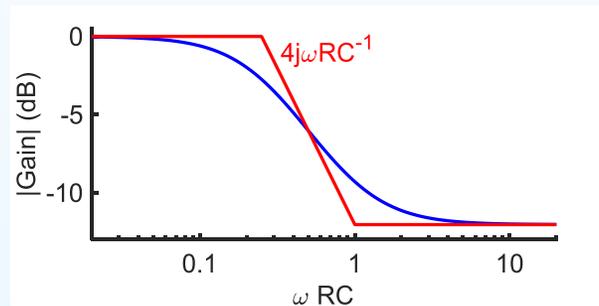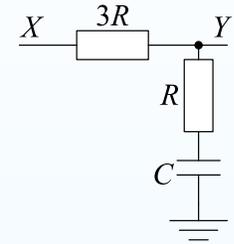Corner freqs: $\frac{0.25}{RC}^-$, $\frac{1}{RC}^+$ LF Asymptote: $H(j\omega) = 1$



Magnitude Response:

Gradient Changes: -20 dB/dec at $\omega = \frac{0.25}{RC}$ and $+20$ at $\omega = \frac{1}{RC}$

Line equations: $H(j\omega) =$ (a) 1 , (b) $\frac{1}{4j\omega RC}$, (c) $\frac{j\omega RC}{4j\omega RC} = 0.25$

Phase Response:

LF asymptote: $\phi = \angle 1 = 0$




RCR Circuit

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}} = \frac{j\omega RC + 1}{4j\omega RC + 1}$$

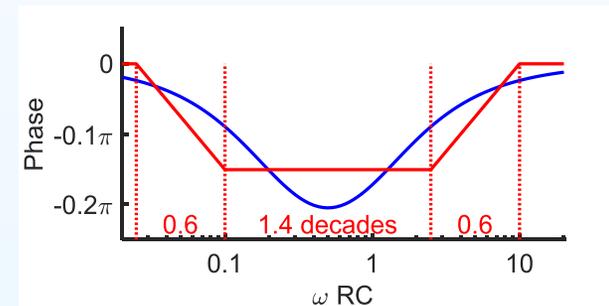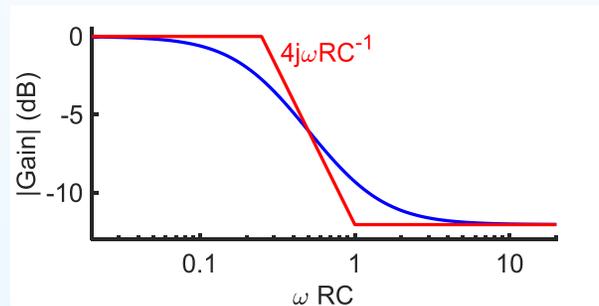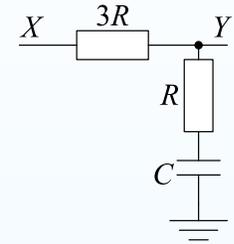Corner freqs: $\frac{0.25}{RC}^-$, $\frac{1}{RC}^+$ LF Asymptote: $H(j\omega) = 1$



Magnitude Response:

Gradient Changes: -20 dB/dec at $\omega = \frac{0.25}{RC}$ and $+20$ at $\omega = \frac{1}{RC}$

Line equations: $H(j\omega) =$ (a) 1 , (b) $\frac{1}{4j\omega RC}$, (c) $\frac{j\omega RC}{4j\omega RC} = 0.25$

Phase Response:

LF asymptote: $\phi = \angle 1 = 0$

Gradient changes of $\pm \frac{\pi}{4}$ /decade at: $\omega = \frac{0.025}{RC}^-$, $\frac{0.1}{RC}^+$, $\frac{2.5}{RC}^+$, $\frac{10}{RC}^-$.




RCR Circuit

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

$$\frac{Y}{X} = \frac{R + \frac{1}{j\omega C}}{3R + R + \frac{1}{j\omega C}} = \frac{j\omega RC + 1}{4j\omega RC + 1}$$

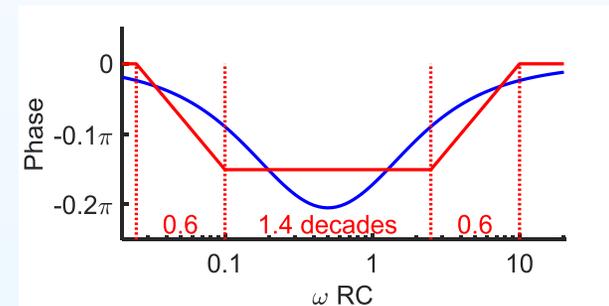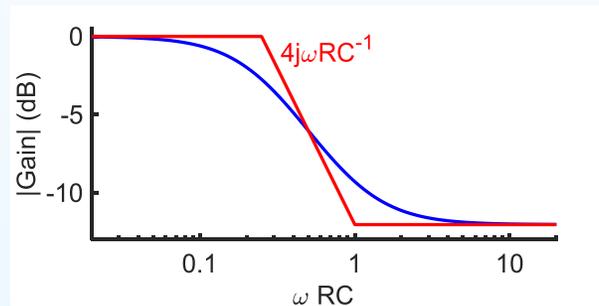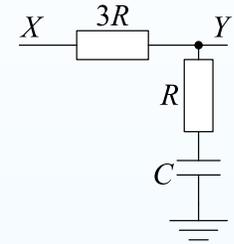Corner freqs: $\frac{0.25}{RC}^-$, $\frac{1}{RC}^+$ LF Asymptote: $H(j\omega) = 1$



Magnitude Response:

Gradient Changes: -20 dB/dec at $\omega = \frac{0.25}{RC}$ and $+20$ at $\omega = \frac{1}{RC}$

Line equations: $H(j\omega) =$ (a) 1, (b) $\frac{1}{4j\omega RC}$, (c) $\frac{j\omega RC}{4j\omega RC} = 0.25$

Phase Response:

LF asymptote: $\phi = \angle 1 = 0$

Gradient changes of $\pm \frac{\pi}{4}$ /decade at: $\omega = \frac{0.025}{RC}^-$, $\frac{0.1}{RC}^+$, $\frac{2.5}{RC}^+$, $\frac{10}{RC}^-$.

At $\omega = \frac{0.1}{RC}$, $\phi = 0 - \frac{\pi}{4} \log_{10} \frac{0.1}{0.025} = -\frac{\pi}{4} \times 0.602 = -0.15\pi$

Summary

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- **Summary**

- **Frequency response:** magnitude and phase of $\frac{Y}{X}$ as a function of ω
 - Only applies to sine waves

Summary

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

- **Frequency response:** magnitude and phase of $\frac{Y}{X}$ as a function of ω
 - Only applies to sine waves
 - Use **log axes** for frequency and gain but **linear** for phase
 - ▷ Decibels = $20 \log_{10} \frac{V_2}{V_1} = 10 \log_{10} \frac{P_2}{P_1}$

Summary

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

- **Frequency response:** magnitude and phase of $\frac{Y}{X}$ as a function of ω
 - Only applies to sine waves
 - Use **log axes** for frequency and gain but **linear** for phase
 - ▷ Decibels = $20 \log_{10} \frac{V_2}{V_1} = 10 \log_{10} \frac{P_2}{P_1}$
- Linear factor $(aj\omega + b)$ gives corner frequency at $\omega = \left| \frac{b}{a} \right|$.
 - Magnitude plot gradient changes by ± 20 dB/decade @ $\omega = \left| \frac{b}{a} \right|$.

Summary

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

- **Frequency response:** magnitude and phase of $\frac{Y}{X}$ as a function of ω
 - Only applies to sine waves
 - Use **log axes** for frequency and gain but **linear** for phase
 - ▷ Decibels = $20 \log_{10} \frac{V_2}{V_1} = 10 \log_{10} \frac{P_2}{P_1}$
- Linear factor $(aj\omega + b)$ gives corner frequency at $\omega = \left| \frac{b}{a} \right|$.
 - Magnitude plot gradient changes by ± 20 dB/decade @ $\omega = \left| \frac{b}{a} \right|$.
 - Phase gradient changes in two places by:
 - ▷ $\pm \frac{\pi}{4}$ rad/decade @ $\omega = 0.1 \times \left| \frac{b}{a} \right|$
 - ▷ $\mp \frac{\pi}{4}$ rad/decade @ $\omega = 10 \times \left| \frac{b}{a} \right|$

Summary

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

- **Frequency response:** magnitude and phase of $\frac{Y}{X}$ as a function of ω
 - Only applies to sine waves
 - Use **log axes** for frequency and gain but **linear** for phase
 - ▷ Decibels = $20 \log_{10} \frac{V_2}{V_1} = 10 \log_{10} \frac{P_2}{P_1}$
- **Linear factor** $(aj\omega + b)$ gives corner frequency at $\omega = \left| \frac{b}{a} \right|$.
 - Magnitude plot gradient changes by ± 20 dB/decade @ $\omega = \left| \frac{b}{a} \right|$.
 - Phase gradient changes in two places by:
 - ▷ $\pm \frac{\pi}{4}$ rad/decade @ $\omega = 0.1 \times \left| \frac{b}{a} \right|$
 - ▷ $\mp \frac{\pi}{4}$ rad/decade @ $\omega = 10 \times \left| \frac{b}{a} \right|$
- **LF/HF asymptotes:** keep only the terms with the lowest/highest power of $j\omega$ in numerator and denominator polynomials

Summary

11: Frequency Responses

- Frequency Response
- Sine Wave Response
- Logarithmic axes
- Logs of Powers +
- Straight Line
- Approximations
- Plot Magnitude Response
- Low and High Frequency Asymptotes
- Phase Approximation +
- Plot Phase Response +
- RCR Circuit
- Summary

- **Frequency response:** magnitude and phase of $\frac{Y}{X}$ as a function of ω
 - Only applies to sine waves
 - Use **log axes** for frequency and gain but **linear** for phase
 - ▷ Decibels = $20 \log_{10} \frac{V_2}{V_1} = 10 \log_{10} \frac{P_2}{P_1}$
- **Linear factor** $(aj\omega + b)$ gives corner frequency at $\omega = \left| \frac{b}{a} \right|$.
 - Magnitude plot gradient changes by ± 20 dB/decade @ $\omega = \left| \frac{b}{a} \right|$.
 - Phase gradient changes in two places by:
 - ▷ $\pm \frac{\pi}{4}$ rad/decade @ $\omega = 0.1 \times \left| \frac{b}{a} \right|$
 - ▷ $\mp \frac{\pi}{4}$ rad/decade @ $\omega = 10 \times \left| \frac{b}{a} \right|$
- **LF/HF asymptotes:** keep only the terms with the lowest/highest power of $j\omega$ in numerator and denominator polynomials

For further details see Hayt Ch 16 or Irwin Ch 12.