

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

# 12: Resonance

# Quadratic Factors



12: Resonance

● Quadratic Factors +

- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +

- Low Pass Filter
- Resonance Peak for LP filter
- Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

# Quadratic Factors



12: Resonance

● Quadratic Factors +

- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance

+

- Low Pass Filter
- Resonance Peak for LP filter
- Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

**Case 1:** If  $b^2 \geq 4ac$  then we can factorize it:

$$F(j\omega) = a(j\omega - p_1)(j\omega - p_2)$$

# Quadratic Factors



12: Resonance

● Quadratic Factors +

- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance

Resonance +

- Low Pass Filter
- Resonance Peak for LP filter
- Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

**Case 1:** If  $b^2 \geq 4ac$  then we can factorize it:

$$F(j\omega) = a(j\omega - p_1)(j\omega - p_2)$$

$$\text{where } p_i = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}.$$

# Quadratic Factors



## 12: Resonance


- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Case 1: If  $b^2 \geq 4ac$  then we can factorize it:

$$F(j\omega) = a(j\omega - p_1)(j\omega - p_2)$$
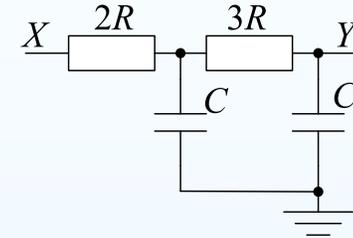
$$\text{where } p_i = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}.$$



$$\frac{Y}{X}(j\omega) = \frac{1}{6R^2C^2(j\omega)^2 + 7RCj\omega + 1}$$

# Quadratic Factors



12: Resonance

● Quadratic Factors +

- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +

- Low Pass Filter
- Resonance Peak for LP filter


- Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Case 1: If  $b^2 \geq 4ac$  then we can factorize it:

$$F(j\omega) = a(j\omega - p_1)(j\omega - p_2)$$
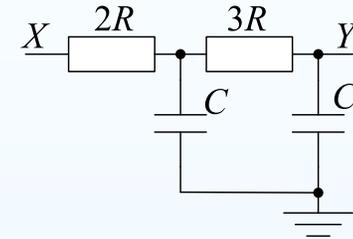
$$\text{where } p_i = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}.$$



$$\begin{aligned} \frac{Y}{X}(j\omega) &= \frac{1}{6R^2C^2(j\omega)^2 + 7RCj\omega + 1} \\ &= \frac{1}{(6j\omega RC + 1)(j\omega RC + 1)} \end{aligned}$$

# Quadratic Factors



12: Resonance

● Quadratic Factors +

- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +

- Low Pass Filter
- Resonance Peak for LP filter


● Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Case 1: If  $b^2 \geq 4ac$  then we can factorize it:

$$F(j\omega) = a(j\omega - p_1)(j\omega - p_2)$$
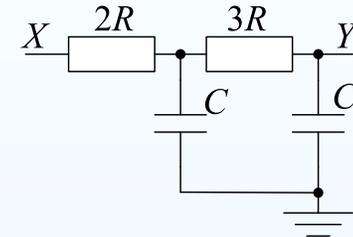
$$\text{where } p_i = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}.$$



$$\begin{aligned} \frac{Y}{X}(j\omega) &= \frac{1}{6R^2C^2(j\omega)^2 + 7RCj\omega + 1} \\ &= \frac{1}{(6j\omega RC + 1)(j\omega RC + 1)} \end{aligned}$$

$$\omega_c = \frac{0.17}{RC}, \frac{1}{RC}$$

# Quadratic Factors



## 12: Resonance



- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Case 1: If  $b^2 \geq 4ac$  then we can factorize it:

$$F(j\omega) = a(j\omega - p_1)(j\omega - p_2)$$
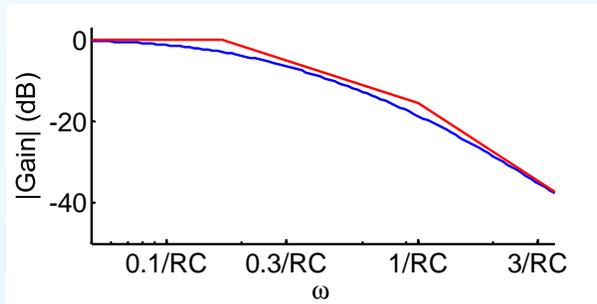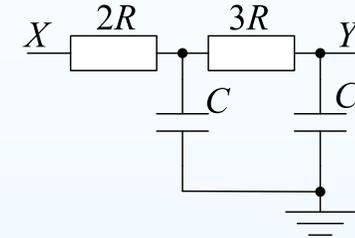
$$\text{where } p_i = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}.$$



$$\begin{aligned} \frac{Y}{X}(j\omega) &= \frac{1}{6R^2C^2(j\omega)^2 + 7RCj\omega + 1} \\ &= \frac{1}{(6j\omega RC + 1)(j\omega RC + 1)} \end{aligned}$$

$$\omega_c = \frac{0.17}{RC}, \frac{1}{RC}$$

# Quadratic Factors



## 12: Resonance



- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Case 1: If  $b^2 \geq 4ac$  then we can factorize it:

$$F(j\omega) = a(j\omega - p_1)(j\omega - p_2)$$
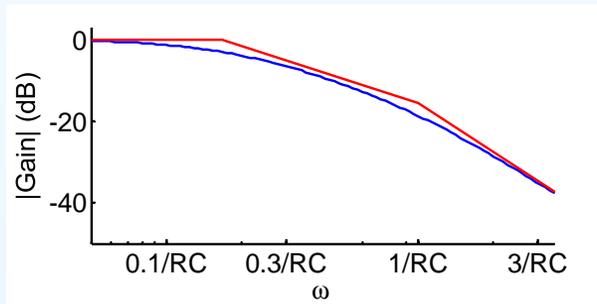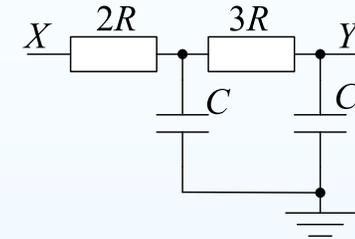
$$\text{where } p_i = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$



$$\begin{aligned} \frac{Y}{X}(j\omega) &= \frac{1}{6R^2C^2(j\omega)^2 + 7RCj\omega + 1} \\ &= \frac{1}{(6j\omega RC + 1)(j\omega RC + 1)} \end{aligned}$$

$$\omega_c = \frac{0.17}{RC}, \quad \frac{1}{RC} = |p_1|, |p_2|$$

# Quadratic Factors



12: Resonance



- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Case 1: If  $b^2 \geq 4ac$  then we can factorize it:

$$F(j\omega) = a(j\omega - p_1)(j\omega - p_2)$$
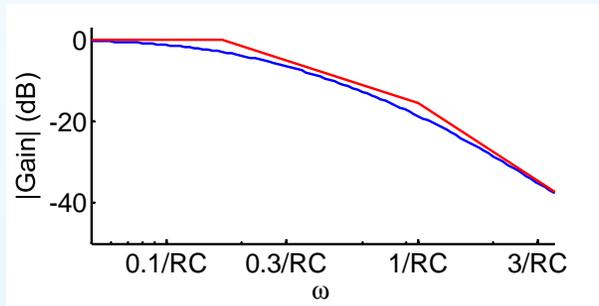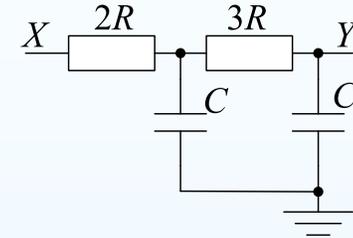
$$\text{where } p_i = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$



$$\begin{aligned} \frac{Y}{X}(j\omega) &= \frac{1}{6R^2C^2(j\omega)^2 + 7RCj\omega + 1} \\ &= \frac{1}{(6j\omega RC + 1)(j\omega RC + 1)} \end{aligned}$$

$$\omega_c = \frac{0.17}{RC}, \quad \frac{1}{RC} = |p_1|, |p_2|$$

Case 2: If  $b^2 < 4ac$ , we cannot factorize with real coefficients so we leave it as a quadratic.

# Quadratic Factors



12: Resonance



- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Case 1: If  $b^2 \geq 4ac$  then we can factorize it:

$$F(j\omega) = a(j\omega - p_1)(j\omega - p_2)$$
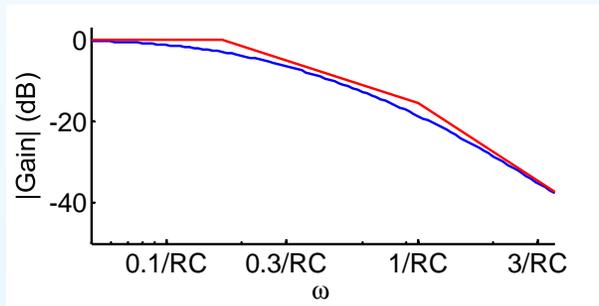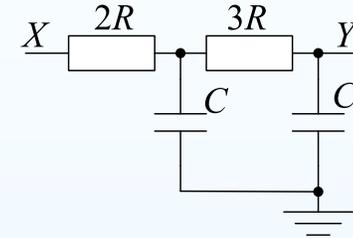
$$\text{where } p_i = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}.$$



$$\begin{aligned} \frac{Y}{X}(j\omega) &= \frac{1}{6R^2C^2(j\omega)^2 + 7RCj\omega + 1} \\ &= \frac{1}{(6j\omega RC + 1)(j\omega RC + 1)} \end{aligned}$$

$$\omega_c = \frac{0.17}{RC}, \quad \frac{1}{RC} = |p_1|, |p_2|$$

Case 2: If  $b^2 < 4ac$ , we cannot factorize with real coefficients so we leave it as a quadratic. Sometimes called a *quadratic resonance*.

# Quadratic Factors



12: Resonance



- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Case 1: If  $b^2 \geq 4ac$  then we can factorize it:

$$F(j\omega) = a(j\omega - p_1)(j\omega - p_2)$$
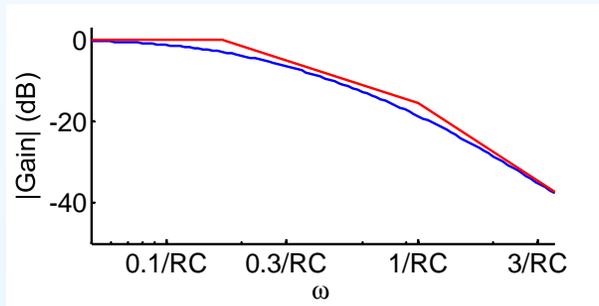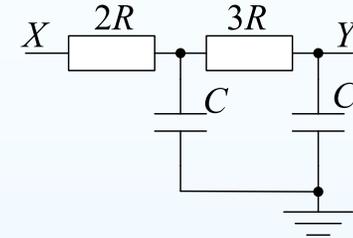
$$\text{where } p_i = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$



$$\begin{aligned} \frac{Y}{X}(j\omega) &= \frac{1}{6R^2C^2(j\omega)^2 + 7RCj\omega + 1} \\ &= \frac{1}{(6j\omega RC + 1)(j\omega RC + 1)} \end{aligned}$$

$$\omega_c = \frac{0.17}{RC}, \quad \frac{1}{RC} = |p_1|, |p_2|$$

Case 2: If  $b^2 < 4ac$ , we cannot factorize with real coefficients so we leave it as a quadratic. Sometimes called a *quadratic resonance*.

Any polynomial with real coefficients can be factored into linear and quadratic factors

# Quadratic Factors



12: Resonance



- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

A quadratic factor in a transfer function is:  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Case 1: If  $b^2 \geq 4ac$  then we can factorize it:

$$F(j\omega) = a(j\omega - p_1)(j\omega - p_2)$$
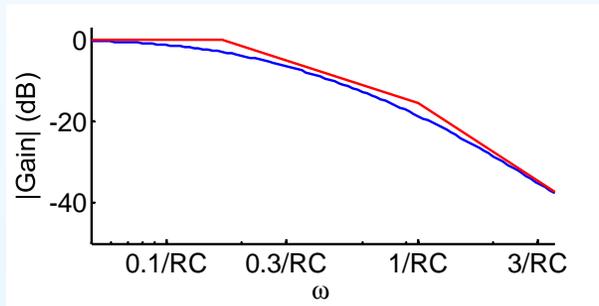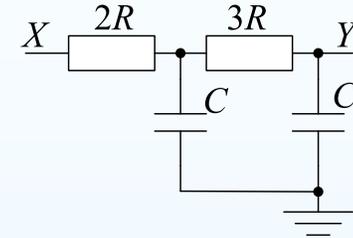
$$\text{where } p_i = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$



$$\begin{aligned} \frac{Y}{X}(j\omega) &= \frac{1}{6R^2C^2(j\omega)^2 + 7RCj\omega + 1} \\ &= \frac{1}{(6j\omega RC + 1)(j\omega RC + 1)} \end{aligned}$$

$$\omega_c = \frac{0.17}{RC}, \quad \frac{1}{RC} = |p_1|, |p_2|$$

Case 2: If  $b^2 < 4ac$ , we cannot factorize with real coefficients so we leave it as a quadratic. Sometimes called a *quadratic resonance*.

Any polynomial with real coefficients can be factored into linear and quadratic factors  $\Rightarrow$  a quadratic factor is as complicated as it gets.

# Damping Factor and Q

## 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

# Damping Factor and Q

## 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:

# Damping Factor and Q

## 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{LF}(j\omega) = c$

# Damping Factor and Q

## 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{LF}(j\omega) = c$ ,  $F_{HF}(j\omega) = a(j\omega)^2$

## Damping Factor and Q

### 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{LF}(j\omega) = c$ ,  $F_{HF}(j\omega) = a(j\omega)^2$

The asymptote magnitudes cross at the *corner frequency*:

# Damping Factor and Q

## 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{LF}(j\omega) = c$ ,  $F_{HF}(j\omega) = a(j\omega)^2$

The asymptote magnitudes cross at the *corner frequency*:

$$\left| a(j\omega_c)^2 \right| = |c| \Rightarrow \omega_c = \sqrt{\frac{c}{a}}.$$

## Damping Factor and Q

### 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{\text{LF}}(j\omega) = c$ ,  $F_{\text{HF}}(j\omega) = a(j\omega)^2$

The asymptote magnitudes cross at the *corner frequency*:

$$\left| a(j\omega_c)^2 \right| = |c| \Rightarrow \omega_c = \sqrt{\frac{c}{a}}.$$

We define the *damping factor*, “zeta”, to be  $\zeta = \frac{b}{2a\omega_c}$

## Damping Factor and Q

### 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{LF}(j\omega) = c$ ,  $F_{HF}(j\omega) = a(j\omega)^2$

The asymptote magnitudes cross at the *corner frequency*:

$$\left| a(j\omega_c)^2 \right| = |c| \Rightarrow \omega_c = \sqrt{\frac{c}{a}}.$$

We define the *damping factor*, “zeta”, to be  $\zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$

## Damping Factor and Q

### 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{\text{LF}}(j\omega) = c$ ,  $F_{\text{HF}}(j\omega) = a(j\omega)^2$

The asymptote magnitudes cross at the *corner frequency*:

$$\left| a(j\omega_c)^2 \right| = |c| \Rightarrow \omega_c = \sqrt{\frac{c}{a}}.$$

We define the *damping factor*, “zeta”, to be  $\zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$

$$\Rightarrow F(j\omega) = c \left( \left( j \frac{\omega}{\omega_c} \right)^2 + 2\zeta \left( j \frac{\omega}{\omega_c} \right) + 1 \right)$$

## Damping Factor and Q

### 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{LF}(j\omega) = c$ ,  $F_{HF}(j\omega) = a(j\omega)^2$

The asymptote magnitudes cross at the *corner frequency*:

$$\left| a(j\omega_c)^2 \right| = |c| \Rightarrow \omega_c = \sqrt{\frac{c}{a}}.$$

We define the *damping factor*, “zeta”, to be  $\zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$

$$\Rightarrow F(j\omega) = c \left( \left( j \frac{\omega}{\omega_c} \right)^2 + 2\zeta \left( j \frac{\omega}{\omega_c} \right) + 1 \right)$$

Properties to notice in this expression:

(a)  $c$  is just an overall scale factor.

## Damping Factor and Q

### 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{LF}(j\omega) = c$ ,  $F_{HF}(j\omega) = a(j\omega)^2$

The asymptote magnitudes cross at the *corner frequency*:

$$\left| a(j\omega_c)^2 \right| = |c| \Rightarrow \omega_c = \sqrt{\frac{c}{a}}.$$

We define the *damping factor*, “zeta”, to be  $\zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$

$$\Rightarrow F(j\omega) = c \left( \left( j \frac{\omega}{\omega_c} \right)^2 + 2\zeta \left( j \frac{\omega}{\omega_c} \right) + 1 \right)$$

Properties to notice in this expression:

- $c$  is just an overall scale factor.
- $\omega_c$  just scales the frequency axis since  $F(j\omega)$  is a function of  $\frac{\omega}{\omega_c}$ .

## Damping Factor and Q

### 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{LF}(j\omega) = c$ ,  $F_{HF}(j\omega) = a(j\omega)^2$

The asymptote magnitudes cross at the *corner frequency*:

$$\left| a(j\omega_c)^2 \right| = |c| \Rightarrow \omega_c = \sqrt{\frac{c}{a}}.$$

We define the *damping factor*, “zeta”, to be  $\zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$

$$\Rightarrow F(j\omega) = c \left( \left( j \frac{\omega}{\omega_c} \right)^2 + 2\zeta \left( j \frac{\omega}{\omega_c} \right) + 1 \right)$$

Properties to notice in this expression:

- $c$  is just an overall scale factor.
- $\omega_c$  just scales the frequency axis since  $F(j\omega)$  is a function of  $\frac{\omega}{\omega_c}$ .
- The shape of the  $F(j\omega)$  graphs is determined entirely by  $\zeta$ .

# Damping Factor and Q

## 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{LF}(j\omega) = c$ ,  $F_{HF}(j\omega) = a(j\omega)^2$

The asymptote magnitudes cross at the *corner frequency*:

$$\left| a(j\omega_c)^2 \right| = |c| \Rightarrow \omega_c = \sqrt{\frac{c}{a}}.$$

We define the *damping factor*, “zeta”, to be  $\zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$

$$\Rightarrow F(j\omega) = c \left( \left( j \frac{\omega}{\omega_c} \right)^2 + 2\zeta \left( j \frac{\omega}{\omega_c} \right) + 1 \right)$$

Properties to notice in this expression:

- $c$  is just an overall scale factor.
- $\omega_c$  just scales the frequency axis since  $F(j\omega)$  is a function of  $\frac{\omega}{\omega_c}$ .
- The shape of the  $F(j\omega)$  graphs is determined entirely by  $\zeta$ .
- The quadratic cannot be factorized  $\Leftrightarrow b^2 < 4ac \Leftrightarrow |\zeta| < 1$ .

# Damping Factor and Q

## 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{LF}(j\omega) = c$ ,  $F_{HF}(j\omega) = a(j\omega)^2$

The asymptote magnitudes cross at the *corner frequency*:

$$\left| a(j\omega_c)^2 \right| = |c| \Rightarrow \omega_c = \sqrt{\frac{c}{a}}.$$

We define the *damping factor*, “zeta”, to be  $\zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$

$$\Rightarrow F(j\omega) = c \left( \left( j \frac{\omega}{\omega_c} \right)^2 + 2\zeta \left( j \frac{\omega}{\omega_c} \right) + 1 \right)$$

Properties to notice in this expression:

- $c$  is just an overall scale factor.
- $\omega_c$  just scales the frequency axis since  $F(j\omega)$  is a function of  $\frac{\omega}{\omega_c}$ .
- The shape of the  $F(j\omega)$  graphs is determined entirely by  $\zeta$ .
- The quadratic cannot be factorized  $\Leftrightarrow b^2 < 4ac \Leftrightarrow |\zeta| < 1$ .
- At  $\omega = \omega_c$ , asymptote gain =  $c$  but  $F(j\omega) = c \times 2j\zeta$ .

# Damping Factor and Q

## 12: Resonance

- Quadratic Factors +
- **Damping Factor and Q**
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Suppose  $b^2 < 4ac$  in  $F(j\omega) = a(j\omega)^2 + b(j\omega) + c$ .

Low/High freq asymptotes:  $F_{LF}(j\omega) = c$ ,  $F_{HF}(j\omega) = a(j\omega)^2$

The asymptote magnitudes cross at the *corner frequency*:

$$\left| a(j\omega_c)^2 \right| = |c| \Rightarrow \omega_c = \sqrt{\frac{c}{a}}.$$

We define the *damping factor*, “zeta”, to be  $\zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$

$$\Rightarrow F(j\omega) = c \left( \left( j \frac{\omega}{\omega_c} \right)^2 + 2\zeta \left( j \frac{\omega}{\omega_c} \right) + 1 \right)$$

Properties to notice in this expression:

- $c$  is just an overall scale factor.
- $\omega_c$  just scales the frequency axis since  $F(j\omega)$  is a function of  $\frac{\omega}{\omega_c}$ .
- The shape of the  $F(j\omega)$  graphs is determined entirely by  $\zeta$ .
- The quadratic cannot be factorized  $\Leftrightarrow b^2 < 4ac \Leftrightarrow |\zeta| < 1$ .
- At  $\omega = \omega_c$ , asymptote gain =  $c$  but  $F(j\omega) = c \times 2j\zeta$ .


Alternatively, we sometimes use the *quality factor*,  $Q \approx \frac{1}{2\zeta} = \frac{a\omega_c}{b}$ .

# Parallel RLC
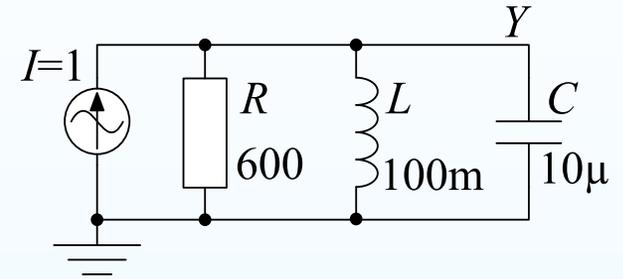
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- **Parallel RLC**
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{j\omega L}{LC(j\omega)^2 + \frac{L}{R}j\omega + 1}$$






# Parallel RLC
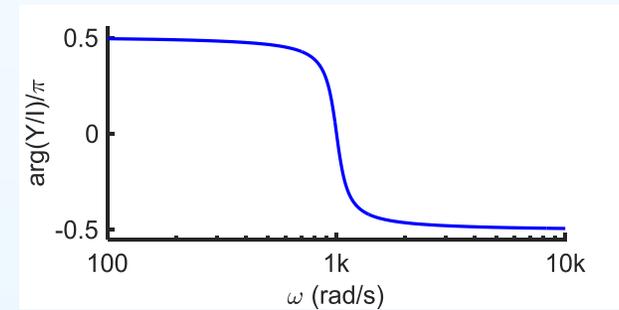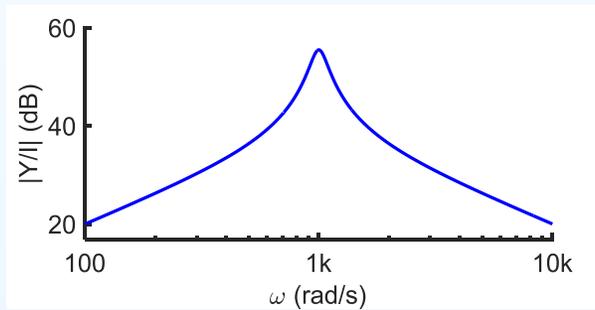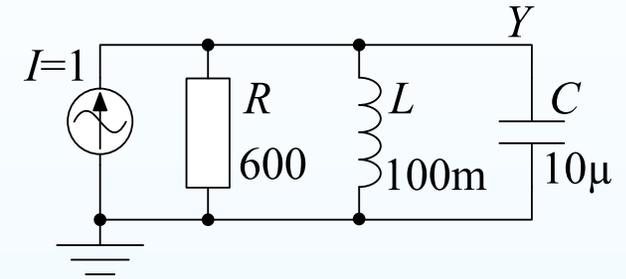
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- **Parallel RLC**
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{j\omega L}{LC(j\omega)^2 + \frac{L}{R}j\omega + 1}$$
$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = 0.083$$



# Parallel RLC




## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- **Parallel RLC**
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{j\omega L}{LC(j\omega)^2 + \frac{L}{R}j\omega + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = 0.083$$

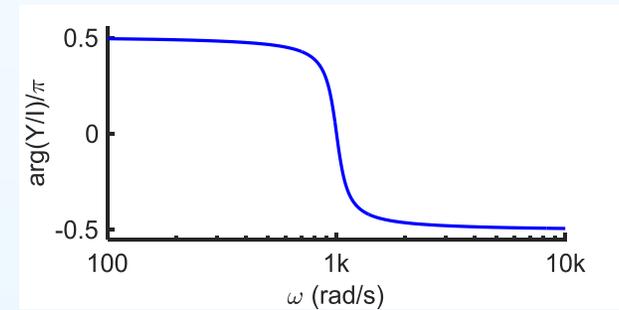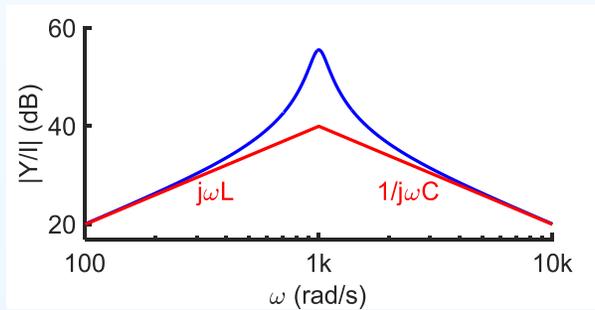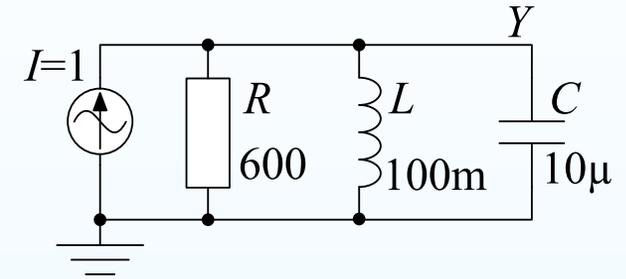Asymptotes:  $j\omega L$  and  $\frac{1}{j\omega C}$ .



# Parallel RLC




## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- **Parallel RLC**
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{j\omega L}{LC(j\omega)^2 + \frac{L}{R}j\omega + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = 0.083$$

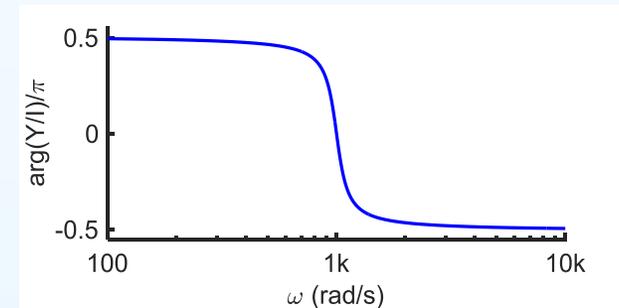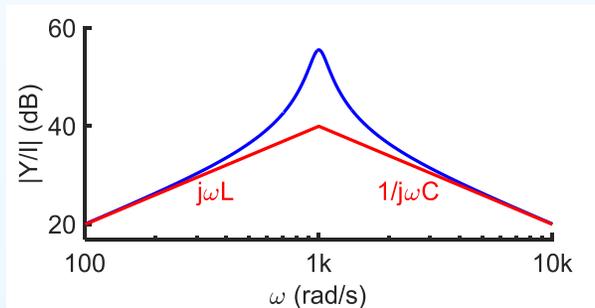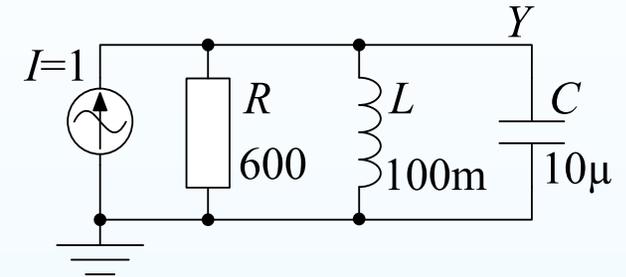Asymptotes:  $j\omega L$  and  $\frac{1}{j\omega C}$ .



Power absorbed by resistor  $\propto Y^2$ . It peaks quite sharply at  $\omega = 1000$ .

# Parallel RLC




## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- **Parallel RLC**
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{j\omega L}{LC(j\omega)^2 + \frac{L}{R}j\omega + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = 0.083$$

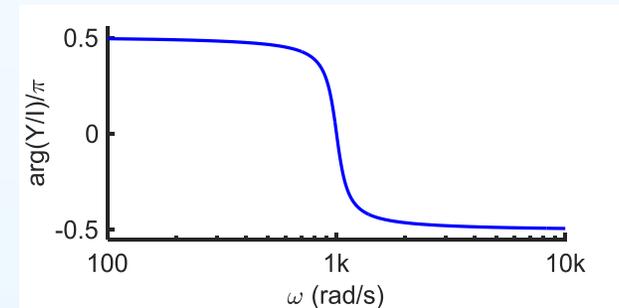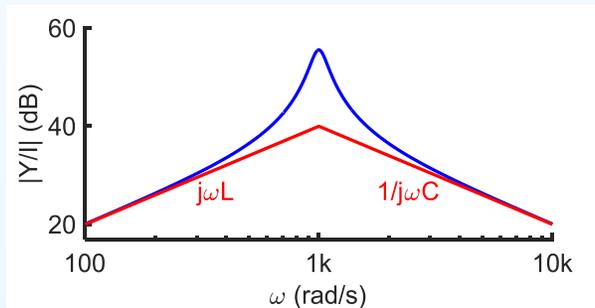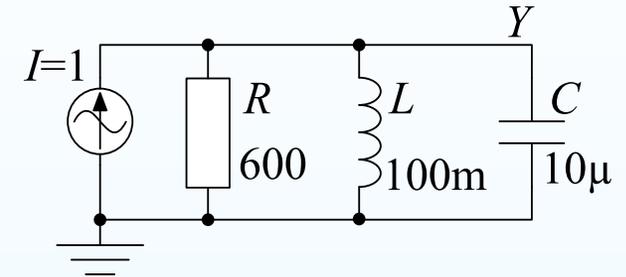Asymptotes:  $j\omega L$  and  $\frac{1}{j\omega C}$ .



Power absorbed by resistor  $\propto Y^2$ . It peaks quite sharply at  $\omega = 1000$ . The resonant frequency,  $\omega_r$ , is when the impedance is purely real: at  $\omega_r = 1000$ ,  $Z_{RLC} = \frac{Y}{I} = R$ .

# Parallel RLC




## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- **Parallel RLC**
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{j\omega L}{LC(j\omega)^2 + \frac{L}{R}j\omega + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = 0.083$$

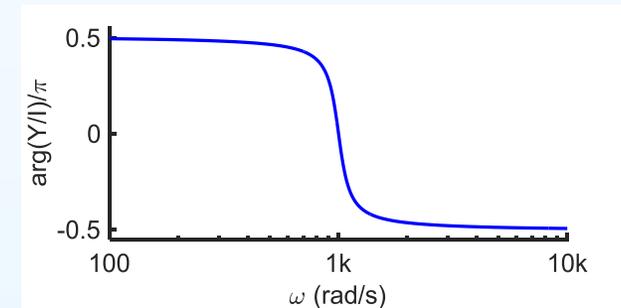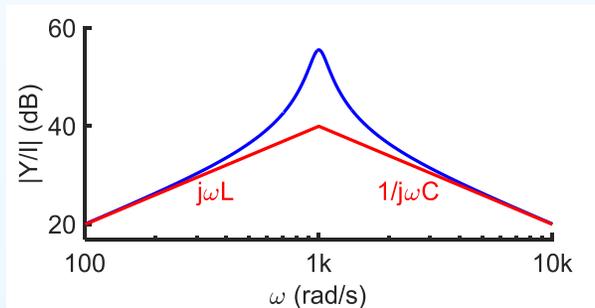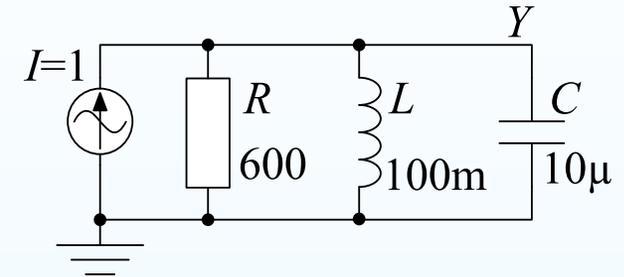Asymptotes:  $j\omega L$  and  $\frac{1}{j\omega C}$ .



Power absorbed by resistor  $\propto Y^2$ . It peaks quite sharply at  $\omega = 1000$ . The **resonant frequency**,  $\omega_r$ , is when the impedance is purely real: at  $\omega_r = 1000$ ,  $Z_{RLC} = \frac{Y}{I} = R$ .

A system with a strong peak in power absorption is a **resonant** system.

# Parallel RLC




## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- **Parallel RLC**
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{j\omega L}{LC(j\omega)^2 + \frac{L}{R}j\omega + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = 0.083$$

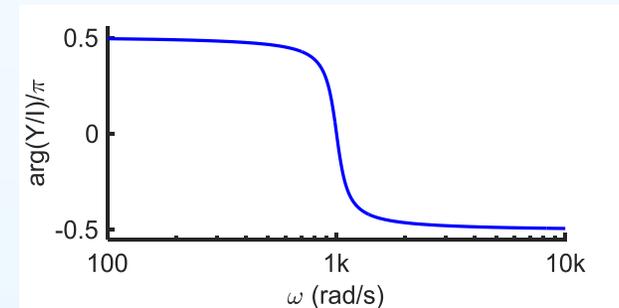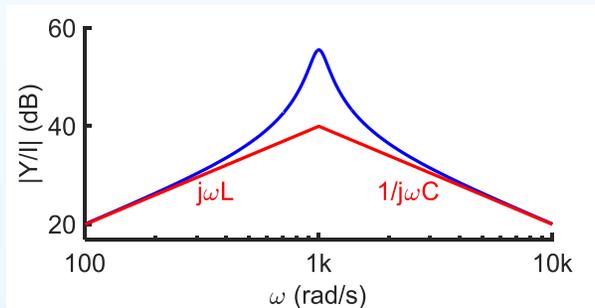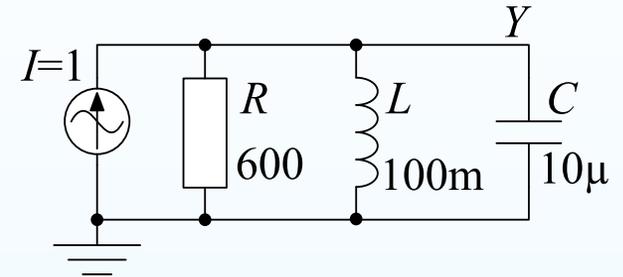Asymptotes:  $j\omega L$  and  $\frac{1}{j\omega C}$ .



Power absorbed by resistor  $\propto Y^2$ . It peaks quite sharply at  $\omega = 1000$ . The **resonant frequency**,  $\omega_r$ , is when the impedance is purely real: at  $\omega_r = 1000$ ,  $Z_{RLC} = \frac{Y}{I} = R$ .


A system with a strong peak in power absorption is a **resonant** system.




# Behaviour at Resonance
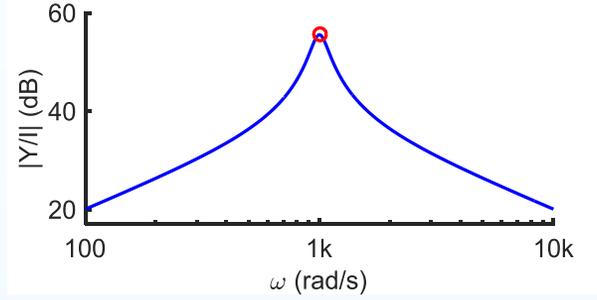
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- **Behaviour at Resonance**
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary




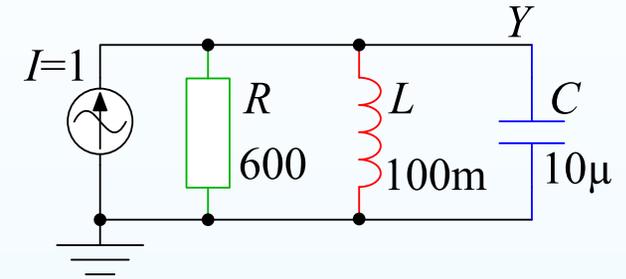
$$\omega = 1000 \Rightarrow Z_L = 100j, Z_C = -100j.$$



# Behaviour at Resonance
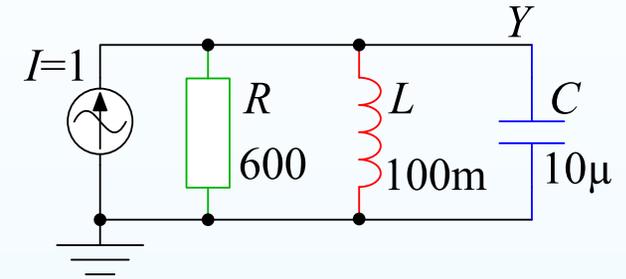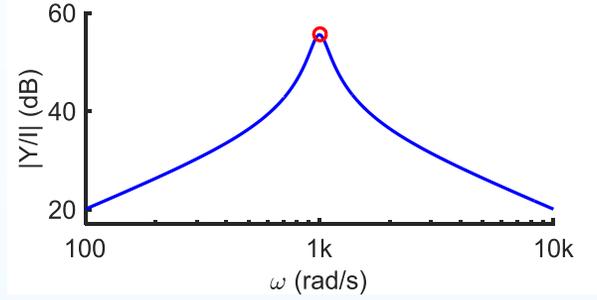
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary





$$\omega = 1000 \Rightarrow Z_L = 100j, Z_C = -100j.$$
$$Z_L = -Z_C \Rightarrow I_L = -I_C$$

# Behaviour at Resonance
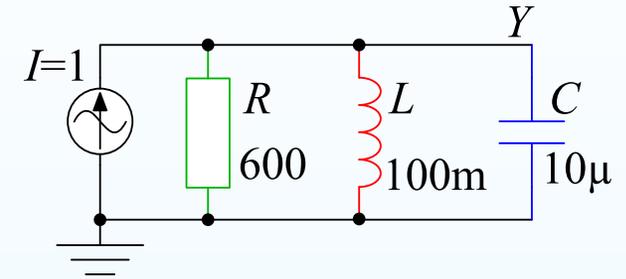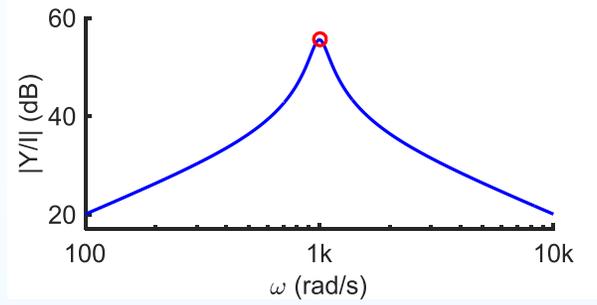
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary



$$\omega = 1000 \Rightarrow Z_L = 100j, Z_C = -100j.$$



$$Z_L = -Z_C \Rightarrow I_L = -I_C$$

$$\Rightarrow I = I_R + I_L + I_C = I_R = 1$$

## Behaviour at Resonance
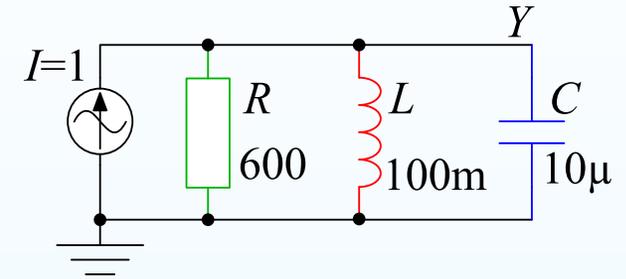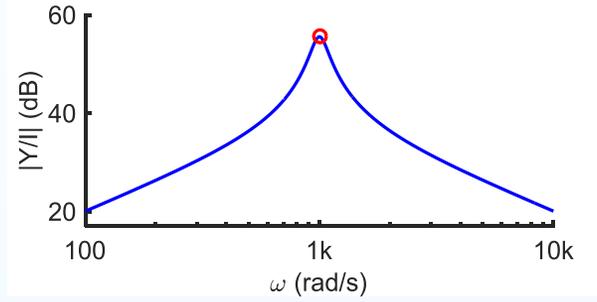
### 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- **Behaviour at Resonance**
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary



$$\omega = 1000 \Rightarrow Z_L = 100j, Z_C = -100j.$$

$$Z_L = -Z_C \Rightarrow I_L = -I_C$$



$$\Rightarrow I = I_R + I_L + I_C = I_R = 1$$

$$\Rightarrow Y = I_R R = 600 \angle 0^\circ = 56 \text{ dBV}$$

# Behaviour at Resonance
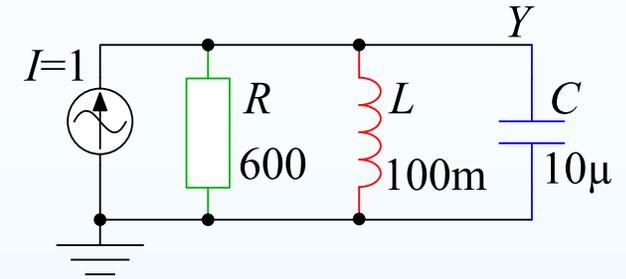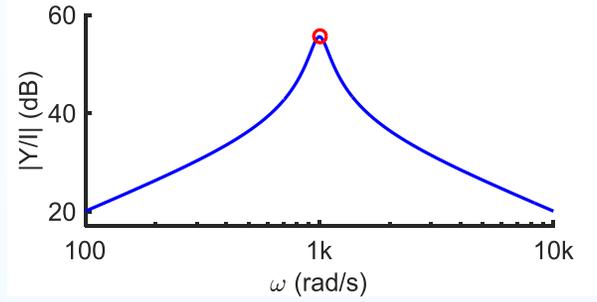
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary



$$\omega = 1000 \Rightarrow Z_L = 100j, Z_C = -100j.$$

$$Z_L = -Z_C \Rightarrow I_L = -I_C$$

$$\Rightarrow I = I_R + I_L + I_C = I_R = 1$$



$$\Rightarrow Y = I_R R = 600 \angle 0^\circ = 56 \text{ dBV}$$

$$\Rightarrow I_L = \frac{Y}{Z_L} = \frac{600}{100j} = -6j$$

# Behaviour at Resonance
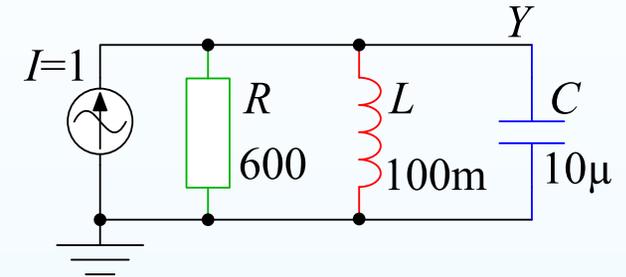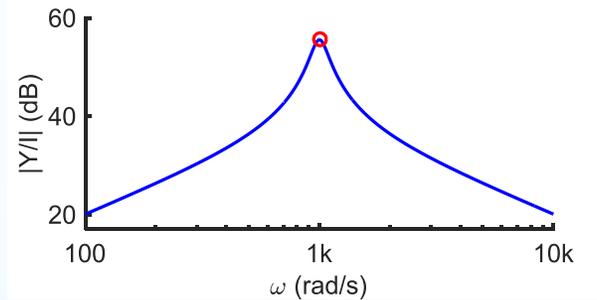
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- **Behaviour at Resonance**
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary




$$\omega = 1000 \Rightarrow Z_L = 100j, Z_C = -100j.$$

$$Z_L = -Z_C \Rightarrow I_L = -I_C$$

$$\Rightarrow I = I_R + I_L + I_C = I_R = 1$$

$$\Rightarrow Y = I_R R = 600 \angle 0^\circ = 56 \text{ dBV}$$


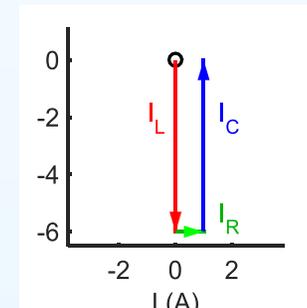
$$\Rightarrow I_L = \frac{Y}{Z_L} = \frac{600}{100j} = -6j$$



# Behaviour at Resonance
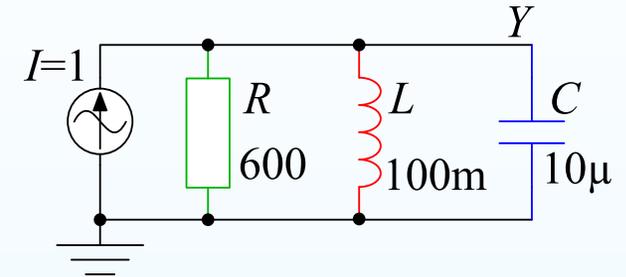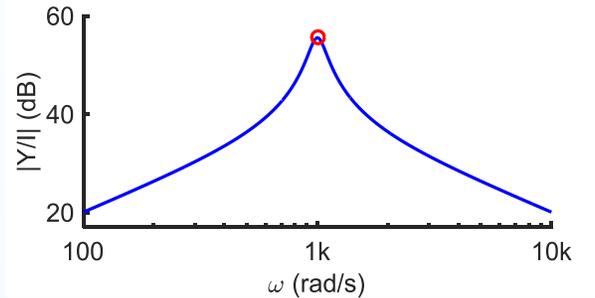
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- **Behaviour at Resonance**
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary





$$\omega = 1000 \Rightarrow Z_L = 100j, Z_C = -100j.$$

$$Z_L = -Z_C \Rightarrow I_L = -I_C$$

$$\Rightarrow I = I_R + I_L + I_C = I_R = 1$$

$$\Rightarrow Y = I_R R = 600 \angle 0^\circ = 56 \text{ dBV}$$

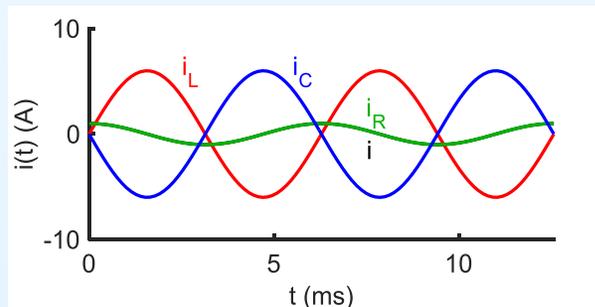
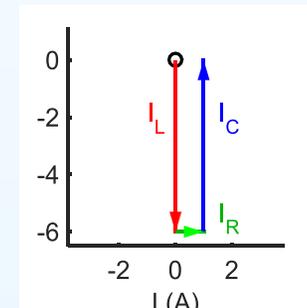
$$\Rightarrow I_L = \frac{Y}{Z_L} = \frac{600}{100j} = -6j$$






# Behaviour at Resonance
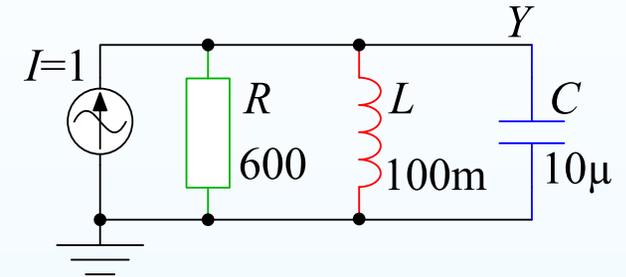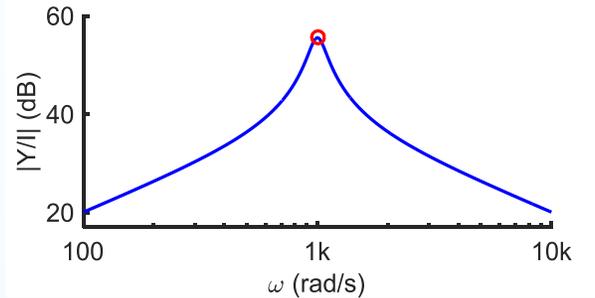
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary



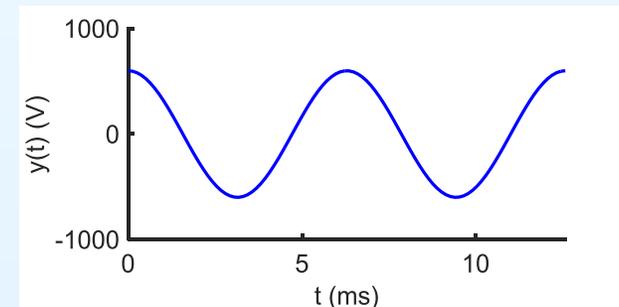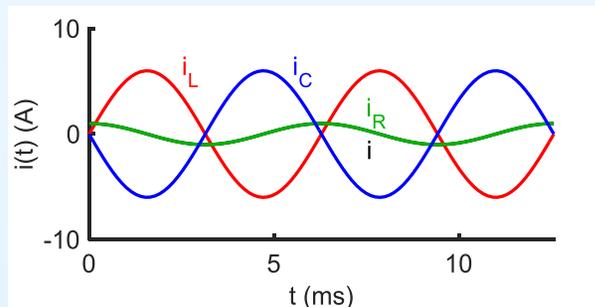
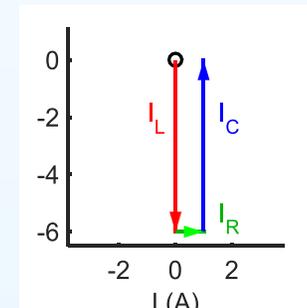
$$\begin{aligned} \omega = 1000 &\Rightarrow Z_L = 100j, Z_C = -100j. \\ Z_L = -Z_C &\Rightarrow I_L = -I_C \\ \Rightarrow I &= I_R + I_L + I_C = I_R = 1 \\ \Rightarrow Y &= I_R R = 600 \angle 0^\circ = 56 \text{ dBV} \\ \Rightarrow I_L &= \frac{Y}{Z_L} = \frac{600}{100j} = -6j \end{aligned}$$






# Behaviour at Resonance
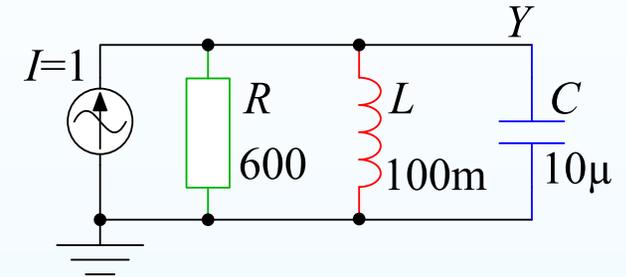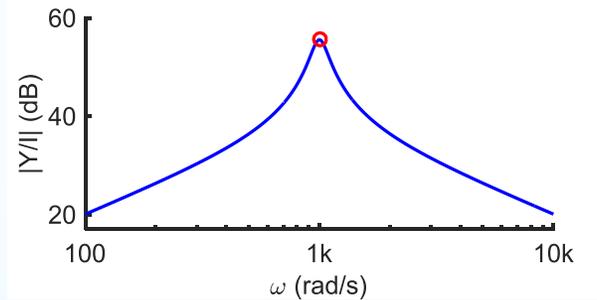
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- **Behaviour at Resonance**
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary


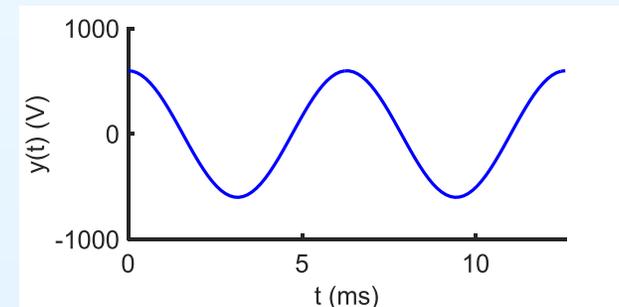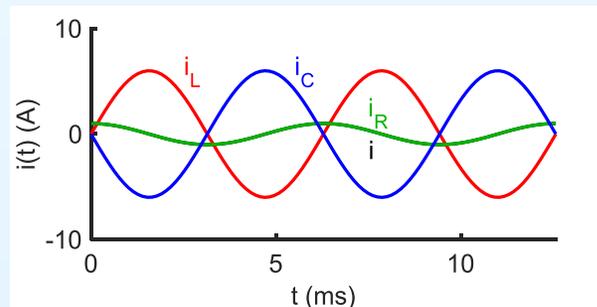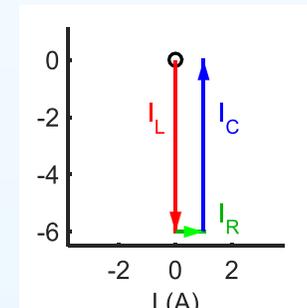
$$\begin{aligned} \omega = 1000 &\Rightarrow Z_L = 100j, Z_C = -100j. \\ Z_L = -Z_C &\Rightarrow I_L = -I_C \\ \Rightarrow I &= I_R + I_L + I_C = I_R = 1 \\ \Rightarrow Y &= I_R R = 600 \angle 0^\circ = 56 \text{ dBV} \\ \Rightarrow I_L &= \frac{Y}{Z_L} = \frac{600}{100j} = -6j \end{aligned}$$




Large currents in  $L$  and  $C$  exactly cancel out  $\Rightarrow I_R = I$  and  $Z = R$  (real)


## Away from resonance
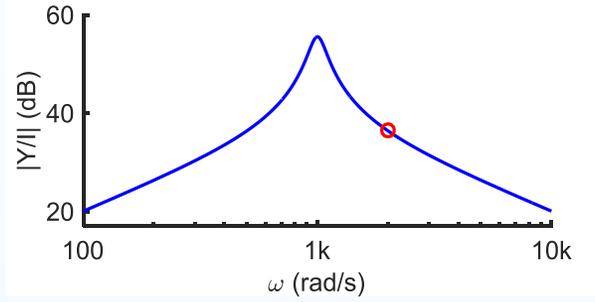
### 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- **Away from resonance**
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary




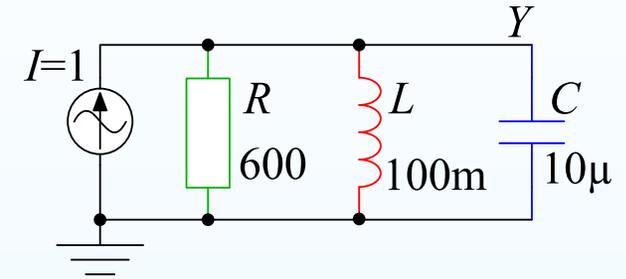
$$\omega = 2000 \Rightarrow Z_L = 200j, Z_C = -50j$$



## Away from resonance
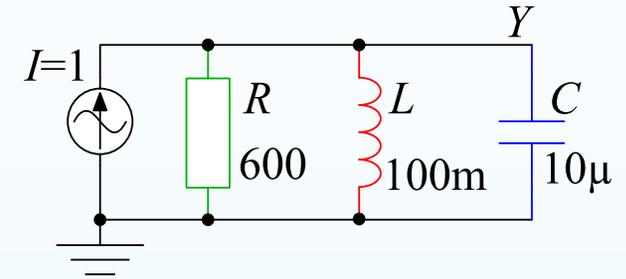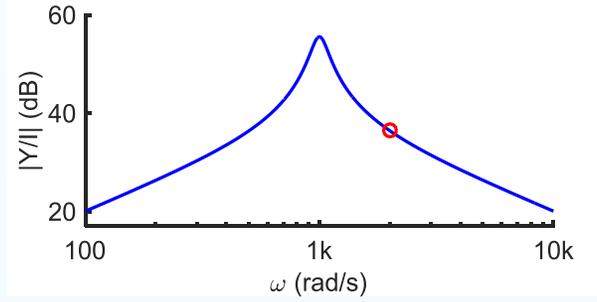
### 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- **Away from resonance**
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary





$$\omega = 2000 \Rightarrow Z_L = 200j, Z_C = -50j$$
$$Z = \left( \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \right)^{-1} = 66 \angle -84^\circ$$

## Away from resonance
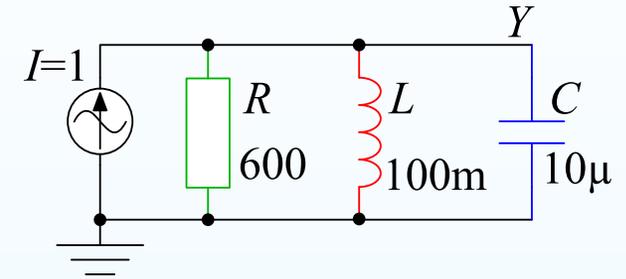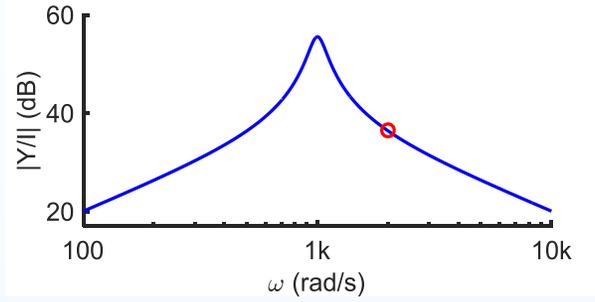
### 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- **Away from resonance**
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary





$$\omega = 2000 \Rightarrow Z_L = 200j, Z_C = -50j$$
$$Z = \left( \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \right)^{-1} = 66 \angle -84^\circ$$
$$Y = I \times Z = 66 \angle -84^\circ = 36 \text{ dBV}$$


# Away from resonance
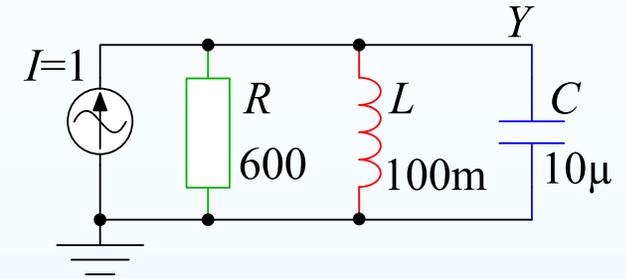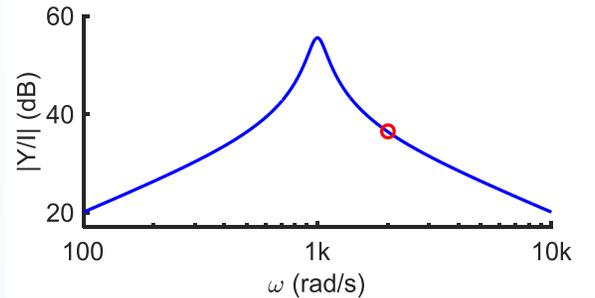
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- **Away from resonance**
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary




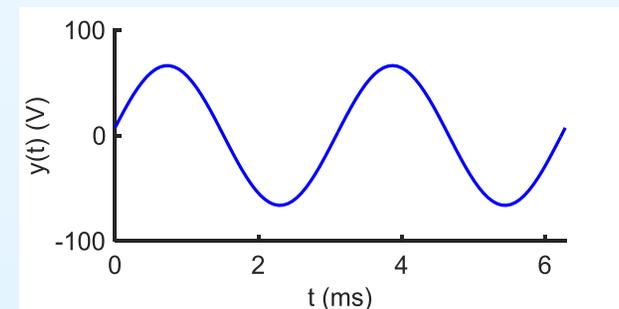
$$\omega = 2000 \Rightarrow Z_L = 200j, Z_C = -50j$$
$$Z = \left( \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \right)^{-1} = 66 \angle -84^\circ$$
$$Y = I \times Z = 66 \angle -84^\circ = 36 \text{ dBV}$$



# Away from resonance
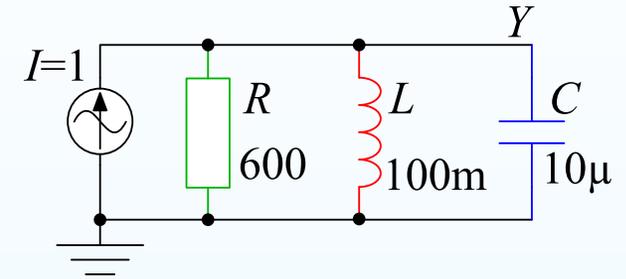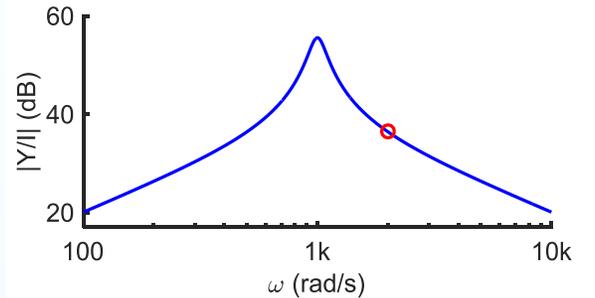
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- **Away from resonance**
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary




$$\omega = 2000 \Rightarrow Z_L = 200j, Z_C = -50j$$

$$Z = \left( \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \right)^{-1} = 66 \angle -84^\circ$$

$$Y = I \times Z = 66 \angle -84^\circ = 36 \text{ dBV}$$


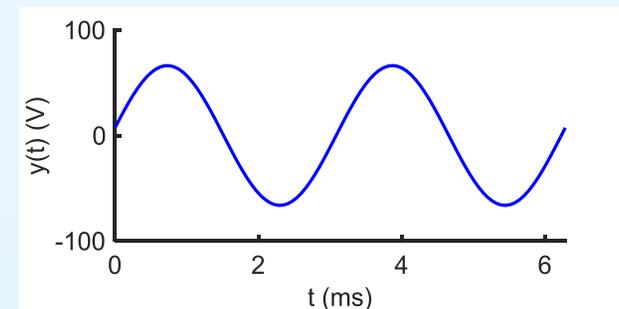
$$I_R = \frac{Y}{R} = 0.11 \angle -84^\circ$$



# Away from resonance
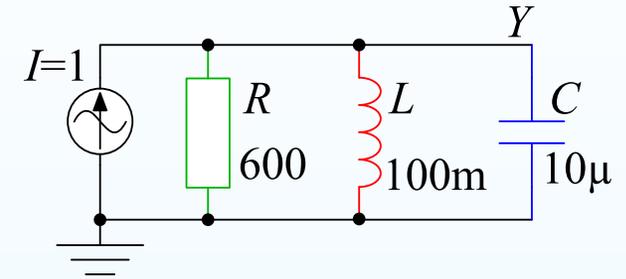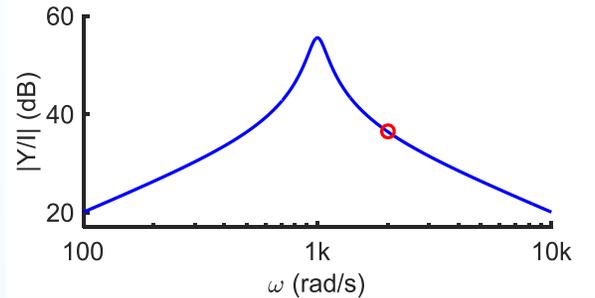
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- **Away from resonance**
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary




$$\omega = 2000 \Rightarrow Z_L = 200j, Z_C = -50j$$

$$Z = \left( \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \right)^{-1} = 66 \angle -84^\circ$$

$$Y = I \times Z = 66 \angle -84^\circ = 36 \text{ dBV}$$

$$I_R = \frac{Y}{R} = 0.11 \angle -84^\circ$$


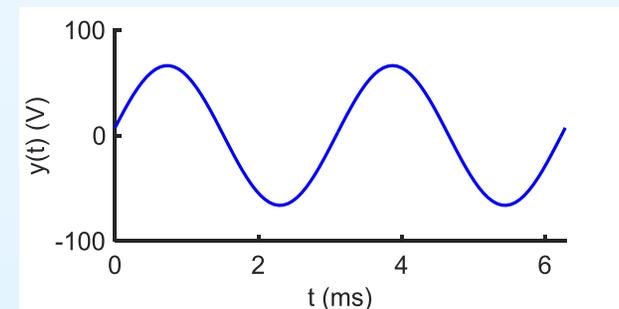
$$I_L = \frac{Y}{Z_L} = 0.33 \angle -174^\circ$$



# Away from resonance
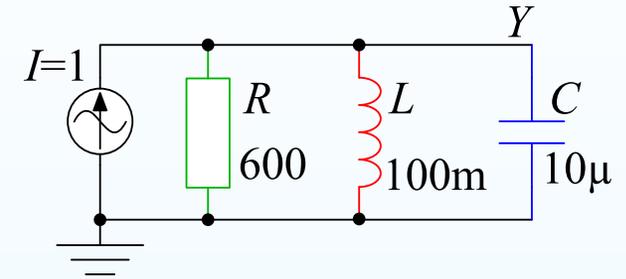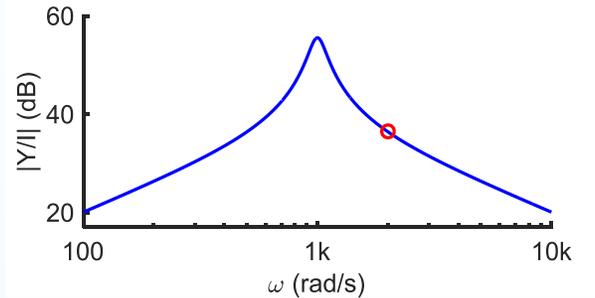
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- **Away from resonance**
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary




$$\omega = 2000 \Rightarrow Z_L = 200j, Z_C = -50j$$

$$Z = \left( \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \right)^{-1} = 66 \angle -84^\circ$$

$$Y = I \times Z = 66 \angle -84^\circ = 36 \text{ dBV}$$

$$I_R = \frac{Y}{R} = 0.11 \angle -84^\circ$$


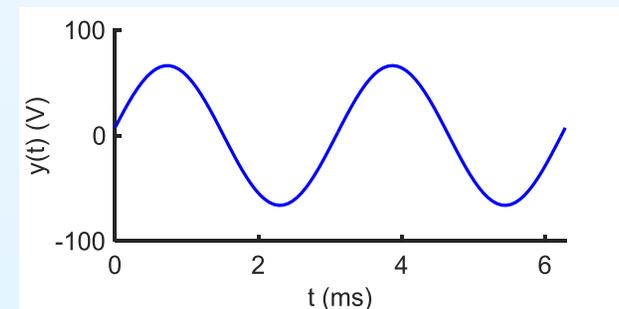
$$I_L = \frac{Y}{Z_L} = 0.33 \angle -174^\circ, I_C = 1.33 \angle +6^\circ$$



# Away from resonance
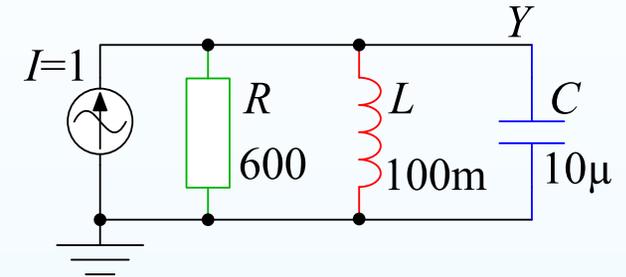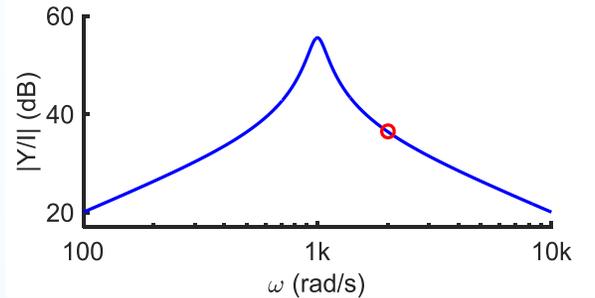
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- **Away from resonance**
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary





$$\omega = 2000 \Rightarrow Z_L = 200j, Z_C = -50j$$

$$Z = \left( \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \right)^{-1} = 66 \angle -84^\circ$$

$$Y = I \times Z = 66 \angle -84^\circ = 36 \text{ dBV}$$

$$I_R = \frac{Y}{R} = 0.11 \angle -84^\circ$$

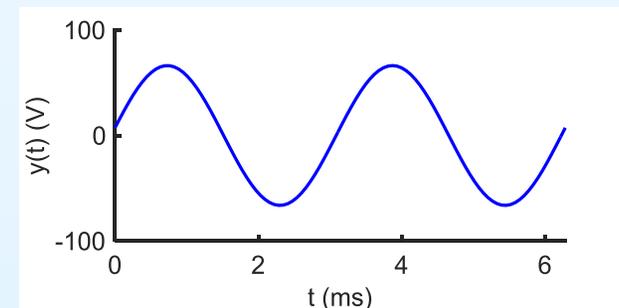
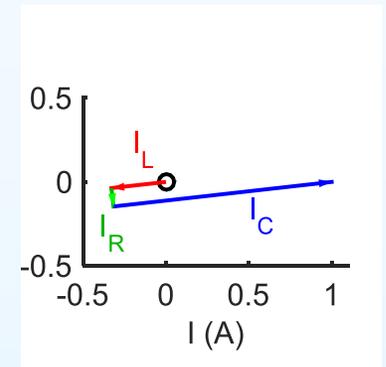
$$I_L = \frac{Y}{Z_L} = 0.33 \angle -174^\circ, I_C = 1.33 \angle +6^\circ$$



# Away from resonance
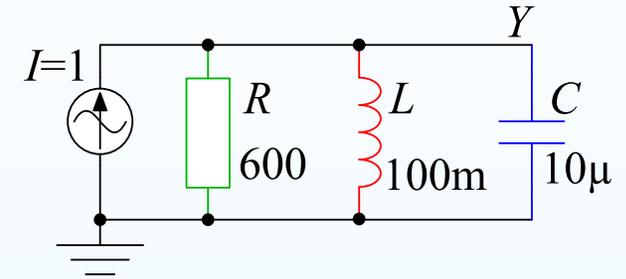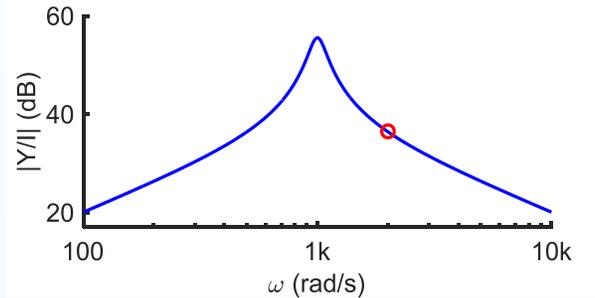
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- **Away from resonance**
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary






$$\omega = 2000 \Rightarrow Z_L = 200j, Z_C = -50j$$

$$Z = \left( \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \right)^{-1} = 66 \angle -84^\circ$$

$$Y = I \times Z = 66 \angle -84^\circ = 36 \text{ dBV}$$

$$I_R = \frac{Y}{R} = 0.11 \angle -84^\circ$$

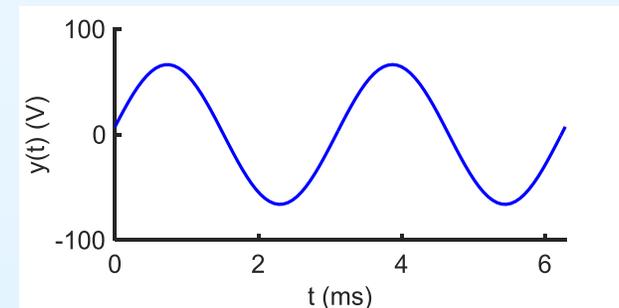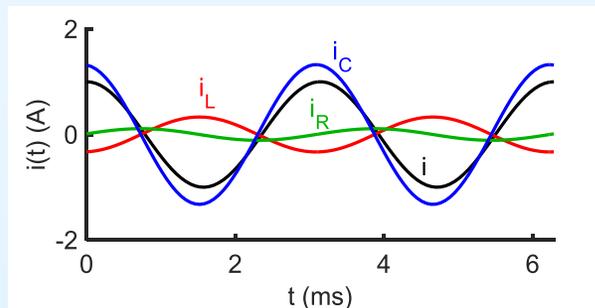
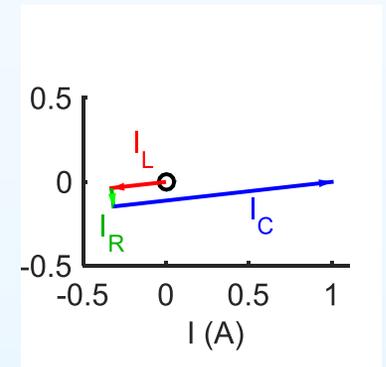
$$I_L = \frac{Y}{Z_L} = 0.33 \angle -174^\circ, I_C = 1.33 \angle +6^\circ$$



# Away from resonance
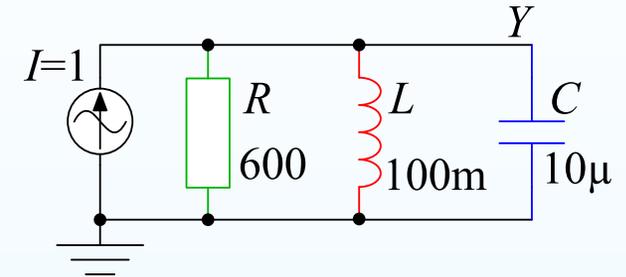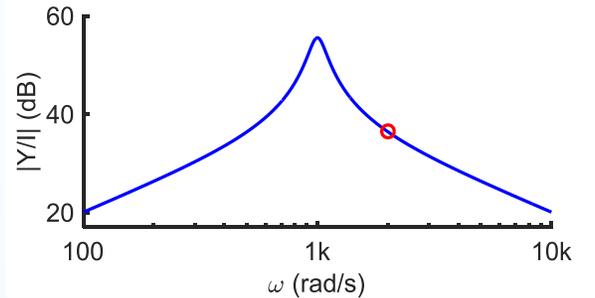
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- **Away from resonance**
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary






$$\omega = 2000 \Rightarrow Z_L = 200j, Z_C = -50j$$

$$Z = \left( \frac{1}{R} + \frac{1}{Z_L} + \frac{1}{Z_C} \right)^{-1} = 66 \angle -84^\circ$$

$$Y = I \times Z = 66 \angle -84^\circ = 36 \text{ dBV}$$

$$I_R = \frac{Y}{R} = 0.11 \angle -84^\circ$$
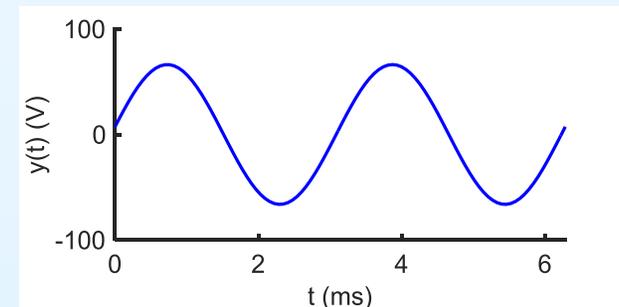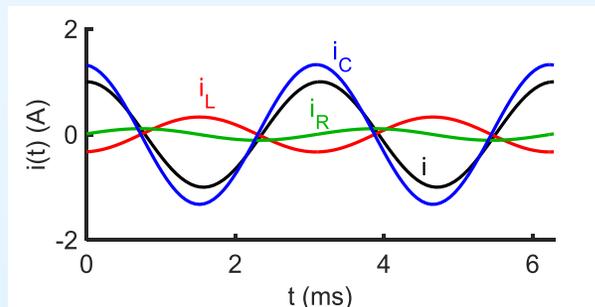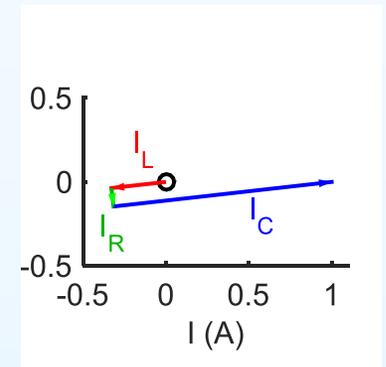
$$I_L = \frac{Y}{Z_L} = 0.33 \angle -174^\circ, I_C = 1.33 \angle +6^\circ$$




Most current now flows through  $C$ , only 0.11 through  $R$ .

# Bandwidth and Q
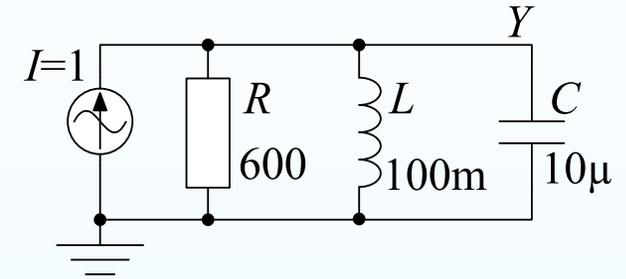
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$




## Bandwidth and Q

### 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$

**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called *half-power bandwidth* or *3dB bandwidth*.

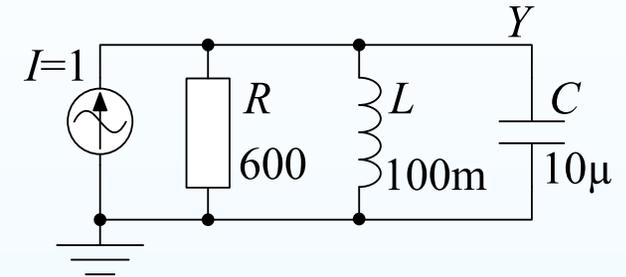



# Bandwidth and Q

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$

**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called *half-power bandwidth* or *3dB bandwidth*.

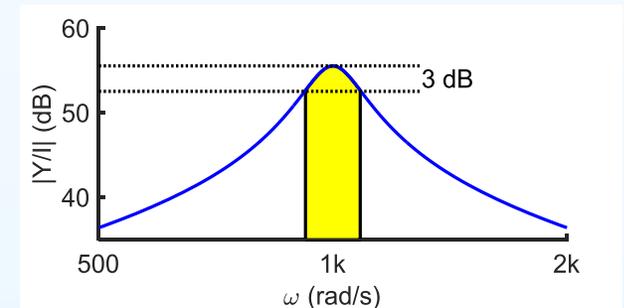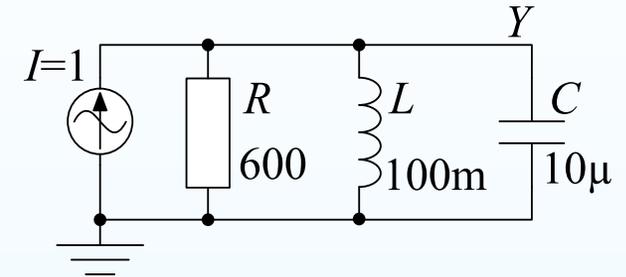

# Bandwidth and Q



## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$

**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called *half-power bandwidth* or *3dB bandwidth*.

$$\left|\frac{Y}{I}\right|^2 = \frac{1}{(1/R)^2 + (\omega C - 1/\omega L)^2}$$

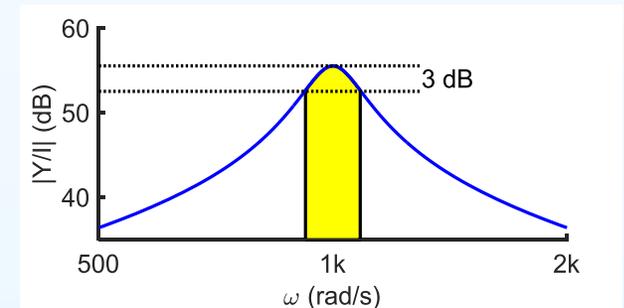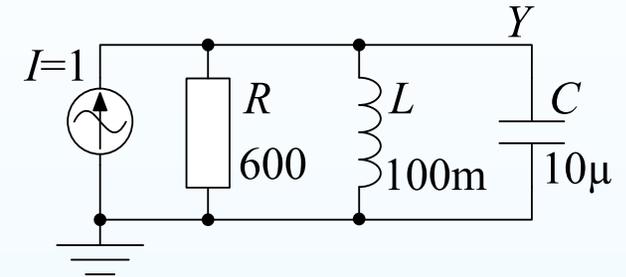

# Bandwidth and Q

## 12: Resonance



- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$

**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called *half-power bandwidth* or *3dB bandwidth*.

$$\left|\frac{Y}{I}\right|^2 = \frac{1}{(1/R)^2 + (\omega C - 1/\omega L)^2}$$

Peak is  $\left|\frac{Y}{I}(\omega_0)\right|^2 = R^2 @ \omega_0 = 1000$

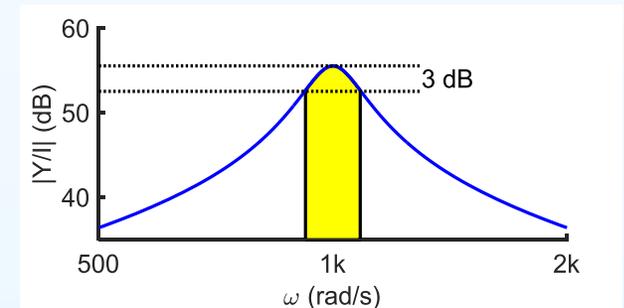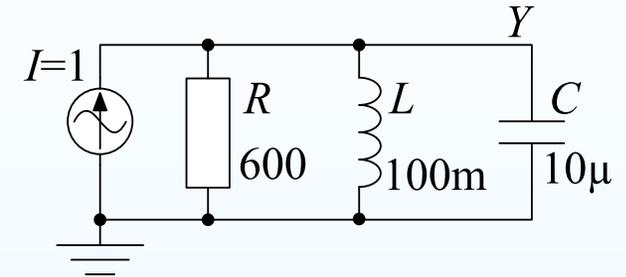

# Bandwidth and Q

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary



$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$

**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called **half-power bandwidth** or **3dB bandwidth**.

$$\left|\frac{Y}{I}\right|^2 = \frac{1}{(1/R)^2 + (\omega C - 1/\omega L)^2}$$

Peak is  $\left|\frac{Y}{I}(\omega_0)\right|^2 = R^2 @ \omega_0 = 1000$

At  $\omega_{3dB}$ :  $\left|\frac{Y}{I}(\omega_{3dB})\right|^2 = \frac{1}{2} \left|\frac{Y}{I}(\omega_0)\right|^2$

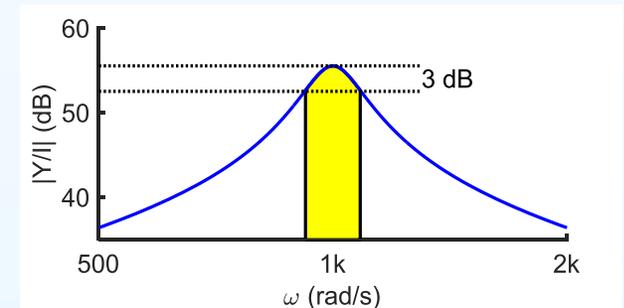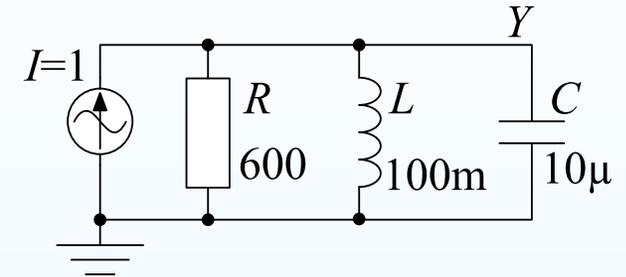

# Bandwidth and Q

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$



**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called **half-power bandwidth** or **3dB bandwidth**.

$$\left|\frac{Y}{I}\right|^2 = \frac{1}{(1/R)^2 + (\omega C - 1/\omega L)^2}$$

Peak is  $\left|\frac{Y}{I}(\omega_0)\right|^2 = R^2 @ \omega_0 = 1000$

At  $\omega_{3dB}$ :  $\left|\frac{Y}{I}(\omega_{3dB})\right|^2 = \frac{1}{2} \left|\frac{Y}{I}(\omega_0)\right|^2$
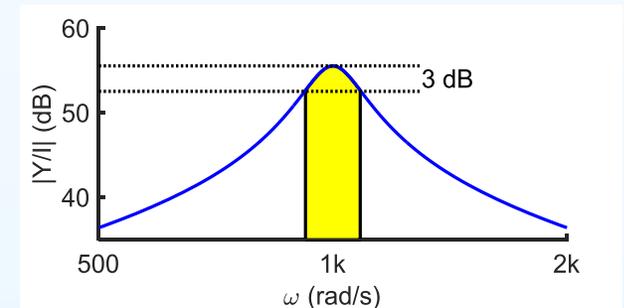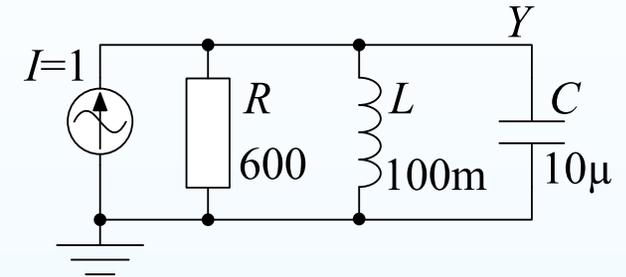
$$\frac{1}{(1/R)^2 + (\omega_{3dB} C - 1/\omega_{3dB} L)^2} = \frac{R^2}{2}$$



# Bandwidth and Q

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$



**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called *half-power bandwidth* or **3dB bandwidth**.

$$\left|\frac{Y}{I}\right|^2 = \frac{1}{(1/R)^2 + (\omega C - 1/\omega L)^2}$$

Peak is  $\left|\frac{Y}{I}(\omega_0)\right|^2 = R^2 @ \omega_0 = 1000$

At  $\omega_{3dB}$ :  $\left|\frac{Y}{I}(\omega_{3dB})\right|^2 = \frac{1}{2} \left|\frac{Y}{I}(\omega_0)\right|^2$
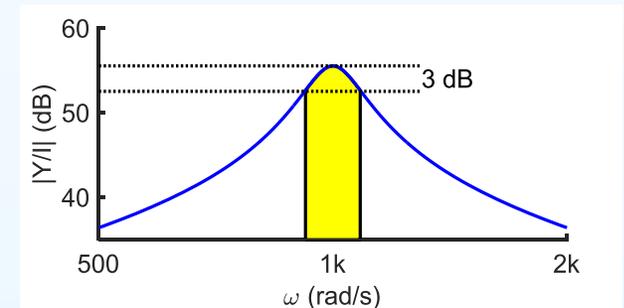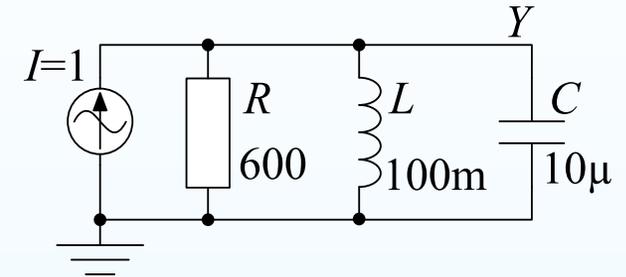
$$\frac{1}{(1/R)^2 + (\omega_{3dB} C - 1/\omega_{3dB} L)^2} = \frac{R^2}{2} \Rightarrow 1 + \left(\omega_{3dB} RC - \frac{R}{\omega_{3dB} L}\right)^2 = 2$$



# Bandwidth and Q

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$

**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called **half-power bandwidth** or **3dB bandwidth**.



$$\left|\frac{Y}{I}\right|^2 = \frac{1}{(1/R)^2 + (\omega C - 1/\omega L)^2}$$

Peak is  $\left|\frac{Y}{I}(\omega_0)\right|^2 = R^2 @ \omega_0 = 1000$

At  $\omega_{3dB}$ :  $\left|\frac{Y}{I}(\omega_{3dB})\right|^2 = \frac{1}{2} \left|\frac{Y}{I}(\omega_0)\right|^2$

$$\frac{1}{(1/R)^2 + (\omega_{3dB} C - 1/\omega_{3dB} L)^2} = \frac{R^2}{2} \Rightarrow 1 + \left(\omega_{3dB} RC - \frac{R}{\omega_{3dB} L}\right)^2 = 2$$
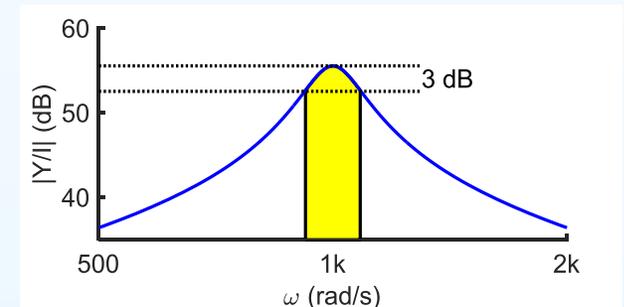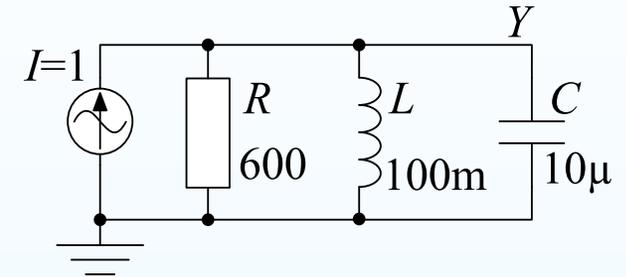
$$\omega_{3dB} RC - R/\omega_{3dB} L = \pm 1$$



# Bandwidth and Q

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$

**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called **half-power bandwidth** or **3dB bandwidth**.



$$\left|\frac{Y}{I}\right|^2 = \frac{1}{(1/R)^2 + (\omega C - 1/\omega L)^2}$$

Peak is  $\left|\frac{Y}{I}(\omega_0)\right|^2 = R^2 @ \omega_0 = 1000$

At  $\omega_{3dB}$ :  $\left|\frac{Y}{I}(\omega_{3dB})\right|^2 = \frac{1}{2} \left|\frac{Y}{I}(\omega_0)\right|^2$

$$\frac{1}{(1/R)^2 + (\omega_{3dB} C - 1/\omega_{3dB} L)^2} = \frac{R^2}{2} \Rightarrow 1 + \left(\omega_{3dB} RC - \frac{R}{\omega_{3dB} L}\right)^2 = 2$$
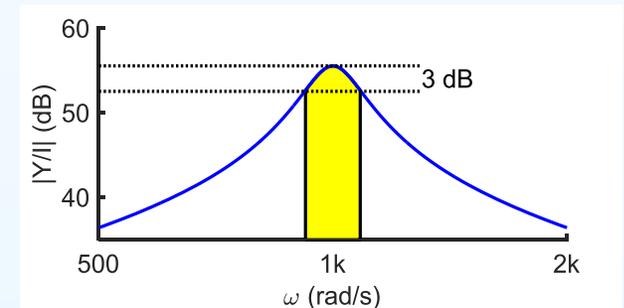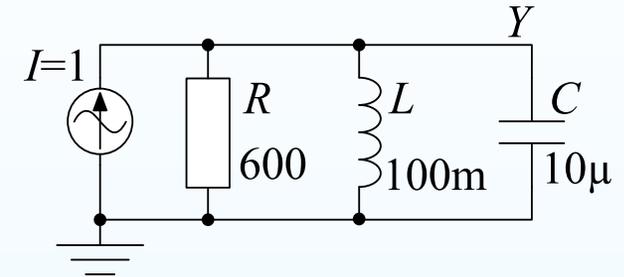
$$\omega_{3dB} RC - R/\omega_{3dB} L = \pm 1 \Rightarrow \omega_{3dB}^2 RLC \pm \omega_{3dB} L - R = 0$$



# Bandwidth and Q

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$

**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called **half-power bandwidth** or **3dB bandwidth**.

$$\left|\frac{Y}{I}\right|^2 = \frac{1}{(1/R)^2 + (\omega C - 1/\omega L)^2}$$



Peak is  $\left|\frac{Y}{I}(\omega_0)\right|^2 = R^2 @ \omega_0 = 1000$

At  $\omega_{3dB}$ :  $\left|\frac{Y}{I}(\omega_{3dB})\right|^2 = \frac{1}{2} \left|\frac{Y}{I}(\omega_0)\right|^2$

$$\frac{1}{(1/R)^2 + (\omega_{3dB} C - 1/\omega_{3dB} L)^2} = \frac{R^2}{2} \Rightarrow 1 + \left(\omega_{3dB} RC - \frac{R}{\omega_{3dB} L}\right)^2 = 2$$

$$\omega_{3dB} RC - R/\omega_{3dB} L = \pm 1 \Rightarrow \omega_{3dB}^2 RLC \pm \omega_{3dB} L - R = 0$$

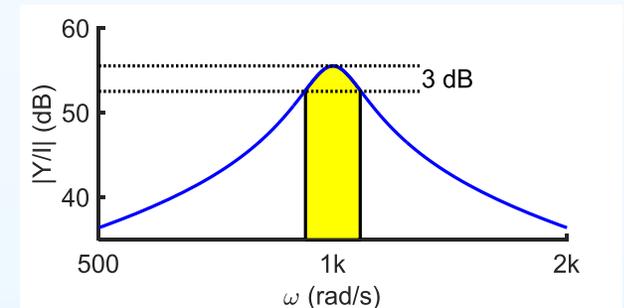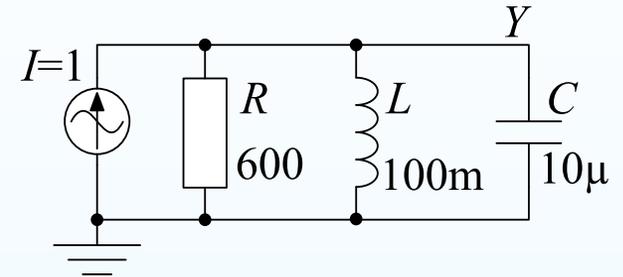Positive roots:  $\omega_{3dB} = \frac{\pm L + \sqrt{L^2 + 4R^2 LC}}{2RLC} = \{920, 1086\} \text{ rad/s}$



# Bandwidth and Q

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$

**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called *half-power bandwidth* or **3dB bandwidth**.

$$\left|\frac{Y}{I}\right|^2 = \frac{1}{(1/R)^2 + (\omega C - 1/\omega L)^2}$$

Peak is  $\left|\frac{Y}{I}(\omega_0)\right|^2 = R^2 @ \omega_0 = 1000$



At  $\omega_{3dB}$ :  $\left|\frac{Y}{I}(\omega_{3dB})\right|^2 = \frac{1}{2} \left|\frac{Y}{I}(\omega_0)\right|^2$

$$\frac{1}{(1/R)^2 + (\omega_{3dB} C - 1/\omega_{3dB} L)^2} = \frac{R^2}{2} \Rightarrow 1 + \left(\omega_{3dB} RC - \frac{R}{\omega_{3dB} L}\right)^2 = 2$$

$$\omega_{3dB} RC - R/\omega_{3dB} L = \pm 1 \Rightarrow \omega_{3dB}^2 RLC \pm \omega_{3dB} L - R = 0$$

Positive roots:  $\omega_{3dB} = \frac{\pm L + \sqrt{L^2 + 4R^2 LC}}{2RLC} = \{920, 1086\} \text{ rad/s}$

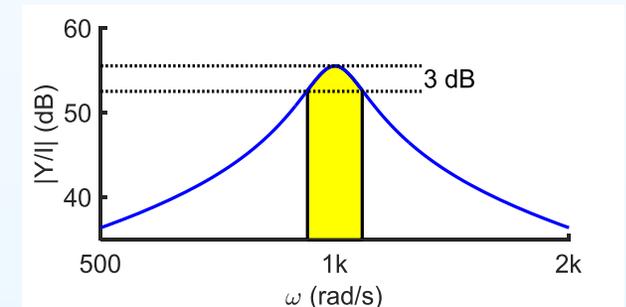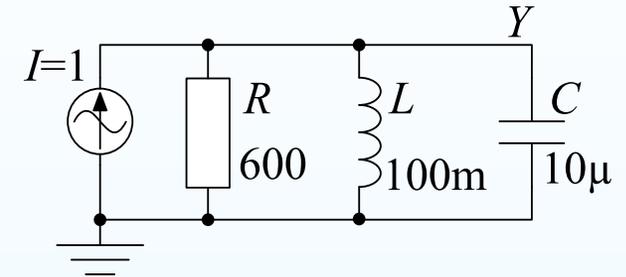**Bandwidth:**  $B = 1086 - 920 = 167 \text{ rad/s}$ .



# Bandwidth and Q

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- **Bandwidth and Q**
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{I} = \frac{1}{1/R + j(\omega C - 1/\omega L)}$$

**Bandwidth** is the range of frequencies for which  $\left|\frac{Y}{I}\right|^2$  is greater than half its peak. Also called *half-power bandwidth* or **3dB bandwidth**.

$$\left|\frac{Y}{I}\right|^2 = \frac{1}{(1/R)^2 + (\omega C - 1/\omega L)^2}$$

Peak is  $\left|\frac{Y}{I}(\omega_0)\right|^2 = R^2 @ \omega_0 = 1000$

At  $\omega_{3dB}$ :  $\left|\frac{Y}{I}(\omega_{3dB})\right|^2 = \frac{1}{2} \left|\frac{Y}{I}(\omega_0)\right|^2$



$$\frac{1}{(1/R)^2 + (\omega_{3dB} C - 1/\omega_{3dB} L)^2} = \frac{R^2}{2} \Rightarrow 1 + \left(\omega_{3dB} RC - \frac{R}{\omega_{3dB} L}\right)^2 = 2$$

$$\omega_{3dB} RC - R/\omega_{3dB} L = \pm 1 \Rightarrow \omega_{3dB}^2 RLC \pm \omega_{3dB} L - R = 0$$

Positive roots:  $\omega_{3dB} = \frac{\pm L + \sqrt{L^2 + 4R^2 LC}}{2RLC} = \{920, 1086\} \text{ rad/s}$

**Bandwidth:**  $B = 1086 - 920 = 167 \text{ rad/s}$ .

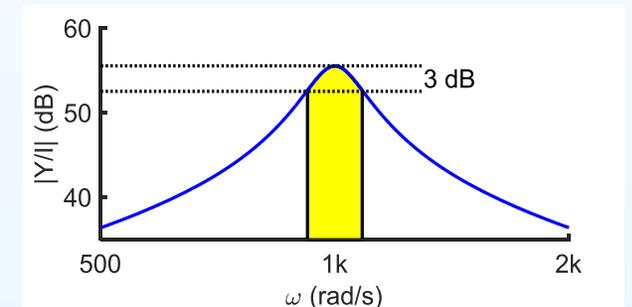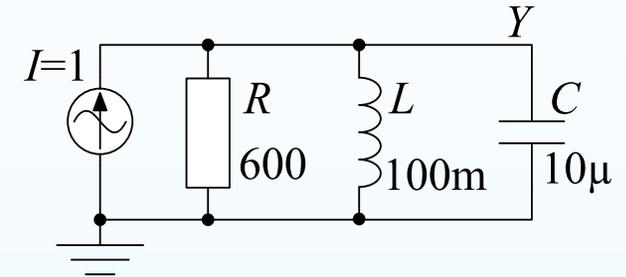**Q factor**  $\approx \frac{\omega_0}{B} = \frac{1}{2\zeta} = 6$ . ( $Q = \text{“Quality”}$ )




# Power and Energy at Resonance




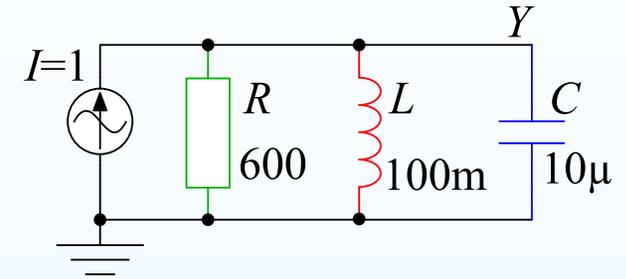
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary



$$@\omega = 1000: Y = 600,$$

$$I_R = 1, I_L = -6j, I_C = +6j$$

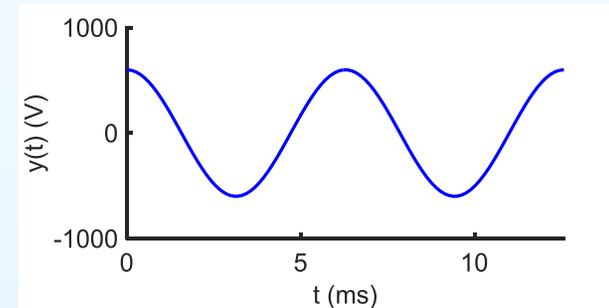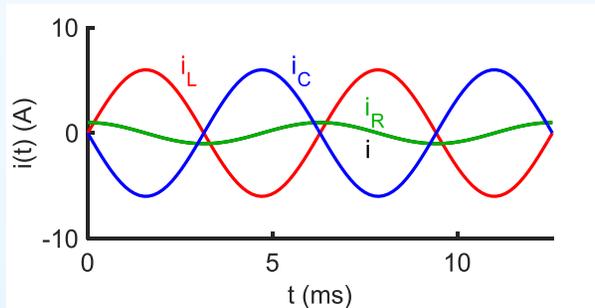


# Power and Energy at Resonance



## 12: Resonance



- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Absorbed Power  $=v(t)i(t)$ :

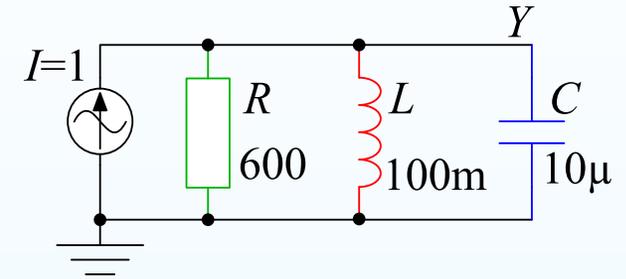

@ $\omega = 1000$ :  $Y = 600$ ,

$I_R = 1, I_L = -6j, I_C = +6j$

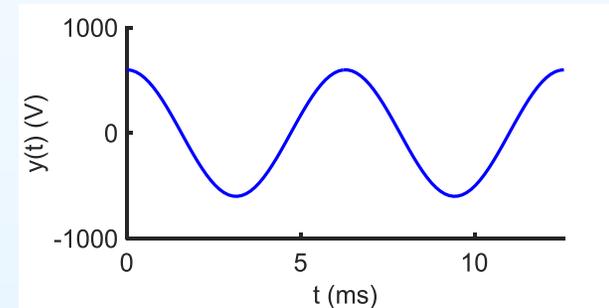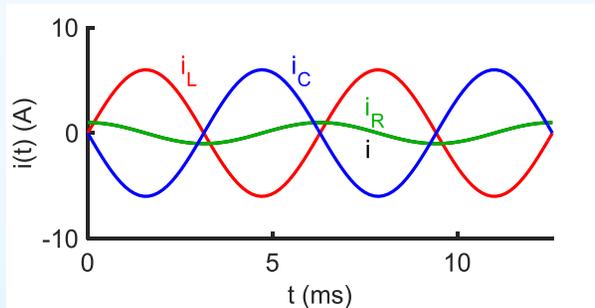


# Power and Energy at Resonance



## 12: Resonance




- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Absorbed Power  $=v(t)i(t)$ :

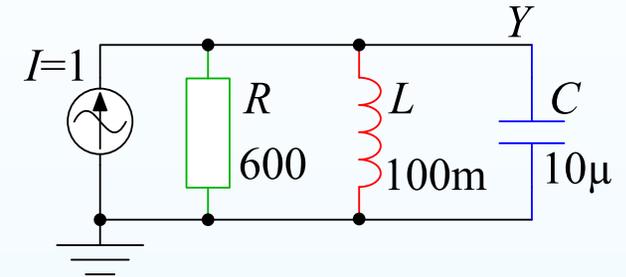

@ $\omega = 1000$ :  $Y = 600$ ,

$I_R = 1, I_L = -6j, I_C = +6j$

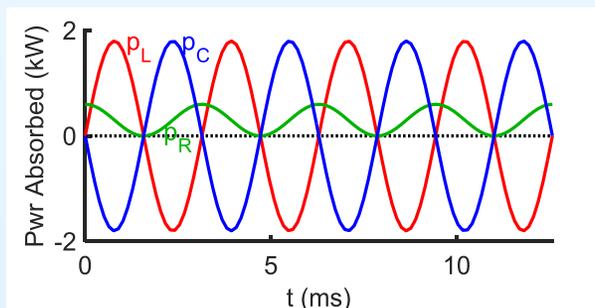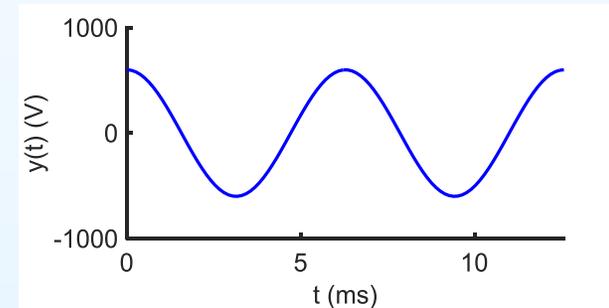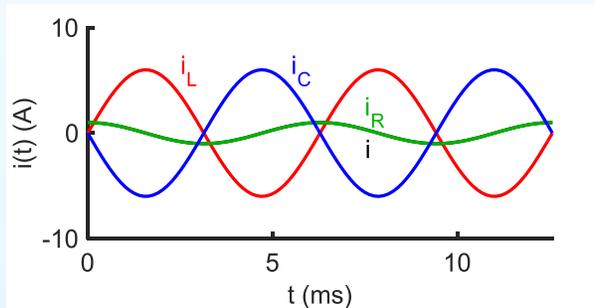


# Power and Energy at Resonance





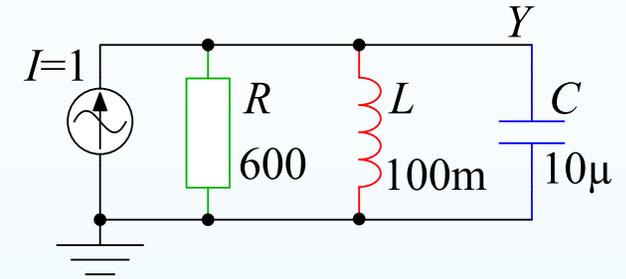
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Absorbed Power  $= v(t)i(t)$ :  
 $P_L$  and  $P_C$  opposite and  $\gg P_R$ .



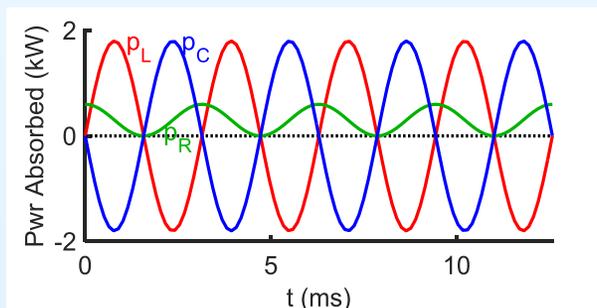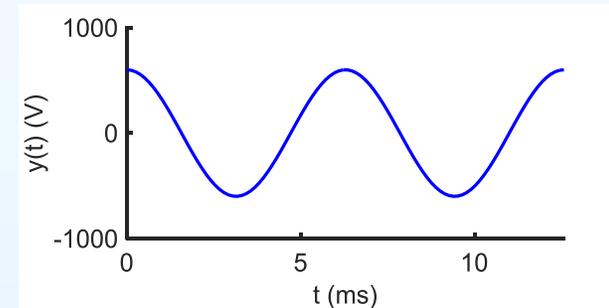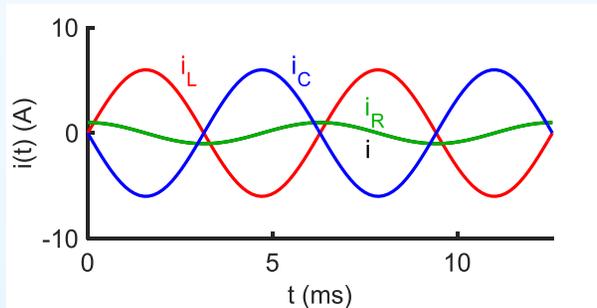@ $\omega = 1000$ :  $Y = 600$ ,  
 $I_R = 1$ ,  $I_L = -6j$ ,  $I_C = +6j$



# Power and Energy at Resonance




## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Absorbed Power  $= v(t)i(t)$ :




$P_L$  and  $P_C$  opposite and  $\gg P_R$ .

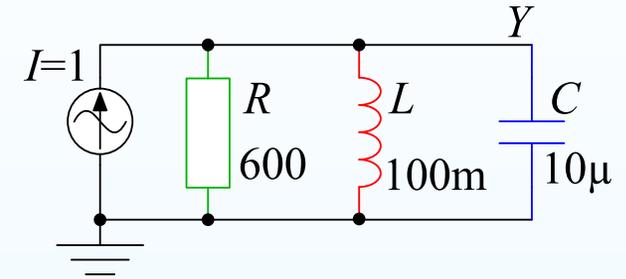Stored Energy  $= \frac{1}{2}Li_L^2 + \frac{1}{2}Cy^2$ :



@ $\omega = 1000$ :  $Y = 600$ ,

$I_R = 1, I_L = -6j, I_C = +6j$

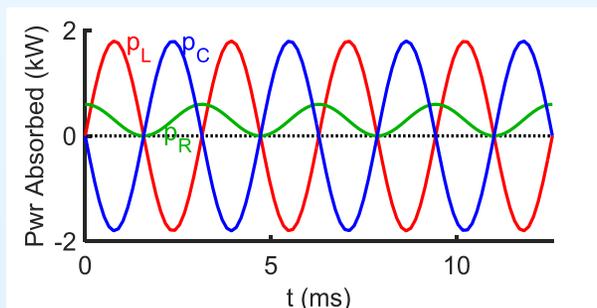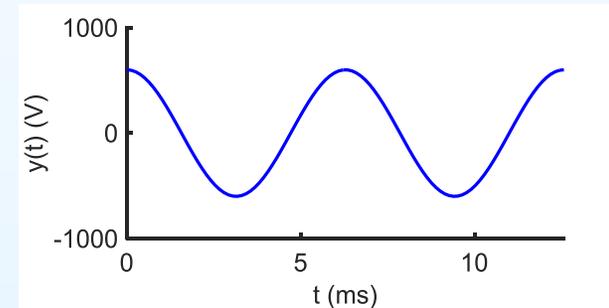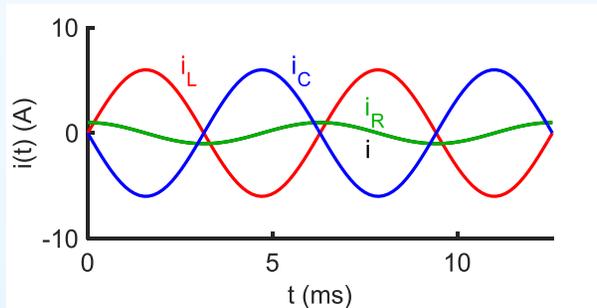

# Power and Energy at Resonance




## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Absorbed Power  $= v(t)i(t)$ :





$P_L$  and  $P_C$  opposite and  $\gg P_R$ .

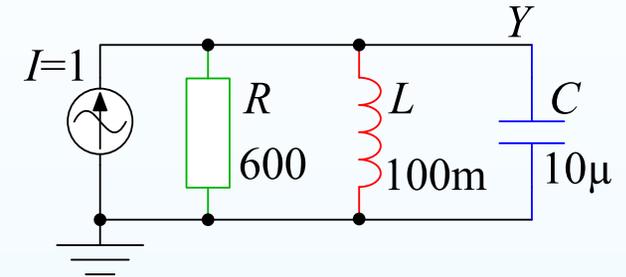Stored Energy  $= \frac{1}{2}Li_L^2 + \frac{1}{2}Cy^2$ :



@ $\omega = 1000$ :  $Y = 600$ ,

$I_R = 1, I_L = -6j, I_C = +6j$

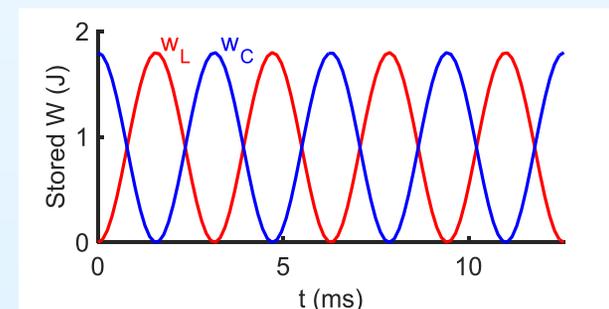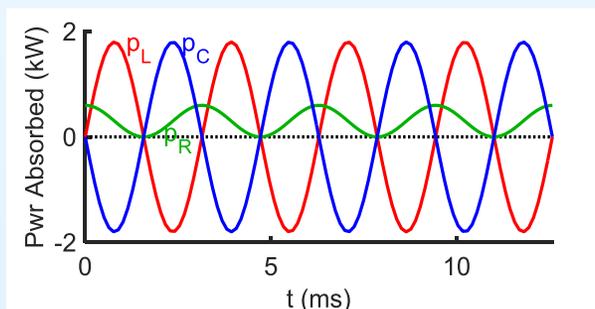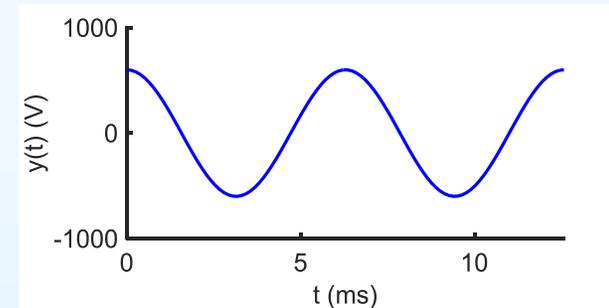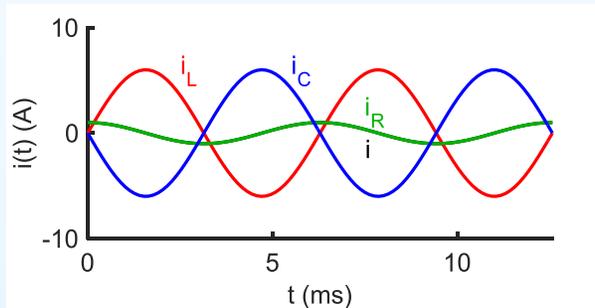

# Power and Energy at Resonance




## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Absorbed Power =  $v(t)i(t)$ :





$P_L$  and  $P_C$  opposite and  $\gg P_R$ .

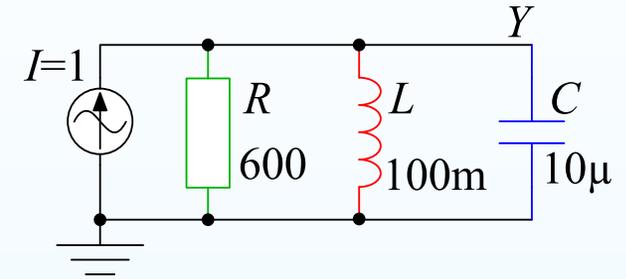Stored Energy =  $\frac{1}{2}Li_L^2 + \frac{1}{2}Cy^2$ :  
sloshes between  $L$  and  $C$ .



@ $\omega = 1000$ :  $Y = 600$ ,

$I_R = 1, I_L = -6j, I_C = +6j$

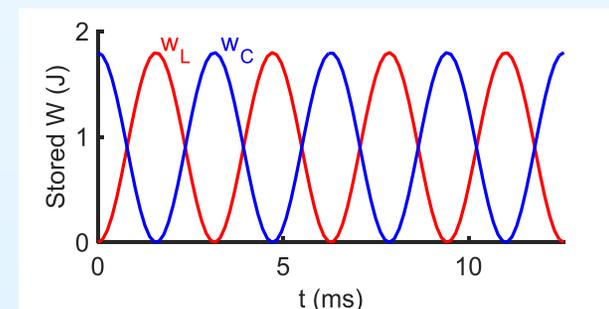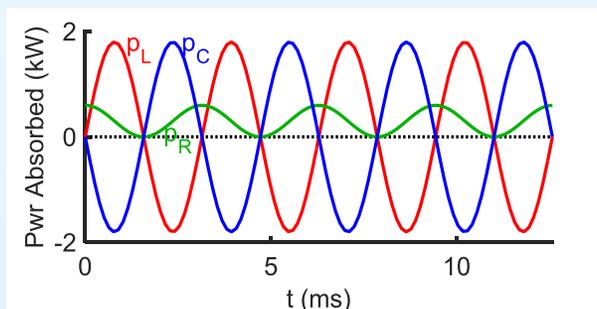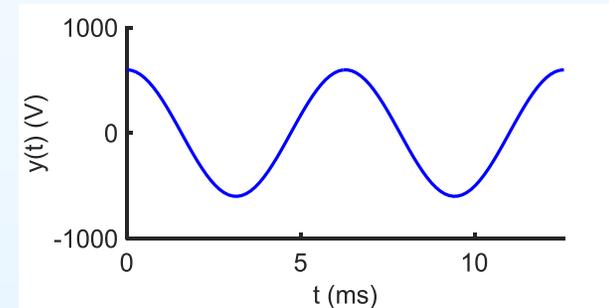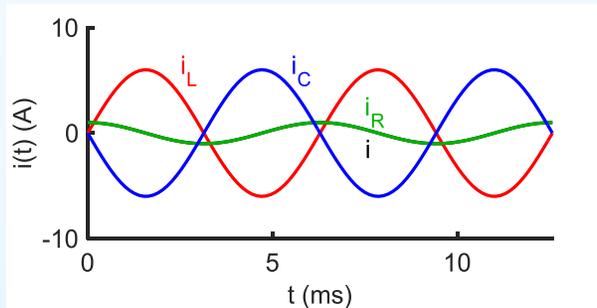

# Power and Energy at Resonance



## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary


Absorbed Power =  $v(t)i(t)$ :

$P_L$  and  $P_C$  opposite and  $\gg P_R$ .

Stored Energy =  $\frac{1}{2}Li_L^2 + \frac{1}{2}Cy^2$ :





sloshes between  $L$  and  $C$ .

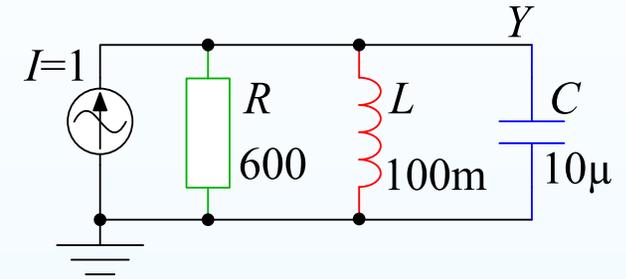$Q \triangleq \omega \times W_{\text{stored}} \div \bar{P}_R$



@ $\omega = 1000$ :  $Y = 600$ ,

$I_R = 1, I_L = -6j, I_C = +6j$

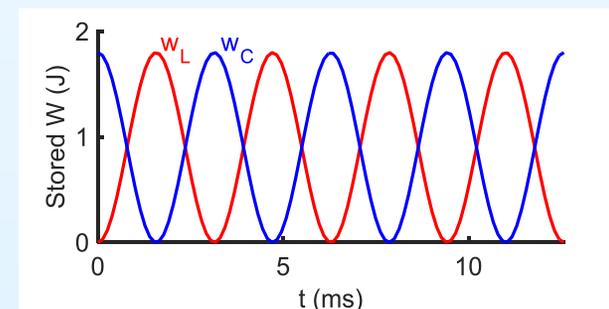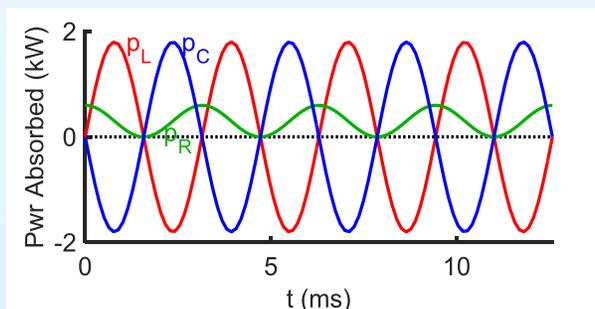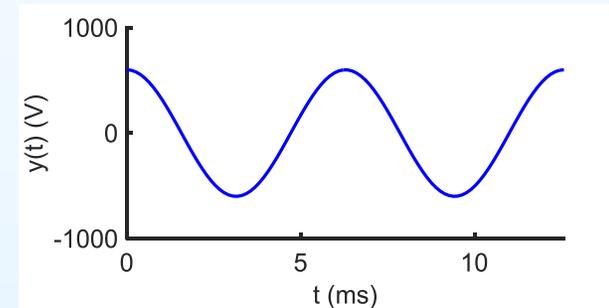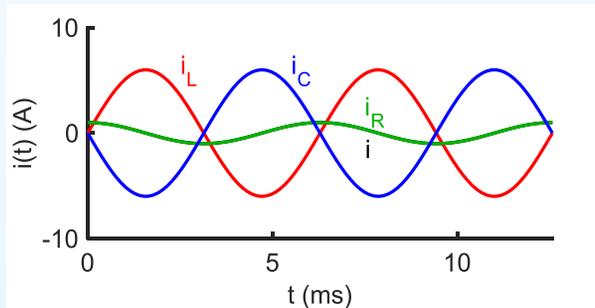

# Power and Energy at Resonance



## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Absorbed Power =  $v(t)i(t)$ :


$P_L$  and  $P_C$  opposite and  $\gg P_R$ .

Stored Energy =  $\frac{1}{2}Li_L^2 + \frac{1}{2}Cy^2$ :

sloshes between  $L$  and  $C$ .





$$Q \triangleq \omega \times W_{\text{stored}} \div \bar{P}_R$$

$$= \omega \times \frac{1}{2}C |IR|^2 \div \frac{1}{2} |I|^2 R = \omega RC$$

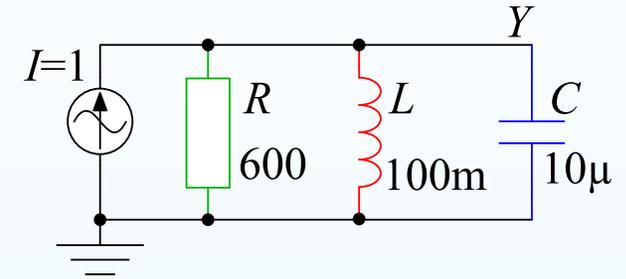

@ $\omega = 1000$ :  $Y = 600$ ,

$I_R = 1, I_L = -6j, I_C = +6j$

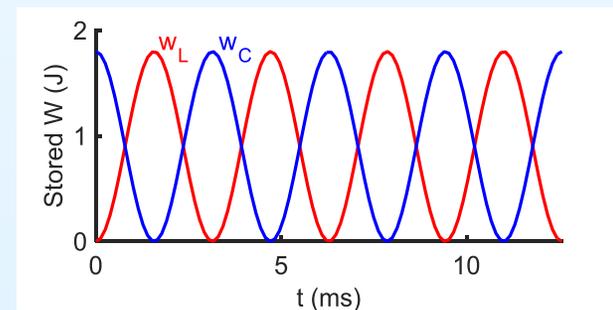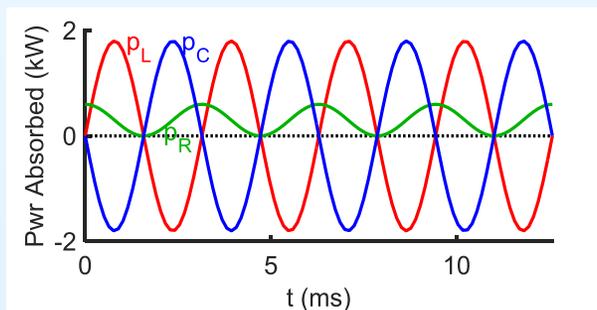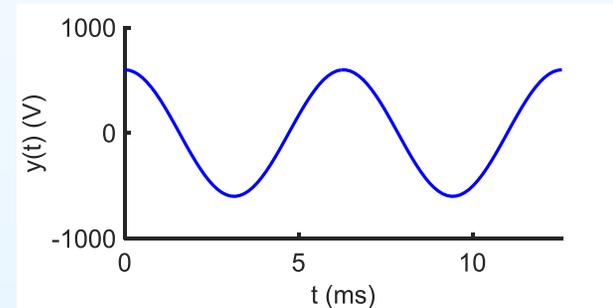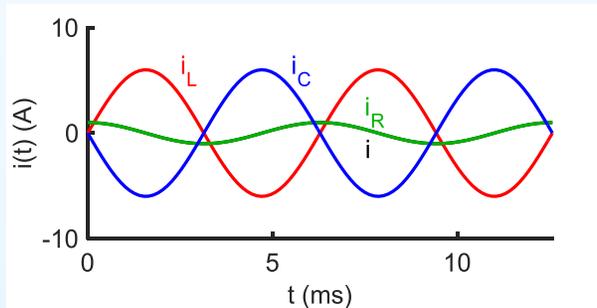

# Power and Energy at Resonance



## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

Absorbed Power =  $v(t)i(t)$ :


$P_L$  and  $P_C$  opposite and  $\gg P_R$ .

Stored Energy =  $\frac{1}{2}Li_L^2 + \frac{1}{2}Cy^2$ :

sloshes between  $L$  and  $C$ .





$$Q \triangleq \omega \times W_{\text{stored}} \div \bar{P}_R$$

$$= \omega \times \frac{1}{2}C |IR|^2 \div \frac{1}{2} |I|^2 R = \omega RC$$

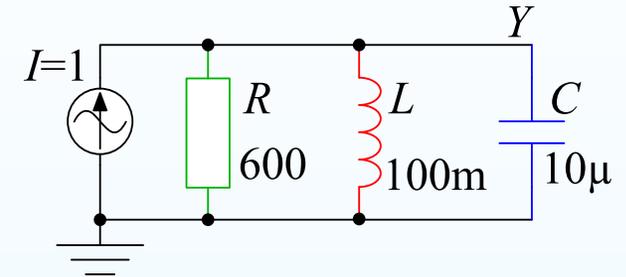

@ $\omega = 1000$ :  $Y = 600$ ,

$I_R = 1, I_L = -6j, I_C = +6j$

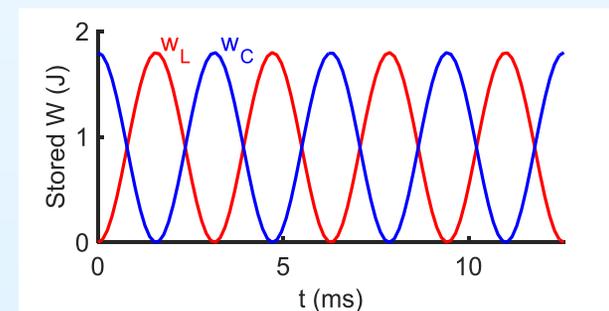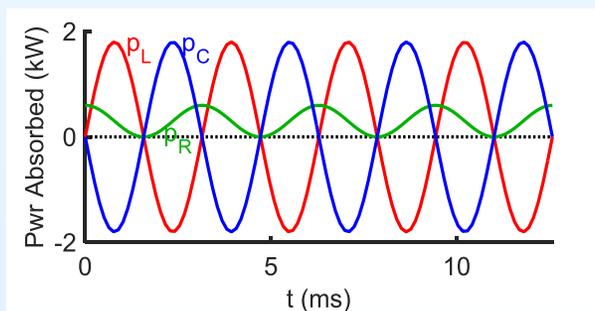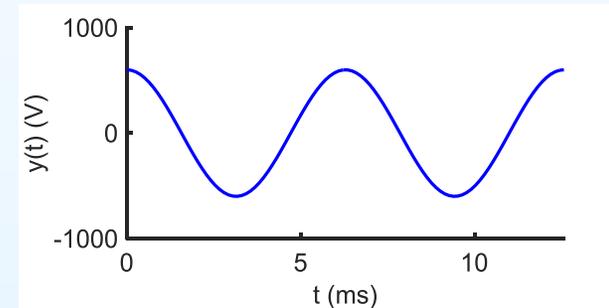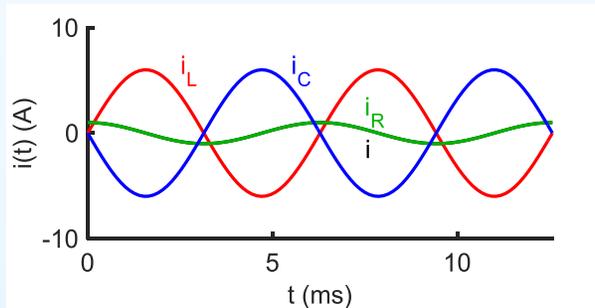


$Q \triangleq \omega \times \text{peak stored energy} \div \text{average power loss.}$

# Low Pass Filter
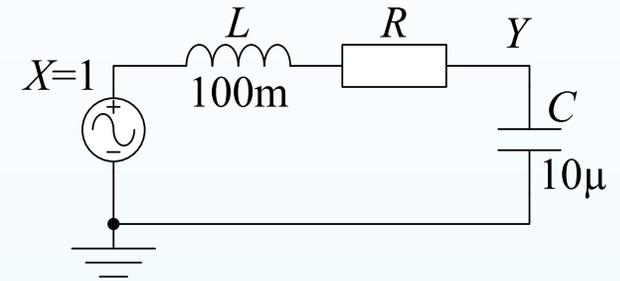
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$




# Low Pass Filter

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

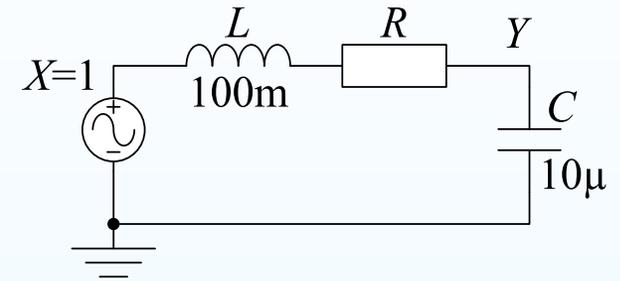Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .



# Low Pass Filter


## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .
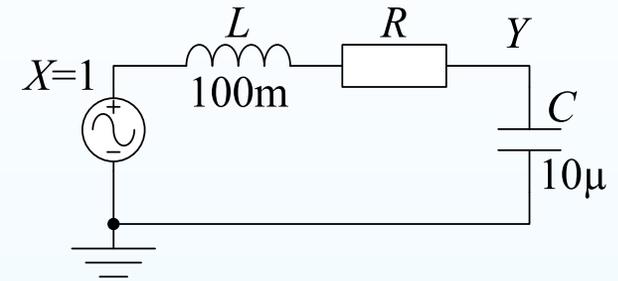
$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$



# Low Pass Filter

## 12: Resonance



- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$
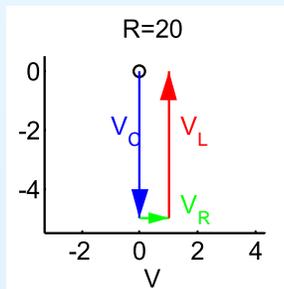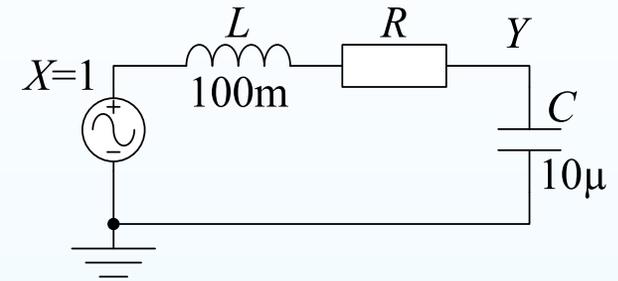
$$@\omega_c : Z_L = -Z_C = 100j, \quad I = \frac{X}{R}$$



# Low Pass Filter

## 12: Resonance



- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$

$$@\omega_c : Z_L = -Z_C = 100j, \quad I = \frac{X}{R}, \quad \left| \frac{Y}{X} \right| = \frac{1}{RC\omega} = \frac{1}{2\zeta}, \quad \angle \frac{Y}{X} = -\frac{\pi}{2}$$

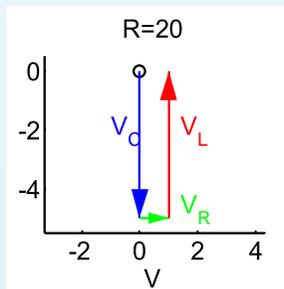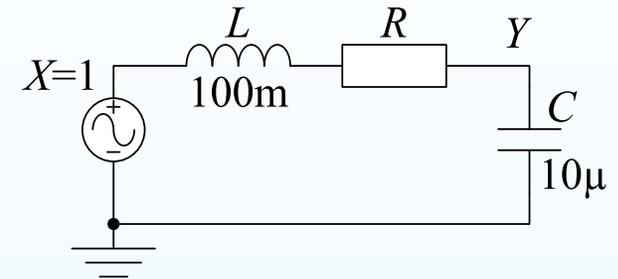

# Low Pass Filter

## 12: Resonance


- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$



Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$

$$@\omega_c : Z_L = -Z_C = 100j, \quad I = \frac{X}{R}, \quad \left| \frac{Y}{X} \right| = \frac{1}{RC\omega} = \frac{1}{2\zeta}, \quad \angle \frac{Y}{X} = -\frac{\pi}{2}$$

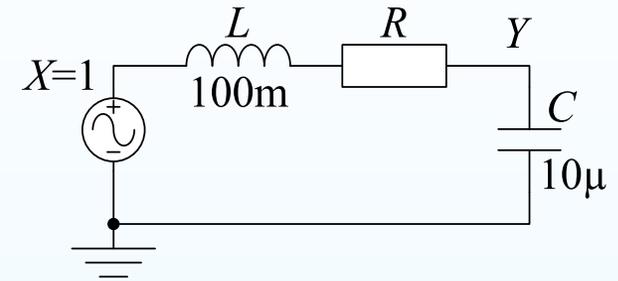

Magnitude Plot:

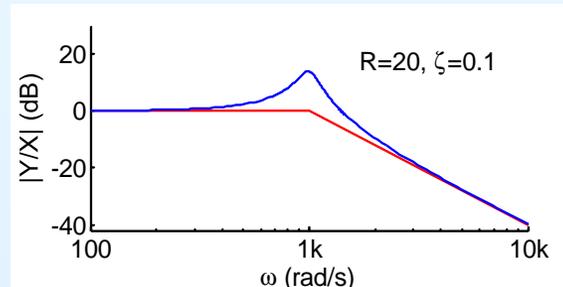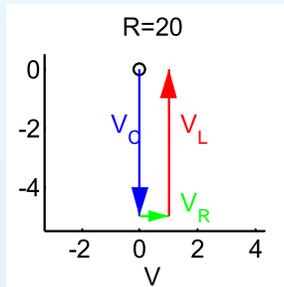

# Low Pass Filter

## 12: Resonance


- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .



$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$

$$@\omega_c : Z_L = -Z_C = 100j, \quad I = \frac{X}{R}, \quad \left| \frac{Y}{X} \right| = \frac{1}{RC\omega} = \frac{1}{2\zeta}, \quad \angle \frac{Y}{X} = -\frac{\pi}{2}$$

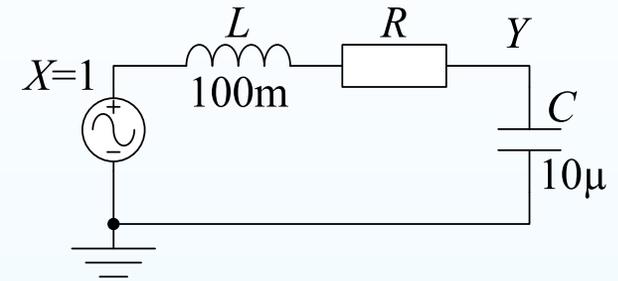

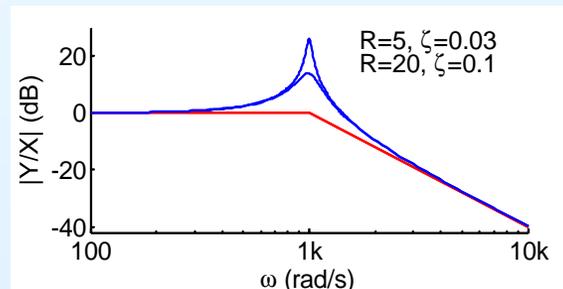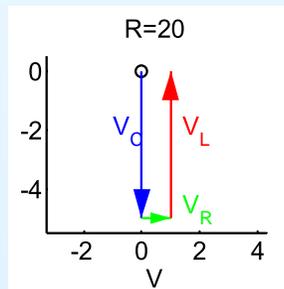**Magnitude Plot:**

Small  $\zeta \Rightarrow$  less loss, higher peak, smaller bandwidth.



# Low Pass Filter

## 12: Resonance


- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$



$$@\omega_c : Z_L = -Z_C = 100j, \quad I = \frac{X}{R}, \quad \left| \frac{Y}{X} \right| = \frac{1}{RC\omega} = \frac{1}{2\zeta}, \quad \angle \frac{Y}{X} = -\frac{\pi}{2}$$

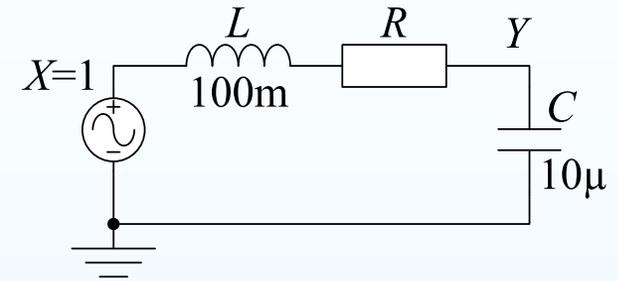
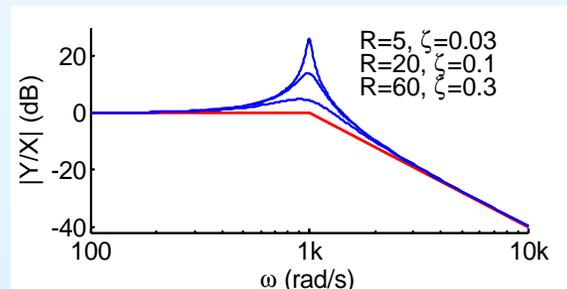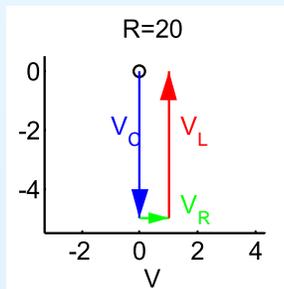
## Magnitude Plot:

Small  $\zeta \Rightarrow$  less loss, higher peak, smaller bandwidth.

Large  $\zeta$  more loss, smaller peak at a lower  $\omega$ , larger bandwidth.



# Low Pass Filter

## 12: Resonance


- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$



$$@\omega_c : Z_L = -Z_C = 100j, \quad I = \frac{X}{R}, \quad \left| \frac{Y}{X} \right| = \frac{1}{RC\omega} = \frac{1}{2\zeta}, \quad \angle \frac{Y}{X} = -\frac{\pi}{2}$$

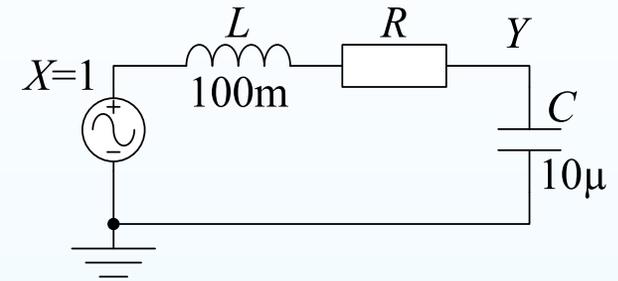
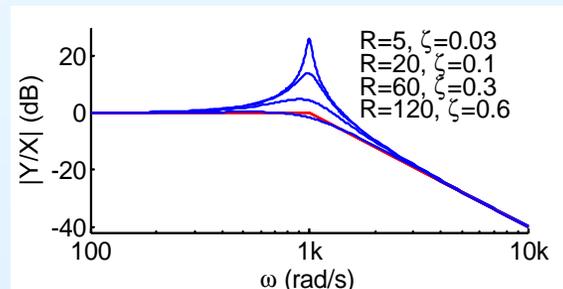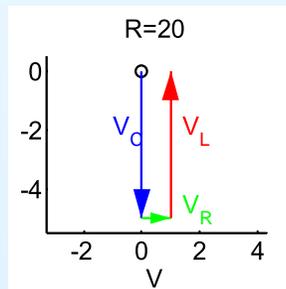
## Magnitude Plot:

Small  $\zeta \Rightarrow$  less loss, higher peak, smaller bandwidth.

Large  $\zeta$  more loss, smaller peak at a lower  $\omega$ , larger bandwidth.



# Low Pass Filter

## 12: Resonance


- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$

$$@\omega_c : Z_L = -Z_C = 100j, \quad I = \frac{X}{R}, \quad \left| \frac{Y}{X} \right| = \frac{1}{RC\omega} = \frac{1}{2\zeta}, \quad \angle \frac{Y}{X} = -\frac{\pi}{2}$$



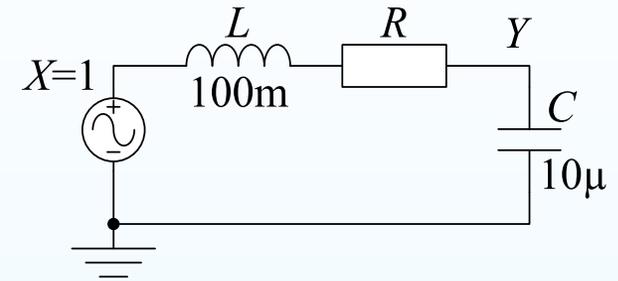


## Magnitude Plot:

Small  $\zeta \Rightarrow$  less loss, higher peak, smaller bandwidth.

Large  $\zeta$  more loss, smaller peak at a lower  $\omega$ , larger bandwidth.

## Phase Plot:

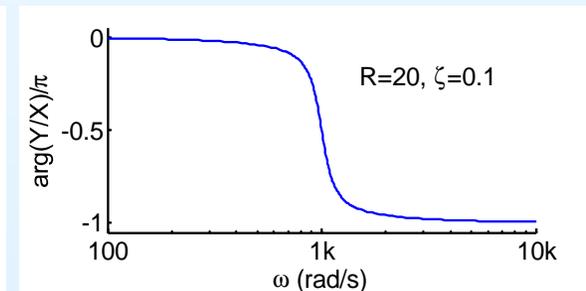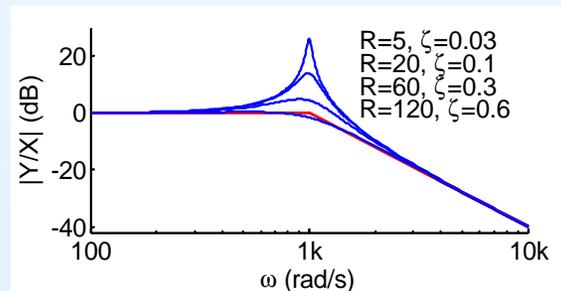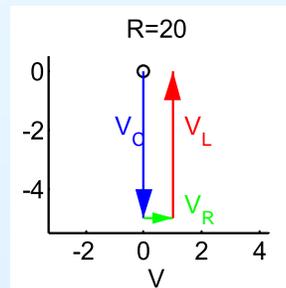

# Low Pass Filter

## 12: Resonance


- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$

$$@\omega_c : Z_L = -Z_C = 100j, \quad I = \frac{X}{R}, \quad \left| \frac{Y}{X} \right| = \frac{1}{RC\omega} = \frac{1}{2\zeta}, \quad \angle \frac{Y}{X} = -\frac{\pi}{2}$$

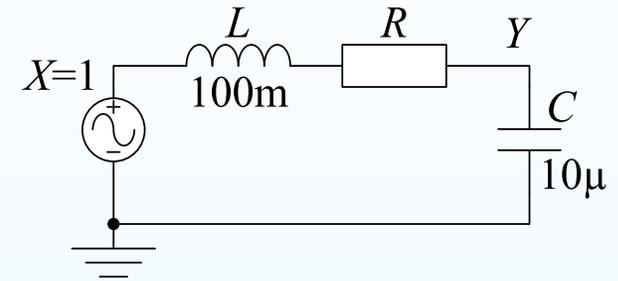




## Magnitude Plot:

Small  $\zeta \Rightarrow$  less loss, higher peak, smaller bandwidth.

Large  $\zeta$  more loss, smaller peak at a lower  $\omega$ , larger bandwidth.
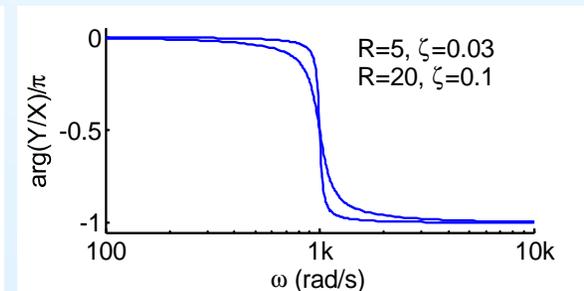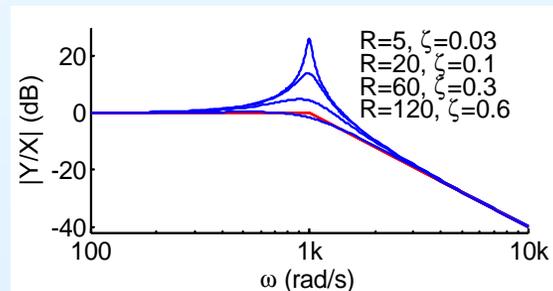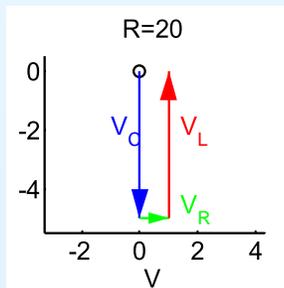
## Phase Plot:

Small  $\zeta \Rightarrow$  fast phase change:  $\pi$  over  $2\zeta$  decades.



# Low Pass Filter

## 12: Resonance


- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$

$$@\omega_c : Z_L = -Z_C = 100j, \quad I = \frac{X}{R}, \quad \left| \frac{Y}{X} \right| = \frac{1}{RC\omega} = \frac{1}{2\zeta}, \quad \angle \frac{Y}{X} = -\frac{\pi}{2}$$

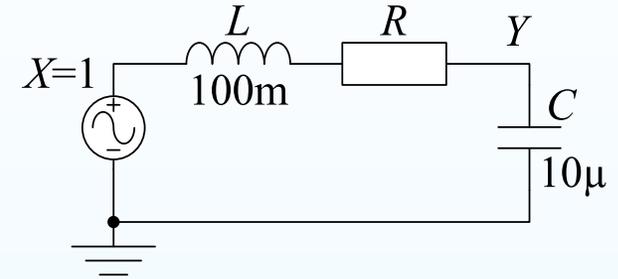




## Magnitude Plot:

Small  $\zeta \Rightarrow$  less loss, higher peak, smaller bandwidth.

Large  $\zeta \Rightarrow$  more loss, smaller peak at a lower  $\omega$ , larger bandwidth.
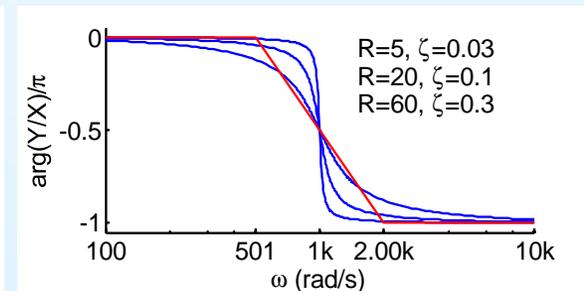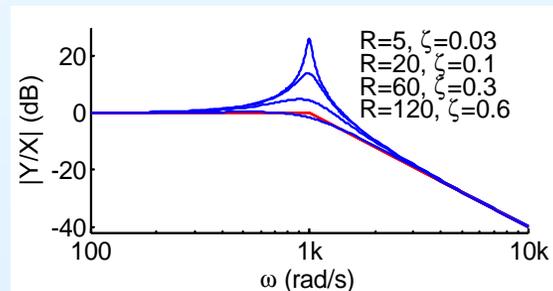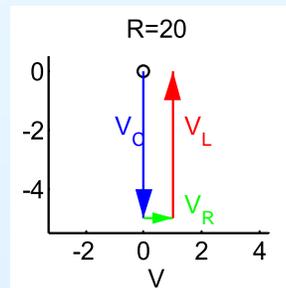
## Phase Plot:

Small  $\zeta \Rightarrow$  fast phase change:  $\pi$  over  $2\zeta$  decades.



# Low Pass Filter

## 12: Resonance


- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$

$$@\omega_c : Z_L = -Z_C = 100j, \quad I = \frac{X}{R}, \quad \left| \frac{Y}{X} \right| = \frac{1}{RC\omega} = \frac{1}{2\zeta}, \quad \angle \frac{Y}{X} = -\frac{\pi}{2}$$

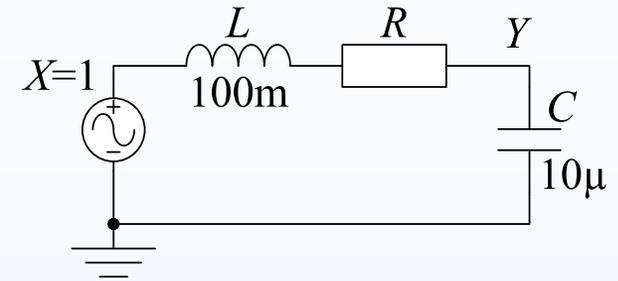




## Magnitude Plot:

Small  $\zeta \Rightarrow$  less loss, higher peak, smaller bandwidth.

Large  $\zeta$  more loss, smaller peak at a lower  $\omega$ , larger bandwidth.
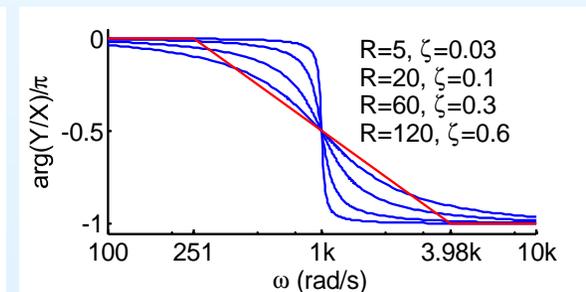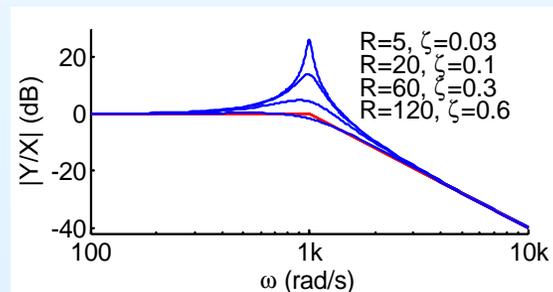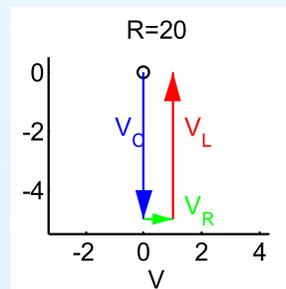
## Phase Plot:

Small  $\zeta \Rightarrow$  fast phase change:  $\pi$  over  $2\zeta$  decades.



# Low Pass Filter

## 12: Resonance


- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- **Low Pass Filter**
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1/j\omega C}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$

Asymptotes: 1 and  $\frac{1}{LC} (j\omega)^{-2}$ .

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{R}{200}$$

$$@\omega_c : Z_L = -Z_C = 100j, \quad I = \frac{X}{R}, \quad \left| \frac{Y}{X} \right| = \frac{1}{RC\omega} = \frac{1}{2\zeta}, \quad \angle \frac{Y}{X} = -\frac{\pi}{2}$$

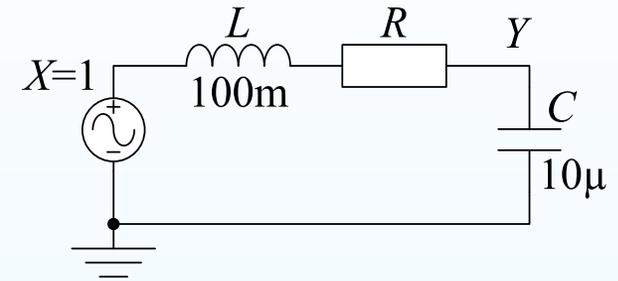

## Magnitude Plot:




Small  $\zeta \Rightarrow$  less loss, higher peak, smaller bandwidth.

Large  $\zeta$  more loss, smaller peak at a lower  $\omega$ , larger bandwidth.
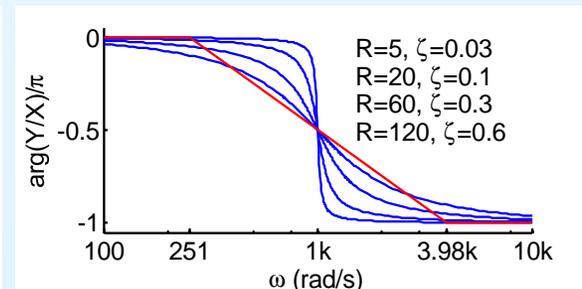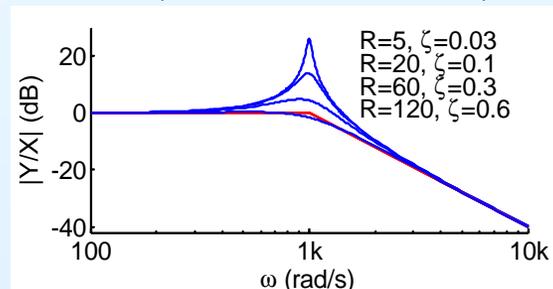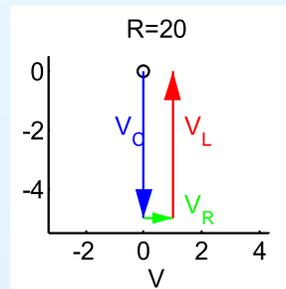
## Phase Plot:

Small  $\zeta \Rightarrow$  fast phase change:  $\pi$  over  $2\zeta$  decades.

$$\angle \frac{Y}{X} \approx \frac{-\pi}{2} \left( 1 + \frac{1}{\zeta} \log_{10} \frac{\omega}{\omega_c} \right) \text{ for } 10^{-\zeta} < \frac{\omega}{\omega_c} < 10^{+\zeta}$$




# Resonance Peak for LP filter
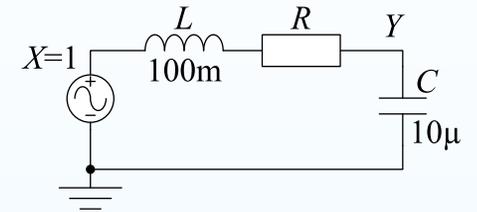
## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$




## Resonance Peak for LP filter

### 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1}$$
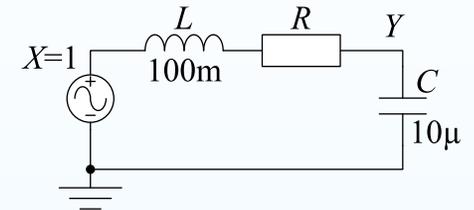
$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$




## Resonance Peak for LP filter

### 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{\left(j\frac{\omega}{\omega_c}\right)^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$
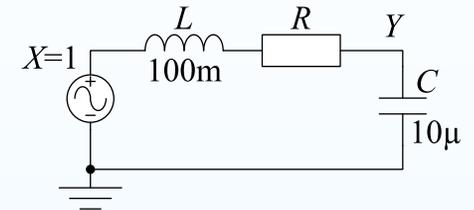
$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$



## Resonance Peak for LP filter


### 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{\left(j\frac{\omega}{\omega_c}\right)^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$

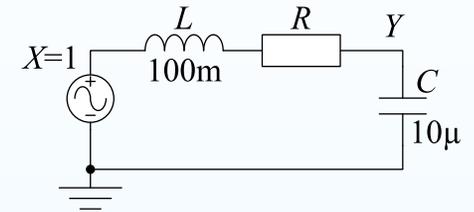$\frac{Y}{X}$  is a function of  $\frac{\omega}{\omega_c}$  so  $\omega_c$  just scales frequency axis (= shift on log axis).



## Resonance Peak for LP filter


### 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{\left(j\frac{\omega}{\omega_c}\right)^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$

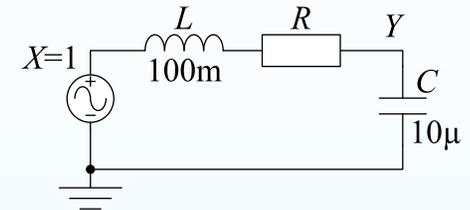$\frac{Y}{X}$  is a function of  $\frac{\omega}{\omega_c}$  so  $\omega_c$  just scales frequency axis (= shift on log axis).  
The *damping factor*,  $\zeta$ , ("zeta") determines the shape of the peak.



# Resonance Peak for LP filter


## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{\left(j\frac{\omega}{\omega_c}\right)^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$


$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$

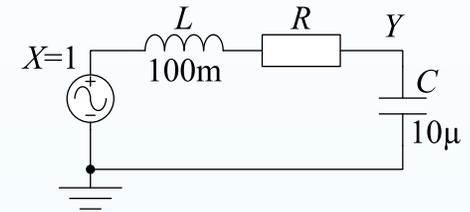$\frac{Y}{X}$  is a function of  $\frac{\omega}{\omega_c}$  so  $\omega_c$  just scales frequency axis (= shift on log axis).  
The *damping factor*,  $\zeta$ , ("zeta") determines the shape of the peak.



Peak frequency:
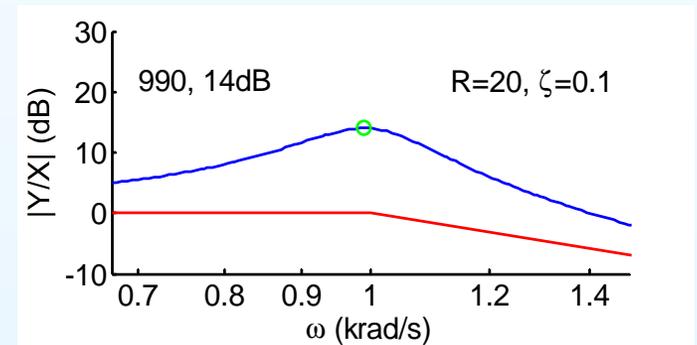
$$\omega_p = \omega_c \sqrt{1 - 2\zeta^2}$$



# Resonance Peak for LP filter


## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{\left(j\frac{\omega}{\omega_c}\right)^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$

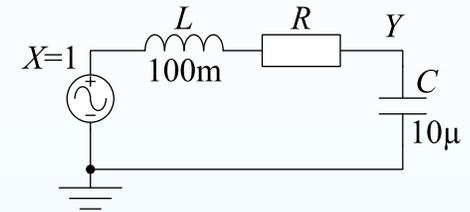
$\frac{Y}{X}$  is a function of  $\frac{\omega}{\omega_c}$  so  $\omega_c$  just scales frequency axis (= shift on log axis).  
The *damping factor*,  $\zeta$ , ("zeta") determines the shape of the peak.



Peak frequency:

$$\omega_p = \omega_c \sqrt{1 - 2\zeta^2}$$

$\zeta \geq 0.71 \Rightarrow$  no peak,

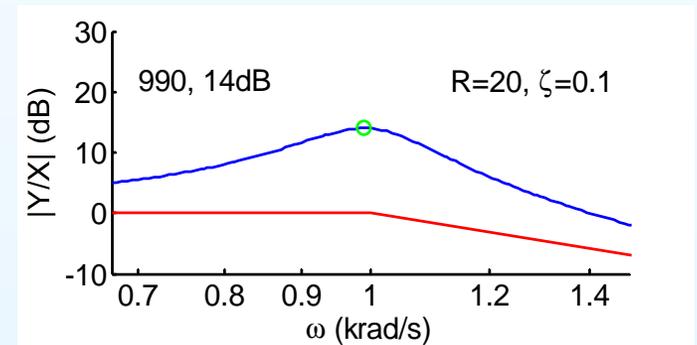

# Resonance Peak for LP filter


## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{\left(j\frac{\omega}{\omega_c}\right)^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$

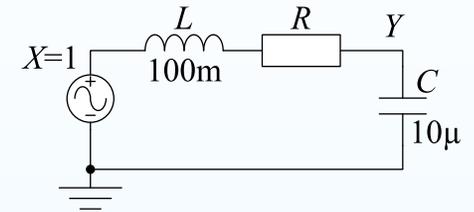$\frac{Y}{X}$  is a function of  $\frac{\omega}{\omega_c}$  so  $\omega_c$  just scales frequency axis (= shift on log axis).  
The *damping factor*,  $\zeta$ , ("zeta") determines the shape of the peak.




Peak frequency:

$$\omega_p = \omega_c \sqrt{1 - 2\zeta^2}$$

$\zeta \geq 0.71 \Rightarrow$  no peak,

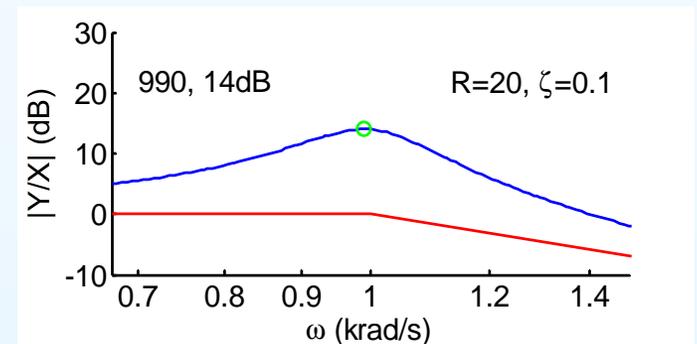$\zeta \geq 1 \Rightarrow$  can factorize



# Resonance Peak for LP filter


## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{\left(j\frac{\omega}{\omega_c}\right)^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$

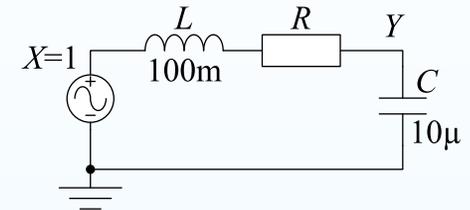$\frac{Y}{X}$  is a function of  $\frac{\omega}{\omega_c}$  so  $\omega_c$  just scales frequency axis (= shift on log axis).  
The *damping factor*,  $\zeta$ , ("zeta") determines the shape of the peak.




Peak frequency:

$$\omega_p = \omega_c \sqrt{1 - 2\zeta^2}$$

$\zeta \geq 0.71 \Rightarrow$  no peak,

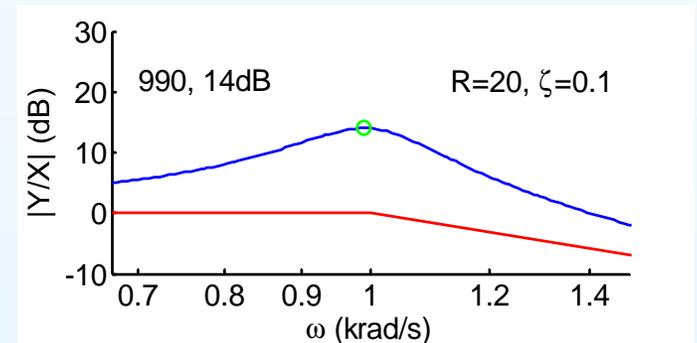$\zeta \geq 1 \Rightarrow$  can factorize



Gain relative to asymptote:

$$@ \omega_p: \frac{1}{2\zeta\sqrt{1-\zeta^2}}$$

$$@ \omega_c: \frac{1}{2\zeta} \approx Q$$

# Resonance Peak for LP filter


## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{\left(j\frac{\omega}{\omega_c}\right)^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$

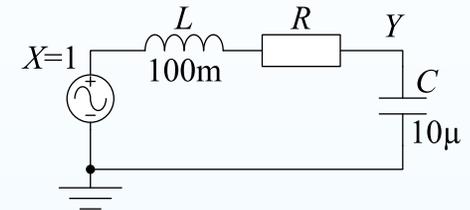$\frac{Y}{X}$  is a function of  $\frac{\omega}{\omega_c}$  so  $\omega_c$  just scales frequency axis (= shift on log axis).  
The *damping factor*,  $\zeta$ , ("zeta") determines the shape of the peak.



Peak frequency:

$$\omega_p = \omega_c \sqrt{1 - 2\zeta^2}$$


$\zeta \geq 0.71 \Rightarrow$  no peak,

$\zeta \geq 1 \Rightarrow$  can factorize

Gain relative to asymptote:

$$@ \omega_p: \frac{1}{2\zeta\sqrt{1-\zeta^2}}$$
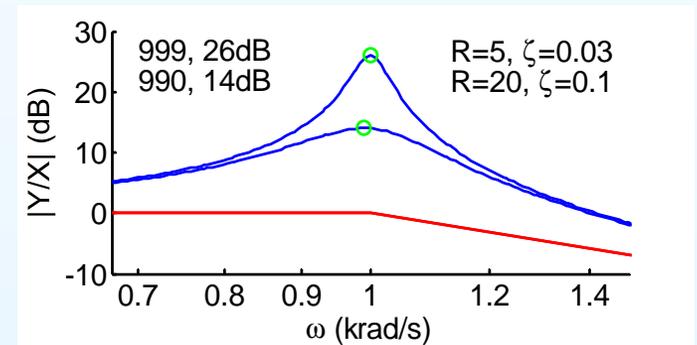
$$@ \omega_c: \frac{1}{2\zeta} \approx Q$$



# Resonance Peak for LP filter


## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{\left(j\frac{\omega}{\omega_c}\right)^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$

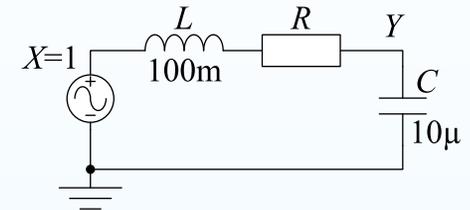$\frac{Y}{X}$  is a function of  $\frac{\omega}{\omega_c}$  so  $\omega_c$  just scales frequency axis (= shift on log axis).  
The *damping factor*,  $\zeta$ , ("zeta") determines the shape of the peak.




Peak frequency:

$$\omega_p = \omega_c \sqrt{1 - 2\zeta^2}$$

$\zeta \geq 0.71 \Rightarrow$  no peak,

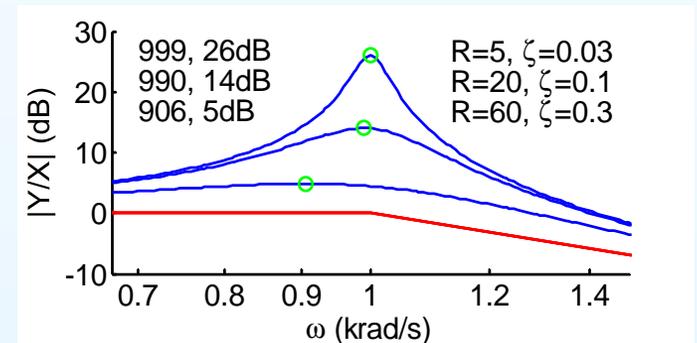$\zeta \geq 1 \Rightarrow$  can factorize



Gain relative to asymptote:

$$@ \omega_p: \frac{1}{2\zeta\sqrt{1-\zeta^2}}$$

$$@ \omega_c: \frac{1}{2\zeta} \approx Q$$

# Resonance Peak for LP filter


## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{\left(j\frac{\omega}{\omega_c}\right)^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$

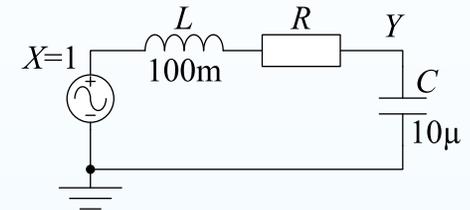$\frac{Y}{X}$  is a function of  $\frac{\omega}{\omega_c}$  so  $\omega_c$  just scales frequency axis (= shift on log axis).  
The *damping factor*,  $\zeta$ , ("zeta") determines the shape of the peak.




Peak frequency:

$$\omega_p = \omega_c \sqrt{1 - 2\zeta^2}$$

$\zeta \geq 0.5 \Rightarrow$  passes under corner,

$\zeta \geq 0.71 \Rightarrow$  no peak,

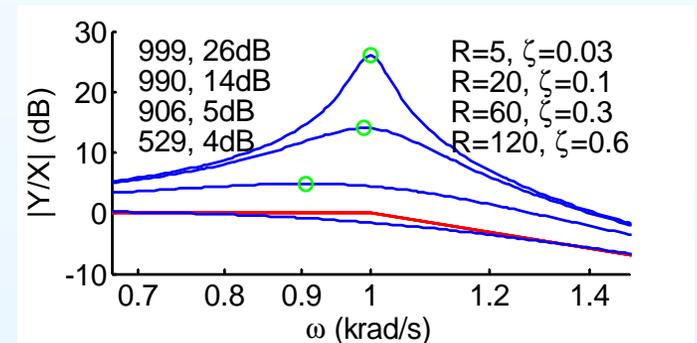$\zeta \geq 1 \Rightarrow$  can factorize



Gain relative to asymptote: @  $\omega_p$ :  $\frac{1}{2\zeta\sqrt{1-\zeta^2}}$  @  $\omega_c$ :  $\frac{1}{2\zeta} \approx Q$


# Resonance Peak for LP filter

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{\left(j\frac{\omega}{\omega_c}\right)^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$
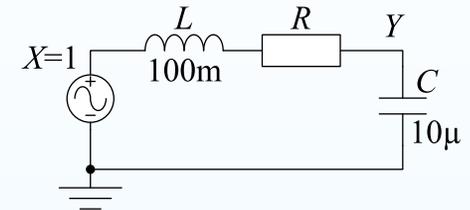
$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$



$\frac{Y}{X}$  is a function of  $\frac{\omega}{\omega_c}$  so  $\omega_c$  just scales frequency axis (= shift on log axis).  
The *damping factor*,  $\zeta$ , (“zeta”) determines the shape of the peak.


Peak frequency:

$$\omega_p = \omega_c \sqrt{1 - 2\zeta^2}$$

$\zeta \geq 0.5 \Rightarrow$  passes under corner,

$\zeta \geq 0.71 \Rightarrow$  no peak,

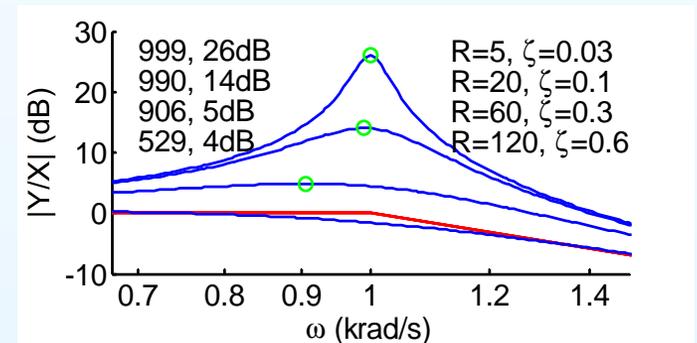$\zeta \geq 1 \Rightarrow$  can factorize



Gain relative to asymptote: @  $\omega_p$ :  $\frac{1}{2\zeta\sqrt{1-\zeta^2}}$  @  $\omega_c$ :  $\frac{1}{2\zeta} \approx Q$

Three frequencies:  $\omega_p$  = peak,  $\omega_c$  = asymptotes cross,  $\omega_r$  = real impedance  
For  $\zeta < 0.3$ ,  $\omega_p \approx \omega_c \approx \omega_r$ . All get called the resonant frequency.

# Resonance Peak for LP filter


## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

$$\frac{Y}{X} = \frac{1}{LC(j\omega)^2 + RCj\omega + 1} = \frac{1}{(j\frac{\omega}{\omega_c})^2 + 2\zeta j\frac{\omega}{\omega_c} + 1}$$

$$\omega_c = \sqrt{\frac{c}{a}} = 1000, \quad \zeta = \frac{b}{2a\omega_c} = \frac{b\omega_c}{2c} = \frac{R}{200}$$

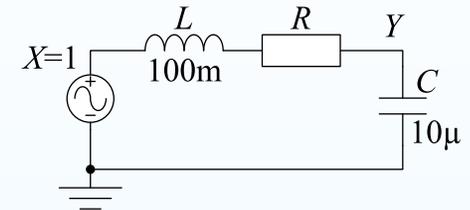$\frac{Y}{X}$  is a function of  $\frac{\omega}{\omega_c}$  so  $\omega_c$  just scales frequency axis (= shift on log axis).  
The *damping factor*,  $\zeta$ , ("zeta") determines the shape of the peak.




Peak frequency:

$$\omega_p = \omega_c \sqrt{1 - 2\zeta^2}$$

$\zeta \geq 0.5 \Rightarrow$  passes under corner,

$\zeta \geq 0.71 \Rightarrow$  no peak,

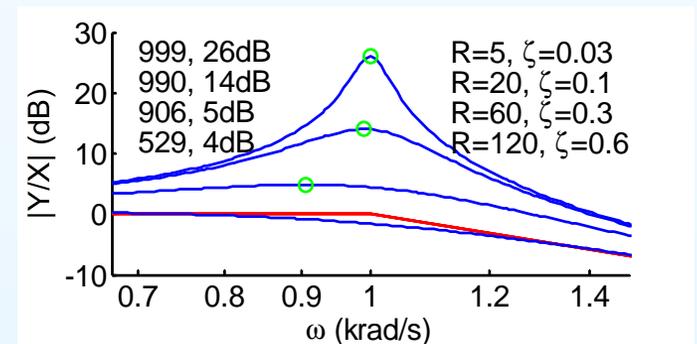$\zeta \geq 1 \Rightarrow$  can factorize



Gain relative to asymptote: @  $\omega_p$ :  $\frac{1}{2\zeta\sqrt{1-\zeta^2}}$  @  $\omega_c$ :  $\frac{1}{2\zeta} \approx Q$

Three frequencies:  $\omega_p$  = peak,  $\omega_c$  = asymptotes cross,  $\omega_r$  = real impedance  
For  $\zeta < 0.3$ ,  $\omega_p \approx \omega_c \approx \omega_r$ . All get called the resonant frequency.

The exact relationship between  $\omega_p$ ,  $\omega_c$  and  $\omega_r$  and the gain at these frequencies is affected by any other corner frequencies in the response.

# Summary

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

- Resonance is a peak in energy absorption

# Summary

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

- Resonance is a peak in energy absorption
  - Parallel or series circuit has a real impedance at  $\omega_r$ 
    - ▷ peak response may be at a slightly different frequency

# Summary

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

- **Resonance** is a peak in energy absorption
  - Parallel or series circuit has a **real impedance** at  $\omega_r$ 
    - ▷ peak response may be at a slightly different frequency
  - The quality factor,  $Q$ , of the resonance is

$$Q \triangleq \frac{\omega_0 \times \text{stored energy}}{\text{power in } R} \approx \frac{\omega_0}{3 \text{ dB bandwidth}} \approx \frac{1}{2\zeta}$$

# Summary

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

- **Resonance** is a peak in energy absorption
  - Parallel or series circuit has a **real impedance** at  $\omega_r$ 
    - ▷ peak response may be at a slightly different frequency
  - The quality factor,  $Q$ , of the resonance is

$$Q \triangleq \frac{\omega_0 \times \text{stored energy}}{\text{power in } R} \approx \frac{\omega_0}{3 \text{ dB bandwidth}} \approx \frac{1}{2\zeta}$$

- **3 dB bandwidth** is where power falls by  $\frac{1}{2}$  or voltage by  $\frac{1}{\sqrt{2}}$

# Summary

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

- **Resonance** is a peak in energy absorption
  - Parallel or series circuit has a **real impedance** at  $\omega_r$ 
    - ▷ peak response may be at a slightly different frequency
  - The quality factor,  $Q$ , of the resonance is
$$Q \triangleq \frac{\omega_0 \times \text{stored energy}}{\text{power in } R} \approx \frac{\omega_0}{3 \text{ dB bandwidth}} \approx \frac{1}{2\zeta}$$
  - **3 dB bandwidth** is where power falls by  $\frac{1}{2}$  or voltage by  $\frac{1}{\sqrt{2}}$
  - The stored energy sloshes between  $L$  and  $C$

# Summary

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

- **Resonance** is a peak in energy absorption
  - Parallel or series circuit has a **real impedance** at  $\omega_r$ 
    - ▷ peak response may be at a slightly different frequency
  - The quality factor,  $Q$ , of the resonance is

$$Q \triangleq \frac{\omega_0 \times \text{stored energy}}{\text{power in } R} \approx \frac{\omega_0}{3 \text{ dB bandwidth}} \approx \frac{1}{2\zeta}$$

- **3 dB bandwidth** is where power falls by  $\frac{1}{2}$  or voltage by  $\frac{1}{\sqrt{2}}$
- The stored energy sloshes between  $L$  and  $C$
- **Quadratic factor:**  $\left(\frac{j\omega}{\omega_c}\right)^2 + 2\zeta\left(\frac{j\omega}{\omega_c}\right) + 1$

# Summary

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

- **Resonance** is a peak in energy absorption
  - Parallel or series circuit has a **real impedance** at  $\omega_r$ 
    - ▷ peak response may be at a slightly different frequency
  - The quality factor,  $Q$ , of the resonance is

$$Q \triangleq \frac{\omega_0 \times \text{stored energy}}{\text{power in } R} \approx \frac{\omega_0}{3 \text{ dB bandwidth}} \approx \frac{1}{2\zeta}$$

- **3 dB bandwidth** is where power falls by  $\frac{1}{2}$  or voltage by  $\frac{1}{\sqrt{2}}$
- The stored energy sloshes between  $L$  and  $C$
- **Quadratic factor:**  $\left(\frac{j\omega}{\omega_c}\right)^2 + 2\zeta\left(\frac{j\omega}{\omega_c}\right) + 1$ 
  - $a(j\omega)^2 + b(j\omega) + c \Rightarrow \omega_c = \sqrt{\frac{c}{a}}$  and  $\zeta = \frac{b}{2a\omega_c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$

# Summary

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

- **Resonance** is a peak in energy absorption
  - Parallel or series circuit has a **real impedance** at  $\omega_r$ 
    - ▷ peak response may be at a slightly different frequency
  - The quality factor,  $Q$ , of the resonance is

$$Q \triangleq \frac{\omega_0 \times \text{stored energy}}{\text{power in } R} \approx \frac{\omega_0}{3 \text{ dB bandwidth}} \approx \frac{1}{2\zeta}$$

- **3 dB bandwidth** is where power falls by  $\frac{1}{2}$  or voltage by  $\frac{1}{\sqrt{2}}$
- The stored energy sloshes between  $L$  and  $C$
- **Quadratic factor:**  $\left(\frac{j\omega}{\omega_c}\right)^2 + 2\zeta\left(\frac{j\omega}{\omega_c}\right) + 1$ 
  - $a(j\omega)^2 + b(j\omega) + c \Rightarrow \omega_c = \sqrt{\frac{c}{a}}$  and  $\zeta = \frac{b}{2a\omega_c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$
  - $\pm 40$  dB/decade slope change in magnitude response

# Summary

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

- **Resonance** is a peak in energy absorption
  - Parallel or series circuit has a **real impedance** at  $\omega_r$ 
    - ▷ peak response may be at a slightly different frequency
  - The quality factor,  $Q$ , of the resonance is

$$Q \triangleq \frac{\omega_0 \times \text{stored energy}}{\text{power in } R} \approx \frac{\omega_0}{3 \text{ dB bandwidth}} \approx \frac{1}{2\zeta}$$

- **3 dB bandwidth** is where power falls by  $\frac{1}{2}$  or voltage by  $\frac{1}{\sqrt{2}}$
- The stored energy sloshes between  $L$  and  $C$

- **Quadratic factor:**  $\left(\frac{j\omega}{\omega_c}\right)^2 + 2\zeta\left(\frac{j\omega}{\omega_c}\right) + 1$

- $a(j\omega)^2 + b(j\omega) + c \Rightarrow \omega_c = \sqrt{\frac{c}{a}}$  and  $\zeta = \frac{b}{2a\omega_c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$
- $\pm 40$  dB/decade slope change in magnitude response
- phase changes rapidly by  $180^\circ$  over  $\omega = 10^{\mp\zeta}\omega_c$

# Summary

## 12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

- **Resonance** is a peak in energy absorption
  - Parallel or series circuit has a **real impedance** at  $\omega_r$ 
    - ▷ peak response may be at a slightly different frequency
  - The quality factor,  $Q$ , of the resonance is

$$Q \triangleq \frac{\omega_0 \times \text{stored energy}}{\text{power in } R} \approx \frac{\omega_0}{3 \text{ dB bandwidth}} \approx \frac{1}{2\zeta}$$

- **3 dB bandwidth** is where power falls by  $\frac{1}{2}$  or voltage by  $\frac{1}{\sqrt{2}}$
- The stored energy sloshes between  $L$  and  $C$

- **Quadratic factor:**  $\left(\frac{j\omega}{\omega_c}\right)^2 + 2\zeta\left(\frac{j\omega}{\omega_c}\right) + 1$

- $a(j\omega)^2 + b(j\omega) + c \Rightarrow \omega_c = \sqrt{\frac{c}{a}}$  and  $\zeta = \frac{b}{2a\omega_c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$
- $\pm 40$  dB/decade slope change in magnitude response
- phase changes rapidly by  $180^\circ$  over  $\omega = 10^{\mp\zeta}\omega_c$
- Gain error in asymptote is  $\frac{1}{2\zeta} \approx Q$  at  $\omega_0$

# Summary

12: Resonance

- Quadratic Factors +
- Damping Factor and Q
- Parallel RLC
- Behaviour at Resonance
- Away from resonance
- Bandwidth and Q
- Power and Energy at Resonance +
- Low Pass Filter
- Resonance Peak for LP filter
- Summary

- **Resonance** is a peak in energy absorption
  - Parallel or series circuit has a **real impedance** at  $\omega_r$ 
    - ▷ peak response may be at a slightly different frequency
  - The quality factor,  $Q$ , of the resonance is
 
$$Q \triangleq \frac{\omega_0 \times \text{stored energy}}{\text{power in } R} \approx \frac{\omega_0}{3 \text{ dB bandwidth}} \approx \frac{1}{2\zeta}$$
  - **3 dB bandwidth** is where power falls by  $\frac{1}{2}$  or voltage by  $\frac{1}{\sqrt{2}}$
  - The stored energy sloshes between  $L$  and  $C$

- **Quadratic factor:**  $\left(\frac{j\omega}{\omega_c}\right)^2 + 2\zeta\left(\frac{j\omega}{\omega_c}\right) + 1$ 
  - $a(j\omega)^2 + b(j\omega) + c \Rightarrow \omega_c = \sqrt{\frac{c}{a}}$  and  $\zeta = \frac{b}{2a\omega_c} = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}}$
  - $\pm 40$  dB/decade slope change in magnitude response
  - phase changes rapidly by  $180^\circ$  over  $\omega = 10^{\mp\zeta}\omega_c$
  - Gain error in asymptote is  $\frac{1}{2\zeta} \approx Q$  at  $\omega_0$

For further details see Hayt Ch 16 or Irwin Ch 12.