

▷ **13: Filters**

Filters

**1st Order Low-Pass
Filter**

**Low-Pass with Gain
Floor**

Opamp filter

Integrator

High Pass Filter

2nd order filter

Sallen-Key Filter

Twin-T Notch Filter

Conformal Filter

Transformations (A)

Conformal Filter

Transformations (B)

Summary

13: Filters

Filters

13: Filters

▷ Filters

1st Order Low-Pass Filter

Low-Pass with Gain Floor

Opamp filter

Integrator

High Pass Filter

2nd order filter

Sallen-Key Filter

Twin-T Notch Filter

Conformal Filter

Transformations (A)

Conformal Filter

Transformations (B)

Summary

A filter is a circuit whose gain varies with frequency. Often a filter aims to allow some frequencies to pass while blocking others.

- Radio/TV: a “tuning” filter blocks all frequencies except the wanted channel
- Loudspeaker: “crossover” filters send the right frequencies to different drive units
- Sampling: an “anti-aliasing filter” eliminates all frequencies above half the sampling rate
 - Phones: Sample rate = 8 kHz : filter eliminates frequencies above 3.4 kHz.
- Computer cables: filter eliminates interference



[Wikipedia]



1st Order Low-Pass Filter

13: Filters

Filters

1st Order

▷ Low-Pass Filter

Low-Pass with Gain Floor

Opamp filter

Integrator

High Pass Filter

2nd order filter

Sallen-Key Filter

Twin-T Notch Filter

Conformal Filter

Transformations (A)

Conformal Filter

Transformations (B)

Summary



$$\frac{Y}{X} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{j\omega RC + 1} = \frac{1}{\frac{j\omega}{p} + 1}$$

$$\text{Corner frequency: } p = \left| \frac{b}{a} \right| = \frac{1}{RC}$$

Asymptotes: 1 and $\frac{p}{j\omega}$

Very low ω : Capacitor = open circuit

Very high ω : Capacitor short circuit

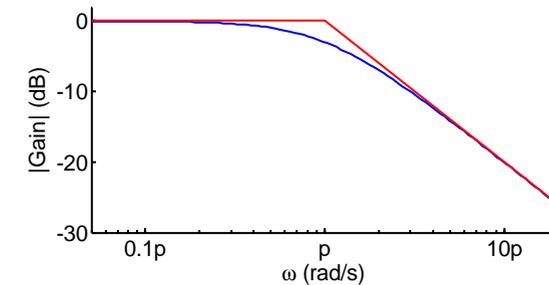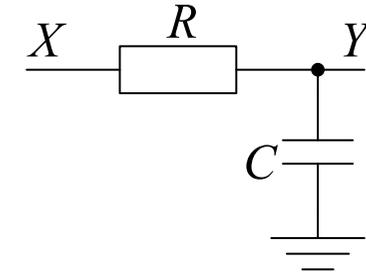

A *low-pass* filter because it allows low frequencies to pass but *attenuates* (makes smaller) high frequencies.

The *order* of a filter: highest power of $j\omega$ in the denominator.
Almost always equals the total number of L and/or C .

Low-Pass with Gain Floor

13: Filters

Filters

1st Order Low-Pass Filter

Low-Pass with Gain Floor

Opamp filter

Integrator

High Pass Filter

2nd order filter

Sallen-Key Filter

Twin-T Notch Filter

Conformal Filter

Transformations (A)

Conformal Filter

Transformations (B)

Summary

$$\frac{Y}{X} = \frac{R+1/j\omega C}{4R+1/j\omega C} = \frac{j\omega RC+1}{j\omega 4RC+1} = \frac{\frac{j\omega}{q}+1}{\frac{j\omega}{p}+1}$$

Corner frequencies: $p = \frac{1}{4RC}$, $q = \frac{1}{RC}$

Asymptotes: 1 and $\frac{1}{4}$

Very low ω :



Capacitor = open circuit

Resistor R unattached. Gain = 1

Very high ω :

Capacitor short circuit

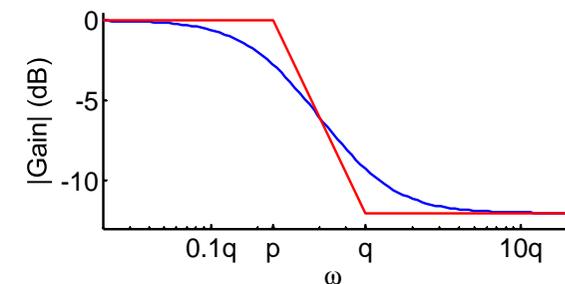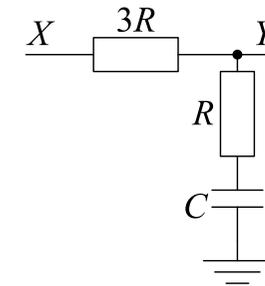Circuit is potential divider with gain $20 \log_{10} \frac{1}{4} = -12 \text{ dB}$.



Opamp filter

13: Filters

Filters

1st Order Low-Pass Filter

Low-Pass with Gain Floor

▷ Opamp filter

Integrator

High Pass Filter

2nd order filter

Sallen-Key Filter

Twin-T Notch Filter

Conformal Filter

Transformations (A)


Conformal Filter

Transformations (B)

Summary

Inverting amplifier so

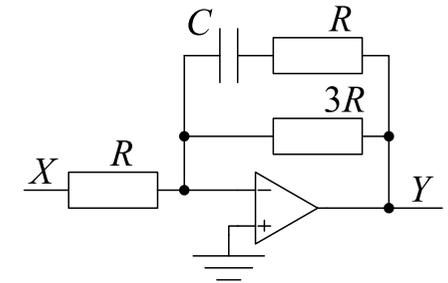
$$\begin{aligned} \frac{Y}{X} &= -\frac{3R \parallel (R + 1/j\omega C)}{R} = -\frac{3R(R + 1/j\omega C)}{R \times (3R + R + 1/j\omega C)} \\ &= -3 \times \frac{R + 1/j\omega C}{4R + 1/j\omega C} = -3 \times \frac{j\omega RC + 1}{j\omega 4RC + 1} \end{aligned}$$



Same transfer function as before except $\times -3 = +9.5$ dB.

Advantages of op-amp circuit:

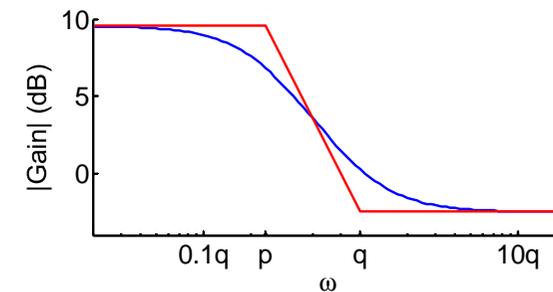1. Can have gain > 1 .
2. Low output impedance - loading does not affect filter
3. Resistive input impedance - does not vary with frequency



Integrator

13: Filters

Filters

1st Order Low-Pass Filter

Low-Pass with Gain Floor

Opamp filter

▷ Integrator

High Pass Filter

2nd order filter

Sallen-Key Filter

Twin-T Notch Filter

Conformal Filter

Transformations (A)

Conformal Filter

Transformations (B)

Summary

$$\frac{Y}{X} = -\frac{1/j\omega C}{R} = -\frac{1}{j\omega RC}$$

Capacitor: $i = C \frac{dv_C}{dt}$

$$i = \frac{x}{R} = -C \frac{dy}{dt}$$

$$\frac{dy}{dt} = \frac{-1}{RC} x$$

$$\int_0^t \frac{dy}{dt} dt = \frac{-1}{RC} \int_0^t x dt$$




$$y(t) = \frac{-1}{RC} \int_0^t x dt + y(0)$$

Note: if $x(t) = \cos \omega t$

$$\int \cos(\omega t) dt = \frac{1}{\omega} \sin(\omega t) \Rightarrow \text{gain} \propto \frac{1}{\omega}.$$

We can limit the LF gain to 20 dB:
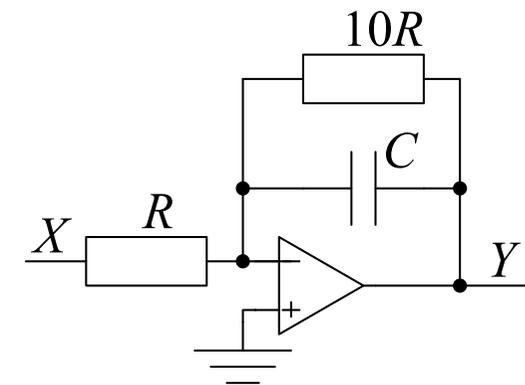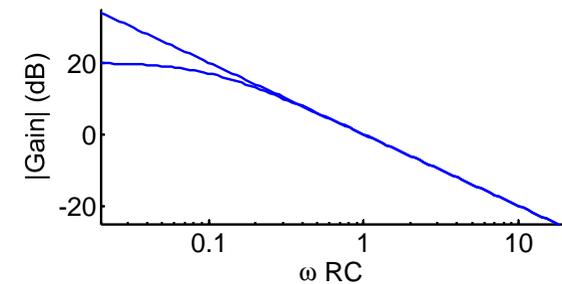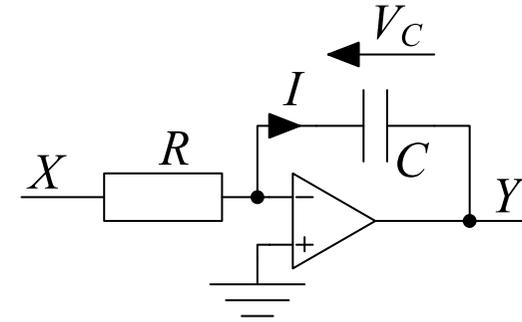
$$\begin{aligned} \frac{Y}{X} &= -\frac{10R \parallel 1/j\omega C}{R} = -\frac{10R \times 1/j\omega C}{R(10R + 1/j\omega C)} \\ &= -\frac{10}{j\omega 10RC + 1} \quad (\omega_c = \frac{0.1}{RC}) \end{aligned}$$



High Pass Filter

13: Filters

Filters

1st Order Low-Pass Filter

Low-Pass with Gain Floor

Opamp filter

Integrator

▷ High Pass Filter

2nd order filter

Sallen-Key Filter

Twin-T Notch Filter

Conformal Filter

Transformations (A)

Conformal Filter

Transformations (B)

Summary

$$\frac{Y}{X} = \frac{R}{R+1/j\omega C} = \frac{j\omega RC}{j\omega RC+1}$$

Corner Freq: $p = \frac{1}{RC}$



Asymptotes: $j\omega RC$ and 1

Very low ω : C open circuit: gain = 0

Very high ω : C short circuit: gain = 1

We can add an op-amp to give a low-impedance output. Or add gain:
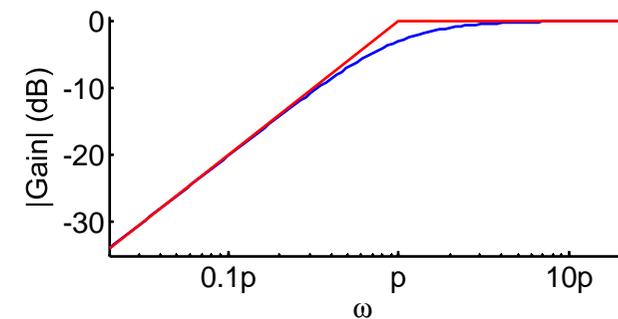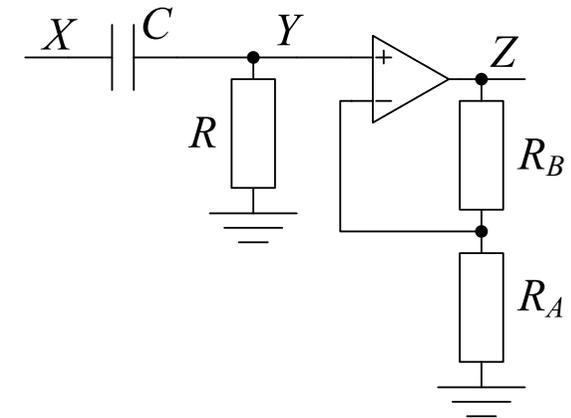
$$\frac{Z}{X} = \left(1 + \frac{R_B}{R_A}\right) \times \frac{j\omega RC}{j\omega RC+1}$$



2nd order filter

13: Filters

Filters

1st Order Low-Pass Filter

Low-Pass with Gain Floor

Opamp filter

Integrator

High Pass Filter

▷ 2nd order filter

Sallen-Key Filter

Twin-T Notch Filter

Conformal Filter


Transformations (A)

Conformal Filter

Transformations (B)

Summary
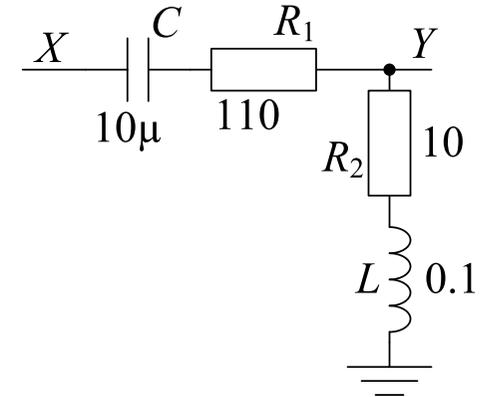
$$\begin{aligned} \frac{Y}{X} &= \frac{R_2 + j\omega L}{1/j\omega C + R_1 + R_2 + j\omega L} \\ &= \frac{LC(j\omega)^2 + R_2 C j\omega}{LC(j\omega)^2 + (R_1 + R_2)C j\omega + 1} \\ &= \frac{j\omega C(j\omega L + R_2)}{LC(j\omega)^2 + (R_1 + R_2)C j\omega + 1} \end{aligned}$$



Asymptotes: $j\omega R_2 C$ and 1

Corner frequencies:

$$+20 \text{ dB/dec at } p = \frac{R_2}{L} = 100 \text{ rad/s}$$

-40 dB/dec at


$$q = \sqrt{\frac{c}{a}} = \frac{1}{\sqrt{LC}} = 1000 \text{ rad/s}$$

Damping factor: $\zeta = \frac{b \operatorname{sgn}(a)}{\sqrt{4ac}} = \frac{qb}{2c} = \frac{q}{2} (R_1 + R_2) C = 0.6$.

Gain error at q is $\frac{1}{2\zeta} = Q = 0.83 = -1.6 \text{ dB}$ (+0.04 dB due to p)

Compare with 1st order:

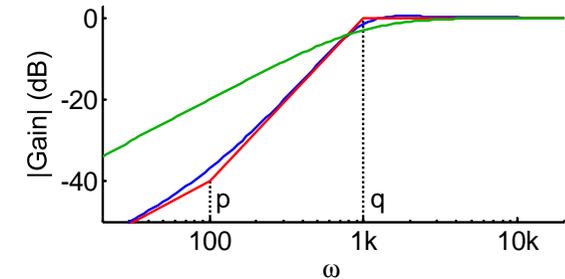2nd order filter attenuates more rapidly than a 1st order filter.



Sallen-Key Filter

13: Filters

Filters

1st Order Low-Pass Filter

Low-Pass with Gain Floor

Opamp filter

Integrator

High Pass Filter

2nd order filter

▷ Sallen-Key Filter

Twin-T Notch Filter



Conformal Filter

Transformations (A)

Conformal Filter

Transformations (B)

Summary

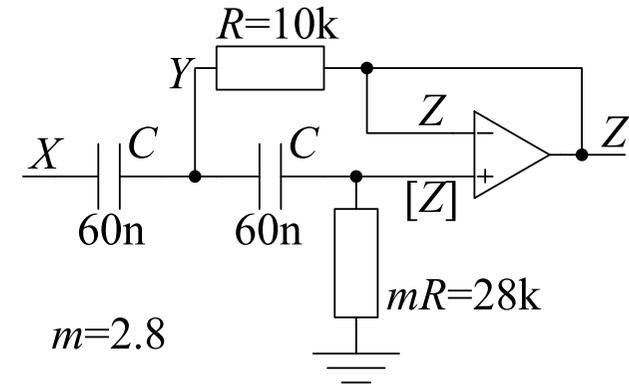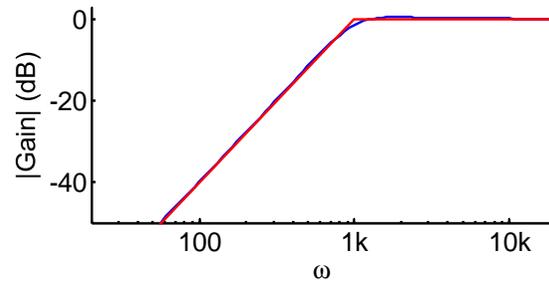

Asymptotes: $\left(\frac{j\omega}{p}\right)^2$ and 1

$$\text{KCL @ } Y: \frac{Y-X}{1/j\omega C} + \frac{Y-Z}{1/j\omega C} + \frac{Y-Z}{R} = 0 \quad [\text{assume } V_+ = V_- = Z]$$

$$\Rightarrow Y(1 + 2j\omega RC) - Z(1 + j\omega RC) = Xj\omega RC$$

$$\text{KCL @ } V_+: \frac{Z}{mR} + \frac{Z-Y}{1/j\omega C} = 0 \Rightarrow Z(1 + j\omega mRC) = Yj\omega mRC$$

$$\text{Sub } Y: Z \frac{(1+j\omega mRC)}{j\omega mRC} (1 + 2j\omega RC) - Z(1 + j\omega RC) = Xj\omega RC$$

$$\Rightarrow \frac{Z}{X} = \frac{m(j\omega RC)^2}{m(j\omega RC)^2 + 2j\omega RC + 1} = \frac{(j\omega/p)^2}{(j\omega/p)^2 + 2\zeta(j\omega/p) + 1}$$

$$\text{Corner freq: } p = \frac{1}{\sqrt{mRC}} = 996 \text{ rad/s}, \quad \zeta = \frac{1}{2Q} = pRC = \frac{1}{\sqrt{m}} = 0.6$$

Sallen-Key: 2nd order filter without inductors. Can easily have gain >1 .

Designing: Choose $m = \zeta^{-2}$; C any convenient value; $R = \frac{\zeta}{pC}$.

Twin-T Notch Filter

13: Filters

Filters

1st Order Low-Pass Filter

Low-Pass with Gain Floor

Opamp filter

Integrator

High Pass Filter

2nd order filter

Sallen-Key Filter

▷ Twin-T Notch Filter

Filter

Conformal Filter

Transformations (A)

Conformal Filter

Transformations (B)

Summary

After much algebra:

$$\frac{Z}{X} = \frac{(1+m)((2j\omega RC)^2 + 1)}{(2j\omega RC)^2 + 4(1-m)j\omega RC + 1}$$

$$= \frac{(1+m)((j\omega/p)^2 + 1)}{(j\omega/p)^2 + 2\zeta(j\omega/p) + 1}$$

$$p = \frac{1}{2RC} = 314, \quad \zeta = 1 - m = 0.1$$

Very low ω : C open circuit

Non-inverting amp, $\frac{Z}{X} = 1 + m$



Very high ω : C short circuit

Non-inverting amp, $\frac{Z}{X} = 1 + m$

At $\omega = p$, $\left(\frac{j\omega}{p}\right)^2 = -1$: numerator = zero resulting in infinite attenuation.

The 3 dB notch width is approximately $2\zeta p = 2(1 - m)p$.

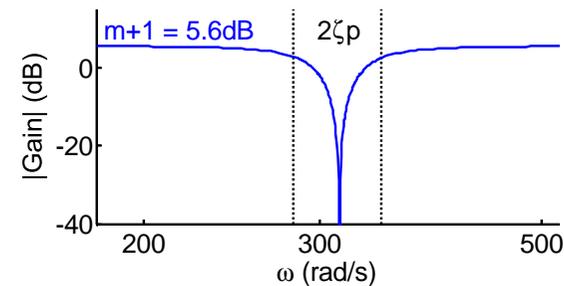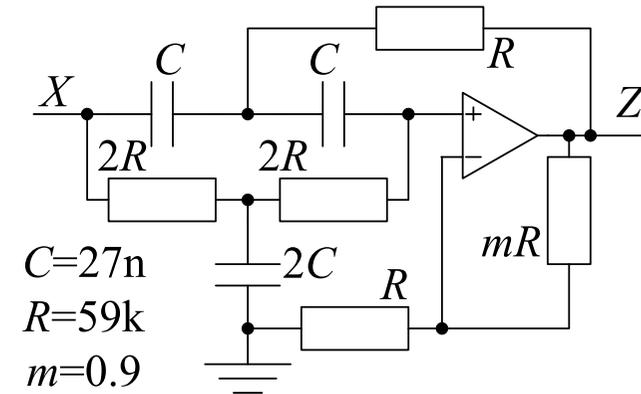Used to remove one specific frequency (e.g. mains hum @ 50 Hz)



Do not try to memorize this circuit



Conformal Filter Transformations (A)

- 13: Filters
- Filters
- 1st Order Low-Pass Filter
- Low-Pass with Gain Floor
- Opamp filter
- Integrator
- High Pass Filter
- 2nd order filter
- Sallen-Key Filter
- Twin-T Notch Filter
- Conformal Filter Transformations
- ▷ (A)
- Conformal Filter Transformations (B)
- Summary


A dimensionless gain, $\frac{V_Y}{V_X}$, can always be written using dimensionless impedance ratio terms: $\frac{Z_R}{Z_C} = j\omega RC$, $\frac{Z_L}{Z_R} = \frac{j\omega L}{R}$, $\frac{Z_L}{Z_C} = -\omega^2 LC$.

Impedance scaling:

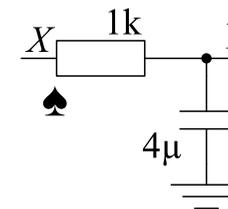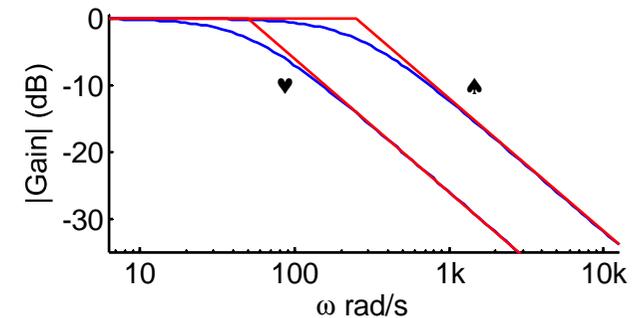
Scale all impedances by k :
 $R' = kR$, $C' = k^{-1}C$, $L' = kL$
 Impedance ratios are unchanged
 so graph stays the same.
 (k is arbitrary)



$k = 20$

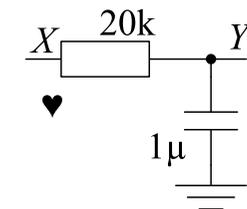

$k = 5$

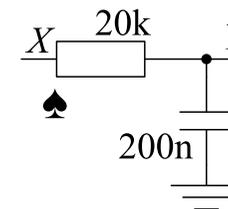

Frequency Shift:

Scale reactive components by k :
 $R' = R$, $C' = kC$, $L' = kL$
 $\Rightarrow Z'(k^{-1}\omega) \equiv Z(\omega)$
 Graph shifts left by a factor of k .

Must scale all reactive components in the circuit by the same factor.

Conformal Filter Transformations (B)

13: Filters

Filters

1st Order Low-Pass Filter

Low-Pass with Gain Floor

Opamp filter

Integrator

High Pass Filter

2nd order filter

Sallen-Key Filter

Twin-T Notch Filter

Conformal Filter

Transformations (A)

Conformal Filter Transformations

▷ (B)

Summary

Change LR circuit to RC:

$$\text{Change } R' = kL, C' = \frac{1}{kR}$$

$$\Rightarrow \frac{Z_{R'}}{Z_{C'}} = j\omega R' C' = \frac{j\omega L}{R} = \frac{Z_L}{Z_R}$$

Impedance ratios are unchanged at all ω so graph stays the same. (k is arbitrary)

Reflect frequency axis around ω_m :



$$\text{Change } R' = \frac{k}{\omega_m C}, C' = \frac{1}{\omega_m k R}$$

$$\Rightarrow \frac{Z_{R'}}{Z_{C'}} \left(\frac{\omega_m^2}{\omega} \right) = \left(\frac{Z_C}{Z_R}(\omega) \right)^*$$


(a) Magnitude graph flips

(b) Phase graph flips and negates since $\angle z^* = -\angle z$.

(k is arbitrary)

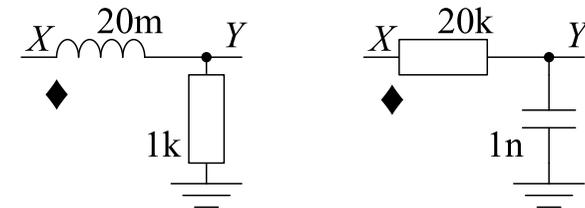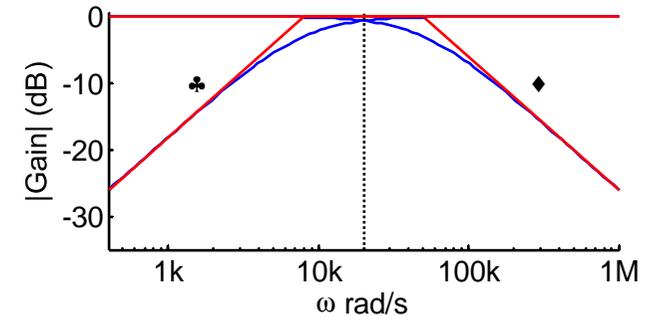

$$k = 10^6$$

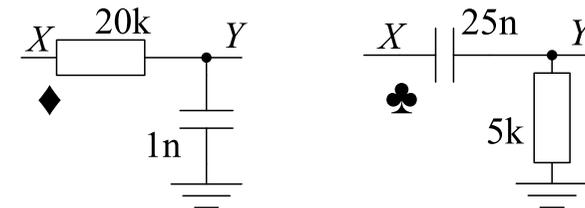

$$k = 0.1, \omega_m = 20 \text{ k}$$

Summary

13: Filters

Filters

1st Order Low-Pass Filter

Low-Pass with Gain Floor

Opamp filter

Integrator

High Pass Filter

2nd order filter

Sallen-Key Filter

Twin-T Notch Filter

Conformal Filter

Transformations (A)

Conformal Filter

Transformations (B)

▷ Summary

- The *order* of a filter is the highest power of $j\omega$ in the transfer function denominator.
- *Active filters* use op-amps and usually avoid the need for inductors.
 - Sallen-Key design for high-pass and low-pass.
 - Twin-T design for notch filter: gain = 0 at notch.
- For filters using R and C only:
 - *Scale R and C* : Substituting $R' = kR$ and $C' = pC$ scales frequency by $(pk)^{-1}$.
 - *Interchange R and C* : Substituting $R' = \frac{k}{\omega_0 C}$ and $C' = \frac{1}{k\omega_0 R}$ flips the frequency response around ω_0 ($\forall k$).
Changes a low-pass filter to high pass and vice-versa.

For further details see Hayt Ch 16 or Irwin Ch 12.