

▷ 14: Power in AC
Circuits

Average Power

Cosine Wave RMS

Power Factor +

Complex Power

Power in R, L, C

Tellegen's Theorem

Power Factor

Correction

Ideal Transformer

Transformer

Applications




Summary

14: Power in AC Circuits

Average Power

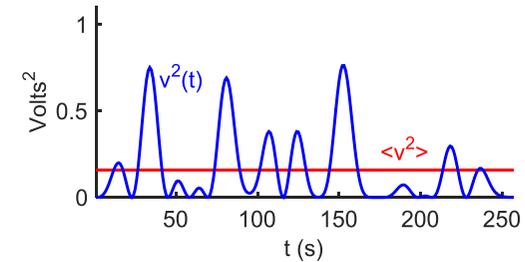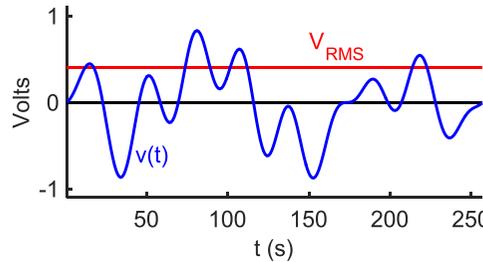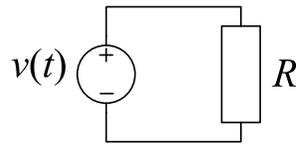14: Power in AC Circuits

- ▷ Average Power
- Cosine Wave RMS
- Power Factor +
- Complex Power
- Power in R, L, C
- Tellegen's Theorem
- Power Factor Correction
- Ideal Transformer
- Transformer Applications
- Summary



Instantaneous Power dissipated in R : $p(t) = \frac{v^2(t)}{R}$

Average Power dissipated in R :

$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{R} \times \frac{1}{T} \int_0^T v^2(t) dt = \frac{\langle v^2(t) \rangle}{R}$$

$\langle v^2(t) \rangle$ is the value of $v^2(t)$ averaged over time

We define the *RMS Voltage* (Root Mean Square): $V_{rms} \triangleq \sqrt{\langle v^2(t) \rangle}$

The average power dissipated in R is $P = \frac{\langle v^2(t) \rangle}{R} = \frac{(V_{rms})^2}{R}$
 V_{rms} is the DC voltage that would cause R to dissipate the same power.

We use *small letters* for time-varying voltages and *capital letters* for time-invariant values.

Cosine Wave RMS

14: Power in AC Circuits

Average Power

▷ Cosine Wave RMS

Power Factor +

Complex Power

Power in R, L, C

Tellegen's Theorem

Power Factor



Correction

Ideal Transformer

Transformer

Applications

Summary

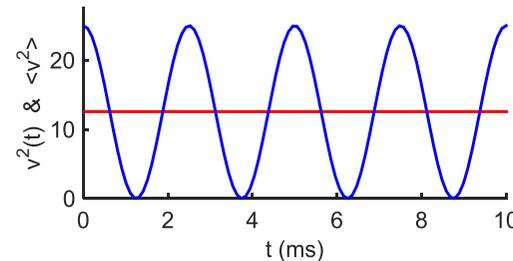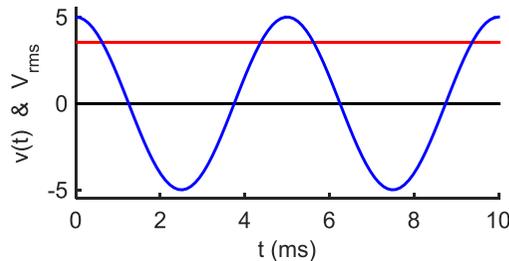

Cosine Wave: $v(t) = 5 \cos \omega t$. Amplitude is $V = 5$ V.

Squared Voltage: $v^2(t) = V^2 \cos^2 \omega t = V^2 \left(\frac{1}{2} + \frac{1}{2} \cos 2\omega t \right)$

Mean Square Voltage: $\langle v^2 \rangle = \frac{V^2}{2}$ since $\cos 2\omega t$ averages to zero.




RMS Voltage: $V_{rms} = \sqrt{\langle v^2 \rangle} = \frac{1}{\sqrt{2}} V = 3.54$ V = \tilde{V}

Note: Power engineers *always* use RMS voltages and currents exclusively and omit the “rms” subscript.

For example UK Mains voltage = 230 V rms = 325 V peak.

In this lecture course only, a \sim overbar means $\div \sqrt{2}$: thus $\tilde{V} = \frac{1}{\sqrt{2}} V$.

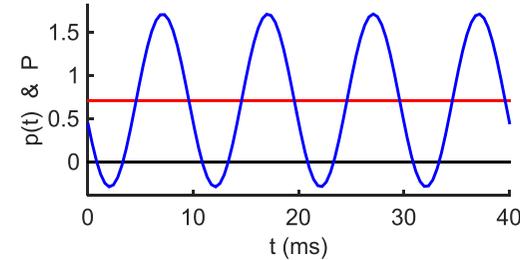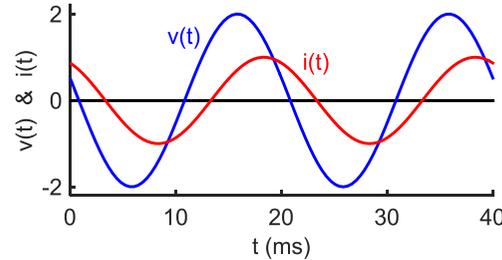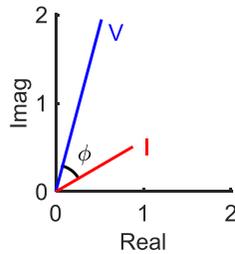
- 14: Power in AC Circuits
- Average Power
- Cosine Wave RMS
- ▷ Power Factor +
- Complex Power
- Power in R, L, C
- Tellegen's Theorem
- Power Factor Correction
- Ideal Transformer
- Transformer Applications
- Summary



Suppose voltage and current phasors are:

$$V = |V| e^{j\theta_V} \Leftrightarrow v(t) = |V| \cos(\omega t + \theta_V)$$

$$I = |I| e^{j\theta_I} \Leftrightarrow i(t) = |I| \cos(\omega t + \theta_I)$$

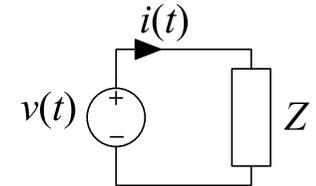

Power dissipated in load Z is

$$\begin{aligned} p(t) &= v(t)i(t) = |V| |I| \cos(\omega t + \theta_V) \cos(\omega t + \theta_I) \\ &= |V| |I| \left(\frac{1}{2} \cos(2\omega t + \theta_V + \theta_I) + \frac{1}{2} \cos(\theta_V - \theta_I) \right) \\ &= \frac{1}{2} |V| |I| \cos(\theta_V - \theta_I) + \frac{1}{2} |V| |I| \cos(2\omega t + \theta_V + \theta_I) \end{aligned}$$

Average power: $P = \frac{1}{2} |V| |I| \cos(\phi)$ where $\phi = \theta_V - \theta_I$

$$= \left| \tilde{V} \right| \left| \tilde{I} \right| \cos(\phi) \quad \cos \phi \text{ is the } \textit{power factor}$$

$\phi > 0 \Leftrightarrow$ a *lagging power factor* (normal case: Current lags Voltage)

$\phi < 0 \Leftrightarrow$ a *leading power factor* (rare case: Current leads Voltage)

[Multiplying Phasors]

From the previous slide, if the phasor voltage and current are $V = |V|e^{j\theta_V}$ and $I = |I|e^{j\theta_I}$, then the corresponding waveforms are $v(t) = |V| \cos(\omega t + \theta_V)$ and $i(t) = |I| \cos(\omega t + \theta_I)$. When you multiply these two waveforms together you get $p(t) = \frac{1}{2}|V||I| \cos(\theta_V - \theta_I) + \frac{1}{2}|V||I| \cos(2\omega t + \theta_V + \theta_I)$. This product contains two components: a constant, or DC, term that doesn't involve t and a second term that is a cosine wave of frequency 2ω .

The time-average of the second term is zero (because a cosine wave of any non-zero frequency goes symmetrically positive and negative and so averages to zero) and so the average power is just equal to the first term: $\frac{1}{2}|V||I| \cos(\theta_V - \theta_I)$. It is easy to see that $V \times I^* = |V|e^{j\theta_V} \times |I|e^{-j\theta_I} = |V||I|e^{j(\theta_V - \theta_I)} = |V||I| \cos(\theta_V - \theta_I) + j|V||I| \sin(\theta_V - \theta_I)$ and so the average power is the real part of $\frac{1}{2}V \times I^*$.

The second term is a cosine wave at a frequency of 2ω and so it is possible to represent this waveform, $\frac{1}{2}|V||I| \cos(2\omega t + \theta_V + \theta_I)$, as a phasor whose value is $\frac{1}{2}V \times I = \frac{1}{2}|V||I|e^{j(\theta_V + \theta_I)}$.

So to sum up, if you multiply together the two sinusoidal waveforms corresponding to phasors V and I , you get two components: (a) a DC component of value $\Re\left(\frac{1}{2}V \times I^*\right)$ and (b) a sinusoidal component of twice the frequency which corresponds to the phasor $\frac{1}{2}V \times I$.

Complex Power

14: Power in AC Circuits

Average Power

Cosine Wave RMS

Power Factor +

▷ Complex Power

Power in R, L, C

Tellegen's Theorem

Power Factor

Correction

Ideal Transformer

Transformer



Applications

Summary

$$\text{If } \tilde{V} = \frac{1}{\sqrt{2}} |V| e^{j\theta_V} \text{ and } \tilde{I} = \frac{1}{\sqrt{2}} |I| e^{j\theta_I}$$

The **complex power** absorbed by Z is $S \triangleq \tilde{V} \times \tilde{I}^*$ where * means complex conjugate.

$$\begin{aligned} \tilde{V} \times \tilde{I}^* &= |\tilde{V}| e^{j\theta_V} \times |\tilde{I}| e^{-j\theta_I} = |\tilde{V}| |\tilde{I}| e^{j(\theta_V - \theta_I)} \\ &= |\tilde{V}| |\tilde{I}| e^{j\phi} = |\tilde{V}| |\tilde{I}| \cos \phi + j |\tilde{V}| |\tilde{I}| \sin \phi \\ &= P + jQ \end{aligned}$$

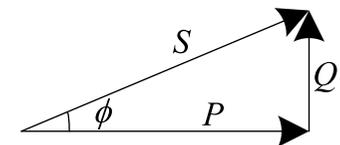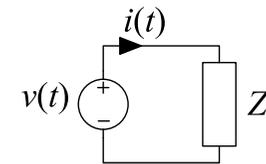

Complex Power: $S \triangleq \tilde{V} \tilde{I}^* = P + jQ$ measured in **Volt-Amps (VA)**

Apparent Power: $|S| \triangleq |\tilde{V}| |\tilde{I}|$ measured in **Volt-Amps (VA)**

Average Power: $P \triangleq \Re(S)$ measured in **Watts (W)**

Reactive Power: $Q \triangleq \Im(S)$ Measured in **Volt-Amps Reactive (VAR)**

Power Factor: $\cos \phi \triangleq \cos(\angle \tilde{V} - \angle \tilde{I}) = \frac{P}{|S|}$

Machines and transformers have capacity limits and power losses that are independent of $\cos \phi$; their ratings are always given in **apparent power**.

Power Company: Costs \propto apparent power, Revenue \propto average power.

Power in R, L, C

14: Power in AC Circuits

Average Power

Cosine Wave RMS

Power Factor +

Complex Power

▷ Power in R, L, C

Tellegen's Theorem

Power Factor

Correction

Ideal Transformer

Transformer

Applications


Summary

For any impedance, Z , complex power absorbed: $S = \tilde{V}\tilde{I}^* = P + jQ$

Using (a) $\tilde{V} = \tilde{I}Z$ (b) $\tilde{I} \times \tilde{I}^* = |\tilde{I}|^2$ we get $S = |\tilde{I}|^2 Z = \frac{|\tilde{V}|^2}{Z^*}$


Resistor: $S = |\tilde{I}|^2 R = \frac{|\tilde{V}|^2}{R} \quad \phi = 0$

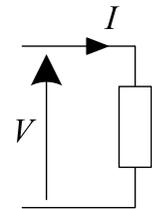Absorbs average power, **no VARs** ($Q = 0$)




Inductor: $S = j |\tilde{I}|^2 \omega L = j \frac{|\tilde{V}|^2}{\omega L} \quad \phi = +90^\circ$

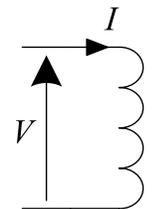No average power, **Absorbs VARs** ($Q > 0$)



Capacitor: $S = -j \frac{|\tilde{I}|^2}{\omega C} = -j |\tilde{V}|^2 \omega C \quad \phi = -90^\circ$

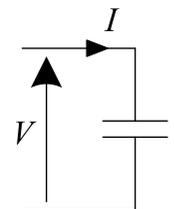No average power, **Generates VARs** ($Q < 0$)



VARs are **generated** by capacitors and **absorbed** by inductors

The phase, ϕ , of the absorbed power, S , equals the phase of Z

Tellegen's Theorem

- 14: Power in AC Circuits
- Average Power
- Cosine Wave RMS
- Power Factor +
- Complex Power
- Power in R, L, C
- Tellegen's
- ▷ Theorem
- Power Factor
- Correction
- Ideal Transformer
- Transformer
- Applications
- Summary

Tellegen's Theorem: The complex power, S , dissipated in any circuit's components sums to zero.

x_n = voltage at node n
 V_b, I_b = voltage/current in branch b
 (obeying passive sign convention)

$$a_{bn} \triangleq \begin{cases} -1 & \text{if } V_b \text{ starts from node } n \\ +1 & \text{if } V_b \text{ ends at node } n \\ 0 & \text{else} \end{cases}$$

e.g. branch 4 goes from 2 to 3 $\Rightarrow a_{4*} = [0, -1, 1]$


Branch voltages: $V_b = \sum_n a_{bn} x_n$ (e.g. $V_4 = x_3 - x_2$)

KCL @ node n : $\sum_b a_{bn} I_b = 0 \Rightarrow \sum_b a_{bn} I_b^* = 0$

Tellegen: $\sum_b V_b I_b^* = \sum_b \sum_n a_{bn} x_n I_b^*$

$$= \sum_n \sum_b a_{bn} I_b^* x_n = \sum_n x_n \sum_b a_{bn} I_b^* = \sum_n x_n \times 0$$

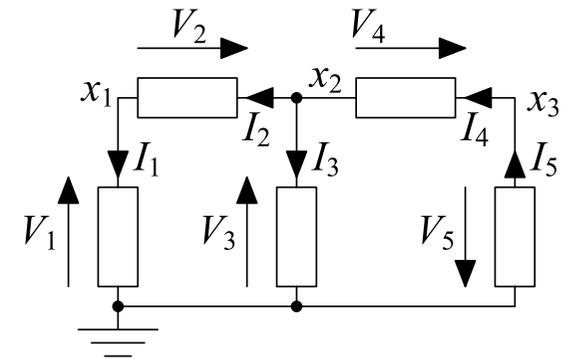Note: $\sum_b S_b = 0 \Rightarrow \sum_b P_b = 0$ and also $\sum_b Q_b = 0$.



	nodes (n)		
a_{bn}	1	2	3
1	1	0	0
2	-1	1	0
3	0	1	0
4	0	-1	1
5	0	0	-1

Power Factor Correction


- 14: Power in AC Circuits
- Average Power
- Cosine Wave RMS
- Power Factor +
- Complex Power
- Power in R, L, C
- Tellegen's Theorem
- Power Factor
- ▷ Correction
- Ideal Transformer
- Transformer Applications
- Summary

$\tilde{V} = 230$. Motor modelled as $5 \parallel 7j \Omega$.

$$\tilde{I} = \frac{\tilde{V}}{R} + \frac{\tilde{V}}{Z_L} = 46 - j32.9 \text{ A} = 56.5 \angle -36^\circ$$

$$S = \tilde{V} \tilde{I}^* = 10.6 + j7.6 \text{ kVA} = 13 \angle 36^\circ \text{ kVA}$$


$$\cos \phi = \frac{P}{|S|} = \cos 36^\circ = 0.81$$

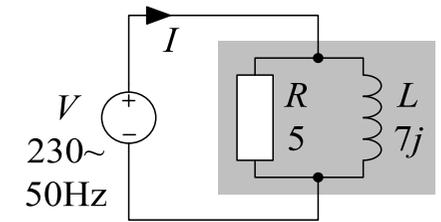

Add parallel capacitor of $300 \mu\text{F}$:

$$Z_C = \frac{1}{j\omega C} = -10.6j \Omega \Rightarrow \tilde{I}_C = 21.7j \text{ A}$$

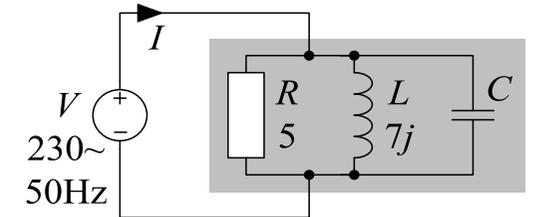
$$\tilde{I} = 46 - j11.2 \text{ A} = 47 \angle -14^\circ \text{ A}$$



$$S_C = \tilde{V} \tilde{I}_C^* = -j5 \text{ kVA}$$

$$S = \tilde{V} \tilde{I}^* = 10.6 + j2.6 \text{ kVA} = 10.9 \angle 14^\circ \text{ kVA}$$

$$\cos \phi = \frac{P}{|S|} = \cos 14^\circ = 0.97$$

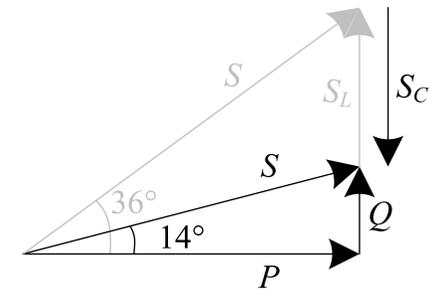

Average power to motor, P , is 10.6 kW in both cases.

$|\tilde{I}|$, reduced from 56.5 \searrow 47 A (-16%) \Rightarrow lower losses.

Effect of C : VARs = 7.6 \searrow 2.6 kVAR, power factor = 0.81 \nearrow 0.97.

Ideal Transformer

- 14: Power in AC Circuits
- Average Power
- Cosine Wave RMS
- Power Factor +
- Complex Power
- Power in R, L, C
- Tellegen's Theorem
- Power Factor Correction
- ▷ Ideal Transformer
- Transformer Applications
- Summary

A transformer has ≥ 2 windings on the same magnetic core.

Ampère's law: $\sum N_r I_r = \frac{l\Phi}{\mu A}$; **Faraday's law:** $\frac{V_r}{N_r} = \frac{d\Phi}{dt}$.

$N_1 : N_2 + N_3$ shows the turns ratio between the windings.

The • indicates the voltage polarity of each winding.

Since Φ is the same for all windings, $\frac{V_1}{N_1} = \frac{V_2}{N_2} = \frac{V_3}{N_3}$.

Assume $\mu \rightarrow \infty \Rightarrow N_1 I_1 + N_2 I_2 + N_3 I_3 = 0$

These two equations allow you to solve circuits and also imply that $\sum S_i = 0$.




Special Case:

For a 2-winding transformer this simplifies to

$V_2 = \frac{N_2}{N_1} V_1$ and $I_L = -I_2 = \frac{N_1}{N_2} I_1$

Hence $\frac{V_1}{I_1} = \left(\frac{N_1}{N_2}\right)^2 \frac{V_2}{I_L} = \left(\frac{N_1}{N_2}\right)^2 Z$

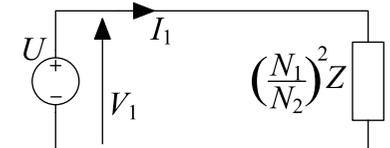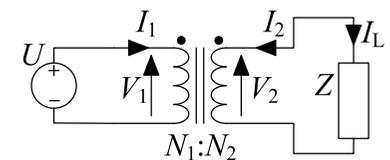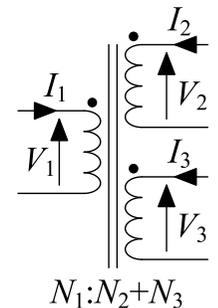Equivalent to a *reflected impedance* of $\left(\frac{N_1}{N_2}\right)^2 Z$



Transformer Applications

14: Power in AC Circuits

Average Power

Cosine Wave RMS

Power Factor +

Complex Power

Power in R, L, C

Tellegen's Theorem

Power Factor

Correction

Ideal Transformer

Transformer

▷ Applications

Summary

Power Transmission

Suppose a power transmission cable has 1Ω resistance.

$$100 \text{ kVA@ } 1 \text{ kV} = 100 \text{ A} \Rightarrow \tilde{I}^2 R = 10 \text{ kW losses.}$$

$$100 \text{ kVA@ } 100 \text{ kV} = 1 \text{ A} \Rightarrow \tilde{I}^2 R = 1 \text{ W losses.}$$

Voltage Conversion

Electronic equipment requires $\leq 20 \text{ V}$ but mains voltage is $240 \text{ V} \sim$.

Interference protection

Microphone on long cable is susceptible to interference from nearby mains cables. An $N : 1$ transformer reduces the microphone voltage by N but reduces interference by N^2 .

Isolation

There is no electrical connection between the windings of a transformer so circuitry (or people) on one side will not be endangered by a failure that results in high voltages on the other side.

Summary

14: Power in AC Circuits

Average Power

Cosine Wave RMS

Power Factor +

Complex Power

Power in R, L, C

Tellegen's Theorem

Power Factor

Correction

Ideal Transformer

Transformer

Applications

▷ Summary

- **Complex Power:** $S = \tilde{V}\tilde{I}^* = P + jQ$ where $\tilde{V} = V_{rms} = \frac{1}{\sqrt{2}}V$.
 - For an impedance Z : $S = |\tilde{I}|^2 Z = \frac{|\tilde{V}|^2}{Z^*}$
 - **Apparent Power:** $|S| = |\tilde{V}| |\tilde{I}|$ used for machine ratings.
 - **Average Power:** $P = \Re(S) = |\tilde{V}| |\tilde{I}| \cos \phi$ (in **Watts**)
 - **Reactive Power:** $Q = \Im(S) = |\tilde{V}| |\tilde{I}| \sin \phi$ (in **VARs**)
 - Power engineers always use \tilde{V} and \tilde{I} and omit the \sim .
- **Tellegen:** In any circuit $\sum_b S_b = 0 \Rightarrow \sum_b P_b = \sum_b Q_b = 0$
- **Power Factor Correction:** add parallel C to generate extra VARs
- **Ideal Transformer:** $V_i \propto N_i$ and $\sum N_i I_i = 0$ (implies $\sum S_i = 0$)

For further details see Hayt Ch 11 or Irwin Ch 9.