

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary


15: Transients (A)

Differential Equation

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

To find $y(t)$:

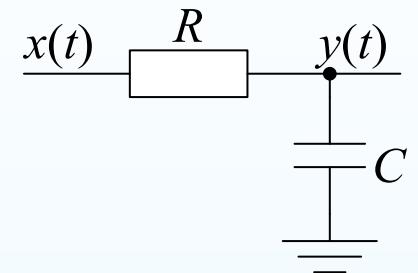


Differential Equation

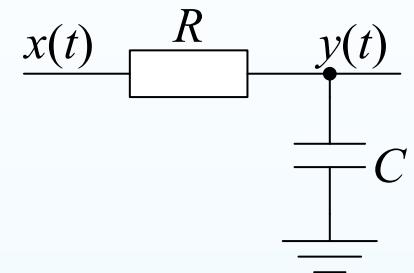15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

To find $y(t)$:
 $x(t)$ constant: Nodal analysis



15: Transients (A)


- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Differential Equation

To find $y(t)$:

$x(t)$ constant: Nodal analysis

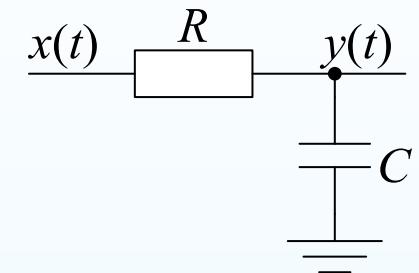$x(t)$ sinusoidal: Phasors + nodal analysis



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary


Differential Equation

To find $y(t)$:

$x(t)$ constant: Nodal analysis

$x(t)$ sinusoidal: Phasors + nodal analysis

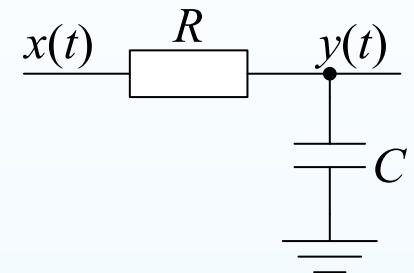$x(t)$ anything else: Differential equation



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Differential Equation


To find $y(t)$:

$x(t)$ constant: Nodal analysis

$x(t)$ sinusoidal: Phasors + nodal analysis

$x(t)$ anything else: Differential equation

$$i(t) = C \frac{dy}{dt}$$

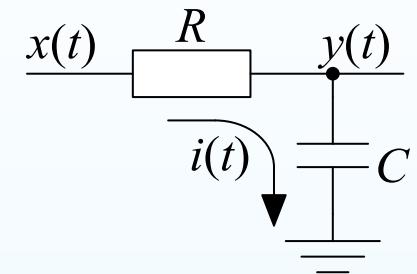

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Differential Equation


To find $y(t)$:

$x(t)$ constant: Nodal analysis

$x(t)$ sinusoidal: Phasors + nodal analysis

$x(t)$ anything else: Differential equation
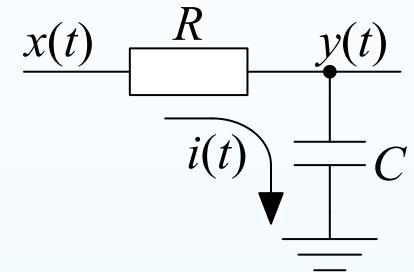
$$i(t) = C \frac{dy}{dt} = \frac{x-y}{R}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Differential Equation


To find $y(t)$:

$x(t)$ constant: Nodal analysis

$x(t)$ sinusoidal: Phasors + nodal analysis

$x(t)$ anything else: Differential equation
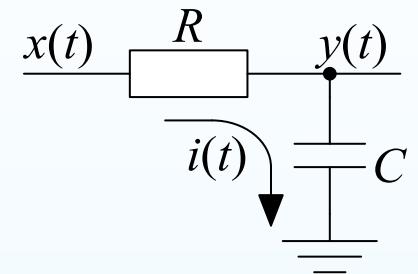
$$i(t) = C \frac{dy}{dt} = \frac{x-y}{R} \Rightarrow RC \frac{dy}{dt} + y = x$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Differential Equation

To find $y(t)$:


$x(t)$ constant: Nodal analysis

$x(t)$ sinusoidal: Phasors + nodal analysis

$x(t)$ anything else: Differential equation

$$i(t) = C \frac{dy}{dt} = \frac{x-y}{R} \Rightarrow RC \frac{dy}{dt} + y = x$$

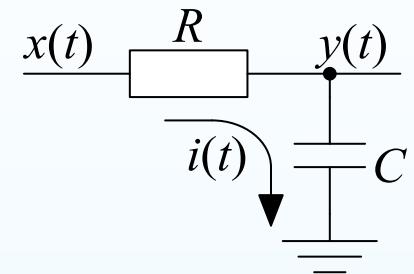General Solution: Particular Integral + Complementary Function



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Differential Equation

To find $y(t)$:

$x(t)$ constant: Nodal analysis


$x(t)$ sinusoidal: Phasors + nodal analysis

$x(t)$ anything else: Differential equation

$$i(t) = C \frac{dy}{dt} = \frac{x-y}{R} \Rightarrow RC \frac{dy}{dt} + y = x$$

General Solution: Particular Integral + Complementary Function

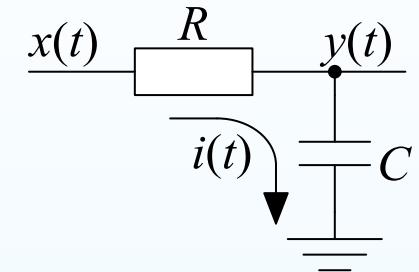Particular Integral: Any solution to $RC \frac{dy}{dt} + y = x$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Differential Equation

To find $y(t)$:

$x(t)$ constant: Nodal analysis

$x(t)$ sinusoidal: Phasors + nodal analysis


$x(t)$ anything else: Differential equation

$$i(t) = C \frac{dy}{dt} = \frac{x-y}{R} \Rightarrow RC \frac{dy}{dt} + y = x$$

General Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $RC \frac{dy}{dt} + y = x$

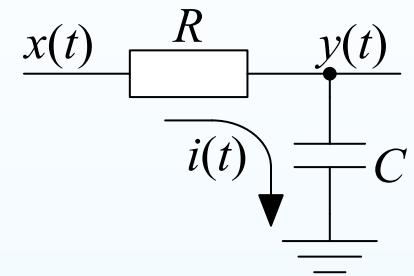If $x(t)$ is piecewise constant or sinusoidal, we will use nodal/phasor analysis to find the *steady state solution* for $y(t)$.



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Differential Equation

To find $y(t)$:

$x(t)$ constant: Nodal analysis

$x(t)$ sinusoidal: Phasors + nodal analysis

$x(t)$ anything else: Differential equation


$$i(t) = C \frac{dy}{dt} = \frac{x-y}{R} \Rightarrow RC \frac{dy}{dt} + y = x$$

General Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $RC \frac{dy}{dt} + y = x$

If $x(t)$ is piecewise constant or sinusoidal, we will use nodal/phasor analysis to find the *steady state solution* for $y(t)$.

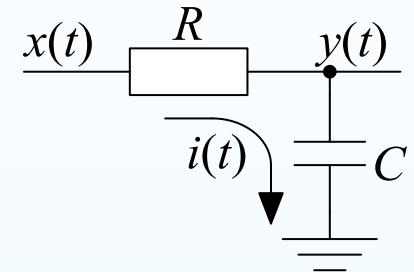Complementary Function: Solution to $RC \frac{dy}{dt} + y = 0$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Differential Equation

To find $y(t)$:

$x(t)$ constant: Nodal analysis

$x(t)$ sinusoidal: Phasors + nodal analysis

$x(t)$ anything else: Differential equation

$$i(t) = C \frac{dy}{dt} = \frac{x-y}{R} \Rightarrow RC \frac{dy}{dt} + y = x$$


General Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $RC \frac{dy}{dt} + y = x$

If $x(t)$ is piecewise constant or sinusoidal, we will use nodal/phasor analysis to find the *steady state solution* for $y(t)$.

Complementary Function: Solution to $RC \frac{dy}{dt} + y = 0$

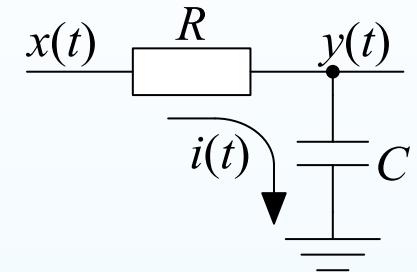Does not depend on $x(t)$, only on the circuit.



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Differential Equation

To find $y(t)$:

$x(t)$ constant: Nodal analysis

$x(t)$ sinusoidal: Phasors + nodal analysis

$x(t)$ anything else: Differential equation

$$i(t) = C \frac{dy}{dt} = \frac{x-y}{R} \Rightarrow RC \frac{dy}{dt} + y = x$$

General Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $RC \frac{dy}{dt} + y = x$


If $x(t)$ is piecewise constant or sinusoidal, we will use nodal/phasor analysis to find the *steady state solution* for $y(t)$.

Complementary Function: Solution to $RC \frac{dy}{dt} + y = 0$

Does not depend on $x(t)$, only on the circuit.

Solution is $y(t) = Ae^{-t/\tau}$

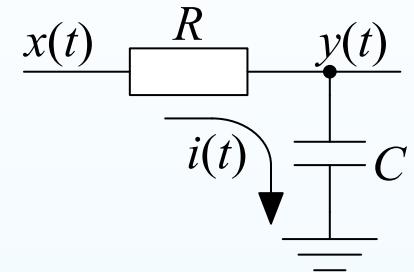where $\tau = RC$ is the *time constant* of the circuit.



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Differential Equation

To find $y(t)$:

$x(t)$ constant: Nodal analysis

$x(t)$ sinusoidal: Phasors + nodal analysis

$x(t)$ anything else: Differential equation

$$i(t) = C \frac{dy}{dt} = \frac{x-y}{R} \Rightarrow RC \frac{dy}{dt} + y = x$$

General Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $RC \frac{dy}{dt} + y = x$

If $x(t)$ is piecewise constant or sinusoidal, we will use nodal/phasor analysis to find the **steady state solution** for $y(t)$.


Complementary Function: Solution to $RC \frac{dy}{dt} + y = 0$

Does not depend on $x(t)$, only on the circuit.

Solution is $y(t) = Ae^{-t/\tau}$

where $\tau = RC$ is the **time constant** of the circuit.

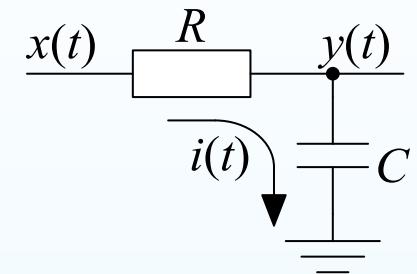The amplitude, A , is determined by the **initial conditions** at $t = 0$.




Piecewise steady state inputs

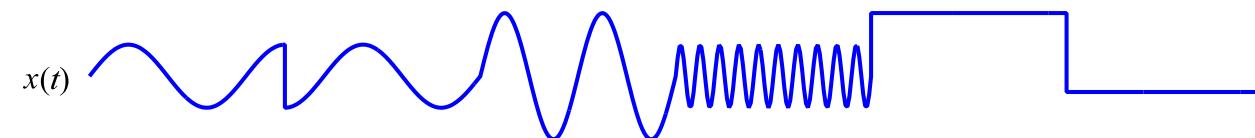15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

We will consider input signals that are sinusoidal or constant for a particular time interval and then suddenly change in amplitude, phase or frequency.



Piecewise steady state inputs



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

We will consider input signals that are sinusoidal or constant for a particular time interval and then suddenly change in amplitude, phase or frequency.

Output is the sum of the steady state and a transient:

$$y(t) = y_{SS}(t) + y_{Tr}(t)$$

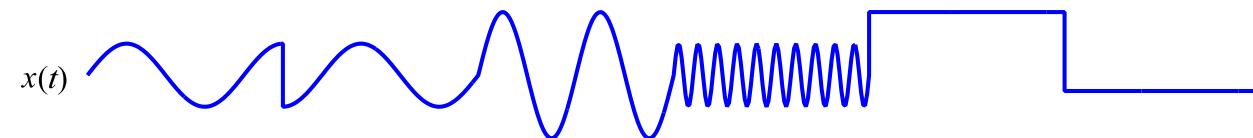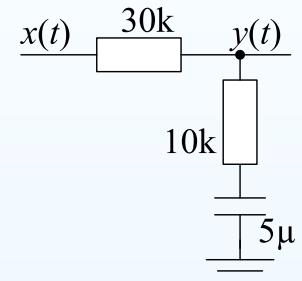

Piecewise steady state inputs

15: Transients (A)



- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

We will consider input signals that are sinusoidal or constant for a particular time interval and then suddenly change in amplitude, phase or frequency.

Output is the sum of the steady state and a transient:

$$y(t) = y_{SS}(t) + y_{Tr}(t)$$

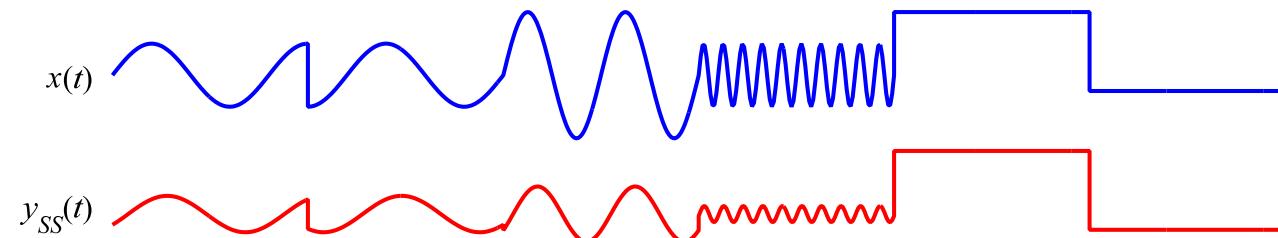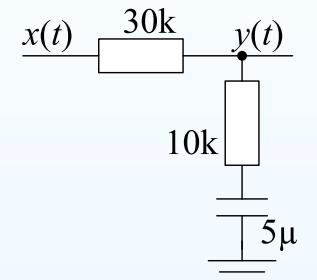Steady state, $y_{SS}(t)$, is the same frequency as the input; use phasors + nodal analysis.



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Piecewise steady state inputs



We will consider input signals that are sinusoidal or constant for a particular time interval and then suddenly change in amplitude, phase or frequency.

Output is the sum of the steady state and a transient:

$$y(t) = y_{SS}(t) + y_{Tr}(t)$$

Steady state, $y_{SS}(t)$, is the same frequency as the input; use phasors + nodal analysis.

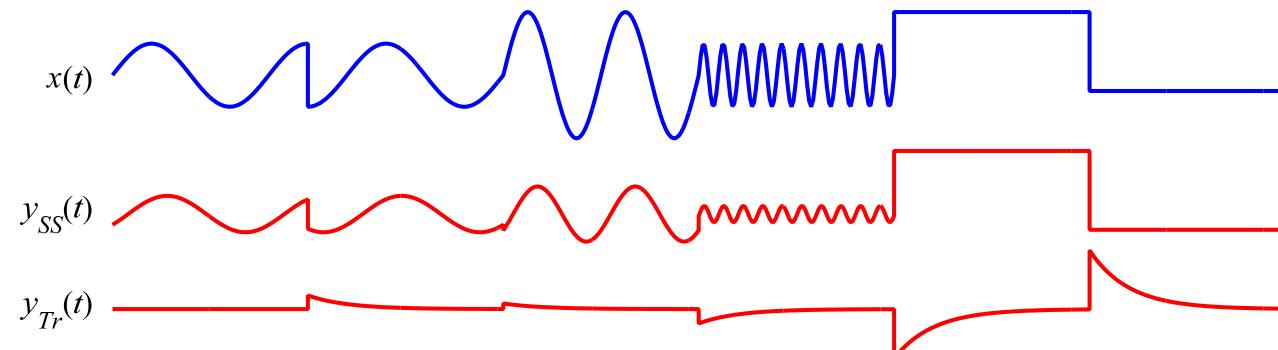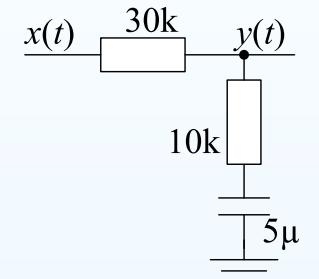Transient is always $y_{Tr}(t) = Ae^{-\frac{t}{\tau}}$ at each change.



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Piecewise steady state inputs



We will consider input signals that are sinusoidal or constant for a particular time interval and then suddenly change in amplitude, phase or frequency.

Output is the sum of the steady state and a transient:

$$y(t) = y_{SS}(t) + y_{Tr}(t)$$

Steady state, $y_{SS}(t)$, is the same frequency as the input; use phasors + nodal analysis.

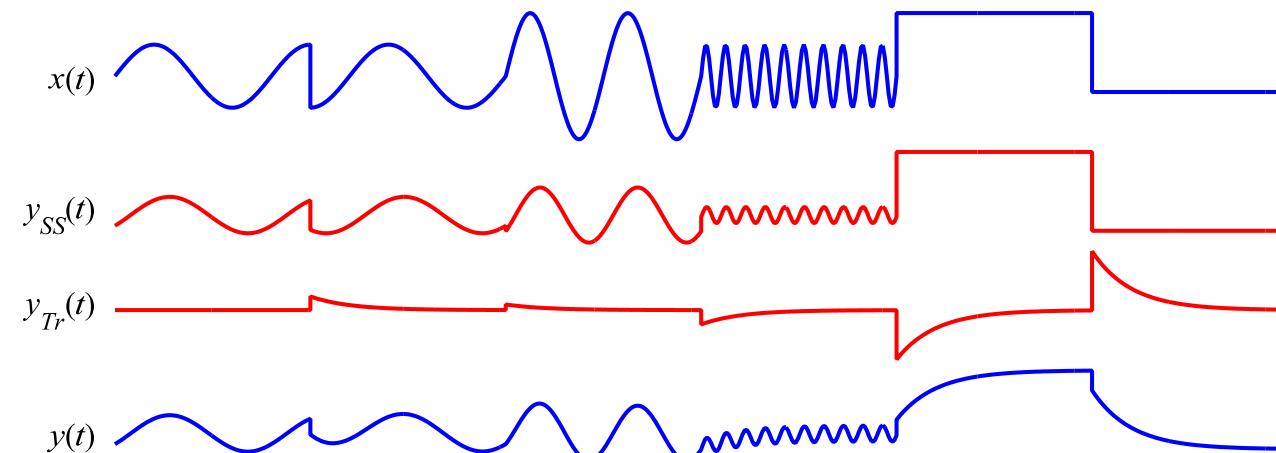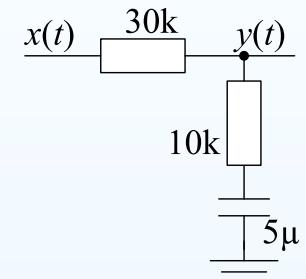Transient is always $y_{Tr}(t) = Ae^{-\frac{t}{\tau}}$ at each change.



15: Transients (A)



- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Step Input

For $t < 0$, $y(t) = x(t) = 1$

For $t \geq 0$, $RC \frac{dy}{dt} + y = x = 4$

Time Const: $\tau = RC = 1 \text{ ms}$

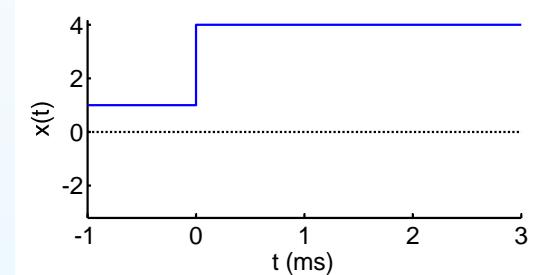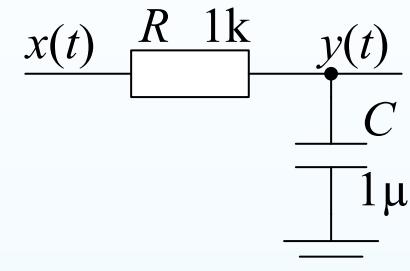

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Step Input




For $t < 0$, $y(t) = x(t) = 1$

For $t \geq 0$, $RC \frac{dy}{dt} + y = x = 4$

Time Const: $\tau = RC = 1 \text{ ms}$

Steady State (Particular Integral)

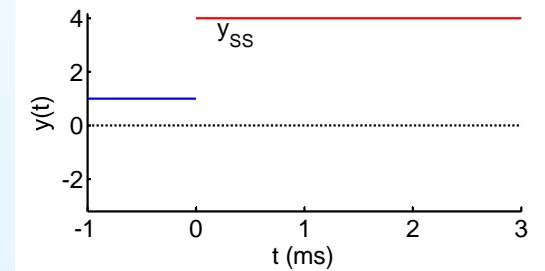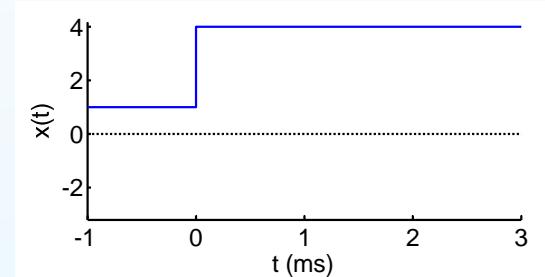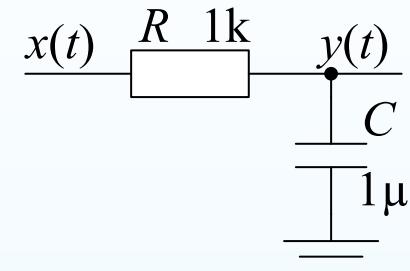$y_{ss}(t) = x(t) = 4 \text{ for } t \geq 0$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Step Input

For $t < 0$, $y(t) = x(t) = 1$

For $t \geq 0$, $RC \frac{dy}{dt} + y = x = 4$




Time Const: $\tau = RC = 1 \text{ ms}$

Steady State (Particular Integral)

$y_{ss}(t) = x(t) = 4 \text{ for } t \geq 0$

Transient (Complementary Function)

$y_{Tr}(t) = Ae^{-t/\tau}$

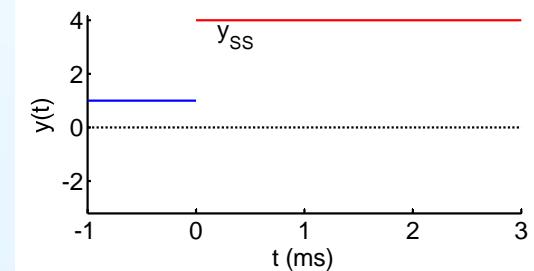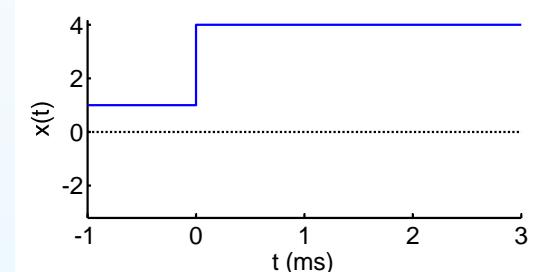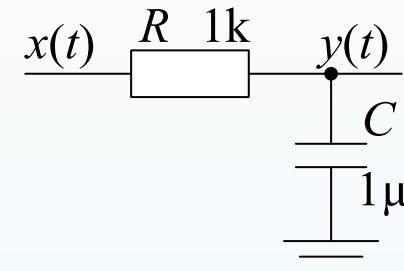

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Step Input

For $t < 0$, $y(t) = x(t) = 1$

For $t \geq 0$, $RC \frac{dy}{dt} + y = x = 4$

Time Const: $\tau = RC = 1 \text{ ms}$

Steady State (Particular Integral)




$y_{SS}(t) = x(t) = 4 \text{ for } t \geq 0$

Transient (Complementary Function)

$$y_{Tr}(t) = Ae^{-t/\tau}$$

Steady State + Transient
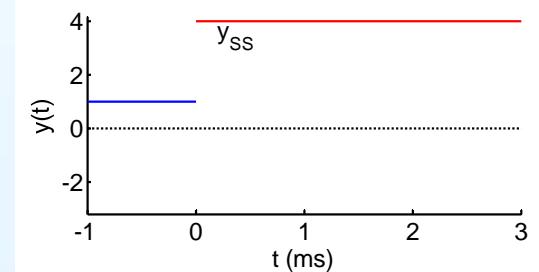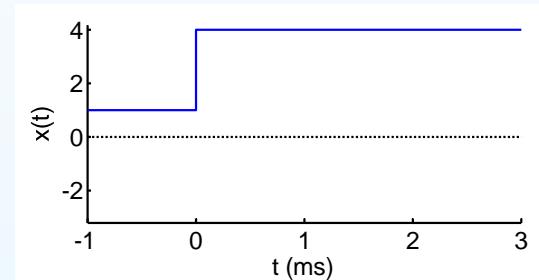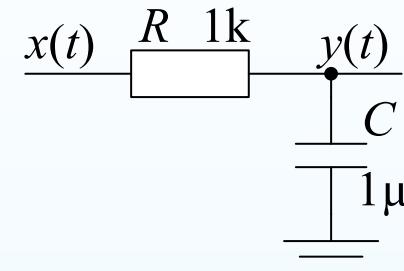
$$y(t) = y_{SS} + y_{Tr} = 4 + Ae^{-t/\tau}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Step Input

For $t < 0$, $y(t) = x(t) = 1$

For $t \geq 0$, $RC \frac{dy}{dt} + y = x = 4$

Time Const: $\tau = RC = 1 \text{ ms}$

Steady State (Particular Integral)

$y_{ss}(t) = x(t) = 4 \text{ for } t \geq 0$

Transient (Complementary Function)




$$y_{Tr}(t) = Ae^{-t/\tau}$$

Steady State + Transient

$$y(t) = y_{ss} + y_{Tr} = 4 + Ae^{-t/\tau}$$

To find A , use capacitor property:

Capacitor voltage never changes abruptly

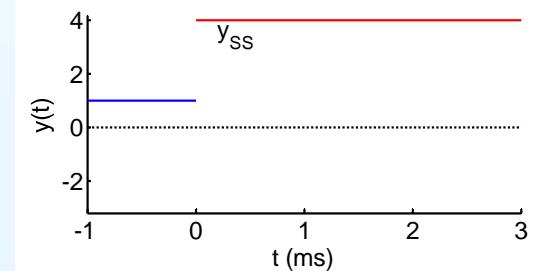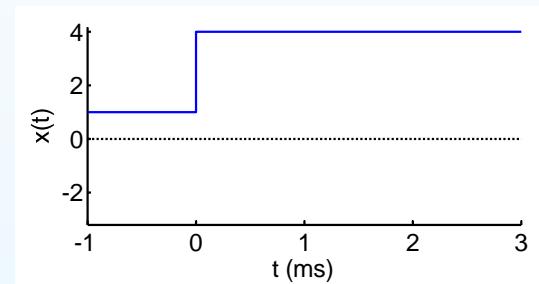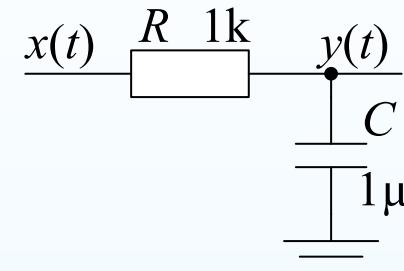

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Step Input

For $t < 0$, $y(t) = x(t) = 1$

For $t \geq 0$, $RC \frac{dy}{dt} + y = x = 4$

Time Const: $\tau = RC = 1 \text{ ms}$

Steady State (Particular Integral)

$y_{ss}(t) = x(t) = 4 \text{ for } t \geq 0$

Transient (Complementary Function)

$$y_{Tr}(t) = Ae^{-t/\tau}$$




Steady State + Transient

$$y(t) = y_{ss} + y_{Tr} = 4 + Ae^{-t/\tau}$$

To find A , use capacitor property:

Capacitor voltage never changes abruptly

$$y(0+) = 4 + A \text{ and } y(0-) = 1$$

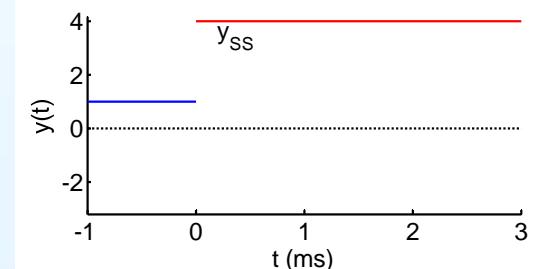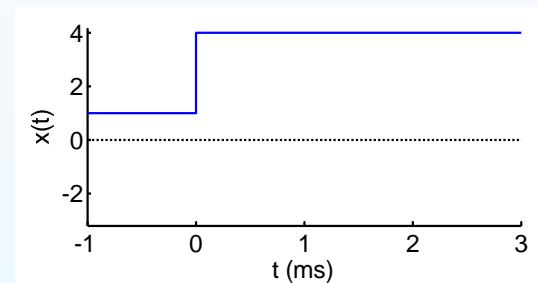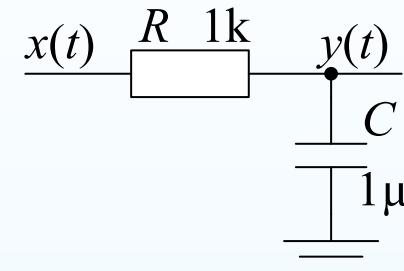

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Step Input

For $t < 0$, $y(t) = x(t) = 1$

For $t \geq 0$, $RC \frac{dy}{dt} + y = x = 4$

Time Const: $\tau = RC = 1 \text{ ms}$

Steady State (Particular Integral)

$y_{ss}(t) = x(t) = 4 \text{ for } t \geq 0$

Transient (Complementary Function)

$$y_{Tr}(t) = Ae^{-t/\tau}$$




Steady State + Transient

$$y(t) = y_{ss} + y_{Tr} = 4 + Ae^{-t/\tau}$$

To find A , use capacitor property:

Capacitor voltage never changes abruptly
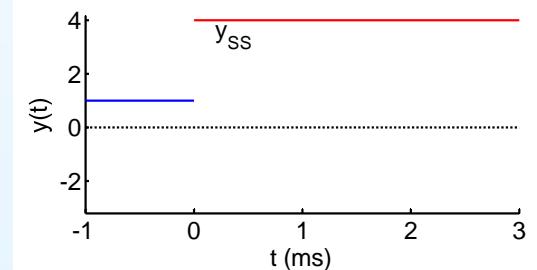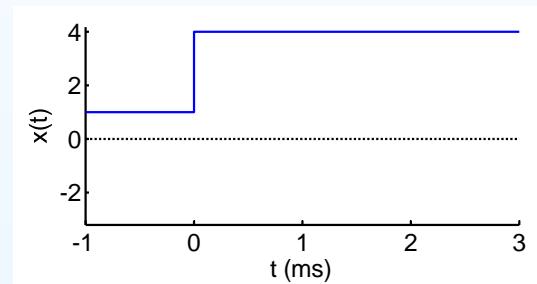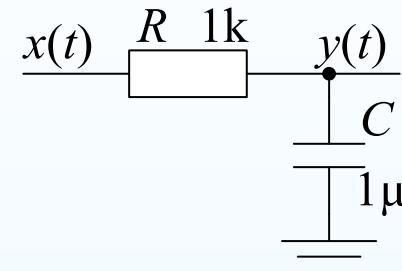
$$y(0+) = 4 + A \text{ and } y(0-) = 1 \Rightarrow 4 + A = 1$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Step Input

For $t < 0$, $y(t) = x(t) = 1$

For $t \geq 0$, $RC \frac{dy}{dt} + y = x = 4$

Time Const: $\tau = RC = 1 \text{ ms}$

Steady State (Particular Integral)

$y_{ss}(t) = x(t) = 4 \text{ for } t \geq 0$

Transient (Complementary Function)

$$y_{Tr}(t) = Ae^{-t/\tau}$$




Steady State + Transient

$$y(t) = y_{ss} + y_{Tr} = 4 + Ae^{-t/\tau}$$

To find A , use capacitor property:

Capacitor voltage never changes abruptly
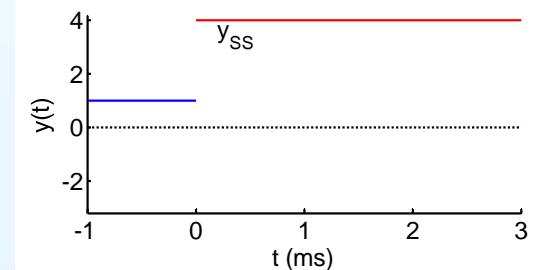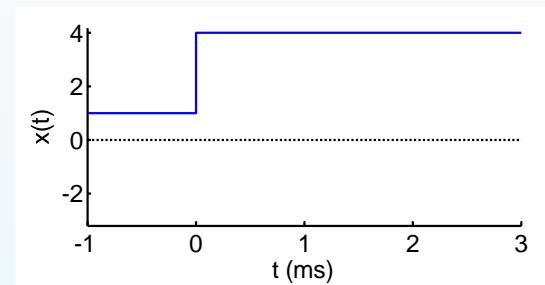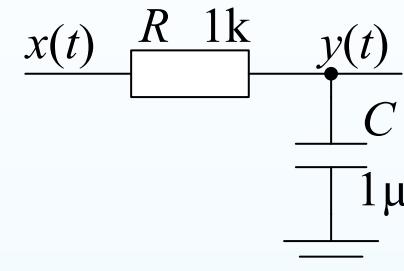
$$y(0+) = 4 + A \text{ and } y(0-) = 1 \Rightarrow 4 + A = 1 \Rightarrow A = -3$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Step Input

For $t < 0$, $y(t) = x(t) = 1$

For $t \geq 0$, $RC \frac{dy}{dt} + y = x = 4$

Time Const: $\tau = RC = 1 \text{ ms}$

Steady State (Particular Integral)

$y_{ss}(t) = x(t) = 4 \text{ for } t \geq 0$

Transient (Complementary Function)

$$y_{Tr}(t) = Ae^{-t/\tau}$$

Steady State + Transient



$$y(t) = y_{ss} + y_{Tr} = 4 + Ae^{-t/\tau}$$

To find A , use capacitor property:

Capacitor voltage never changes abruptly

$$y(0+) = 4 + A \text{ and } y(0-) = 1 \Rightarrow 4 + A = 1 \Rightarrow A = -3$$
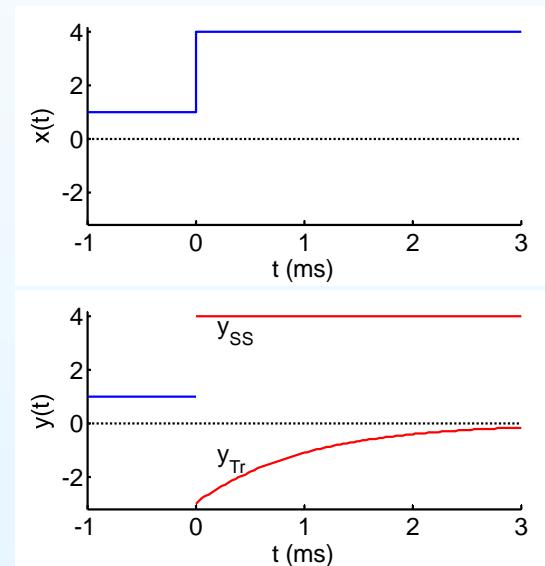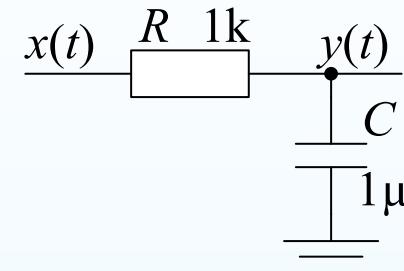
$$\text{So transient: } y_{Tr}(t) = -3e^{-t/\tau}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Step Input

For $t < 0$, $y(t) = x(t) = 1$

For $t \geq 0$, $RC \frac{dy}{dt} + y = x = 4$

Time Const: $\tau = RC = 1 \text{ ms}$

Steady State (Particular Integral)

$y_{ss}(t) = x(t) = 4 \text{ for } t \geq 0$

Transient (Complementary Function)



$$y_{Tr}(t) = Ae^{-t/\tau}$$

Steady State + Transient

$$y(t) = y_{ss} + y_{Tr} = 4 + Ae^{-t/\tau}$$

To find A , use capacitor property:

Capacitor voltage never changes abruptly

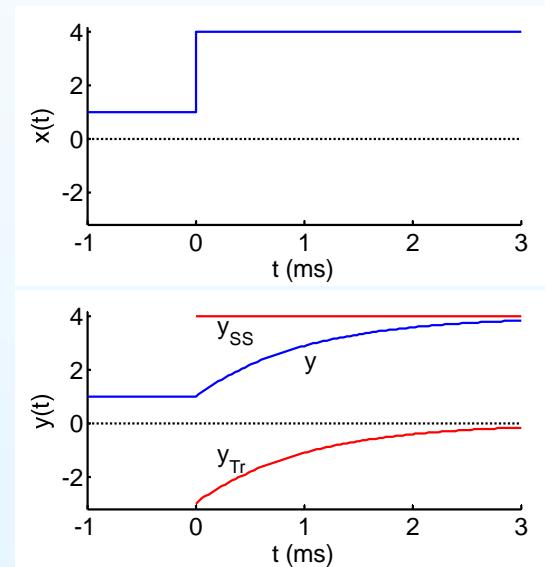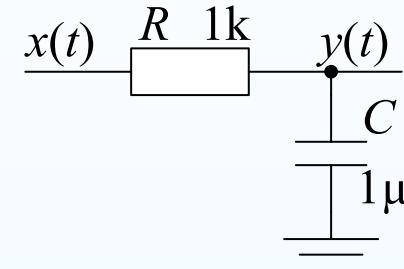

$$y(0+) = 4 + A \text{ and } y(0-) = 1 \Rightarrow 4 + A = 1 \Rightarrow A = -3$$

$$\text{So transient: } y_{Tr}(t) = -3e^{-t/\tau} \text{ and total } y(t) = 4 - 3e^{-t/\tau}$$

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Step Input

For $t < 0$, $y(t) = x(t) = 1$

For $t \geq 0$, $RC \frac{dy}{dt} + y = x = 4$

Time Const: $\tau = RC = 1 \text{ ms}$

Steady State (Particular Integral)

$y_{ss}(t) = x(t) = 4 \text{ for } t \geq 0$

Transient (Complementary Function)




$$y_{Tr}(t) = Ae^{-t/\tau}$$

Steady State + Transient

$$y(t) = y_{ss} + y_{Tr} = 4 + Ae^{-t/\tau}$$

To find A , use capacitor property:

Capacitor voltage never changes abruptly

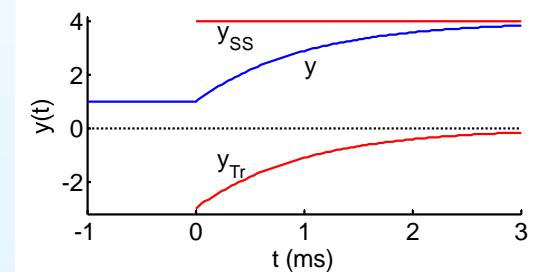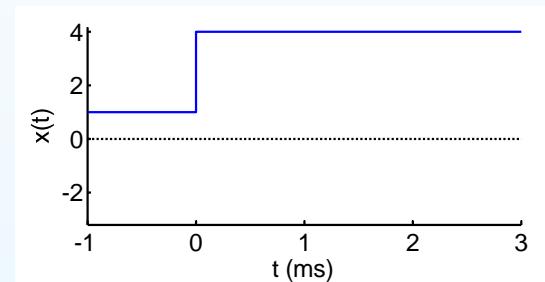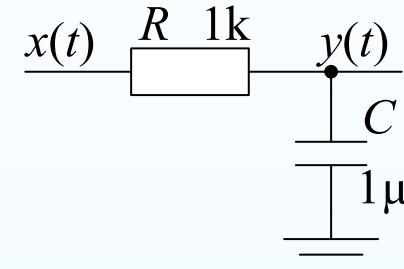

$$y(0+) = 4 + A \text{ and } y(0-) = 1 \Rightarrow 4 + A = 1 \Rightarrow A = -3$$

$$\text{So transient: } y_{Tr}(t) = -3e^{-t/\tau} \text{ and total } y(t) = 4 - 3e^{-t/\tau}$$

Transient amplitude \Leftarrow capacitor voltage continuity: $v_C(0+) = v_C(0-)$


Negative exponentials

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Positive exponentials grow to $\pm\infty$:

$$e^t$$

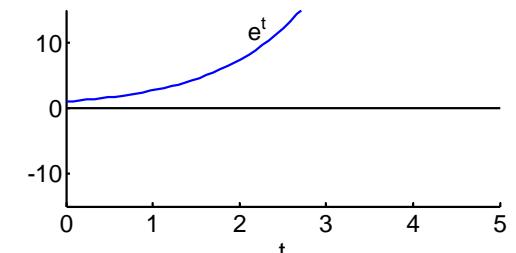


Negative exponentials

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Positive exponentials grow to $\pm\infty$:

$$e^t, 3e^{t/4}$$

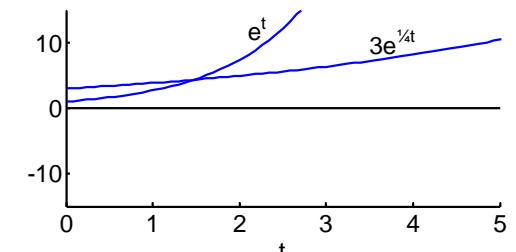


Negative exponentials

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Positive exponentials grow to $\pm\infty$:

$$e^t, 3e^{t/4}, -2e^{t/2}$$

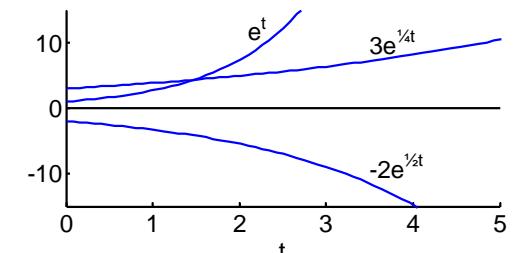

Negative exponentials

15: Transients (A)



- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Positive exponentials grow to $\pm\infty$:

$$e^t, 3e^{t/4}, -2e^{t/2}$$

Negative exponentials decay to 0:

$$2e^{-t}$$

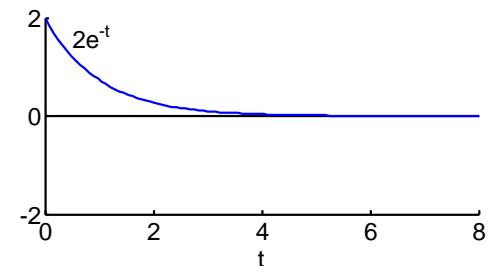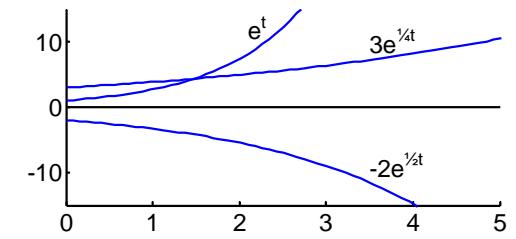

Negative exponentials

15: Transients (A)



- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Positive exponentials grow to $\pm\infty$:

$$e^t, 3e^{t/4}, -2e^{t/2}$$

Negative exponentials decay to 0:

$$2e^{-t}, e^{-t/4}$$

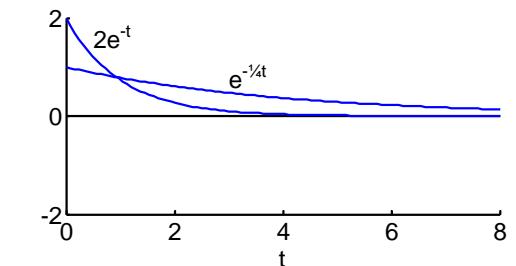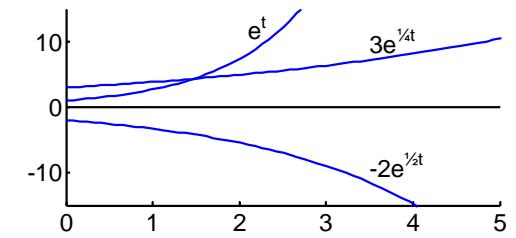

Negative exponentials

15: Transients (A)



- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Positive exponentials grow to $\pm\infty$:

$$e^t, 3e^{t/4}, -2e^{t/2}$$

Negative exponentials decay to 0:

$$2e^{-t}, e^{-t/4}, -2e^{-t/2}$$

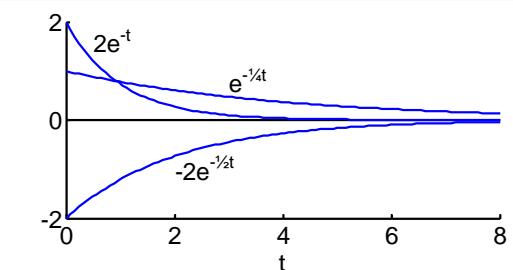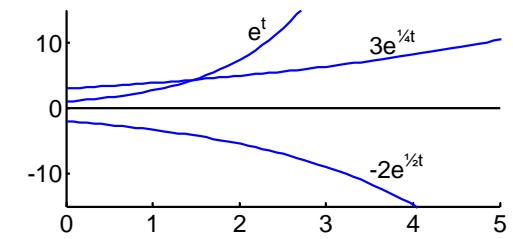

Negative exponentials

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage
- Continuity
- Summary



Positive exponentials grow to $\pm\infty$:

$$e^t, 3e^{t/4}, -2e^{t/2}$$

Negative exponentials decay to 0:

$$2e^{-t}, e^{-t/4}, -2e^{-t/2}$$

Transients are negative exponentials.

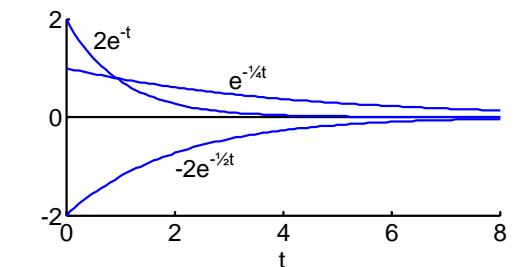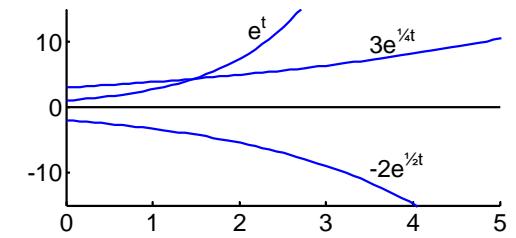


Negative exponentials

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Positive exponentials grow to $\pm\infty$:

$$e^t, 3e^{t/4}, -2e^{t/2}$$


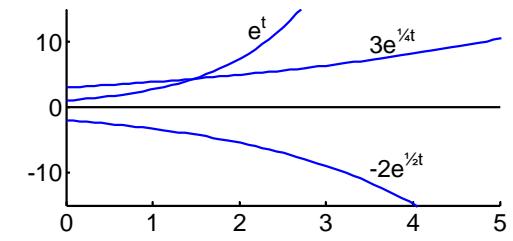


Negative exponentials decay to 0:

$$2e^{-t}, e^{-t/4}, -2e^{-t/2}$$

Transients are negative exponentials.

Decay rate of $e^{-t/a}$

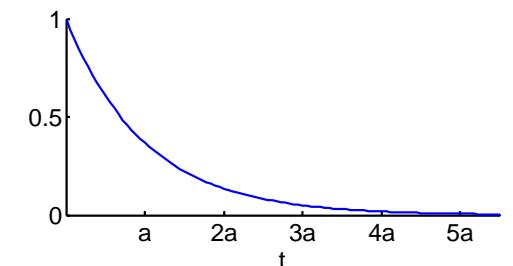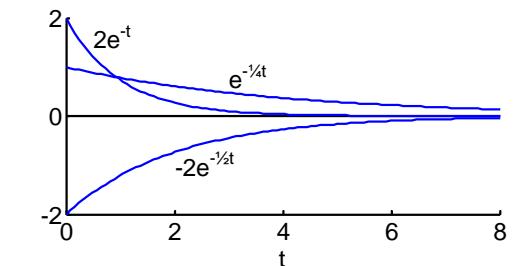


Negative exponentials

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage
- Continuity
- Summary

Positive exponentials grow to $\pm\infty$:


$$e^t, 3e^{t/4}, -2e^{t/2}$$

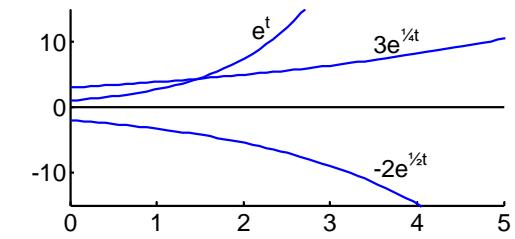

Negative exponentials decay to 0:


$$2e^{-t}, e^{-t/4}, -2e^{-t/2}$$

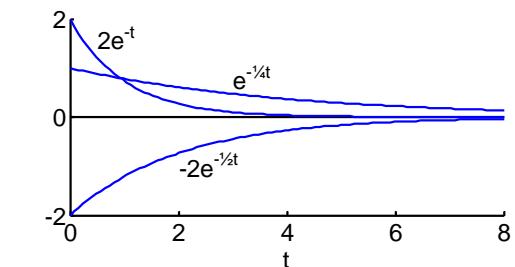Transients are **negative** exponentials.



Decay rate of $e^{-t/a}$

37% after 1 time constant

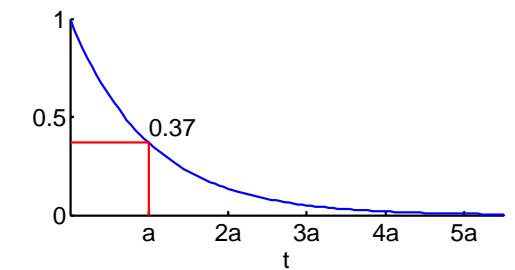


Negative exponentials

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage
- Continuity
- Summary

Positive exponentials grow to $\pm\infty$:


$$e^t, 3e^{t/4}, -2e^{t/2}$$

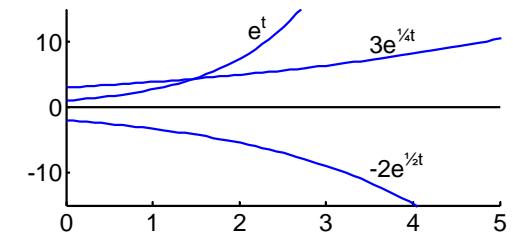

Negative exponentials decay to 0:

$$2e^{-t}, e^{-t/4}, -2e^{-t/2}$$


Transients are negative exponentials.

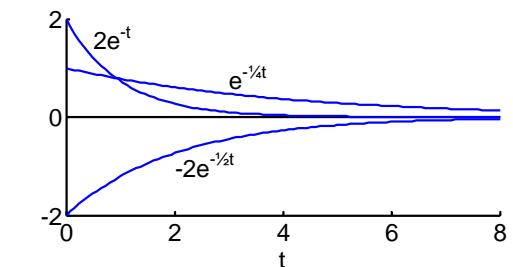

Decay rate of $e^{-t/a}$

37% after 1 time constant

5% after 3

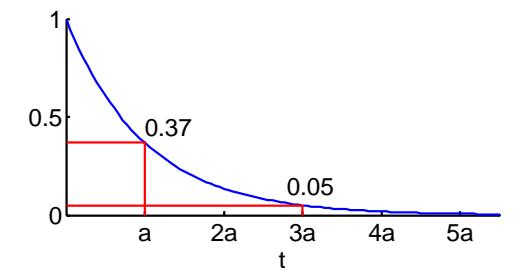


Negative exponentials

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Positive exponentials grow to $\pm\infty$:


$$e^t, 3e^{t/4}, -2e^{t/2}$$

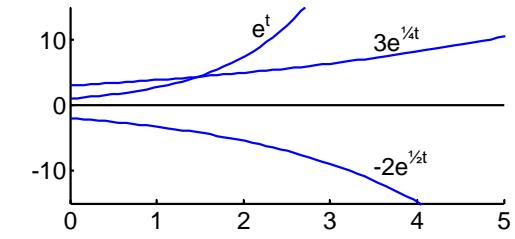

Negative exponentials decay to 0:

$$2e^{-t}, e^{-t/4}, -2e^{-t/2}$$


Transients are negative exponentials.

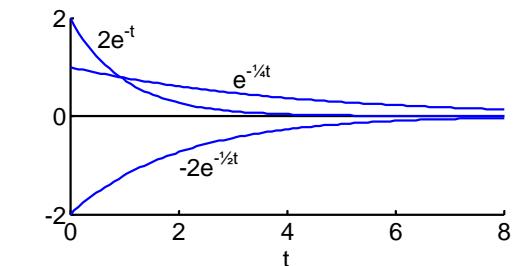

Decay rate of $e^{-t/a}$

37% after 1 time constant

5% after 3, <1% after 5

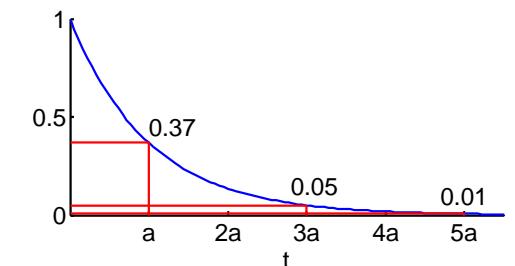


Negative exponentials

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Positive exponentials grow to $\pm\infty$:


$$e^t, 3e^{t/4}, -2e^{t/2}$$

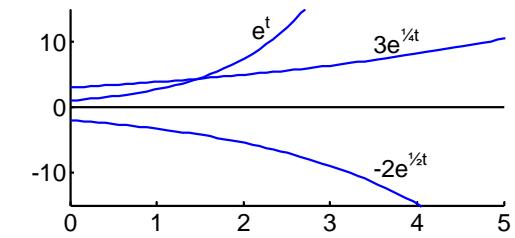

Negative exponentials decay to 0:

$$2e^{-t}, e^{-t/4}, -2e^{-t/2}$$

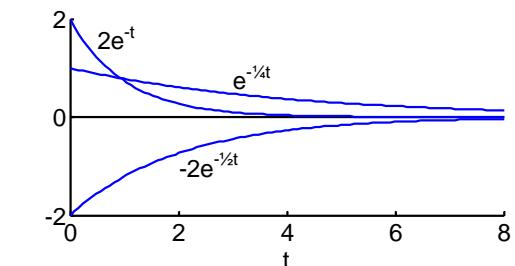
Transients are **negative exponentials**.



Decay rate of $e^{-t/a}$


37% after 1 time constant

5% after 3, <1% after 5

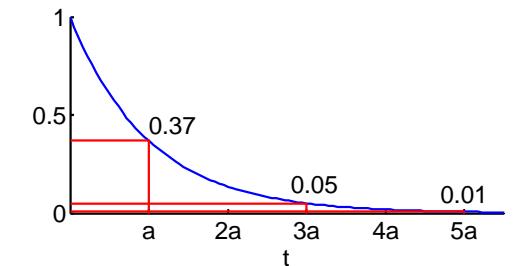

Gradient of $e^{-t/a}$

Gradient at t hits zero at $t + a$.

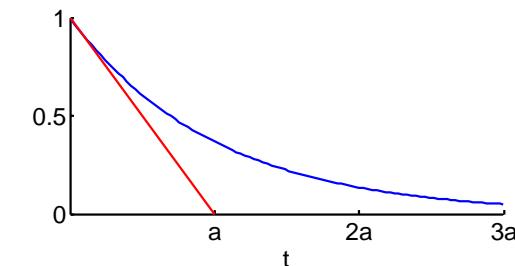


Negative exponentials

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Positive exponentials grow to $\pm\infty$:


$$e^t, 3e^{t/4}, -2e^{t/2}$$

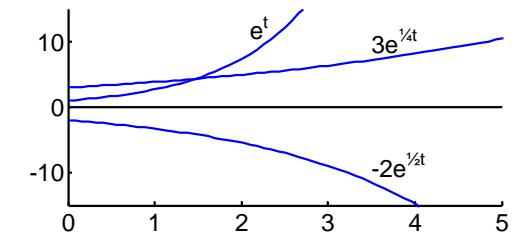

Negative exponentials decay to 0:

$$2e^{-t}, e^{-t/4}, -2e^{-t/2}$$

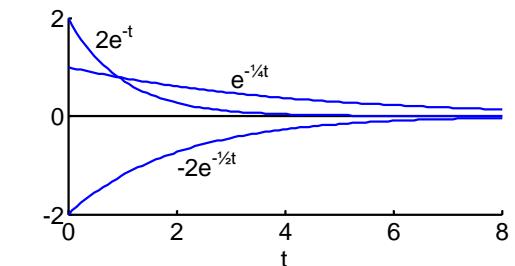
Transients are **negative** exponentials.



Decay rate of $e^{-t/a}$

37% after 1 time constant


5% after 3, <1% after 5

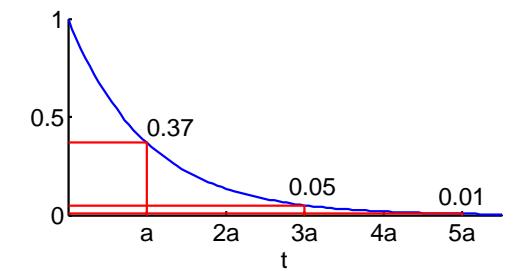

Gradient of $e^{-t/a}$

Gradient at t hits zero at $t + a$.

True for any t .

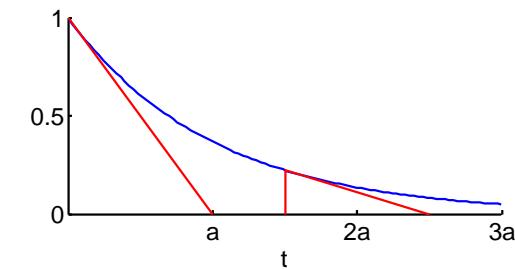


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- **Exponential Time Delays**
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Exponential Time Delays

Negative exponential with a final value of F .

$$y(t) = F + (A - F) e^{-(t-T_A)/\tau}$$

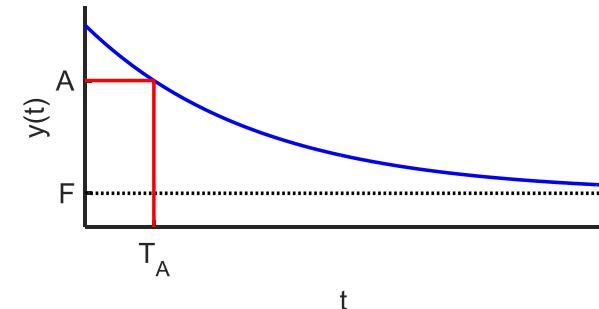


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- **Exponential Time Delays**
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Exponential Time Delays

Negative exponential with a final value of F .

$$y(t) = F + (A - F) e^{-(t-T_A)/\tau}$$

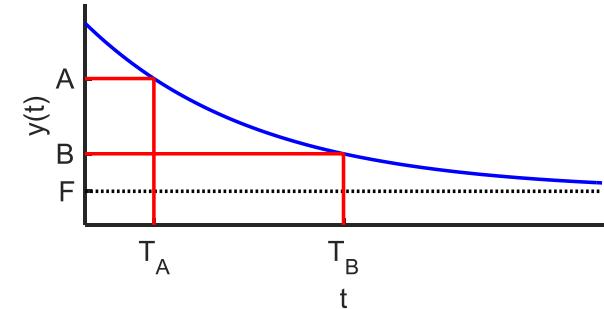

How long does it take to go from A to B ?


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- **Exponential Time Delays**
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Exponential Time Delays

Negative exponential with a final value of F .

$$y(t) = F + (A - F) e^{-(t-T_A)/\tau}$$

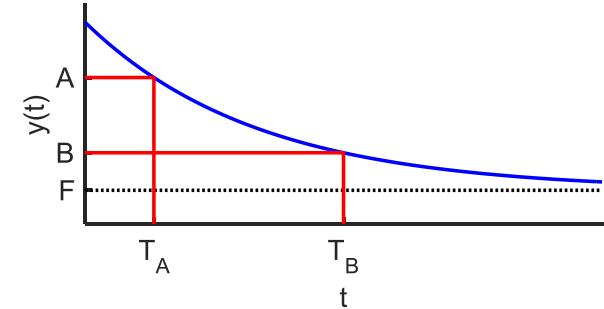

How long does it take to go from A to B ?

At $t = T_B$:

$$y(T_B) = B = F + (A - F) e^{-(T_B-T_A)/\tau}$$


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- **Exponential Time Delays**
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Exponential Time Delays

Negative exponential with a final value of F .

$$y(t) = F + (A - F) e^{-(t-T_A)/\tau}$$

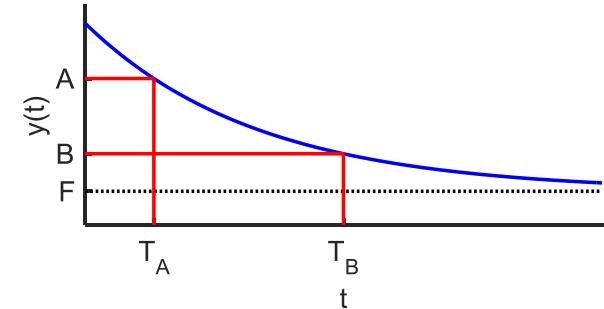

How long does it take to go from A to B ?

At $t = T_B$:

$$y(T_B) = B = F + (A - F) e^{-(T_B - T_A)/\tau}$$

$$\frac{B-F}{A-F} = e^{-(T_B - T_A)/\tau}$$


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- **Exponential Time Delays**
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Exponential Time Delays

Negative exponential with a final value of F .

$$y(t) = F + (A - F) e^{-(t-T_A)/\tau}$$

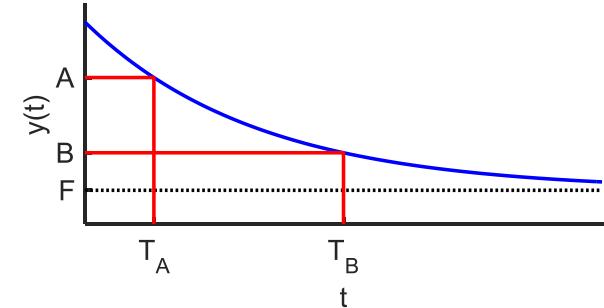

How long does it take to go from A to B ?

At $t = T_B$:

$$y(T_B) = B = F + (A - F) e^{-(T_B - T_A)/\tau}$$

$$\frac{B-F}{A-F} = e^{-(T_B - T_A)/\tau}$$

$$\text{Hence } T_B - T_A = \tau \ln \left(\frac{A-F}{B-F} \right) = \tau \ln \left(\frac{\text{initial distance to } F}{\text{final distance to } F} \right)$$


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- **Exponential Time Delays**
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Exponential Time Delays

Negative exponential with a final value of F .

$$y(t) = F + (A - F) e^{-(t-T_A)/\tau}$$

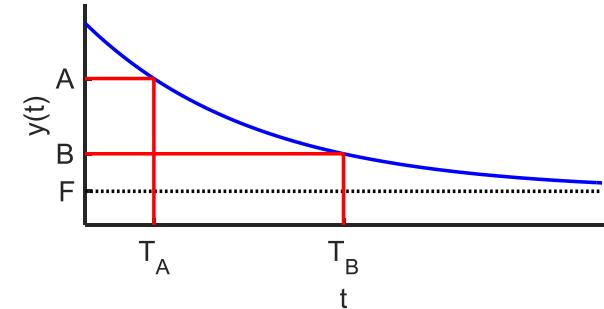

How long does it take to go from A to B ?

At $t = T_B$:

$$y(T_B) = B = F + (A - F) e^{-(T_B-T_A)/\tau}$$

$$\frac{B-F}{A-F} = e^{-(T_B-T_A)/\tau}$$

$$\text{Hence } T_B - T_A = \tau \ln \left(\frac{A-F}{B-F} \right) = \tau \ln \left(\frac{\text{initial distance to } F}{\text{final distance to } F} \right)$$


Useful formula - worth remembering.

Inductor Transients

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- **Inductor Transients**
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

We know $i = \frac{x-y}{R}$

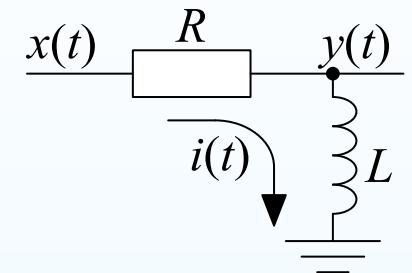


Inductor Transients

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- **Inductor Transients**
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

We know $i = \frac{x-y}{R}$

$$y(t) = L \frac{di}{dt}$$

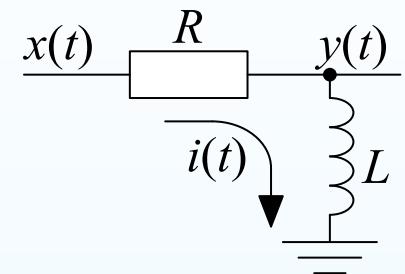


Inductor Transients

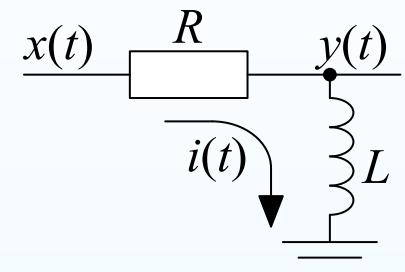15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- **Inductor Transients**
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

We know $i = \frac{x-y}{R}$
 $y(t) = L \frac{di}{dt} = \frac{L}{R} \times \frac{d(x-y)}{dt}$




15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- **Inductor Transients**
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Inductor Transients

We know $i = \frac{x-y}{R}$
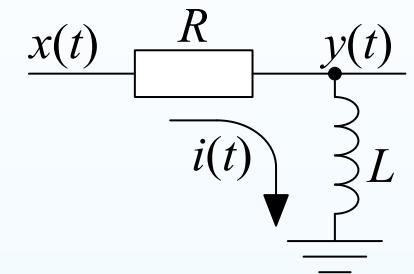
$$y(t) = L \frac{di}{dt} = \frac{L}{R} \times \frac{d(x-y)}{dt} = \frac{L}{R} \frac{dx}{dt} - \frac{L}{R} \frac{dy}{dt}$$




Inductor Transients

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

We know $i = \frac{x-y}{R}$
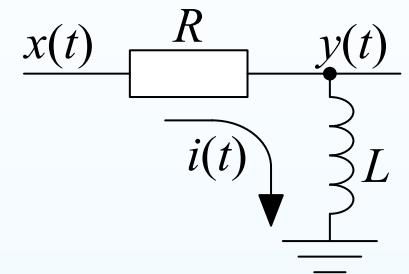
$$y(t) = L \frac{di}{dt} = \frac{L}{R} \times \frac{d(x-y)}{dt} = \frac{L}{R} \frac{dx}{dt} - \frac{L}{R} \frac{dy}{dt}$$
$$\Rightarrow \frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$$




15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Inductor Transients

We know $i = \frac{x-y}{R}$
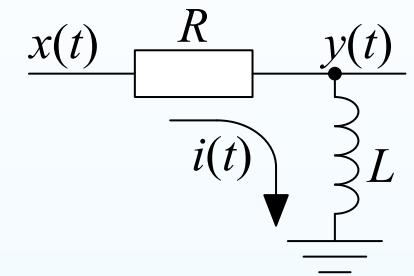
$$y(t) = L \frac{di}{dt} = \frac{L}{R} \times \frac{d(x-y)}{dt} = \frac{L}{R} \frac{dx}{dt} - \frac{L}{R} \frac{dy}{dt}$$
$$\Rightarrow \frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$$



Solution: Particular Integral + Complementary Function


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- **Inductor Transients**
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Inductor Transients

We know $i = \frac{x-y}{R}$
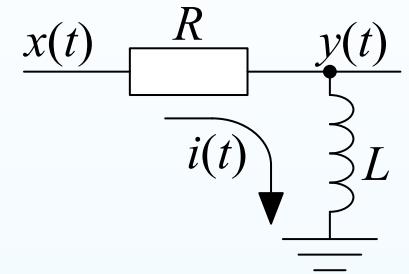
$$y(t) = L \frac{di}{dt} = \frac{L}{R} \times \frac{d(x-y)}{dt} = \frac{L}{R} \frac{dx}{dt} - \frac{L}{R} \frac{dy}{dt}$$
$$\Rightarrow \frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$$



Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $\frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- **Inductor Transients**
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Inductor Transients

We know $i = \frac{x-y}{R}$
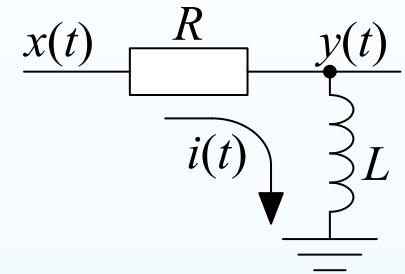
$$y(t) = L \frac{di}{dt} = \frac{L}{R} \times \frac{d(x-y)}{dt} = \frac{L}{R} \frac{dx}{dt} - \frac{L}{R} \frac{dy}{dt}$$
$$\Rightarrow \frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$$



Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $\frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$

If $x(t)$ is piecewise constant or sinusoidal, we will use nodal/phasor analysis to find the **steady state solution**, $y_{SS}(t)$.


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- **Inductor Transients**
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Inductor Transients

We know $i = \frac{x-y}{R}$
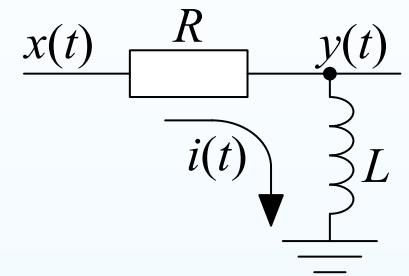
$$y(t) = L \frac{di}{dt} = \frac{L}{R} \times \frac{d(x-y)}{dt} = \frac{L}{R} \frac{dx}{dt} - \frac{L}{R} \frac{dy}{dt}$$
$$\Rightarrow \frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$$



Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $\frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$

If $x(t)$ is piecewise constant or sinusoidal, we will use nodal/phasor analysis to find the **steady state solution**, $y_{SS}(t)$.

Complementary Function: Solution to $\frac{L}{R} \frac{dy}{dt} + y = 0$


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- **Inductor Transients**
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Inductor Transients

We know $i = \frac{x-y}{R}$
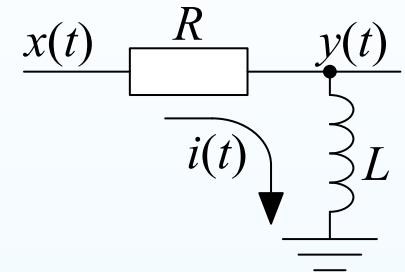
$$y(t) = L \frac{di}{dt} = \frac{L}{R} \times \frac{d(x-y)}{dt} = \frac{L}{R} \frac{dx}{dt} - \frac{L}{R} \frac{dy}{dt}$$
$$\Rightarrow \frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$$



Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $\frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$

If $x(t)$ is piecewise constant or sinusoidal, we will use nodal/phasor analysis to find the **steady state solution**, $y_{SS}(t)$.

Complementary Function: Solution to $\frac{L}{R} \frac{dy}{dt} + y = 0$

Does not depend on $x(t)$, only on the circuit.


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- **Inductor Transients**
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Inductor Transients

We know $i = \frac{x-y}{R}$
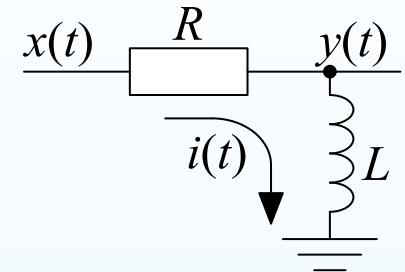
$$y(t) = L \frac{di}{dt} = \frac{L}{R} \times \frac{d(x-y)}{dt} = \frac{L}{R} \frac{dx}{dt} - \frac{L}{R} \frac{dy}{dt}$$
$$\Rightarrow \frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$$



Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $\frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$

If $x(t)$ is piecewise constant or sinusoidal, we will use nodal/phasor analysis to find the **steady state solution**, $y_{SS}(t)$.

Complementary Function: Solution to $\frac{L}{R} \frac{dy}{dt} + y = 0$

Does not depend on $x(t)$, only on the circuit.

Solution is $y_{Tr}(t) = Ae^{-t/\tau}$

where $\tau = \frac{L}{R}$ is the **time constant** of the circuit.


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- **Inductor Transients**
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Inductor Transients

We know $i = \frac{x-y}{R}$
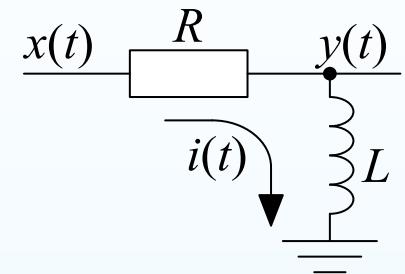
$$y(t) = L \frac{di}{dt} = \frac{L}{R} \times \frac{d(x-y)}{dt} = \frac{L}{R} \frac{dx}{dt} - \frac{L}{R} \frac{dy}{dt}$$
$$\Rightarrow \frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$$



Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $\frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$

If $x(t)$ is piecewise constant or sinusoidal, we will use nodal/phasor analysis to find the **steady state solution**, $y_{SS}(t)$.

Complementary Function: Solution to $\frac{L}{R} \frac{dy}{dt} + y = 0$

Does not depend on $x(t)$, only on the circuit.

Solution is $y_{Tr}(t) = Ae^{-t/\tau}$

where $\tau = \frac{L}{R}$ is the **time constant** of the circuit.

1st order transient is **always** $y_{Tr}(t) = Ae^{-t/\tau}$ where $\tau = RC$ or $\frac{L}{R}$


15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- **Inductor Transients**
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Inductor Transients

We know $i = \frac{x-y}{R}$
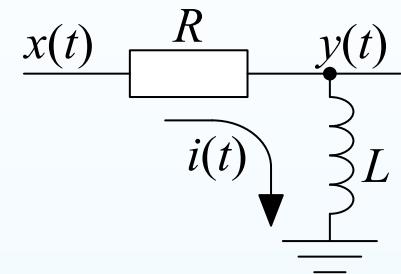
$$y(t) = L \frac{di}{dt} = \frac{L}{R} \times \frac{d(x-y)}{dt} = \frac{L}{R} \frac{dx}{dt} - \frac{L}{R} \frac{dy}{dt}$$
$$\Rightarrow \frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$$



Solution: Particular Integral + Complementary Function

Particular Integral: Any solution to $\frac{L}{R} \frac{dy}{dt} + y = \frac{L}{R} \frac{dx}{dt}$

If $x(t)$ is piecewise constant or sinusoidal, we will use nodal/phasor analysis to find the **steady state solution**, $y_{SS}(t)$.

Complementary Function: Solution to $\frac{L}{R} \frac{dy}{dt} + y = 0$

Does not depend on $x(t)$, only on the circuit.

Solution is $y_{Tr}(t) = Ae^{-t/\tau}$

where $\tau = \frac{L}{R}$ is the **time constant** of the circuit.

1st order transient is **always** $y_{Tr}(t) = Ae^{-t/\tau}$ where $\tau = RC$ or $\frac{L}{R}$


Amplitude $A \Leftarrow$ no abrupt change in capacitor voltage or inductor current.

Linearity

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- **Linearity**
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

1st order circuit has only one C or L .

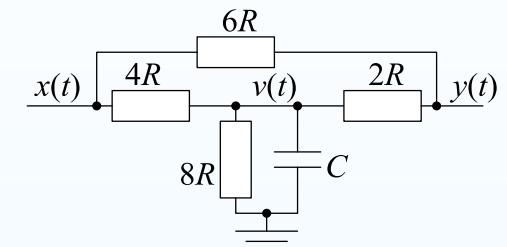


Linearity

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- **Linearity**
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

1st order circuit has only one C or L .

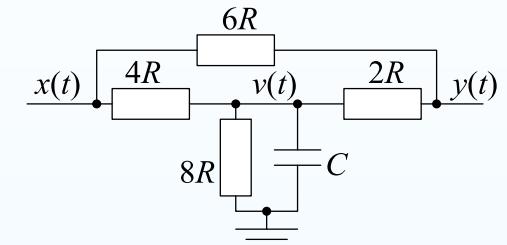Make a Thévenin equivalent of the network connected to the terminals of C .





15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Linearity

1st order circuit has only one C or L .

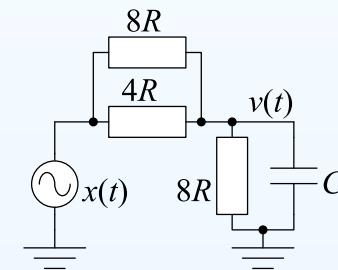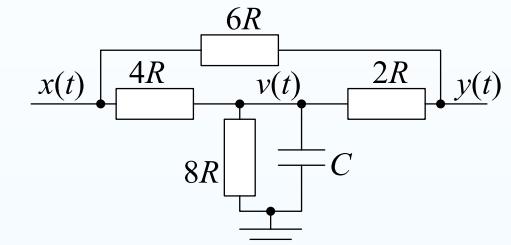Make a Thévenin equivalent of the network connected to the terminals of C . Remember x is a voltage source but y is not.





15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Linearity

1st order circuit has only one C or L .

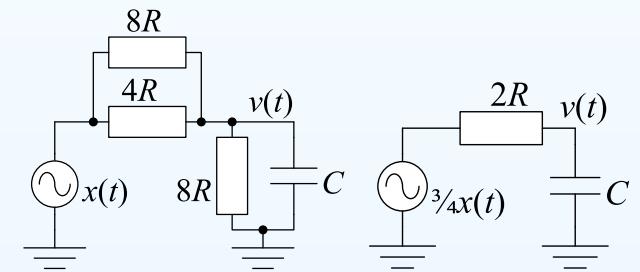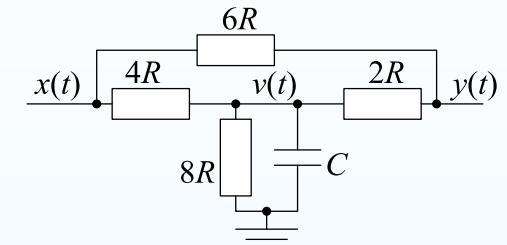Make a Thévenin equivalent of the network connected to the terminals of C . Remember x is a voltage source but y is not.



15: Transients (A)



- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- **Linearity**
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Linearity

1st order circuit has only one C or L .

Make a Thévenin equivalent of the network connected to the terminals of C . Remember x is a voltage source but y is not.
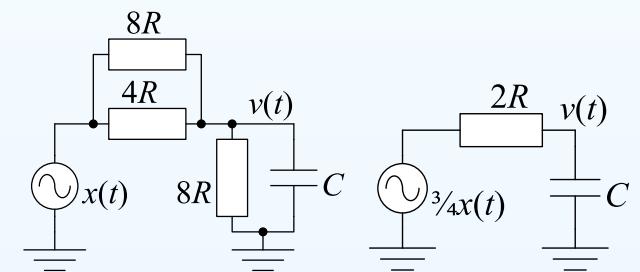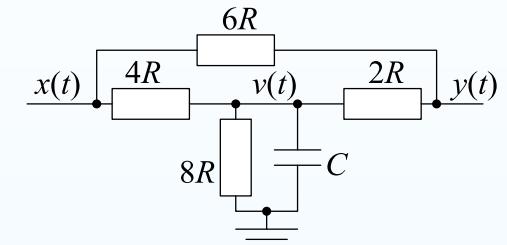
$$\begin{aligned} \text{Now } v(t) &= v_{SS}(t) + v_{Tr}(t) \\ &= v_{SS}(t) + Ae^{-t/\tau} \end{aligned}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- **Linearity**
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary



Linearity

1st order circuit has only one C or L .

Make a Thévenin equivalent of the network connected to the terminals of C . Remember x is a voltage source but y is not.

$$\begin{aligned}v(t) &= v_{SS}(t) + v_{Tr}(t) \\&= v_{SS}(t) + Ae^{-t/\tau}\end{aligned}$$

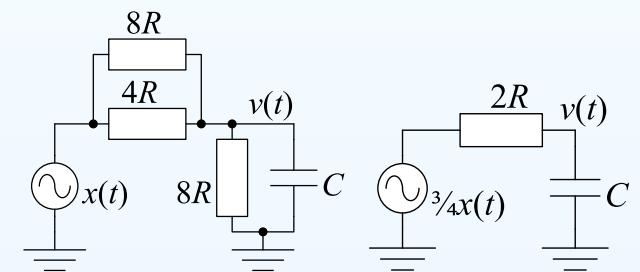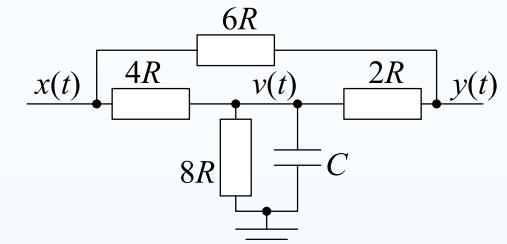Time constant is $\tau = R_{Th}C$
where R_{Th} is the Thévenin resistance.



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- **Linearity**
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Linearity




1st order circuit has only one C or L .

Make a Thévenin equivalent of the network connected to the terminals of C . Remember x is a voltage source but y is not.

$$\begin{aligned}v(t) &= v_{SS}(t) + v_{Tr}(t) \\&= v_{SS}(t) + Ae^{-t/\tau}\end{aligned}$$

Time constant is $\tau = R_{Th}C$
where R_{Th} is the Thévenin resistance.

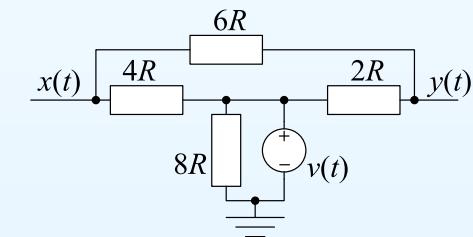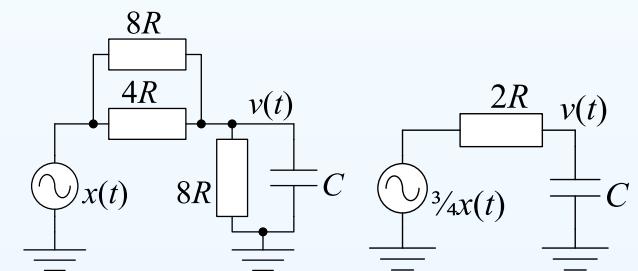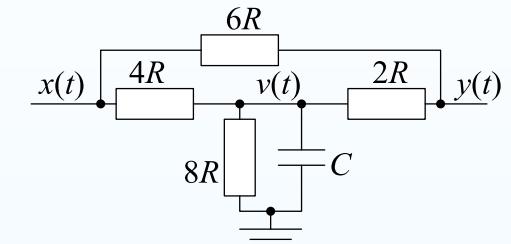Replace the capacitor with a voltage source $v(t)$; all voltages and currents in the circuit will remain unchanged.



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- **Linearity**
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Linearity

1st order circuit has only one C or L .




Make a Thévenin equivalent of the network connected to the terminals of C . Remember x is a voltage source but y is not.

$$\begin{aligned}v(t) &= v_{SS}(t) + v_{Tr}(t) \\&= v_{SS}(t) + Ae^{-t/\tau}\end{aligned}$$

Time constant is $\tau = R_{Th}C$
where R_{Th} is the Thévenin resistance.

Replace the capacitor with a voltage source $v(t)$; all voltages and currents in the circuit will remain unchanged.
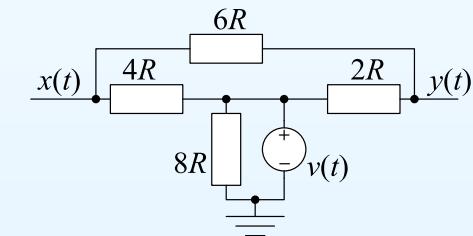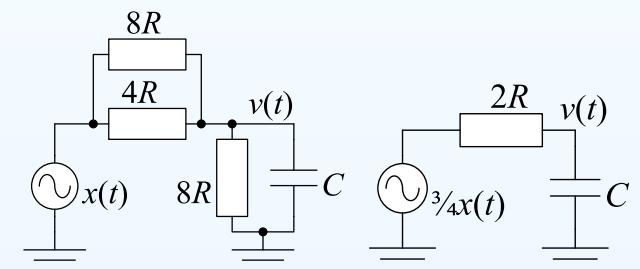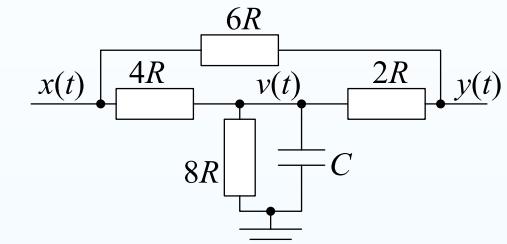
$$\text{Linearity: } y = ax + bv = ax + bv_{SS} + bv_{Tr}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- **Linearity**
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Linearity

1st order circuit has only one C or L .




Make a Thévenin equivalent of the network connected to the terminals of C . Remember x is a voltage source but y is not.

$$\begin{aligned}v(t) &= v_{SS}(t) + v_{Tr}(t) \\&= v_{SS}(t) + Ae^{-t/\tau}\end{aligned}$$

Time constant is $\tau = R_{Th}C$
where R_{Th} is the Thévenin resistance.

Replace the capacitor with a voltage source $v(t)$; all voltages and currents in the circuit will remain unchanged.
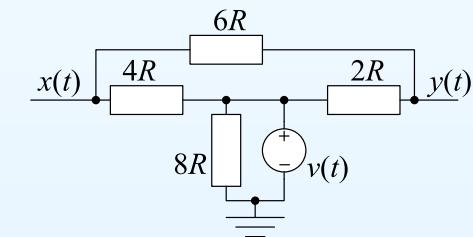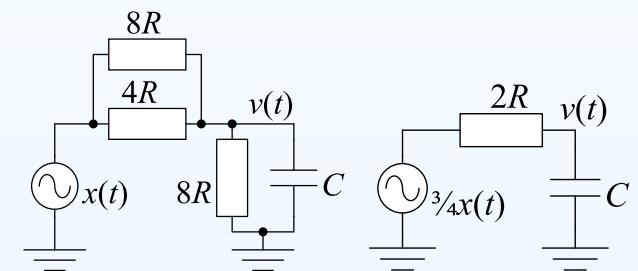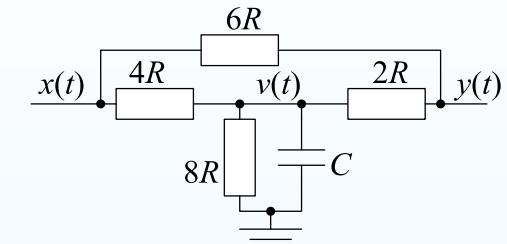
$$\text{Linearity: } y = ax + bv = ax + bv_{SS} + bv_{Tr} = y_{SS} + bv_{Tr}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- **Linearity**
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Linearity

1st order circuit has only one C or L .

Make a Thévenin equivalent of the network connected to the terminals of C . Remember x is a voltage source but y is not.




$$\begin{aligned}v(t) &= v_{SS}(t) + v_{Tr}(t) \\&= v_{SS}(t) + Ae^{-t/\tau}\end{aligned}$$

Time constant is $\tau = R_{Th}C$
where R_{Th} is the Thévenin resistance.

Replace the capacitor with a voltage source $v(t)$; all voltages and currents in the circuit will remain unchanged.

$$\text{Linearity: } y = ax + bv = ax + bv_{SS} + bv_{Tr} = y_{SS} + bv_{Tr}$$

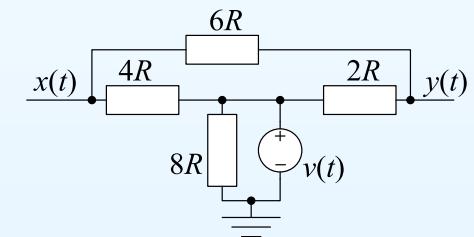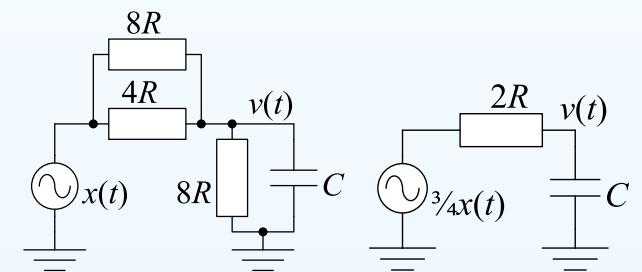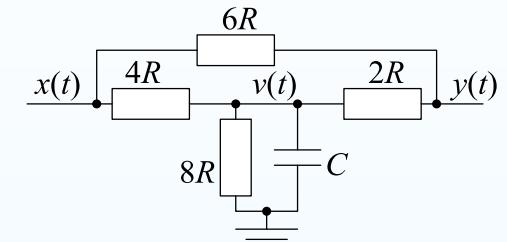All voltages and currents in a circuit have the same transient (but scaled).



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- **Linearity**
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Linearity

1st order circuit has only one C or L .

Make a Thévenin equivalent of the network connected to the terminals of C . Remember x is a voltage source but y is not.

$$\begin{aligned}v(t) &= v_{SS}(t) + v_{Tr}(t) \\&= v_{SS}(t) + Ae^{-t/\tau}\end{aligned}$$




Time constant is $\tau = R_{Th}C$
where R_{Th} is the Thévenin resistance.

Replace the capacitor with a voltage source $v(t)$; all voltages and currents in the circuit will remain unchanged.

$$\text{Linearity: } y = ax + bv = ax + bv_{SS} + bv_{Tr} = y_{SS} + bv_{Tr}$$

All voltages and currents in a circuit have the same transient (but scaled).

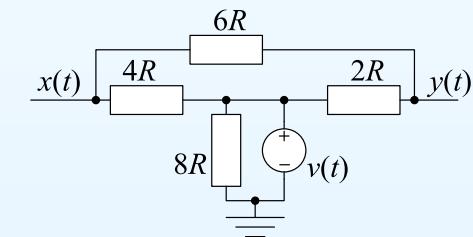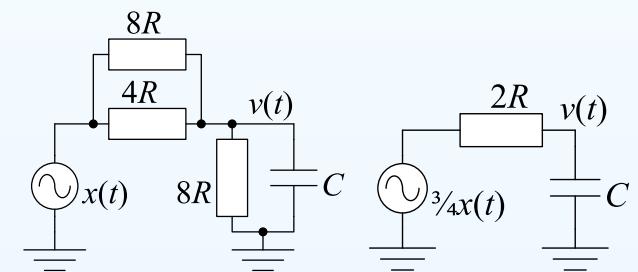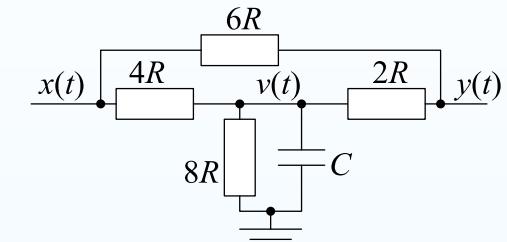The *circuit's time constant* is $\tau = R_{Th}C$ or $\frac{L}{R_{Th}}$ where R_{Th} is the Thévenin resistance of the network connected to C or L .





Transient Amplitude

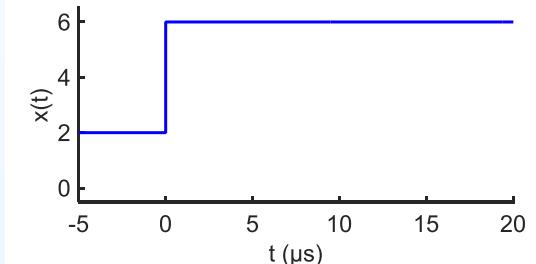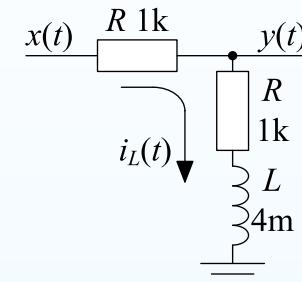15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State ($DC \Rightarrow Z_L = 0$)





Transient Amplitude

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_L = 0$)
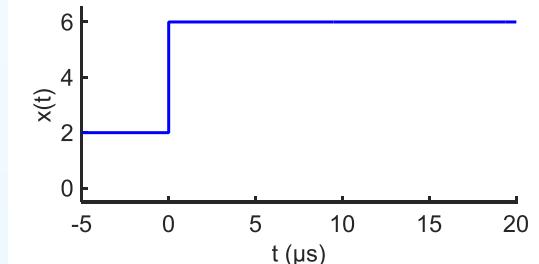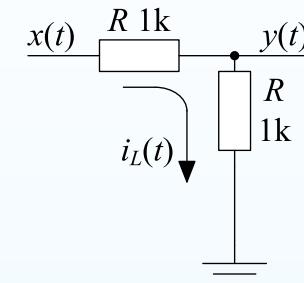
$$\text{Potential divider: } y_{SS} = \frac{1}{2}x$$



Transient Amplitude




15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

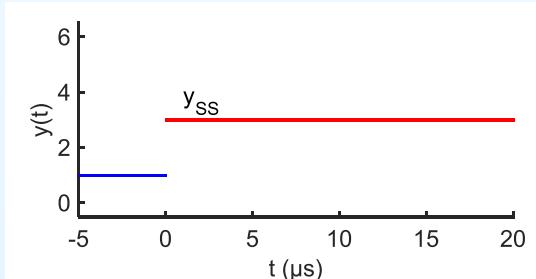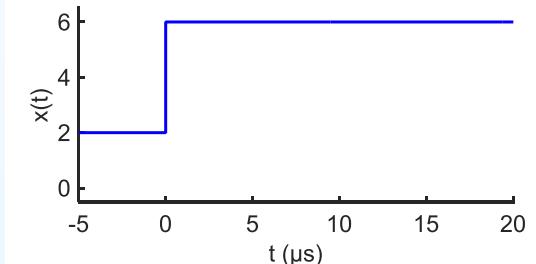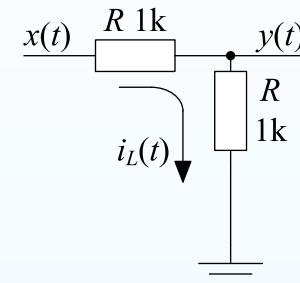

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude




Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Inductor Current Continuity
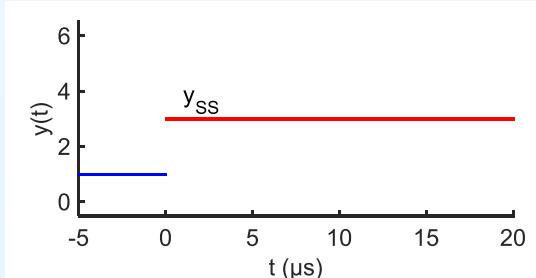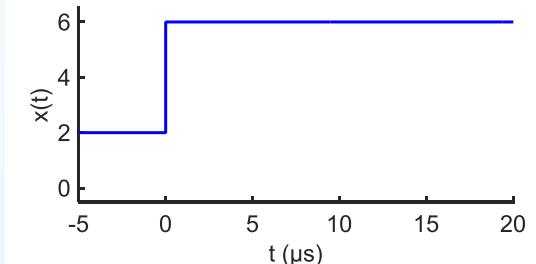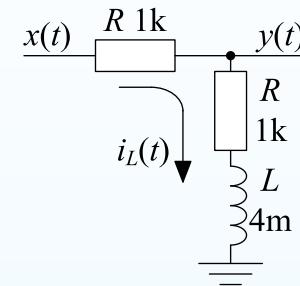
$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude

Find Steady State (DC $\Rightarrow Z_L = 0$)




Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Inductor Current Continuity

$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$

At $t = 0+$

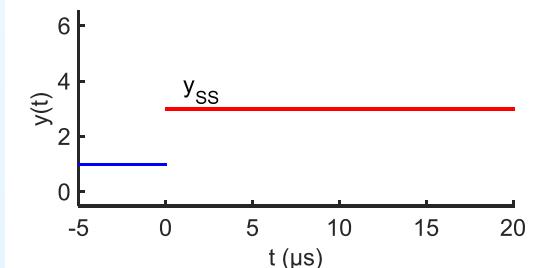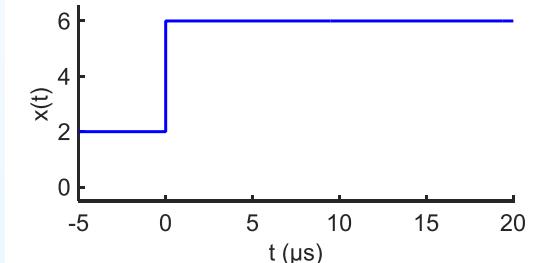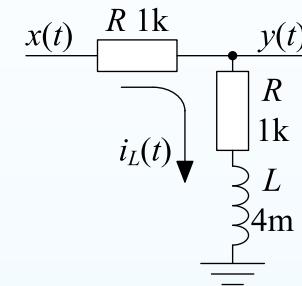

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude

Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$




$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Inductor Current Continuity

$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$

At $t = 0+$
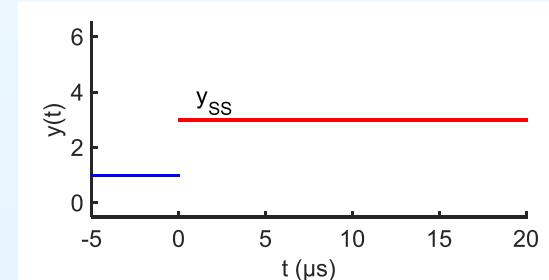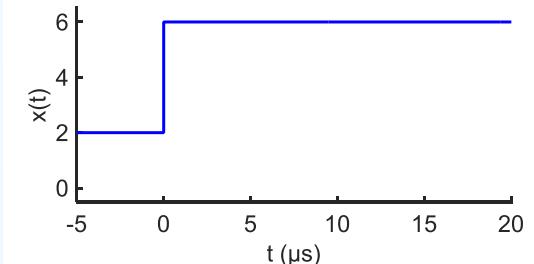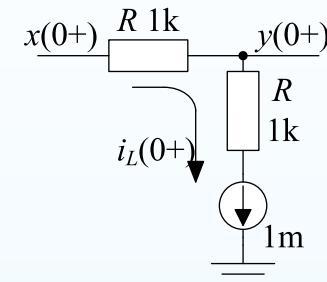
$$x - y = 1 \text{ mA} \times 1 \text{ k} = 1$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude

Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$




Inductor Current Continuity

$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$

At $t = 0+$

$$x - y = 1 \text{ mA} \times 1 \text{ k} = 1$$

$$y(0+) = x(0+) - 1 = 5$$

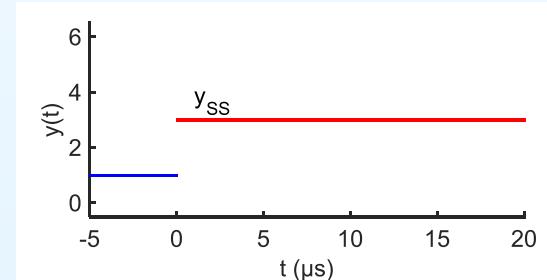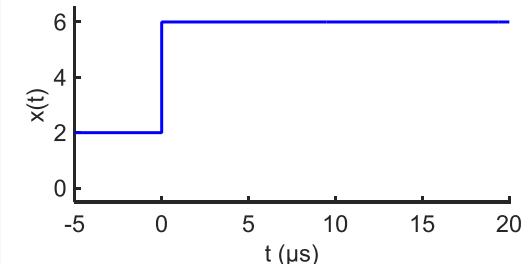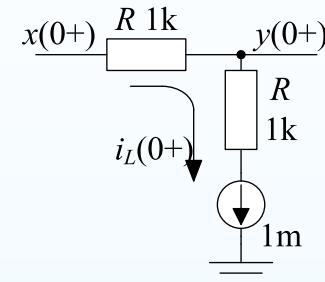

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude

Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Inductor Current Continuity




$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$

At $t = 0+$

$$x - y = 1 \text{ mA} \times 1 \text{ k} = 1$$

$$y(0+) = x(0+) - 1 = 5$$

Time Constant

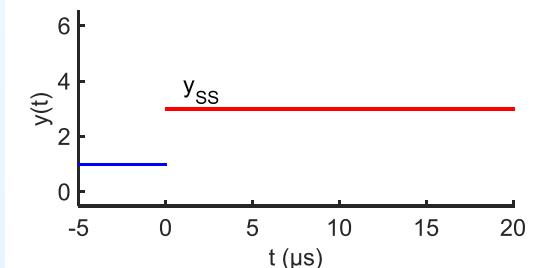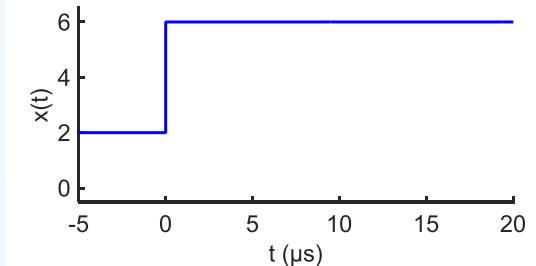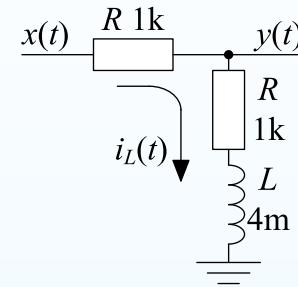

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude

Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Inductor Current Continuity

$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$




At $t = 0+$

$$x - y = 1 \text{ mA} \times 1 \text{ k} = 1$$

$$y(0+) = x(0+) - 1 = 5$$

Time Constant
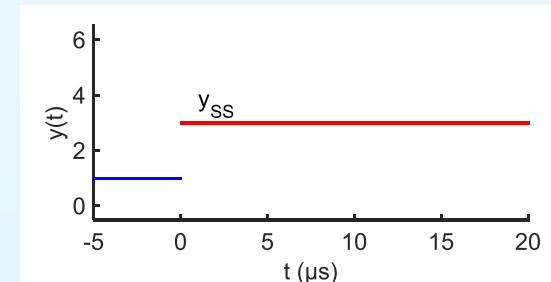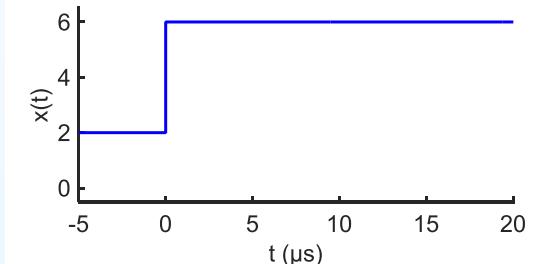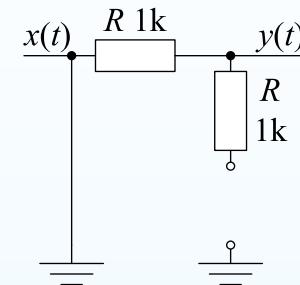
$$\text{Set } x \equiv 0 \rightarrow R_{Th} = 2 \text{ k}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude

Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Inductor Current Continuity

$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$

At $t = 0+$




$$x - y = 1 \text{ mA} \times 1 \text{ k} = 1$$

$$y(0+) = x(0+) - 1 = 5$$

Time Constant

Set $x \equiv 0 \rightarrow R_{Th} = 2 \text{ k}$
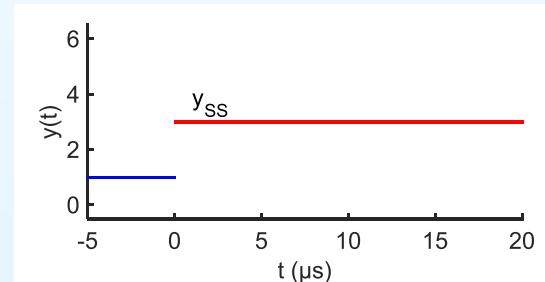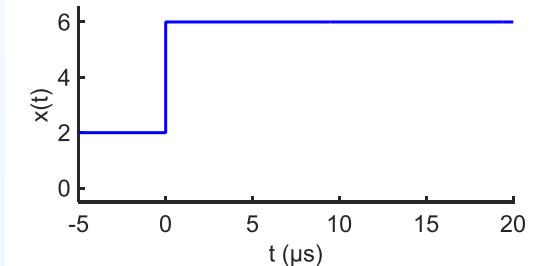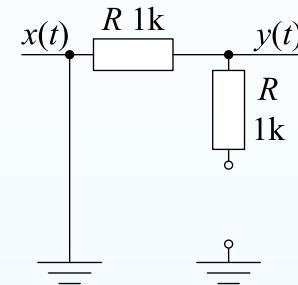
$$\tau = \frac{L}{R_{Th}} = 2 \mu\text{s}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude

Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Inductor Current Continuity

$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$

At $t = 0+$

$$x - y = 1 \text{ mA} \times 1 \text{ k} = 1$$




$$y(0+) = x(0+) - 1 = 5$$

Time Constant

Set $x \equiv 0 \rightarrow R_{Th} = 2 \text{ k}$

$$\tau = \frac{L}{R_{Th}} = 2 \mu\text{s}$$

Result

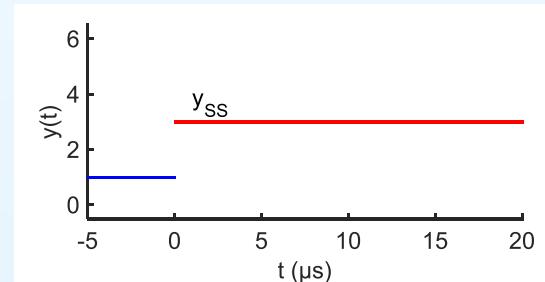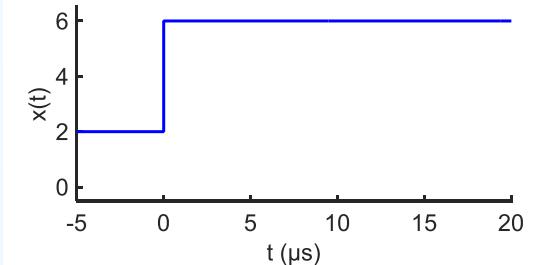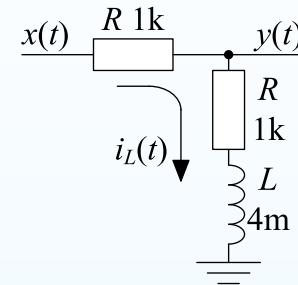

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude

Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Inductor Current Continuity

$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$

At $t = 0+$

$$x - y = 1 \text{ mA} \times 1 \text{ k} = 1$$

$$y(0+) = x(0+) - 1 = 5$$




Time Constant

Set $x \equiv 0 \rightarrow R_{Th} = 2 \text{ k}$

$$\tau = \frac{L}{R_{Th}} = 2 \mu\text{s}$$

Result
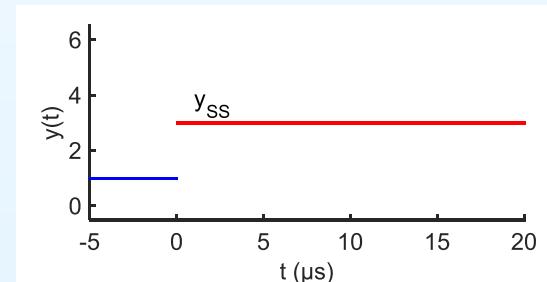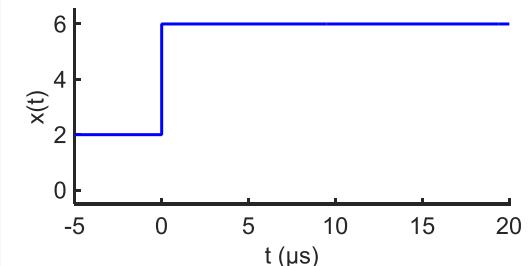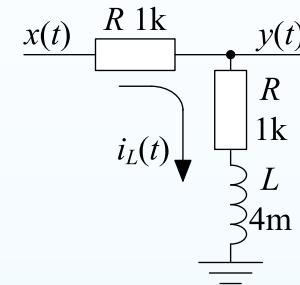
$$y = y_{SS} + (y(0+) - y_{SS}) e^{-t/\tau}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude

Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Inductor Current Continuity

$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$

At $t = 0+$

$$x - y = 1 \text{ mA} \times 1 \text{ k} = 1$$

$$y(0+) = x(0+) - 1 = 5$$




Time Constant

Set $x \equiv 0 \rightarrow R_{Th} = 2 \text{ k}$

$$\tau = \frac{L}{R_{Th}} = 2 \mu\text{s}$$

Result
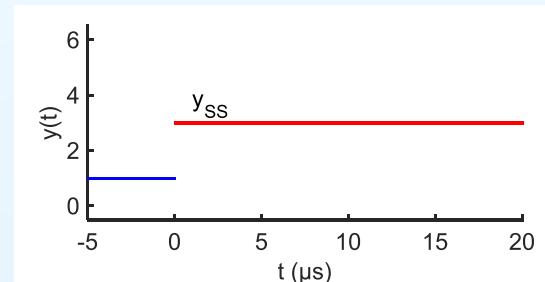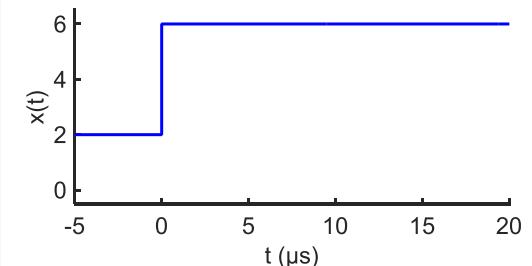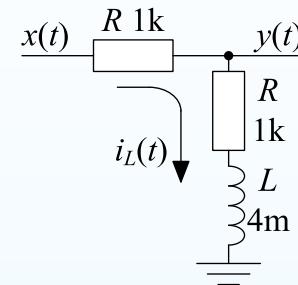
$$\begin{aligned} y &= y_{SS} + (y(0+) - y_{SS}) e^{-t/\tau} \\ &= 3 + (5 - 3) e^{-t/2} \end{aligned}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude

Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Inductor Current Continuity

$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$

At $t = 0+$

$$x - y = 1 \text{ mA} \times 1 \text{ k} = 1$$

$$y(0+) = x(0+) - 1 = 5$$




Time Constant

Set $x \equiv 0 \rightarrow R_{Th} = 2 \text{ k}$

$$\tau = \frac{L}{R_{Th}} = 2 \mu\text{s}$$

Result
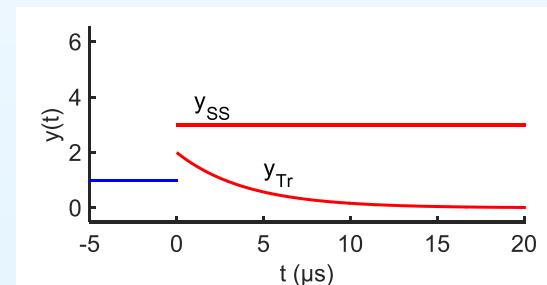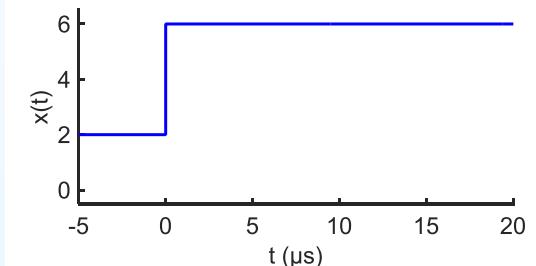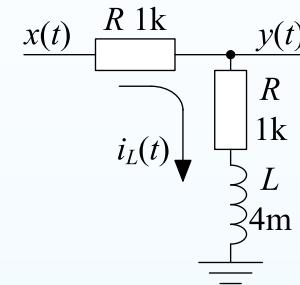
$$\begin{aligned} y &= y_{SS} + (y(0+) - y_{SS}) e^{-t/\tau} \\ &= 3 + (5 - 3) e^{-t/2} \\ &= 3 + 2e^{-t/2} \end{aligned}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Transient Amplitude

Find Steady State (DC $\Rightarrow Z_L = 0$)

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Inductor Current Continuity

$$i_{SS}(0-) = 1 \text{ mA} \Rightarrow i_L(0+) = 1 \text{ mA}$$

At $t = 0+$

$$x - y = 1 \text{ mA} \times 1 \text{ k} = 1$$

$$y(0+) = x(0+) - 1 = 5$$




Time Constant

Set $x \equiv 0 \rightarrow R_{Th} = 2 \text{ k}$

$$\tau = \frac{L}{R_{Th}} = 2 \mu\text{s}$$

Result
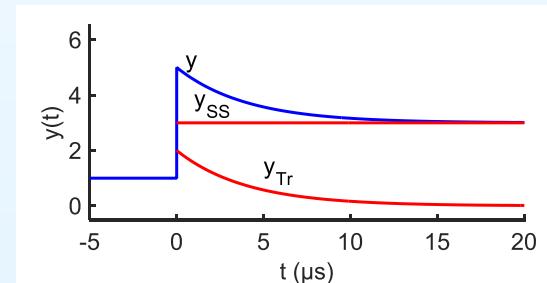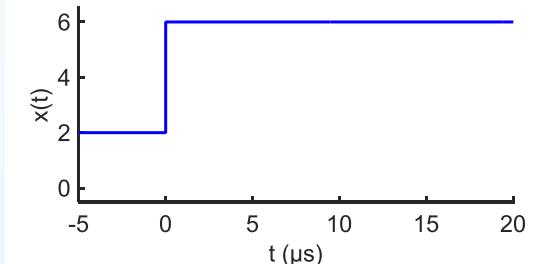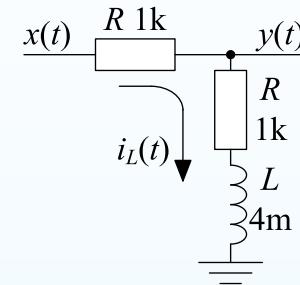
$$\begin{aligned} y &= y_{SS} + (y(0+) - y_{SS}) e^{-t/\tau} \\ &= 3 + (5 - 3) e^{-t/2} \\ &= 3 + 2e^{-t/2} \end{aligned}$$





Capacitor Voltage Continuity

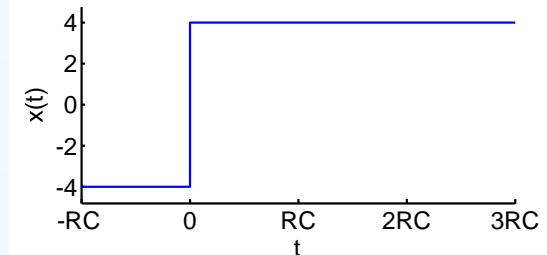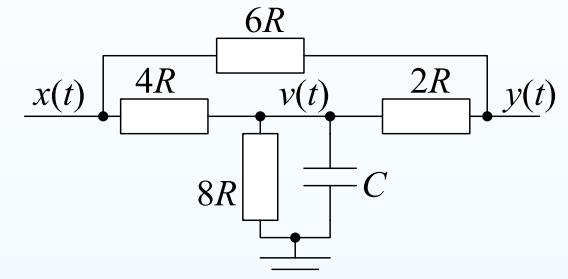15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State ($DC \Rightarrow Z_C = \infty$)





Capacitor Voltage Continuity

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_C = \infty$)
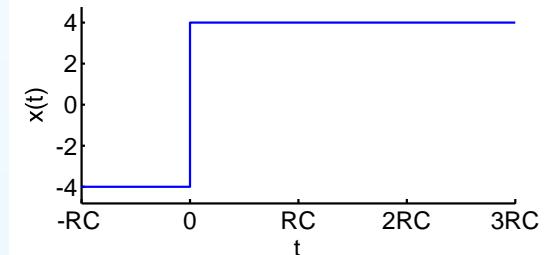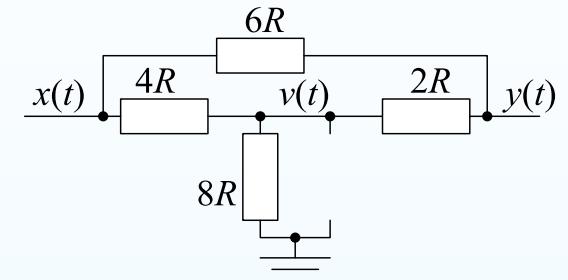
$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$



Capacitor Voltage Continuity



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_C = \infty$)

$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$
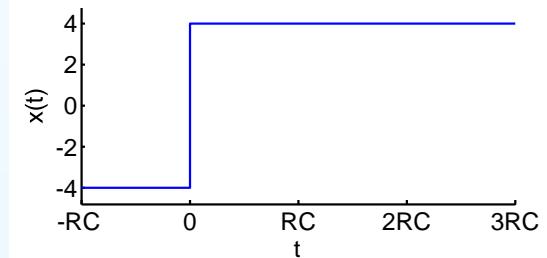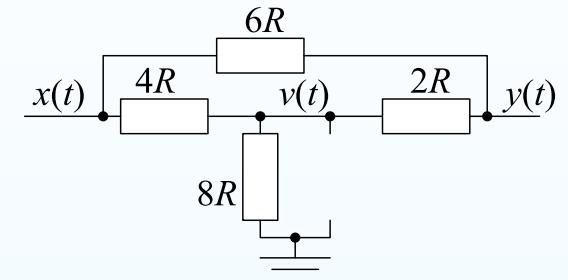
$$\text{KCL @ Y: } \frac{y-v}{2R} + \frac{y-x}{6R} = 0$$



Capacitor Voltage Continuity

15: Transients (A)




- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_C = \infty$)

$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{y-v}{2R} + \frac{y-x}{6R} = 0$$
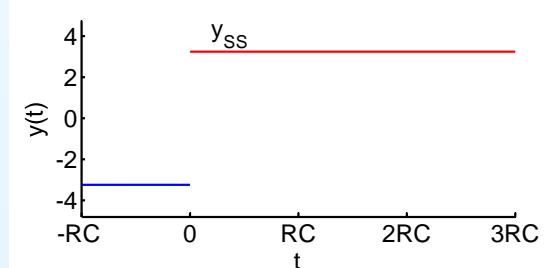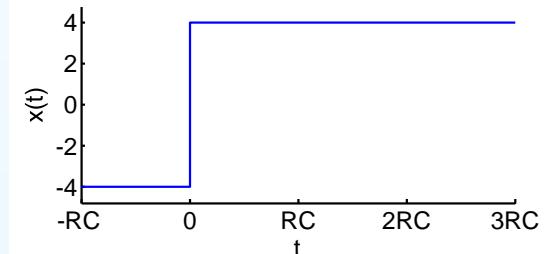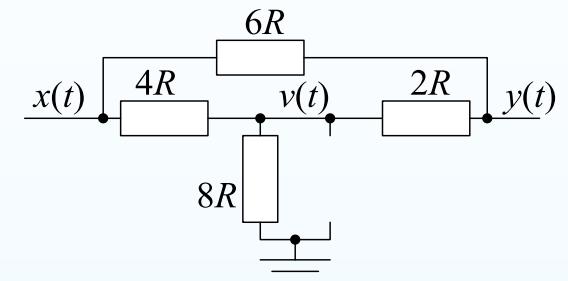
$$v_{SS} = \frac{3}{4}x, y_{SS} = \frac{13}{16}x$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Capacitor Voltage Continuity

Find Steady State (DC $\Rightarrow Z_C = \infty$)




$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{y-v}{2R} + \frac{y-x}{6R} = 0$$

$$v_{SS} = \frac{3}{4}x, y_{SS} = \frac{13}{16}x$$

Capacitor Voltage Continuity
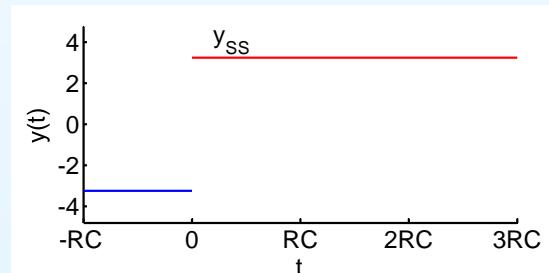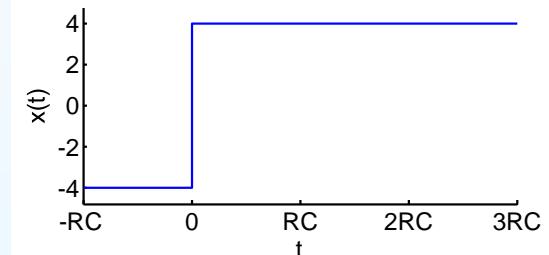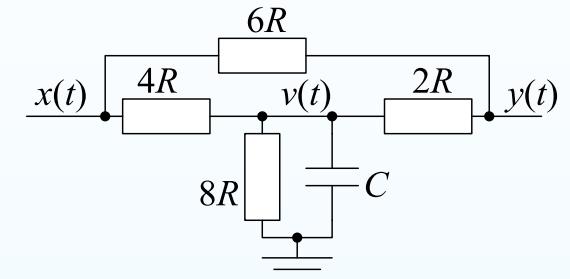
$$v_{SS}(0-) = -3 \Rightarrow v(0+) = -3$$



Capacitor Voltage Continuity

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_C = \infty$)

$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$




$$\text{KCL @ Y: } \frac{y-v}{2R} + \frac{y-x}{6R} = 0$$

$$v_{SS} = \frac{3}{4}x, y_{SS} = \frac{13}{16}x$$

Capacitor Voltage Continuity

$$v_{SS}(0-) = -3 \Rightarrow v(0+) = -3$$

At $t = 0+$: $x = 4$ and $v = -3$

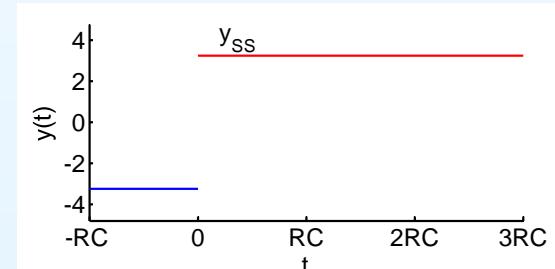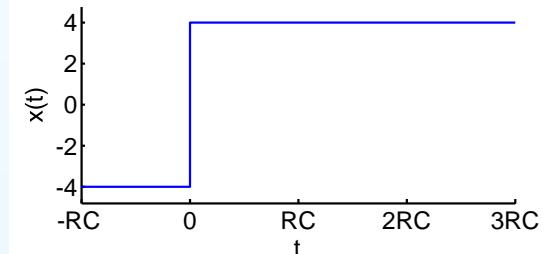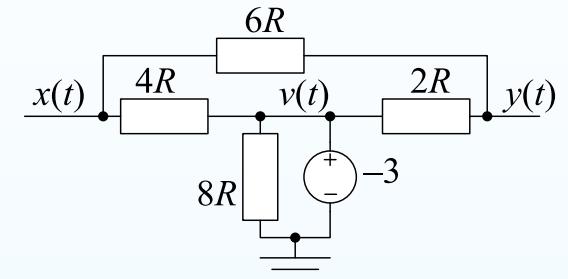

Capacitor Voltage Continuity

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_C = \infty$)

$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{y-v}{2R} + \frac{y-x}{6R} = 0$$




$$v_{SS} = \frac{3}{4}x, y_{SS} = \frac{13}{16}x$$

Capacitor Voltage Continuity

$$v_{SS}(0-) = -3 \Rightarrow v(0+) = -3$$

At $t = 0+$: $x = 4$ and $v = -3$
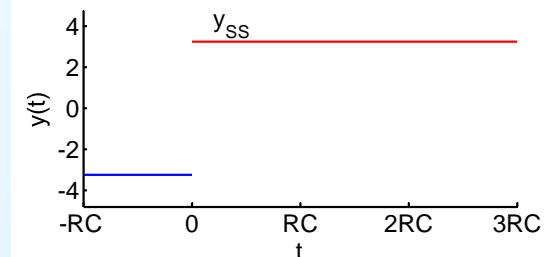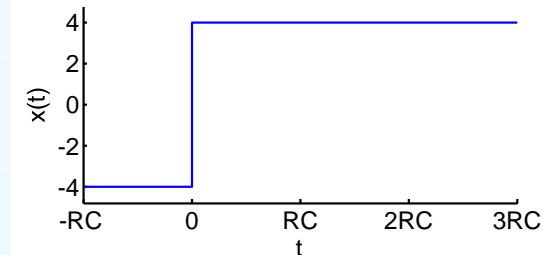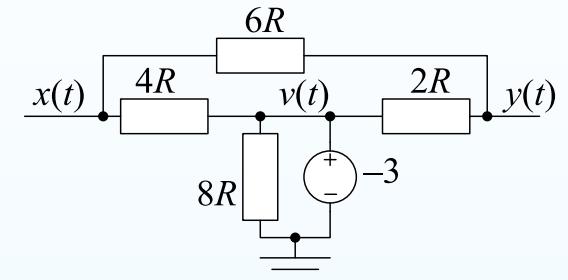
$$\text{KCL @ Y: } \frac{y-(-3)}{2R} + \frac{y-4}{6R} = 0$$



Capacitor Voltage Continuity

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_C = \infty$)

$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{y-v}{2R} + \frac{y-x}{6R} = 0$$

$$v_{SS} = \frac{3}{4}x, y_{SS} = \frac{13}{16}x$$




Capacitor Voltage Continuity

$$v_{SS}(0-) = -3 \Rightarrow v(0+) = -3$$

At $t = 0+$: $x = 4$ and $v = -3$

$$\text{KCL @ Y: } \frac{y-(-3)}{2R} + \frac{y-4}{6R} = 0$$
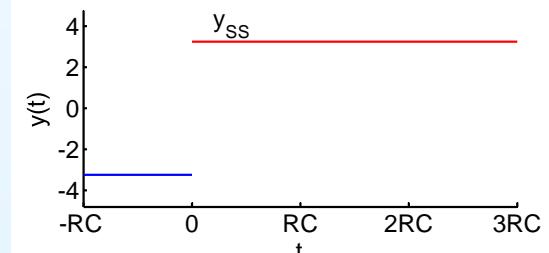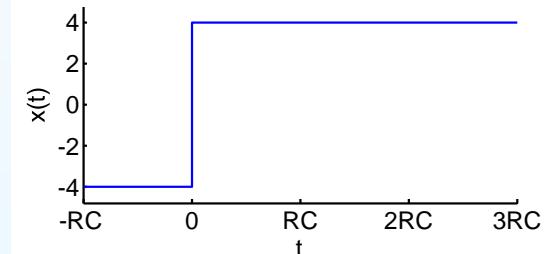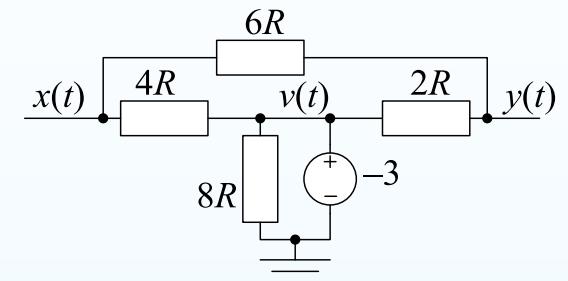
$$y(0+) = \frac{-9+4}{4} = -\frac{5}{4}$$



Capacitor Voltage Continuity

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_C = \infty$)

$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{y-v}{2R} + \frac{y-x}{6R} = 0$$

$$v_{SS} = \frac{3}{4}x, y_{SS} = \frac{13}{16}x$$

Capacitor Voltage Continuity

$$v_{SS}(0-) = -3 \Rightarrow v(0+) = -3$$




At $t = 0+$: $x = 4$ and $v = -3$

$$\text{KCL @ Y: } \frac{y-(-3)}{2R} + \frac{y-4}{6R} = 0$$

$$y(0+) = \frac{-9+4}{4} = -\frac{5}{4}$$

Time Constant
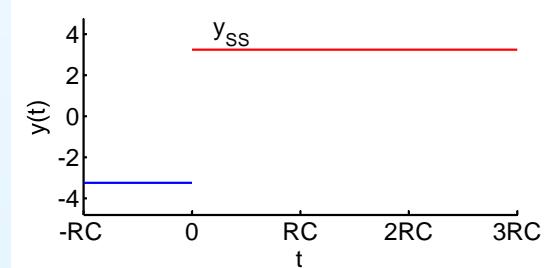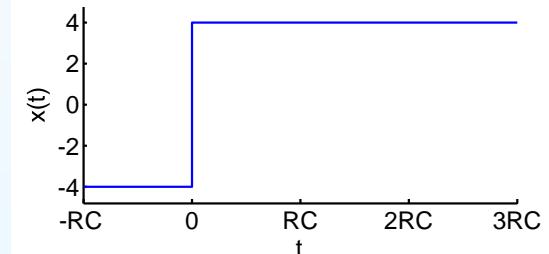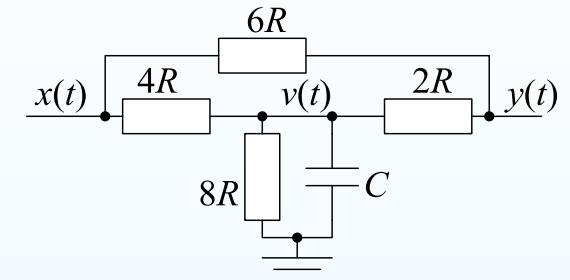
$$\tau = R_{Th}C = 2RC \text{ (from earlier slide)}$$



Capacitor Voltage Continuity

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_C = \infty$)

$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{y-v}{2R} + \frac{y-x}{6R} = 0$$

$$v_{SS} = \frac{3}{4}x, y_{SS} = \frac{13}{16}x$$

Capacitor Voltage Continuity

$$v_{SS}(0-) = -3 \Rightarrow v(0+) = -3$$

At $t = 0+$: $x = 4$ and $v = -3$

$$\text{KCL @ Y: } \frac{y-(-3)}{2R} + \frac{y-4}{6R} = 0$$




$$y(0+) = \frac{-9+4}{4} = -\frac{5}{4}$$

Time Constant

$$\tau = R_{Th}C = 2RC \text{ (from earlier slide)}$$

Result
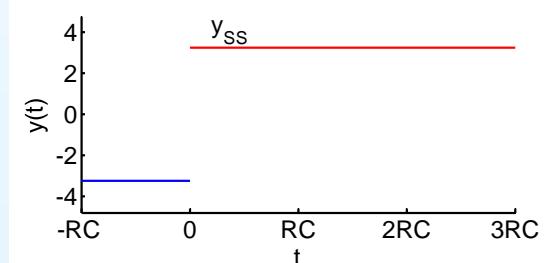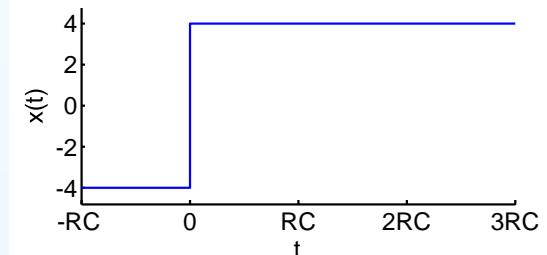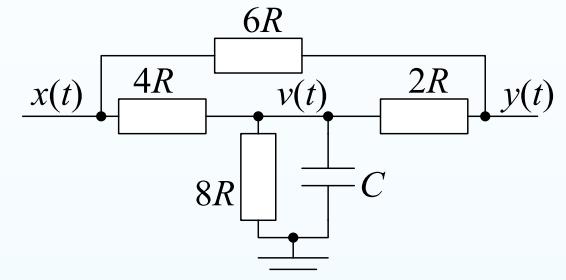
$$y = y_{SS} + (y(0+) - y_{SS}(0+)) e^{-t/\tau}$$



Capacitor Voltage Continuity

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_C = \infty$)

$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{y-v}{2R} + \frac{y-x}{6R} = 0$$

$$v_{SS} = \frac{3}{4}x, y_{SS} = \frac{13}{16}x$$

Capacitor Voltage Continuity

$$v_{SS}(0-) = -3 \Rightarrow v(0+) = -3$$

At $t = 0+$: $x = 4$ and $v = -3$

$$\text{KCL @ Y: } \frac{y-(-3)}{2R} + \frac{y-4}{6R} = 0$$




$$y(0+) = \frac{-9+4}{4} = -\frac{5}{4}$$

Time Constant

$$\tau = R_{Th}C = 2RC \text{ (from earlier slide)}$$

Result
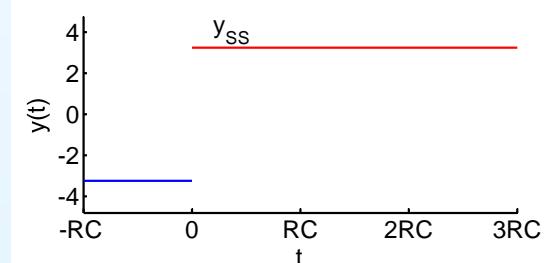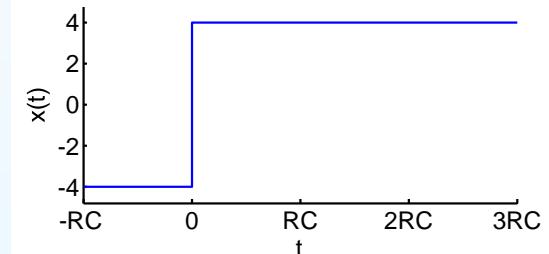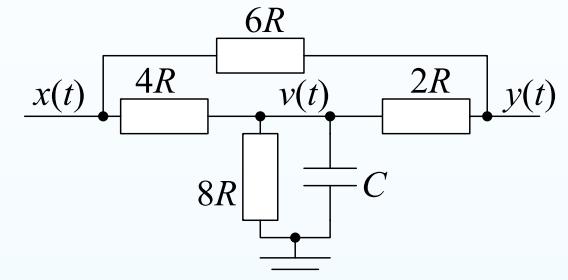
$$\begin{aligned} y &= y_{SS} + (y(0+) - y_{SS}) e^{-t/\tau} \\ &= \frac{13}{4} + \left(-\frac{5}{4} - \frac{13}{4}\right) e^{-t/2RC} \end{aligned}$$



Capacitor Voltage Continuity

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Find Steady State (DC $\Rightarrow Z_C = \infty$)

$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{y-v}{2R} + \frac{y-x}{6R} = 0$$

$$v_{SS} = \frac{3}{4}x, y_{SS} = \frac{13}{16}x$$

Capacitor Voltage Continuity

$$v_{SS}(0-) = -3 \Rightarrow v(0+) = -3$$

At $t = 0+$: $x = 4$ and $v = -3$

$$\text{KCL @ Y: } \frac{y-(-3)}{2R} + \frac{y-4}{6R} = 0$$




$$y(0+) = \frac{-9+4}{4} = -\frac{5}{4}$$

Time Constant

$$\tau = R_{Th}C = 2RC \text{ (from earlier slide)}$$

Result
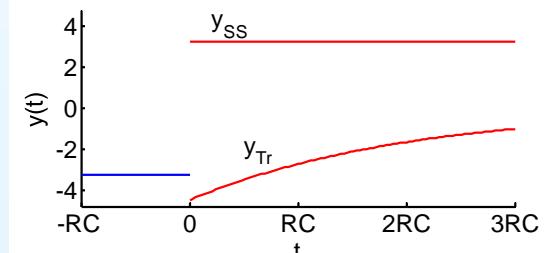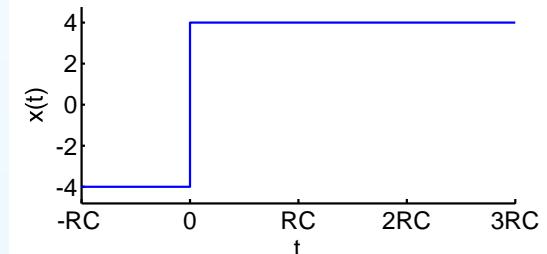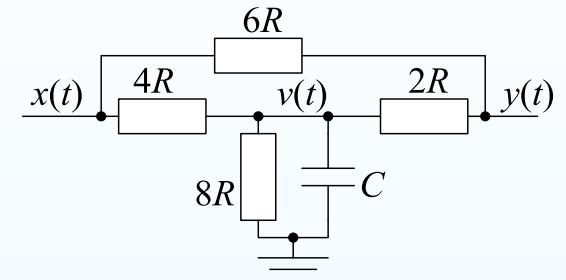
$$\begin{aligned} y &= y_{SS} + (y(0+) - y_{SS}) e^{-t/\tau} \\ &= \frac{13}{4} + \left(-\frac{5}{4} - \frac{13}{4}\right) e^{-t/\tau} \\ &= \frac{13}{4} - \frac{18}{4} e^{-t/\tau} = 3\frac{1}{4} - 4\frac{1}{2} e^{-t/2RC} \end{aligned}$$



15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity**
- Summary

Capacitor Voltage Continuity

Find Steady State (DC $\Rightarrow Z_C = \infty$)

$$\text{KCL @ V: } \frac{v-x}{4R} + \frac{v}{8R} + \frac{v-y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{y-v}{2R} + \frac{y-x}{6R} = 0$$

$$v_{SS} = \frac{3}{4}x, y_{SS} = \frac{13}{16}x$$

Capacitor Voltage Continuity

$$v_{SS}(0-) = -3 \Rightarrow v(0+) = -3$$

At $t = 0+$: $x = 4$ and $v = -3$

$$\text{KCL @ Y: } \frac{y-(-3)}{2R} + \frac{y-4}{6R} = 0$$




$$y(0+) = \frac{-9+4}{4} = -\frac{5}{4}$$

Time Constant

$$\tau = R_{Th}C = 2RC \text{ (from earlier slide)}$$

Result
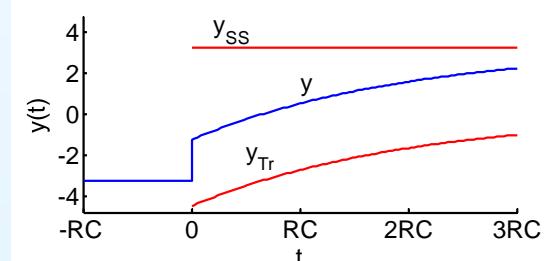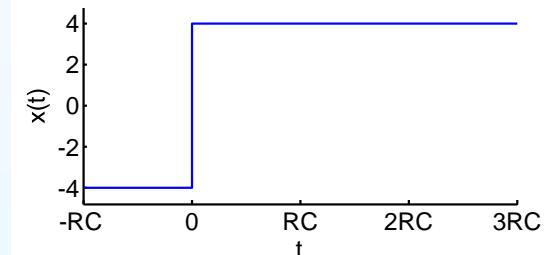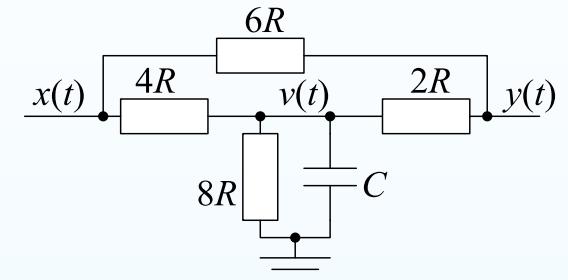
$$\begin{aligned} y &= y_{SS} + (y(0+) - y_{SS}(0+)) e^{-t/\tau} \\ &= \frac{13}{4} + \left(-\frac{5}{4} - \frac{13}{4}\right) e^{-t/\tau} \\ &= \frac{13}{4} - \frac{18}{4} e^{-t/\tau} = 3\frac{1}{4} - 4\frac{1}{2} e^{-t/2RC} \end{aligned}$$



Summary

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

- 1st order circuits: include one C or one L .
 - v_C or i_L never change abruptly. The output, y , is not necessarily continuous unless it equals v_C .

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity
- Summary

Summary

- 1st order circuits: include one C or one L .
 - v_C or i_L never change abruptly. The output, y , is not necessarily continuous unless it equals v_C .
- Circuit time constant: $\tau = R_{Th}C$ or $\frac{L}{R_{Th}}$
 - R_{Th} is the Thévenin resistance seen by C or L .
 - Same τ for all voltages and currents.

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity

● **Summary**

Summary

- 1st order circuits: include one C or one L .
 - v_C or i_L never change abruptly. The output, y , is not necessarily continuous unless it equals v_C .
- Circuit time constant: $\tau = R_{Th}C$ or $\frac{L}{R_{Th}}$
 - R_{Th} is the Thévenin resistance seen by C or L .
 - Same τ for all voltages and currents.
- Output = Steady State + Transient
 - **Steady State:** use nodal/Phasor analysis when input is piecewise constant or piecewise sinusoidal. The steady state has the **same frequency as the input signal**.

Summary

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity

● Summary

- 1st order circuits: include one C or one L .
 - v_C or i_L never change abruptly. The output, y , is not necessarily continuous unless it equals v_C .
- Circuit time constant: $\tau = R_{Th}C$ or $\frac{L}{R_{Th}}$
 - R_{Th} is the Thévenin resistance seen by C or L .
 - Same τ for all voltages and currents.
- Output = Steady State + Transient
 - **Steady State:** use nodal/Phasor analysis when input is piecewise constant or piecewise sinusoidal. The steady state has the **same frequency as the input signal**.
 - **Transient:** Find $v_C(0-)$ or $i_L(0-)$: unchanged at $t = 0+$
Find $y(0+)$ assuming source of $v_C(0+)$ or $i_L(0+)$
Amplitude **never** complex, **never** depends on t .

Summary

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity

● Summary

- 1st order circuits: include one C or one L .
 - v_C or i_L never change abruptly. The output, y , is not necessarily continuous unless it equals v_C .
- Circuit time constant: $\tau = R_{Th}C$ or $\frac{L}{R_{Th}}$
 - R_{Th} is the Thévenin resistance seen by C or L .
 - Same τ for all voltages and currents.
- Output = Steady State + Transient
 - **Steady State:** use nodal/Phasor analysis when input is piecewise constant or piecewise sinusoidal. The steady state has the **same frequency as the input signal**.
 - **Transient:** Find $v_C(0-)$ or $i_L(0-)$: unchanged at $t = 0+$
Find $y(0+)$ assuming source of $v_C(0+)$ or $i_L(0+)$
Amplitude **never** complex, **never** depends on t .
 - $y(t) = y_{SS}(t) + (y(0+) - y_{SS}(0+)) e^{-t/\tau}$

Summary

15: Transients (A)

- Differential Equation
- Piecewise steady state inputs
- Step Input
- Negative exponentials
- Exponential Time Delays
- Inductor Transients
- Linearity
- Transient Amplitude
- Capacitor Voltage Continuity

● Summary

- 1st order circuits: include one C or one L .
 - v_C or i_L never change abruptly. The output, y , is not necessarily continuous unless it equals v_C .
- Circuit time constant: $\tau = R_{Th}C$ or $\frac{L}{R_{Th}}$
 - R_{Th} is the Thévenin resistance seen by C or L .
 - Same τ for all voltages and currents.
- Output = Steady State + Transient
 - **Steady State:** use nodal/Phasor analysis when input is piecewise constant or piecewise sinusoidal. The steady state has the **same frequency as the input signal**.
 - **Transient:** Find $v_C(0-)$ or $i_L(0-)$: unchanged at $t = 0+$
Find $y(0+)$ assuming source of $v_C(0+)$ or $i_L(0+)$
Amplitude **never** complex, **never** depends on t .
 - $y(t) = y_{SS}(t) + (y(0+) - y_{SS}(0+)) e^{-t/\tau}$

See Hayt Ch 8 or Irwin Ch 7.