

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

16: Transients (B)


Piecewise steady state inputs

16: Transients (B)

● Piecewise steady state inputs

- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

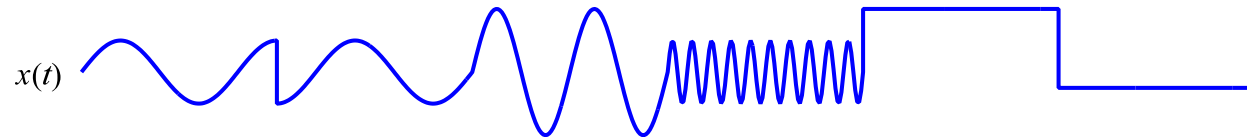We will consider input signals that are sinusoidal or constant for a particular time interval and then suddenly change in amplitude, phase or frequency.



Piecewise steady state inputs

16: Transients (B)


● Piecewise steady state inputs

- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary


We will consider input signals that are sinusoidal or constant for a particular time interval and then suddenly change in amplitude, phase or frequency.

Output is the sum of the steady state and a transient:

$$y(t) = y_{SS}(t) + y_{Tr}(t)$$

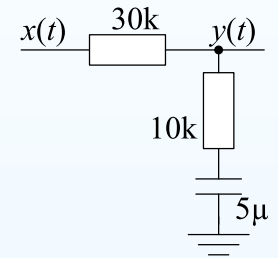

[only one C or L]

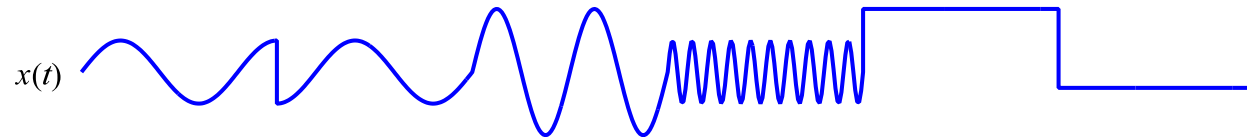

Piecewise steady state inputs

16: Transients (B)

● Piecewise steady state inputs


- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

We will consider input signals that are sinusoidal or constant for a particular time interval and then suddenly change in amplitude, phase or frequency.


Output is the sum of the steady state and a transient:

$$y(t) = y_{SS}(t) + y_{Tr}(t)$$

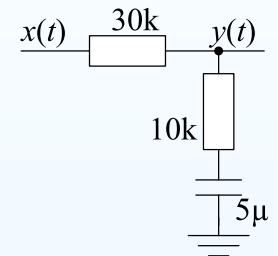Steady state, $y_{SS}(t)$, is the same frequency as the input; use phasors + nodal analysis.



[only one C or L]

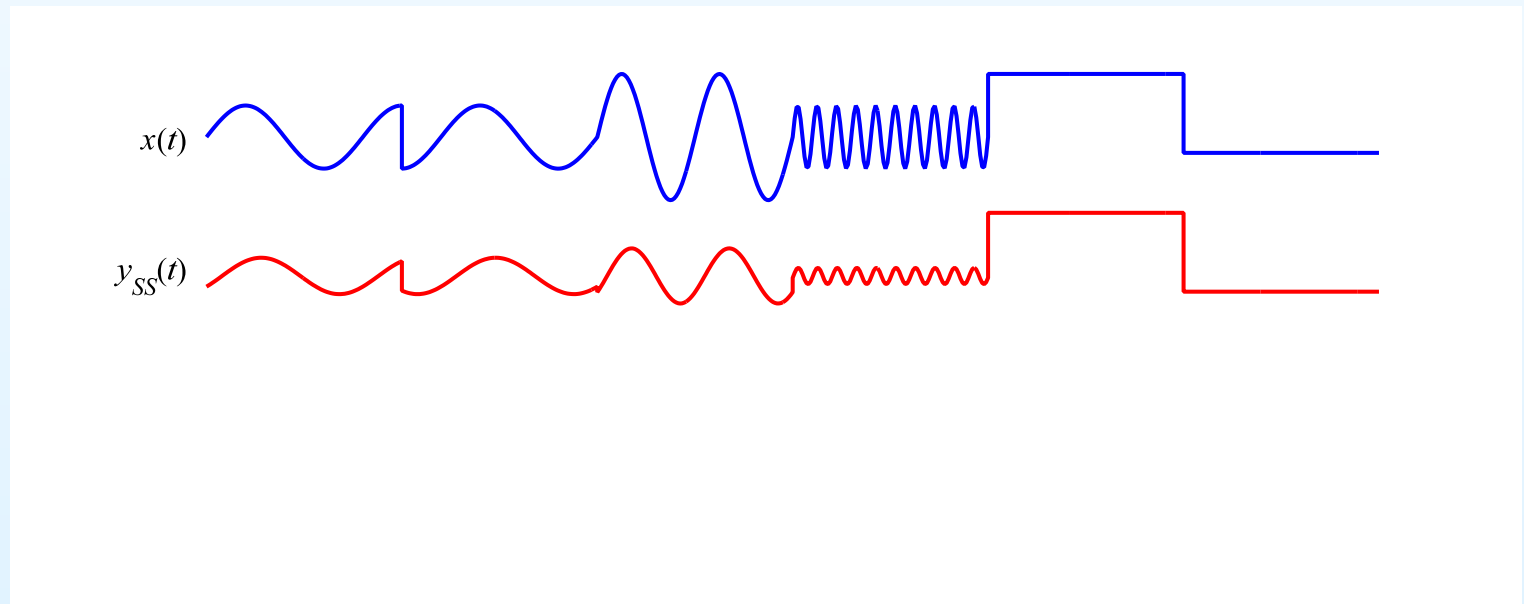

Piecewise steady state inputs

16: Transients (B)

● Piecewise steady state inputs

- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary


We will consider input signals that are sinusoidal or constant for a particular time interval and then suddenly change in amplitude, phase or frequency.

Output is the sum of the steady state and a transient:


$$y(t) = y_{SS}(t) + y_{Tr}(t)$$

Steady state, $y_{SS}(t)$, is the same frequency as the input; use phasors + nodal analysis.

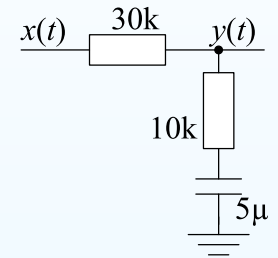Transient is always $y_{Tr}(t) = Ae^{-\frac{t}{\tau}}$ at each change.



[only one C or L]

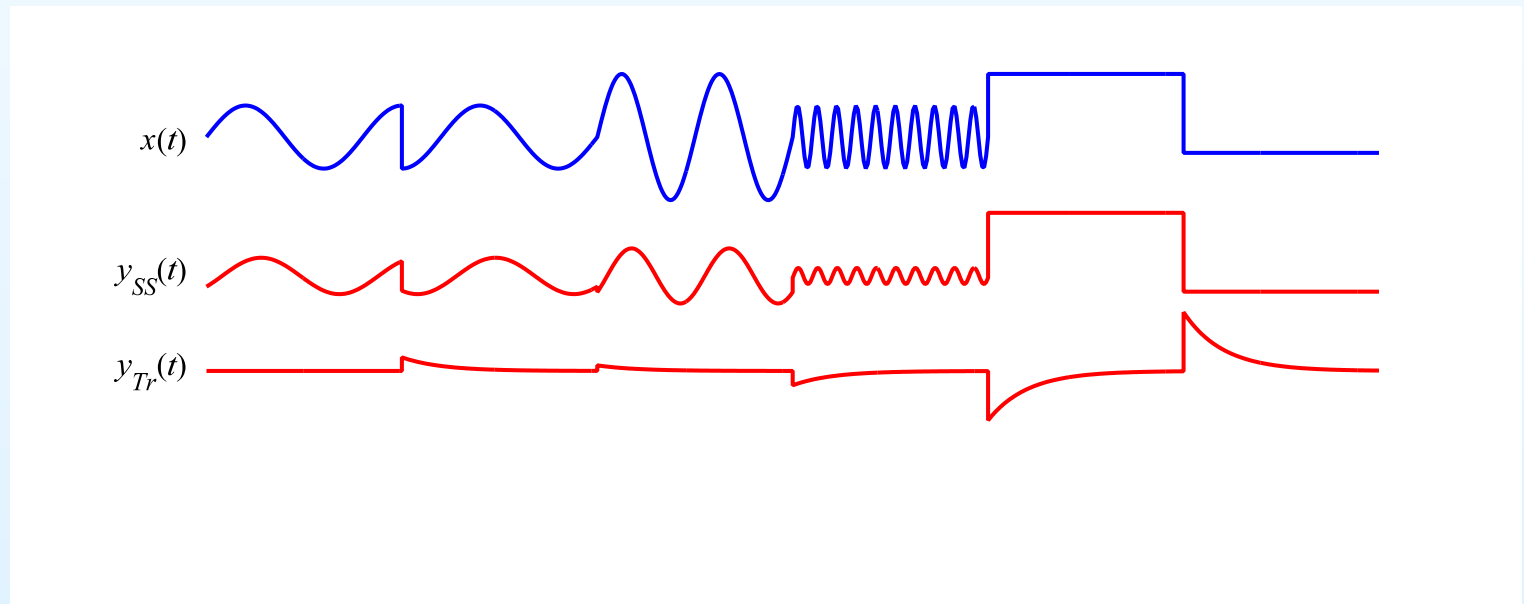

Piecewise steady state inputs

16: Transients (B)

● Piecewise steady state inputs

- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary


We will consider input signals that are sinusoidal or constant for a particular time interval and then suddenly change in amplitude, phase or frequency.

Output is the sum of the steady state and a transient:


$$y(t) = y_{SS}(t) + y_{Tr}(t)$$

Steady state, $y_{SS}(t)$, is the same frequency as the input; use phasors + nodal analysis.

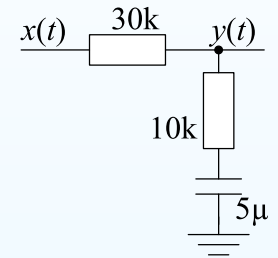Transient is always $y_{Tr}(t) = Ae^{-\frac{t}{\tau}}$ at each change.



[only one C or L]

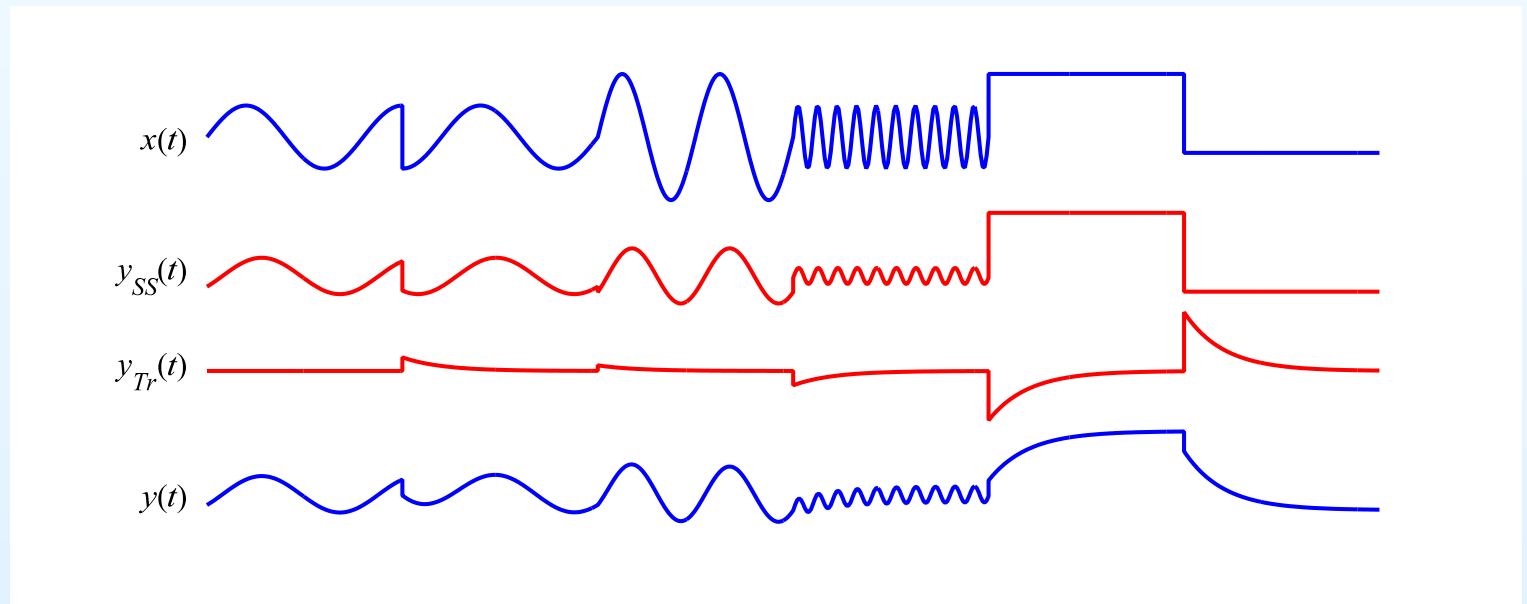

Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs

- **Sinusoidal Input**

- Multiple Discontinuities

- Switched Circuit

- Transfer Function

- Transient from Transfer Function



- Opamp Circuit Transient

- Summary

For $t < 0$: $y(t) = x(t) = 0$

For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$

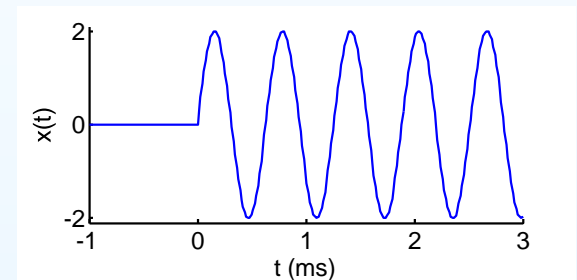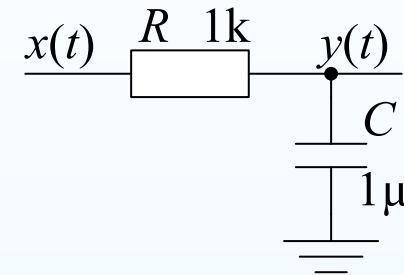$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$



Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs
- **Sinusoidal Input**
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary



For $t < 0$: $y(t) = x(t) = 0$

For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$

$$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$$

Steady State (for $t \geq 0$)
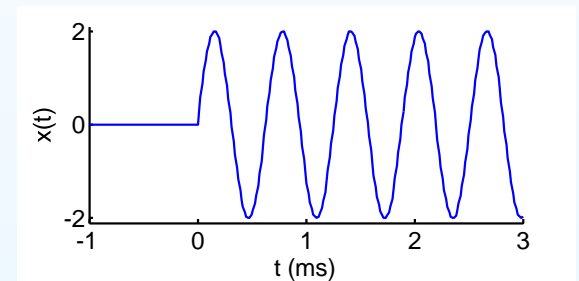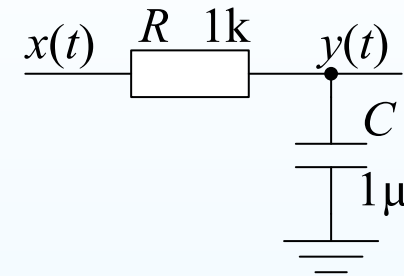
$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$



Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs
- **Sinusoidal Input**
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

For $t < 0$: $y(t) = x(t) = 0$



For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$

$$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$
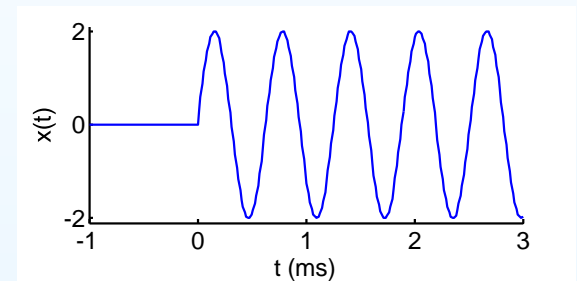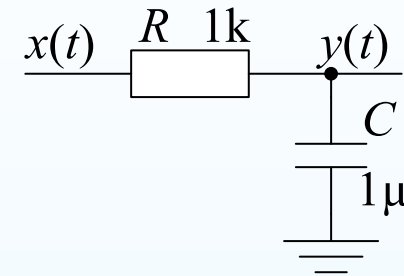
$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$



Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

For $t < 0$: $y(t) = x(t) = 0$

For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$



$$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$
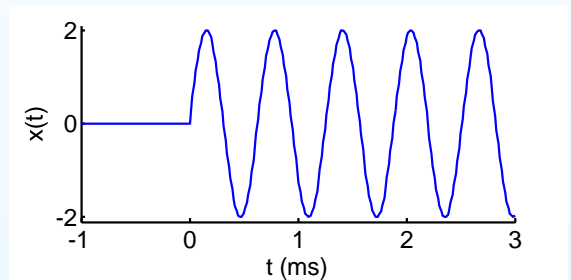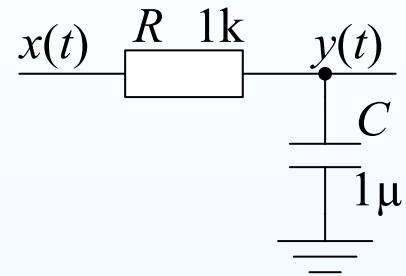
$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$



Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

For $t < 0$: $y(t) = x(t) = 0$

For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$




$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$
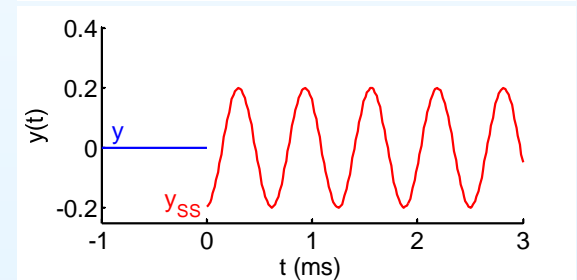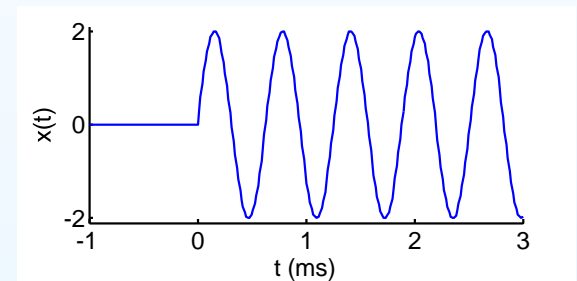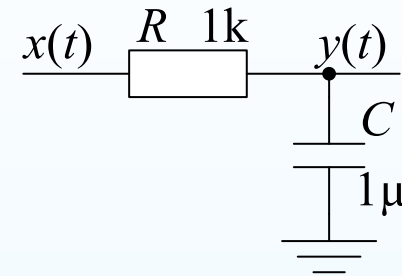
$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$



Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

$$\text{For } t < 0: y(t) = x(t) = 0$$

$$\text{For } t \geq 0: x = 2 \sin \omega t \Rightarrow X = -2j$$

$$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$$

Steady State (for $t \geq 0$)




$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$

$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$

Steady State + Transient
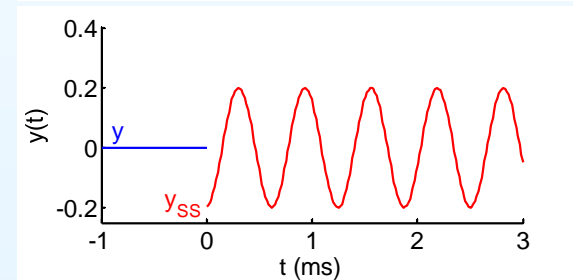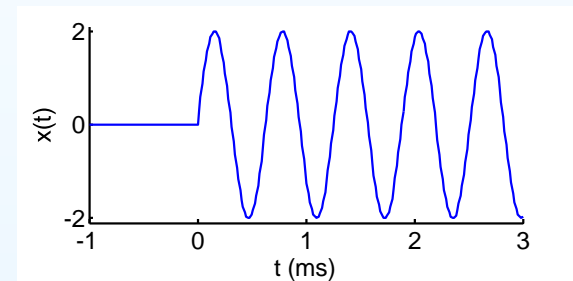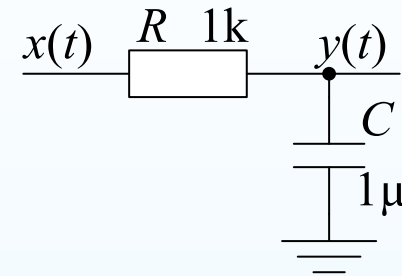
$$y(t) = 0.2 \cos(\omega t - 174^\circ) + Ae^{-t/\tau}$$



Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs

- **Sinusoidal Input**

- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function

- Opamp Circuit Transient
- Summary

For $t < 0$: $y(t) = x(t) = 0$

For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$

$$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$




$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$

Steady State + Transient

$$y(t) = 0.2 \cos(\omega t - 174^\circ) + Ae^{-t/\tau}$$

Transient Amplitude

$$y(0+) = 0.2 \cos(-174^\circ) + A$$

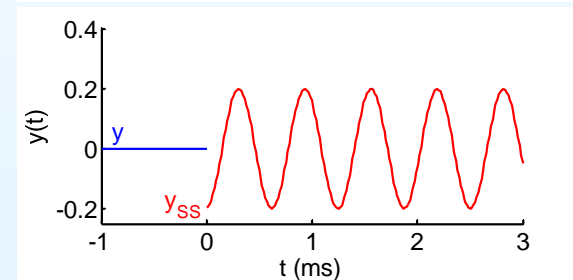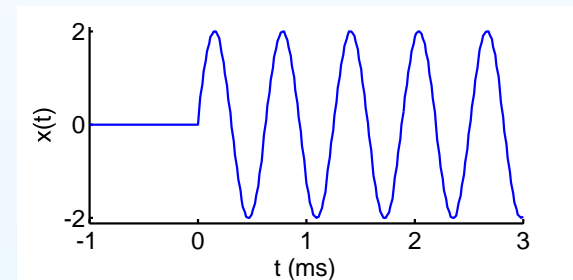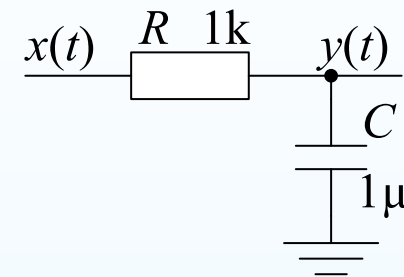

Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

$$\text{For } t < 0: y(t) = x(t) = 0$$

$$\text{For } t \geq 0: x = 2 \sin \omega t \Rightarrow X = -2j$$

$$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$




$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$

Steady State + Transient

$$y(t) = 0.2 \cos(\omega t - 174^\circ) + Ae^{-t/\tau}$$

Transient Amplitude
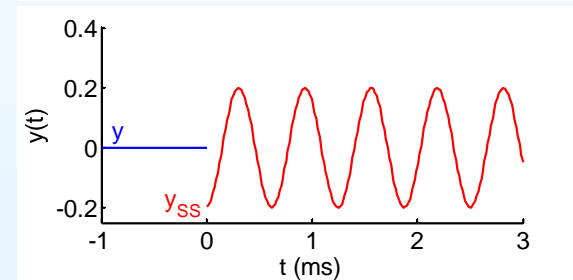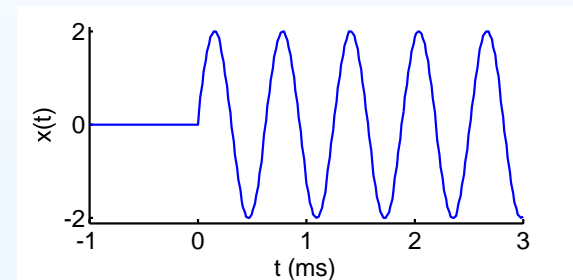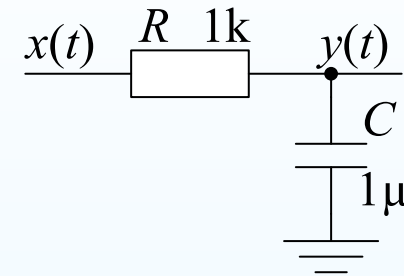
$$\begin{aligned} y(0+) &= 0.2 \cos(-174^\circ) + A \\ &= -0.198 + A \end{aligned}$$



Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs

- **Sinusoidal Input**

- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function

- Opamp Circuit Transient
- Summary

For $t < 0$: $y(t) = x(t) = 0$

For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$

$$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$

$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$




Steady State + Transient

$$y(t) = 0.2 \cos(\omega t - 174^\circ) + Ae^{-t/\tau}$$

Transient Amplitude

$$\begin{aligned} y(0+) &= 0.2 \cos(-174^\circ) + A \\ &= -0.198 + A \end{aligned}$$

$$y(0+) = y(0-) = 0$$

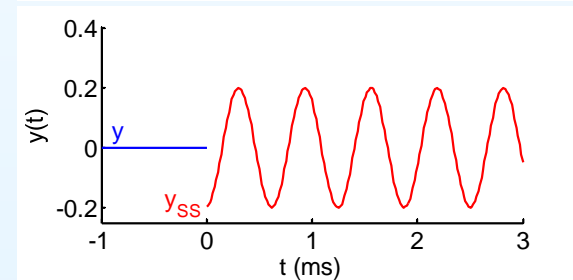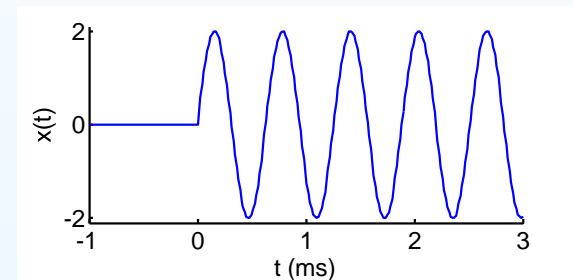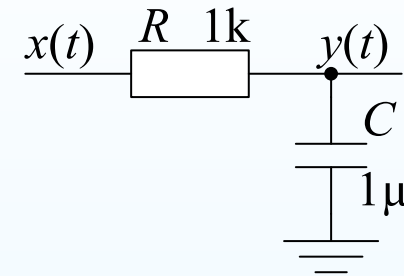

Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

$$\text{For } t < 0: y(t) = x(t) = 0$$

$$\text{For } t \geq 0: x = 2 \sin \omega t \Rightarrow X = -2j$$

$$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$

$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$




Steady State + Transient

$$y(t) = 0.2 \cos(\omega t - 174^\circ) + Ae^{-t/\tau}$$

Transient Amplitude

$$\begin{aligned} y(0+) &= 0.2 \cos(-174^\circ) + A \\ &= -0.198 + A \end{aligned}$$
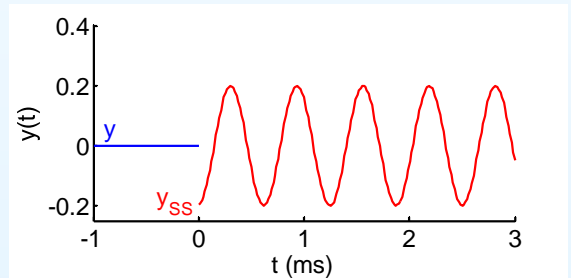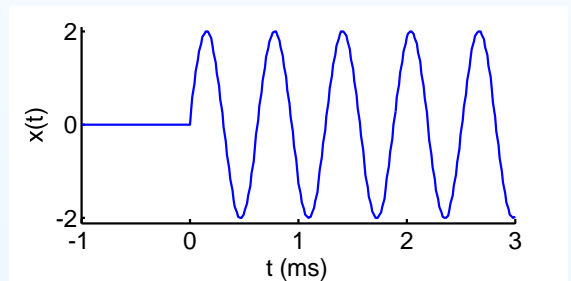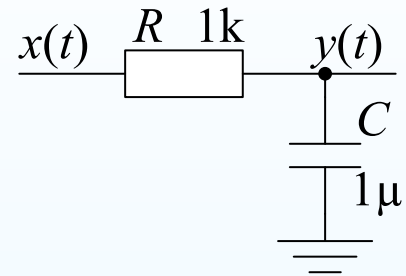
$$y(0+) = y(0-) = 0 \Rightarrow A = 0.198$$



Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

For $t < 0$: $y(t) = x(t) = 0$

For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$

$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$

$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$




Steady State + Transient

$$y(t) = 0.2 \cos(\omega t - 174^\circ) + Ae^{-t/\tau}$$

Transient Amplitude

$$\begin{aligned} y(0+) &= 0.2 \cos(-174^\circ) + A \\ &= -0.198 + A \end{aligned}$$
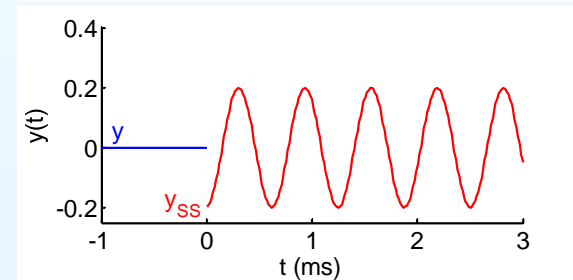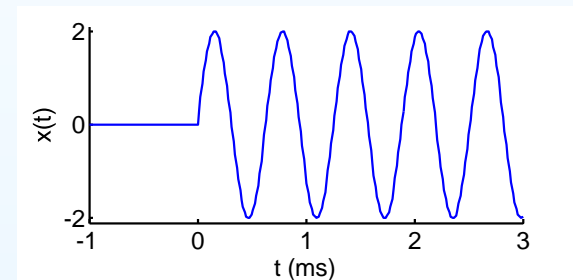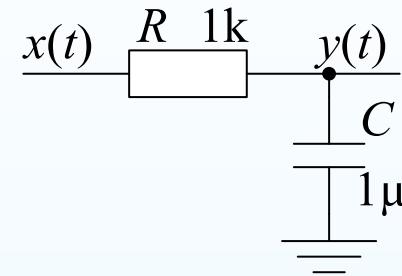
$$y(0+) = y(0-) = 0 \Rightarrow A = 0.198 \Rightarrow y_{Tr}(t) = 0.198e^{-t/\tau}$$



Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

For $t < 0$: $y(t) = x(t) = 0$

For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$

$$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$

$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$




Steady State + Transient

$$y(t) = 0.2 \cos(\omega t - 174^\circ) + Ae^{-t/\tau}$$

Transient Amplitude

$$\begin{aligned} y(0+) &= 0.2 \cos(-174^\circ) + A \\ &= -0.198 + A \end{aligned}$$
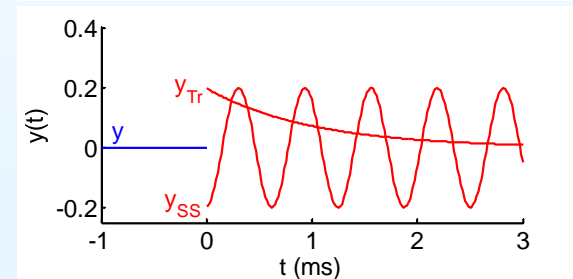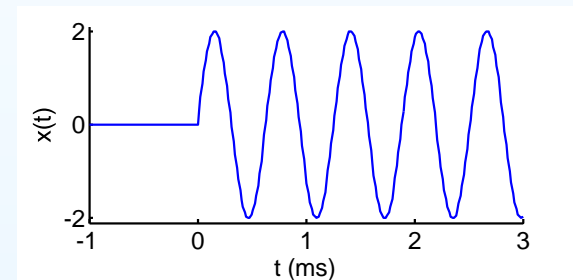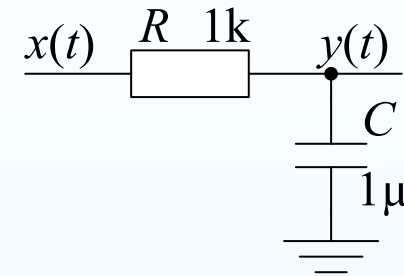
$$y(0+) = y(0-) = 0 \Rightarrow A = 0.198 \Rightarrow y_{Tr}(t) = 0.198e^{-t/\tau}$$



Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

For $t < 0$: $y(t) = x(t) = 0$

For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$

$$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$

$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$

Steady State + Transient

$$y(t) = 0.2 \cos(\omega t - 174^\circ) + Ae^{-t/\tau}$$




Transient Amplitude

$$\begin{aligned} y(0+) &= 0.2 \cos(-174^\circ) + A \\ &= -0.198 + A \end{aligned}$$

$$y(0+) = y(0-) = 0 \Rightarrow A = 0.198 \Rightarrow y_{Tr}(t) = 0.198e^{-t/\tau}$$

Complete Expression for $y(t)$
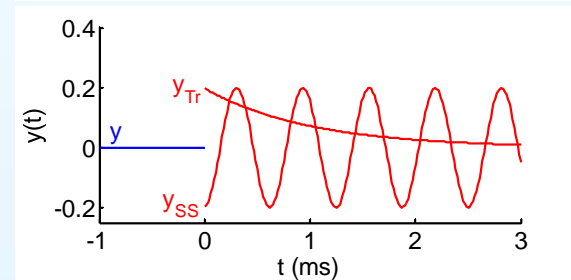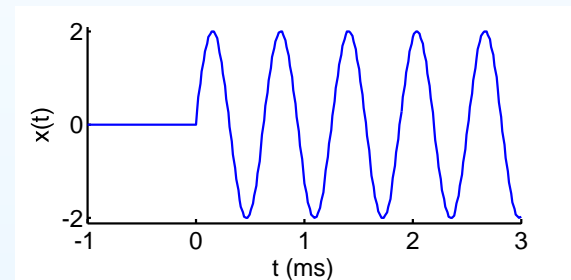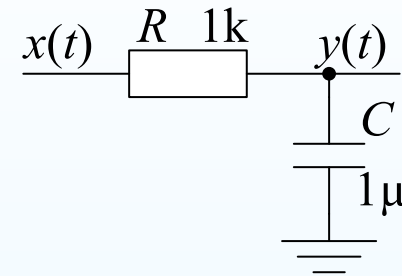
$$y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$$



Sinusoidal Input

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

For $t < 0$: $y(t) = x(t) = 0$

For $t \geq 0$: $x = 2 \sin \omega t \Rightarrow X = -2j$

$\tau = RC = 1 \text{ ms}, \omega = 10 \text{ krad/s}$

Steady State (for $t \geq 0$)

$$\frac{Y}{X} = \frac{1}{j\omega RC + 1} = 0.1 \angle -84^\circ$$

$$Y = X \times \frac{Y}{X} = -2j \times 0.1 \angle -84^\circ$$

$$y_{SS}(t) = 0.2 \cos(\omega t - 174^\circ)$$

Steady State + Transient

$$y(t) = 0.2 \cos(\omega t - 174^\circ) + Ae^{-t/\tau}$$




Transient Amplitude

$$\begin{aligned} y(0+) &= 0.2 \cos(-174^\circ) + A \\ &= -0.198 + A \end{aligned}$$

$$y(0+) = y(0-) = 0 \Rightarrow A = 0.198 \Rightarrow y_{Tr}(t) = 0.198e^{-t/\tau}$$



Complete Expression for $y(t)$
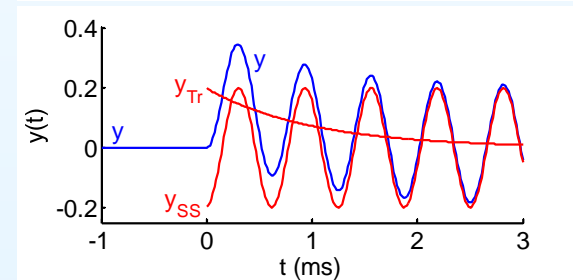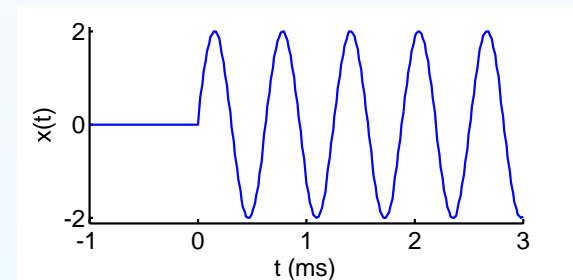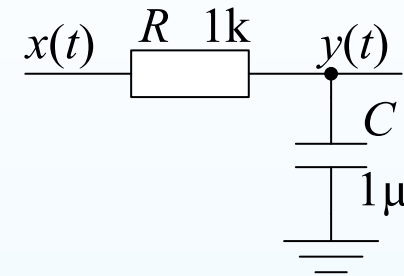
$$y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$$



Multiple Discontinuities

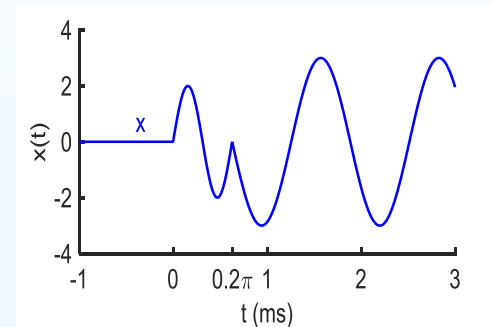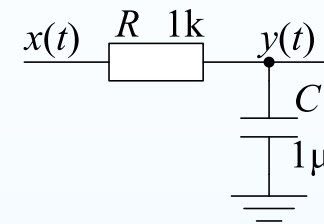For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$





Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)
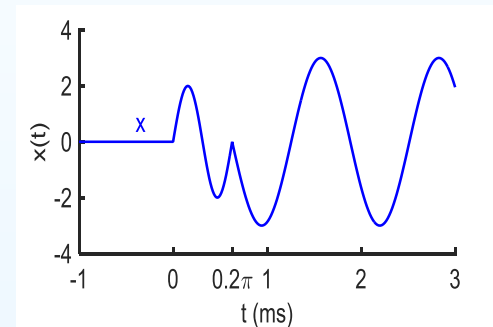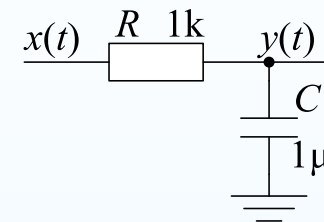
$$X = -3j, \omega_2 = 5 \text{ k}$$
$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$



Multiple Discontinuities



For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$
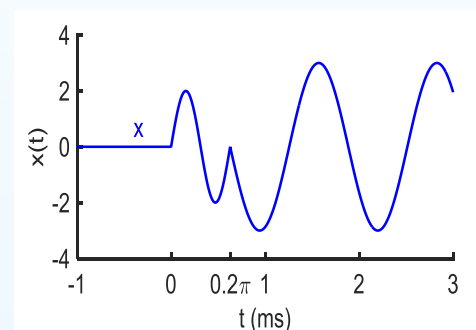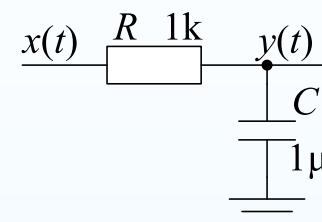
$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$



Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$
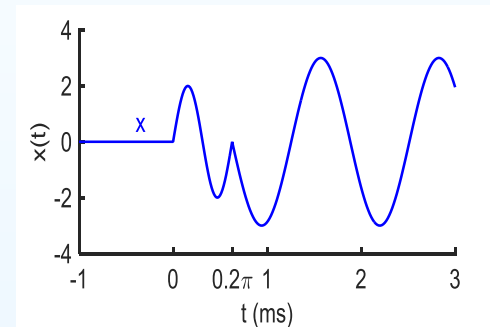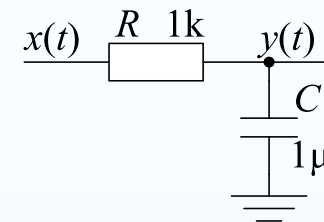
$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$




Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$
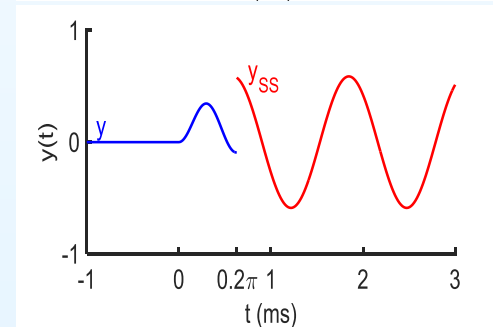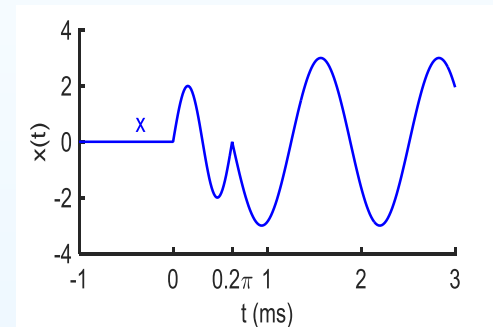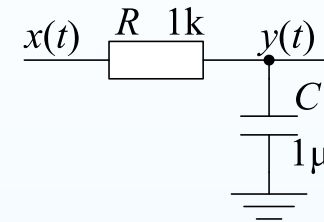
$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
 prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$




$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$

$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$

Steady State + Transient (for $t \geq 0.63$ ms)
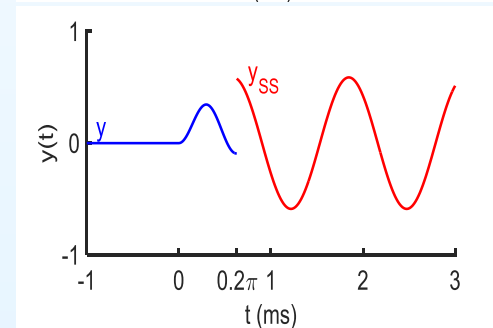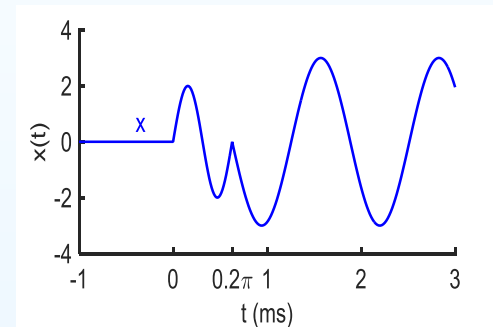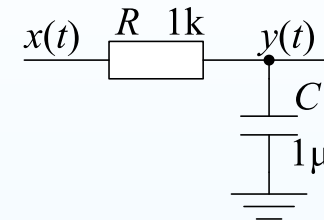
$$y = 0.59 \cos(\omega_2 t - 169^\circ) + Be^{-(t-0.00063)/\tau}$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
 prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$




$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$

Steady State + Transient (for $t \geq 0.63$ ms)

$$y = 0.59 \cos(\omega_2 t - 169^\circ) + B e^{-(t-0.00063)/\tau}$$

Transient Amplitude (at $t = 0.63$ ms)
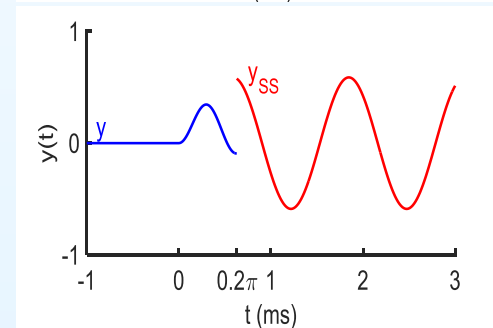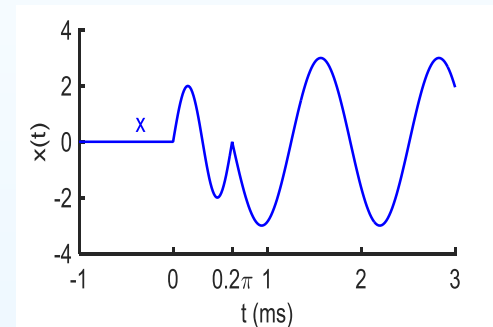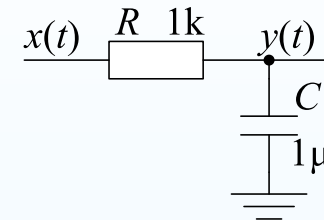
$$y(0.00063+) = 0.59 \cos(0.00063\omega_2 - 169^\circ) + B$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
 prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$




$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$

Steady State + Transient (for $t \geq 0.63$ ms)

$$y = 0.59 \cos(\omega_2 t - 169^\circ) + B e^{-(t-0.00063)/\tau}$$

Transient Amplitude (at $t = 0.63$ ms)
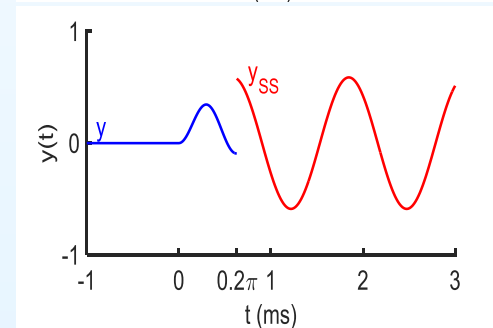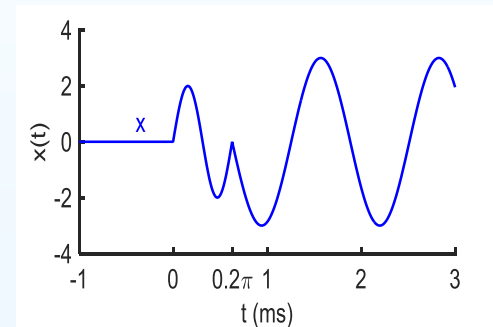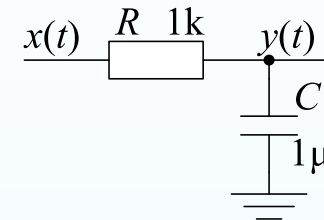
$$\begin{aligned} y(0.00063+) &= 0.59 \cos(0.00063\omega_2 - 169^\circ) + B \\ &= 0.577 + B \end{aligned}$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
 prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$

$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$




Steady State + Transient (for $t \geq 0.63$ ms)

$$y = 0.59 \cos(\omega_2 t - 169^\circ) + B e^{-(t-0.00063)/\tau}$$

Transient Amplitude (at $t = 0.63$ ms)

$$\begin{aligned} y(0.00063+) &= 0.59 \cos(0.00063\omega_2 - 169^\circ) + B \\ &= 0.577 + B \end{aligned}$$
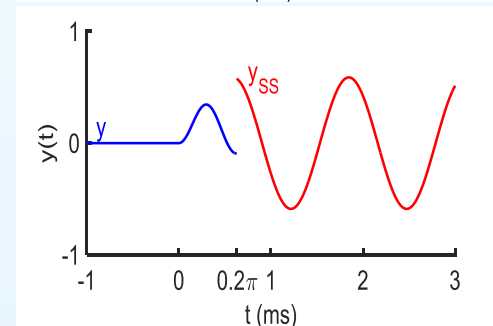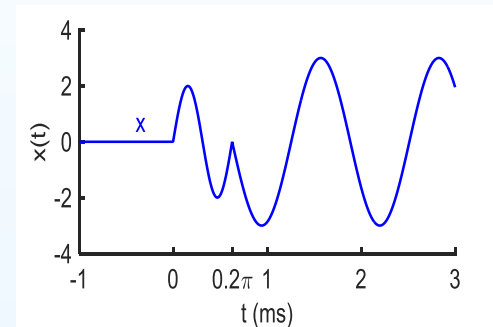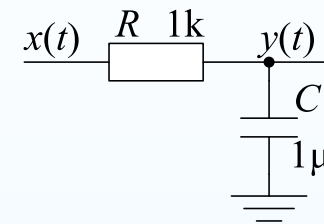
$$y(0.00063-) = 0.2 \cos(0.00063\omega_1 - 174^\circ) + 0.198e^{-0.00063/\tau} = -0.092$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
 prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$

$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$




Steady State + Transient (for $t \geq 0.63$ ms)

$$y = 0.59 \cos(\omega_2 t - 169^\circ) + B e^{-(t-0.00063)/\tau}$$

Transient Amplitude (at $t = 0.63$ ms)

$$\begin{aligned} y(0.00063+) &= 0.59 \cos(0.00063\omega_2 - 169^\circ) + B \\ &= 0.577 + B \end{aligned}$$
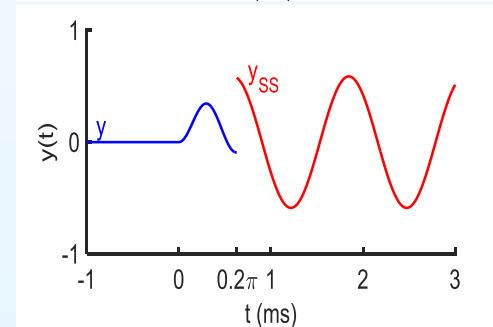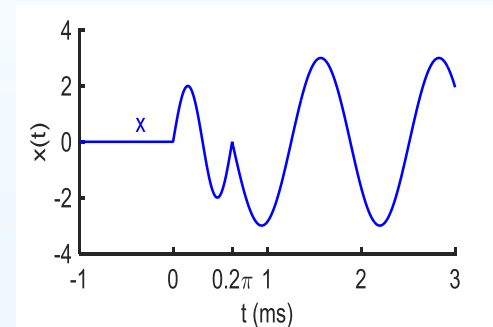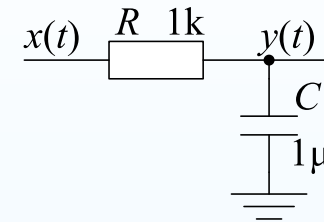
$$\begin{aligned} y(0.00063-) &= 0.2 \cos(0.00063\omega_1 - 174^\circ) + 0.198e^{-0.00063/\tau} = -0.092 \\ \Rightarrow 0.577 + B &= -0.092 \Rightarrow B = -0.67 \end{aligned}$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
 prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$

$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$




Steady State + Transient (for $t \geq 0.63$ ms)

$$y = 0.59 \cos(\omega_2 t - 169^\circ) + B e^{-(t-0.00063)/\tau}$$

Transient Amplitude (at $t = 0.63$ ms)

$$\begin{aligned} y(0.00063+) &= 0.59 \cos(0.00063\omega_2 - 169^\circ) + B \\ &= 0.577 + B \end{aligned}$$
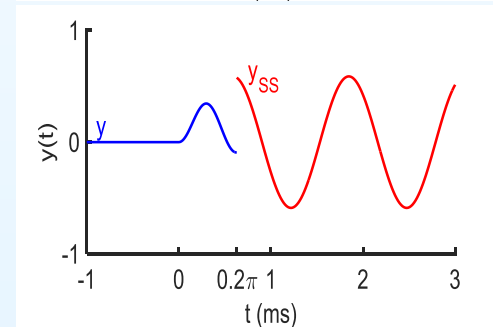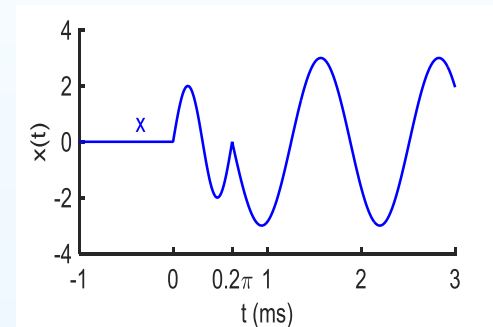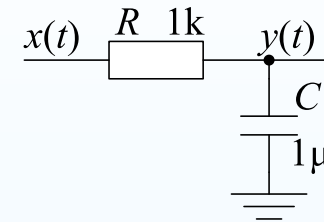
$$\begin{aligned} y(0.00063-) &= 0.2 \cos(0.00063\omega_1 - 174^\circ) + 0.198e^{-0.00063/\tau} = -0.092 \\ \Rightarrow 0.577 + B &= -0.092 \Rightarrow B = -0.67 \Rightarrow y_{Tr} = -0.67e^{-(t-0.00063)/\tau} \end{aligned}$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
 prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$

$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$




Steady State + Transient (for $t \geq 0.63$ ms)

$$y = 0.59 \cos(\omega_2 t - 169^\circ) + B e^{-(t-0.00063)/\tau}$$

Transient Amplitude (at $t = 0.63$ ms)

$$\begin{aligned} y(0.00063+) &= 0.59 \cos(0.00063\omega_2 - 169^\circ) + B \\ &= 0.577 + B \end{aligned}$$
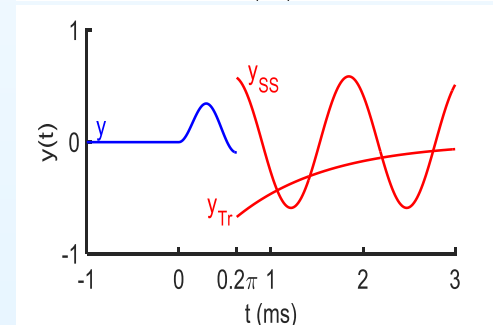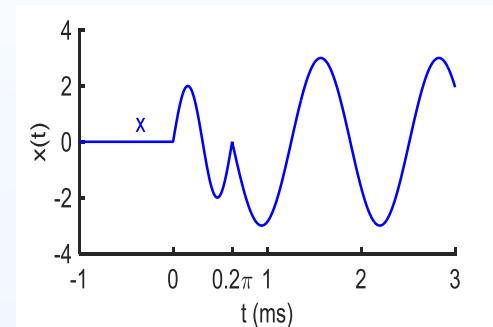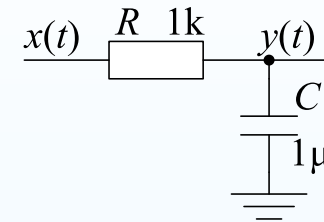
$$\begin{aligned} y(0.00063-) &= 0.2 \cos(0.00063\omega_1 - 174^\circ) + 0.198e^{-0.00063/\tau} = -0.092 \\ \Rightarrow 0.577 + B &= -0.092 \Rightarrow B = -0.67 \Rightarrow y_{Tr} = -0.67e^{-(t-0.00063)/\tau} \end{aligned}$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
 prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$

$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$

Steady State + Transient (for $t \geq 0.63$ ms)

$$y = 0.59 \cos(\omega_2 t - 169^\circ) + B e^{-(t-0.00063)/\tau}$$




Transient Amplitude (at $t = 0.63$ ms)

$$\begin{aligned} y(0.00063+) &= 0.59 \cos(0.00063\omega_2 - 169^\circ) + B \\ &= 0.577 + B \end{aligned}$$

$$\begin{aligned} y(0.00063-) &= 0.2 \cos(0.00063\omega_1 - 174^\circ) + 0.198e^{-0.00063/\tau} = -0.092 \\ \Rightarrow 0.577 + B &= -0.092 \Rightarrow B = -0.67 \Rightarrow y_{Tr} = -0.67e^{-(t-0.00063)/\tau} \end{aligned}$$

Complete Expression for $y(t)$ (for $t \geq 0.63$ ms)
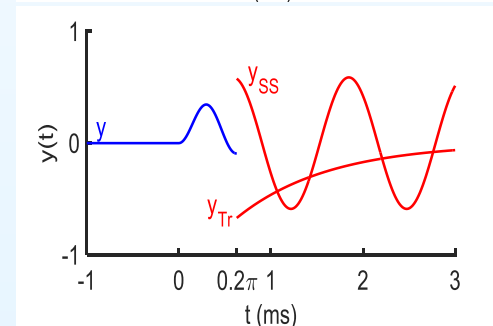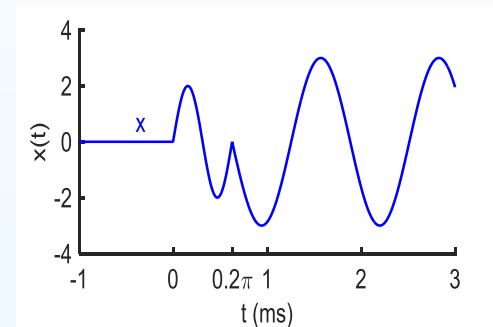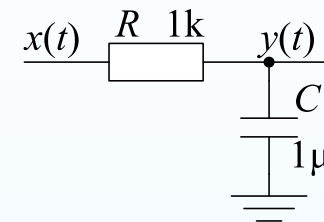
$$y(t) = 0.59 \cos(\omega_2 t - 169^\circ) - 0.67e^{-(t-0.00063)/\tau}$$



Multiple Discontinuities

For $0 \leq t < 0.2\pi$ ms: $X = -2j$, $\omega_1 = 10$ k, $\tau = 1$ ms
 prev page $\Rightarrow y(t) = 0.2 \cos(\omega t - 174^\circ) + 0.198e^{-t/\tau}$

Steady State (for $t \geq 0.0002\pi = 0.63$ ms)

$$X = -3j, \omega_2 = 5 \text{ k}$$

$$\frac{Y}{X} = \frac{1}{j\omega_2 RC + 1} = 0.2 \angle -79^\circ$$

$$Y = X \times \frac{Y}{X} = -3j \times 0.2 \angle -79^\circ$$

$$y_{SS}(t) = 0.59 \cos(\omega_2 t - 169^\circ)$$

Steady State + Transient (for $t \geq 0.63$ ms)

$$y = 0.59 \cos(\omega_2 t - 169^\circ) + B e^{-(t-0.00063)/\tau}$$




Transient Amplitude (at $t = 0.63$ ms)

$$\begin{aligned} y(0.00063+) &= 0.59 \cos(0.00063\omega_2 - 169^\circ) + B \\ &= 0.577 + B \end{aligned}$$

$$\begin{aligned} y(0.00063-) &= 0.2 \cos(0.00063\omega_1 - 174^\circ) + 0.198e^{-0.00063/\tau} = -0.092 \\ \Rightarrow 0.577 + B &= -0.092 \Rightarrow B = -0.67 \Rightarrow y_{Tr} = -0.67e^{-(t-0.00063)/\tau} \end{aligned}$$

Complete Expression for $y(t)$ (for $t \geq 0.63$ ms)
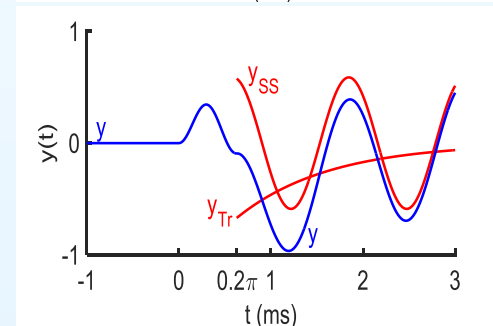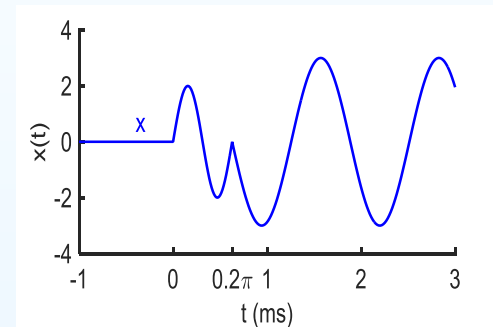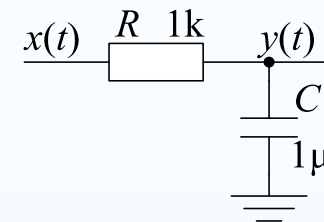
$$y(t) = 0.59 \cos(\omega_2 t - 169^\circ) - 0.67e^{-(t-0.00063)/\tau}$$





Switched Circuit

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- **Switched Circuit**
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :

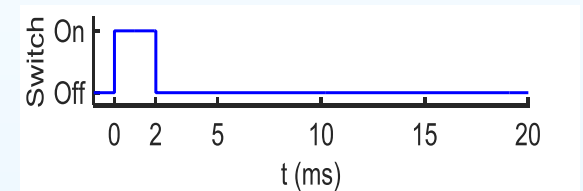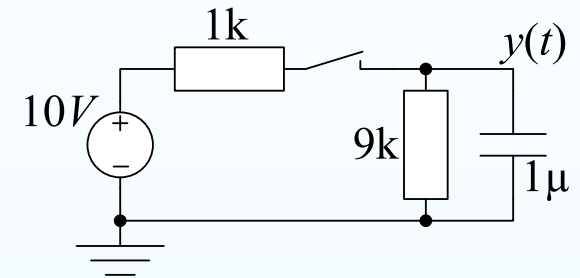



Switched Circuit

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :

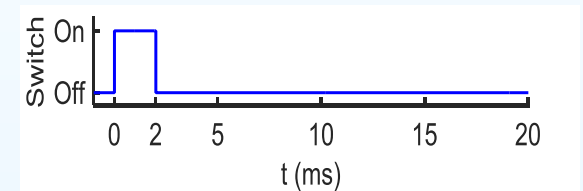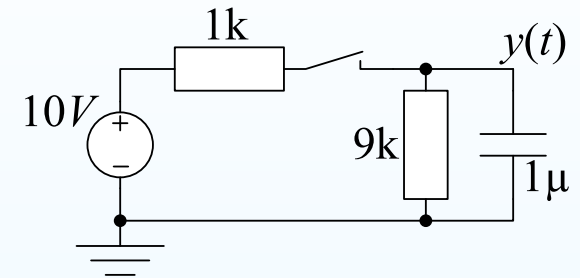Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$



Switched Circuit



16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :

Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$

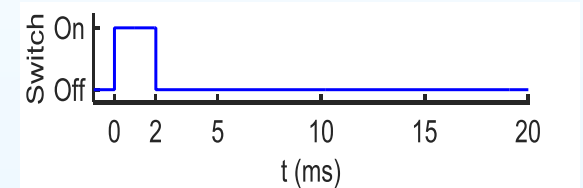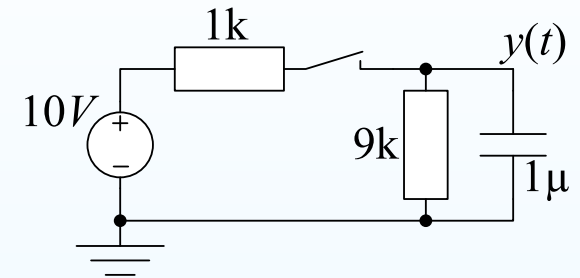Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$



Switched Circuit

16: Transients (B)



- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :

Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$

Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$

Switch closed at $t = 0$.

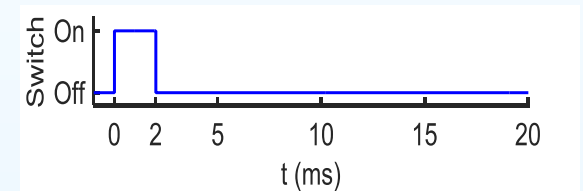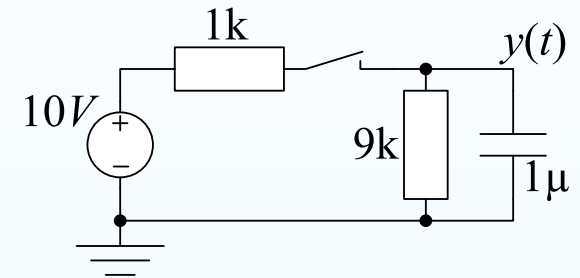

Switched Circuit

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary



Operating the switch changes τ :

Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$

Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$

Switch closed at $t = 0$.
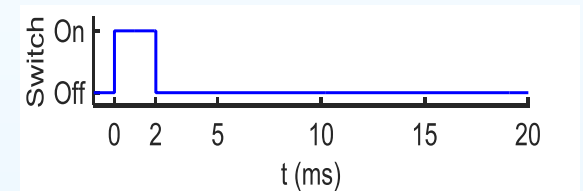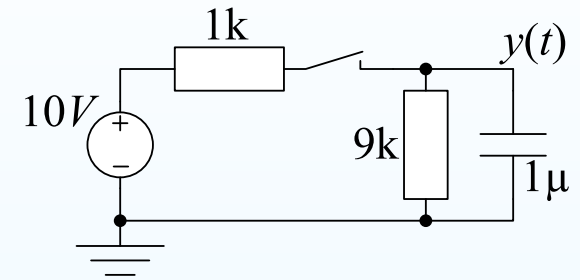
$$y_{SS} = 10 \times \frac{9}{10} = 9\text{ V}$$



Switched Circuit

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :



Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$

Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$

Switch closed at $t = 0$.

$$y_{SS} = 10 \times \frac{9}{10} = 9\text{ V}$$

$$y(t) = 9 - 9e^{-t/\tau_C}$$

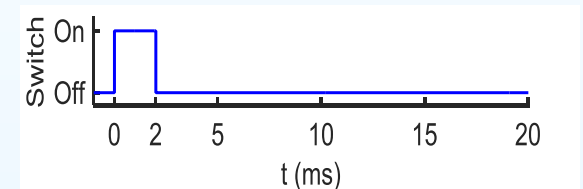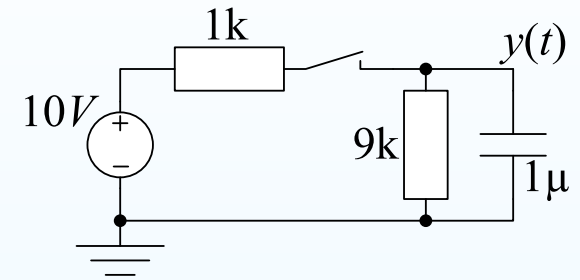

Switched Circuit

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :




Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$

Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$

Switch closed at $t = 0$.

$$y_{SS} = 10 \times \frac{9}{10} = 9\text{ V}$$

$$y(t) = 9 - 9e^{-t/\tau_C}$$

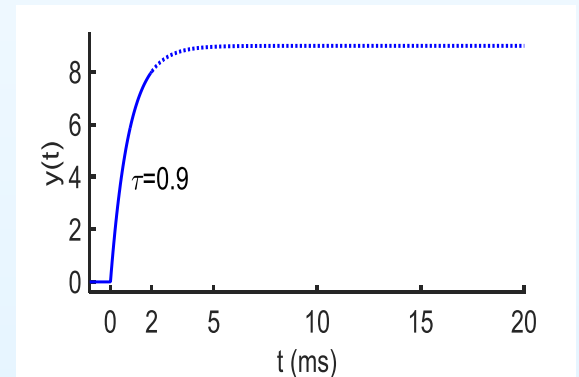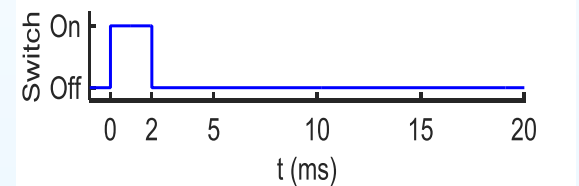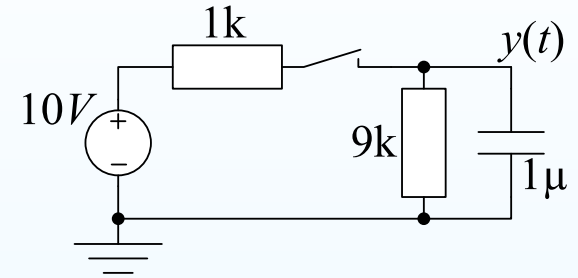

Switched Circuit

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :

Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$




Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$

Switch closed at $t = 0$.

$$y_{SS} = 10 \times \frac{9}{10} = 9\text{ V}$$

$$y(t) = 9 - 9e^{-t/\tau_C}$$

$$y(2^-) = 9 - 9e^{-2/0.9} = 8.02$$

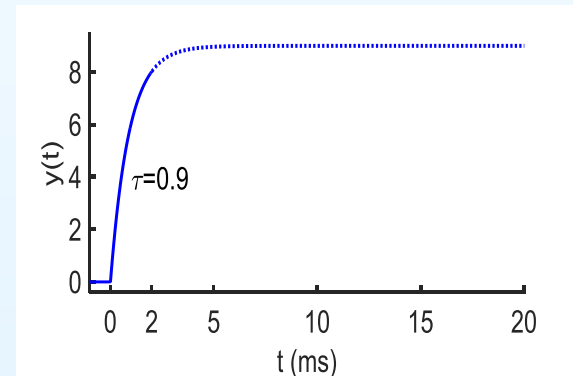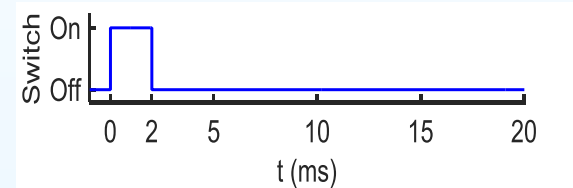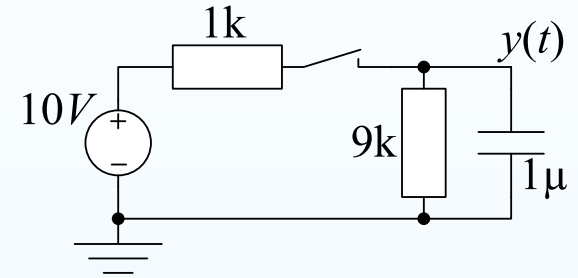

Switched Circuit

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :

Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$

Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$




Switch closed at $t = 0$.

$$y_{SS} = 10 \times \frac{9}{10} = 9\text{ V}$$

$$y(t) = 9 - 9e^{-t/\tau_C}$$

$$y(2^-) = 9 - 9e^{-2/0.9} = 8.02$$

Switch opened at $t = 2$.

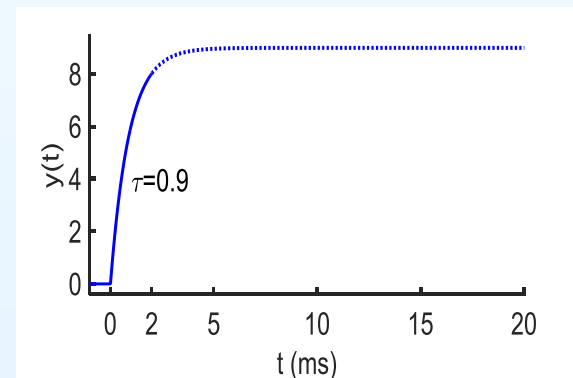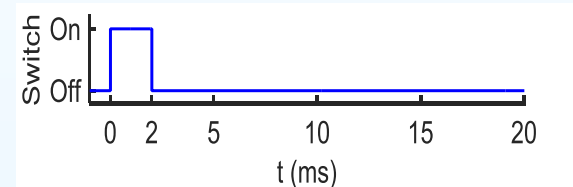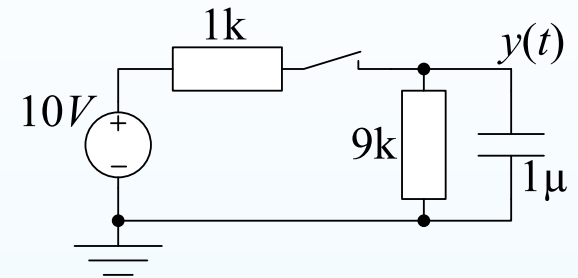

Switched Circuit

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :

Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$

Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$

Switch closed at $t = 0$.

$$y_{SS} = 10 \times \frac{9}{10} = 9\text{ V}$$




$$y(t) = 9 - 9e^{-t/\tau_C}$$

$$y(2^-) = 9 - 9e^{-2/0.9} = 8.02$$

Switch opened at $t = 2$.

$$y_{SS} = 0\text{ V}$$

$$y(t) = 0 + Ae^{-(t-2)/\tau_O}$$

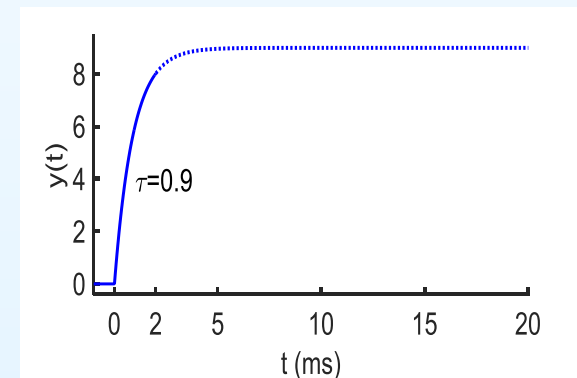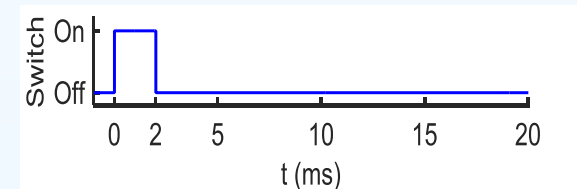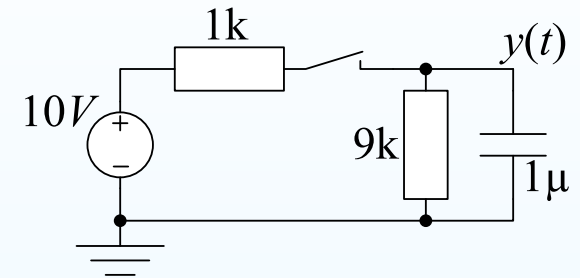

Switched Circuit

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :

Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$

Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$

Switch closed at $t = 0$.

$$y_{SS} = 10 \times \frac{9}{10} = 9\text{ V}$$

$$y(t) = 9 - 9e^{-t/\tau_C}$$




$$y(2^-) = 9 - 9e^{-2/0.9} = 8.02$$

Switch opened at $t = 2$.

$$y_{SS} = 0\text{ V}$$

$$y(t) = 0 + Ae^{-(t-2)/\tau_O}$$

$$y(2^+) = A = y(2^-) = 8.02$$

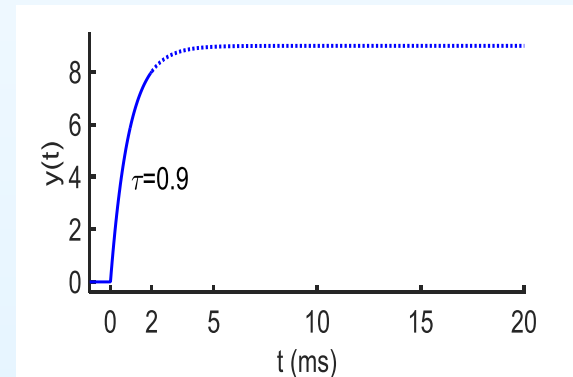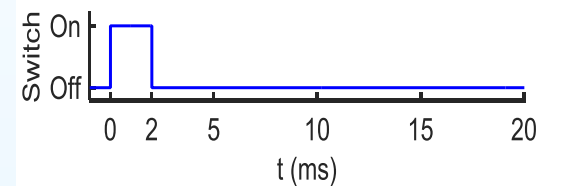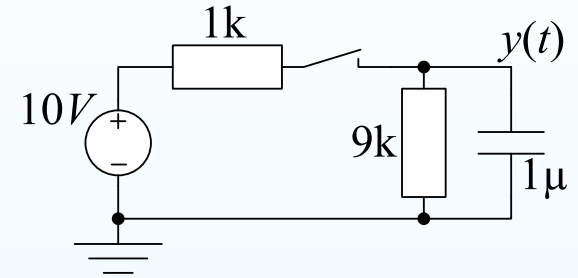

Switched Circuit

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :

Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$

Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$

Switch closed at $t = 0$.

$$y_{SS} = 10 \times \frac{9}{10} = 9\text{ V}$$

$$y(t) = 9 - 9e^{-t/\tau_C}$$




$$y(2^-) = 9 - 9e^{-2/0.9} = 8.02$$

Switch opened at $t = 2$.

$$y_{SS} = 0\text{ V}$$

$$y(t) = 0 + Ae^{-(t-2)/\tau_O}$$

$$y(2^+) = A = y(2^-) = 8.02$$

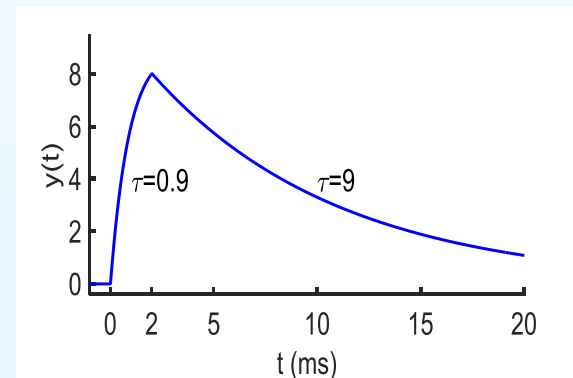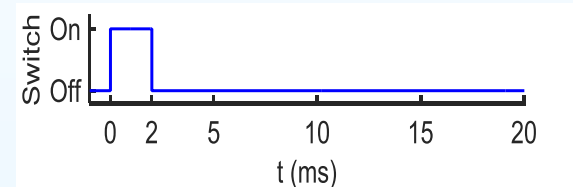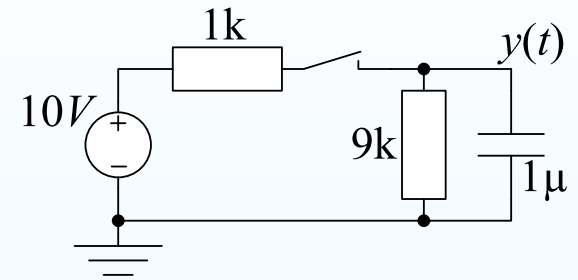

Switched Circuit

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

Operating the switch changes τ :

Closed: $\tau_C = (1\text{ k} \parallel 9\text{ k}) \times C = 0.9\text{ ms}$

Open: $\tau_O = 9\text{ k} \times C = 9\text{ ms}$

Switch closed at $t = 0$.

$$y_{SS} = 10 \times \frac{9}{10} = 9\text{ V}$$

$$y(t) = 9 - 9e^{-t/\tau_C}$$

$$y(2^-) = 9 - 9e^{-2/0.9} = 8.02$$




Switch opened at $t = 2$.

$$y_{SS} = 0\text{ V}$$

$$y(t) = 0 + Ae^{-(t-2)/\tau_O}$$

$$y(2^+) = A = y(2^-) = 8.02$$


$$y(20) = 8.02e^{-(20-2)/9} = 1.09$$

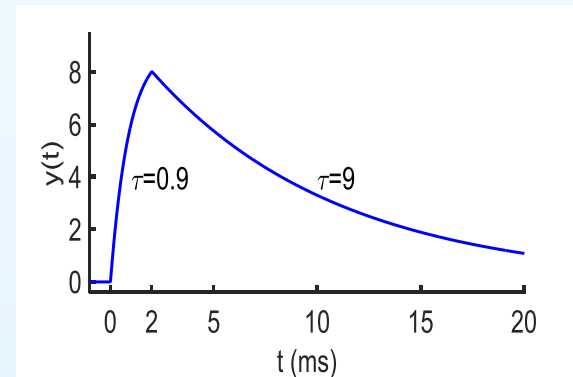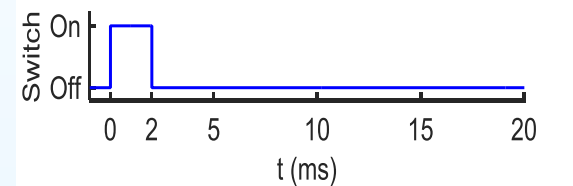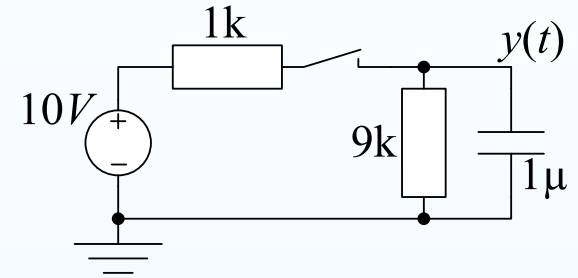

Transfer Function

Phasor nodal analysis:

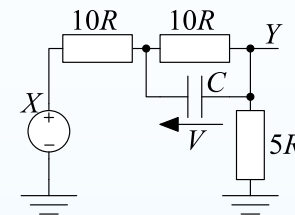
$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5}$$



Transfer Function

Phasor nodal analysis:
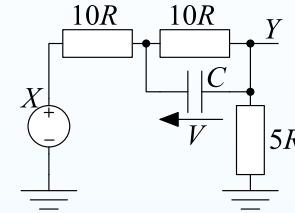
$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$




Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$
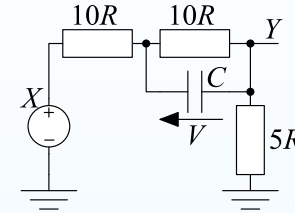
$$\text{Corner frequencies: } p = \frac{1}{10RC}, q = \frac{1}{6RC}$$




Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

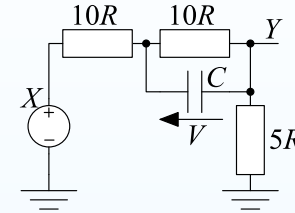Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$





Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

$$\text{Corner frequencies: } p = \frac{1}{10RC}, q = \frac{1}{6RC}, \text{ HF gain} = \frac{1}{3}$$

Thévenin Equivalent driving C :

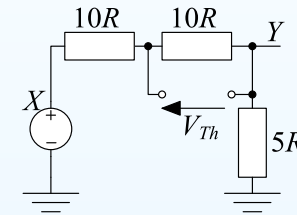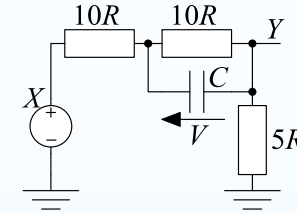

Transfer Function



Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

$$\text{Corner frequencies: } p = \frac{1}{10RC}, q = \frac{1}{6RC}, \text{ HF gain} = \frac{1}{3}$$

Thévenin Equivalent driving C :
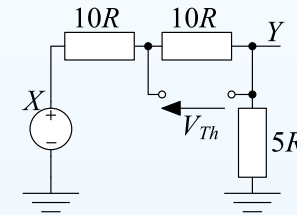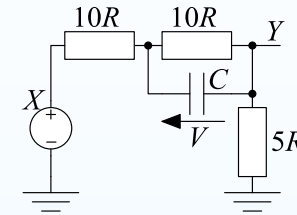
$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R$$



Transfer Function

Phasor nodal analysis:



$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$

Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R$$
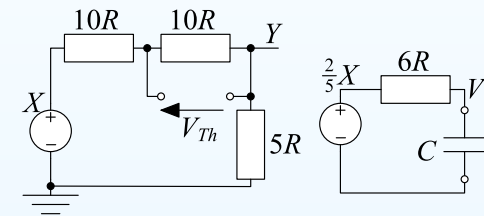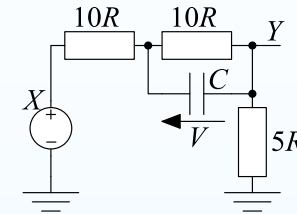
$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1}$$



Transfer Function

Phasor nodal analysis:



$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$

Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$
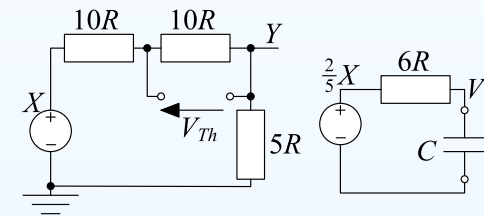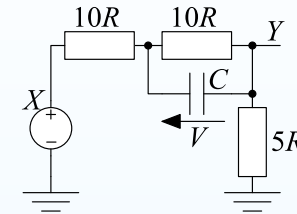
$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1}$$



Transfer Function

Phasor nodal analysis:



$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$

Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$
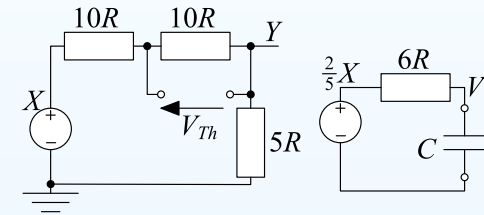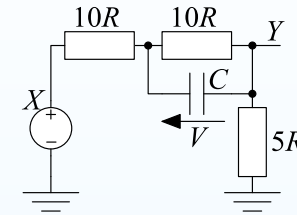
$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$



Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$



Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$

Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$

$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$

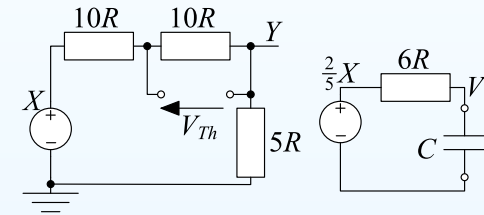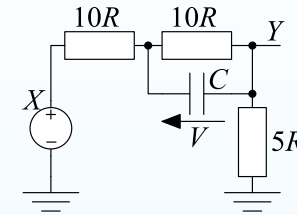Denominator is always $(j\omega\tau + 1)$



Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$




Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$

$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$

Denominator is always $(j\omega\tau + 1)$

Linearity: $Y = aX + bV$

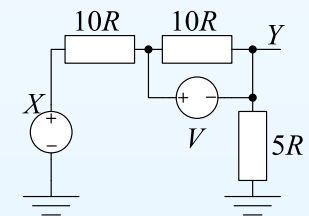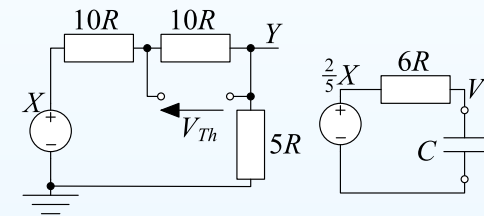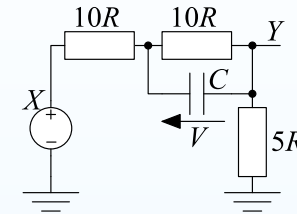


Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

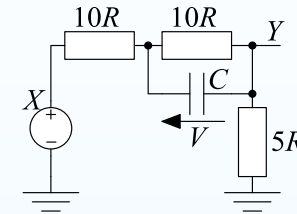Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$




Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$

$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$

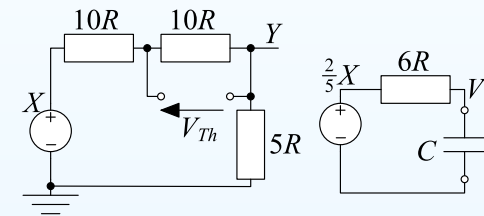
Denominator is always $(j\omega\tau + 1)$



Linearity: $Y = aX + bV$

KCL @ supernode:
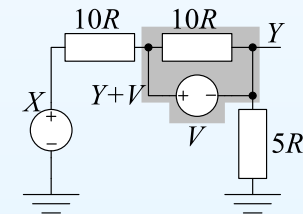
$$\frac{(Y+V)-X}{10R} + \frac{Y}{5R} = 0 \Rightarrow 3Y + V - X = 0$$




Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

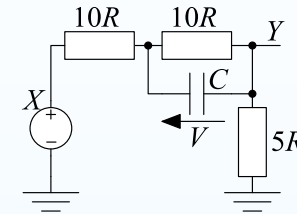Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$




Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$

$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$

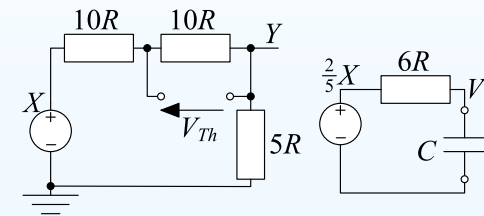Denominator is always $(j\omega\tau + 1)$




Linearity: $Y = aX + bV$

KCL @ supernode:

$$\frac{(Y+V) - X}{10R} + \frac{Y}{5R} = 0 \Rightarrow 3Y + V - X = 0$$

$$Y = \frac{1}{3}X - \frac{1}{3}V$$

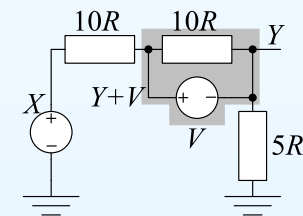


Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

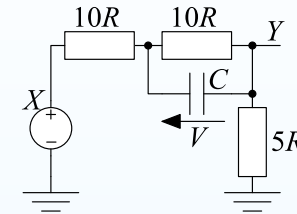Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$




Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$

$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$

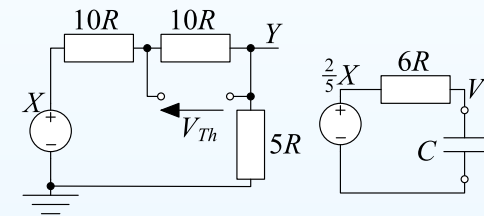Denominator is always $(j\omega\tau + 1)$




Linearity: $Y = aX + bV$

KCL @ supernode:

$$\frac{(Y+V)-X}{10R} + \frac{Y}{5R} = 0 \Rightarrow 3Y + V - X = 0$$
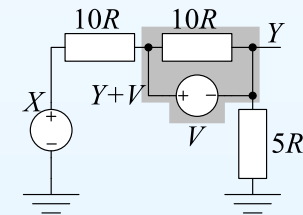
$$Y = \frac{1}{3}X - \frac{1}{3}V = \frac{1}{3}X - \frac{2}{15}X \left(\frac{1}{j\omega\tau + 1} \right)$$




Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

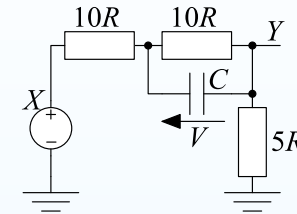Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$




Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$

$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$

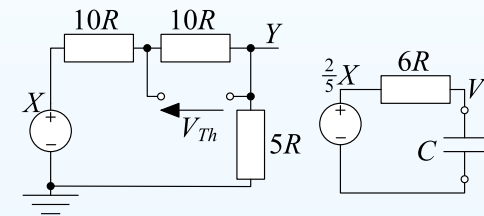Denominator is always $(j\omega\tau + 1)$




Linearity: $Y = aX + bV$

KCL @ supernode:

$$\frac{(Y+V)-X}{10R} + \frac{Y}{5R} = 0 \Rightarrow 3Y + V - X = 0$$
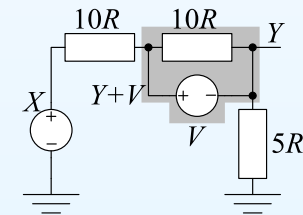
$$Y = \frac{1}{3}X - \frac{1}{3}V = \frac{1}{3}X - \frac{2}{15}X \left(\frac{1}{j\omega\tau + 1} \right) = \frac{X}{15} \left(\frac{5j\omega\tau + 3}{j\omega\tau + 1} \right)$$




Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

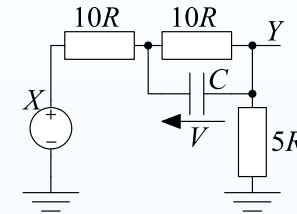Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$




Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$

$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$

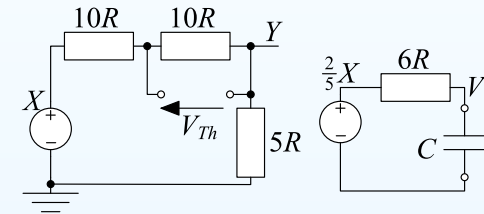Denominator is always $(j\omega\tau + 1)$




Linearity: $Y = aX + bV$

KCL @ supernode:

$$\frac{(Y+V)-X}{10R} + \frac{Y}{5R} = 0 \Rightarrow 3Y + V - X = 0$$

$$Y = \frac{1}{3}X - \frac{1}{3}V = \frac{1}{3}X - \frac{2}{15}X \left(\frac{1}{j\omega\tau + 1} \right) = \frac{X}{15} \left(\frac{5j\omega\tau + 3}{j\omega\tau + 1} \right)$$

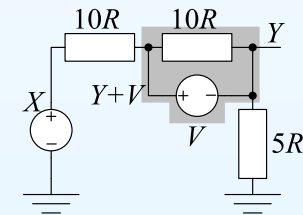Denominator of bV is unchanged by adding aX




Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

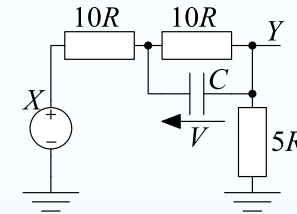Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$




Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$

$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$

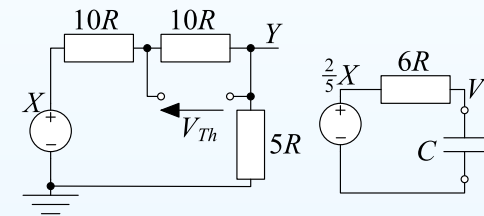Denominator is always $(j\omega\tau + 1)$




Linearity: $Y = aX + bV$

KCL @ supernode:

$$\frac{(Y+V)-X}{10R} + \frac{Y}{5R} = 0 \Rightarrow 3Y + V - X = 0$$

$$Y = \frac{1}{3}X - \frac{1}{3}V = \frac{1}{3}X - \frac{2}{15}X \left(\frac{1}{j\omega\tau + 1} \right) = \frac{X}{15} \left(\frac{5j\omega\tau + 3}{j\omega\tau + 1} \right)$$

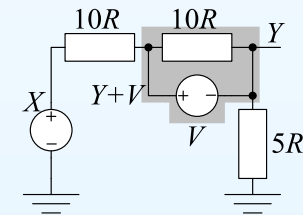Denominator of bV is unchanged by adding aX




(1) Denominator corner frequency is always $\frac{1}{\tau}$ for any transfer function in the circuit.

Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

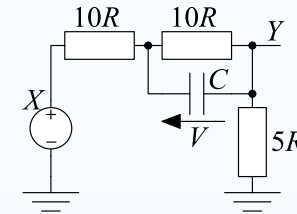Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$




Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$

$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$

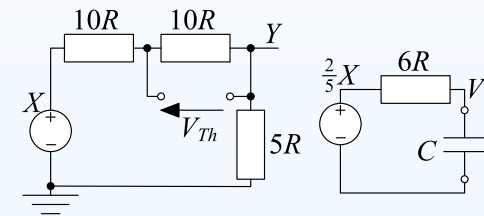Denominator is always $(j\omega\tau + 1)$




Linearity: $Y = aX + bV$

KCL @ supernode:

$$\frac{(Y+V)-X}{10R} + \frac{Y}{5R} = 0 \Rightarrow 3Y + V - X = 0$$

$$Y = \frac{1}{3}X - \frac{1}{3}V = \frac{1}{3}X - \frac{2}{15}X \left(\frac{1}{j\omega\tau + 1} \right) = \frac{X}{15} \left(\frac{5j\omega\tau + 3}{j\omega\tau + 1} \right)$$

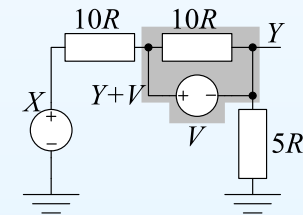Denominator of bV is unchanged by adding aX



(1) Denominator corner frequency is always $\frac{1}{\tau}$ for any transfer function in the circuit.


(2) $V = 0$ at $\omega = \infty$, so since $Y = aX + bV$, $a = \frac{Y}{X} \Big|_{\omega=\infty}$ (= HF-gain)

Transfer Function

Phasor nodal analysis:

$$\frac{Y}{X} = \frac{5R}{15R + \frac{10R}{1 + 10j\omega RC}} = \frac{10j\omega RC + 1}{30j\omega RC + 5} = 0.2 \frac{\frac{j\omega}{p} + 1}{\frac{j\omega}{q} + 1}$$

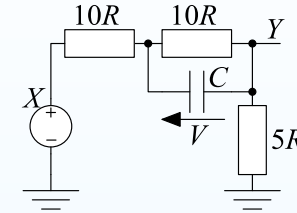Corner frequencies: $p = \frac{1}{10RC}$, $q = \frac{1}{6RC}$, HF gain = $\frac{1}{3}$




Thévenin Equivalent driving C :

$$V_{Th} = \frac{2}{5}X, R_{Th} = 10R \parallel 15R = 6R, \tau = 6RC$$

$$V = \frac{2}{5}X \times \frac{1}{6j\omega RC + 1} = \frac{2}{5}X \times \frac{1}{j\omega\tau + 1}$$

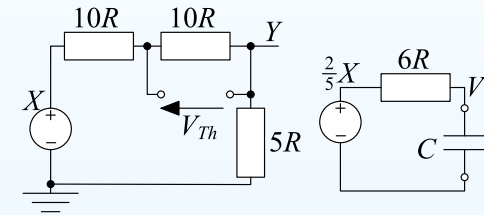Denominator is always $(j\omega\tau + 1)$




Linearity: $Y = aX + bV$

KCL @ supernode:

$$\frac{(Y+V)-X}{10R} + \frac{Y}{5R} = 0 \Rightarrow 3Y + V - X = 0$$

$$Y = \frac{1}{3}X - \frac{1}{3}V = \frac{1}{3}X - \frac{2}{15}X \left(\frac{1}{j\omega\tau + 1} \right) = \frac{X}{15} \left(\frac{5j\omega\tau + 3}{j\omega\tau + 1} \right)$$

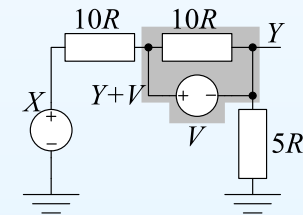Denominator of bV is unchanged by adding aX





(1) Denominator corner frequency is always $\frac{1}{\tau}$ for any transfer function in the circuit.

(2) $V = 0$ at $\omega = \infty$, so since $Y = aX + bV$, $a = \frac{Y}{X} \Big|_{\omega=\infty}$ (= HF-gain)

V is never discontinuous so ΔY discontinuity = HF-gain \times ΔX discontinuity

Transient from Transfer Function



Calculate Transfer Function

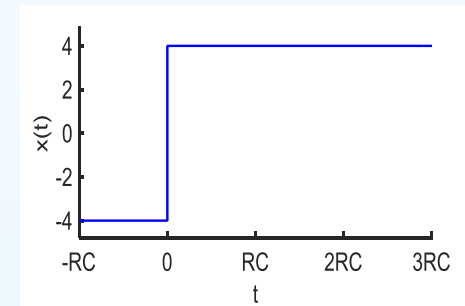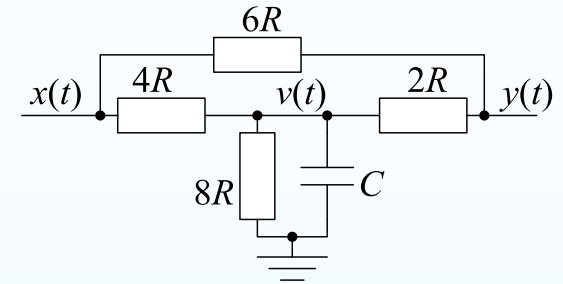

Transient from Transfer Function

Calculate Transfer Function
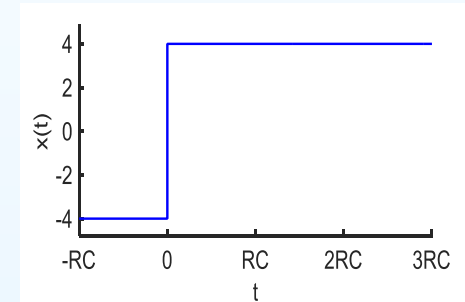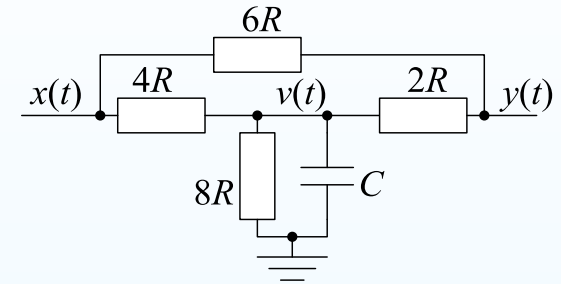
$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$





Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$
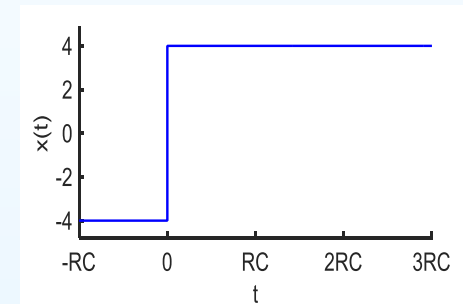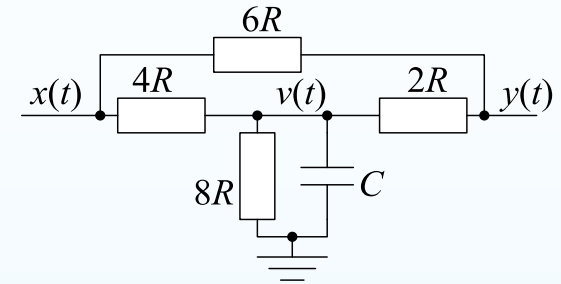
$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$





Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$
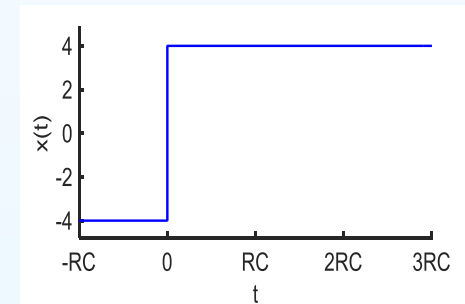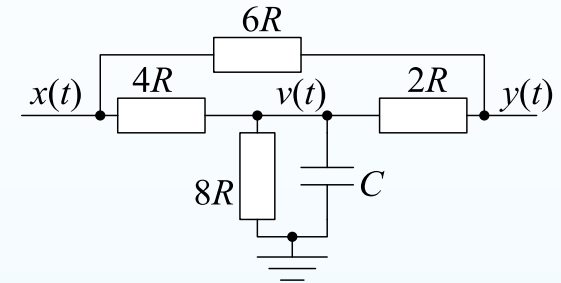
$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$



Transient from Transfer Function



Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$
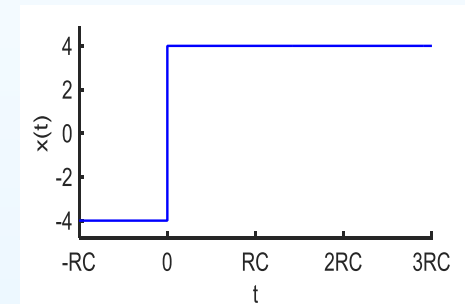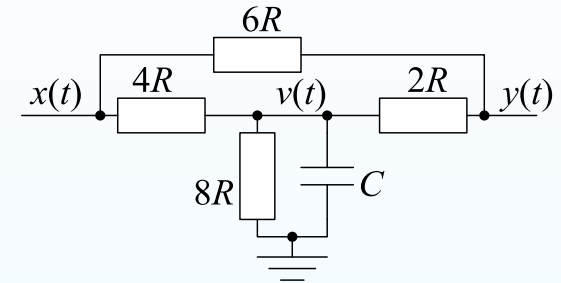
$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$



Transient from Transfer Function

Calculate Transfer Function



$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State

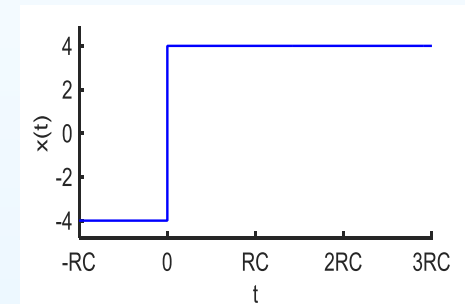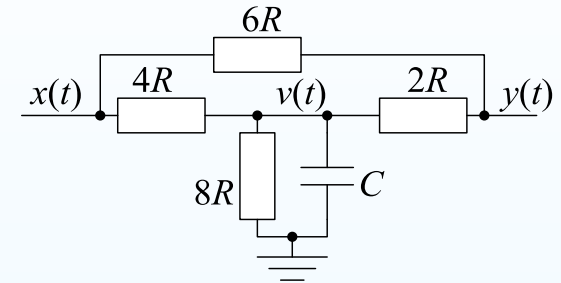

Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$



$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State
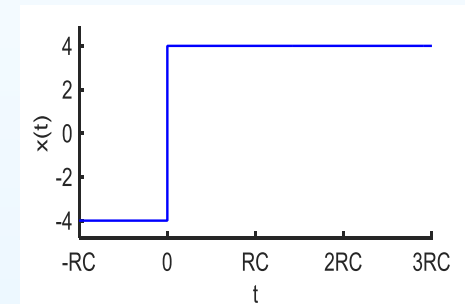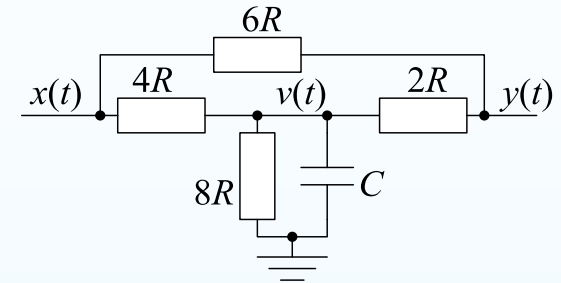
$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$



Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$



$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State

$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$
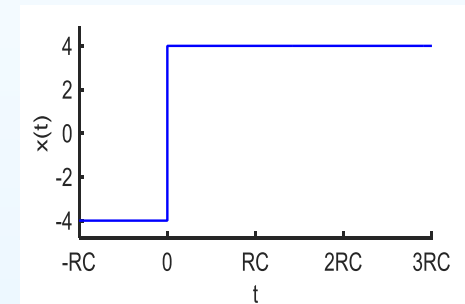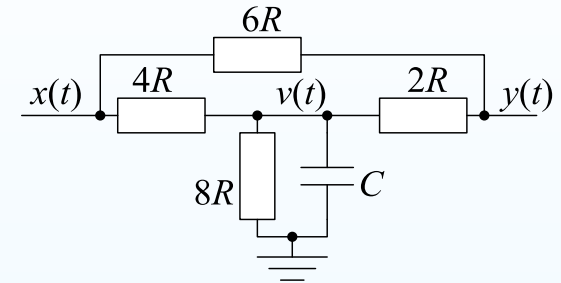
$$t \geq 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times +4 = +3\frac{1}{4}$$



Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$




$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State

$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$
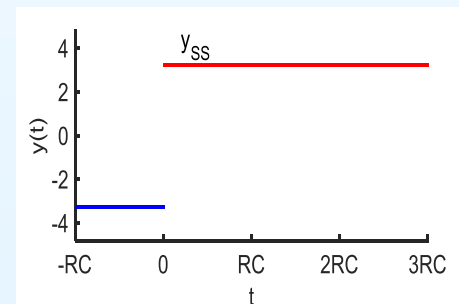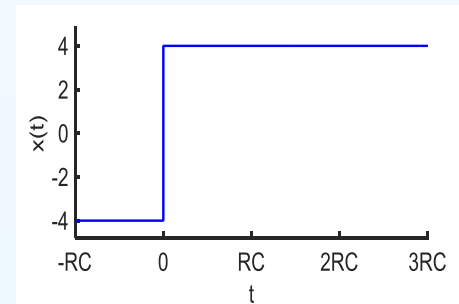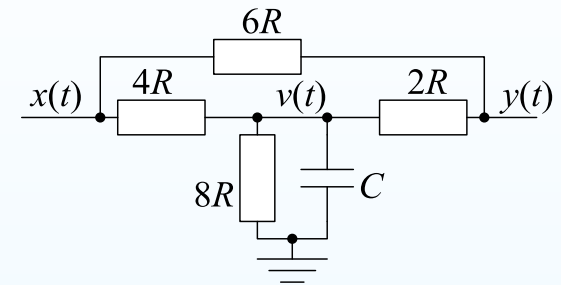
$$t \geq 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times +4 = +3\frac{1}{4}$$



Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$




Steady State

$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$

$$t \geq 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times +4 = +3\frac{1}{4}$$

Steady State + Transient (for $t > 0$)
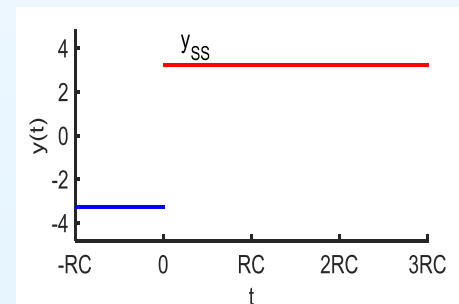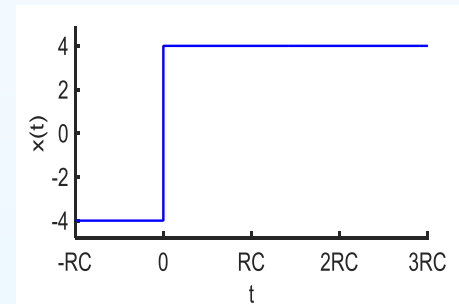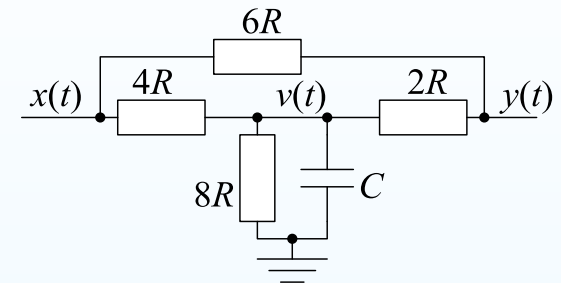
$$t \geq 0: y = 3\frac{1}{4} + Ae^{-t/\tau}$$



Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State




$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$

$$t \geq 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times +4 = +3\frac{1}{4}$$

Steady State + Transient (for $t > 0$)

$$t \geq 0: y = 3\frac{1}{4} + Ae^{-t/\tau}$$

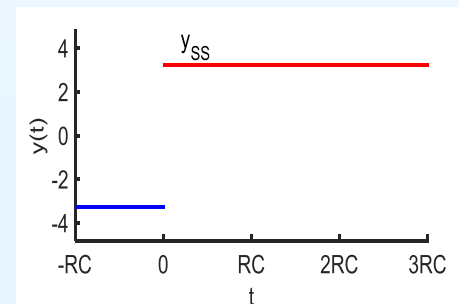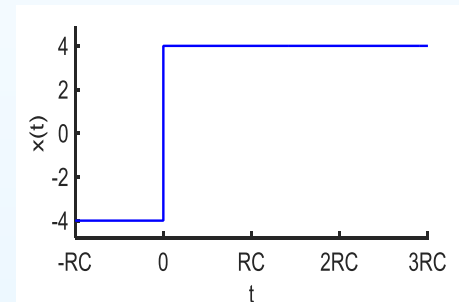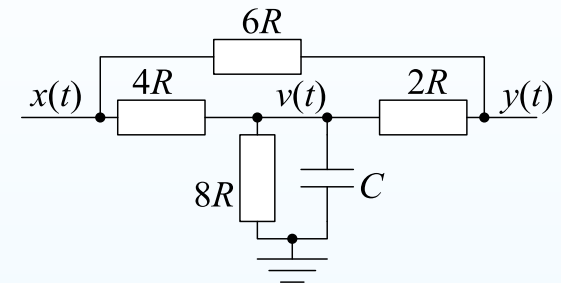Discontinuity Gain (= HF Gain @ $\omega = \infty$)



Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State

$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$




$$t \geq 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times +4 = +3\frac{1}{4}$$

Steady State + Transient (for $t > 0$)

$$t \geq 0: y = 3\frac{1}{4} + Ae^{-t/\tau}$$

Discontinuity Gain (= HF Gain @ $\omega = \infty$)
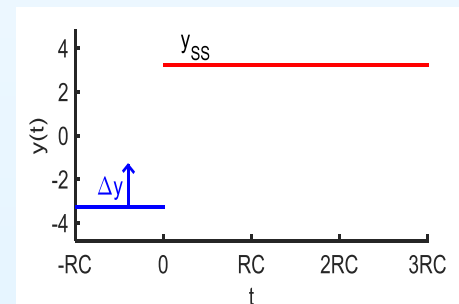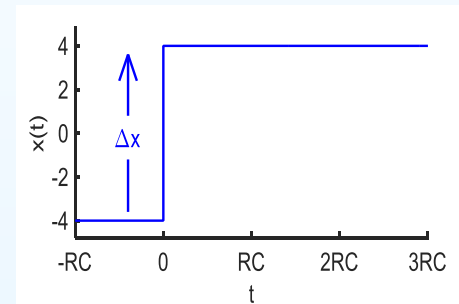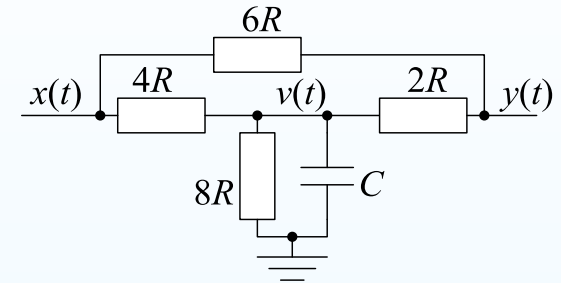
$$\Delta y = y(0+) - y(0-) = \frac{1}{4}\Delta x = \frac{1}{4} \times 8 = 2$$



Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State

$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$

$$t \geq 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times +4 = +3\frac{1}{4}$$




Steady State + Transient (for $t > 0$)

$$t \geq 0: y = 3\frac{1}{4} + Ae^{-t/\tau}$$

Discontinuity Gain (= HF Gain @ $\omega = \infty$)

$$\Delta y = y(0+) - y(0-) = \frac{1}{4}\Delta x = \frac{1}{4} \times 8 = 2$$
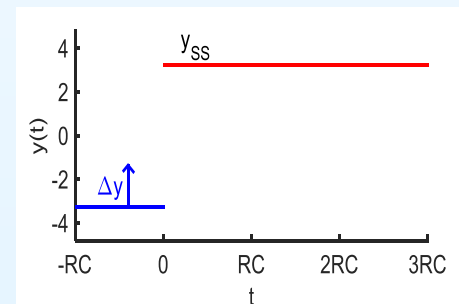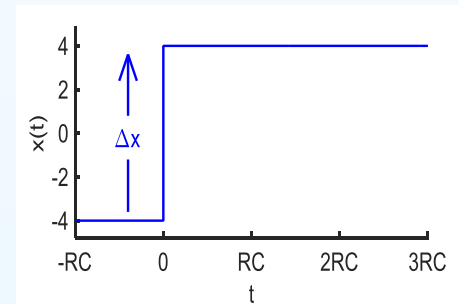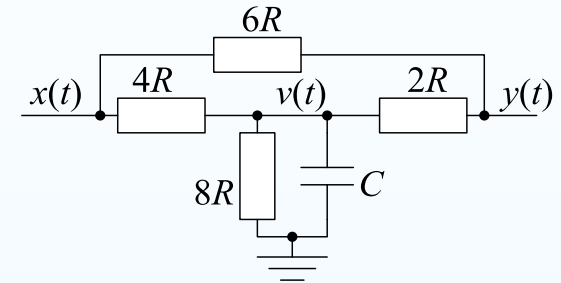
$$\left(3\frac{1}{4} + A\right) - \left(-3\frac{1}{4}\right) = 2$$



Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State

$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$

$$t \geq 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times +4 = +3\frac{1}{4}$$




Steady State + Transient (for $t > 0$)

$$t \geq 0: y = 3\frac{1}{4} + Ae^{-t/\tau}$$

Discontinuity Gain (= HF Gain @ $\omega = \infty$)

$$\Delta y = y(0+) - y(0-) = \frac{1}{4}\Delta x = \frac{1}{4} \times 8 = 2$$
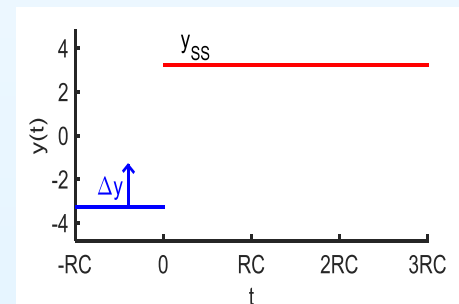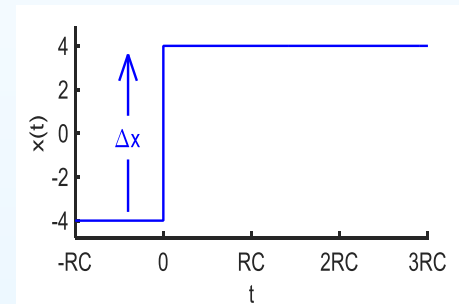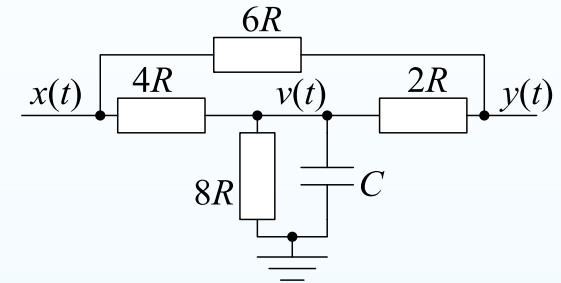
$$\left(3\frac{1}{4} + A\right) - \left(-3\frac{1}{4}\right) = 2 \Rightarrow A = -4\frac{1}{2}$$



Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State

$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$

$$t \geq 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times +4 = +3\frac{1}{4}$$




Steady State + Transient (for $t > 0$)

$$t \geq 0: y = 3\frac{1}{4} + Ae^{-t/\tau}$$

Discontinuity Gain (= HF Gain @ $\omega = \infty$)

$$\Delta y = y(0+) - y(0-) = \frac{1}{4}\Delta x = \frac{1}{4} \times 8 = 2$$
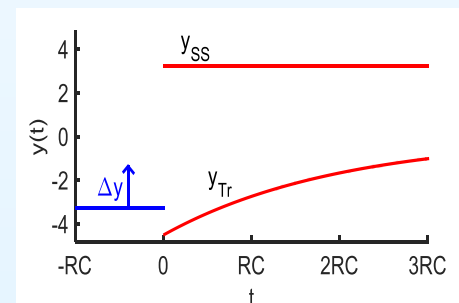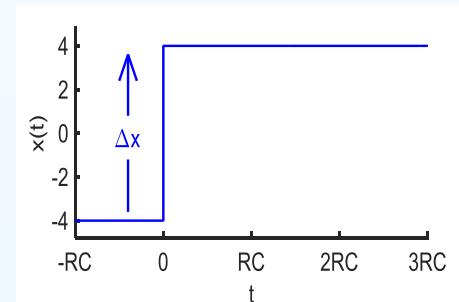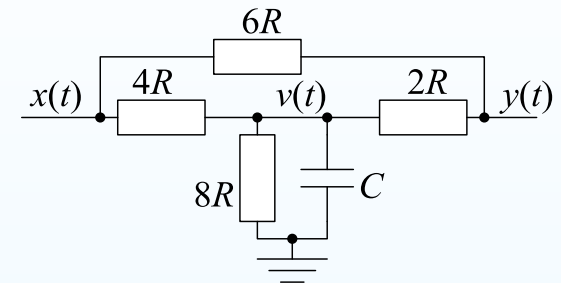
$$\left(3\frac{1}{4} + A\right) - \left(-3\frac{1}{4}\right) = 2 \Rightarrow A = -4\frac{1}{2}$$



Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State

$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$

$$t \geq 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times +4 = +3\frac{1}{4}$$

Steady State + Transient (for $t > 0$)

$$t \geq 0: y = 3\frac{1}{4} + Ae^{-t/\tau}$$




Discontinuity Gain (= HF Gain @ $\omega = \infty$)

$$\Delta y = y(0+) - y(0-) = \frac{1}{4}\Delta x = \frac{1}{4} \times 8 = 2$$

$$(3\frac{1}{4} + A) - (-3\frac{1}{4}) = 2 \Rightarrow A = -4\frac{1}{2}$$

Complete Expression
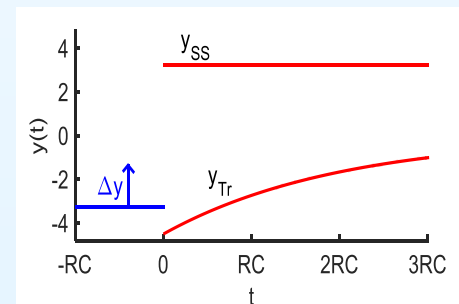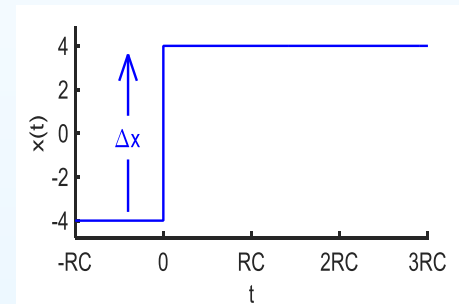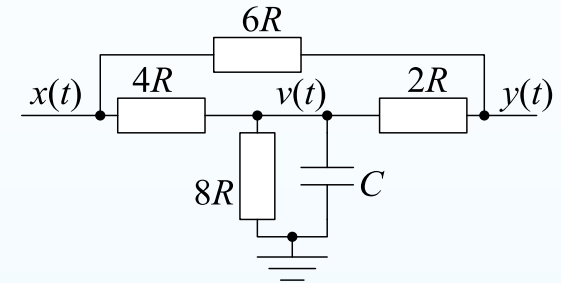
$$t \geq 0: y(t) = 3\frac{1}{4} - 4\frac{1}{2}e^{-t/2RC}$$



Transient from Transfer Function

Calculate Transfer Function

$$\text{KCL @ V: } \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ Y: } \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

$$\text{DC gain: } \frac{13}{16}, \text{ HF gain: } \frac{8}{32} = \frac{1}{4}, \tau = \frac{32RC}{16} = 2RC$$

Steady State

$$t < 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times -4 = -3\frac{1}{4}$$

$$t \geq 0: y_{SS}(t) = \frac{13}{16}x(t) = \frac{13}{16} \times +4 = +3\frac{1}{4}$$

Steady State + Transient (for $t > 0$)

$$t \geq 0: y = 3\frac{1}{4} + Ae^{-t/\tau}$$




Discontinuity Gain (= HF Gain @ $\omega = \infty$)

$$\Delta y = y(0+) - y(0-) = \frac{1}{4}\Delta x = \frac{1}{4} \times 8 = 2$$

$$(3\frac{1}{4} + A) - (-3\frac{1}{4}) = 2 \Rightarrow A = -4\frac{1}{2}$$



Complete Expression
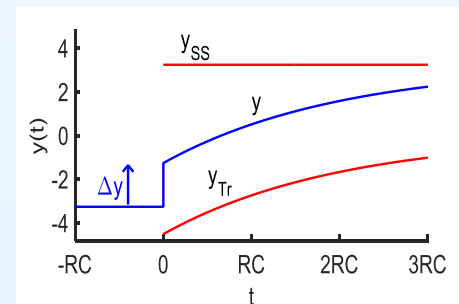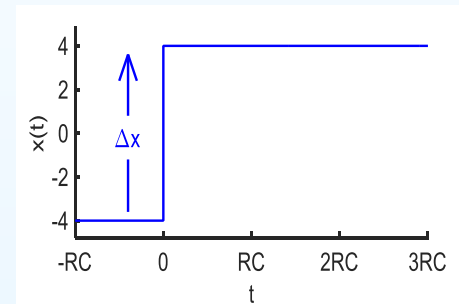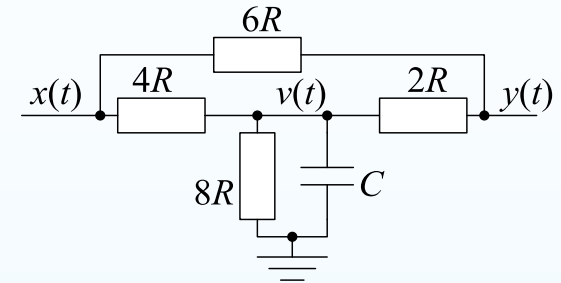
$$t \geq 0: y(t) = 3\frac{1}{4} - 4\frac{1}{2}e^{-t/2RC}$$



Opamp Circuit Transient

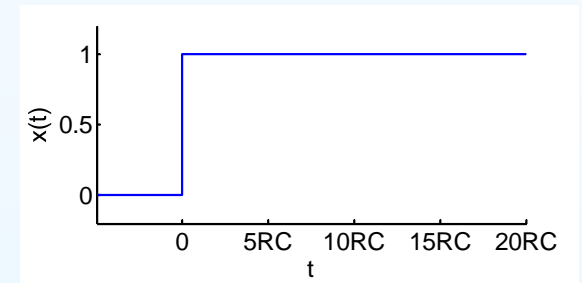
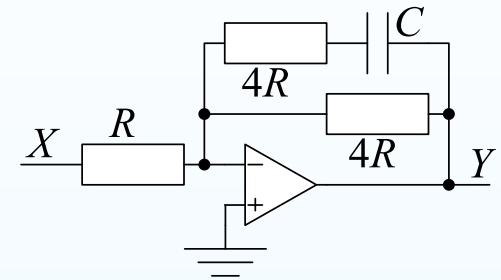
Calculate Transfer Function (Inverting Amplifier)



Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)
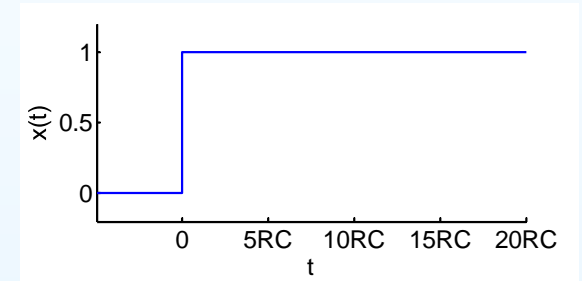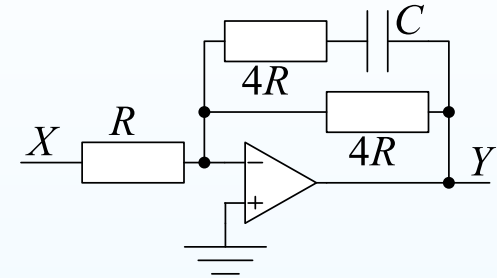
$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R\left(4R + \frac{1}{j\omega C}\right)}{4R + \left(4R + \frac{1}{j\omega C}\right)} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$





Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

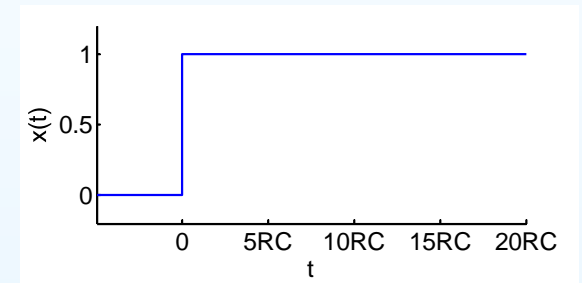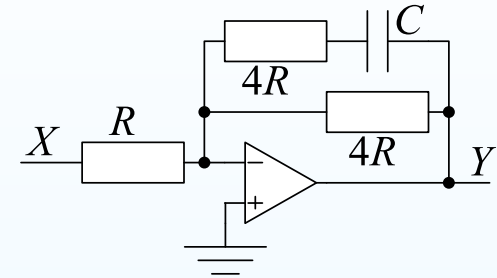



Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R\left(4R + \frac{1}{j\omega C}\right)}{4R + \left(4R + \frac{1}{j\omega C}\right)} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

Steady State

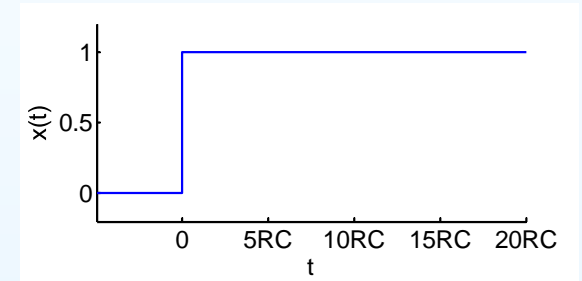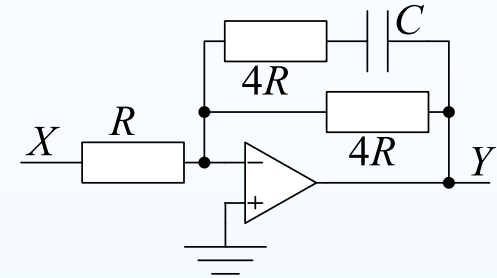

Opamp Circuit Transient



Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R\left(4R + \frac{1}{j\omega C}\right)}{4R + \left(4R + \frac{1}{j\omega C}\right)} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$

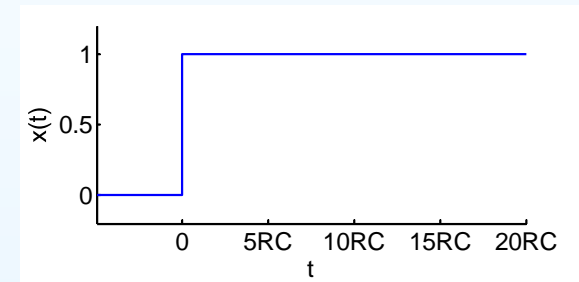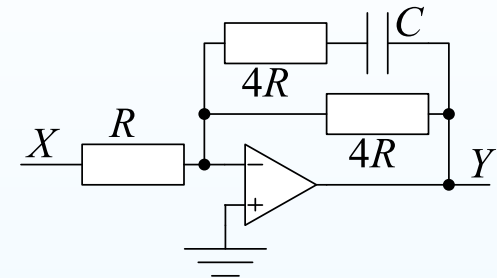

Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)



$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$
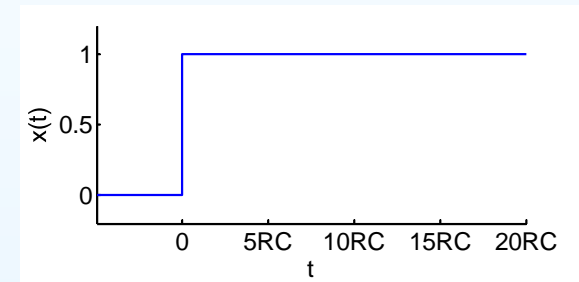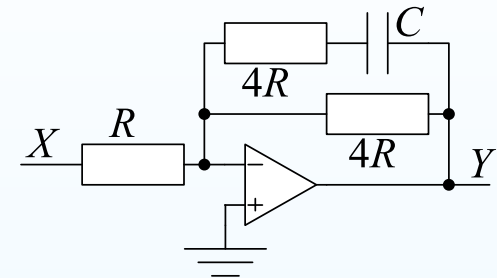
$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$



Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)




$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$
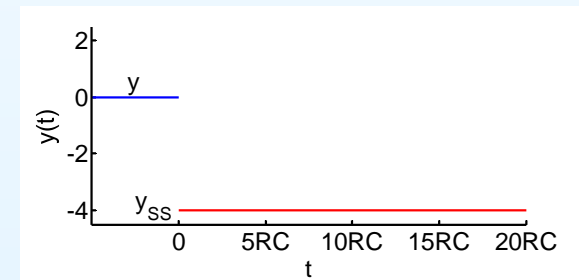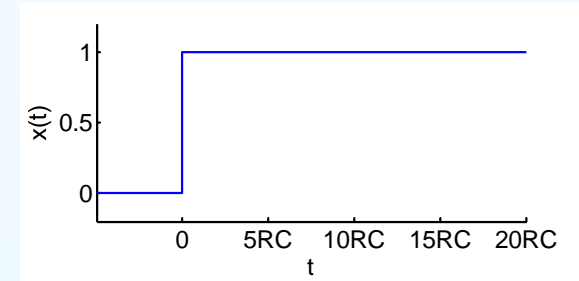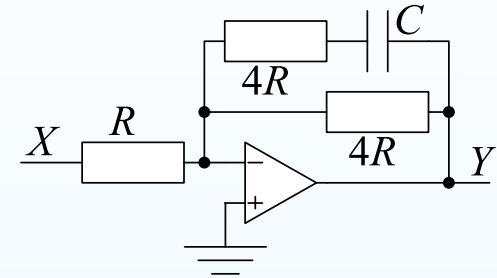
$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$



Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$




Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$

$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$

Steady State + Transient

$$t \geq 0: y = -4 + Ae^{-t/\tau}$$

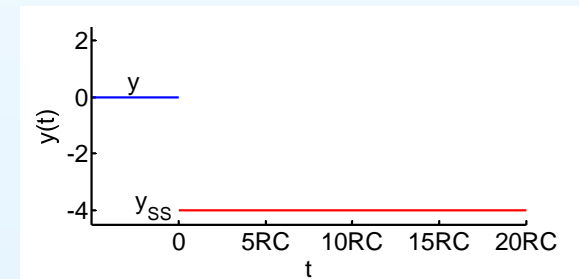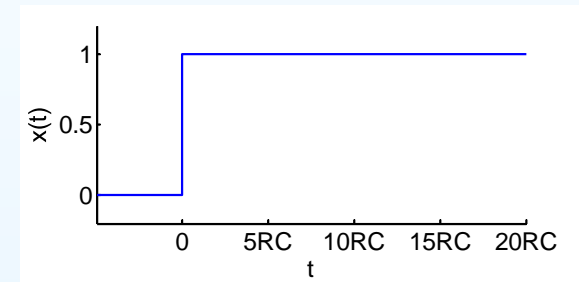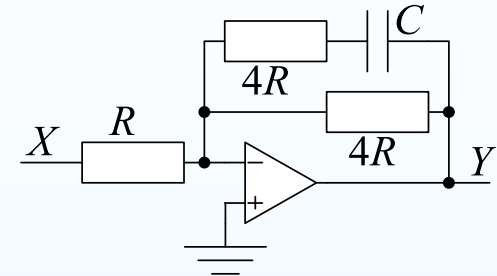

Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

Steady State




$$t < 0: y_{SS}(t) = -4v(t) = 0$$

$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$

Steady State + Transient

$$t \geq 0: y = -4 + Ae^{-t/\tau}$$

Discontinuity Gain (= HF Gain)

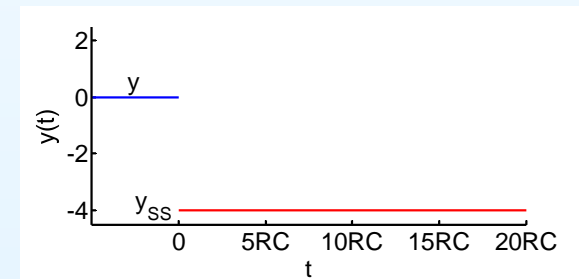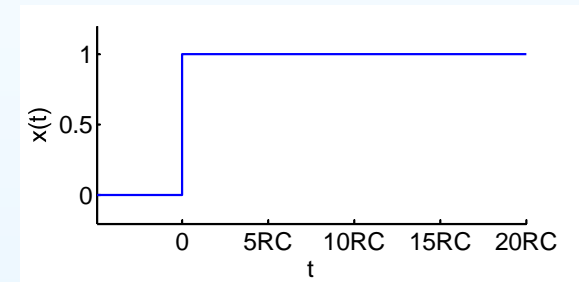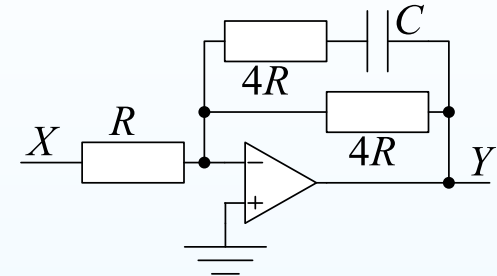

Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$




$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$

Steady State + Transient

$$t \geq 0: y = -4 + Ae^{-t/\tau}$$

Discontinuity Gain (= HF Gain)
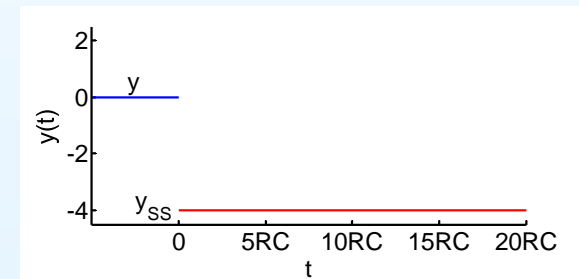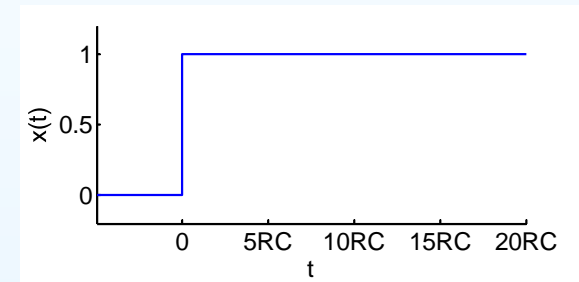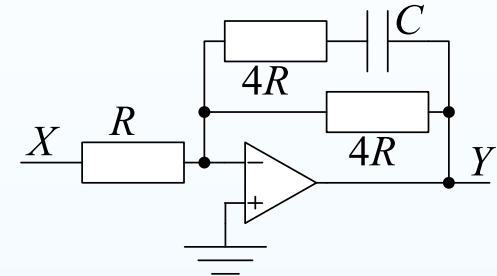
$$y(0+) - y(0-) = -2(x(0+) - x(0-)) = -2$$



Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$

$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$




Steady State + Transient

$$t \geq 0: y = -4 + Ae^{-t/\tau}$$

Discontinuity Gain (= HF Gain)

$$y(0+) - y(0-) = -2(x(0+) - x(0-)) = -2$$

$$(-4 + A) - (0) = -2$$

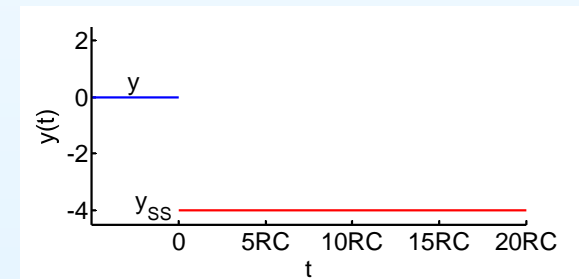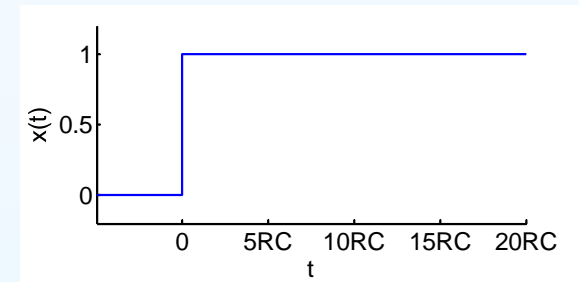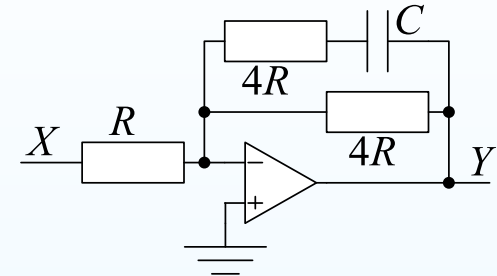

Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$

$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$




Steady State + Transient

$$t \geq 0: y = -4 + Ae^{-t/\tau}$$

Discontinuity Gain (= HF Gain)

$$y(0+) - y(0-) = -2(x(0+) - x(0-)) = -2$$
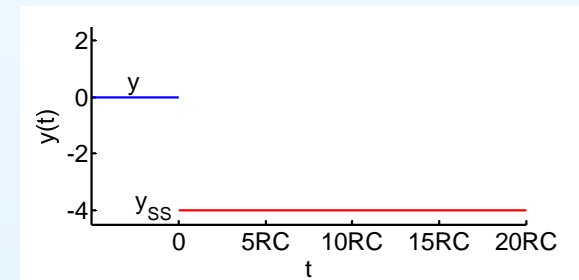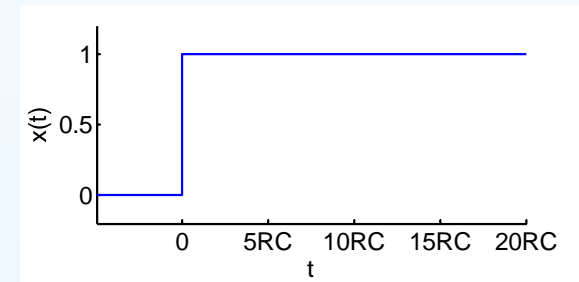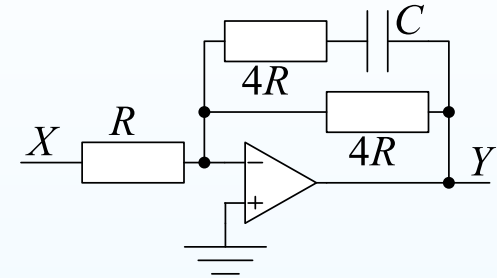
$$(-4 + A) - (0) = -2 \Rightarrow A = 2$$



Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$

$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$




Steady State + Transient

$$t \geq 0: y = -4 + Ae^{-t/\tau}$$

Discontinuity Gain (= HF Gain)

$$y(0+) - y(0-) = -2(x(0+) - x(0-)) = -2$$
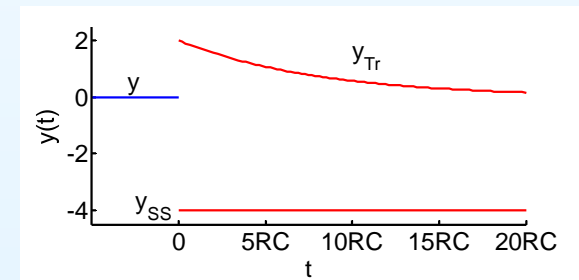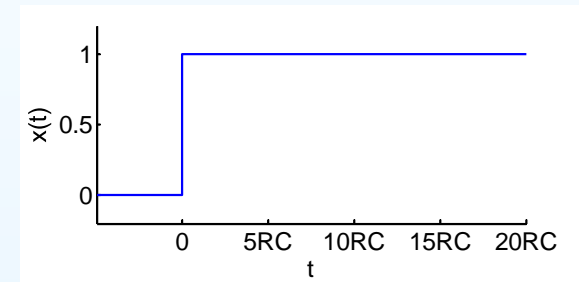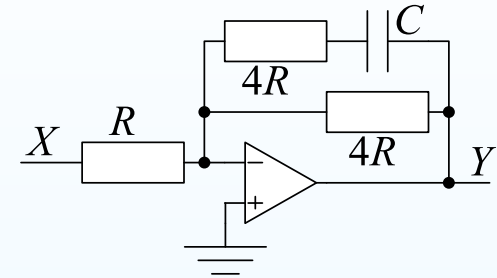
$$(-4 + A) - (0) = -2 \Rightarrow A = 2$$




Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

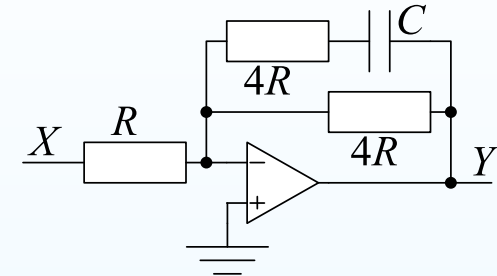

Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$

$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$

Steady State + Transient

$$t \geq 0: y = -4 + Ae^{-t/\tau}$$



Discontinuity Gain (= HF Gain)

$$y(0+) - y(0-) = -2(x(0+) - x(0-)) = -2$$

$$(-4 + A) - (0) = -2 \Rightarrow A = 2$$

Complete Expression

$$t \geq 0: y(t) = -4 + 2e^{-t/8RC}$$

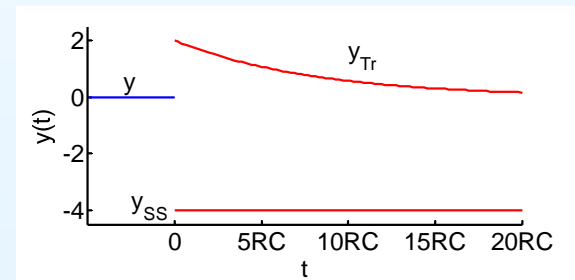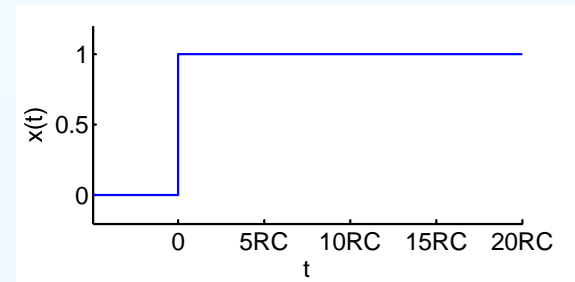


Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

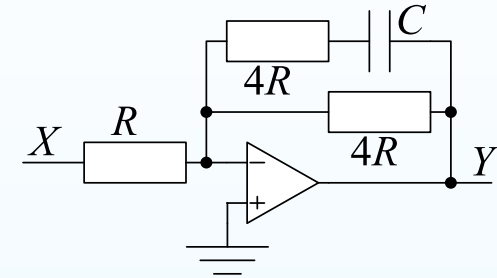

Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$

$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$

Steady State + Transient

$$t \geq 0: y = -4 + Ae^{-t/\tau}$$



Discontinuity Gain (= HF Gain)

$$y(0+) - y(0-) = -2(x(0+) - x(0-)) = -2$$

$$(-4 + A) - (0) = -2 \Rightarrow A = 2$$

Complete Expression

$$t \geq 0: y(t) = -4 + 2e^{-t/8RC}$$

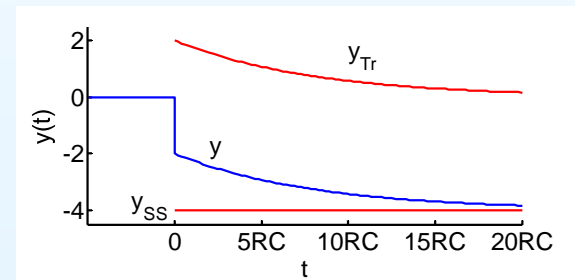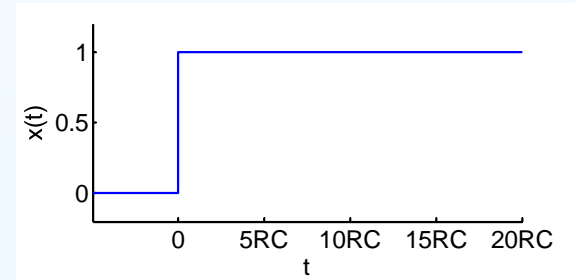


Opamp Circuit Transient

Calculate Transfer Function (Inverting Amplifier)

$$\frac{Y}{X} = -\frac{Z_F}{R} = -\frac{1}{R} \times \frac{4R(4R + \frac{1}{j\omega C})}{4R + (4R + \frac{1}{j\omega C})} = -4 \frac{4j\omega RC + 1}{8j\omega RC + 1}$$

DC gain: -4 , HF gain: -2 , $\tau = 8RC$

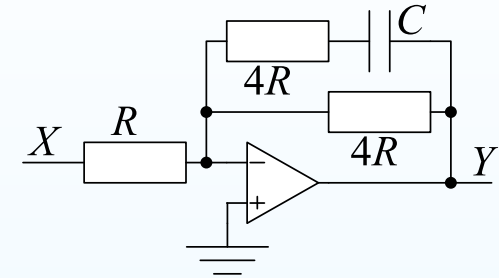

Steady State

$$t < 0: y_{SS}(t) = -4v(t) = 0$$

$$t \geq 0: y_{SS}(t) = -4v(t) = -4 \times 1 = -4$$

Steady State + Transient

$$t \geq 0: y = -4 + Ae^{-t/\tau}$$



Discontinuity Gain (= HF Gain)

$$y(0+) - y(0-) = -2(x(0+) - x(0-)) = -2$$

$$(-4 + A) - (0) = -2 \Rightarrow A = 2$$

Complete Expression

$$t \geq 0: y(t) = -4 + 2e^{-t/8RC}$$

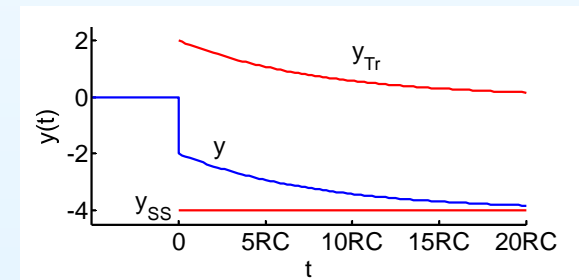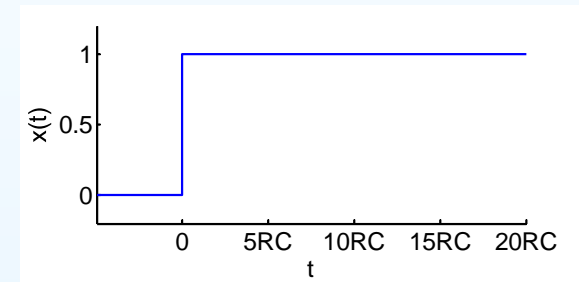

For opamp circuits get τ from the transfer function because R_{Th} is difficult to work out.

Summary

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- **Summary**

- **1st order transients: circuits with only one C or L**

Summary

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- **Summary**

- **1st order transients:** circuits with only one C or L
- Transients arise from **abrupt changes** in the frequency, phase or amplitude of the input signal or else a switch changing

Summary

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- **Summary**

- **1st order transients:** circuits with only one C or L
- Transients arise from **abrupt changes** in the frequency, phase or amplitude of the input signal or else a switch changing
- Output is **steady state + transient**

Summary

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- **Summary**

- **1st order transients:** circuits with only one C or L
- Transients arise from **abrupt changes** in the frequency, phase or amplitude of the input signal or else a switch changing
- Output is **steady state + transient**
- **Steady state:** nodal analysis \rightarrow transfer function

Summary

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- Summary

- **1st order transients:** circuits with only one C or L
- Transients arise from **abrupt changes** in the frequency, phase or amplitude of the input signal or else a switch changing
- Output is **steady state + transient**
- **Steady state:** nodal analysis \rightarrow transfer function
- **Transient:** $Ae^{-t/\tau}$ where:

Summary

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- **Summary**

- **1st order transients:** circuits with only one C or L
- Transients arise from **abrupt changes** in the frequency, phase or amplitude of the input signal or else a switch changing
- Output is **steady state + transient**
- **Steady state:** nodal analysis \rightarrow transfer function
- **Transient:** $Ae^{-t/\tau}$ where:
 - Two methods to find τ :
 - ▷ **Thévenin seen by L or C :** $\tau = R_{Th}C$ or $\frac{L}{R_{Th}}$
 - ▷ **Transfer function denominator:** $(aj\omega + b) \Rightarrow \tau = \frac{1}{\omega_c} = \frac{a}{b}$

Summary

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- **Summary**

- **1st order transients:** circuits with only one C or L
- Transients arise from **abrupt changes** in the frequency, phase or amplitude of the input signal or else a switch changing
- Output is **steady state + transient**
- **Steady state:** nodal analysis \rightarrow transfer function
- **Transient:** $Ae^{-t/\tau}$ where:
 - Two methods to find τ :
 - ▷ **Thévenin seen by L or C :** $\tau = R_{Th}C$ or $\frac{L}{R_{Th}}$
 - ▷ **Transfer function denominator:** $(aj\omega + b) \Rightarrow \tau = \frac{1}{\omega_c} = \frac{a}{b}$
 - Two methods to find A :
 - ▷ **Continuity:** $\Delta V_C = 0$ or $\Delta I_L = 0$
 - ▷ **Discontinuity gain:** $\Delta \text{output} = \text{HF gain} \times \Delta \text{input}$

Summary

16: Transients (B)

- Piecewise steady state inputs
- Sinusoidal Input
- Multiple Discontinuities
- Switched Circuit
- Transfer Function
- Transient from Transfer Function
- Opamp Circuit Transient
- **Summary**

- **1st order transients:** circuits with only one C or L
- Transients arise from **abrupt changes** in the frequency, phase or amplitude of the input signal or else a switch changing
- Output is **steady state + transient**
- **Steady state:** nodal analysis \rightarrow transfer function
- **Transient:** $Ae^{-t/\tau}$ where:
 - Two methods to find τ :
 - ▷ **Thévenin seen by L or C :** $\tau = R_{Th}C$ or $\frac{L}{R_{Th}}$
 - ▷ **Transfer function denominator:** $(aj\omega + b) \Rightarrow \tau = \frac{1}{\omega_c} = \frac{a}{b}$
 - Two methods to find A :
 - ▷ **Continuity:** $\Delta V_C = 0$ or $\Delta I_L = 0$
 - ▷ **Discontinuity gain:** $\Delta \text{output} = \text{HF gain} \times \Delta \text{input}$

For further details see Hayt Ch 8 or Irwin Ch 7.