

▷ **17: Transmission Lines**

- Transmission Lines**
- Transmission Line Equations** +
- Solution to Transmission Line Equations**
- Forward Wave**
- Forward + Backward Waves**
- Power Flow**
- Reflections**
- Reflection Coefficients**
- Driving a line**
- Multiple Reflections**
- Transmission Line Characteristics** +
- Summary**

17: Transmission Lines

Transmission Lines

17: Transmission Lines

▷ Transmission Lines

Transmission Line Equations +

Solution to Transmission Line Equations

Forward Wave

Forward + Backward Waves

Power Flow

Reflections


Reflection Coefficients

Driving a line

Multiple Reflections

Transmission Line Characteristics +

Summary

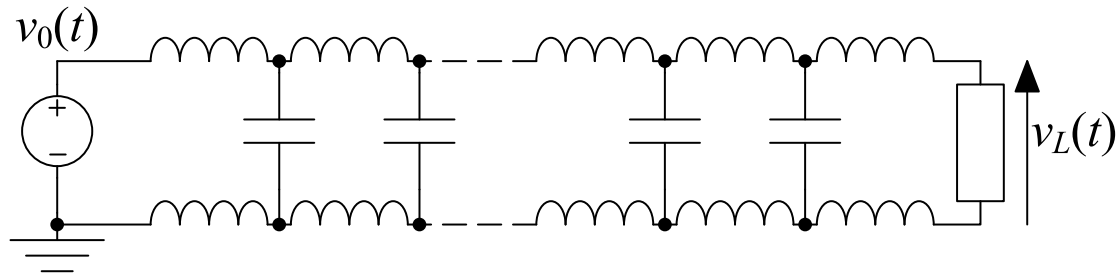

Previously assume that any change in $v_0(t)$ appears instantly at $v_L(t)$.

This is not true.

In fact signals travel at around half the speed of light ($c = 30 \text{ cm/ns}$).

Reason: all wires have capacitance to ground and to neighbouring conductors and also self-inductance. It takes time to change the current through an inductor or voltage across a capacitor.

A *transmission line* is a wire with a uniform geometry along its length: the capacitance and inductance of any segment is proportional to its length. We represent as a large number of small inductors and capacitors spaced along the line.

The signal speed along a transmission line is predictable.


- 17: Transmission Lines
- Transmission Lines
- Transmission Line Equations +
- Solution to Transmission Line Equations
- Forward Wave
- Forward + Backward Waves
- Power Flow
- Reflections
- Reflection Coefficients
- Driving a line
- Multiple Reflections
- Transmission Line Characteristics +
- Summary

A short section of line δx long:

$v(x, t)$ and $i(x, t)$ depend on both position and time.

Small $\delta x \Rightarrow$ ignore 2nd order derivatives:
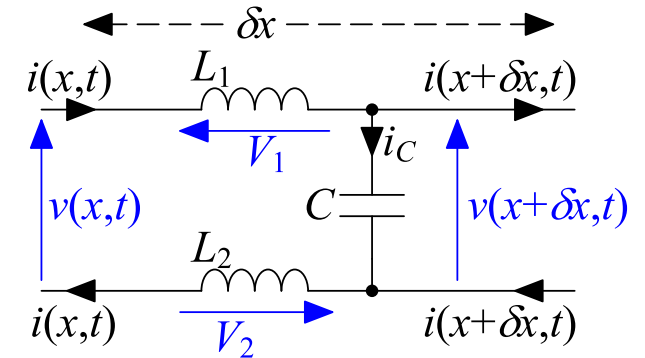
$$\frac{\partial v(x, t)}{\partial t} = \frac{\partial v(x + \delta x, t)}{\partial t} \triangleq \frac{\partial v}{\partial t}$$



Basic Equations

KVL: $v(x, t) = V_2 + v(x + \delta x, t) + V_1$

KCL: $i(x, t) = i_C + i(x + \delta x, t)$

Capacitor equation: $C \frac{\partial v}{\partial t} = i_C = i(x, t) - i(x + \delta x, t) = -\frac{\partial i}{\partial x} \delta x$

Inductor equation (L_1 and L_2 have the same current):

$$(L_1 + L_2) \frac{\partial i}{\partial t} = V_1 + V_2 = v(x, t) - v(x + \delta x, t) = -\frac{\partial v}{\partial x} \delta x$$

Transmission Line Equations

$$C_0 \frac{\partial v}{\partial t} = -\frac{\partial i}{\partial x}$$

$$L_0 \frac{\partial i}{\partial t} = -\frac{\partial v}{\partial x}$$

where $C_0 = \frac{C}{\delta x}$ is the capacitance per unit length (Farads/m) and $L_0 = \frac{L_1 + L_2}{\delta x}$ is the total inductance per unit length (Henries/m).

[Partial Derivatives]

When we differentiate a function of two variables, we keep one of the variables fixed while differentiating with respect to the other; this is called a partial derivative and is written with a curly version of the letter “ d ”. Thus

$$\frac{\partial v}{\partial x} \triangleq \lim_{\delta x \rightarrow 0} \frac{v(x + \delta x, t) - v(x, t)}{\delta x} \quad \text{and} \quad \frac{\partial v}{\partial t} \triangleq \lim_{\delta t \rightarrow 0} \frac{v(x, t + \delta t) - v(x, t)}{\delta t}.$$

Higher order derivatives may be obtained by differentiating the partial derivatives again to give

$$\frac{\partial^2 v}{\partial x^2} \triangleq \frac{\partial}{\partial x} \left(\frac{\partial v}{\partial x} \right), \quad \frac{\partial^2 v}{\partial t^2} \triangleq \frac{\partial}{\partial t} \left(\frac{\partial v}{\partial t} \right) \quad \text{and} \quad \frac{\partial^2 v}{\partial x \partial t} \triangleq \frac{\partial}{\partial x} \left(\frac{\partial v}{\partial t} \right).$$

Provided the second order partial derivatives are continuous, the order of differentiation doesn't matter so that $\frac{\partial^2 v}{\partial x \partial t} = \frac{\partial^2 v}{\partial t \partial x}$.

If we take the normal Taylor series with respect to x , $v(x + \delta x, t) = v(x, t) + \frac{\partial v(x, t)}{\partial x} \delta x + O(\delta x^2)$, and differentiate each term with respect to t , we get

$$\frac{\partial v(x + \delta x, t)}{\partial t} = \frac{\partial v(x, t)}{\partial t} + \frac{\partial^2 v(x, t)}{\partial t \partial x} \delta x + O(\delta x^2).$$

If $\delta x \rightarrow 0$, then we get $\frac{\partial v(x + \delta x, t)}{\partial t} \rightarrow \frac{\partial v(x, t)}{\partial t}$ as assumed on the previous slide.

[Deriving the Transmission Line Equations]

This note provides slightly more detail about how we derive the transmission line equations. By expanding $v(x + \delta x, t)$ and $i(x + \delta x, t)$ as Taylor Series in x , we can write

$$v(x + \delta x, t) = v(x, t) + \delta x \frac{\partial v}{\partial x}(x, t) + O(\delta x^2) \quad \text{and} \quad i(x + \delta x, t) = i(x, t) + \delta x \frac{\partial i}{\partial x}(x, t) + O(\delta x^2).$$

From the diagram on the previous page, the voltage across the capacitor is $v(x + \delta x, t)$ and so the capacitor equation is

$$C \frac{\partial v}{\partial t}(x + \delta x, t) = i(x, t) - i(x + \delta x, t).$$

Substituting in the Taylor series expansions for $v(x + \delta x, t)$ and $i(x + \delta x, t)$ and also substituting $C = C_0 \delta x$ results in

$$\begin{aligned} C_0 \delta x \left(\frac{\partial v}{\partial t}(x, t) + \delta x \frac{\partial^2 v}{\partial x \partial t}(x, t) + O(\delta x^2) \right) &= -\delta x \frac{\partial i}{\partial x}(x, t) - O(\delta x^2) \\ \Rightarrow C_0 \left(\frac{\partial v}{\partial t}(x, t) + \delta x \frac{\partial^2 v}{\partial x \partial t}(x, t) + O(\delta x^2) \right) &= -\frac{\partial i}{\partial x}(x, t) - O(\delta x). \end{aligned}$$

Finally, we let $\delta x \rightarrow 0$ and so all the terms that are $O(\delta x)$ or smaller disappear which leaves

$$C_0 \frac{\partial v}{\partial t}(x, t) = -\frac{\partial i}{\partial x}(x, t).$$

The inductor equation, $L_0 \frac{\partial i}{\partial t} = -\frac{\partial v}{\partial x}$, can be derived in a similar way.

Solution to Transmission Line Equations

17: Transmission Lines

Transmission Lines Transmission Line Equations +

Solution to Transmission Line Equations

Forward Wave Forward + Backward Waves

Power Flow

Reflections

Reflection Coefficients

Driving a line

Multiple Reflections

Transmission Line Characteristics +

Summary

$$\text{Transmission Line Equations: } C_0 \frac{\partial v}{\partial t} = -\frac{\partial i}{\partial x} \quad L_0 \frac{\partial i}{\partial t} = -\frac{\partial v}{\partial x}$$

$$\text{General solution: } v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$$

$$i(t, x) = \frac{f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right)}{Z_0}$$

$$\text{where } u = \sqrt{\frac{1}{L_0 C_0}} \text{ and } Z_0 = \sqrt{\frac{L_0}{C_0}} .$$

u is the *propagation velocity* and Z_0 is the *characteristic impedance*.

$f()$ and $g()$ can be *any* differentiable functions.

Verify by substitution:

$$\begin{aligned} -\frac{\partial i}{\partial x} &= -\left(\frac{-f'\left(t - \frac{x}{u}\right) - g'\left(t + \frac{x}{u}\right)}{Z_0} \times \frac{1}{u} \right) \\ &= C_0 \left(f'\left(t - \frac{x}{u}\right) + g'\left(t + \frac{x}{u}\right) \right) = C_0 \frac{\partial v}{\partial t} \end{aligned}$$

Forward Wave

- 17: Transmission Lines
- Transmission Lines
- Transmission Line Equations +
- Solution to Transmission Line Equations
- ▷ Forward Wave
- Forward + Backward Waves
- Power Flow
- Reflections
- Reflection Coefficients
- Driving a line
- Multiple Reflections
- Transmission Line Characteristics +
- Summary

Suppose:

$$u = 15 \text{ cm/ns}$$

$$\text{and } g(t) \equiv 0$$

$$\Rightarrow v(x, t) = f\left(t - \frac{x}{u}\right)$$



- At $x = 0 \text{ cm}$ [▲],
 $v_S(t) = f\left(t - \frac{0}{u}\right)$
- At $x = 45 \text{ cm}$ [▲],
 $v(45, t) = f\left(t - \frac{45}{u}\right)$
 $f\left(t - \frac{45}{u}\right)$ is exactly the same as $f(t)$ but delayed by $\frac{45}{u} = 3 \text{ ns}$.
- At $x = 90 \text{ cm}$ [▲], $v_R(t) = f\left(t - \frac{90}{u}\right)$; now delayed by 6 ns.

Waveform at $x = 0$ completely determines the waveform everywhere else.

Snapshot at $t_0 = 4 \text{ ns}$:

the waveform has just arrived at the point
 $x = ut_0 = 60 \text{ cm}$.

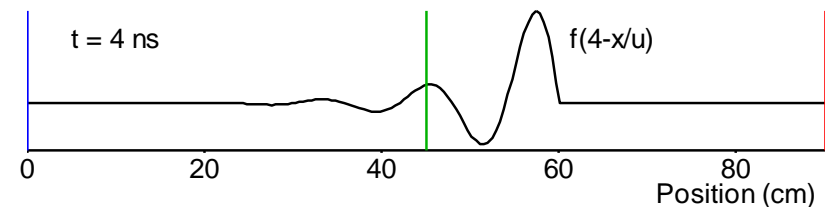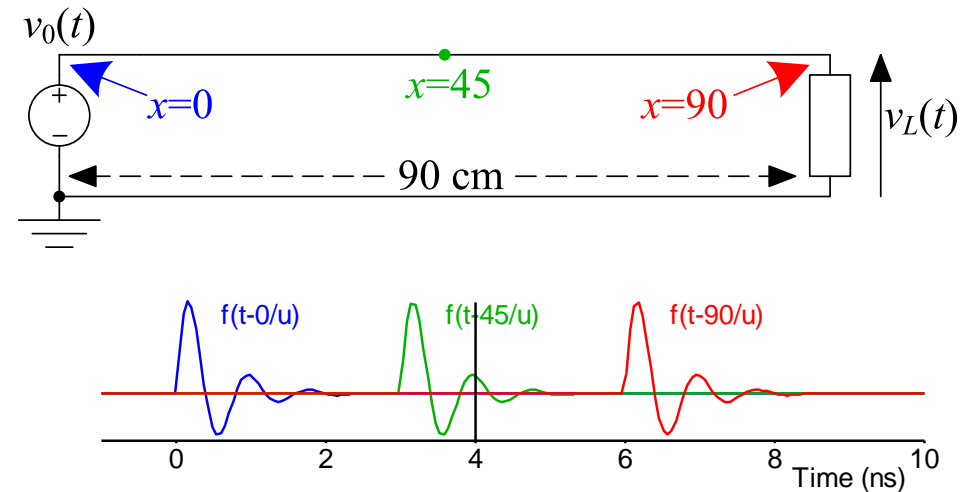$f\left(t - \frac{x}{u}\right)$ is a wave travelling forward (i.e. towards $+x$) along the line.



Forward + Backward Waves


- 17: Transmission Lines
- Transmission Lines
- Transmission Line Equations +
- Solution to Transmission Line Equations
- Forward Wave
- ▷ Forward + Backward Waves
- Power Flow
- Reflections
- Reflection Coefficients
- Driving a line
- Multiple Reflections
- Transmission Line Characteristics +
- Summary

Similarly $g(t + \frac{x}{u})$ is a wave travelling backwards, i.e. in the $-x$ direction.

$$v(x, t) = f(t - \frac{x}{u}) + g(t + \frac{x}{u})$$

At $x = 0$ cm [▲],

$$v_S(t) = f(t) + g(t)$$

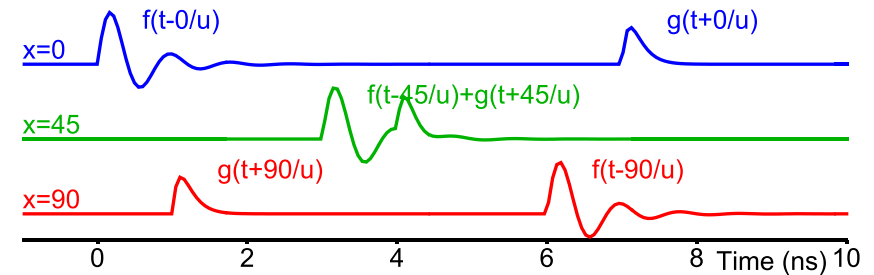


At $x = 45$ cm [▲], g is only 1 ns behind f and they add together.

At $x = 90$ cm [▲], g starts at $t = 1$ and f starts at $t = 6$.

A vertical line on the diagram gives a **snapshot** of the entire line at a time instant t .

f and g first meet at $t = 3.5$ and $x = 52.5$.

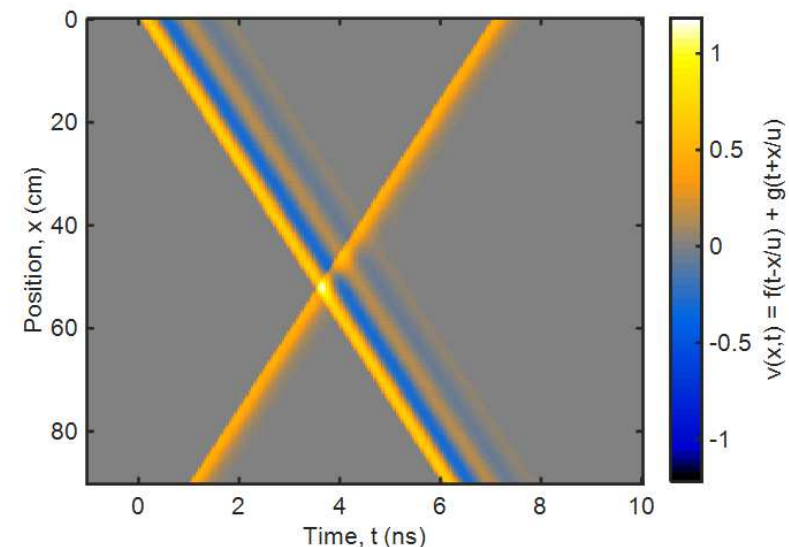
Magically, f and g pass through each other entirely unaltered.



Power Flow

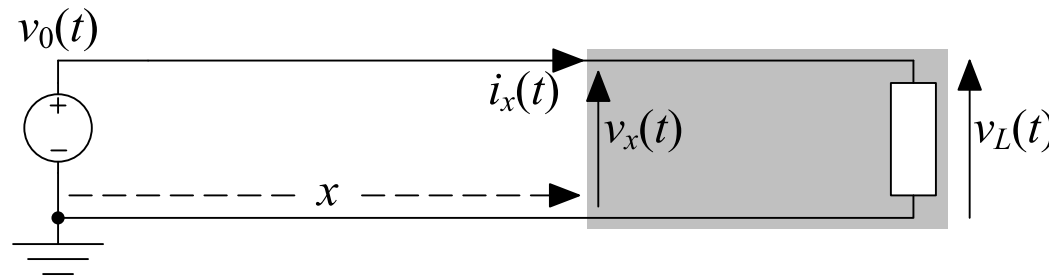- 17: Transmission Lines
- Transmission Lines
- Transmission Line Equations +
- Solution to Transmission Line Equations
- Forward Wave
- Forward + Backward Waves
- ▷ Power Flow
- Reflections
- Reflection Coefficients
- Driving a line
- Multiple Reflections
- Transmission Line Characteristics +
- Summary

Define $f_x(t) = f(t - \frac{x}{u})$ and $g_x(t) = g(t + \frac{x}{u})$ to be the forward and backward waveforms at any point, x .



i is **always** measured in the +ve x direction.

Then $v_x(t) = f_x(t) + g_x(t)$ and $i_x(t) = Z_0^{-1} (f_x(t) - g_x(t))$.

Note: Knowing the waveform $f_x(t)$ or $g_x(t)$ at any position x , tells you it at all other positions: $f_y(t) = f_x(t - \frac{y-x}{u})$ and $g_y(t) = g_x(t + \frac{y-x}{u})$.

Power Flow

The power transferred into the shaded region across the boundary at x is

$$P_x(t) = v_x(t)i_x(t) = Z_0^{-1} (f_x(t) + g_x(t))(f_x(t) - g_x(t))$$

$$= \frac{f_x^2(t)}{Z_0} - \frac{g_x^2(t)}{Z_0}$$


f_x carries power **into** shaded area and g_x carries power **out** independently.

Power travels in the **same direction as the wave**.

The same power as would be absorbed by a [fictitious] resistor of value Z_0 .

Reflections

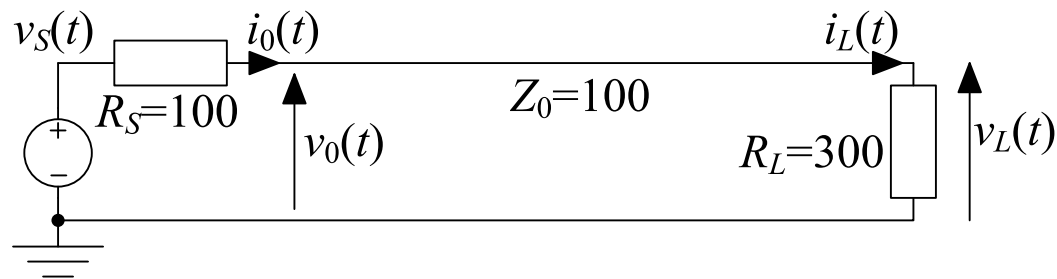- 17: Transmission Lines
- Transmission Lines
- Transmission Line Equations +
- Solution to Transmission Line Equations
- Forward Wave
- Forward + Backward Waves
- Power Flow
- ▷ Reflections
- Reflection Coefficients
- Driving a line
- Multiple Reflections
- Transmission Line Characteristics +
- Summary



$$v_x = f_x + g_x$$

$$i_x = Z_0^{-1} (f_x - g_x)$$

From Ohm's law at $x = L$, we have $v_L(t) = i_L(t)R_L$



Hence $(f_L(t) + g_L(t)) = Z_0^{-1} (f_L(t) - g_L(t)) R_L$

From this: $g_L(t) = \frac{R_L - Z_0}{R_L + Z_0} \times f_L(t)$

We define the *reflection coefficient*: $\rho_L = \frac{g_L(t)}{f_L(t)} = \frac{R_L - Z_0}{R_L + Z_0} = +0.5$

Substituting $g_L(t) = \rho_L f_L(t)$ gives
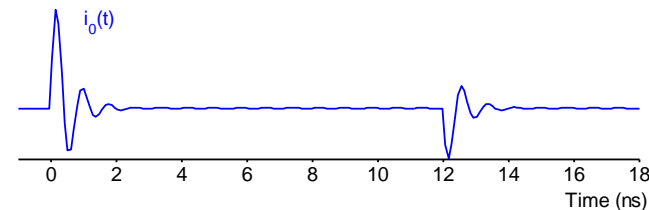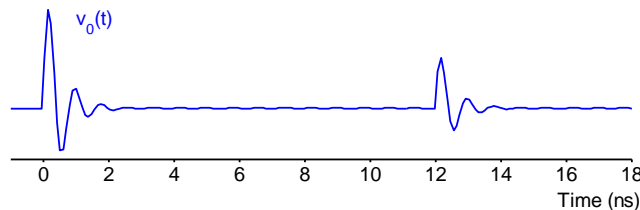
$$v_L(t) = (1 + \rho_L) f_L(t) \text{ and } i_L(t) = (1 - \rho_L) Z_0^{-1} f_L(t)$$



At source end: $g_0(t) = \rho_L f_0(t - \frac{2L}{u})$ i.e. delayed by $\frac{2L}{u} = 12$ ns.

Note that the reflected **current** has been multiplied by $-\rho$.

Reflection Coefficients


- 17: Transmission Lines
- Transmission Lines
- Transmission Line Equations +
- Solution to Transmission Line Equations
- Forward Wave
- Forward + Backward Waves
- Power Flow
- Reflections
- ▷ Reflection Coefficients
- Driving a line
- Multiple Reflections
- Transmission Line Characteristics +
- Summary

$$\rho = \frac{R - Z_0}{R + Z_0} = \frac{\frac{R}{Z_0} - 1}{\frac{R}{Z_0} + 1}$$

$$\frac{v_L(t)}{f(t)} = 1 + \rho$$

$$\frac{i_L(t)Z_0}{f(t)} = 1 - \rho$$

ρ depends on the ratio $\frac{R}{Z_0}$.

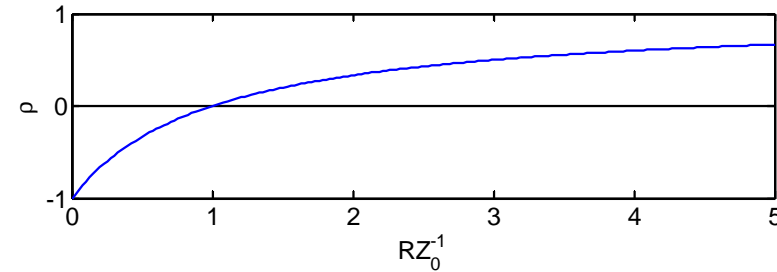

$\frac{R}{Z_0}$	ρ	$\frac{v_L(t)}{f(t)}$	$\frac{i_L(t)Z_0}{f(t)}$	Comment
∞	+1	2	0	Open circuit: $v_L = 2f$, $i_L \equiv 0$
3	+0.5	1.5	0.5	$R > Z_0 \Rightarrow \rho > 0$
1	0	1	1	Matched: No reflection at all
$\frac{1}{3}$	-0.5	0.5	1.5	$R < Z_0 \Rightarrow \rho < 0$
0	-1	0	2	Short circuit: $v_L \equiv 0$, $i_L = \frac{2f}{Z_0}$

Note: Reverse mapping is $R = \frac{v_L}{i_L} = \frac{1+\rho}{1-\rho} \times Z_0$


Remember: $\rho \in \{-1, +1\}$ and increases with R .



Driving a line

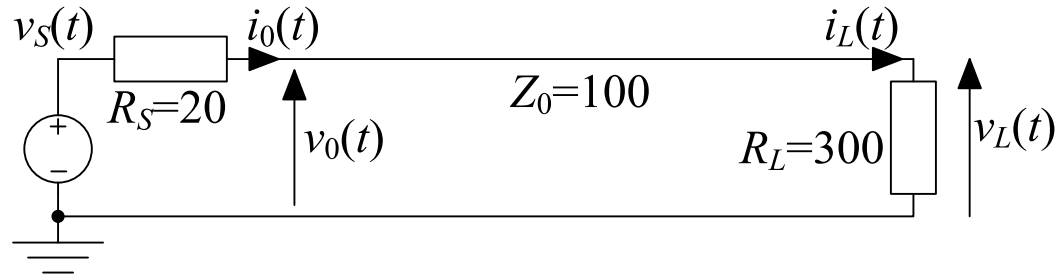17: Transmission Lines

- Transmission Lines
- Transmission Line Equations +
- Solution to Transmission Line Equations
- Forward Wave
- Forward + Backward Waves
- Power Flow
- Reflections
- Reflection Coefficients
- ▷ Driving a line
- Multiple Reflections
- Transmission Line Characteristics +
- Summary



$$v_x = f_x + g_x$$

$$i_x = \frac{f_x - g_x}{Z_0}$$

From Ohm's law at $x = 0$, we have $v_0(t) = v_S(t) - i_0(t)R_S$ where R_S is the Thévenin resistance of the voltage source.

Substituting $v_0(t) = f_0 + g_0$ and $i_0(t) = \frac{f_0 - g_0}{Z_0}$ leads to:

$$f_0(t) = \frac{Z_0}{R_S + Z_0} v_S(t) + \frac{R_S - Z_0}{R_S + Z_0} g_0(t) \triangleq \tau_0 v_S(t) + \rho_0 g_0(t)$$


So $f_0(t)$ is the superposition of two terms:

- (1) Input $v_S(t)$ multiplied by $\tau_0 = \frac{Z_0}{R_S + Z_0}$ which is the same as a potential divider if you replace the line with a [fictitious] resistor Z_0 .
- (2) The incoming backward wave, $g_0(t)$, multiplied by a reflection coefficient: $\rho_0 = \frac{R_S - Z_0}{R_S + Z_0}$.

For $R_S = 20$: $\tau_0 = \frac{100}{20+100} = 0.83$ and $\rho_0 = \frac{20-100}{20+100} = -0.67$.

Multiple Reflections

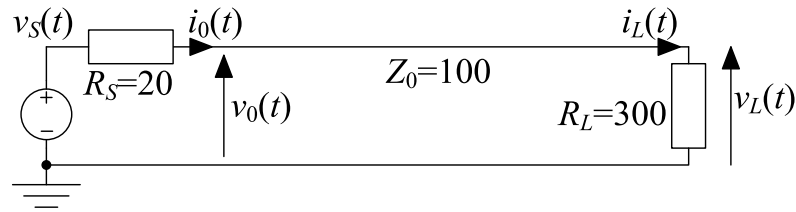- 17: Transmission Lines
- Transmission Lines
- Transmission Line Equations +
- Solution to Transmission Line Equations
- Forward Wave
- Forward + Backward Waves
- Power Flow
- Reflections
- Reflection Coefficients
- Driving a line
 - Multiple Reflections
- Transmission Line Characteristics +
- Summary



$$\rho_0 = -\frac{2}{3}$$

$$\rho_L = \frac{1}{2}$$

$$v_x = f_x + g_x$$





Each extra bit of f_0 is delayed by $\frac{2L}{u}$ ($=12$ ns) and multiplied by $\rho_L \rho_0$:

$$f_0(t) = \sum_{i=0}^{\infty} \tau_0 \rho_L^i \rho_0^i v_S \left(t - \frac{2Li}{u} \right)$$

$$g_L(t) = \rho_L f_0 \left(t - \frac{L}{u} \right)$$

$$v_0(t) = f_0(t) + g_L \left(t - \frac{L}{u} \right)$$
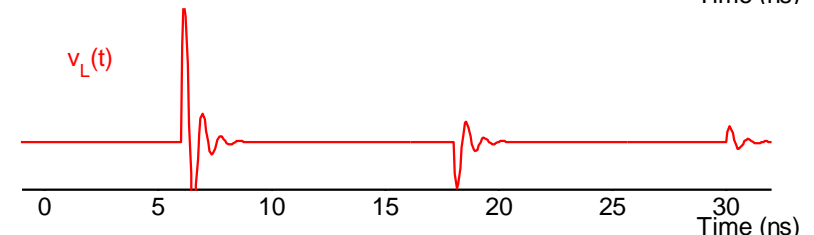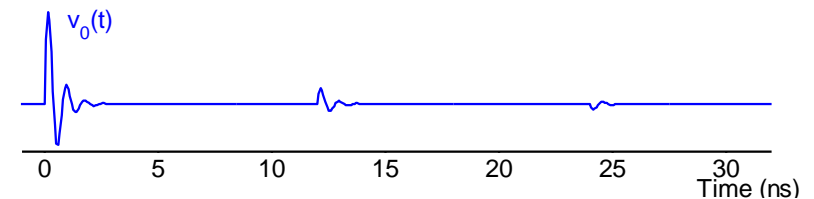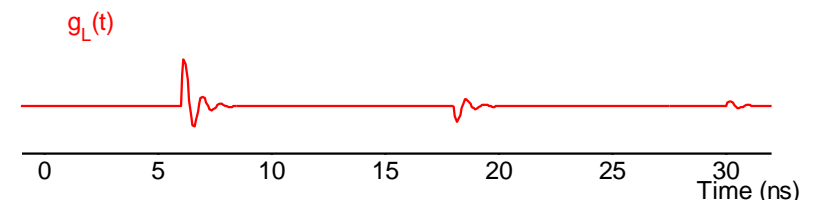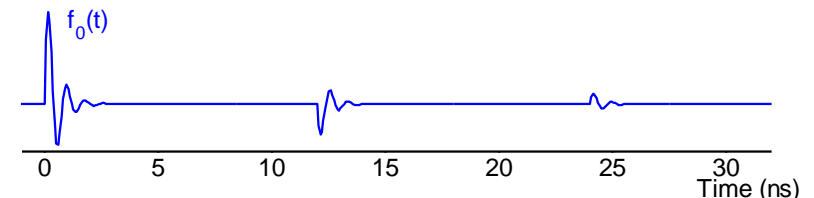
$$v_L(t) = f_0 \left(t - \frac{L}{u} \right) + g_L(t)$$



17: Transmission Lines

Transmission Lines
Transmission Line Equations +

Solution to
Transmission Line Equations

Forward Wave
Forward + Backward Waves

Power Flow

Reflections
Reflection Coefficients

Driving a line

Multiple Reflections

Transmission Line
Characteristics +

Summary

Integrated circuits & Printed circuit boards

High speed digital or high frequency analog interconnections

$$Z_0 \approx 100 \Omega, u \approx 15 \text{ cm/ns.}$$

Long Cables

Coaxial cable ("coax"): unaffected by external fields; use for antennae and instrumentation.




$$Z_0 = 50 \text{ or } 75 \Omega, u \approx 25 \text{ cm/ns.}$$

Twisted Pairs: cheaper and thinner than coax and resistant to magnetic fields; use for computer network and telephone cabling. $Z_0 \approx 100 \Omega, u \approx 19 \text{ cm/ns.}$

When do you have to bother?


Answer: **long cables or high frequencies**. You can completely ignore transmission line effects if $\text{length} \ll \frac{u}{\text{frequency}} = \text{wavelength}$.

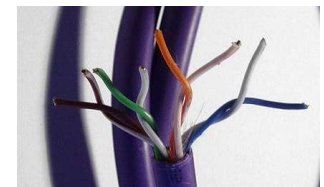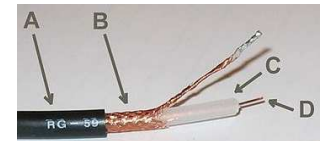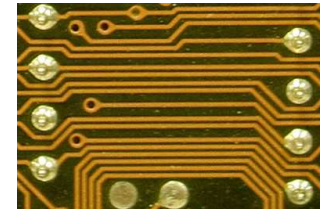- Audio ($< 20 \text{ kHz}$) never matters.
- Computers (1 GHz) usually matters.
- Radio/TV usually matters.




[Transmission Line Grounds]

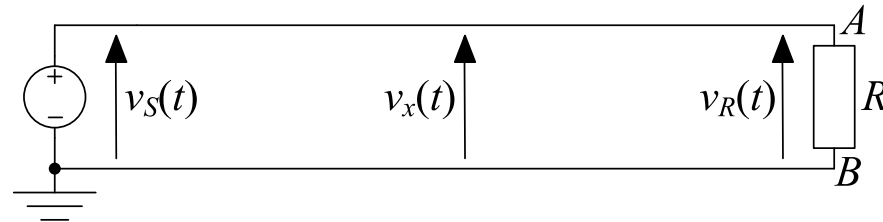For long coaxial or twisted pair cables, the “ground” wire has significant inductance and so its two ends are not necessarily at the same voltage. This means that $v_x(t)$, $f_x(t)$ and $g_x(t)$ are measured relative to the “ground” at position x as shown. It follows that potential differences like $v_R(t) = v_A(t) - v_B(t)$ make sense but talking about $v_A(t)$ on its own is meaningless.



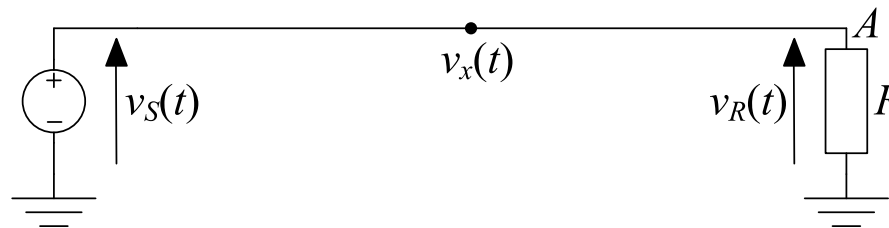Integrated circuits and printed circuit boards normally have a low impedance “ground plane” covering the entire circuit; in a multilayer printed circuit board this typically forms one entire layer. In this case we have a single ground reference for the whole circuit and it now makes sense to talk about the voltage “at” a node and to say $v_R(t) = v_A(t)$.



Summary

17: Transmission Lines

Transmission Lines
Transmission Line Equations +

Solution to
Transmission Line Equations

Forward Wave
Forward + Backward Waves

Power Flow

Reflections
Reflection Coefficients

Driving a line
Multiple Reflections

Transmission Line Characteristics +

▷ Summary

- Signals travel at around $u \approx \frac{1}{2}c = 15 \text{ cm/ns}$.
Only matters for high frequencies or long cables.

- **Forward and backward waves** travel along the line:

$$f_x(t) = f_0 \left(t - \frac{x}{u} \right) \quad \text{and} \quad g_x(t) = g_0 \left(t + \frac{x}{u} \right)$$

- Knowing f_x and g_x at **any single x position** tells you everything
- **Voltage and current** are: $v_x = f_x + g_x$ and $i_x = \frac{f_x - g_x}{Z_0}$
- **Terminating line with R** at $x = L$ links the forward and backward waves:
 - backward wave is $g_L = \rho_L f_L$ where $\rho_L = \frac{R - Z_0}{R + Z_0}$
 - the **reflection coefficient**, $\rho_L \in \{-1, +1\}$ and increases with R
 - $R = Z_0$ avoids reflections: **matched** termination.
 - Reflections go on for ever unless one or both ends are matched.
 - f is infinite sum of copies of the input signal delayed successively by the round-trip delay, $\frac{2L}{u}$, and multiplied by $\rho_L \rho_0$.