

18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

18: Phasors and Transmission Lines

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line:

$$v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right) \quad \text{and}$$
$$i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$$

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line: $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$ and
 $i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$

We can use phasors to eliminate t from the equations if $f()$ and $g()$ are sinusoidal with the same ω

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line: $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$ and
 $i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$

We can use phasors to eliminate t from the equations if $f()$ and $g()$ are sinusoidal with the same ω : $f(t) = A \cos(\omega t + \phi) \Rightarrow F = Ae^{j\phi}$.

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line: $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$ and
 $i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$

We can use phasors to eliminate t from the equations **if $f()$ and $g()$ are sinusoidal with the same ω** : $f(t) = A \cos(\omega t + \phi) \Rightarrow F = Ae^{j\phi}$.

Then $f_x(t) = f\left(t - \frac{x}{u}\right) = A \cos\left(\omega\left(t - \frac{x}{u}\right) + \phi\right)$

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line: $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$ and
 $i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$

We can use phasors to eliminate t from the equations if $f()$ and $g()$ are sinusoidal with the same ω : $f(t) = A \cos(\omega t + \phi) \Rightarrow F = Ae^{j\phi}$.

Then $f_x(t) = f\left(t - \frac{x}{u}\right) = A \cos\left(\omega\left(t - \frac{x}{u}\right) + \phi\right)$

$$\Rightarrow F_x = Ae^{j\left(-\frac{\omega}{u}x + \phi\right)}$$

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line: $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$ and
 $i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$

We can use phasors to eliminate t from the equations if $f()$ and $g()$ are sinusoidal with the same ω : $f(t) = A \cos(\omega t + \phi) \Rightarrow F = Ae^{j\phi}$.

Then $f_x(t) = f\left(t - \frac{x}{u}\right) = A \cos\left(\omega\left(t - \frac{x}{u}\right) + \phi\right)$

$$\Rightarrow F_x = Ae^{j\left(-\frac{\omega}{u}x + \phi\right)} = Ae^{j\phi} e^{-j\frac{\omega}{u}x}$$

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line: $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$ and
 $i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$

We can use phasors to eliminate t from the equations if $f()$ and $g()$ are sinusoidal with the same ω : $f(t) = A \cos(\omega t + \phi) \Rightarrow F = Ae^{j\phi}$.

Then $f_x(t) = f\left(t - \frac{x}{u}\right) = A \cos\left(\omega\left(t - \frac{x}{u}\right) + \phi\right)$

$$\Rightarrow F_x = Ae^{j\left(-\frac{\omega}{u}x + \phi\right)} = Ae^{j\phi} e^{-j\frac{\omega}{u}x} = F_0 e^{-jkx}$$

where the *wavenumber* is $k \triangleq \frac{\omega}{u}$.

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line: $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$ and
 $i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$

We can use phasors to eliminate t from the equations if $f()$ and $g()$ are sinusoidal with the same ω : $f(t) = A \cos(\omega t + \phi) \Rightarrow F = Ae^{j\phi}$.

Then $f_x(t) = f\left(t - \frac{x}{u}\right) = A \cos\left(\omega\left(t - \frac{x}{u}\right) + \phi\right)$

$$\Rightarrow F_x = Ae^{j\left(-\frac{\omega}{u}x + \phi\right)} = Ae^{j\phi} e^{-j\frac{\omega}{u}x} = F_0 e^{-jkx}$$

where the *wavenumber* is $k \triangleq \frac{\omega}{u}$.

Units: ω is “radians per second”, k is “radians per metre” (note $k \propto \omega$).

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line: $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$ and
 $i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$

We can use phasors to eliminate t from the equations if $f()$ and $g()$ are sinusoidal with the same ω : $f(t) = A \cos(\omega t + \phi) \Rightarrow F = Ae^{j\phi}$.

Then $f_x(t) = f\left(t - \frac{x}{u}\right) = A \cos\left(\omega\left(t - \frac{x}{u}\right) + \phi\right)$

$$\Rightarrow F_x = Ae^{j\left(-\frac{\omega}{u}x + \phi\right)} = Ae^{j\phi} e^{-j\frac{\omega}{u}x} = F_0 e^{-jkx}$$

where the *wavenumber* is $k \triangleq \frac{\omega}{u}$.

Units: ω is “radians per second”, k is “radians per metre” (note $k \propto \omega$).

Similarly $G_x = G_0 e^{+jkx}$.

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line: $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$ and
 $i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$

We can use phasors to eliminate t from the equations if $f()$ and $g()$ are sinusoidal with the same ω : $f(t) = A \cos(\omega t + \phi) \Rightarrow F = Ae^{j\phi}$.

Then $f_x(t) = f\left(t - \frac{x}{u}\right) = A \cos\left(\omega\left(t - \frac{x}{u}\right) + \phi\right)$

$$\Rightarrow F_x = Ae^{j\left(-\frac{\omega}{u}x + \phi\right)} = Ae^{j\phi} e^{-j\frac{\omega}{u}x} = F_0 e^{-jkx}$$

where the *wavenumber* is $k \triangleq \frac{\omega}{u}$.

Units: ω is “radians per second”, k is “radians per metre” (note $k \propto \omega$).

Similarly $G_x = G_0 e^{+jkx}$.

Everything is time-invariant: **phasors do not depend on t .**

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line: $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$ and
 $i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$

We can use phasors to eliminate t from the equations if $f()$ and $g()$ are sinusoidal with the same ω : $f(t) = A \cos(\omega t + \phi) \Rightarrow F = Ae^{j\phi}$.

Then $f_x(t) = f\left(t - \frac{x}{u}\right) = A \cos\left(\omega\left(t - \frac{x}{u}\right) + \phi\right)$

$$\Rightarrow F_x = Ae^{j\left(-\frac{\omega}{u}x + \phi\right)} = Ae^{j\phi} e^{-j\frac{\omega}{u}x} = F_0 e^{-jkx}$$

where the *wavenumber* is $k \triangleq \frac{\omega}{u}$.

Units: ω is “radians per second”, k is “radians per metre” (note $k \propto \omega$).

Similarly $G_x = G_0 e^{+jkx}$.

Everything is time-invariant: **phasors do not depend on t** .

Nice things about sine waves:

(1) a time delay is just a phase shift

Phasors and transmission lines

18: Phasors and
Transmission Lines

● Phasors and transmission
lines

- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

For a transmission line: $v(t, x) = f\left(t - \frac{x}{u}\right) + g\left(t + \frac{x}{u}\right)$ and
 $i(t, x) = Z_0^{-1} \left(f\left(t - \frac{x}{u}\right) - g\left(t + \frac{x}{u}\right) \right)$

We can use phasors to eliminate t from the equations if $f()$ and $g()$ are sinusoidal with the same ω : $f(t) = A \cos(\omega t + \phi) \Rightarrow F = Ae^{j\phi}$.

Then $f_x(t) = f\left(t - \frac{x}{u}\right) = A \cos\left(\omega\left(t - \frac{x}{u}\right) + \phi\right)$

$$\Rightarrow F_x = Ae^{j\left(-\frac{\omega}{u}x + \phi\right)} = Ae^{j\phi} e^{-j\frac{\omega}{u}x} = F_0 e^{-jkx}$$

where the *wavenumber* is $k \triangleq \frac{\omega}{u}$.

Units: ω is “radians per second”, k is “radians per metre” (note $k \propto \omega$).

Similarly $G_x = G_0 e^{+jkx}$.

Everything is time-invariant: **phasors do not depend on t .**

Nice things about sine waves:

- (1) a time delay is just a phase shift
- (2) sum of delayed sine waves is another sine wave

Phasor Relationships

Time Domain	Phasor	Notes
$f(t) = A \cos(\omega t + \phi)$	$F = Ae^{j\phi}$	F indep of t

Phasor Relationships

Time Domain	Phasor	Notes
$f(t) = A \cos(\omega t + \phi)$ $f_x(t) = f\left(t - \frac{x}{u}\right)$	$F = Ae^{j\phi}$	F indep of t

Phasor Relationships

Time Domain	Phasor	Notes
$f(t) = A \cos(\omega t + \phi)$ $f_x(t) = f\left(t - \frac{x}{u}\right)$ $= A \cos\left(\omega t + \phi - \frac{\omega}{u}x\right)$	$F = Ae^{j\phi}$	F indep of t

Phasor Relationships

Time Domain	Phasor	Notes
$f(t) = A \cos(\omega t + \phi)$ $f_x(t) = f\left(t - \frac{x}{u}\right)$ $= A \cos\left(\omega t + \phi - \frac{\omega}{u}x\right)$	$F = Ae^{j\phi}$ $F_x = Ae^{j\left(\phi - \frac{\omega}{u}x\right)}$	F indep of t

Phasor Relationships

Time Domain	Phasor	Notes
$f(t) = A \cos(\omega t + \phi)$ $f_x(t) = f\left(t - \frac{x}{u}\right)$ $= A \cos\left(\omega t + \phi - \frac{\omega}{u}x\right)$	$F = Ae^{j\phi}$ $F_x = Ae^{j\left(\phi - \frac{\omega}{u}x\right)}$ $= Fe^{-jkx}$	F indep of t

Phasor Relationships

Time Domain	Phasor	Notes
$f(t) = A \cos(\omega t + \phi)$	$F = Ae^{j\phi}$	F indep of t
$f_x(t) = f\left(t - \frac{x}{u}\right)$ $= A \cos\left(\omega t + \phi - \frac{\omega}{u}x\right)$	$F_x = Ae^{j\left(\phi - \frac{\omega}{u}x\right)}$ $= Fe^{-jkx}$	$ F_x \equiv F $ indep of x

Phasor Relationships

Time Domain	Phasor	Notes
$f(t) = A \cos(\omega t + \phi)$	$F = Ae^{j\phi}$	F indep of t
$f_x(t) = f\left(t - \frac{x}{u}\right)$ $= A \cos\left(\omega t + \phi - \frac{\omega}{u}x\right)$	$F_x = Ae^{j\left(\phi - \frac{\omega}{u}x\right)}$ $= Fe^{-jkx}$	$ F_x \equiv F $ indep of x
$f_y(t) = f_x\left(t - \frac{(y-x)}{u}\right)$	$F_y = F_x e^{-jk(y-x)}$	

Phasor Relationships

Time Domain	Phasor	Notes
$f(t) = A \cos(\omega t + \phi)$	$F = Ae^{j\phi}$	F indep of t
$f_x(t) = f\left(t - \frac{x}{u}\right)$ $= A \cos\left(\omega t + \phi - \frac{\omega}{u}x\right)$	$F_x = Ae^{j\left(\phi - \frac{\omega}{u}x\right)}$ $= Fe^{-jkx}$	$ F_x \equiv F $ indep of x
$f_y(t) = f_x\left(t - \frac{(y-x)}{u}\right)$	$F_y = F_x e^{-jk(y-x)}$	Delayed by $\frac{y-x}{u}$

Phasor Relationships

Time Domain	Phasor	Notes
$f(t) = A \cos(\omega t + \phi)$	$F = Ae^{j\phi}$	F indep of t
$f_x(t) = f\left(t - \frac{x}{u}\right)$ $= A \cos\left(\omega t + \phi - \frac{\omega}{u}x\right)$	$F_x = Ae^{j\left(\phi - \frac{\omega}{u}x\right)}$ $= Fe^{-jkx}$	$ F_x \equiv F $ indep of x
$f_y(t) = f_x\left(t - \frac{(y-x)}{u}\right)$ $g_y(t) = g_x\left(t + \frac{(y-x)}{u}\right)$	$F_y = F_x e^{-jk(y-x)}$ $G_y = G_x e^{+jk(y-x)}$	Delayed by $\frac{y-x}{u}$ Advanced by $\frac{y-x}{u}$

Phasor Relationships

Time Domain	Phasor	Notes
$f(t) = A \cos(\omega t + \phi)$	$F = Ae^{j\phi}$	F indep of t
$f_x(t) = f\left(t - \frac{x}{u}\right)$ $= A \cos\left(\omega t + \phi - \frac{\omega}{u}x\right)$	$F_x = Ae^{j\left(\phi - \frac{\omega}{u}x\right)}$ $= Fe^{-jkx}$	$ F_x \equiv F $ indep of x
$f_y(t) = f_x\left(t - \frac{(y-x)}{u}\right)$	$F_y = F_x e^{-jk(y-x)}$	Delayed by $\frac{y-x}{u}$
$g_y(t) = g_x\left(t + \frac{(y-x)}{u}\right)$	$G_y = G_x e^{+jk(y-x)}$	Advanced by $\frac{y-x}{u}$
$v_x(t) = f_x(t) + g_x(t)$	$V_x = F_x + G_x$	


Phasor Relationships

Time Domain	Phasor	Notes
$f(t) = A \cos(\omega t + \phi)$	$F = Ae^{j\phi}$	F indep of t
$f_x(t) = f\left(t - \frac{x}{u}\right)$ $= A \cos\left(\omega t + \phi - \frac{\omega}{u}x\right)$	$F_x = Ae^{j\left(\phi - \frac{\omega}{u}x\right)}$ $= Fe^{-jkx}$	$ F_x \equiv F $ indep of x
$f_y(t) = f_x\left(t - \frac{(y-x)}{u}\right)$	$F_y = F_x e^{-jk(y-x)}$	Delayed by $\frac{y-x}{u}$
$g_y(t) = g_x\left(t + \frac{(y-x)}{u}\right)$	$G_y = G_x e^{+jk(y-x)}$	Advanced by $\frac{y-x}{u}$
$v_x(t) = f_x(t) + g_x(t)$	$V_x = F_x + G_x$	
$i_x(t) = \frac{f_x(t) - g_x(t)}{Z_0}$	$I_x = \frac{F_x - G_x}{Z_0}$	

Phasor Reflection

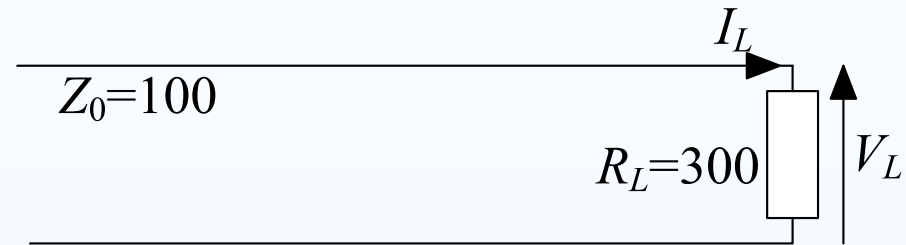18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- **Phasor Reflection**
- Standing Waves
- Summary
- Merry Xmas




Phasors obey Ohm's law: $\frac{V_L}{I_L} = R_L$

Phasor Reflection

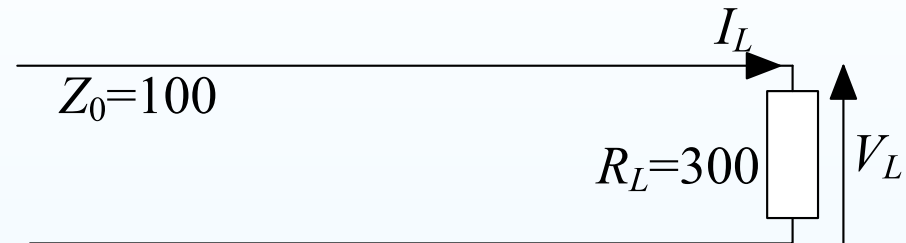18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- **Phasor Reflection**
- Standing Waves
- Summary
- Merry Xmas




Phasors obey Ohm's law:
$$\frac{V_L}{I_L} = R_L = \frac{F_L + G_L}{Z_0^{-1}(F_L - G_L)}$$

Phasor Reflection

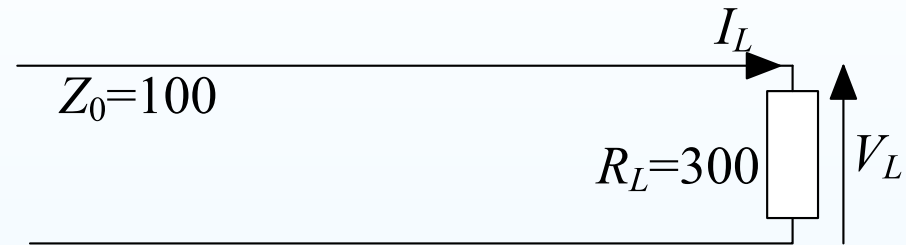18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- **Phasor Reflection**
- Standing Waves
- Summary
- Merry Xmas




Phasors obey Ohm's law: $\frac{V_L}{I_L} = R_L = \frac{F_L + G_L}{Z_0^{-1}(F_L - G_L)}$

So $G_L = \rho_L F_L$ where $\rho_L = \frac{R_L - Z_0}{R_L + Z_0}$

Phasor Reflection

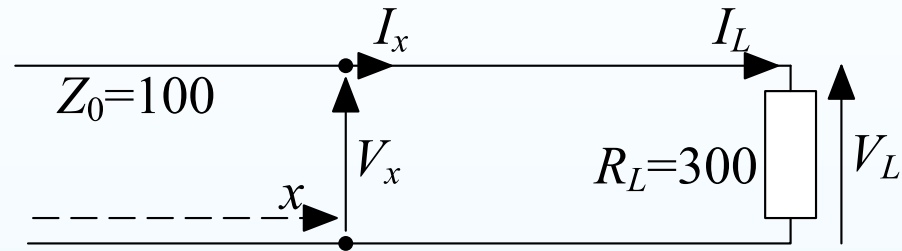18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas



Phasors obey Ohm's law: $\frac{V_L}{I_L} = R_L = \frac{F_L + G_L}{Z_0^{-1}(F_L - G_L)}$


So $G_L = \rho_L F_L$ where $\rho_L = \frac{R_L - Z_0}{R_L + Z_0}$

At any x , $\frac{G_x}{F_x} = \frac{G_L e^{-jk(L-x)}}{F_L e^{+jk(L-x)}}$

Phasor Reflection

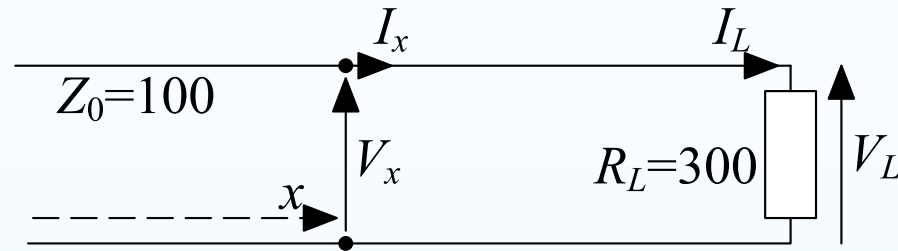18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- **Phasor Reflection**
- Standing Waves
- Summary
- Merry Xmas



Phasors obey Ohm's law: $\frac{V_L}{I_L} = R_L = \frac{F_L + G_L}{Z_0^{-1}(F_L - G_L)}$


So $G_L = \rho_L F_L$ where $\rho_L = \frac{R_L - Z_0}{R_L + Z_0}$

At any x , $\frac{G_x}{F_x} = \frac{G_L e^{-jk(L-x)}}{F_L e^{+jk(L-x)}} = \rho_L e^{-2jk(L-x)}$

Phasor Reflection

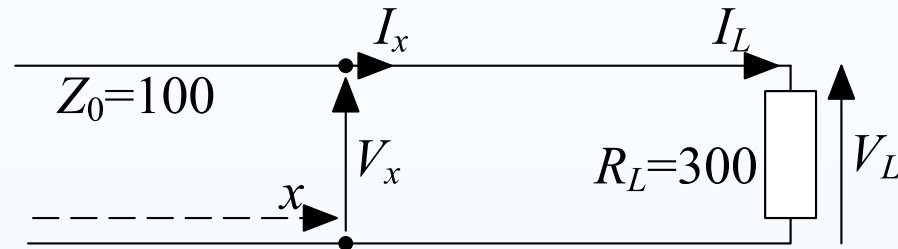18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- **Phasor Reflection**
- Standing Waves
- Summary
- Merry Xmas



Phasors obey Ohm's law: $\frac{V_L}{I_L} = R_L = \frac{F_L + G_L}{Z_0^{-1}(F_L - G_L)}$

So $G_L = \rho_L F_L$ where $\rho_L = \frac{R_L - Z_0}{R_L + Z_0}$


At any x , $\frac{G_x}{F_x} = \frac{G_L e^{-jk(L-x)}}{F_L e^{+jk(L-x)}} = \rho_L e^{-2jk(L-x)}$

Ohm's law at the load determines the ratio $\frac{G_x}{F_x}$ everywhere on the line.

Phasor Reflection

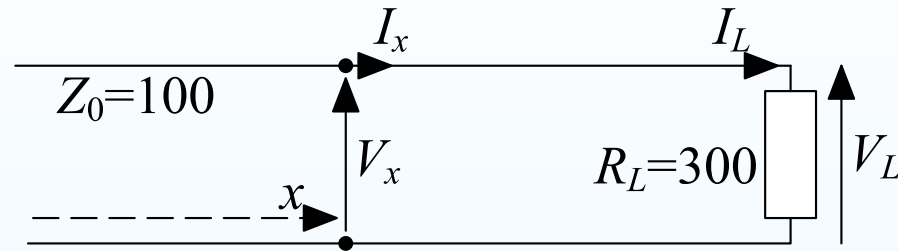18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- **Phasor Reflection**
- Standing Waves
- Summary
- Merry Xmas



Phasors obey Ohm's law: $\frac{V_L}{I_L} = R_L = \frac{F_L + G_L}{Z_0^{-1}(F_L - G_L)}$

So $G_L = \rho_L F_L$ where $\rho_L = \frac{R_L - Z_0}{R_L + Z_0}$

At any x , $\frac{G_x}{F_x} = \frac{G_L e^{-jk(L-x)}}{F_L e^{+jk(L-x)}} = \rho_L e^{-2jk(L-x)}$


Ohm's law at the load determines the ratio $\frac{G_x}{F_x}$ everywhere on the line.

Note that $\left| \frac{G_x}{F_x} \right| \equiv |\rho_L|$ has the same value for all x .

Phasor Reflection

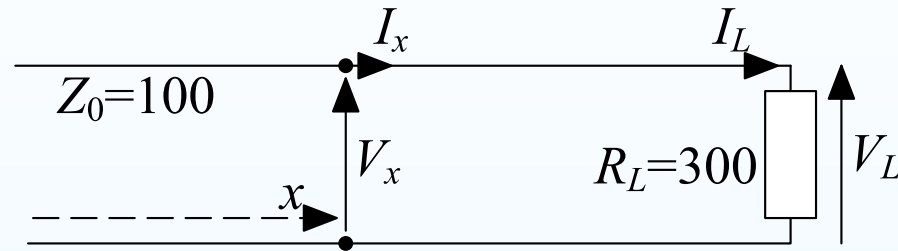18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- **Phasor Reflection**
- Standing Waves
- Summary
- Merry Xmas



Phasors obey Ohm's law: $\frac{V_L}{I_L} = R_L = \frac{F_L + G_L}{Z_0^{-1}(F_L - G_L)}$

So $G_L = \rho_L F_L$ where $\rho_L = \frac{R_L - Z_0}{R_L + Z_0}$

At any x , $\frac{G_x}{F_x} = \frac{G_L e^{-jk(L-x)}}{F_L e^{+jk(L-x)}} = \rho_L e^{-2jk(L-x)}$

Ohm's law at the load determines the ratio $\frac{G_x}{F_x}$ everywhere on the line.


Note that $\left| \frac{G_x}{F_x} \right| \equiv |\rho_L|$ has the same value for all x .

$$V_x = F_x + G_x$$

Phasor Reflection

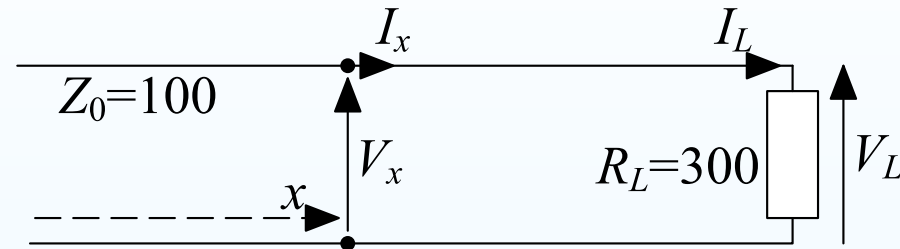18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas



Phasors obey Ohm's law: $\frac{V_L}{I_L} = R_L = \frac{F_L + G_L}{Z_0^{-1}(F_L - G_L)}$

So $G_L = \rho_L F_L$ where $\rho_L = \frac{R_L - Z_0}{R_L + Z_0}$

At any x , $\frac{G_x}{F_x} = \frac{G_L e^{-jk(L-x)}}{F_L e^{+jk(L-x)}} = \rho_L e^{-2jk(L-x)}$

Ohm's law at the load determines the ratio $\frac{G_x}{F_x}$ everywhere on the line.


Note that $\left| \frac{G_x}{F_x} \right| \equiv |\rho_L|$ has the same value for all x .

$V_x = F_x + G_x = F_x (1 + \rho_L e^{-2jk(L-x)})$

Phasor Reflection

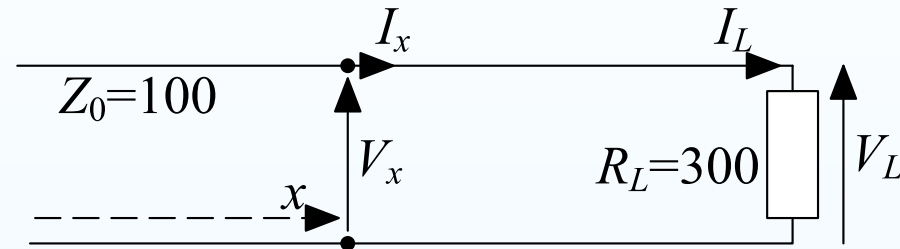18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas



$$\text{Phasors obey Ohm's law: } \frac{V_L}{I_L} = R_L = \frac{F_L + G_L}{Z_0^{-1}(F_L - G_L)}$$

$$\text{So } G_L = \rho_L F_L \text{ where } \rho_L = \frac{R_L - Z_0}{R_L + Z_0}$$

$$\text{At any } x, \frac{G_x}{F_x} = \frac{G_L e^{-jk(L-x)}}{F_L e^{+jk(L-x)}} = \rho_L e^{-2jk(L-x)}$$

Ohm's law at the load determines the ratio $\frac{G_x}{F_x}$ everywhere on the line.

Note that $\left| \frac{G_x}{F_x} \right| \equiv |\rho_L|$ has the same value for all x .


$$V_x = F_x + G_x = F_x (1 + \rho_L e^{-2jk(L-x)})$$

$$I_x = Z_0^{-1} (F_x - G_x)$$

Phasor Reflection

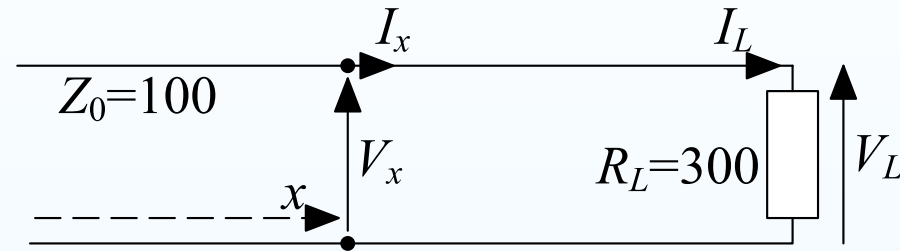18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas



Phasors obey Ohm's law: $\frac{V_L}{I_L} = R_L = \frac{F_L + G_L}{Z_0^{-1}(F_L - G_L)}$

So $G_L = \rho_L F_L$ where $\rho_L = \frac{R_L - Z_0}{R_L + Z_0}$

At any x , $\frac{G_x}{F_x} = \frac{G_L e^{-jk(L-x)}}{F_L e^{+jk(L-x)}} = \rho_L e^{-2jk(L-x)}$

Ohm's law at the load determines the ratio $\frac{G_x}{F_x}$ everywhere on the line.

Note that $\left| \frac{G_x}{F_x} \right| \equiv |\rho_L|$ has the same value for all x .


$$V_x = F_x + G_x = F_x (1 + \rho_L e^{-2jk(L-x)})$$

$$I_x = Z_0^{-1} (F_x - G_x) = Z_0^{-1} F_x (1 - \rho_L e^{-2jk(L-x)})$$

Phasor Reflection

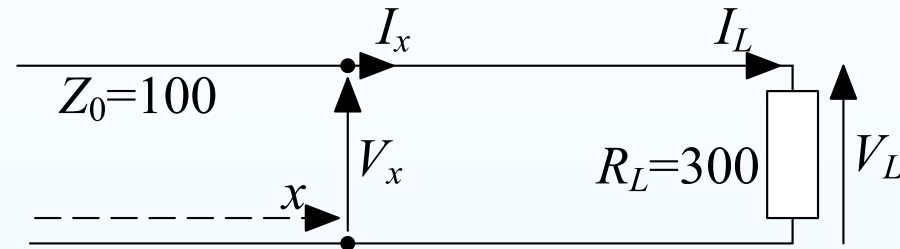18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- **Phasor Reflection**
- Standing Waves
- Summary
- Merry Xmas



Phasors obey Ohm's law: $\frac{V_L}{I_L} = R_L = \frac{F_L + G_L}{Z_0^{-1}(F_L - G_L)}$

So $G_L = \rho_L F_L$ where $\rho_L = \frac{R_L - Z_0}{R_L + Z_0}$

At any x , $\frac{G_x}{F_x} = \frac{G_L e^{-jk(L-x)}}{F_L e^{+jk(L-x)}} = \rho_L e^{-2jk(L-x)}$

Ohm's law at the load determines the ratio $\frac{G_x}{F_x}$ everywhere on the line.

Note that $\left| \frac{G_x}{F_x} \right| \equiv |\rho_L|$ has the same value for all x .

$$V_x = F_x + G_x = F_x (1 + \rho_L e^{-2jk(L-x)})$$

$$I_x = Z_0^{-1} (F_x - G_x) = Z_0^{-1} F_x (1 - \rho_L e^{-2jk(L-x)})$$


The exponent $-2jk(L-x)$ is the phase delay from travelling from x to L and back again (hence the factor 2).

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

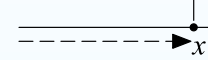


$$I_L$$

$$V_x$$

$$R_L = 300$$

$$V_L$$

$$\rho = 0.5$$



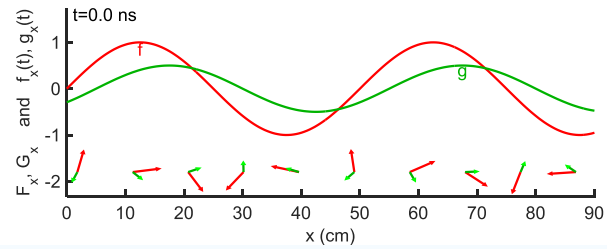


Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

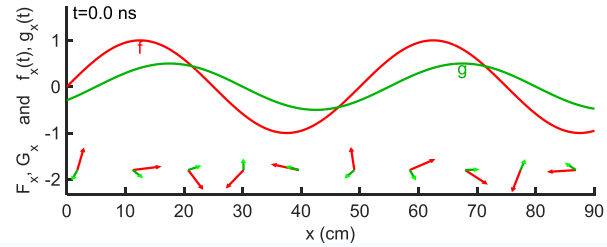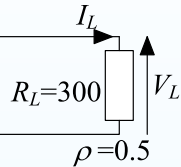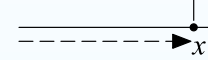



Forward wave phasor: $F_x = F e^{-jkx}$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

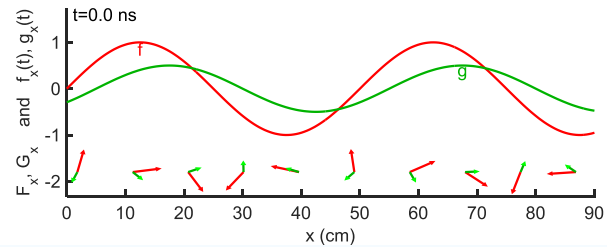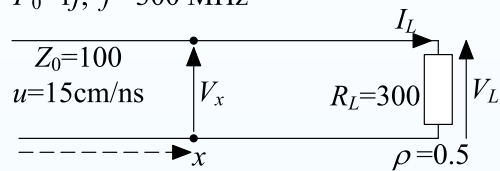

Forward wave phasor: $F_x = F e^{-jkx}$



Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)}$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

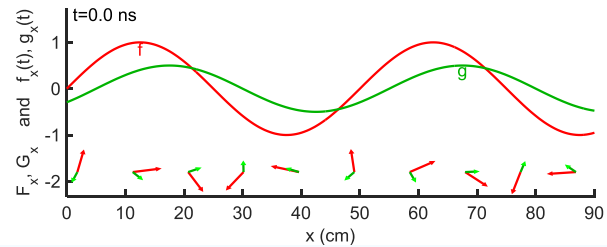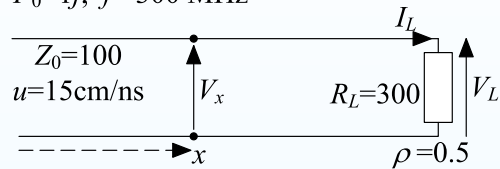

Forward wave phasor: $F_x = F e^{-jkx}$



Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

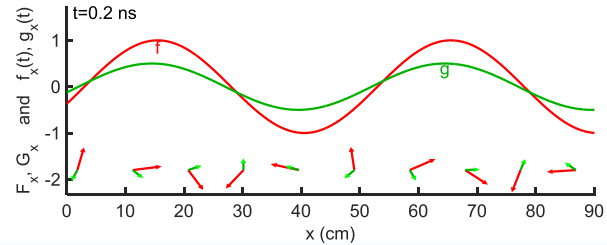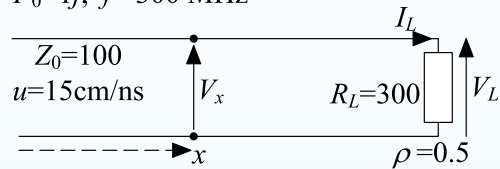

Forward wave phasor: $F_x = F e^{-jkx}$



Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

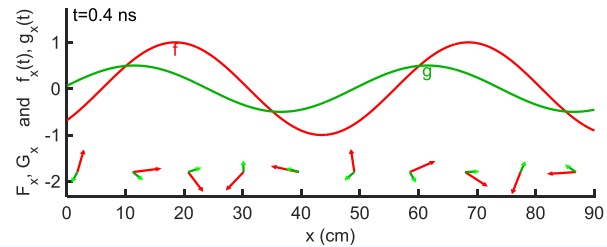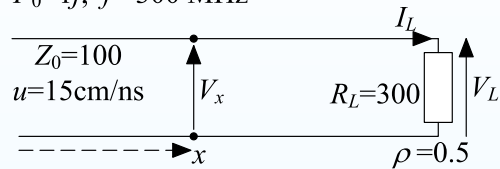

Forward wave phasor: $F_x = F e^{-jkx}$



Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

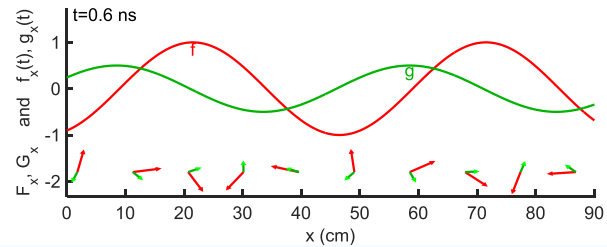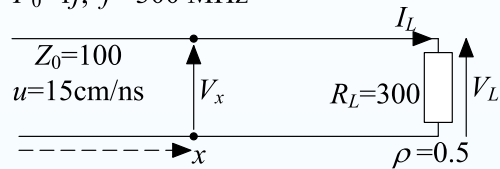

Forward wave phasor: $F_x = F e^{-jkx}$



Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

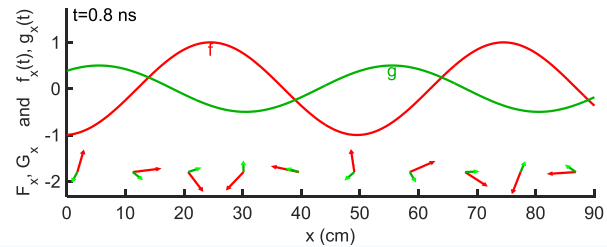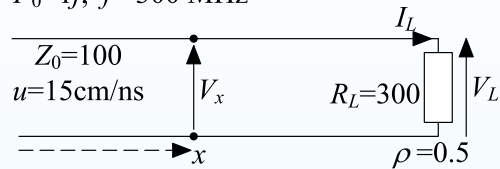

Forward wave phasor: $F_x = F e^{-jkx}$



Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

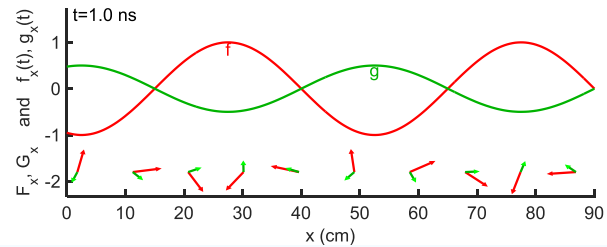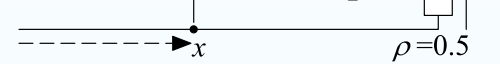

Forward wave phasor: $F_x = F e^{-jkx}$



Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

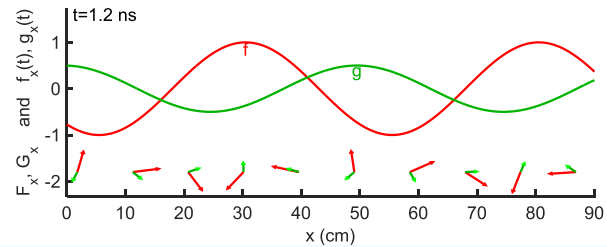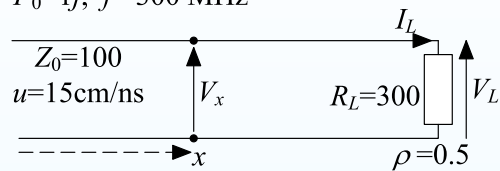

Forward wave phasor: $F_x = F e^{-jkx}$



Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

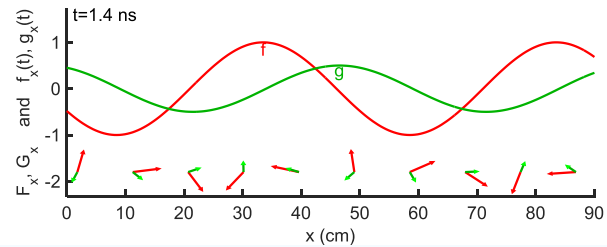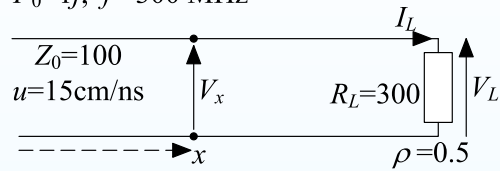

Forward wave phasor: $F_x = F e^{-jkx}$



Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

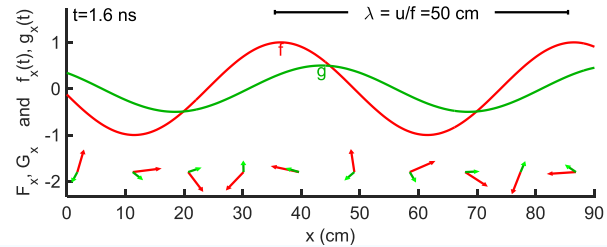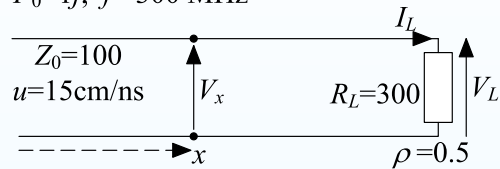

Forward wave phasor: $F_x = F e^{-jkx}$


Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

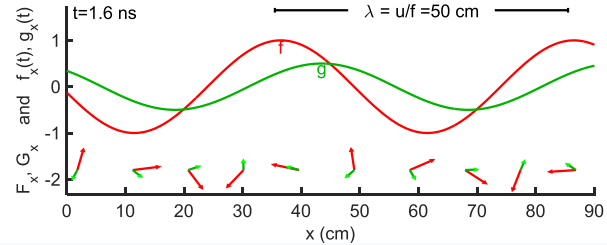

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$


Line Voltage phasor: $V_x = F_x + G_x$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

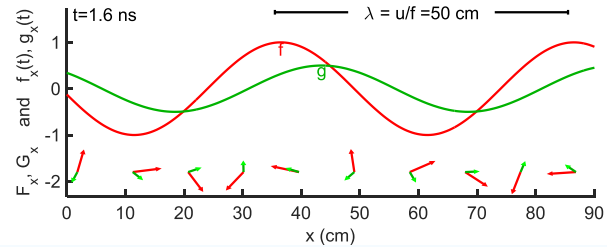

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$


Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$



$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

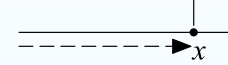

$$R_L = 300$$

$$\rho = 0.5$$

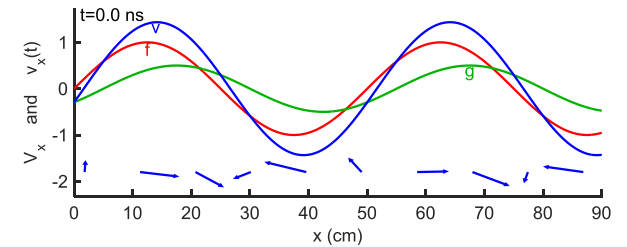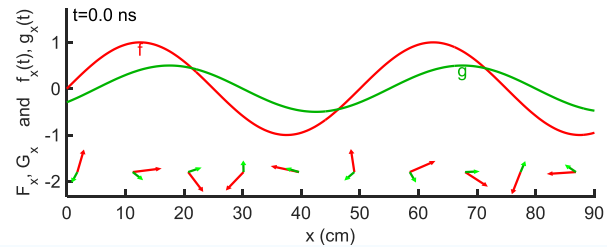

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$



Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

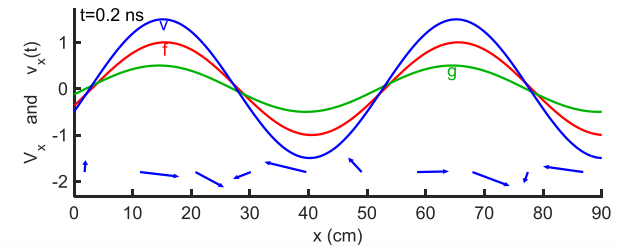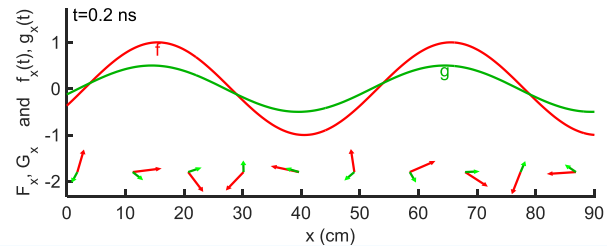

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$


Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$



$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

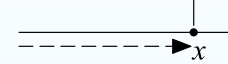

$$R_L = 300$$

$$\rho = 0.5$$

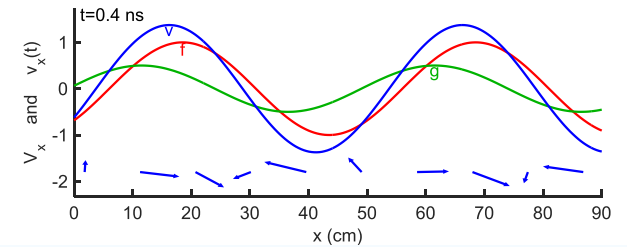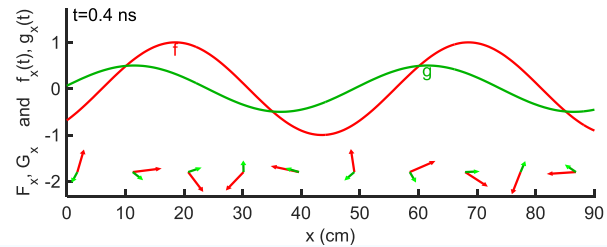

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$




Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

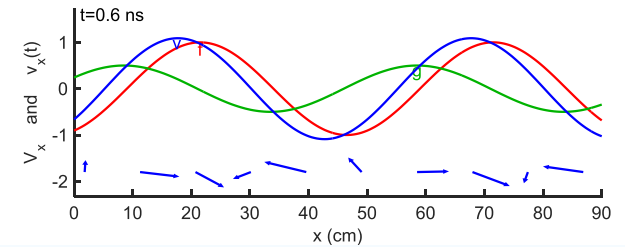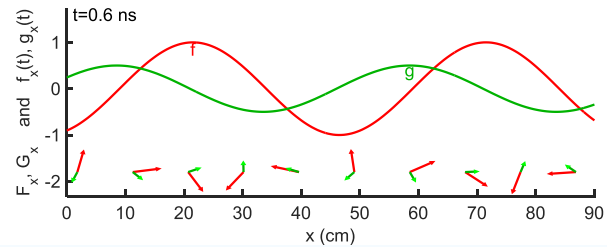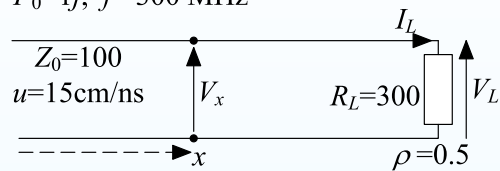

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$




Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

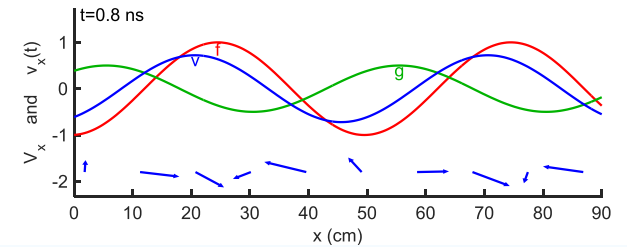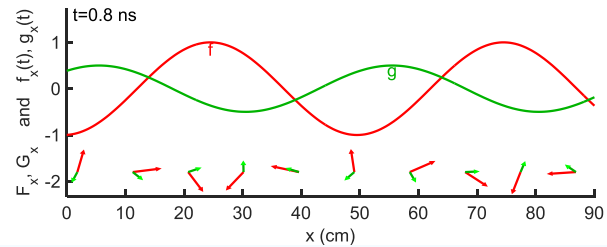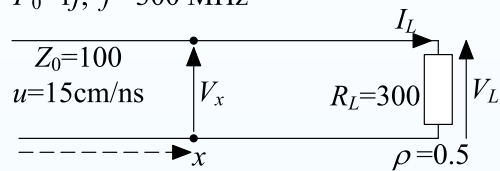

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$




Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

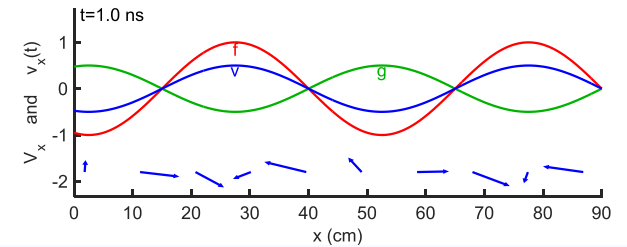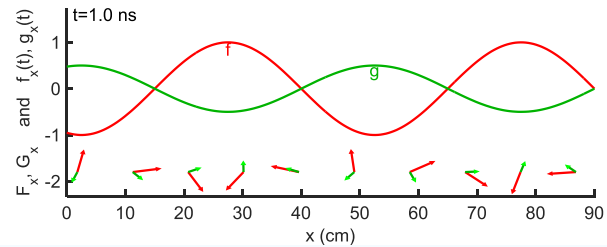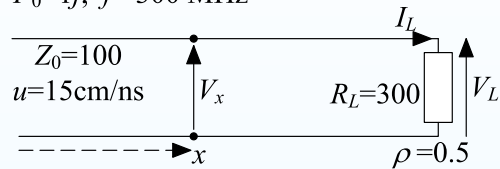

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$





Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

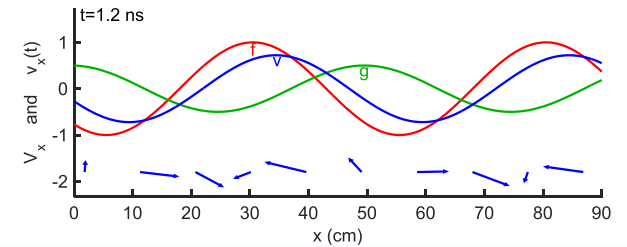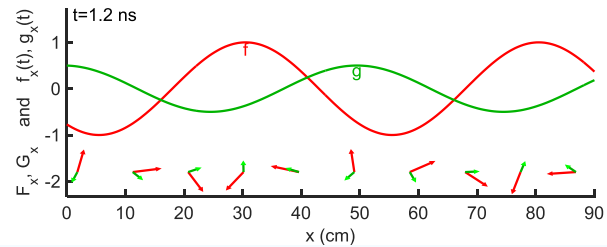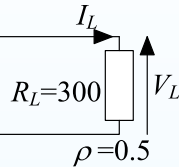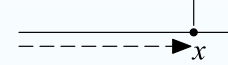

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$




Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

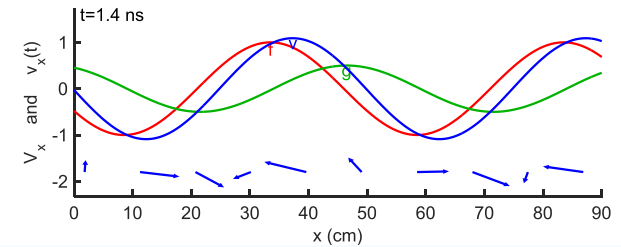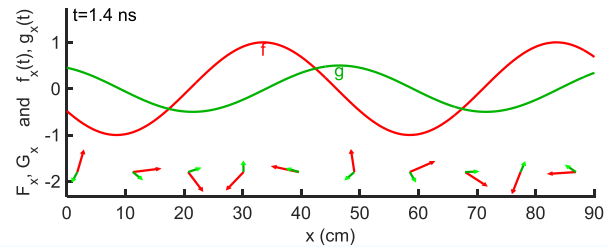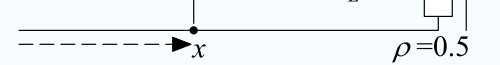

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$





Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

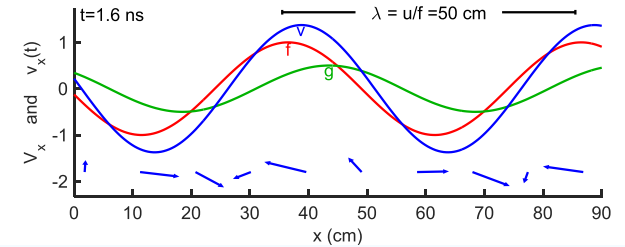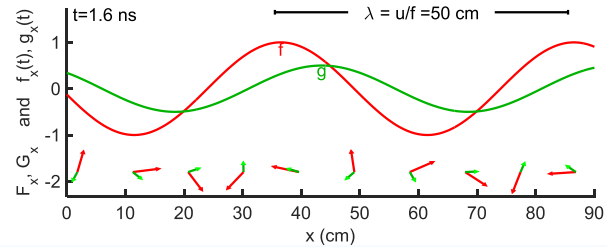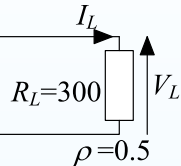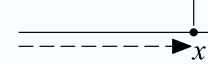

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$



Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

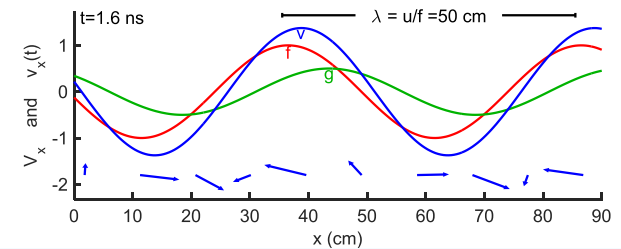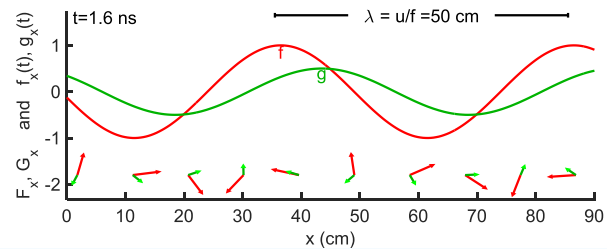

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$





Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

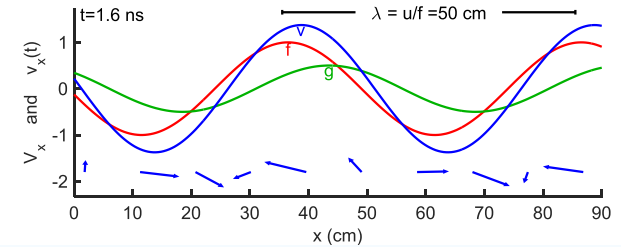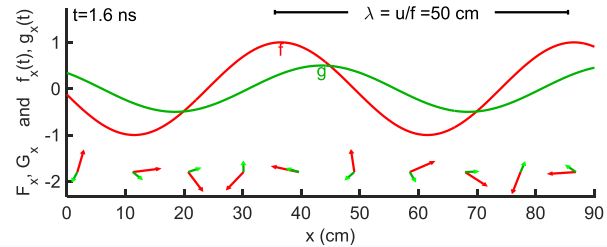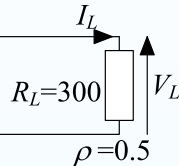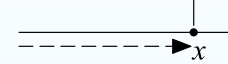

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$





Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

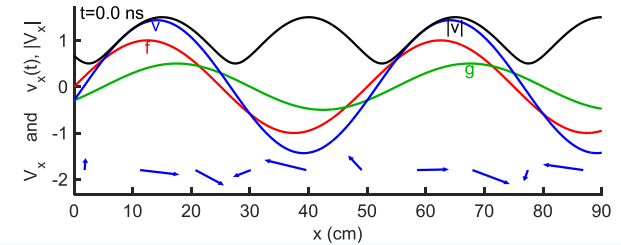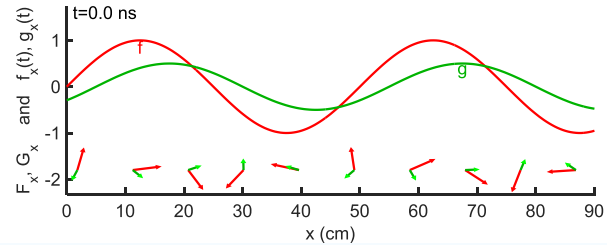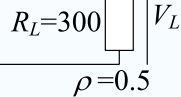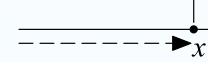

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$




Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

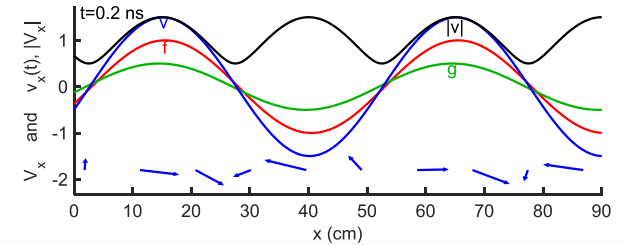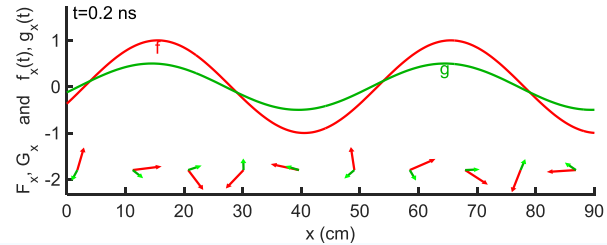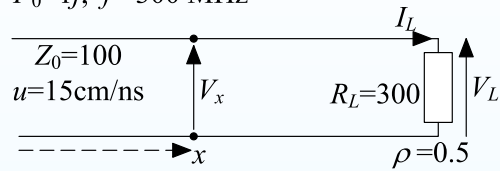

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$



Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

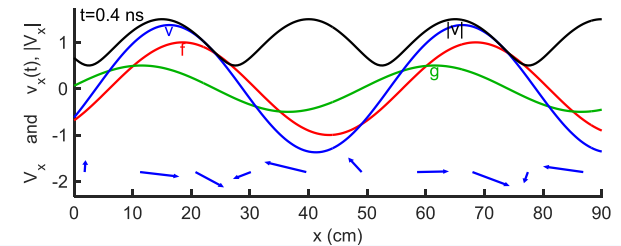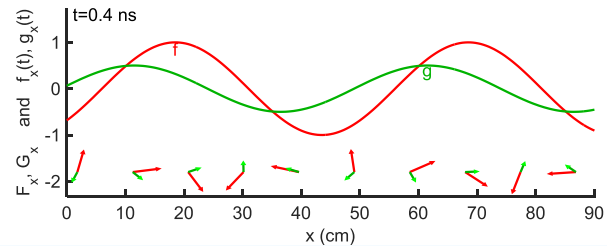

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$




Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

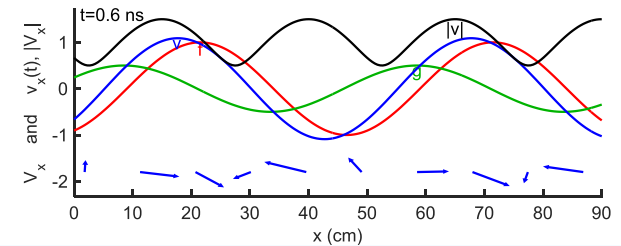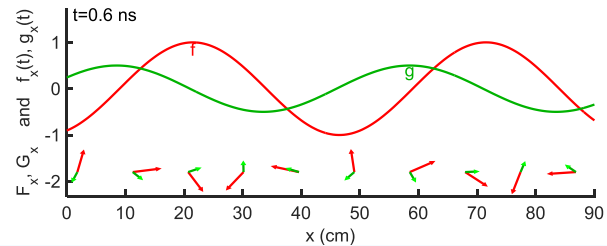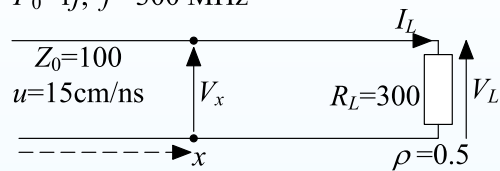

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$




Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

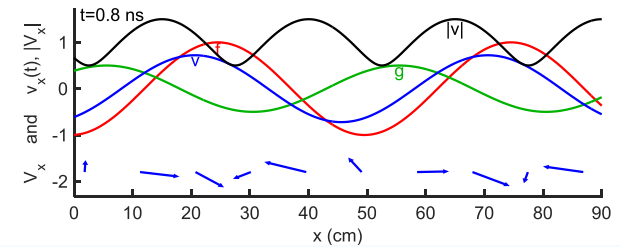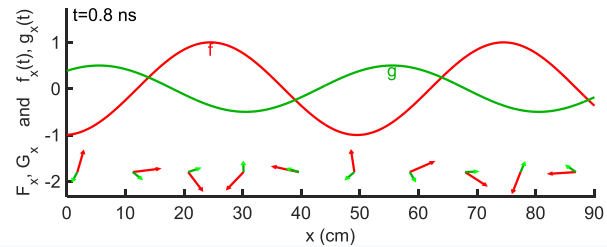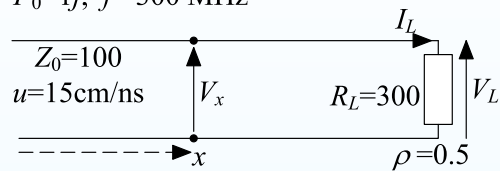

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$




Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

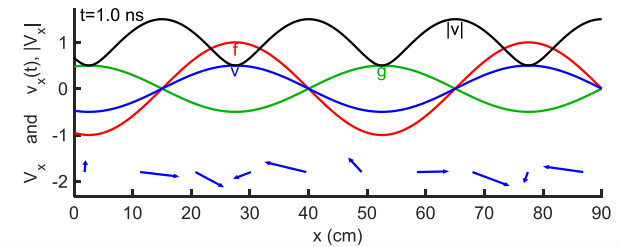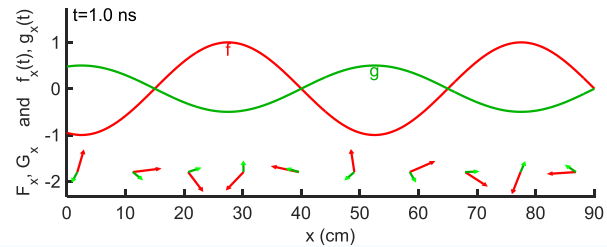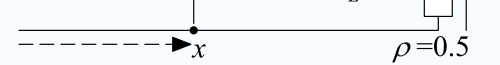

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$




Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

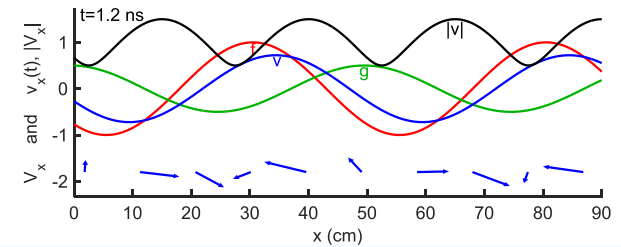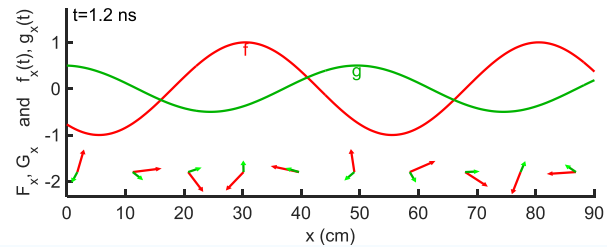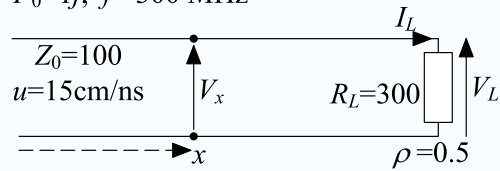

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$




Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

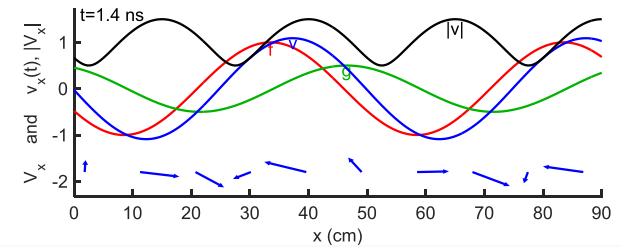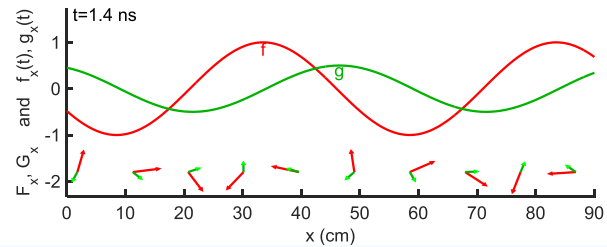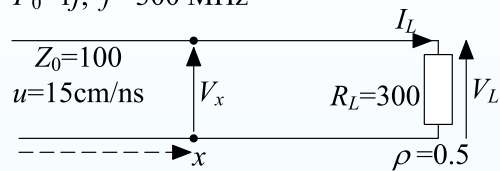

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$





Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

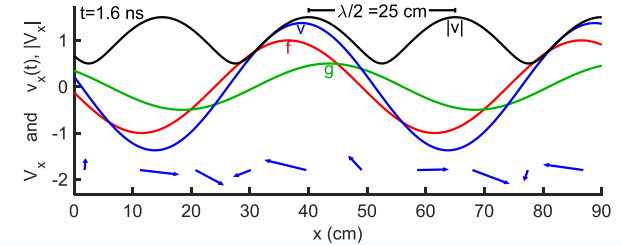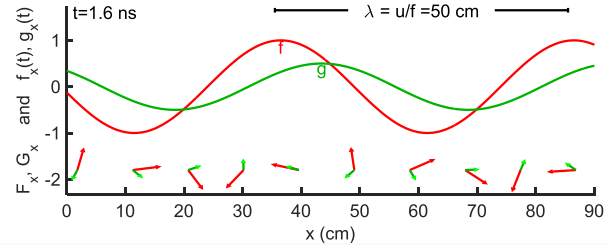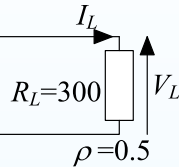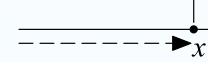

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$





Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

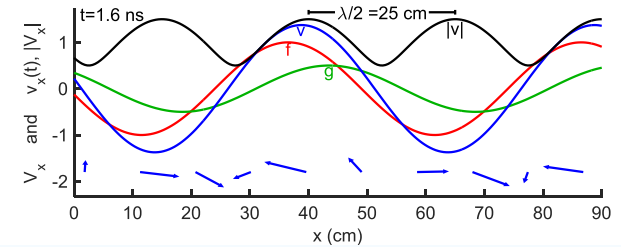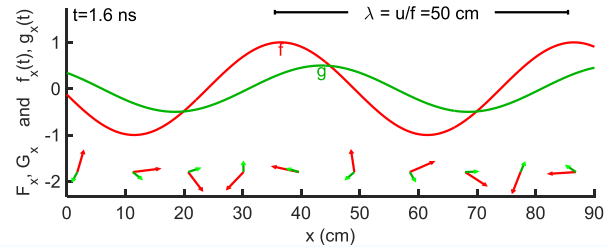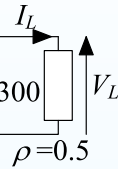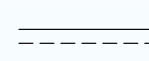

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**





Max amplitude equals $1 + |\rho_L|$ at values of x where F_x and G_x are in phase. This occurs every $\frac{\lambda}{2}$ away from L

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

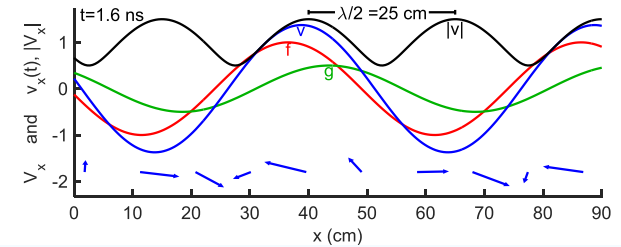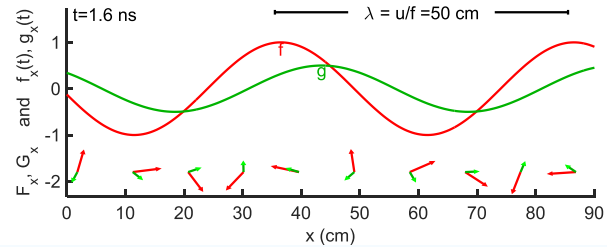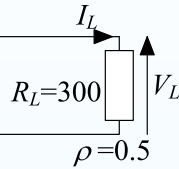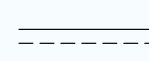

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**





Max amplitude equals $1 + |\rho_L|$ at values of x where F_x and G_x are in phase. This occurs every $\frac{\lambda}{2}$ away from L where λ is the **wavelength**, $\lambda = \frac{2\pi}{k} = \frac{u}{f}$.

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

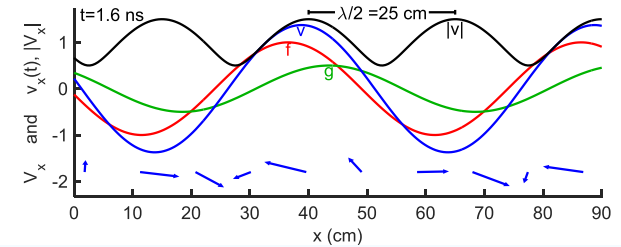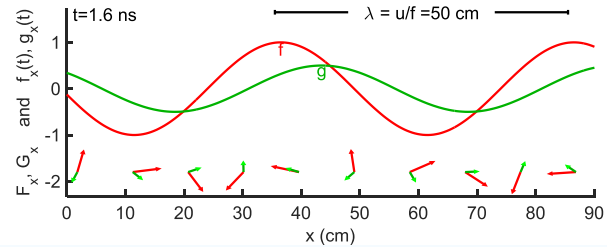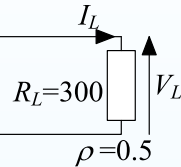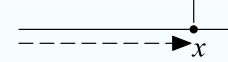

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Max amplitude equals $1 + |\rho_L|$ at values of x where F_x and G_x are in phase. This occurs every $\frac{\lambda}{2}$ away from L where λ is the **wavelength**, $\lambda = \frac{2\pi}{k} = \frac{u}{f}$.




Min amplitude equals $1 - |\rho_L|$ at values of x where F_x and G_x are out of phase.

Standing Waves

$$F_0 = 1j, f = 300 \text{ MHz}$$

$$Z_0 = 100$$

$$u = 15 \text{ cm/ns}$$

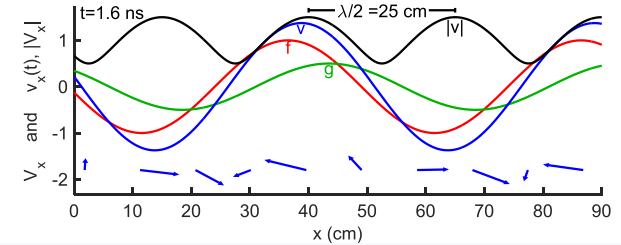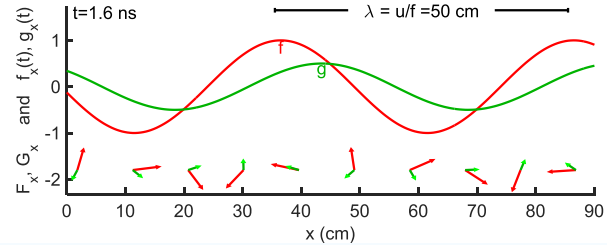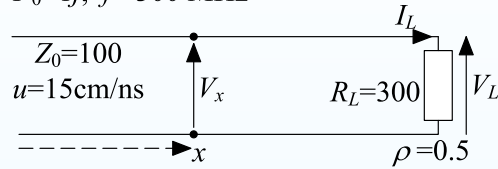

Forward wave phasor: $F_x = F e^{-jkx}$

Backward wave phasor: $G_x = \rho_L F_x e^{-2jk(L-x)} = \rho_L F e^{-2jkL} e^{+jkx}$

Line Voltage phasor: $V_x = F_x + G_x = F e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Line Voltage Amplitude: $|V_x| = |F| |1 + \rho_L e^{-2jk(L-x)}|$ **varies with x but not t**

Max amplitude equals $1 + |\rho_L|$ at values of x where F_x and G_x are in phase. This occurs every $\frac{\lambda}{2}$ away from L where λ is the **wavelength**, $\lambda = \frac{2\pi}{k} = \frac{u}{f}$.

Min amplitude equals $1 - |\rho_L|$ at values of x where F_x and G_x are out of phase.

Standing waves arise whenever a periodic wave meets its reflection: e.g. ponds, musical instruments, microwave ovens.

Summary

18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- Phasor Reflection
- Standing Waves
- **Summary**
- Merry Xmas

- Use phasors if **forward and backward waves are sinusoidal with the same ω .**

Summary

- Use phasors if **forward and backward waves are sinusoidal with the same ω .**

- $f_x(t) = f\left(t - \frac{x}{u}\right) \rightarrow F_x = F_0 e^{-jkx}$

- $g_x(t) = g\left(t + \frac{x}{u}\right) \rightarrow G_x = G_0 e^{+jkx}$

Summary

- Use phasors if **forward and backward waves are sinusoidal with the same ω** .

- $f_x(t) = f\left(t - \frac{x}{u}\right) \rightarrow F_x = F_0 e^{-jkx}$

- $g_x(t) = g\left(t + \frac{x}{u}\right) \rightarrow G_x = G_0 e^{+jkx}$

- ▷ $k = \frac{\omega}{u}$ is the **wavenumber** in “radians per metre”

Summary

- Use phasors if **forward and backward waves are sinusoidal with the same ω** .
 - $f_x(t) = f\left(t - \frac{x}{u}\right) \rightarrow F_x = F_0 e^{-jkx}$
 - $g_x(t) = g\left(t + \frac{x}{u}\right) \rightarrow G_x = G_0 e^{+jkx}$
 - ▷ $k = \frac{\omega}{u}$ is the **wavenumber** in “radians per metre”
- Time delays \simeq phase shifts: $F_y = F_x e^{-jk(y-x)}$

Summary

- Use phasors if **forward and backward waves are sinusoidal with the same ω** .
 - $f_x(t) = f\left(t - \frac{x}{u}\right) \rightarrow F_x = F_0 e^{-jkx}$
 - $g_x(t) = g\left(t + \frac{x}{u}\right) \rightarrow G_x = G_0 e^{+jkx}$
 - ▷ $k = \frac{\omega}{u}$ is the **wavenumber** in “radians per metre”
- Time delays \simeq phase shifts: $F_y = F_x e^{-jk(y-x)}$
- When a periodic wave meets its reflection you get a **standing wave**:

Summary

- Use phasors if **forward and backward waves are sinusoidal with the same ω** .
 - $f_x(t) = f\left(t - \frac{x}{u}\right) \rightarrow F_x = F_0 e^{-jkx}$
 - $g_x(t) = g\left(t + \frac{x}{u}\right) \rightarrow G_x = G_0 e^{+jkx}$
 - ▷ $k = \frac{\omega}{u}$ is the **wavenumber** in “radians per metre”
- Time delays \simeq phase shifts: $F_y = F_x e^{-jk(y-x)}$
- When a periodic wave meets its reflection you get a **standing wave**:
 - Oscillation amplitude varies with x : $\propto |1 + \rho_L e^{-2jk(L-x)}|$

Summary

18: Phasors and Transmission Lines

- Phasors and transmission lines
- Phasor Relationships
- Phasor Reflection
- Standing Waves
- Summary
- Merry Xmas

- Use phasors if **forward and backward waves are sinusoidal with the same ω** .
 - $f_x(t) = f\left(t - \frac{x}{u}\right) \rightarrow F_x = F_0 e^{-jkx}$
 - $g_x(t) = g\left(t + \frac{x}{u}\right) \rightarrow G_x = G_0 e^{+jkx}$
 - ▷ $k = \frac{\omega}{u}$ is the **wavenumber** in “radians per metre”
- Time delays \simeq phase shifts: $F_y = F_x e^{-jk(y-x)}$
- When a periodic wave meets its reflection you get a **standing wave**:
 - Oscillation amplitude varies with x : $\propto |1 + \rho_L e^{-2jk(L-x)}|$
 - Max amplitude of $(1 + |\rho_L|)$ occurs every $\frac{\lambda}{2}$

Merry Xmas

