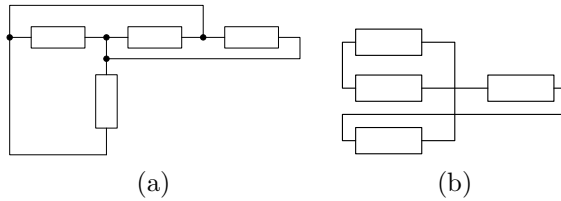


E1.1 Circuit Analysis


Problem Sheet 1 (Lectures 1 & 2)

Key: [A]= easy ... [E]=hard


- [A] One of the following circuits is a series circuit and the other is a parallel circuit. Explain which is which.



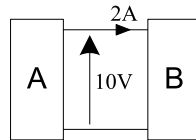
- [B] Find the power absorbed by each of the subcircuits *A* and *B* given that the voltage and current are 10 V and 2 A as shown.



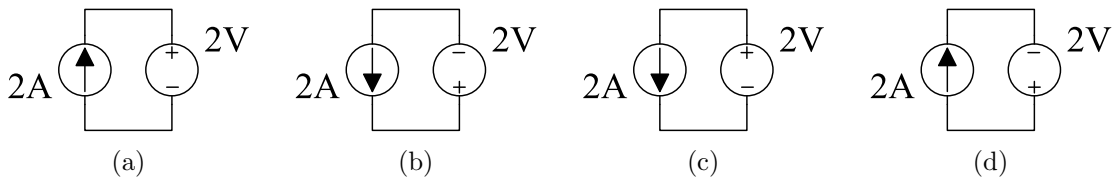
- [B] For each of the four circuits below, find the power absorbed by the voltage source (P_V), the power absorbed by the current source (P_I) and the total power absorbed ($P_V + P_I$).



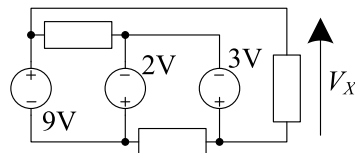
- [B] Determine the voltage V_X in the following circuit.



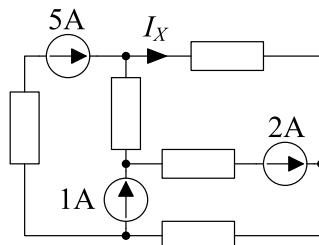
- [B] Determine the current I_X in the following circuit.



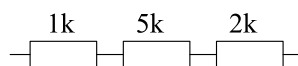
- [B] What single resistor is equivalent to the three resistor sub-circuit shown below?



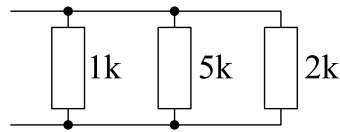
7. [B] What single resistor is equivalent to the three resistor sub-circuit shown below?



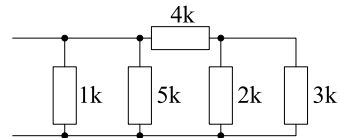
8. [C] What single resistor is equivalent to the five resistor sub-circuit shown below?



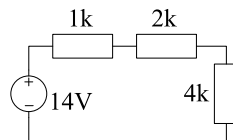
9. [A] If a resistor has a conductance of $8 \mu\text{S}$, what is its resistance?
10. [B] Determine the voltage across each of the resistors in the following circuit and the power dissipated in each of them. Calculate the power supplied by the voltage source.



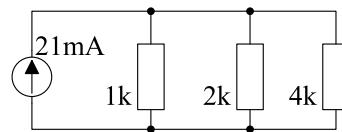
11. [B] Determine the current through each of the resistors in the following circuit and the power dissipated in each of them. Calculate the power supplied by the current source.



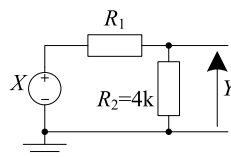12. [B] Determine R_1 so that $Y = \frac{1}{4}X$.



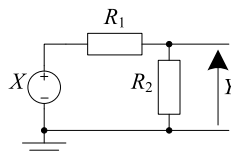13. [B] Choose R_1 and R_2 so that $Y = 0.1X$ and $R_1 + R_2 = 10 \text{ M}\Omega$.



14. [D] You have a supply of resistors that have the values $\{10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82\} \times 10^n \Omega$ for all integer values of n . Thus, for example, a resistor of 390Ω is available and the next higher value is 470Ω . Show how, by combining two resistors in each case, it is possible to make networks whose equivalent resistance is (a) $3 \text{ k}\Omega$, (b) $4 \text{ k}\Omega$ and (c) as close as possible to $3.5 \text{ k}\Omega$. Determine the worst case percentage error that might arise if, instead of combining resistors, you just pick the closest one available.