

E1.1 Circuit Analysis

Problem Sheet 4 (lectures 9 & 10)

Key: [A]= easy ... [E]=hard

Note: A “dimensioned sketch” should show the values on the x and y axes corresponding to significant places on the corresponding graph.

- [B] For each of the following waveforms, determine the corresponding phasor in both the form $a + jb$ and $r\angle\theta$.
 - $8 \cos \omega t$.
 - $3 \cos \omega t + 4 \sin \omega t$.
 - $2 \cos(\omega t + \frac{\pi}{4})$.
 - $8 \sin \omega t$.
 - $-2 \cos \omega t$.
 - $-4 \sin(\omega t - \frac{\pi}{2})$.
 - $8 \cos(\omega t + \frac{\pi}{4}) + 5 \sin(\omega t - \frac{\pi}{4})$.
- [B] For each of the following phasors, determine the corresponding waveform in both the form $a \cos \omega t + b \sin \omega t$ and $a \cos(\omega t + \theta)$. (a) 1, (b) -2 , (c) $3j$, (d) $-4j$, (e) $j - 1$, (f) $3 - 4j$, (g) $2e^{j\frac{\pi}{2}}$, (h) $4e^{-j\frac{\pi}{6}}$.
- [B] For each of the following cases say which of the two waveforms or phasors leads the other:
 - $\sin \omega t$ and $\cos \omega t$.
 - $\sin(\omega t + \pi)$ and $\cos \omega t$.
 - $\sin(\omega t - \pi)$ and $\cos \omega t$.
 - $(1 + j)$ and $(2 + j)$.
 - $(1 + j)$ and $(1 - j)$.
 - $(-1 + j)$ and $(-1 - j)$.
 - 1 and $1\angle 350^\circ$.
- [B] Draw a dimensioned sketch of the waveform of i in the circuit of Fig. 4(a) when v has the waveform shown in Fig. 4(b).

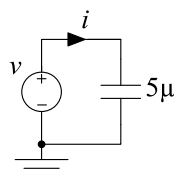


Fig. 4(a)

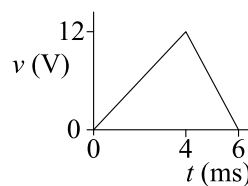


Fig. 4(b)

- [B] For each of the circuits shown in Fig. 5(a)-(d) determine the average value of $y(t)$ when $x(t) = 4 + 2 \cos \omega t$ for some non-zero frequency ω .

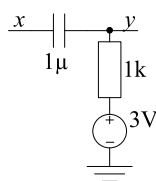


Fig. 5(a)

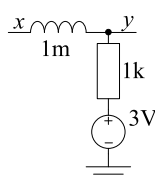


Fig. 5(b)

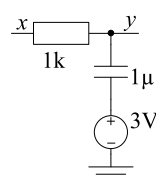


Fig. 5(c)

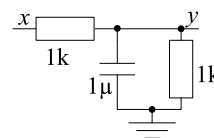


Fig. 5(d)

- [B] Find the value of a single inductor equivalent to the circuit shown in Fig. 6.

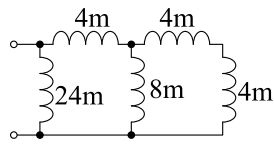


Fig. 6

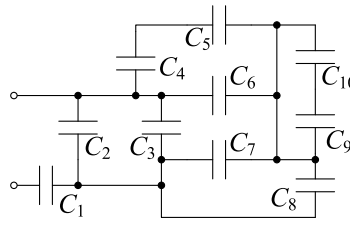


Fig. 7

7. [B] Find the value of a single capacitor equivalent to the circuit shown in Fig. 7 given that each of the capacitors has a value of $1 \mu\text{F}$.
8. [B] Find the average value of v in the circuit of Fig. 8 if $u(t) = 2 + 3 \cos \omega t$.

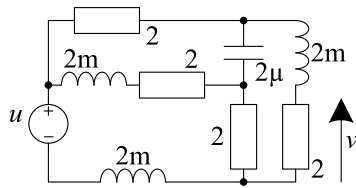


Fig. 8

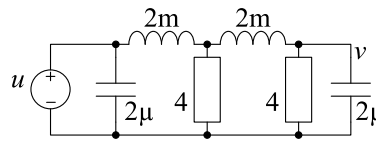


Fig. 9

9. [B] Find the average value of v in the circuit of Fig. 9 if $u(t) = 8 - 2 \cos \omega t$.
10. [B] Find the complex impedance of the circuit shown in Fig. 10 for (a) $\omega = 0$, (b) $\omega = 1000$, (c) $\omega = 2000$ and (d) $\omega = \infty$.

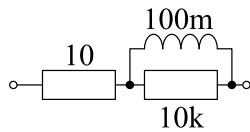


Fig. 10

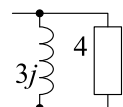


Fig. 11(a)

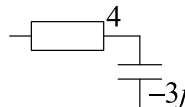


Fig. 11(b)

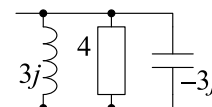


Fig. 11(c)

11. [B] The components in Fig. 11 are labelled with their impedances. Calculate both the complex impedance and the complex admittance for each of the three networks.
12. [B] The components in Fig. 12 are labelled with their impedances. Determine the values of a parallel inductor and resistor that will have the same overall impedance at (a) 1 kHz and (b) 10 kHz. Hint: first calculate the admittance of the original network.

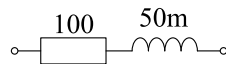


Fig. 12

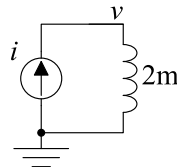


Fig. 13(a)

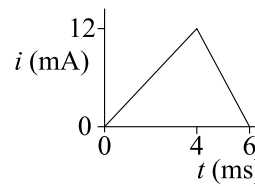


Fig. 13(b)

13. [C] Draw a dimensioned sketch of the waveform of $v(t)$ in the circuit of Fig. 13(a) when i has the waveform shown in Fig. 13(b).

14. [C] The three current i_1 , i_2 , i_3 in Fig. 14 are equal to $5 \cos(\omega t + \frac{3\pi}{4})$, $2 \cos(\omega t + \frac{\pi}{4})$ and $\sqrt{8} \cos \omega t$ but not necessarily in that order. Determine which current is which and find both the phasor I and time-waveform $i(t)$.

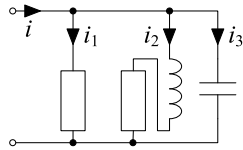


Fig. 14

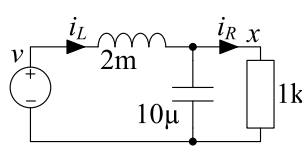


Fig. 17(a)

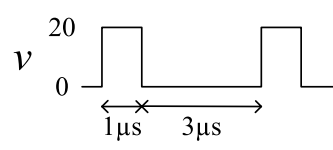


Fig. 17(b)

15. [D] Draw a dimensioned sketch of the waveform of i in the circuit of Fig. 15 when v has the waveform shown in Fig. 4(b) given that at time $t = 0$, (a) $i(0) = 0$ and (b) $i(0) = 2$ A.
16. [D] Draw a dimensioned sketch of the waveform of v in the circuit of Fig. 16(a) when i has the waveform shown in Fig. 16(b) given that at time $t = 0$, (a) $v(0) = 0$ and (b) $v(0) = -5$ V.

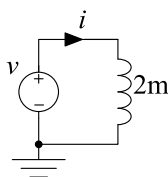


Fig. 15

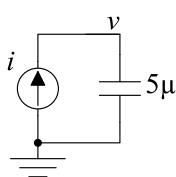


Fig. 16(a)

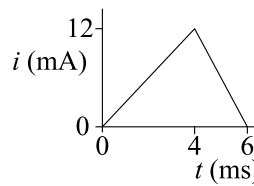


Fig. 16(b)

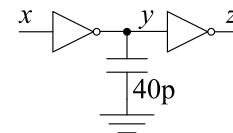


Fig. 18

17. [D] In the circuit of Fig. 17(a), the voltage v has the periodic waveform shown in Fig. 17(b) with a period of $4 \mu\text{s}$ and an amplitude of 20 V.
- State the duty cycle of v .
 - Determine the average value of x .
 - Determine the average value of i_R .
 - Determine the average value of i_L .
 - Assuming that x is constant (at its average value), draw a dimensioned sketch of the waveform of $i_L(t)$ and determine its maximum and minimum values.
 - Assuming that x is constant (at its average value), determine the average, positive peak and negative peak of the powers absorbed by each of R , L and C .
18. [D] In the circuit of Fig. 18, the output logic levels from the inverter are 0 V and 5 V and the inverter has a maximum output current of ± 2 mA. The inverter senses a low voltage when its input is < 1.5 V. If x changes from logic 0 to logic 1, determine the delay until z changes. Ignore the inverter input currents and any delays inside the inverters themselves.