

E1.1 Circuit Analysis

Problem Sheet 7 (Lectures 17 & 18)

Key: [A]= easy ... [E]=hard

Note: In this problem sheet u and Z_0 are the propagation velocity and characteristic impedance of a transmission line and the forward and backward waves at the point x are $f_x(t) = f(t - \frac{x}{u})$ and $g_x(t) = g(t + \frac{x}{u})$ with, in the case of sinusoidal waves, the corresponding phasors being F_x and G_x .

- [A] Find the propagation velocity, u , and characteristic impedance, Z_0 , of a transmission line whose capacitance and inductance are 50 pF/m and 500 nH/m respectively. Express the propagation velocity also as a fraction of the speed of light.
- [B] The line in Fig. 2 has $Z_0 = 100 \Omega$. For each of the cases below, calculate the reflection coefficients at both ends of the line and describe the waves that would arise from a short positive pulse at V_S .
 - $R_S = 10$ and $R_L = 100$.
 - $R_S = 10$ and $R_L = 1000$.
 - $R_S = 100$ and $R_L = 1000$.

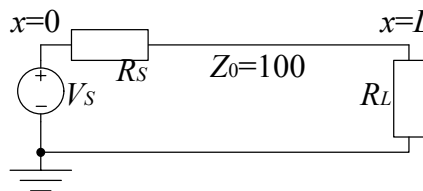


Fig. 2

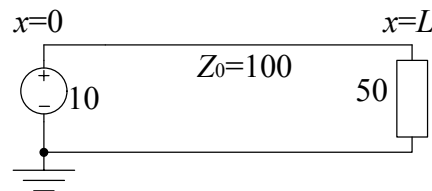


Fig. 3

- [C] The line in Fig. 3 is driven by a 10 V DC voltage source. Determine the voltage and current in the line and hence the forward and backward waves $f(t - \frac{x}{u})$ and $g(t + \frac{x}{u})$. Determine also the power carried by the two waves and verify that their difference equals the total power delivered to the load.

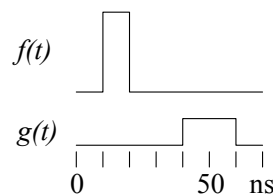


Fig. 4

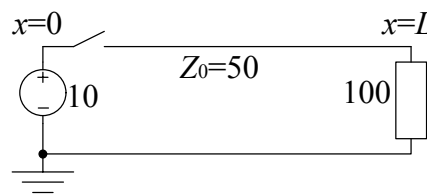


Fig. 5

- [C] A transmission line has a propagation velocity of 15 cm/ns and a characteristic impedance of 100 Ω . The forward and backward waves are shown in Fig. 4 and have amplitudes of 9 V and 3 V respectively. Draw dimensioned sketches of the voltage and current waveforms at (a) $x = 0$ and (b) $x = 300$ cm. In each case, give the value of the peak voltage and peak current.
- [C] The transmission line shown in Fig. 5 has a propagation velocity of 15 cm/ns and a characteristic impedance of 50 Ω . The length of the line is $L = 300$ cm.
 - Determine the reflection coefficients at both ends of the line when the switch is held closed.
 - Calculate the steady state DC forward and backward waves when the switch has been closed for a long time.
 - If the switch is closed at time $t = 0$, determine the forward and backward waves at $x = 0$. Hence determine the voltage waveforms at $x = 0$ and $x = L$.
- [C] A length of transmission line with $Z_0 = 100$ and $u = 20$ cm/ns is terminated in a short circuit at $x = L$. Find the shortest lengths of line, L , for which the impedance at 20 MHz at $x = 0$ will equal (a) 50 pF and (b) 1 μ H.

7. [C] In Fig. 7, $L = 5$ m, $u = 20$ cm/ns, $Z_0 = 100$, $R_L = 50$ and the frequency of operation is 50 MHz.
- If the forward wave phasor at $x = 0$ is $F_0 = 6j$, determine the forward wave phasors, F_x , at $x = 1, 2, 3, 4$ and 5 metres.
 - Calculate the reflection coefficient at $x = L$.
 - Determine the backward wave phasors, G_x , at $x = 0, 1, 2, 3, 4$ and 5.
 - Determine the line voltage phasors, V_x , at $x = 0, 1, 2, 3, 4$ and 5.
 - Determine the Voltage Standing Wave Ratio: $VSWR = \frac{\max(|V_x|)}{\min(|V_x|)}$.
 - Determine the line impedance, $\frac{V_0}{I_0}$, at $x = 0$.

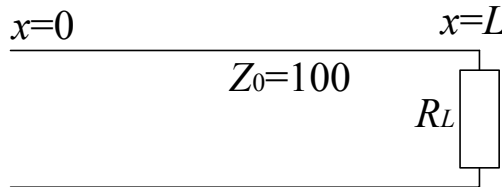


Fig. 7

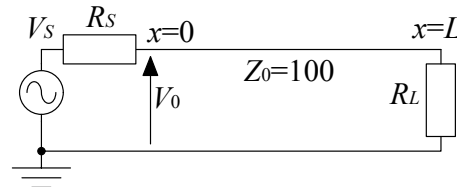


Fig. 9

8. [C] Repeat question 7 for $R_L = 100$.
9. [C] In Fig. 9, $L = 1$ m, $u = 15$ cm/ns, $Z_0 = 100$, $R_S = 10$, $R_L = 150$ and the frequency of operation is 20 MHz.
- Calculate the reflection coefficient, ρ_L at $x = L$. Hence calculate the phasor ratio $\frac{G_0}{F_0}$ at $x = 0$.
 - Calculate the line impedance $\frac{V_0}{I_0}$ at $x = 0$.
 - By treating the circuit at the source end as a potential divider, calculate V_0 if $V_S = 10$.
 - Calculate F_0 and hence calculate F_L , G_L and the load voltage, V_L .
 - Calculate the complex power supplied by the source.