

IMPERIAL COLLEGE LONDON

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
EXAMINATIONS 2007

EEE/ISE PART I: MEng, BEng and ACGI

ANALYSIS OF CIRCUITS

Wednesday, 6 June 10:00 am

Corrected Copy

Time allowed: 2:00 hours

There are FOUR questions on this paper.

Q1 is compulsory.

Answer Q1 and any two of questions 2-4.

Q1 carries 40% of the marks. Questions 2 to 4 carry equal marks (30% each).


Any special instructions for invigilators and information for candidates are on page 1.

Examiners responsible

First Marker(s) : D.G. Haigh, D.G. Haigh


Second Marker(s) : P.D. Mitcheson, P.D. Mitcheson

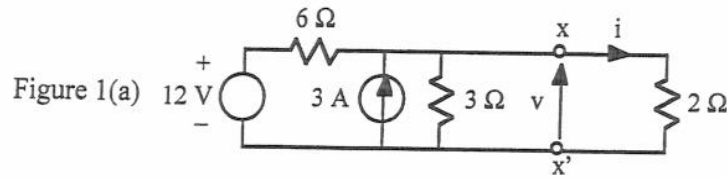- 1 a) Use source transformations to derive a simplified equivalent circuit for the sub-circuit in Figure 1 (a) to the left of the terminals x, x' . Hence, determine the current i when the sub-circuit is connected to the 2Ω resistor.




[4]

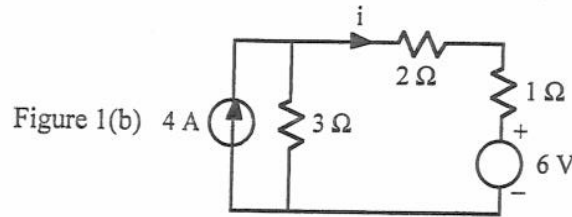- b) Use the principle of superposition to find current i in the circuit in Figure 1(b):




[4]

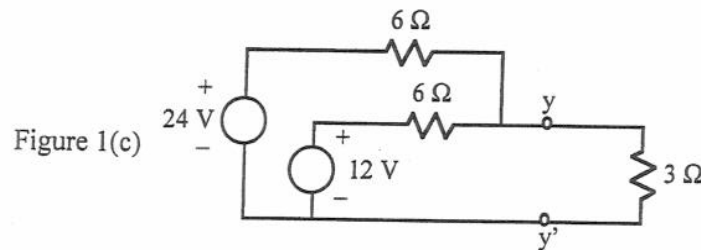- c) Find the Norton equivalent circuit (current source with resistor in parallel with it) for the sub-circuit in Figure 1(c) to the left of the terminals y, y' . What is the voltage across the 3Ω resistor when it is connected to the sub-circuit?




[4]

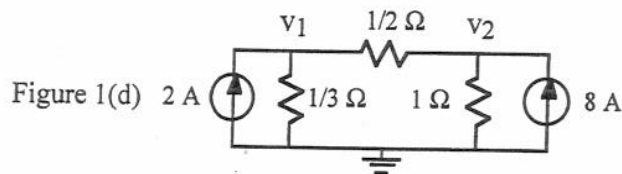- d) Use nodal analysis to determine the nodal voltages v_1 and v_2 in the circuit of Figure 1(d):




[4]

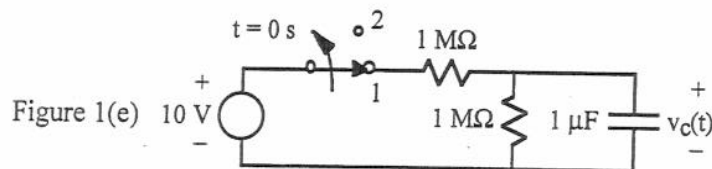
- e) In the circuit of Figure 1(e), the switch remains in position 1 for a long time before moving to position 2 at time $t = 0$ s. Find (i) capacitor voltage $v_c(t)$ at $t = 0$ s before the switch moves, (ii) final value of $v_c(t)$ for $t \rightarrow \infty$, (iii) the time constant for $t \geq 0$ s and (iv) an equation for $v_c(t)$ as a function of time.



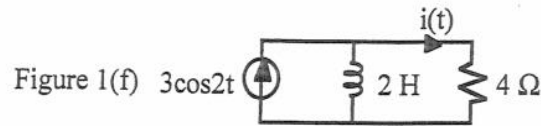
- f) Draw the phasor equivalent circuit for the circuit in Figure 1(f). Hence determine the phasor for the current $i(t)$ in the $4\ \Omega$ resistor. Hence, derive an expression for $i(t)$. [4]



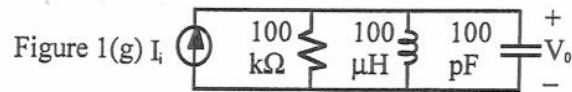
- g) Figure 1(g) shows a parallel LC tuned-circuit with loss, driven by a current source (which could represent the output of a transistor). The transfer function V_o/I_i has the form of a bandpass filter. For this circuit, determine the centre frequency in rads/sec, the Q-factor and the bandwidth in rads/sec. [4]



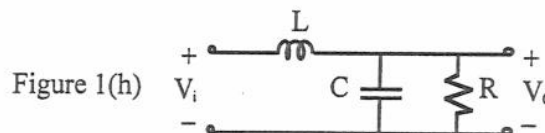
- h) For the filter circuit shown in Figure 1(h), determine the frequency response function $H(j\omega) = V_o/V_i$. By considering the behaviour of $H(j\omega)$ at the resonant frequency, at zero frequency and for frequency $\omega \rightarrow \infty$, show that the filter is a low-pass filter. [4]



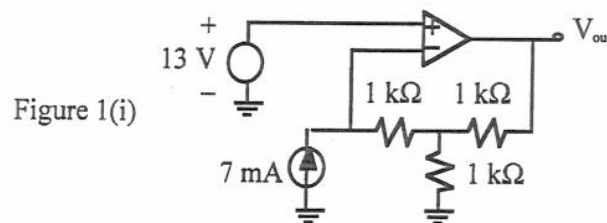- i) For the filter circuit shown in Figure 1(i), where the op-amp may be assumed to be ideal, determine the voltage V_{out} . [4]



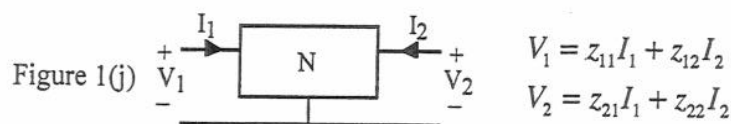- j) A linear 2-port circuit with its 2-port impedance description is given in Figure 1(j). Determine, in terms of the z-parameters z_{11} , z_{12} , z_{21} and z_{22} , expressions for (i) the voltage gain V_2/V_1 when port 2 is terminated in an open-circuit and (ii) the current gain I_2/I_1 when port 2 is terminated in a short-circuit. [4]



- 2 a) Give definitions for the voltage between two nodes in a circuit and the current flowing through an element in a circuit in terms of electrical charge Q , work (or energy) E and time t .

State Kirchoff's current law as it may be applied to any node in a circuit.

State Kirchoff's voltage law as it may be applied to any set of elements that form a loop in a circuit.

State how in general how the voltage across an element in a circuit is related to the voltages at its two nodes.

[6]

- b) The circuit in Figure 2.1 consists of resistors and DC current sources only:

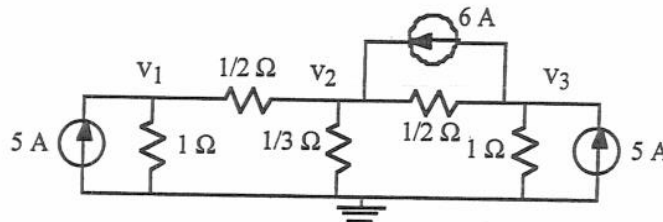


Figure 2.1 Circuit for Question 2(b)

Write the set of nodal equations that describe the circuit and may be used to solve for the node voltages, v_1 , v_2 , and v_3 (Do not solve the equations). You may use a by-inspection method if you wish.

[10]

- c) State two methods that may be used to solve sets of linear simultaneous equations, such as those that are obtained in nodal analysis. List briefly their features, positive and/or negative.

[5]

- d) The circuit in Figure 2.2 consists of a DC current source, two DC voltage sources and some resistors specified by their conductances (in Siemens):

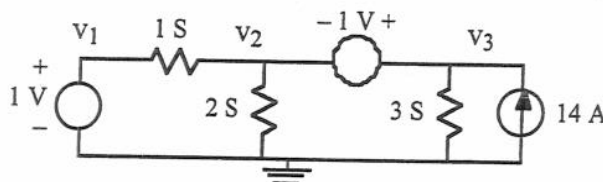


Figure 2.2 Circuit for Question 2(d)

Write the set of nodal equations that describe the circuit and solve them in order to determine the node voltages, v_1 , v_2 , and v_3 .

[9]

3. a) Write down the phasors corresponding to the following current functions (for convenience, angles are shown in degrees):
- i) $i_1(t) = 5\cos(2t - 90^\circ)$
 - ii) $i_2(t) = 6\sin(t + 45^\circ)$
 - iii) $i_3(t) = -2\cos(2t)$
- [6]
- b) Give expressions for the impedance of an inductor of inductance value L and of a capacitor of capacitance value C as a function of frequency ω in both rectangular and polar forms.
- [4]
- c) Two elements of impedance z_1 and z_2 are connected in series across a voltage source V_s . Draw a sketch showing the circuit. Choose and indicate an orientation for the voltage v_2 across z_2 , and state the *voltage divider rule* that determines v_2 in terms of V_s and the two impedances z_1 and z_2 .
- [2]

- d) Consider the circuit in Figure 3.1:

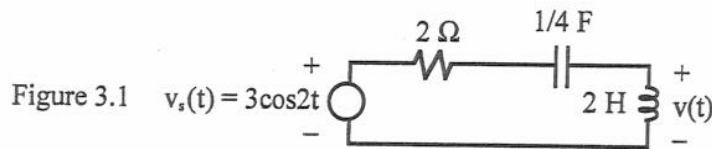


Figure 3.1 Circuit for Question 3(d)

- i) Draw the phasor equivalent circuit for this circuit.
 - ii) Carry out circuit analysis to determine the phasor form \bar{V} of voltage $v(t)$.
 - iii) Convert the phasor \bar{V} into the corresponding time domain form $v(t)$.
- [12]
- e) The circuit in Figure 3.2 has a periodic current excitation that consists of a fundamental sinusoidal component and its 2nd harmonic component, as shown:

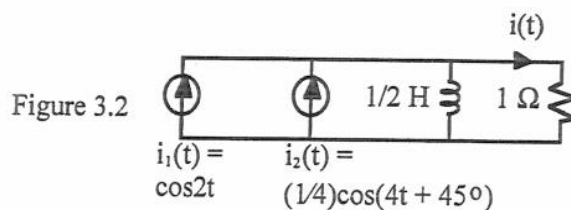


Figure 3.2 Circuit for Question 3(e)

Show the two phasor equivalent circuits which can be used to solve for $i(t)$ using the principle of superposition (Do not complete the solution for $i(t)$).

[6]

4. a) The *dependent source*, or controlled source, is a key element in circuit analysis because it can be used to model active elements. The dependent source is a 2-port circuit where the independent signal variable at the input port and the dependent signal variable at the output port may be a voltage or current, leading to four types of dependent source.
- Draw symbols for the four types of dependent source, showing clearly the input and output signal variables.
 - Give an equation for each of the four types of dependent source that expresses the dependent output variable as a function of the independent input variable, assuming that the sources may be treated as linear elements.
 - State the units of the gain, defined as output variable divided by input variable for each of the four types of dependent source.

[12]

- b) The circuit in Figure 4.1 contains a voltage-controlled current source, as well as an independent current source and two resistors. Node voltage v_1 is the controlling voltage for the voltage-controlled current source.

Determine the current i in this circuit. It is recommended to use nodal analysis with the method of tapping and then un-taping the dependent source.

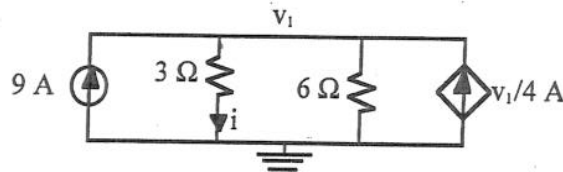


Figure 4.1 Circuit for Question 4(b)

[8]

- c) Of the four types of dependent sources, identify one type most suitable to model the field-effect transistor and one type most suitable to model the voltage operational amplifier.

Show how the terminals of these dependent sources should be connected given that the dependent source has 4 terminals and the operational amplifier and transistor have only 3 terminals.

[4]

- d) The sub-circuit in Figure 4.2 contains a resistor and a current-controlled voltage source. Suggest three values for the gain of the dependent source, r_m , such that the sub-circuit is equivalent to (i) a resistance of 10Ω , (ii) a short circuit and (iii) a resistance of -10Ω , respectively.


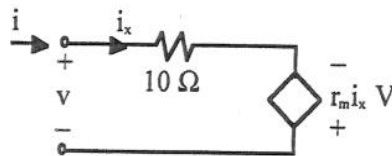


Figure 4.2 Circuit for Question 4(d)

[6]


SOLUTIONS

Q1. a)

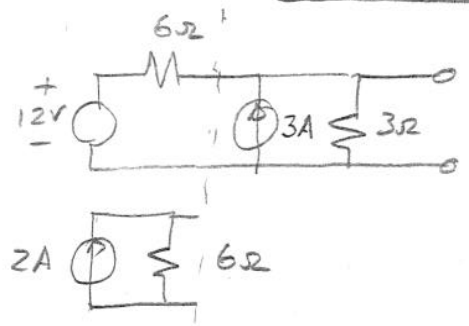

KEY	
A	Application
B	Bookwork
T	Theory

A

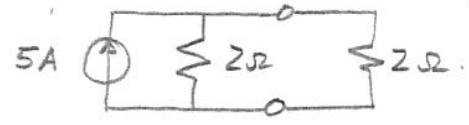

$$i = \frac{5}{2} = 2.5A$$

4

b) Replace V-source by s/c :

$$i_1 = 4/2 = 2A$$

Replace I-source by o/c :

$$i_2 = -6/6 = -1A$$


$$i = i_1 + i_2 = 1A$$

A

4

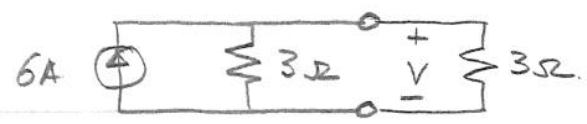c) $i_{s/c} = \frac{24}{6} + \frac{12}{6} = 6A$

$$R_{eq} = 6\Omega // 6\Omega = 3\Omega$$



$$V = 3A \times 3\Omega = 9V$$

A

4

d) Nodal equations

$$(3+2)V_1 - 2V_2 = 2$$

$$-2V_1 + (1+2)V_2 = 8$$

$$5V_1 - 2V_2 = 2$$

$$-2V_1 + 3V_2 = 8$$

$$\left(5 - \frac{4}{3}\right)V_1 = 2 + \frac{16}{3}$$

$$V_1 = 2V \quad V_2 = \frac{1}{2}(5V_1 - 2) = 4V$$

A

4

e) $V_{co} = 5V$

$$V_{\infty} = 0V$$


$$\tau = 10^6 \times 10^{-6} = 1s$$

$$V_c(t) = V_{co} + (V_{\infty} - V_{co})(1 - e^{-t/\tau})$$

A

4

f)

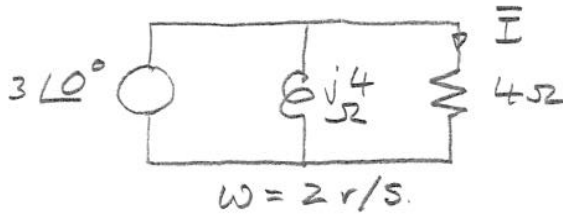

A

$$\bar{I} = \frac{j4}{4+j4} \times 3\angle 0^\circ = \frac{4\angle 90^\circ}{4\sqrt{2}\angle 45^\circ} \times 3\angle 0^\circ = \frac{3}{\sqrt{2}} \angle 45^\circ$$

$$i(t) = \frac{3}{\sqrt{2}} \cos(2t + 45^\circ)$$

4

g) For tuned-circuit,

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(10^{-4} \cdot 10^{-10})}} = 10^7 \text{ rad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{10^5}{10^7 \cdot 10^{-4}} = 100$$

$$\omega_B = \frac{\omega_0}{Q} = 10^5 \text{ rad/sec}$$

4

h) using voltage divider rule:


$$H(j\omega) = \frac{V_o}{V_i} = \frac{z_2}{z_1 + z_2} = \frac{1}{1 + z_1 Y_2}$$

$$= \frac{1}{1 + j\omega L(j\omega C + \frac{1}{R})} = \frac{1}{(j\omega)^2 LC + j\omega \frac{L}{R} + 1}$$

ω	$ H $
0	$\frac{1}{R\sqrt{LC}}$
ω_0	$\frac{1}{R\sqrt{LC}}$
$\rightarrow \infty$	0

∴ Filter is a Lowpass filter

4

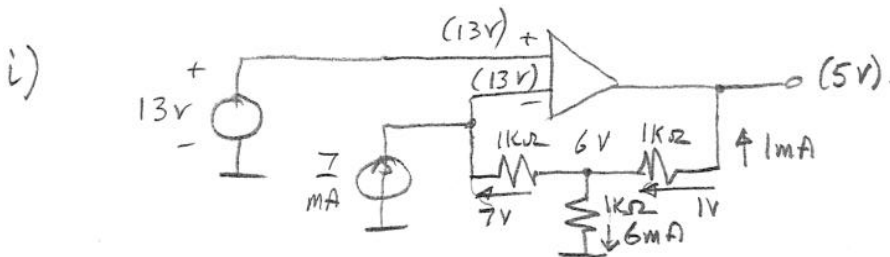

$$V_{out} = 5V$$

4

j)

$$V_1 = z_{11} I_1 + z_{12} I_2$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

$$I_2 = 0, \frac{V_2}{V_1} = \frac{z_{21} I_1}{z_{11} I_1} = \frac{z_{21}}{z_{11}} \quad ; \quad V_2 = 0, 0 = z_{21} I_1 + z_{12} I_2$$

$$\frac{I_2}{I_1} = -\frac{z_{21}}{z_{12}}$$

4

2

a) Voltage between two nodes = E/Q , where E is energy needed to move charge between the nodes.
Current = dQ/dt , i.e. rate of flow of charge.


B

Net sum of currents in elements incident at node is zero.

Net sum of element voltage drops (or rises) is zero.

⑥ Element voltages are differences of nodal voltages.

b)

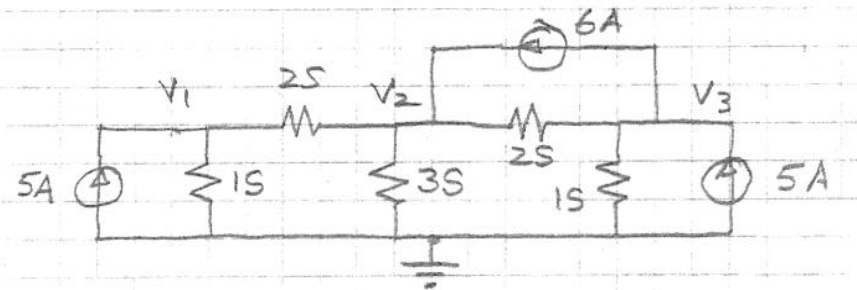

A


$$\begin{bmatrix} 3 & -2 & 0 \\ -2 & 7 & -2 \\ 0 & -2 & 3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 6 \\ -1 \end{bmatrix}$$

⑩

c) Substitution - Easy to understand - Very long
Gaussian elimination - Algorithmic - Easy to program

B

d)

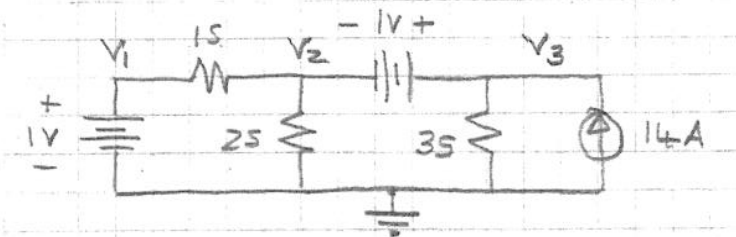

$$\begin{bmatrix} 1 & -1 & 0 \\ -1 & 3 & 0 \\ 0 & 0 & 3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 14 \end{bmatrix}$$

$$V_2 - V_3 = -1 \quad V_1 = 1$$

A

$$\begin{bmatrix} -1 & 3 & 3 \\ 1 & 0 & 0 \\ 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 14 \\ 1 \\ -1 \end{bmatrix} \quad \begin{bmatrix} -1 & 6 \\ 1 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 11 \\ 1 \end{bmatrix}$$

⑨

30

$$[6][V_2] = 12 \quad V_2 = 2V, \quad V_1 = 1V, \quad V_3 = 3V$$

3 a) $\bar{I}_1 = 5 \angle -90^\circ = -j5$
 $\bar{I}_2 = 6 \angle -45^\circ = 3\sqrt{2} - j3\sqrt{2}$
 $\bar{I}_3 = 2 \angle 180^\circ = -2$

⑥

A



b) $Z_L = j\omega L = \omega L \angle 90^\circ$
 $Z_C = \frac{1}{j\omega C} = \frac{1}{\omega C} \angle -90^\circ$

B

④

B

②

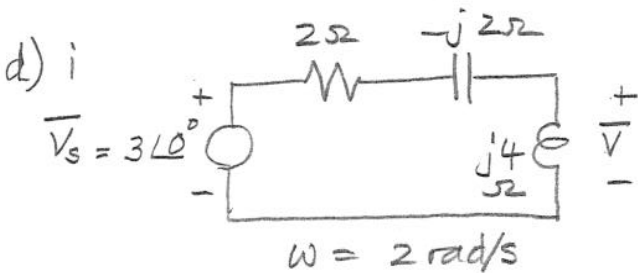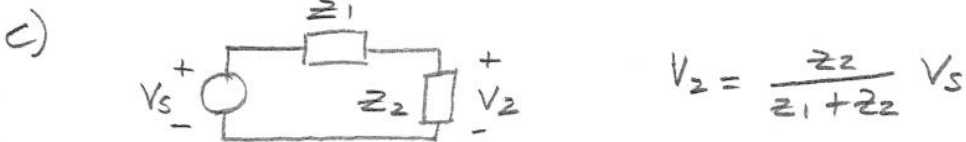


ii Use voltage division:
 $\bar{V} = \frac{Z_2}{Z_1 + Z_2} \bar{V}_s = \frac{j4}{2 - j2 + j4} 3 \angle 0^\circ$
 $= \frac{4 \angle 90^\circ}{2\sqrt{2} \angle 45^\circ} 3 \angle 0^\circ$
 $= 3\sqrt{2} \angle 45^\circ$

A

⑫ iii $v(t) = 3\sqrt{2} \cos(2t + 45^\circ)$

e)

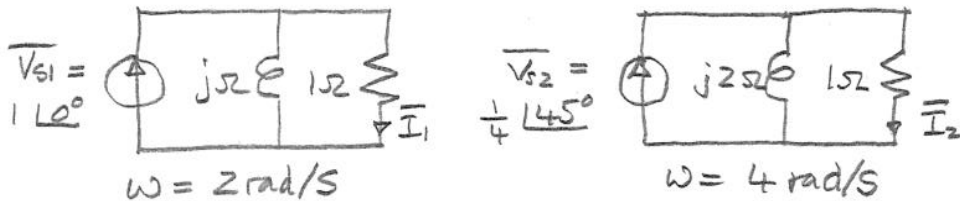


A

⑥

30

4 a) i)

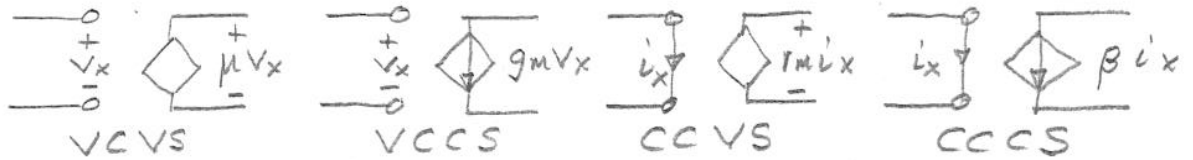

B

ii) $V_o = \mu V_x$ $I_o = g_m V_x$ $V_o = r_m i_x$ $I_o = \beta i_x$

iii) μ Dimensionless g_m A/V r_m V/A β Dimensionless

12

b) Tape the dependent source:

$\frac{1}{4}V_1 \rightarrow I_c$

Nodal analysis:

$$\frac{V_1}{3} + \frac{V_1}{6} = 9 + I_c$$

Untape source:

$$I_c = \frac{1}{4}V_1$$

$$\frac{V_1}{2} - \frac{1}{4}V_1 = 9$$


$$V_1 = 36 \text{ V}$$

$$i = \frac{V_1}{3} = 12 \text{ A}$$

A

8

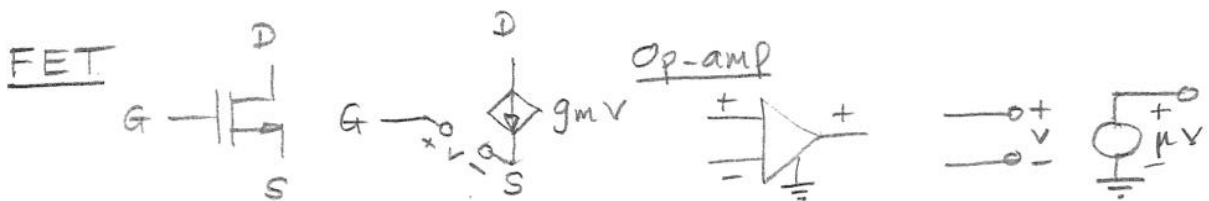c) For the FET - VCCS
For the op-amp - VCVS



B

4

d) By analysis:

$$\begin{aligned} V &= 10 i_x - r_m i_x \\ &= (10 - r_m) i_x \\ &= (10 - r_m) i \end{aligned}$$

A

∴ Equivalent to Thevenin resistance of $10 - r_m \Omega$

\equiv Res $r_m (\Omega)$

10 0

0 10

-10 20

6

30