

**Revision Lecture 2:**

**▷ Transients & Lines**

**Transients: Basic Ideas**

**Steady States**

**Determining Time Constant**

**Determining Transient Amplitude**

**Transmission Lines Basics**

**Reflections**

**Sinewaves and Phasors**

**Standing Waves**

# Revision Lecture 2: Transients & Lines

# Transients: Basic Ideas

## Revision Lecture 2: Transients & Lines

### Transients: Basic Ideas

#### Steady States

#### Determining Time Constant

#### Determining Transient Amplitude

#### Transmission Lines Basics

#### Reflections

#### Sinewaves and Phasors

#### Standing Waves

- Transients happen in response to a **sudden change**
  - Input voltage/current abruptly changes its magnitude, frequency or phase
  - A switch alters the circuit
- 1st order circuits only: one capacitor/inductor
- All voltage/current waveforms are: **Steady State + Transient**
  - **Steady States**: find with nodal analysis or transfer function
    - ▷ Note: **Steady State** is not the same as **DC Level**
    - ▷ Need steady states before **and** after the sudden change
  - **Transient**: Always a negative exponential:  $Ae^{-\frac{t}{\tau}}$ 
    - ▷ Time Constant:  $\tau = RC$  or  $\frac{L}{R}$  where  $R$  is the Thévenin resistance at the terminals of  $C$  or  $L$
    - ▷ Find transient amplitude,  $A$ , from continuity since  $V_C$  or  $I_L$  cannot change instantly.
    - ▷  $\tau$  and  $A$  can also be found from the transfer function.

# Steady States

A **steady-state** output assumes the input frequency, phase and amplitude are constant forever. You need to determine **two**  $y_{SS}(t)$  steady state outputs: one for **before** the transient ( $t < 0$ ) and one **after** ( $t \geq 0$ ). At  $t = 0$ ,  $y_{SS}(0-)$  means the first one and  $y_{SS}(0+)$  means the second.

## Method 1: Nodal analysis

Input voltage is DC ( $\omega = 0$ )

$$\Rightarrow Z_L = 0 \text{ (for capacitor: } Z_C = \infty)$$

So  $L$  acts as a short circuit

Potential divider:  $y_{SS} = \frac{1}{2}x$



$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

## Method 2: Transfer function

$$\frac{Y}{X}(j\omega) = \frac{R+j\omega L}{2R+j\omega L}$$

$$\text{set } \omega = 0: \frac{Y}{X}(0) = \frac{1}{2}$$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

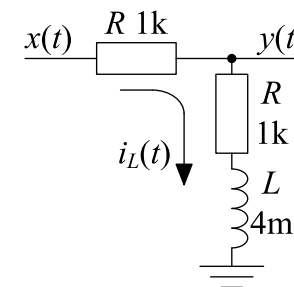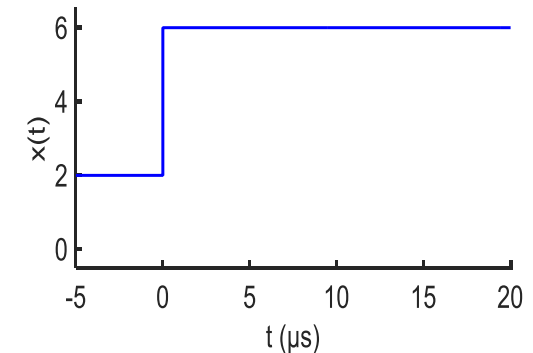

**Sinusoidal input**  $\Rightarrow$  **Sinusoidal steady state**  $\Rightarrow$  use phasors.

Then convert phasors to time waveforms to calculate the actual output voltages  $y_{SS}(0-)$  and  $y_{SS}(0+)$  at  $t = 0$ .



# Determining Time Constant

## Method 1: Thévenin

- (a) Remove the capacitor/inductor
- (b) Set all sources to zero (including the input voltage source). Leave output unconnected.
- (c) Calculate the Thévenin resistance between the capacitor/inductor terminals:

$$R_{Th} = 8R \parallel 4R \parallel (6R + 2R) = 2R$$

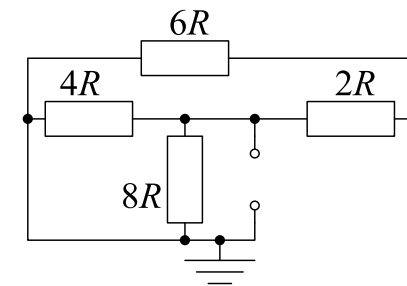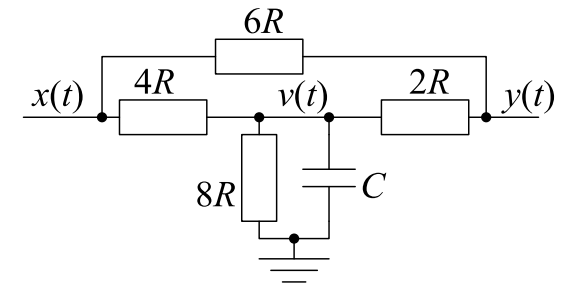- (d) Time constant:  $= R_{Th}C$  or  $\frac{L}{R_{Th}}$   
 $\tau = R_{Th}C = 2RC$



## Method 2: Transfer function

- (a) Calculate transfer function using nodal analysis

$$\text{KCL @ } V: \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ } Y: \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Eliminate } V \text{ to get transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

- (b) Time Constant  $= \frac{1}{\text{Denominator corner frequency}}$

$$\omega_d = \frac{16}{32RC} \Rightarrow \tau = \frac{1}{\omega_d} = 2RC$$

# Determining Transient Amplitude

Revision Lecture 2:  
Transients & Lines

Transients: Basic  
Ideas

Steady States

Determining Time  
Constant

Determining  
Transient

▷ Amplitude

Transmission Lines  
Basics

Reflections

Sinewaves and  
Phasors

Standing Waves

After an input change at  $t = 0$ ,  $y(t) = y_{SS}(t) + Ae^{-\frac{t}{\tau}}$ .

$\Rightarrow y(0+) = y_{SS}(0+) + A \Rightarrow A = y(0+) - y_{SS}(0+)$

Method: (a) calculate true output  $y(0+)$ , (b) subtract  $y_{SS}(0+)$  to get  $A$


(i) Version 1:  $v_C$  or  $i_L$  continuity

$x(0-) = 2 \Rightarrow i_L(0-) = 1 \text{ mA}$

Continuity  $\Rightarrow i_L(0+) = i_L(0-)$

Replace  $L$  with a 1 mA current source

$y(0+) = x(0+) - iR = 6 - 1 = 5$

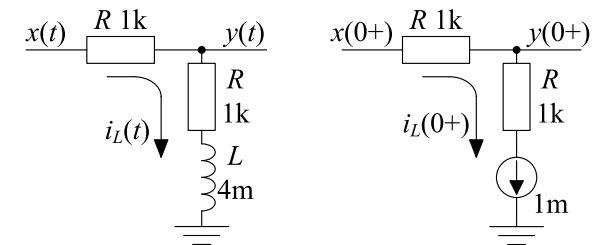

(i) Version 2: Transfer function

$$H(j\omega) = \frac{Y}{X}(j\omega) = \frac{R+j\omega L}{2R+j\omega L}$$



Input step,  $\Delta x = x(0+) - x(0-) = +4$

$y(0+) = y(0-) + H(j\infty) \times \Delta x$

$$= 1 + \Delta y = 1 + 1 \times 4 = 5$$

(ii)  $A = y(0+) - y_{SS}(0+) = 5 - 3 = 2$

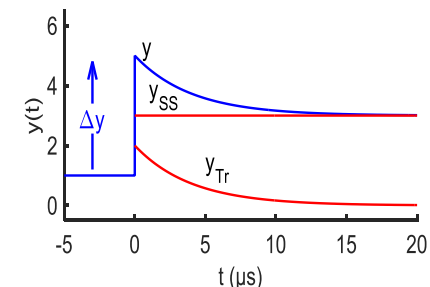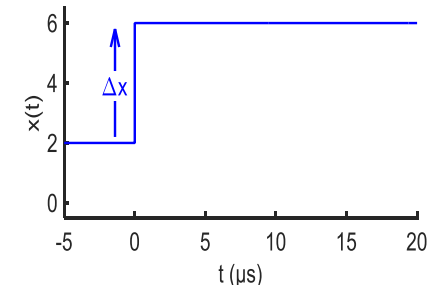(iii)  $y(t) = y_{SS}(t) + Ae^{-t/\tau}$   
 $= 3 + 2e^{-t/2\mu}$



# Transmission Lines Basics


- Revision Lecture 2: Transients & Lines
- Transients: Basic Ideas
- Steady States
- Determining Time Constant
- Determining Transient Amplitude
- Transmission Lines
  - ▷ Basics
  - Reflections
  - Sinewaves and Phasors
  - Standing Waves

Transmission Line: constant  $L_0$  and  $C_0$  : inductance/capacitance per metre.


**Forward wave** travels along the line:  $f_x(t) = f_0 \left( t - \frac{x}{u} \right)$ .

Velocity  $u = \sqrt{\frac{1}{L_0 C_0}} \approx \frac{1}{2}c = 15 \text{ cm/ns}$

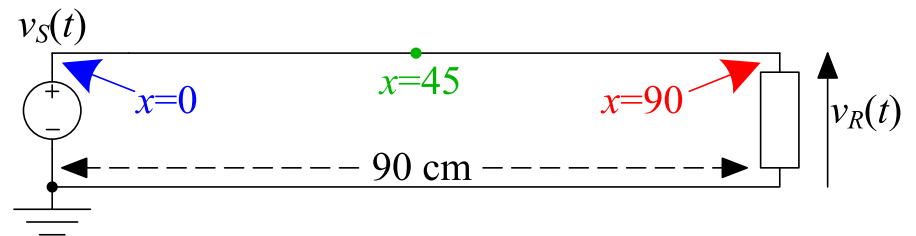$f_x(t)$  equals  $f_0(t)$  but delayed by  $\frac{x}{u}$ .



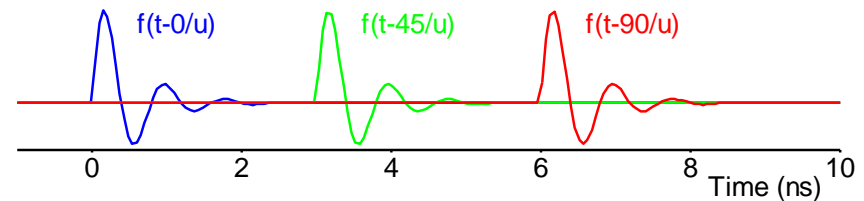Knowing  $f_x(t)$  for  $x = x_0$  fixes it for all other  $x$ .



**Backward wave:**  $g_x(t)$  is the same but travelling  $\leftarrow$ :  $g_x(t) = g_0 \left( t + \frac{x}{u} \right)$ .

**Voltage and current are:**  $v_x = f_x + g_x$  and  $i_x = \frac{f_x - g_x}{Z_0}$  where  $i_x$  is positive in the  $+x$  direction ( $\rightarrow$ ) and  $Z_0 = \sqrt{\frac{L_0}{C_0}}$


Waveforms of  $f_x$  and  $g_x$  are determined by the connections at both ends.

# Reflections

- Revision Lecture 2:
- Transients & Lines

---

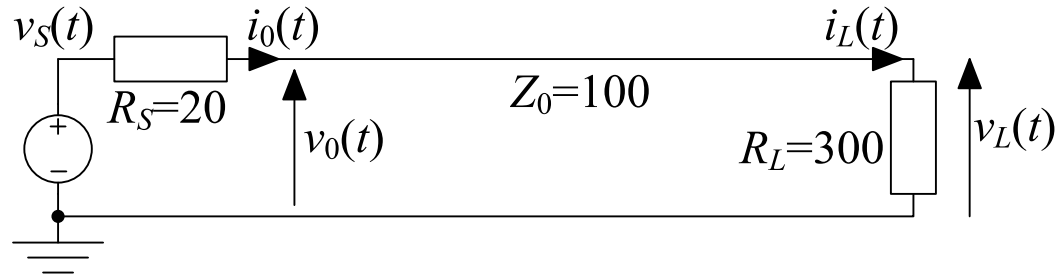- Transients: Basic Ideas
- Steady States
- Determining Time Constant
- Determining Transient Amplitude
- Transmission Lines Basics
- ▷ Reflections
- Sinewaves and Phasors
- Standing Waves



$$v_x = f_x + g_x$$

$$i_x = \frac{f_x - g_x}{Z_0}$$

At  $x = L$ , Ohm's law  $\Rightarrow \frac{v_L(t)}{i_L(t)} = R_L \Rightarrow g_L(t) = \frac{R_L - Z_0}{R_L + Z_0} \times f_L(t)$ .

Reflection coefficient:  $\rho_L = \frac{g_L(t)}{f_L(t)} = \frac{R_L - Z_0}{R_L + Z_0}$

$\rho_L \in [-1, +1]$  and increases with  $R_L$

Knowing  $f_x(t)$  for  $x = x_0$  now tells you  $f_x, g_x, v_x, i_x \forall x$

At  $x = 0$ :  $f_0(t) = \frac{Z_0}{R_S + Z_0} v_S(t) + \frac{R_S - Z_0}{R_S + Z_0} g_0(t) = \tau_0 v_S(t) + \rho_0 g_0(t)$

Wave bounces back and forth getting smaller with each reflection:

$$v_S(t) \xrightarrow{\times \tau_0} f_0(t) \xrightarrow{\times \rho_L} g_0(t + \frac{2L}{u}) \xrightarrow{\times \rho_0} f_0(t + \frac{2L}{u}) \xrightarrow{\times \rho_L} g_0(t + \frac{4L}{u}) \xrightarrow{\times \rho_0} \dots$$

Infinite sum:

$$f_0(t) = \tau_0 v_S(t) + \tau_0 \rho_L \rho_0 v_S(t - \frac{2L}{u}) + \dots = \sum_{i=0}^{\infty} \tau_0 \rho_L^i \rho_0^i v_S(t - \frac{2Li}{u})$$


# Sinewaves and Phasors

- Revision Lecture 2: Transients & Lines
- Transients: Basic Ideas
- Steady States
- Determining Time Constant
- Determining Transient Amplitude
- Transmission Lines Basics
- Reflections
  - Sinewaves and Phasors
- Standing Waves

Sinewaves are easier because:

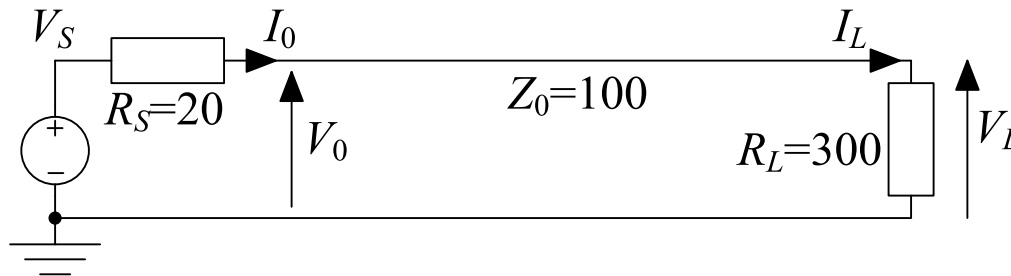1. Use phasors to eliminate  $t$ :  $f_0(t) = A \cos(\omega t + \phi) \Leftrightarrow F_0 = Ae^{j\phi}$
2. Time delays are just phase shifts:  
 $f_x(t) = A \cos(\omega(t - \frac{x}{u}) + \phi) \Leftrightarrow F_x = Ae^{j(\phi - \frac{\omega}{u}x)} = F_0 e^{-jkx}$   
 $k = \frac{\omega}{u} = \frac{2\pi}{\lambda}$  is the **wavenumber**: radians per metre (c.f.  $\omega$  in rad/s)

As before:  $V_x = F_x + G_x$  and  $I_x = \frac{F_x - G_x}{Z_0}$



As before:

$$G_L = \rho_L F_L$$

$$F_0 = \tau_0 V_S + \rho_0 G_0$$

But  $G_0 = F_0 \rho_L e^{-2jkL}$  : roundtrip delay of  $\frac{2L}{u}$  + reflection at  $x = L$ .  
 Substituting for  $G_0$  in source end equation:  $F_0 = \tau_0 V_S + \rho_0 F_0 \rho_L e^{-2jkL}$   
 $\Rightarrow F_0 = \frac{\tau_0}{1 - \rho_0 \rho_L \exp(-2jkL)} V_S$  so no infinite sums needed 😊



# Standing Waves

## Revision Lecture 2: Transients & Lines

### Transients: Basic Ideas

#### Steady States

#### Determining Time Constant

#### Determining Transient Amplitude

#### Transmission Lines

#### Basics

#### Reflections

#### Sinewaves and Phasors


#### ▷ Standing Waves

Standing waves arise whenever a wave meets its reflection:

at positions where the two waves are **in phase** their amplitudes **add** but where they are **anti-phase** their amplitudes **subtract**.

At any point  $x$ ,
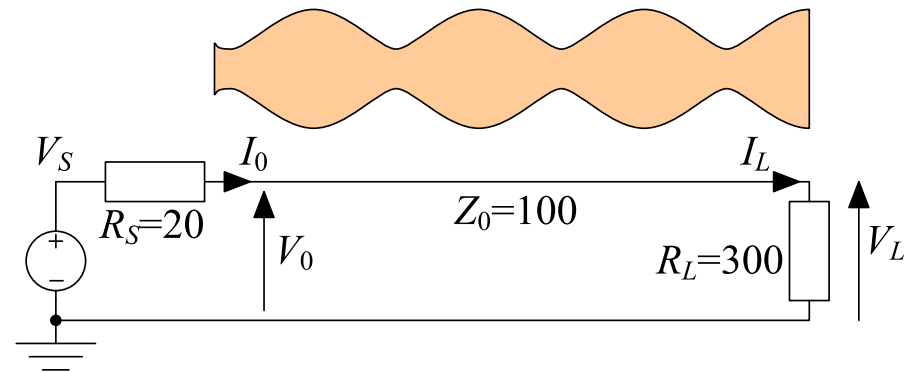
$$\text{delay of } \frac{x}{u} \Rightarrow F_x = F_0 e^{-jkx}$$



Backward wave:  $G_x = \rho_L F_x e^{-2jk(L-x)}$ : reflection + delay of  $2 \frac{L-x}{u}$

Voltage at  $x$ :  $V_x = F_x + G_x = F_0 e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Voltage Magnitude :  $|V_x| = |F_0| |1 + \rho_L e^{-2jk(L-x)}|$ : depends on  $x$

If  $\rho_L \geq 0$ , **max magnitude** is  $(1 + \rho_L) |F_0|$  whenever  $e^{-2jk(L-x)} = +1$   
 $\Rightarrow x = L$  or  $x = L - \frac{\pi}{k}$  or  $x = L - \frac{2\pi}{k}$  or ...

**Min magnitude** is  $(1 - \rho_L) |F_0|$  whenever  $e^{-2jk(L-x)} = -1$   
 $\Rightarrow x = L - \frac{\pi}{2k}$  or  $x = L - \frac{3\pi}{2k}$  or  $x = L - \frac{5\pi}{2k}$  or ...