#### Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

# Exam

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

# Exam Format

Question 1 (40%): eight short parts covering the whole syllabus.

Questions 2 and 3: single topic questions (answer both)

#### **Syllabus**

Does include: Everything in the notes.

Does not include: Two-port parameters (2008:1j), Gaussian elimination (2007:2c), Application areas (2008:3d), Nullators and Norators (2008:4c), Small-signal component models (2008:4e), Gain-bandwidth product (2006:4c), Zener Diodes (2008/9 syllabus), Non-ideal models of L, C and transformer (2011/12 syllabus), Transmission lines VSWR and crank diagram (2011/12 syllabus).

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

• All the points in a circuit joined together with zero-resistance wires make up a single node. The voltage is the same at any point in a node.

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- All the points in a circuit joined together with zero-resistance wires make up a single node. The voltage is the same at any point in a node.
- Choose one node in a circuit to be the reference node. Measure all node voltages relative to this one.

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- All the points in a circuit joined together with zero-resistance wires make up a single node. The voltage is the same at any point in a node.
- Choose one node in a circuit to be the reference node. Measure all node voltages relative to this one.
- Voltage across a component is the difference between the voltages at the two ends.  $V_{AB} = V_A V_B$ .

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- All the points in a circuit joined together with zero-resistance wires make up a single node. The voltage is the same at any point in a node.
- Choose one node in a circuit to be the reference node. Measure all node voltages relative to this one.
- Voltage across a component is the difference between the voltages at the two ends.  $V_{AB} = V_A V_B$ .
- Passive sign convention: Current and voltage arrows for a 2-terminal component are in opposite directions.

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- All the points in a circuit joined together with zero-resistance wires make up a single node. The voltage is the same at any point in a node.
- Choose one node in a circuit to be the reference node. Measure all node voltages relative to this one.
- Voltage across a component is the difference between the voltages at the two ends.  $V_{AB} = V_A V_B$ .
- Passive sign convention: Current and voltage arrows for a 2-terminal component are in opposite directions.
- Components are in parallel if they are joined together at both ends. Components in parallel have the same voltage across them.

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- All the points in a circuit joined together with zero-resistance wires make up a single node. The voltage is the same at any point in a node.
- Choose one node in a circuit to be the reference node. Measure all node voltages relative to this one.
- Voltage across a component is the difference between the voltages at the two ends.  $V_{AB} = V_A V_B$ .
- Passive sign convention: Current and voltage arrows for a 2-terminal component are in opposite directions.
- Components are in parallel if they are joined together at both ends. Components in parallel have the same voltage across them.
- Components are in series if the same current is forced to flow through each one.

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- All the points in a circuit joined together with zero-resistance wires make up a single node. The voltage is the same at any point in a node.
- Choose one node in a circuit to be the reference node. Measure all node voltages relative to this one.
- Voltage across a component is the difference between the voltages at the two ends.  $V_{AB} = V_A V_B$ .
- Passive sign convention: Current and voltage arrows for a 2-terminal component are in opposite directions.
- Components are in parallel if they are joined together at both ends. Components in parallel have the same voltage across them.
- Components are in series if the same current is forced to flow through each one.
- KCL (Kirchoff's Current Law): The total current going out of a node (or any collection of nodes) sums to zero.

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Ohm's law relates the voltage drop across a resistor to the current flowing in it:

V = IZ



Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Ohm's law relates the voltage drop across a resistor to the current flowing in it:

V = IZ



Passive Sign Convention: V and I arrows must point in opposite directions (otherwise you need a - sign in Ohm's law)

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Ohm's law relates the voltage drop across a resistor to the current flowing in it:

V = IZ



Passive Sign Convention: V and I arrows must point in opposite directions (otherwise you need a - sign in Ohm's law)

Voltage arrow means  $V = V_{tip} - V_{base} = V_{AB}$  (subscript order opposite from vectors)

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Ohm's law relates the voltage drop across a resistor to the current flowing in it:

V = IZ



Passive Sign Convention: V and I arrows must point in opposite directions (otherwise you need a - sign in Ohm's law)

Voltage arrow means  $V = V_{tip} - V_{base} = V_{AB}$  (subscript order opposite from vectors)

Ohm's law still true if all currents are in mA and all impedances in  $k\Omega$ .

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Ohm's law relates the voltage drop across a resistor to the current flowing in it:

V = IZ



Passive Sign Convention: V and I arrows must point in opposite directions (otherwise you need a - sign in Ohm's law)

Voltage arrow means  $V = V_{tip} - V_{base} = V_{AB}$  (subscript order opposite from vectors)

Ohm's law still true if all currents are in mA and all impedances in  $k\Omega$ .

Ohm's law still true if all currents and all voltages are RMS values:  $\tilde{V} = \tilde{I}Z$  where  $\tilde{V} = \frac{V}{\sqrt{2}}$  for a voltage phasor V.

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick any node as the voltage reference. Label its voltage as 0 V. Label any dependent sources with  $V_S$ ,  $I_S$ , ....
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with  $X, Y, \ldots$ , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each "normal" node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each "super-node". A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components linking these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick any node as the voltage reference. Label its voltage as 0 V. Label any dependent sources with  $V_S$ ,  $I_S$ , ....
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with  $X, Y, \ldots$ , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each "normal" node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each "super-node". A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components linking these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick any node as the voltage reference. Label its voltage as 0 V. Label any dependent sources with  $V_S$ ,  $I_S$ , ....
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with  $X, Y, \ldots$ , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each "normal" node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each "super-node". A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components linking these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick any node as the voltage reference. Label its voltage as 0 V. Label any dependent sources with  $V_S$ ,  $I_S$ , ....
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with  $X, Y, \ldots$ , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each "normal" node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each "super-node". A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components linking these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick any node as the voltage reference. Label its voltage as 0 V. Label any dependent sources with  $V_S$ ,  $I_S$ , ....
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with  $X, Y, \ldots$ , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each "normal" node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each "super-node". A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components linking these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick any node as the voltage reference. Label its voltage as 0 V. Label any dependent sources with  $V_S$ ,  $I_S$ , ....
- (2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.
- (3) Pick an unlabelled node and label it with  $X, Y, \ldots$ , then loop back to step (2) until all nodes are labelled.
- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each "normal" node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each "super-node". A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components linking these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

(1) Pick any node as the voltage reference. Label its voltage as 0 V. Label any dependent sources with  $V_S$ ,  $I_S$ , ....

(2) If any voltage sources are connected to a labelled node, label their other ends by adding the value of the source onto the voltage of the labelled end.

(3) Pick an unlabelled node and label it with  $X, Y, \ldots$ , then loop back to step (2) until all nodes are labelled.

- (4) For each **dependent source**, write down an equation that expresses its value in terms of other node voltages.
- (5) Write down a KCL equation for each "normal" node (i.e. one that is not connected to a floating voltage source).
- (6) Write down a KCL equation for each "super-node". A super-node consists of a set of nodes that are joined by floating voltage sources and includes any other components linking these nodes.
- (7) Solve the set of simultaneous equations that you have written down.

Revision Lecture 1: Nodal

Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes



Revision Lecture 1: Nodal

Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

#### (1) Pick reference node.



Revision Lecture 1: Nodal

- Analysis
- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick reference node.
- (2) Label nodes: 8



Revision Lecture 1: Nodal

- Analysis
- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick reference node.
- (2) Label nodes: 8, X



- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick reference node.
- (2) Label nodes: 8, X and X + 2 since
  - it is joined to X via a voltage source.



- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick reference node.
- (2) Label nodes: 8, X and X + 2 since it is joined to X via a voltage source.
- (3) Write KCL equations but count all the nodes connected via floating voltage sources as a single "super-node" giving one equation

$$\frac{X-8}{1} + \frac{X}{2} + \frac{(X+2)-0}{3} = 0$$





Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
  Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick reference node.
- (2) Label nodes: 8, X and X + 2 since it is joined to X via a voltage source.
- (3) Write KCL equations but count all the nodes connected via floating voltage sources as a single "super-node" giving one equation

 $\frac{X-8}{1} + \frac{X}{2} + \frac{(X+2)-0}{3} = 0$ 

Ohm's law always involves the difference between the voltages at either end of a resistor. (Obvious but easily forgotten)



Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
  Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- (1) Pick reference node.
- (2) Label nodes: 8, X and X + 2 since it is joined to X via a voltage source.
- (3) Write KCL equations but count all the nodes connected via floating voltage sources as a single "super-node" giving one equation

 $\frac{X-8}{1} + \frac{X}{2} + \frac{(X+2)-0}{3} = 0$ 

Ohm's law always involves the difference between the voltages at either end of a resistor. (Obvious but easily forgotten)

(4) Solve the equations: X = 4



0

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Components in series form a voltage divider: Voltages  $\propto R$ .

$$\frac{V_k}{V_{Total}} = \frac{R_k}{R_{Total}}$$



Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Components in series form a voltage divider: Voltages  $\propto R$ .

 $\frac{V_k}{V_{Total}} = \frac{R_k}{R_{Total}}$ 

Components in parallel form a current divider: Currents  $\propto G$ .

$$\frac{I_k}{I_{Total}} = \frac{G_k}{G_{Total}}$$





Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Components in series form a voltage divider: Voltages  $\propto R$ .

 $\frac{V_k}{V_{Total}} = \frac{R_k}{R_{Total}}$ 

Components in parallel form a current divider: Currents  $\propto G$ .

$$\frac{I_k}{I_{Total}} = \frac{G_k}{G_{Total}}$$



$$X = \frac{G_1 V_1 + G_2 V_2 + G_3 V_3}{G_{Total}}$$







Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Components in series form a voltage divider: Voltages  $\propto R$ .

 $\frac{V_k}{V_{Total}} = \frac{R_k}{R_{Total}}$ 

Components in parallel form a current divider: Currents  $\propto G$ .

$$\frac{I_k}{I_{Total}} = \frac{G_k}{G_{Total}}$$

Summing Junction: X is a weighted average with weights  $\propto G$ .

$$X = \frac{G_1 V_1 + G_2 V_2 + G_3 V_3}{G_{Total}}$$
  
Also works if  $V_k$  is zero (less obvious).







# **Superposition**

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any voltage or current in a circuit is the sum of the effects of the sources taken one at a time.

# **Superposition**

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any voltage or current in a circuit is the sum of the effects of the sources taken one at a time.

To use superposition:

# **Superposition**

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
  Dividers
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any voltage or current in a circuit is the sum of the effects of the sources taken one at a time.

To use superposition:

- Set all the sources to zero except for the first one and find the voltage at each node
  - A zero-valued voltage source is a short circuit
  - A zero-valued current source is an open circuit
# **Superposition**

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
  Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any voltage or current in a circuit is the sum of the effects of the sources taken one at a time.

To use superposition:

- Set all the sources to zero except for the first one and find the voltage at each node
  - A zero-valued voltage source is a short circuit
  - A zero-valued current source is an open circuit
- Repeat for each of the sources and add up the results to get a formula for the voltage at each node.

# **Superposition**

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
  Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any voltage or current in a circuit is the sum of the effects of the sources taken one at a time.

To use superposition:

- Set all the sources to zero except for the first one and find the voltage at each node
  - A zero-valued voltage source is a short circuit
  - A zero-valued current source is an open circuit
- Repeat for each of the sources and add up the results to get a formula for the voltage at each node.
- Express all dependent source values in terms of node voltages and eliminate them from the formulae. A source is dependent if its value is determined by the voltages/currents elsewhere in the circuit.

Revision Lecture 1: Nodal Analysis

• Exam

- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

#### **Problem:** Find X in terms of $U_1$ and $U_2$ .



Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

#### Problem: Find X in terms of $U_1$ and $U_2$ .

• If we set  $U_2 = 0$  then the current source becomes an *open circuit* 



Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

#### Problem: Find X in terms of $U_1$ and $U_2$ .

• If we set  $U_2 = 0$  then the current source becomes an *open circuit* 





Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Problem: Find X in terms of  $U_1$  and  $U_2$ .

• If we set  $U_2 = 0$  then the current source becomes an *open circuit* and now the 3 k plays no part in the circuit.





Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Problem: Find X in terms of  $U_1$  and  $U_2$ .

• If we set  $U_2 = 0$  then the current source becomes an *open circuit* and now the 3 k plays no part in the circuit.





Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

**Problem:** Find X in terms of  $U_1$  and  $U_2$ .

• If we set  $U_2 = 0$  then the current source becomes an *open circuit* and now the 3 k plays no part in the circuit.

2 k and 1 k form a potential divider and so  $X = \frac{1 \text{ k}}{2 \text{ k}+1 \text{ k}} = \frac{1}{3}U_1$ .





Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

**Problem:** Find X in terms of  $U_1$  and  $U_2$ .

• If we set  $U_2 = 0$  then the current source becomes an *open circuit* and now the 3 k plays no part in the circuit.

2 k and 1 k form a potential divider and so  $X = \frac{1 \text{ k}}{2 \text{ k}+1 \text{ k}} = \frac{1}{3}U_1$ .

• If we set  $U_1 = 0$  then the voltage source becomes a *short circuit* 





Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

**Problem:** Find X in terms of  $U_1$  and  $U_2$ .

• If we set  $U_2 = 0$  then the current source becomes an *open circuit* and now the 3 k plays no part in the circuit.

2 k and 1 k form a potential divider and so  $X = \frac{1 \text{ k}}{2 \text{ k}+1 \text{ k}} = \frac{1}{3}U_1$ .

• If we set  $U_1 = 0$  then the voltage source becomes a *short circuit* 





Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Problem: Find X in terms of  $U_1$  and  $U_2$ .

• If we set  $U_2 = 0$  then the current source becomes an *open circuit* and now the 3 k plays no part in the circuit.

2 k and 1 k form a potential divider and so  $X = \frac{1 \text{ k}}{2 \text{ k}+1 \text{ k}} = \frac{1}{3}U_1$ .

• If we set  $U_1 = 0$  then the voltage source becomes a *short circuit* and the 2 k and 1 k are in parallel.

$$2 k || 1 k = \frac{2 k \times 1 k}{2 k + 1 k} = \frac{2}{3} k.$$





Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

**Problem:** Find X in terms of  $U_1$  and  $U_2$ .

• If we set  $U_2 = 0$  then the current source becomes an *open circuit* and now the 3 k plays no part in the circuit.

2 k and 1 k form a potential divider and so  $X = \frac{1 \text{ k}}{2 \text{ k}+1 \text{ k}} = \frac{1}{3}U_1$ .

• If we set  $U_1 = 0$  then the voltage source becomes a *short circuit* and the 2 k and 1 k are in parallel.

$$2 \text{ k} || 1 \text{ k} = \frac{2 \text{ k} \times 1 \text{ k}}{2 \text{ k} + 1 \text{ k}} = \frac{2}{3} \text{ k}.$$
  
Now  $X = \frac{2}{3}U_2$ .





Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Problem: Find X in terms of  $U_1$  and  $U_2$ .

• If we set  $U_2 = 0$  then the current source becomes an *open circuit* and now the 3 k plays no part in the circuit.

2 k and 1 k form a potential divider and so  $X = \frac{1 \text{ k}}{2 \text{ k}+1 \text{ k}} = \frac{1}{3}U_1$ .

If we set U<sub>1</sub> = 0 then the voltage source becomes a short circuit and the 2 k and 1 k are in parallel.

 $2 k || 1 k = \frac{2 k \times 1 k}{2 k + 1 k} = \frac{2}{3} k.$ Now  $X = \frac{2}{3}U_2$ .





• Combining these two gives  $X = \frac{1}{3}U_1 + \frac{2}{3}U_2$ .

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any complicated linear circuit with two terminals is exactly equivalent to either of two simpler circuits with only two components. Any measurement will give the same result on any of the three circuits.



Original

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any complicated linear circuit with two terminals is exactly equivalent to either of two simpler circuits with only two components. Any measurement will give the same result on any of the three circuits.



Original

Thévenin

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any complicated linear circuit with two terminals is exactly equivalent to either of two simpler circuits with only two components. Any measurement will give the same result on any of the three circuits.



Original

Thévenin

Norton

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any complicated linear circuit with two terminals is exactly equivalent to either of two simpler circuits with only two components. Any measurement will give the same result on any of the three circuits.



Common measurements are:

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any complicated linear circuit with two terminals is exactly equivalent to either of two simpler circuits with only two components. Any measurement will give the same result on any of the three circuits.



Common measurements are:

• Thévenin Resistance,  $R_{Th}$ : Resistance between the terminals when all sources are set to zero (same for Thévenin and Norton).

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any complicated linear circuit with two terminals is exactly equivalent to either of two simpler circuits with only two components. Any measurement will give the same result on any of the three circuits.



Common measurements are:

- Thévenin Resistance,  $R_{Th}$ : Resistance between the terminals when all sources are set to zero (same for Thévenin and Norton).
- Open circuit voltage (= voltage when drawing zero current from the terminals): =  $V_{Th} = I_{No}R_{Th}$ .

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Any complicated linear circuit with two terminals is exactly equivalent to either of two simpler circuits with only two components. Any measurement will give the same result on any of the three circuits.



Common measurements are:

- Thévenin Resistance,  $R_{Th}$ : Resistance between the terminals when all sources are set to zero (same for Thévenin and Norton).
- Open circuit voltage (= voltage when drawing zero current from the terminals): =  $V_{Th} = I_{No}R_{Th}$ .
- Short circuit current:  $= I_{No} = \frac{V_{Th}}{R_{Th}}$ .

# **Op Amps**

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- Ideal Op Amp: (a) Zero input current, (b) Infinite gain
  (b) ⇒ V<sub>+</sub> = V<sub>-</sub> provided the circuit has negative feedback.
- Negative Feedback: An increase in  $V_{out}$  causes $(V_+ V_-)$  to decrease.



# **Op Amps**

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- Ideal Op Amp: (a) Zero input current, (b) Infinite gain
  (b) ⇒ V<sub>+</sub> = V<sub>-</sub> provided the circuit has negative feedback.
- Negative Feedback: An increase in  $V_{out}$  causes $(V_+ V_-)$  to decrease. Non-inverting amplifier

$$Y = \left(1 + \frac{3}{1}\right)X$$



# **Op Amps**

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

- Ideal Op Amp: (a) Zero input current, (b) Infinite gain
  (b) ⇒ V<sub>+</sub> = V<sub>-</sub> provided the circuit has negative feedback.
- Negative Feedback: An increase in  $V_{out}$  causes $(V_+ V_-)$  to decrease. Non-inverting amplifier
  - $Y = \left(1 + \frac{3}{1}\right)X$



#### Inverting amplifier





Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Blocks are labelled with their gains and connected using adder/subtractors shown as circles. Adder inputs are marked + for add or - for subtract.



Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Blocks are labelled with their gains and connected using adder/subtractors shown as circles. Adder inputs are marked + for add or - for subtract.

$$X + U F + G + H + Y$$

To analyse:

1. Label the inputs, the outputs and the output of each adder.

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Blocks are labelled with their gains and connected using adder/subtractors shown as circles. Adder inputs are marked + for add or - for subtract.



- 1. Label the inputs, the outputs and the output of each adder.
- 2. Write down an equation for each variable:
  - U = X FGU
  - Follow signals back though the blocks until you meet a labelled node.

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Blocks are labelled with their gains and connected using adder/subtractors shown as circles. Adder inputs are marked + for add or - for subtract.

$$X + U F \bullet G \bullet H + Y$$

- 1. Label the inputs, the outputs and the output of each adder.
- 2. Write down an equation for each variable:
  - U = X FGU, Y = FU + FGHU
  - Follow signals back though the blocks until you meet a labelled node.

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Blocks are labelled with their gains and connected using adder/subtractors shown as circles. Adder inputs are marked + for add or - for subtract.



- 1. Label the inputs, the outputs and the output of each adder.
- 2. Write down an equation for each variable:
  - U = X FGU, Y = FU + FGHU
  - Follow signals back though the blocks until you meet a labelled node.
- 3. Solve the equations (eliminate intermediate node variables):
  - U(1+FG) = X

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Blocks are labelled with their gains and connected using adder/subtractors shown as circles. Adder inputs are marked + for add or - for subtract.

$$X + U F \bullet G \bullet H + Y$$

- 1. Label the inputs, the outputs and the output of each adder.
- 2. Write down an equation for each variable:
  - U = X FGU, Y = FU + FGHU
  - Follow signals back though the blocks until you meet a labelled node.
- 3. Solve the equations (eliminate intermediate node variables):

• 
$$U(1+FG) = X \Rightarrow U = \frac{X}{1+FG}$$

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Blocks are labelled with their gains and connected using adder/subtractors shown as circles. Adder inputs are marked + for add or - for subtract.

$$X + U F \bullet G \bullet H + Y$$

- 1. Label the inputs, the outputs and the output of each adder.
- 2. Write down an equation for each variable:
  - U = X FGU, Y = FU + FGHU
  - Follow signals back though the blocks until you meet a labelled node.
- 3. Solve the equations (eliminate intermediate node variables):
  - $U(1+FG) = X \Rightarrow U = \frac{X}{1+FG}$
  - Y = (1 + GH)FU

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Blocks are labelled with their gains and connected using adder/subtractors shown as circles. Adder inputs are marked + for add or - for subtract.

$$X + U F \bullet G \bullet H + Y$$

- 1. Label the inputs, the outputs and the output of each adder.
- 2. Write down an equation for each variable:
  - U = X FGU, Y = FU + FGHU
  - Follow signals back though the blocks until you meet a labelled node.
- 3. Solve the equations (eliminate intermediate node variables):
  - $U(1+FG) = X \Rightarrow U = \frac{X}{1+FG}$
  - $Y = (1 + GH)FU = \frac{(1+GH)F}{1+FG}X$

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Blocks are labelled with their gains and connected using adder/subtractors shown as circles. Adder inputs are marked + for add or - for subtract.

$$\begin{array}{c|c} X + & U & F \\ \hline & & & & \\ \hline & & \\ \hline & & & \\ \hline \end{array} \\ \hline & & & \\ \hline \end{array} \\ \hline \\ \hline & & & \\ \hline \end{array} \end{array}$$

To analyse:

- 1. Label the inputs, the outputs and the output of each adder.
- 2. Write down an equation for each variable:
  - U = X FGU, Y = FU + FGHU
  - Follow signals back though the blocks until you meet a labelled node.
- 3. Solve the equations (eliminate intermediate node variables):
  - $U(1+FG) = X \Rightarrow U = \frac{X}{1+FG}$
  - $Y = (1 + GH)FU = \frac{(1+GH)F}{1+FG}X$

[Note: "Wires" carry information not current: KCL not valid]

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Each diode in a circuit is in one of two modes; each has an equality condition and an inequality condition:

- Off:  $I_D = 0$ ,  $V_D < 0.7$
- On:  $V_D = 0.7$ ,  $I_D > 0$
- (a) Guess the mode
- (b) Do nodal analysis assuming the equality condition
- (c) Check the inequality condition. If the inequality condition fails, you made the wrong guess.

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Each diode in a circuit is in one of two modes; each has an equality condition and an inequality condition:

- Off:  $I_D = 0$ ,  $V_D < 0.7$
- On:  $V_D = 0.7$ ,  $I_D > 0$
- (a) Guess the mode
- (b) Do nodal analysis assuming the equality condition
- (c) Check the inequality condition. If the inequality condition fails, you made the wrong guess.
  - Assume Diode Off

X = 5 + 2 = 7



Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Each diode in a circuit is in one of two modes; each has an equality condition and an inequality condition:

- Off:  $I_D = 0$ ,  $V_D < 0.7$
- On:  $V_D = 0.7$ ,  $I_D > 0$
- (a) Guess the mode
- (b) Do nodal analysis assuming the equality condition
- (c) Check the inequality condition. If the inequality condition fails, you made the wrong guess.
  - Assume Diode Off

X = 5 + 2 = 7 $V_D = 2$ 



Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Each diode in a circuit is in one of two modes; each has an equality condition and an inequality condition:

- Off:  $I_D = 0$ ,  $V_D < 0.7$
- On:  $V_D = 0.7$ ,  $I_D > 0$
- (a) Guess the mode
- (b) Do nodal analysis assuming the equality condition
- (c) Check the inequality condition. If the inequality condition fails, you made the wrong guess.
  - Assume Diode Off

X = 5 + 2 = 7 $V_D = 2$  Fail:  $V_D > 0.7$ 


## **Diodes**

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Each diode in a circuit is in one of two modes; each has an equality condition and an inequality condition:

- Off:  $I_D = 0, V_D < 0.7$
- On:  $V_D = 0.7$ ,  $I_D > 0$
- (a) Guess the mode
- (b) Do nodal analysis assuming the equality condition
- (c) Check the inequality condition. If the inequality condition fails, you made the wrong guess.
  - Assume Diode Off

X = 5 + 2 = 7 $V_D = 2$  Fail:  $V_D > 0.7$ 

Assume Diode On

X = 5 + 0.7 = 5.7



## **Diodes**

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Each diode in a circuit is in one of two modes; each has an equality condition and an inequality condition:

- Off:  $I_D = 0, V_D < 0.7$
- On:  $V_D = 0.7, I_D > 0$
- (a) Guess the mode
- (b) Do nodal analysis assuming the equality condition
- (c) Check the inequality condition. If the inequality condition fails, you made the wrong guess.
  - Assume Diode Off

X = 5 + 2 = 7 $V_D = 2$  Fail:  $V_D > 0.7$ 

Assume Diode On

$$X = 5 + 0.7 = 5.7$$
$$I_D + \frac{0.7}{1 \,\mathrm{k}} = 2 \,\mathrm{mA}$$



Revision Lecture 1 - 13 / 13

## **Diodes**

Revision Lecture 1: Nodal Analysis

- Exam
- Basic Concepts
- Ohm's Law
- Nodal Analysis
- Nodal Analysis Example
- Voltage and Current
- Dividers
- Superposition
- Superposition Example
- Thévenin and Norton
- Op Amps
- Block Diagrams
- Diodes

Each diode in a circuit is in one of two modes; each has an equality condition and an inequality condition:

- Off:  $I_D = 0, V_D < 0.7$
- On:  $V_D = 0.7$ ,  $I_D > 0$
- (a) Guess the mode
- (b) Do nodal analysis assuming the equality condition
- (c) Check the inequality condition. If the inequality condition fails, you made the wrong guess.
  - Assume Diode Off

X = 5 + 2 = 7 $V_D = 2$  Fail:  $V_D > 0.7$ 

Assume Diode On

$$X = 5 + 0.7 = 5.7$$
  
 $I_D + \frac{0.7}{1 \text{ k}} = 2 \text{ mA} \text{ OK: } I_D > 0$ 

