

Revision Lecture 4:

▷ **Transients & Lines**

**Transients: Basic
Ideas**

Steady States

**Determining Time
Constant**

**Determining
Transient Amplitude**

**Transmission Lines
Basics**

Reflections

**Sinewaves and
Phasors**

Standing Waves

Revision Lecture 4: Transients & Lines

Transients: Basic Ideas

Revision Lecture 4: Transients & Lines

Transients: Basic Ideas

Steady States

Determining Time Constant

Determining Transient Amplitude

Transmission Lines Basics

Reflections

Sinewaves and Phasors

Standing Waves

- Transients happen in response to a **sudden change**
 - Input voltage/current abruptly changes its magnitude, frequency or phase
 - A switch alters the circuit
- 1st order circuits only: one capacitor/inductor
- All voltage/current waveforms are: **Steady State + Transient**
 - **Steady States**: find with nodal analysis or transfer function
 - ▷ Note: **Steady State** is not the same as **DC Level**
 - ▷ Need steady states before **and** after the sudden change
 - **Transient**: Always a negative exponential: $Ae^{-\frac{t}{\tau}}$
 - ▷ Time Constant: $\tau = RC$ or $\frac{L}{R}$ where R is the Thévenin resistance at the terminals of C or L
 - ▷ Find transient amplitude, A , from continuity since V_C or I_L cannot change instantly.
 - ▷ τ and A can also be found from the transfer function.

Steady States

A **steady-state** output assumes the input frequency, phase and amplitude are constant forever. You need to determine **two** $y_{SS}(t)$ steady state outputs: one for **before** the transient ($t < 0$) and one **after** ($t \geq 0$). At $t = 0$, $y_{SS}(0-)$ means the first one and $y_{SS}(0+)$ means the second.

Method 1: Nodal analysis

Input voltage is DC ($\omega = 0$)

$$\Rightarrow Z_L = 0 \text{ (for capacitor: } Z_C = \infty)$$

So L acts as a short circuit

Potential divider: $y_{SS} = \frac{1}{2}x$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Method 2: Transfer function



$$\frac{Y}{X}(j\omega) = \frac{R+j\omega L}{2R+j\omega L}$$

$$\text{set } \omega = 0: \frac{Y}{X}(0) = \frac{1}{2}$$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Sinusoidal input \Rightarrow **Sinusoidal steady state** \Rightarrow use phasors.

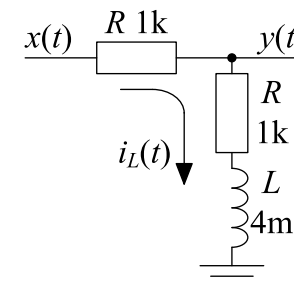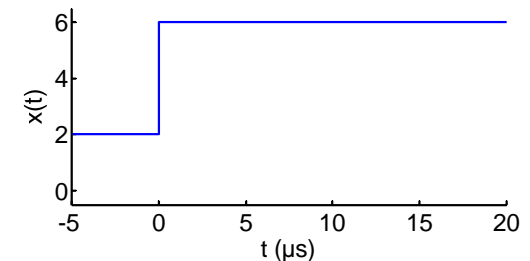Then convert phasors to time waveforms to calculate the actual output voltages $y_{SS}(0-)$ and $y_{SS}(0+)$ at $t = 0$.





Determining Time Constant

Method 1: Thévenin

- (a) Remove the capacitor/inductor
- (b) Set all sources to zero (including the input voltage source). Leave output unconnected.
- (c) Calculate the Thévenin resistance between the capacitor/inductor terminals:

$$R_{Th} = 8R \parallel 4R \parallel (6R + 2R) = 2R$$

- (d) Time constant: $= R_{Th}C$ or $\frac{L}{R_{Th}}$
 $\tau = R_{Th}C = 2RC$

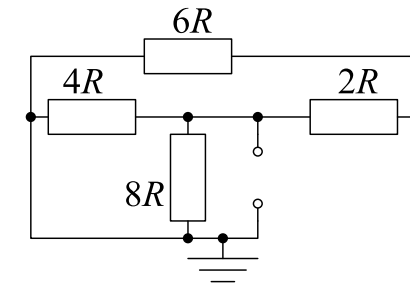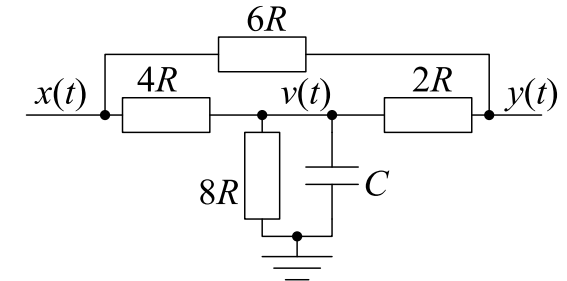

Method 2: Transfer function

- (a) Calculate transfer function using nodal analysis

$$\text{KCL @ } V: \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ } Y: \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Eliminate } V \text{ to get transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

- (b) Time Constant $= \frac{1}{\text{Denominator corner frequency}}$

$$\omega_d = \frac{16}{32RC} \Rightarrow \tau = \frac{1}{\omega_d} = 2RC$$

Determining Transient Amplitude

Revision Lecture 4:
Transients & Lines

Transients: Basic
Ideas

Steady States

Determining Time
Constant

Determining
Transient

▷ Amplitude

Transmission Lines
Basics

Reflections

Sinewaves and
Phasors

Standing Waves

After an input change at $t = 0$, $y(t) = y_{SS}(t) + Ae^{-\frac{t}{\tau}}$.

$\Rightarrow y(0+) = y_{SS}(0+) + A \Rightarrow A = y(0+) - y_{SS}(0+)$

Method: (a) calculate true output $y(0+)$, (b) subtract $y_{SS}(0+)$ to get A




(i) Version 1: v_C or i_L continuity

$x(0-) = 2 \Rightarrow i_L(0-) = 1 \text{ mA}$

Continuity $\Rightarrow i_L(0+) = i_L(0-)$

Replace L with a 1 mA current source

$y(0+) = x(0+) - iR = 6 - 1 = 5$

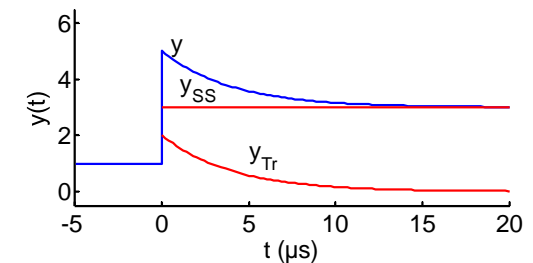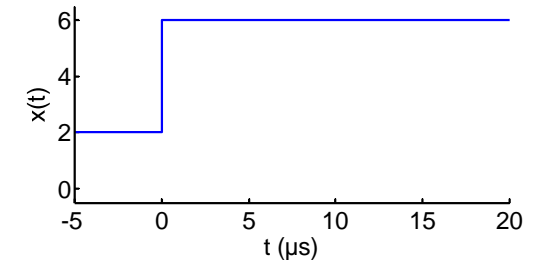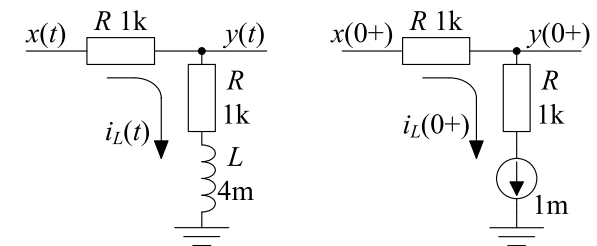

(i) Version 2: Transfer function

$$H(j\omega) = \frac{Y}{X}(j\omega) = \frac{R+j\omega L}{2R+j\omega L}$$

Input step, $\Delta x = x(0+) - x(0-) = +4$

$y(0+) = y(0-) + H(j\infty) \times \Delta x$

$$= 1 + 1 \times 4 = 5$$

(ii) $A = y(0+) - y_{SS}(0+) = 5 - 3 = 2$

(iii) $y(t) = y_{SS}(t) + Ae^{-t/\tau}$
 $= 3 + 2e^{-t/2\mu}$

Transmission Lines Basics

- Revision Lecture 4:
Transients & Lines


- Transients: Basic Ideas
- Steady States
- Determining Time Constant
- Determining Transient Amplitude
- Transmission Lines
 - ▷ Basics
 - Reflections
 - Sinewaves and Phasors
 - Standing Waves

Transmission Line: constant L_0 and C_0 : inductance/capacitance per metre.


Forward wave travels along the line: $f_x(t) = f_0 \left(t - \frac{x}{u} \right)$.

Velocity $u = \sqrt{\frac{1}{L_0 C_0}} \approx \frac{1}{2}c = 15 \text{ cm/ns}$

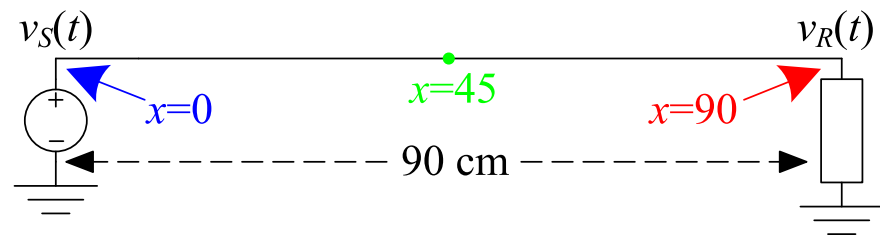$f_x(t)$ equals $f_0(t)$ but delayed by $\frac{x}{u}$.



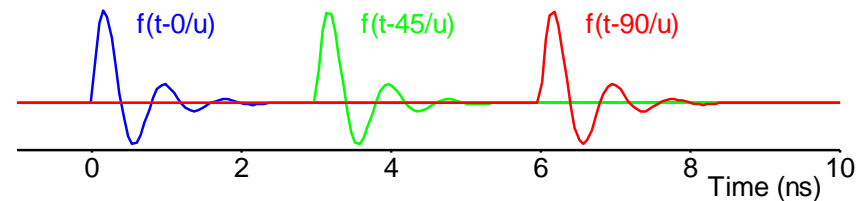Knowing $f_x(t)$ for $x = x_0$ fixes it for all other x .



Backward wave: $g_x(t)$ is the same but travelling \leftarrow : $g_x(t) = g_0 \left(t + \frac{x}{u} \right)$.


Voltage and current are: $v_x = f_x + g_x$ and $i_x = \frac{f_x - g_x}{Z_0}$ where i_x is positive in the $+x$ direction (\rightarrow) and $Z_0 = \sqrt{\frac{L_0}{C_0}}$

Waveforms of f_x and g_x are determined by the connections at both ends.

Reflections

- Revision Lecture 4:
- Transients & Lines

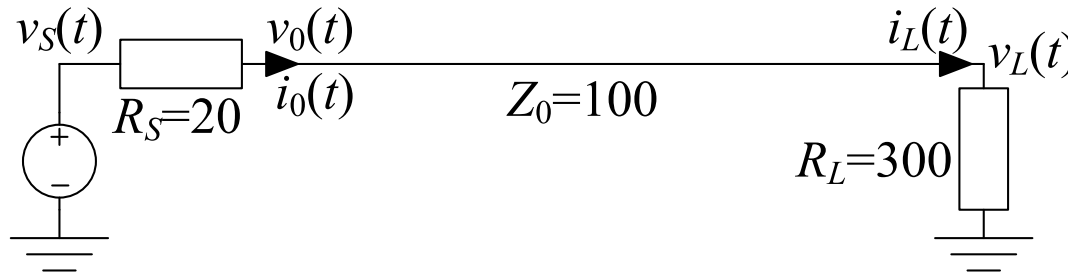- Transients: Basic Ideas
- Steady States
- Determining Time Constant
- Determining Transient Amplitude
- Transmission Lines Basics
- ▷ Reflections
- Sinewaves and Phasors
- Standing Waves



$$v_x = f_x + g_x$$

$$i_x = \frac{f_x - g_x}{Z_0}$$

At $x = L$, Ohm's law $\Rightarrow \frac{v_L(t)}{i_L(t)} = R_L \Rightarrow g_L(t) = \frac{R_L - Z_0}{R_L + Z_0} \times f_L(t)$.

Reflection coefficient: $\rho_L = \frac{g_L(t)}{f_L(t)} = \frac{R_L - Z_0}{R_L + Z_0}$

$\rho_L \in [-1, +1]$ and increases with R_L

Knowing $f_x(t)$ for $x = x_0$ now tells you $f_x, g_x, v_x, i_x \forall x$

At $x = 0$: $f_0(t) = \frac{Z_0}{R_S + Z_0} v_S(t) + \frac{R_S - Z_0}{R_S + Z_0} g_0(t) = \tau_0 v_S(t) + \rho_0 g_0(t)$

Wave bounces back and forth getting smaller with each reflection:

$$v_S(t) \xrightarrow{\times \tau_0} f_0(t) \xrightarrow{\times \rho_L} g_0(t + \frac{2L}{u}) \xrightarrow{\times \rho_0} f_0(t + \frac{2L}{u}) \xrightarrow{\times \rho_L} g_0(t + \frac{4L}{u}) \xrightarrow{\times \rho_0} \dots$$

Infinite sum:

$$f_0(t) = \tau_0 v_S(t) + \tau_0 \rho_L \rho_0 v_S(t - \frac{2L}{u}) + \dots = \sum_{i=0}^{\infty} \tau_0 \rho_L^i \rho_0^i v_S(t - \frac{2Li}{u})$$


Sinewaves and Phasors

- Revision Lecture 4: Transients & Lines
- Transients: Basic Ideas
- Steady States
- Determining Time Constant
- Determining Transient Amplitude
- Transmission Lines Basics
- Reflections
 - Sinewaves and Phasors
- Standing Waves

Sinewaves are easier because:

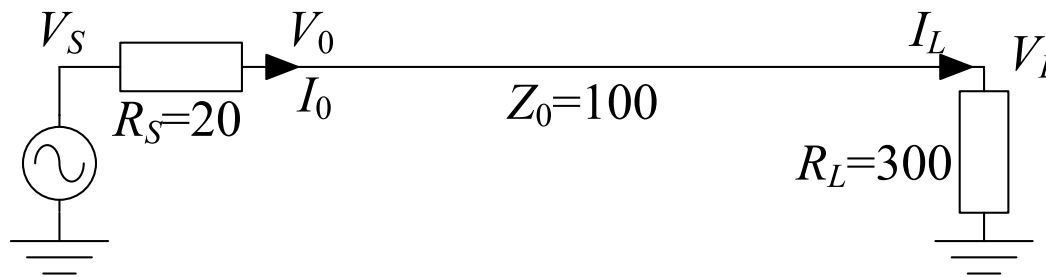1. Use phasors to eliminate t : $f_0(t) = A \cos(\omega t + \phi) \Leftrightarrow F_0 = Ae^{j\phi}$
2. Time delays are just phase shifts:
 $f_x(t) = A \cos(\omega(t - \frac{x}{u}) + \phi) \Leftrightarrow F_x = Ae^{j(\phi - \frac{\omega}{u}x)} = F_0 e^{-jkx}$
 k is the **wavenumber**: radians per metre (c.f. ω in rad per second)

As before: $V_x = F_x + G_x$ and $I_x = \frac{F_x - G_x}{Z_0}$



As before:

$$G_L = \rho_L F_L$$

$$F_0 = \tau_0 V_S + \rho_0 G_0$$

But $G_0 = F_0 \rho_L e^{-2jkL}$: roundtrip delay of $\frac{2L}{u}$ + reflection at $x = L$.
 Substituting for G_0 in source end equation: $F_0 = \tau_0 V_S + \rho_0 F_0 \rho_L e^{-2jkL}$
 $\Rightarrow F_0 = \frac{\tau_0}{1 - \rho_0 \rho_L \exp(-2jkL)} V_S$ so no infinite sums needed ☺

Standing Waves

Revision Lecture 4: Transients & Lines

Transients: Basic Ideas

Steady States

Determining Time Constant

Determining Transient Amplitude

Transmission Lines Basics

Reflections

Sinewaves and Phasors


▷ Standing Waves

Standing waves arise whenever a wave meets its reflection:

at places where the two waves are **in phase** their amplitudes add but where they are **anti-phase** their amplitudes subtract.

At any point x ,
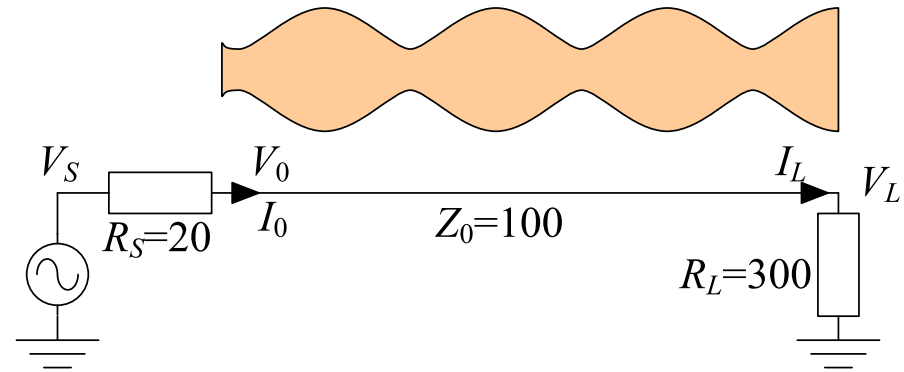
$$\text{delay of } \frac{x}{u} \Rightarrow F_x = F_0 e^{-jkx}$$



Backward wave: $G_x = \rho_L F_x e^{-2jk(L-x)}$: reflection + delay of $2 \frac{L-x}{u}$

Voltage at x : $V_x = F_x + G_x = F_0 e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Voltage Magnitude : $|V_x| = |F_0| |1 + \rho_L e^{-2jk(L-x)}|$: depends on x

If $\rho_L \geq 0$, **max magnitude** is $(1 + \rho_L) |F_0|$ whenever $e^{-2jk(L-x)} = +1$
 $\Rightarrow x = L$ or $x = L - \frac{\pi}{k}$ or $x = L - \frac{2\pi}{k}$ or ...

Min magnitude is $(1 - \rho_L) |F_0|$ whenever $e^{-2jk(L-x)} = -1$
 $\Rightarrow x = L - \frac{\pi}{2k}$ or $x = L - \frac{3\pi}{2k}$ or $x = L - \frac{5\pi}{2k}$ or ...