

**Revision Lecture 1:
Nodal Analysis &
Fre-**

▷ quency Responses

Exam

Nodal Analysis

Op Amps

Block Diagrams

Diodes

Reactive Components

Phasors

**Plotting Frequency
Responses**

LF and HF

Asymptotes

**Corner frequencies
(linear factors)**

**Sketching Magnitude
Responses (linear
factors)**

Filters

Resonance

Revision Lecture 1: Nodal Analysis & Frequency Responses

Exam Format

Question 1 (40%): eight short parts covering the whole syllabus.

Questions 2 and 3: single topic questions (answer both)

Syllabus

Does include: Everything in the notes.

Does not include: Two-port parameters (2008:1j), Gaussian elimination (2007:2c), Application areas (2008:3d), Nullators and Norators (2008:4c), Small-signal component models (2008:4e), Gain-bandwidth product (2006:4c), Zener Diodes (2008/9 syllabus), Non-ideal models of L, C and transformer (2011/12 syllabus), Transmission lines VSWR and crank diagram (2011/12 syllabus).

Nodal Analysis

Revision Lecture 1: Nodal Analysis & Frequency Responses

Exam

▷ Nodal Analysis

Op Amps

Block Diagrams

Diodes

Reactive Components

Phasors

Plotting Frequency Responses

LF and HF

Asymptotes

Corner frequencies (linear factors)

Sketching Magnitude Responses (linear factors)

Filters



Resonance

- (1) Pick reference node.
- (2) Label nodes: 8, X and $X + 2$ since it is joined to X via a voltage source.
- (3) Write KCL equations but count all the nodes connected via floating voltage sources as a single “super-node” giving one equation

$$\frac{X-8}{1} + \frac{X}{2} + \frac{(X+2)-0}{3} = 0$$

Ohm's law always involves the difference between the voltages at **either end of a resistor**. (Obvious but easily forgotten)

- (4) Solve the equations: $X = 4$

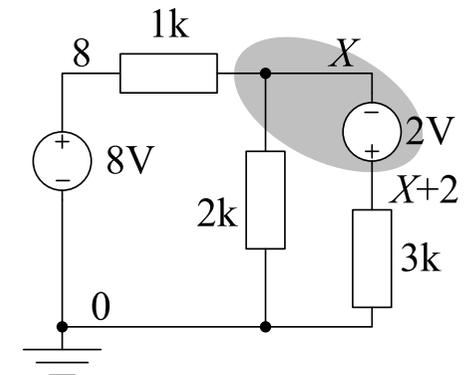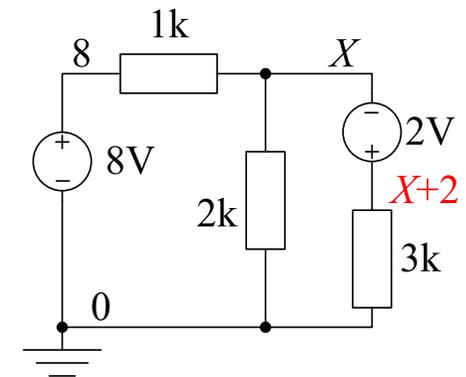

Op Amps

Revision Lecture 1:
Nodal Analysis &
Frequency Responses

Exam

Nodal Analysis

▷ Op Amps

Block Diagrams

Diodes

Reactive Components

Phasors

Plotting Frequency
Responses

LF and HF

Asymptotes

Corner frequencies
(linear factors)

Sketching Magnitude
Responses (linear
factors)


Filters

Resonance

- **Ideal Op Amp:** (a) Zero input current, (b) Infinite gain
(b) $\Rightarrow V_+ = V_-$ provided the circuit has **negative feedback**.
- **Negative Feedback:** An increase in V_{out} makes $(V_+ - V_-)$ decrease.


Non-inverting amplifier

$$Y = \left(1 + \frac{3}{1}\right) X$$

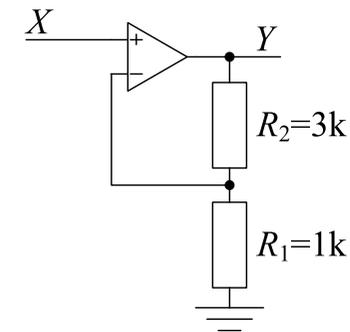

Inverting amplifier
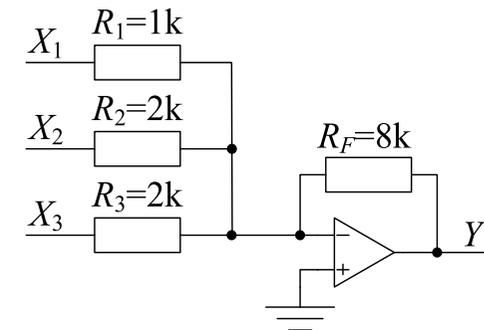
$$Y = \frac{-8}{1} X_1 + \frac{-8}{2} X_2 + \frac{-8}{2} X_3$$



Nodal Analysis: Use two separate KCL equations at V_+ and V_- .

Do not do KCL at V_{out} except to find the op-amp output current.

Block Diagrams

Revision Lecture 1:
Nodal Analysis &
Frequency Responses

Exam

Nodal Analysis

Op Amps

▷ Block Diagrams

Diodes

Reactive Components

Phasors

Plotting Frequency
Responses

LF and HF

Asymptotes


Corner frequencies
(linear factors)

Sketching Magnitude
Responses (linear
factors)

Filters

Resonance

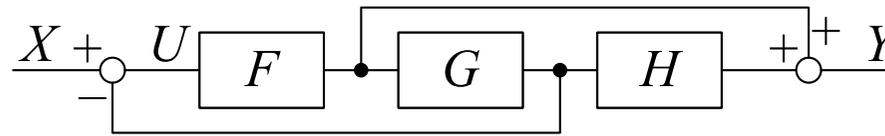Blocks are labelled with their gains and connected using adder/subtractors shown as circles. Adder inputs are marked + for add or – for subtract.



To analyse:

1. Label the inputs, the outputs and the output of each adder.

2. Write down an equation for each variable:

- $U = X - FGU, \quad Y = FU + FGHU$
- Follow signals back through the blocks until you meet a labelled node.

3. Solve the equations (eliminate intermediate node variables):

- $U(1 + FG) = X \quad \Rightarrow \quad U = \frac{X}{1+FG}$
- $Y = (1 + GH)FU = \frac{(1+GH)F}{1+FG} X$

[Note: “Wires” carry information not current: KCL not valid]

Diodes

Revision Lecture 1: Nodal Analysis & Frequency Responses

Exam

Nodal Analysis

Op Amps

Block Diagrams

▷ Diodes

Reactive Components

Phasors

Plotting Frequency Responses

LF and HF

Asymptotes

Corner frequencies (linear factors)

Sketching Magnitude Responses (linear factors)

Filters

Resonance

Each diode in a circuit is in one of two modes; each has an **equality** condition and an **inequality** condition:

- Off: $I_D = 0, V_D < 0.7 \Rightarrow$ Diode = open circuit
- On: $V_D = 0.7, I_D > 0 \Rightarrow$ Diode = 0.7 V voltage source

- (a) Guess the mode
- (b) Do nodal analysis assuming the equality condition
- (c) Check the inequality condition. If the inequality condition fails, you made the wrong guess.

- Assume Diode Off


$$X = 5 + 2 = 7$$

$$V_D = 2 \quad \text{Fail: } V_D > 0.7$$

- Assume Diode On

$$X = 5 + 0.7 = 5.7$$
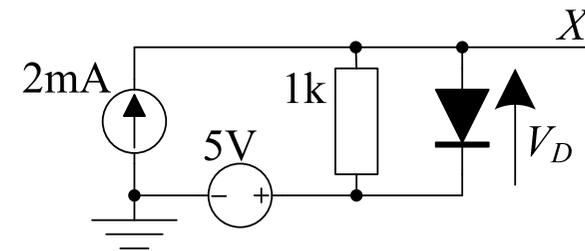
$$I_D + \frac{0.7}{1\text{k}} = 2\text{ mA} \quad \text{OK: } I_D > 0$$



Reactive Components

Revision Lecture 1:
Nodal Analysis &
Frequency Responses

Exam

Nodal Analysis

Op Amps

Block Diagrams

Diodes

Reactive

▷ Components

Phasors

Plotting Frequency
Responses

LF and HF

Asymptotes

Corner frequencies
(linear factors)

Sketching Magnitude
Responses (linear
factors)

Filters

Resonance

- Impedances: $R, j\omega L, \frac{1}{j\omega C} = \frac{-j}{\omega C}$.
 - Admittances: $\frac{1}{R}, \frac{1}{j\omega L} = \frac{-j}{\omega L}, j\omega C$
- In a capacitor or inductor, the Current and Voltage are 90° apart :
 - CIVIL: Capacitor - I leads V ; Inductor - I lags V
- Average current (or DC current) through a capacitor is always zero
- Average voltage across an inductor is always zero
- Average power absorbed by a capacitor or inductor is always zero

Phasors

Revision Lecture 1:
Nodal Analysis &
Frequency Responses

Exam

Nodal Analysis

Op Amps

Block Diagrams

Diodes

Reactive Components

▷ Phasors

Plotting Frequency
Responses

LF and HF

Asymptotes

Corner frequencies
(linear factors)

Sketching Magnitude
Responses (linear
factors)

Filters

Resonance

A phasor represents a **time-varying sinusoidal waveform** by a **fixed complex number**.

Waveform

$$x(t) = F \cos \omega t - G \sin \omega t$$

$$x(t) = A \cos(\omega t + \theta)$$

$$\max(x(t)) = A$$


Phasor

$$X = F + jG$$

$$X = Ae^{j\theta} = A\angle\theta$$

$$|X| = A$$

[Note minus sign]

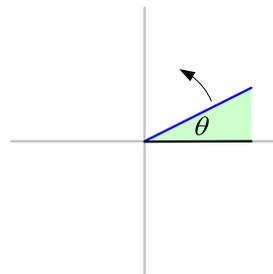

$x(t)$ is the projection of a rotating rod onto the real (horizontal) axis.

$X = F + jG$ is its starting position at $t = 0$.

$$\text{RMS Phasor: } \tilde{V} = \frac{1}{\sqrt{2}}V \quad \Rightarrow \quad |\tilde{V}|^2 = \langle x^2(t) \rangle$$

$$\text{Complex Power: } \tilde{V}\tilde{I}^* = |\tilde{I}|^2 Z = \frac{|\tilde{V}|^2}{Z^*} = P + jQ$$

P is average power (Watts), Q is reactive power (VARs)




Plotting Frequency Responses

- Revision Lecture 1: Nodal Analysis & Frequency Responses
- Exam
- Nodal Analysis
- Op Amps
- Block Diagrams
- Diodes
- Reactive Components
- Phasors
 - Plotting Frequency Responses
- LF and HF Asymptotes
- Corner frequencies (linear factors)
- Sketching Magnitude Responses (linear factors)
- Filters
- Resonance

- Plot the magnitude response and phase response as separate graphs. Use **log scale** for frequency and magnitude and **linear scale** for phase: this gives graphs that can be approximated by straight line segments.
- If $\frac{V_2}{V_1} = A(j\omega)^k = A \times j^k \times \omega^k$ (where A is real)
 - magnitude is a **straight line with gradient k** :

$$\log \left| \frac{V_2}{V_1} \right| = \log |A| + k \log \omega$$
 - phase is a **constant $k \times \frac{\pi}{2}$** ($+\pi$ if $A < 0$):

$$\angle \left(\frac{V_2}{V_1} \right) = \angle A + k \angle j = \angle A + k \frac{\pi}{2}$$
- Measure magnitude response using **decibels** = $20 \log_{10} \left| \frac{V_2}{V_1} \right|$. A gradient of k on log axes is equivalent to $20k$ dB/decade ($\times 10$ in frequency) or $6k$ dB/octave ($\times 2$ in frequency).

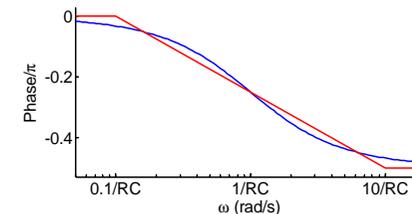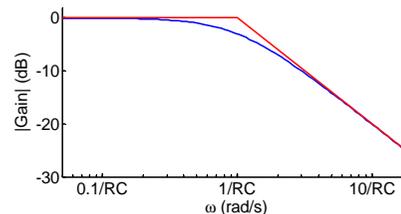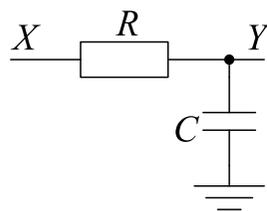

$$\frac{Y}{X} = \frac{1}{R + \frac{1}{j\omega C}} = \frac{1}{j\omega RC + 1} = \frac{1}{\frac{j\omega}{\omega_c} + 1} \quad \text{where } \omega_c = \frac{1}{RC}$$

LF and HF Asymptotes

Revision Lecture 1: Nodal Analysis & Frequency Responses

Exam

Nodal Analysis

Op Amps

Block Diagrams

Diodes

Reactive Components

Phasors

Plotting Frequency Responses

LF and HF

▷ Asymptotes

Corner frequencies (linear factors)


Sketching Magnitude Responses (linear factors)

Filters


Resonance

- Frequency response is always a ratio of two polynomials in $j\omega$ with real coefficients that depend on the component values.
 - The terms with the **lowest** power of $j\omega$ on top and bottom gives the **low-frequency** asymptote
 - The terms with the **highest** power of $j\omega$ on top and bottom gives the **high-frequency** asymptote.
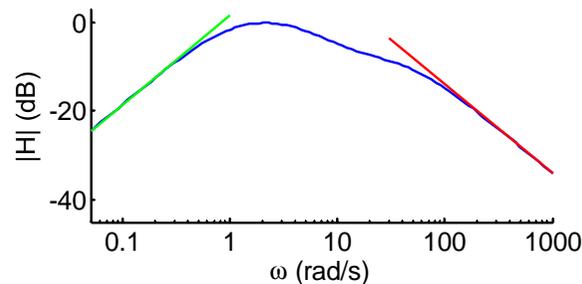
$$\text{Example: } H(j\omega) = \frac{60(j\omega)^2 + 720(j\omega)}{3(j\omega)^3 + 165(j\omega)^2 + 762(j\omega) + 600}$$


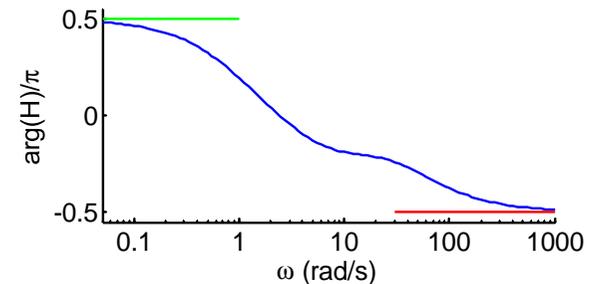
$$\text{LF: } H(j\omega) \simeq 1.2j\omega$$
$$\text{HF: } H(j\omega) \simeq 20(j\omega)^{-1}$$



Corner frequencies (linear factors)

Revision Lecture 1: Nodal Analysis & Frequency Responses

Exam

Nodal Analysis

Op Amps

Block Diagrams

Diodes

Reactive Components

Phasors

Plotting Frequency Responses

LF and HF

Asymptotes

▷ Corner frequencies (linear factors)

Sketching Magnitude Responses (linear factors)

Filters

Resonance

- We can factorize the numerator and denominator into linear terms of the form $(aj\omega + b) \simeq \begin{cases} b & \omega < \left| \frac{b}{a} \right| \\ aj\omega & \omega > \left| \frac{b}{a} \right| \end{cases}$.
- At the corner frequency, $\omega_c = \left| \frac{b}{a} \right|$, the slope of the magnitude response changes by ± 1 (± 20 dB/decade) because the linear term introduces another factor of ω into the numerator or denominator for $\omega > \omega_c$.
- The phase changes by $\pm \frac{\pi}{2}$ because the linear term introduces another factor of j into the numerator or denominator for $\omega > \omega_c$.
 - The phase change is **gradual** and takes place over the range $0.1\omega_c$ to $10\omega_c$ ($\pm \frac{\pi}{2}$ spread over two decades in ω).
- When a and b are real and positive, it is often convenient to write $(aj\omega + b) = b \left(\frac{j\omega}{\omega_c} + 1 \right)$.
- The **corner frequencies** are the absolute values of the roots of the numerator and denominator polynomials (values of $j\omega$).

Sketching Magnitude Responses (linear factors)

Revision Lecture 1: Nodal Analysis & Frequency Responses

Exam

Nodal Analysis

Op Amps

Block Diagrams

Diodes

Reactive Components

Phasors

Plotting Frequency Responses

LF and HF Asymptotes

Corner frequencies (linear factors)

Sketching Magnitude Responses (linear factors)

Filters

Resonance

1. Find corner frequencies: (a) factorize the numerator/denominator polynomials or (b) find their roots
2. Find LF and HF asymptotes. $A(j\omega)^k$ has a slope of k ; substitute $\omega = \omega_c$ to get the response at first/last corner frequency.
3. At a corner frequency, the gradient of the magnitude response changes by ± 1 (± 20 dB/decade). $+$ for numerator (top line) and $-$ for denominator (bottom line).
4. $|H(j\omega_2)| = \left(\frac{\omega_2}{\omega_1}\right)^k |H(j\omega_1)|$ if the gradient between them is k .


$$H(j\omega) = 1.2 \frac{j\omega \left(\frac{j\omega}{12} + 1\right)}{\left(\frac{j\omega}{1} + 1\right) \left(\frac{j\omega}{4} + 1\right) \left(\frac{j\omega}{50} + 1\right)}$$

$$\text{LF: } 1.2j\omega \Rightarrow |H(j1)| = 1.2 \text{ (1.6 dB)}$$

$$|H(j4)| = \left(\frac{4}{1}\right)^0 \times 1.2 = 1.2$$

$$|H(j12)| = \left(\frac{12}{4}\right)^{-1} \times 1.2 = 0.4$$

$$|H(j50)| = \left(\frac{50}{12}\right)^0 \times 0.4 = 0.4 \text{ (-8 dB)}. \text{ As a check: HF: } 20(j\omega)^{-1}$$

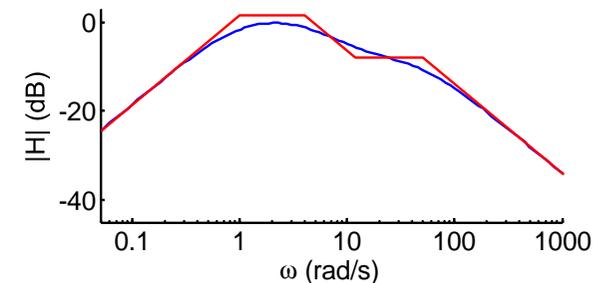

[Sketching Responses (linear factors): Summary]

LF and HF asymptotes

The LF and HF asymptotes give you both the *magnitude* and *phase* at very low and very high frequencies. The LF asymptote is found by taking the terms with the lowest power of ω in numerator and denominator; the HF asymptote is found by taking the terms with the highest power of ω .

Magnitude response

The corner frequency for a linear factor $(aj\omega + b)$ is at $\omega_c = \left| \frac{b}{a} \right|$. At each corner frequency, the slope of the magnitude response changes by ± 6 dB/octave ($= \pm 20$ dB/decade). The change is +ve for numerator corner frequencies and -ve for denominator corner frequencies. An octave is a factor of 2 in frequency and a decade is a factor of 10 in frequency. The number of decades between ω_1 and ω_2 is given by $\log_{10} \frac{\omega_2}{\omega_1}$.

Phase Response

For each corner frequency, ω_c , the slope of the phase response changes *twice*: once at $0.1\omega_c$ and once, in the opposite direction, at $10\omega_c$. The change in slope is always $\pm 0.25\pi$ rad/decade. If a and b have the same sign (normal case), then the first slope change (at $0.1\omega_c$) is in the same direction as that of the magnitude response (+ve for numerator and -ve for denominator); if a and b have opposite signs (rare), then the sign of the slope change is reversed. The second slope change (at $10\omega_c$) always has the opposite sign from the first.

Filters

Revision Lecture 1: Nodal Analysis & Frequency Responses

Exam

Nodal Analysis

Op Amps

Block Diagrams

Diodes

Reactive Components

Phasors

Plotting Frequency Responses

LF and HF

Asymptotes



Corner frequencies (linear factors)

Sketching Magnitude Responses (linear factors)

▷ Filters

Resonance

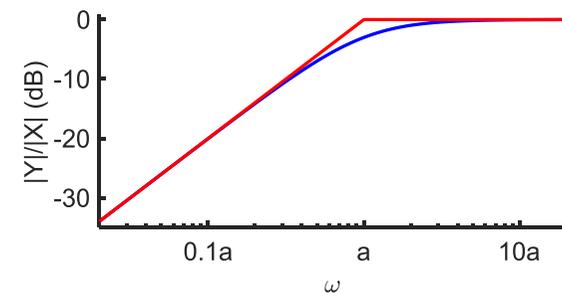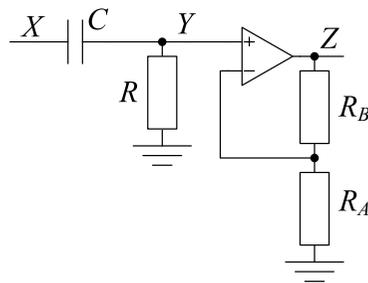- Filter: a circuit designed to amplify some frequencies and/or attenuate others. Very widely used.
- The **order** of the filter is the highest power of $j\omega$ in the denominator of the frequency response.
- Often use op-amps to provide a low impedance output.



$$\frac{Y}{X} = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{j\omega RC + 1} = \frac{j\omega RC}{\frac{j\omega}{a} + 1}$$

$$\frac{Z}{X} = \frac{Z}{Y} \times \frac{Y}{X} = \left(1 + \frac{R_B}{R_A}\right) \times \frac{j\omega RC}{\frac{j\omega}{a} + 1}$$

Resonance


- Resonant circuits have quadratic factors that cannot be factorized
 - $H(j\omega) = a(j\omega)^2 + bj\omega + c = c \left(\left(\frac{j\omega}{\omega_0} \right)^2 + 2\zeta \left(\frac{j\omega}{\omega_0} \right) + 1 \right)$
 - Corner frequency:** $\omega_0 = \sqrt{\frac{c}{a}}$ determines the horizontal position
 - Damping Factor:** $\zeta = \frac{b\omega_0}{2c} = \frac{b}{\sqrt{4ac}}$ determines the response shape
 - Equivalently **Quality Factor:** $Q \triangleq \frac{\omega \times \text{Average Stored Energy}}{\text{Average Power Dissipation}} \approx \frac{1}{2\zeta} = \frac{c}{b\omega_0}$
- At $\omega = \omega_0$, outer terms cancel ($a(j\omega)^2 = -c$): $\Rightarrow H(j\omega) = jb\omega_0 = 2jc\zeta$
 - $|H(j\omega_0)| = 2\zeta$ times the straight line approximation at ω_0 .
 - 3 dB bandwidth of peak $\simeq 2\zeta\omega_0 \approx \frac{\omega_0}{Q}$. $\Delta\text{phase} = \pm\pi$ over 2ζ decades

$$R = 5, 20, 60, 120$$

$$\zeta = \frac{1}{40}, \frac{1}{10}, \frac{3}{10}, \frac{6}{10}$$

$$Q = \frac{|Z_C(\omega_0) \text{ or } Z_L(\omega_0)|}{R} = 20, 5, \frac{5}{3}, \frac{5}{6}$$
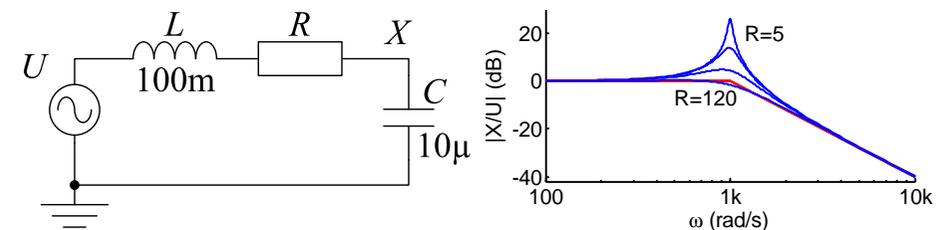
$$\frac{\text{Gain@}\omega_0}{\text{CornerGain}} = \frac{1}{2\zeta} \approx Q$$



$$\frac{X}{U} = \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{(j\omega)^2 LC + j\omega RC + 1}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}, \quad \zeta = \frac{R}{2} \sqrt{\frac{C}{L}}, \quad Q = \frac{\omega_0 L}{R} = \frac{1}{2\zeta}$$

Revision Lecture 2:

▷ **Transients & Lines**

Transients: Basic Ideas

Steady States

Determining Time Constant

Determining Transient Amplitude

Transmission Lines Basics

Reflections

Sinewaves and Phasors

Standing Waves

Revision Lecture 2: Transients & Lines

Transients: Basic Ideas

Revision Lecture 2: Transients & Lines

Transients: Basic Ideas

Steady States

Determining Time Constant

Determining Transient Amplitude

Transmission Lines Basics

Reflections

Sinewaves and Phasors

Standing Waves

- Transients happen in response to a **sudden change**
 - Input voltage/current abruptly changes its magnitude, frequency or phase
 - A switch alters the circuit
- 1st order circuits only: one capacitor/inductor
- All voltage/current waveforms are: **Steady State + Transient**
 - **Steady States**: find with nodal analysis or transfer function
 - ▷ Note: **Steady State** is not the same as **DC Level**
 - ▷ Need steady states before **and** after the sudden change
 - **Transient**: Always a negative exponential: $Ae^{-\frac{t}{\tau}}$
 - ▷ Time Constant: $\tau = RC$ or $\frac{L}{R}$ where R is the Thévenin resistance at the terminals of C or L
 - ▷ Find transient amplitude, A , from continuity since V_C or I_L cannot change instantly.
 - ▷ τ and A can also be found from the transfer function.

Steady States

A **steady-state** output assumes the input frequency, phase and amplitude are constant forever. You need to determine **two** $y_{SS}(t)$ steady state outputs: one for **before** the transient ($t < 0$) and one **after** ($t \geq 0$). At $t = 0$, $y_{SS}(0-)$ means the first one and $y_{SS}(0+)$ means the second.

Method 1: Nodal analysis

Input voltage is DC ($\omega = 0$)

$$\Rightarrow Z_L = 0 \text{ (for capacitor: } Z_C = \infty)$$

So L acts as a short circuit

Potential divider: $y_{SS} = \frac{1}{2}x$



$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

Method 2: Transfer function

$$\frac{Y}{X}(j\omega) = \frac{R+j\omega L}{2R+j\omega L}$$

$$\text{set } \omega = 0: \frac{Y}{X}(0) = \frac{1}{2}$$

$$y_{SS}(0-) = 1, y_{SS}(0+) = 3$$

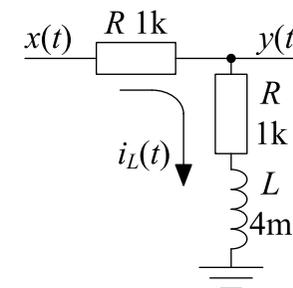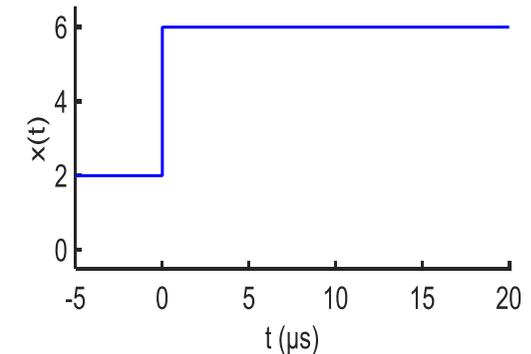

Sinusoidal input \Rightarrow **Sinusoidal steady state** \Rightarrow use phasors.

Then convert phasors to time waveforms to calculate the actual output voltages $y_{SS}(0-)$ and $y_{SS}(0+)$ at $t = 0$.


Determining Time Constant

Method 1: Thévenin

- (a) Remove the capacitor/inductor
- (b) Set all sources to zero (including the input voltage source). Leave output unconnected.
- (c) Calculate the Thévenin resistance between the capacitor/inductor terminals:

$$R_{Th} = 8R \parallel 4R \parallel (6R + 2R) = 2R$$

- (d) Time constant: $= R_{Th}C$ or $\frac{L}{R_{Th}}$
 $\tau = R_{Th}C = 2RC$

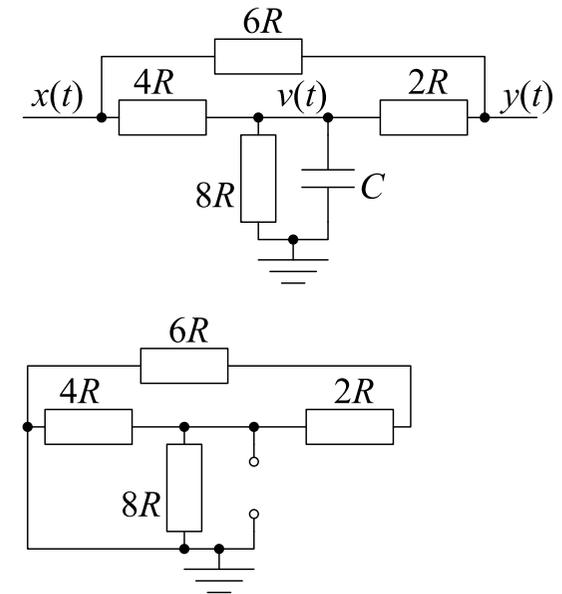

Method 2: Transfer function

- (a) Calculate transfer function using nodal analysis

$$\text{KCL @ } V: \frac{V-X}{4R} + \frac{V}{8R} + j\omega CV + \frac{V-Y}{2R} = 0$$

$$\text{KCL @ } Y: \frac{Y-V}{2R} + \frac{Y-X}{6R} = 0$$

$$\rightarrow \text{Eliminate } V \text{ to get transfer Function: } \frac{Y}{X} = \frac{8j\omega RC + 13}{32j\omega RC + 16}$$

- (b) Time Constant = $\frac{1}{\text{Denominator corner frequency}}$

$$\omega_d = \frac{16}{32RC} \Rightarrow \tau = \frac{1}{\omega_d} = 2RC$$

Determining Transient Amplitude

Revision Lecture 2:
Transients & Lines

Transients: Basic
Ideas

Steady States

Determining Time
Constant

Determining
Transient

▷ Amplitude

Transmission Lines
Basics

Reflections

Sinewaves and
Phasors

Standing Waves

After an input change at $t = 0$, $y(t) = y_{SS}(t) + Ae^{-\frac{t}{\tau}}$.

$\Rightarrow y(0+) = y_{SS}(0+) + A \Rightarrow A = y(0+) - y_{SS}(0+)$

Method: (a) calculate true output $y(0+)$, (b) subtract $y_{SS}(0+)$ to get A




(i) Version 1: v_C or i_L continuity

$x(0-) = 2 \Rightarrow i_L(0-) = 1 \text{ mA}$

Continuity $\Rightarrow i_L(0+) = i_L(0-)$

Replace L with a 1 mA current source

$y(0+) = x(0+) - iR = 6 - 1 = 5$

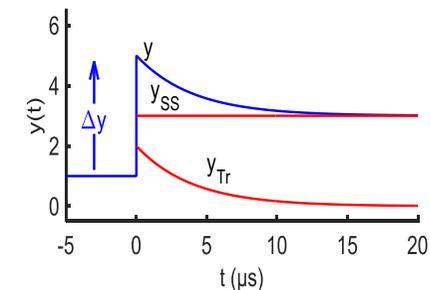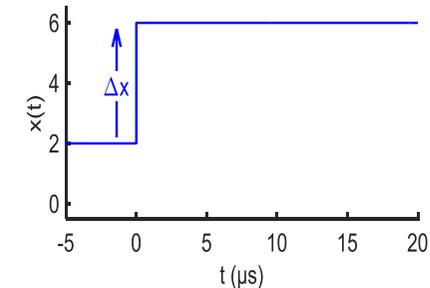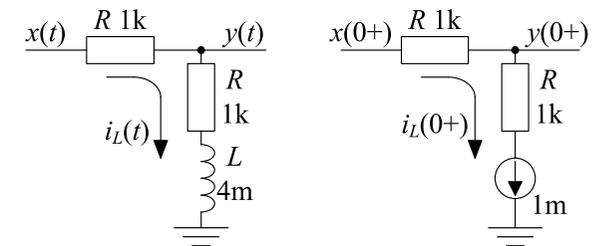

(i) Version 2: Transfer function

$$H(j\omega) = \frac{Y}{X}(j\omega) = \frac{R+j\omega L}{2R+j\omega L}$$

Input step, $\Delta x = x(0+) - x(0-) = +4$

$y(0+) = y(0-) + H(j\infty) \times \Delta x$

$$= 1 + \Delta y = 1 + 1 \times 4 = 5$$

(ii) $A = y(0+) - y_{SS}(0+) = 5 - 3 = 2$

(iii) $y(t) = y_{SS}(t) + Ae^{-t/\tau}$
 $= 3 + 2e^{-t/2\mu}$

Transmission Lines Basics

- Revision Lecture 2:
Transients & Lines


- Transients: Basic Ideas
- Steady States
- Determining Time Constant
- Determining Transient Amplitude
- Transmission Lines
 - ▷ Basics
 - Reflections
 - Sinewaves and Phasors
 - Standing Waves

Transmission Line: constant L_0 and C_0 : inductance/capacitance per metre.


Forward wave travels along the line: $f_x(t) = f_0 \left(t - \frac{x}{u} \right)$.

Velocity $u = \sqrt{\frac{1}{L_0 C_0}} \approx \frac{1}{2}c = 15 \text{ cm/ns}$

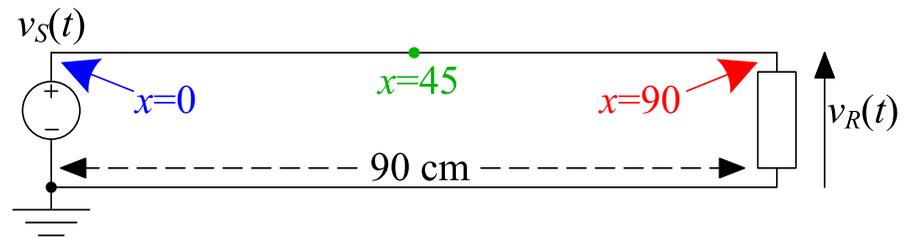$f_x(t)$ equals $f_0(t)$ but delayed by $\frac{x}{u}$.



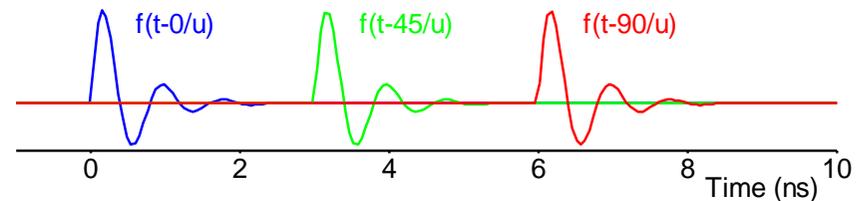Knowing $f_x(t)$ for $x = x_0$ fixes it for all other x .



Backward wave: $g_x(t)$ is the same but travelling \leftarrow : $g_x(t) = g_0 \left(t + \frac{x}{u} \right)$.


Voltage and current are: $v_x = f_x + g_x$ and $i_x = \frac{f_x - g_x}{Z_0}$ where i_x is positive in the $+x$ direction (\rightarrow) and $Z_0 = \sqrt{\frac{L_0}{C_0}}$

Waveforms of f_x and g_x are determined by the connections at both ends.

Reflections

- Revision Lecture 2:
- Transients & Lines

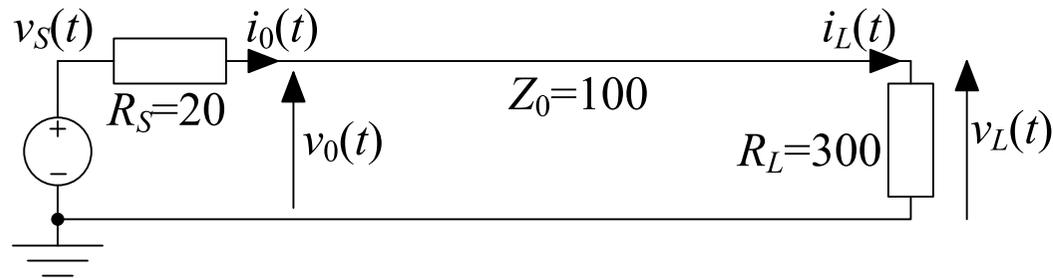- Transients: Basic Ideas
- Steady States
- Determining Time Constant
- Determining Transient Amplitude
- Transmission Lines Basics
- ▷ Reflections
- Sinewaves and Phasors
- Standing Waves



$$v_x = f_x + g_x$$

$$i_x = \frac{f_x - g_x}{Z_0}$$

At $x = L$, Ohm's law $\Rightarrow \frac{v_L(t)}{i_L(t)} = R_L \Rightarrow g_L(t) = \frac{R_L - Z_0}{R_L + Z_0} \times f_L(t)$.

Reflection coefficient: $\rho_L = \frac{g_L(t)}{f_L(t)} = \frac{R_L - Z_0}{R_L + Z_0}$

$\rho_L \in [-1, +1]$ and increases with R_L

Knowing $f_x(t)$ for $x = x_0$ now tells you $f_x, g_x, v_x, i_x \forall x$

At $x = 0$: $f_0(t) = \frac{Z_0}{R_S + Z_0} v_S(t) + \frac{R_S - Z_0}{R_S + Z_0} g_0(t) = \tau_0 v_S(t) + \rho_0 g_0(t)$

Wave bounces back and forth getting smaller with each reflection:

$$v_S(t) \xrightarrow{\times \tau_0} f_0(t) \xrightarrow{\times \rho_L} g_0(t + \frac{2L}{u}) \xrightarrow{\times \rho_0} f_0(t + \frac{2L}{u}) \xrightarrow{\times \rho_L} g_0(t + \frac{4L}{u}) \xrightarrow{\times \rho_0} \dots$$

Infinite sum:

$$f_0(t) = \tau_0 v_S(t) + \tau_0 \rho_L \rho_0 v_S(t - \frac{2L}{u}) + \dots = \sum_{i=0}^{\infty} \tau_0 \rho_L^i \rho_0^i v_S(t - \frac{2Li}{u})$$


Sinewaves and Phasors

- Revision Lecture 2: Transients & Lines
- Transients: Basic Ideas
- Steady States
- Determining Time Constant
- Determining Transient Amplitude
- Transmission Lines Basics
- Reflections
 - Sinewaves and Phasors
- Standing Waves

Sinewaves are easier because:

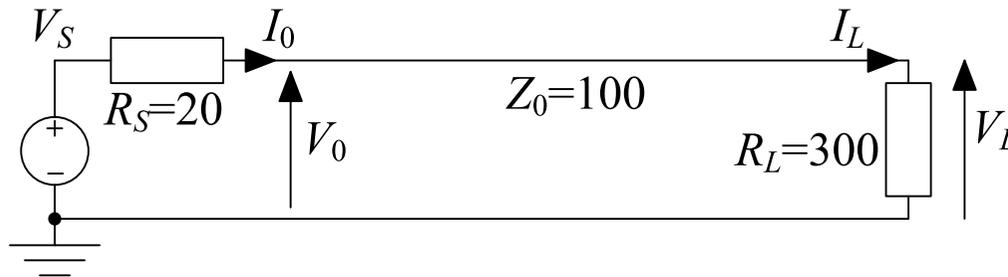1. Use phasors to eliminate t : $f_0(t) = A \cos(\omega t + \phi) \Leftrightarrow F_0 = Ae^{j\phi}$
2. Time delays are just phase shifts:
 $f_x(t) = A \cos(\omega(t - \frac{x}{u}) + \phi) \Leftrightarrow F_x = Ae^{j(\phi - \frac{\omega}{u}x)} = F_0 e^{-jkx}$
 $k = \frac{\omega}{u} = \frac{2\pi}{\lambda}$ is the **wavenumber**: radians per metre (c.f. ω in rad/s)

As before: $V_x = F_x + G_x$ and $I_x = \frac{F_x - G_x}{Z_0}$



As before:

$$G_L = \rho_L F_L$$

$$F_0 = \tau_0 V_S + \rho_0 G_0$$

But $G_0 = F_0 \rho_L e^{-2jkL}$: roundtrip delay of $\frac{2L}{u}$ + reflection at $x = L$.
 Substituting for G_0 in source end equation: $F_0 = \tau_0 V_S + \rho_0 F_0 \rho_L e^{-2jkL}$
 $\Rightarrow F_0 = \frac{\tau_0}{1 - \rho_0 \rho_L \exp(-2jkL)} V_S$ so no infinite sums needed 😊

Standing Waves

Revision Lecture 2: Transients & Lines

Transients: Basic Ideas

Steady States

Determining Time Constant

Determining Transient Amplitude

Transmission Lines

Basics

Reflections

Sinewaves and Phasors


▷ Standing Waves

Standing waves arise whenever a wave meets its reflection:

at positions where the two waves are **in phase** their amplitudes **add** but where they are **anti-phase** their amplitudes **subtract**.

At any point x ,
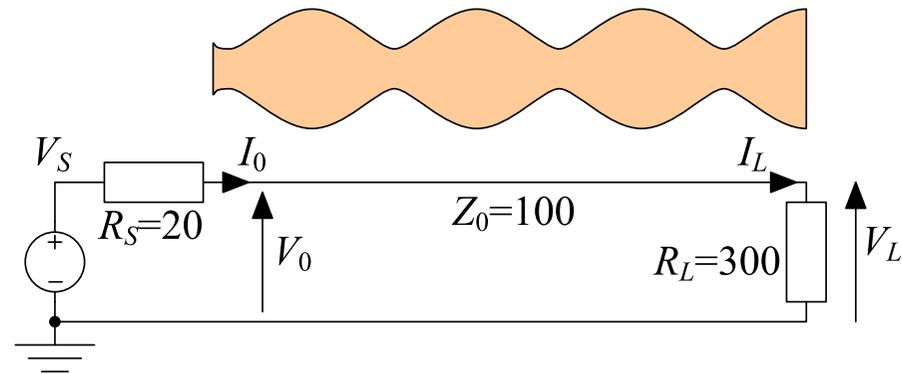
$$\text{delay of } \frac{x}{u} \Rightarrow F_x = F_0 e^{-jkx}$$



Backward wave: $G_x = \rho_L F_x e^{-2jk(L-x)}$: reflection + delay of $2 \frac{L-x}{u}$

Voltage at x : $V_x = F_x + G_x = F_0 e^{-jkx} (1 + \rho_L e^{-2jk(L-x)})$

Voltage Magnitude : $|V_x| = |F_0| |1 + \rho_L e^{-2jk(L-x)}|$: depends on x

If $\rho_L \geq 0$, **max magnitude** is $(1 + \rho_L) |F_0|$ whenever $e^{-2jk(L-x)} = +1$
 $\Rightarrow x = L$ or $x = L - \frac{\pi}{k}$ or $x = L - \frac{2\pi}{k}$ or ...

Min magnitude is $(1 - \rho_L) |F_0|$ whenever $e^{-2jk(L-x)} = -1$
 $\Rightarrow x = L - \frac{\pi}{2k}$ or $x = L - \frac{3\pi}{2k}$ or $x = L - \frac{5\pi}{2k}$ or ...