


## Lecture 13

# Adder Circuits

### Objectives

- Understand how to add both signed and unsigned numbers
- Appreciate how the delay of an adder circuit depends on the data values that are being added together

## Full Adder

 

$$\begin{array}{r} P \\ Q \\ + CI \\ \hline C \quad S \end{array}$$

Output is a 2-bit number counting how many inputs are high

P	Q	CI	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$C = P \cdot Q + P \cdot CI + Q \cdot CI$$

$$S = P \oplus Q \oplus CI$$

- Symmetric function of the inputs
- Self-dual: Invert all inputs  $\Rightarrow$  invert all outputs  
If  $k$  inputs high initially then  $3-k$  high when inverted  
Inverting all bits of an  $n$ -bit number make  $x \rightarrow 2^n - 1 - x$
- Note:  $P \oplus Q \oplus CI = (P \oplus Q) \oplus CI = P \oplus (Q \oplus CI)$
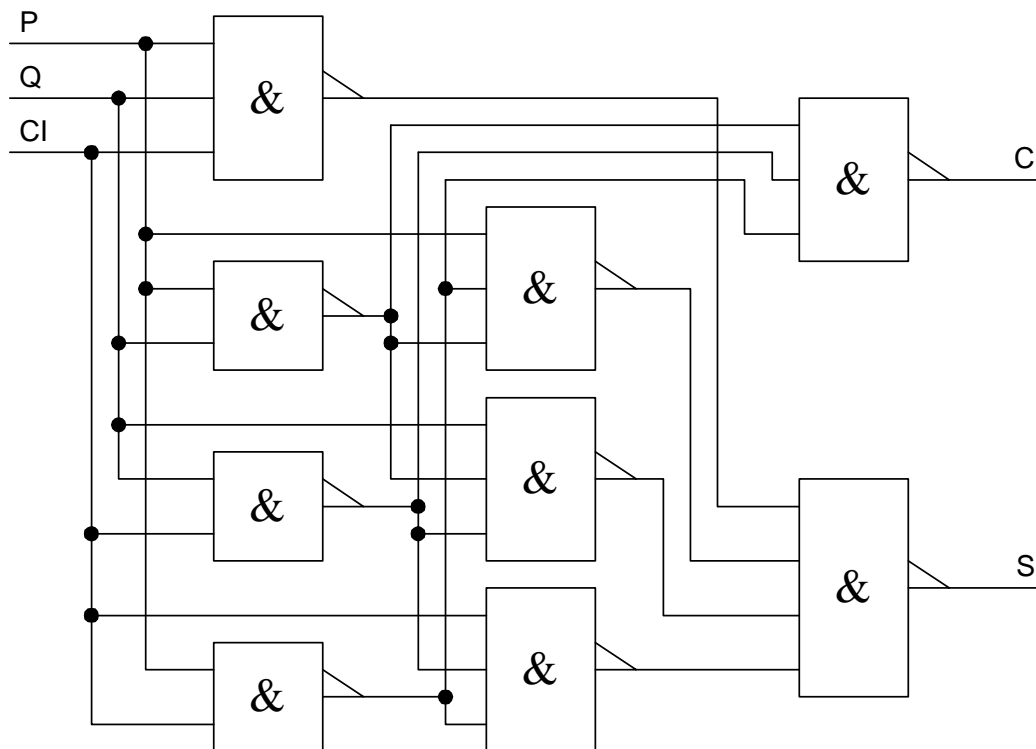
## Full Adder Circuit

9-gate full-adder NAND implementation (do not memorize)




Propagation delays:

From	To	Delay
P,Q or Cl	S	3
P,Q or Cl	C	2

Complexity: 25 gate inputs  $\Rightarrow$  50 transistors but use of complex gates can reduce this somewhat.

 
## N-bit adder

We can make an adder of arbitrary size by cascading full adder sections:



The main reason for using 2's complement notation for signed numbers is that:

 **Signed and unsigned** numbers can use identical circuitry




## Adder Size Selection

The number of bits needed in an adder is determined by the range of values that can be taken by its **output**.

If we add two 4-bit numbers, the answer can be in the range:

- 0 to 30 for *unsigned* numbers
- -16 to +14 for *signed* numbers

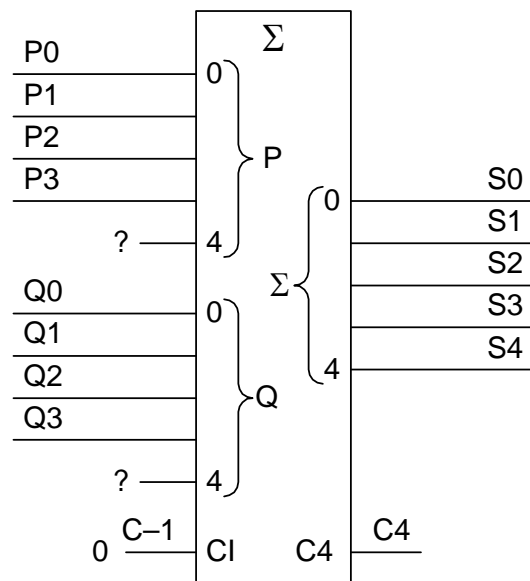In both cases we need a 5-bit adder to avoid any possibility of overflow:



We need to expand the input numbers to 5 bits. How do we do this ?

## Expanding Binary Numbers

### Unsigned numbers

Expand an unsigned number by adding the appropriate number of 0's at the MSB end:

5	0101	00000101
13	1101	00001101

### Signed numbers

Expand a signed number by duplicating the MSB the appropriate number of times:

5	0101	00000101
-3	1101	11111101

This is known as *sign extension*

---

## Shrinking Binary Numbers

### Unsigned


Can delete any number of bits from the MSB end so long as they are all 0's.

### Signed


Can delete any number of bits from the MSB end so long as they are all the same as the MSB that remains.

## Adding Unsigned Numbers

To avoid overflow, we use a 5-bit adder:

 

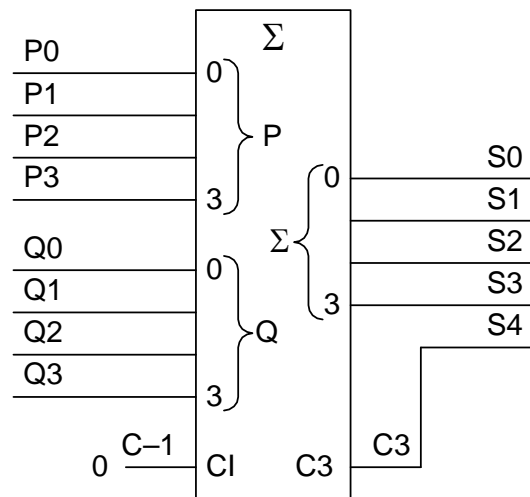
The MSB stage is performing the addition:  $0 + 0 + C_3$ . Thus  $S_4$  always equals  $C_3$  and  $C_4$  always equals 0.



We can use a 4-bit adder with  $C_3$  as an answer bit.

## Adding Signed Numbers

To avoid overflow, we use a 5-bit adder:

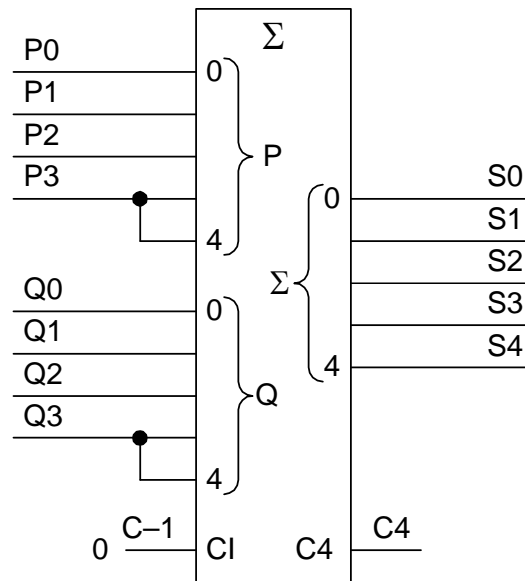

This is different from the unsigned case because P4 and Q4 are no longer constants. [We cannot simplify this circuit by removing the MSB stage.](#)

If P and Q have different signs then S4 will not equal C3.


e.g. P=0000, Q=1111  
 Unsigned P+Q=01111, Signed P+Q=11111

Some minor simplifications are possible:

- If the C4 output is not required, the circuitry that generates it can be removed.
- S4 can be generated directly from P3, Q3 and C3 which reduces the circuitry needed for the last stage.



## Adder Propagation Delay

 

Delays within each stage (in gate delays):

$$P, Q, CI \rightarrow S = 3 \quad P, Q, CI \rightarrow C = 2$$

Worst-case delay is:

$$P_0 \rightarrow C_0 \rightarrow C_1 \rightarrow C_2 \rightarrow S_3 = 3 \times 2 + 3 = 9$$

Note: We also have  $Q_0 \rightarrow S_3 = 9$  and  $C_{-1} \rightarrow S_3 = 9$

For an N-bit adder, the worst delay is  $(N-1) \times 2 + 3 = 2N+1$

Example of worst case delay:


- Initially:  $P_{3:0}=0000, Q_{3:0}=1111 \Rightarrow S_{4:0}=01111$
- Change to:  $P_{3:0}=0001, Q_{3:0}=1111 \Rightarrow S_{4:0}=10000$

## Delays are Data-Dependent

To determine the delay of a circuit, we need to specify:

1. The circuit
2. The initial value of all the inputs
3. Which of the inputs changes

 Example: What is the propagation delay  $A \rightarrow Q$  ?



Answer 1 ( $B=0$ ):

- Initially:  $A=0, B=0 \Rightarrow X=1, Y=0, Z=0, Q=0$
- Then:  $A \uparrow \Rightarrow Y \uparrow \Rightarrow Q \uparrow$                       2 gate delays


Answer 2 ( $B=1$ ):

- Initially:  $A=0, B=1 \Rightarrow X=1, Y=0, Z=1, Q=1$
- Then:  $A \uparrow \Rightarrow X \downarrow \Rightarrow Z \downarrow \Rightarrow Q \downarrow$                       3 gate delays
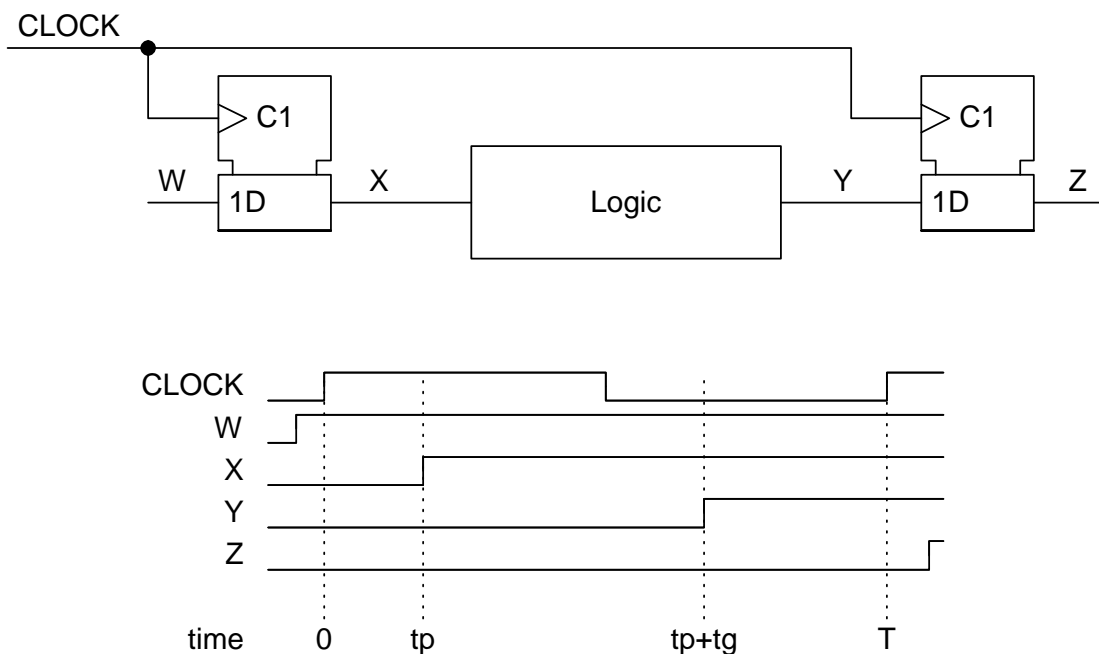
## Worst-Case Delays

We are normally interested only in the worst-case delay from a change in any input to any of the outputs.

The worst-case delay determines the maximum clock speed in a synchronous circuit:



$$tp + tg + ts < T$$

Since the clock speed must be chosen to ensure that the circuit always works, it is only the worst-case logic delay that matters.

## Quiz

1. In an full adder, why is it normally more important to reduce the delay from CI to C than to reduce the delay from P to S ?
2. How many bits are required to represent the number  $A+B$  if A and B are (a) 8-bit *unsigned* numbers or alternatively (b) 8-bit *signed* numbers.
3. How do you convert a 4-bit *signed* number into an 8-bit signed number ?
4. How do you convert a 4-bit *unsigned* number into an 8-bit signed number ?
5. How is it possible for the propagation delay of a circuit from an input to an output to depend on the value of the other inputs ?

## Lecture 14


# Fast Adder Circuits (1)

### Objectives

- Understand how the propagation delay of an adder can be reduced by inverting alternate bits.
- Understand how the propagation delay of an adder can be reduced still further by means of carry lookahead.


## Standard N-bit Adder

Delay of standard N-bit adder =  $2N+1$

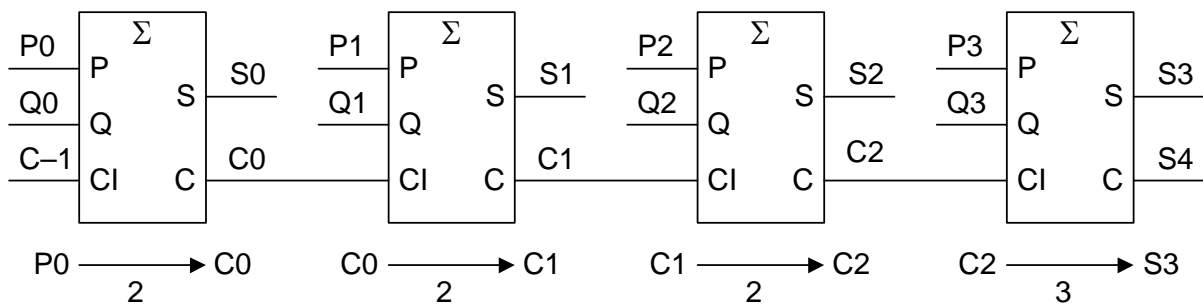


Delay of carry path within each full adder = 2

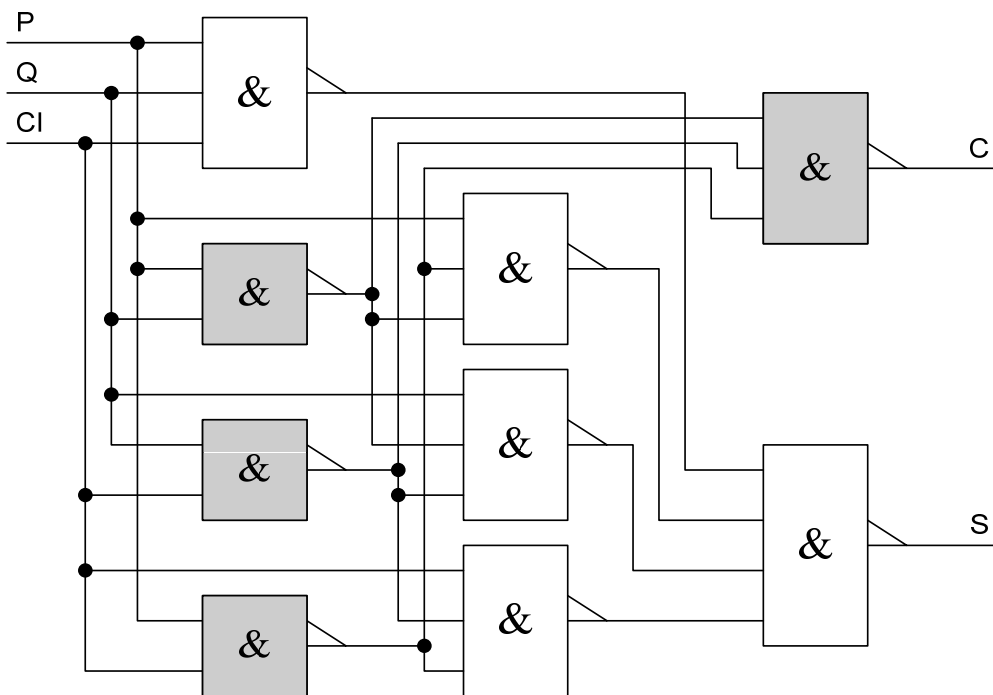Carry path consists of three 2-input + one 3-input NANDs



 
## Faster Adder Circuits: 1

Because a full-adder is *self-dual*, it will still work if for alternate stages we invert both the inputs and the outputs:




Now consider only the Carry signals:

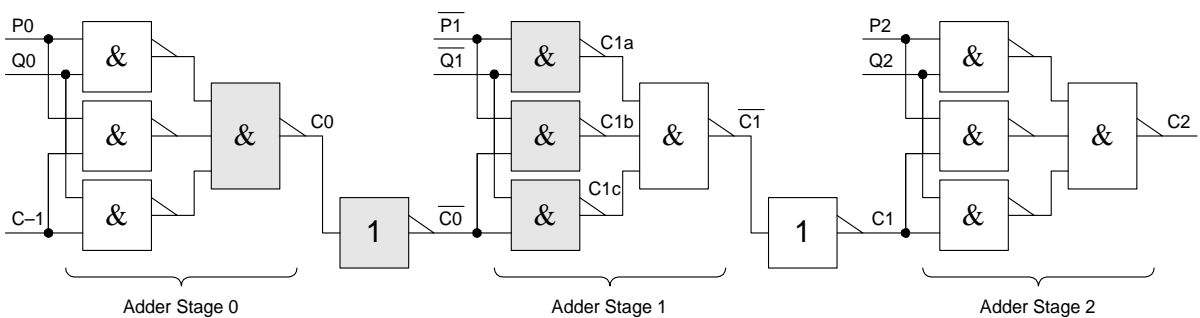


By merging the shaded gates we can reduce the delay to one gate per adder stage.

## Fast Adder Circuits: 1 (part 2)

 

 We can merge the 3-NAND and inverter into the final column of gates as shown; this gives one delay per stage:



The signals  $C1a$ ,  $C1b$ ,  $C1c$  form an *AND-bundle*:  $C1$  is true only if all of them are high. We don't need the signal  $C1$  directly so the shaded gate can be omitted.




## Fast Adder Circuits: 1 (part 3)

### Even stages:

Delays:

$P, Q, CI \rightarrow S \quad 3$

$P, Q, CI \rightarrow C \quad 1$

 

30 gate inputs  $\Rightarrow$  60 transistors

### Odd stages:


Delays:

$P, Q \rightarrow S \quad 5$

$P, Q \rightarrow C \quad 2$

$CI \rightarrow S \quad 4$

$CI \rightarrow C \quad 1$

 


33 gate inputs  $\Rightarrow$  66 transistors

Bundles are denoted by a single wire with a / through it.

22% more transistors but twice as fast.
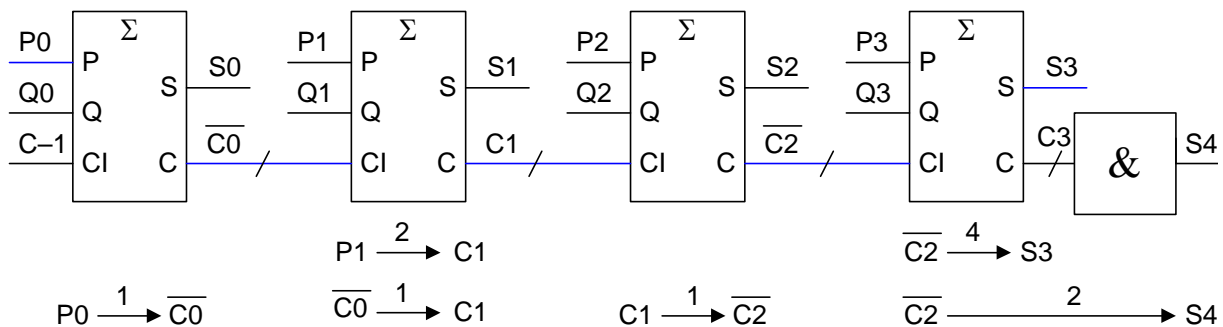
## Fast Adder Circuits: 1 (part 4)

For an N-bit adder we alternate the two modules (with a normalish first stage):



Worst case delay is:

$$P_0 \rightarrow !C_0 \rightarrow C_1 \rightarrow !C_2 \rightarrow S_3 = 7 \text{ gate delays}$$

Note that:

- Delay to  $S_4$  is shorter than delay to  $S_3$
- Delay from  $P_1$  is the same as delay from  $P_0$
- Worst-case example:  
Initially:  $P_{3:0}=0000$ ,  $Q_{3:0}=1111$ , then  $P_0 \uparrow$

Delay for N-bit adder (N even) is  $N+3$   
(compare with  $2N+1$  for original circuit)

## Carry Lookahead (1)

For each bit of an N-bit adder we get a carry out ( $CO=1$ ) if two or more of P,Q,CI are equal to 1.

There are three possibilities:

- P,Q=00:            C=0 always            *Carry Inhibit*
- P,Q=01 or 10:    C=CI                    *Carry Propagate*
- P,Q=11:            C=1 always            *Carry Generate*

We define three signals:

- $CG = P \cdot Q$       Carry Generate
- $CP = P \oplus Q$       Carry Propagate
- $CGP = P + Q$       Carry Generate or Propagate

We get a carry out from a bit position either if that bit generates a carry ( $CG=1$ ) or else if it propagates the carry and there is a carry in from the previous bit ( $CP \cdot CI = 1$ ):

$$C = CG + CP \cdot CI$$

Since  $CGP = CG + CP$ , an alternate expression is:

$$C = CG + CGP \cdot CI$$

The second expression is usually used since  $P + Q$  is easier and faster to generate than  $P \oplus Q$ .

## Carry Lookahead (2)

Consider all the ways in which we get a carry out of bit position 3:

- |   |                  |
|---|------------------|
| 1) Bit 3 generates a carry:   | 1???             |
|   | + <u>1???</u>    |
| 2) Bit 2 generates a carry <u>and</u><br>bit 3 propagates it.   | 11??             |
|   | + <u>01??</u>    |
| 3) Bit 1 generates a carry <u>and</u><br>bit 2 propagates it <u>and</u><br>bit 3 propagates it.                                   | 101?             |
|   | + <u>011?</u>    |
| 4) Bit 0 generates a carry <u>and</u><br>bit 1 propagates it <u>and</u><br>bit 2 propagates it <u>and</u><br>bit 3 propagates it. | 1011             |
|   | + <u>0101</u>    |
| 5) The C-1 input is high <u>and</u><br>bits 0,1,2 and 3 all propagate the carry.  | 1011             |
|   | + <u>0100</u> +1 |


Thus

$$C_3 = C_G3 + C_P3 \cdot C_G2 + C_P3 \cdot C_P2 \cdot C_G1 + C_P3 \cdot C_P2 \cdot C_P1 \cdot C_G0 + C_P3 \cdot C_P2 \cdot C_P1 \cdot C_P0 \cdot C_{-1}$$

As before, we can use  $C_{GPn}$  in place of  $C_{Pn}$ .
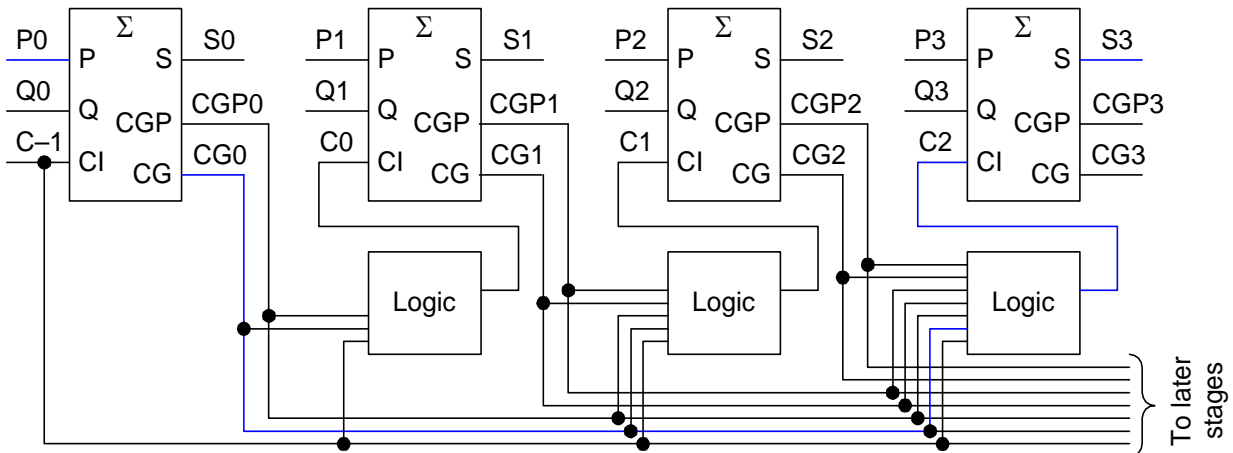
## Carry Lookahead (3)

Each stage must now generate CP and CGP instead of C:



$$C_0 = CG_0 + CGP_0 \cdot C_{-1}$$

$$C_1 = CG_1 + CGP_1 \cdot CG_0 + CGP_1 \cdot CGP_0 \cdot C_{-1}$$

$$C_2 = CG_2 + CGP_2 \cdot CG_1 + CGP_2 \cdot CGP_1 \cdot CG_0 + CGP_2 \cdot CGP_1 \cdot CGP_0 \cdot C_{-1}$$

Worst-case propagation delay:

$$P_0 \rightarrow CG_0 = 1 \text{ gate delay (} CG_0 = P_0 \cdot Q_0 \text{)}$$

$$CG_0 \rightarrow C_2 = 2 \text{ gate delays (see above expression)}$$

$$C_2 \rightarrow S_3 = 3 \text{ gate delays (from full adder circuit)}$$

$$\text{Total} = 6 \text{ gate delays (independent of adder length)}$$

## Carry Lookahead (4)

Carry lookahead circuit complexity for N-bit adder:

- Expression for  $C_n$  involves  $n+2$  product terms each containing an average of  $\frac{1}{2}(n+3)$  input signals.
- Direct implementation of equations for all  $N$  carry signals involves approx  $N^3/3$  transistors.


$$N = 64 \Rightarrow N^3/3 = 90,000$$

- By using a complex CMOS gate, we can actually generate  $C_n$  using only  $4n+6$  transistors so all  $N$  signals require approx  $2N^2$  transistors.

$$N = 64 \Rightarrow 2N^2 = 8,000$$

Actual gain is not as great as this because for large  $n$ , the expression for  $C_n$  is too big to use a single gate.

 - $C_{-1}$ ,  $CG_0$  and  $CGP_0$  must drive  $N-1$  logic blocks. For large  $N$  we must use a chain of buffers to reduce delay:



The circuit delay is thus not quite independent of  $N$ .

## Quiz

1. What does it mean to say that a full-adder is *self-dual* ?
2. How does placing an inverter between each stage of a multi-bit adder allow the merging of gates in consecutive stages ?
3. In a 4-bit adder, give an example of a propagation delay that *increases* when alternate bits are inverted.
4. Why is a carry-lookahead adder generally implemented using CGP rather than CP outputs ?

## Lecture 15

**Fast Adder Circuits (2)**

## Objectives

- Understand the *carry skip* technique for reducing the propagation delay of an adder circuit.
- Understand how the *carry save* technique can be used when adding together several numbers.


## Summary So Far:

- Cascading full adders:  
2N+1 gate delays, 50N transistors
- Use self-duality to invert odd-numbered stages:  
N+3 gate delays, 61N transistors
- Carry lookahead:  
6 gate delays, between  $2N^2$  and  $0.3N^3$  transistors




## Carry Skip (1)

Consider a 12-bit adder:

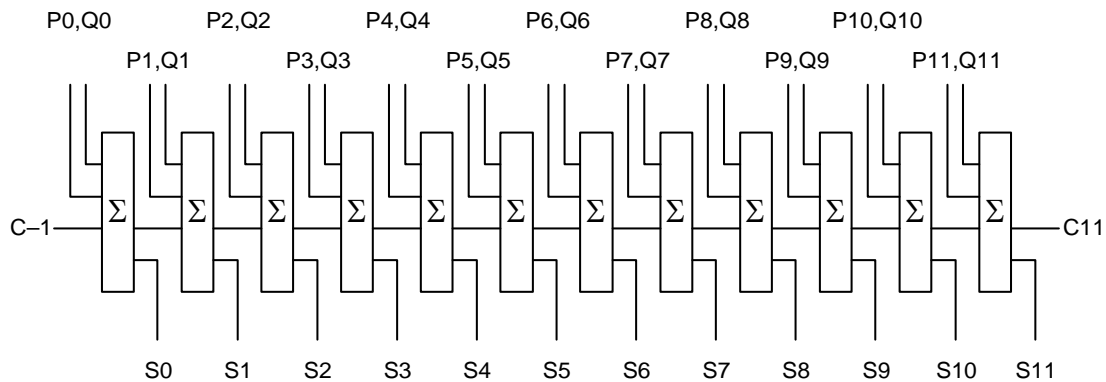


The worst-case delay path is from  $C_{-1}$  to  $S_{11}$ .

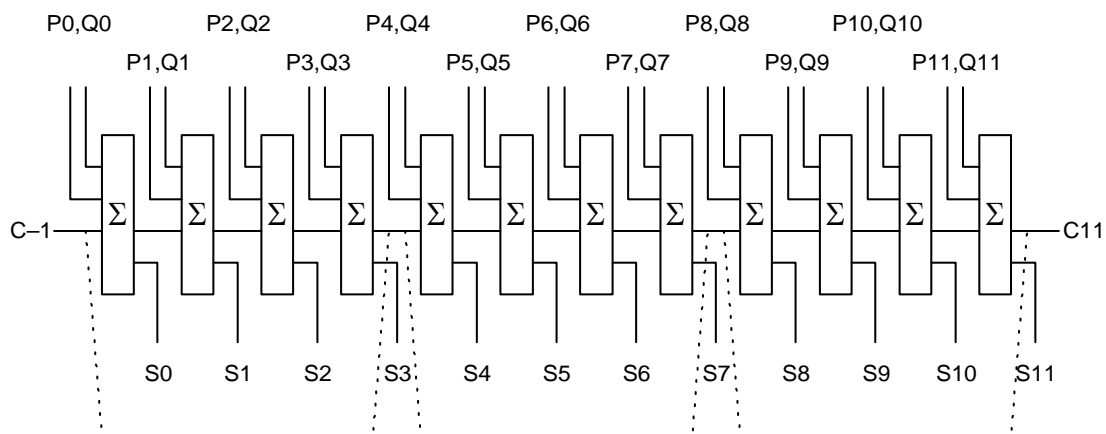In *carry skip*, we speed up this path by allowing the carry signal to skip over several adder stages at a time:


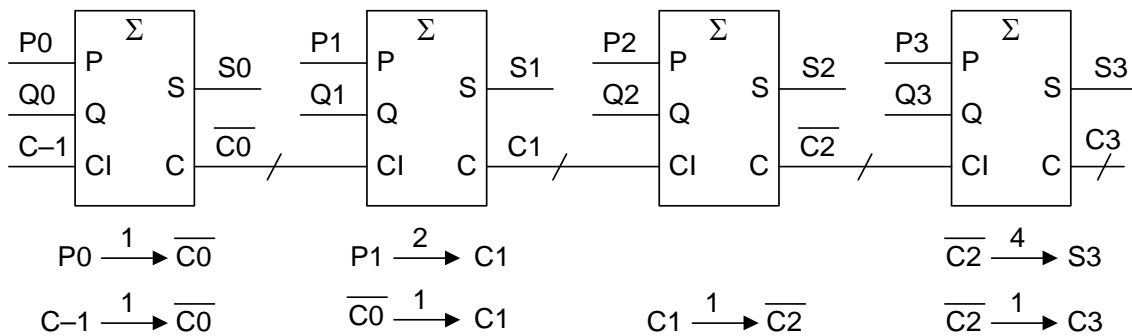
## Carry Skip (2)

Consider our fast adder circuit without carry lookahead (but using alternate-bit inversion):



There are two possible sorts of addition sum:

- *All bits propagate the carry*  $\Rightarrow C_3 = C_{-1}$ :

0101	0101
1010	1010
0	1
<u>01111</u>	<u>10000</u>

$$C_{-1} \uparrow \rightarrow C_3 \uparrow = 4 \text{ gate delays}$$


- *At least one bit doesn't propagate the carry*  
 $\Rightarrow C_3$  is completely independent of  $C_{-1}$ :

0101	0101
1110	1110
0	1
<u>10011</u>	<u>10100</u>

$$C_{-1} \uparrow \rightarrow C_3 = 0 \text{ gate delays}$$
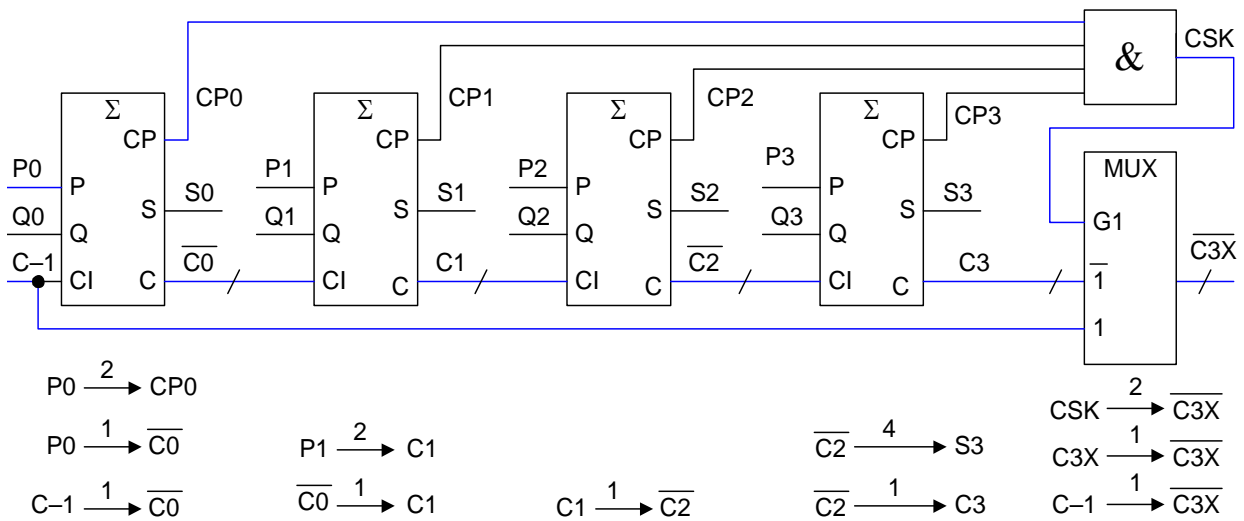
### Carry Skip (3)

We speed up  $C-1 \rightarrow C3$  by detecting when all bits propagate the carry and using a multiplexer to allow  $C-1$  to skip all the way to  $C3$ :



Calculate Carry Propagate ( $CP = P \oplus Q$ ) for each bit. Call this 2 gate delays since XOR gates are slow.  $CSK=1$  if all bits propagate the carry.


- Case 1: All bits propagate the carry  
 $C-1 \rightarrow !C3X = 1$  gate delay (via multiplexer)
- Case 2: At least one bit inhibits or propagates the carry  
 $\Rightarrow$  **C-1 does not affect C3**

Longest delays to  $!C3X$  and  $S3$ :

- $P0 \rightarrow !C3X = 5$  (via either  $!C0$  or  $CSK$ )
- $P0 \rightarrow S3 = 7$


## Carry Skip (4)

### Multiplexer Details

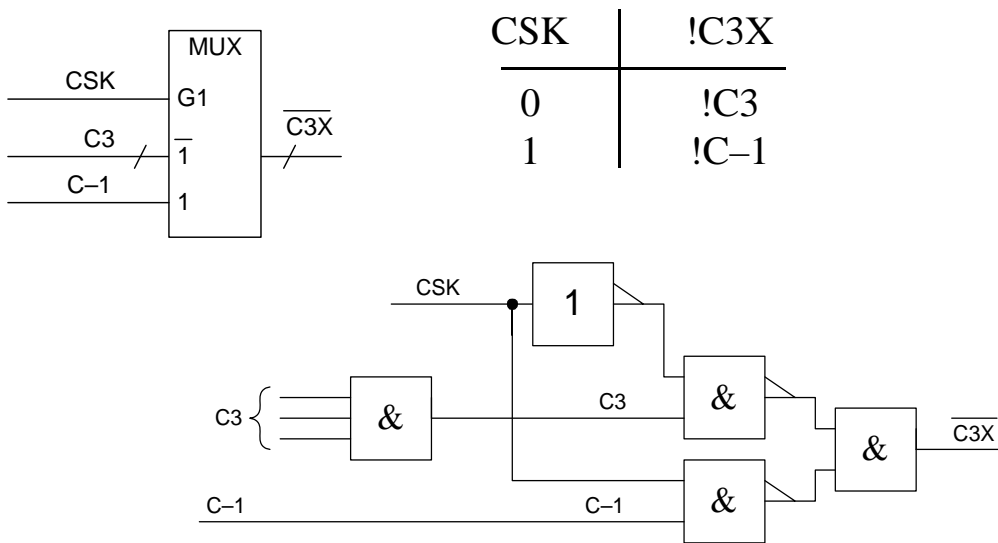

We merge both AND gates:

 
- the 3-AND gate merges into the following NAND
- the 2-AND gate merges into the next adder stage



C-1 → !C3X now equals 1 gate delay.

## Carry Skip (5)

Combine 4 blocks to make a 16-bit adder:

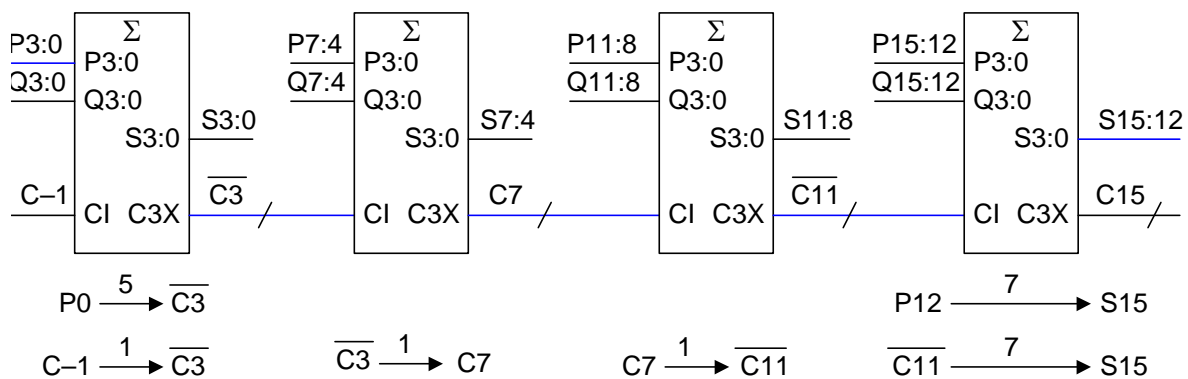

Worst-case delay is:

$$P_0 \rightarrow \overline{C_3} \rightarrow C_7 \rightarrow \overline{C_{11}} \rightarrow S_{15} = 14 \text{ gate delays}$$

Each additional block of 4 bits gives a delay of only 1 gate delay: this corresponds to  $\frac{1}{4}$  gate delay per bit.

For an N-bit adder we have a delay of  $\frac{1}{4}N+10$ . We can reduce this still further by having larger super-blocks.

### Carry circuit delays:


Simple	$2N+1$
Bit-inversion	$N+3$
Carry Skip	$\frac{1}{4}N+10$
Carry Lookahead	6

- but lots of circuitry and high gate fanout  $\Rightarrow$  more delay
 
## Adding lots of numbers

In multiplication circuits and digital filters we need to add lots of numbers together.

Suppose we want to add together five four-bit unsigned numbers: V, W, X, Y and Z.




If we use carry-lookahead adders, each stage will have 6 gate delays.

Total delay to add together K values will be  $(K-1) \times 6$ .

Thus  $K=16$  gives a delay of 90 gate delays.
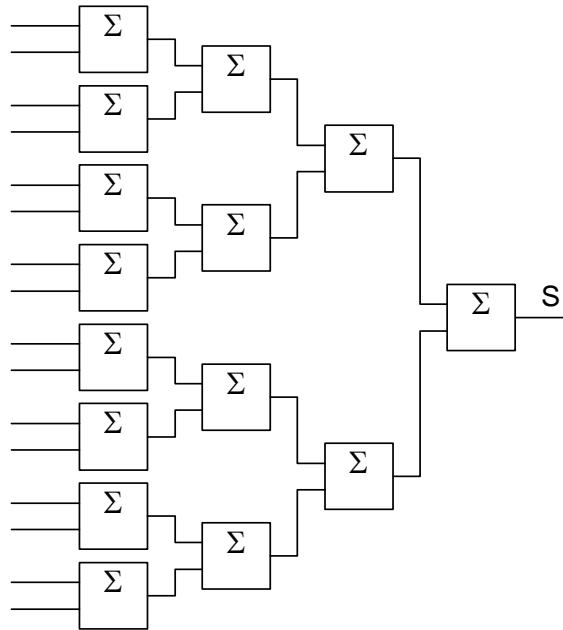
## Addition Tree

In practice we use a tree arrangement of adders:



Number of values, K	16	8	4	2	1
$\log_2(K)$	4	3	2	1	0

Each column of adders adds a delay of 6 and halves the number of values needing to be added together.


Equivalently, each column of adders reduces  $\log_2 K$  by one.

Hence the total delay is  $\log_2 K \times 6$  giving a delay of 24 to add together 16 values.

The total number of adders required is still  $K-1$  as before.
 
## Carry-Save Adder

Take a normal 4-bit adder but *don't connect up the carries*:




We have  $P+Q+R = 2C + S$

E.g.  $P=9, Q=12, R=13$   
gives  $C=13, S=8$

P:	1001
Q:	1100
R:	1101
S:	1000
C:	1101_

We call this a *carry-save* adder: it reduces the addition of 3 numbers to the addition of 2 numbers.

 The propagation delay is 3 gates regardless of the number of bits. The amount of circuitry is much less than a carry-lookahead adder.




The circuit reduces  $\log_2 K$  by 0.585 (from 1.585 to 1.0) for a delay of 3. The overall delay we can expect is therefore  $\log_2 K \times 3/0.585 = \log_2 K \times 5.13$ . This is *better* than carry lookahead for *less circuitry*.


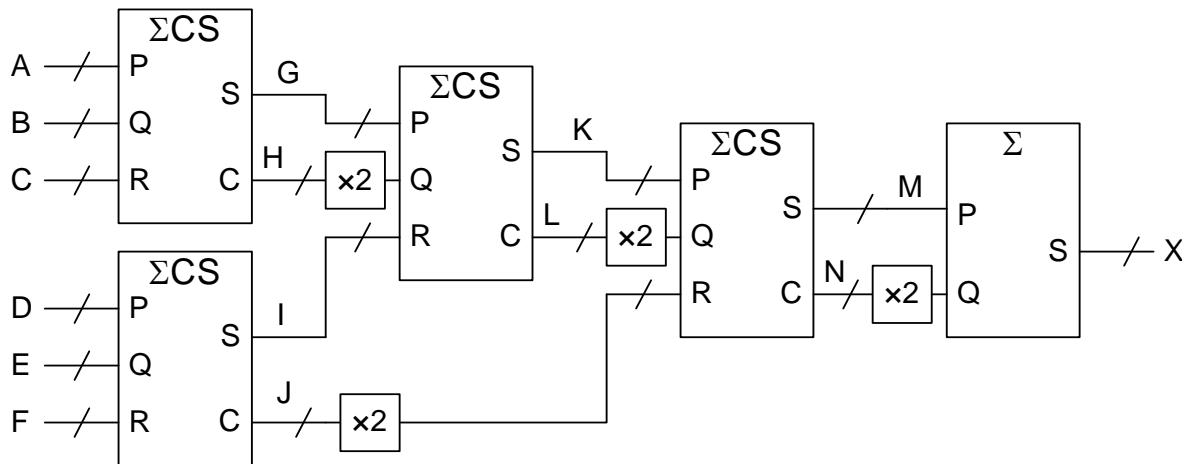
## Carry Save Example

We will calculate:  $13+10+5+11+12+1 = 52$




A: 1101	G: _0010	
B: 1010	2H: 1101_	
C: 0101	I: _0110	
<hr/> G: 0010	<hr/> K: 11110	M: 01000
H: 1101_	L: _0010_	2N: 1011__
		<hr/> X: 0110100
D: 1011	K: 11110	
E: 1100	2L: 0010_	
F: 0001	2J: 1001_	
<hr/> I: 0110	<hr/> M: 01000	
J: 1001_	N: 1011__	

- Notes:**
1. x2 requires no logic: just connect wires appropriately
  2. No logic required for adder columns with only 1 input
  3. All adders are actually only 4 bits wide
  4. Final addition M+2N requires a proper adder
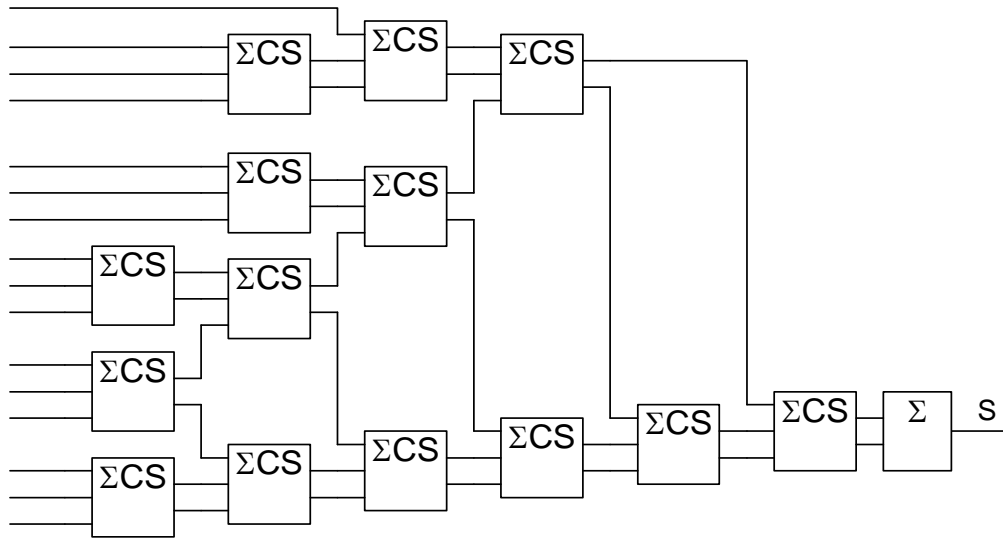
## Carry-Save Tree

We can construct a tree to add sixteen values together:



Number of values, K	16	13	9	6	4	3	2	1
$\log_2(K)$	4	3.7	3.17	2.58	2	1.58	1	0
Delay	0	3	6	9	12	15	18	24
$\Delta\text{Delay}/\Delta\log_2(K)$	10	5.65	5.13	5.13	7.23	5.13	6	

- The final stage must be a normal adder because we need to obtain a single output.
- The delay is the same as for a conventional lookahead-adder tree but uses much less circuitry.
- The irregularity of the tree causes a reduction in efficiency but this is relatively small (and becomes even smaller for large K).
- Inverting alternate stages will speed up both tree circuits still further but requires more circuitry.

*Merry Christmas*



*The End*

## Quiz

1. In a 4-bit adder, how can you tell from  $P_{0:3}$  and  $Q_{0:3}$  whether or not  $C_3$  is dependent on  $C_{-1}$  ?
2. A multiplexer normally has 2 gate delays from its data inputs to its output. How is this reduced to 1 gate delay in the carry skip circuit ?
3. If five 4-bit numbers are added together, how many bits are needed to represent the result ?