 


Notation:

*Unless explicitly indicated otherwise, digital circuits throughout this paper are drawn with their inputs on the left and their outputs on the right. The notation  $X2:0$  denotes the three-bit number  $X2$ ,  $X1$  and  $X0$ . The least significant bit of a binary number is always designated bit 0. The numerical value of the number  $X2:0$  is given by  $x$ .*

1. *Figure 1.1* shows the circuit for a successive approximation Analog-to-Digital converter having an input voltage  $V$  and a two's-complement signed 8-bit output  $X7:0$  in the range  $-128$  to  $+127$ . One LSB of the converter is equal to  $0.2$  V and input voltages in the range  $\pm 0.1$  V are converted to the value 0.
  - (a) If the input voltage  $V$  equals  $-10.45$  V, determine the value of the output  $X7:0$ . [3]
  - (b) Give the sequence of values taken at  $X7:0$  during the process of converting an input voltage of  $-10.45$  V and give the corresponding voltages at  $W$ . [11]
  - (c) The aperture of the sampling switch is  $50$  ns and the propagation delays of the D/A converter and comparator are  $100$  ns and  $60$  ns respectively. Neglecting any propagation delays in the control logic, calculate the minimum time to convert an input voltage. You may assume that  $X7:0$  is set to the correct initial value before the conversion process begins. [3]
  - (d) If the comparator input current lies in the range  $\pm 2$   $\mu$ A, calculate the minimum value of  $C$  to ensure that the capacitor voltage changes by no more than  $\frac{1}{2}$  LSB during the conversion time found in part (c). [3]




*Figure 1.1*

2. The state of a synchronous state machine is represented by a 3-bit number  $Q2:0$ . It has two inputs,  $A$  and  $B$ , and two outputs  $X$  and  $Y$ . The state table shown in *Table 2.1* gives the next state and outputs. All state transitions and outputs are synchronized with the clock.


- (a) Draw a state diagram for the state machine using the relative positions of the states shown in *Figure 2.1*. Your diagram should indicate the state transitions and the output signals. Transitions from a state to itself should be omitted. [8]
- (b) If inputs  $A$  and  $B$  have the waveforms shown in *Figure 2.2*, determine the state sequence and the waveforms of  $X$  and  $Y$ . The clock rising edges are indicated by vertical lines and the state machine is initially in state 0. [6]
- (c) Determine Boolean expressions for  $D2$ ,  $D1$ ,  $D0$ ,  $X$  and  $Y$  that are as simple as possible. [6]

D2:0/X,Y		A,B			
		00	01	11	10
Q2:0	0	0	1		6
	1	0	1	3	
	2	0/1,0		7/1,0	6/1,0
	3		1	3	2
	4	0/0,1	1/0,1		6/0,1
	5	4	5	7	
	6	0		7	6
	7		5	7	6

*Table 2.1*

 

*Figure 2.1*

 

*Figure 2.2*

3. In a binary data transmission scheme, each transmitted bit occupies a bitcell having a duration of  $1 \mu\text{s}$ . For a logical 0, the transmitted signal is low throughout the bitcell whereas for a logical 1, a short pulse is transmitted at the start of the bitcell. In order to prevent long intervals without any transmitted pulses, the transmitter inserts an additional bitcell containing a pulse whenever four consecutive zero bits have been transmitted. *Figure 3.1* illustrates the transmission of the bit sequence 1110000101 in which the inserted bitcell is marked with \*. The frequency of *CLOCK* is 8 MHz.

- (a) The output signal, *D*, of the transmitter is connected to the receiver circuit of *Figure 3.2* which consists of a 6-bit counter and four gates. On each rising edge of *CLOCK* the counter increments unless *D* is high in which case it resets to 0. All pulses on *D* last for exactly one *CLOCK* cycle with signal transitions occurring slightly after the *CLOCK* rising edge.

Draw a timing diagram showing the data sequence of *Figure 3.1* and the resultant waveforms of *D*, *V*, *W*, *X* and *Y*. On your diagram, show the decimal value of *Q5:0* during each output pulse on *X* or *Y*. Do not attempt to show the waveform of *CLOCK* on your diagram. [10]

- (b) Modify the circuit so that output pulses are suppressed for the bitcell that immediately follows a sequence of four consecutive 0 bits. You may use any standard logic elements provided you fully specify their operation. [10]

 


Figure 3.1

 


Figure 3.2

4. In this question,  $P3:0$ ,  $Q$ ,  $R2:0$ ,  $D3:0$  and  $Y7:0$  all represent unsigned binary numbers whose numerical values are given respectively by  $p$ ,  $q$ ,  $r$ ,  $d$  and  $y$ .
- (a) The input to the “DIV” logic module shown in *Figure 4.1* is a number  $p$  in the range 0 to 9. The module outputs are the 1-bit quotient,  $q$ , and the 3-bit remainder,  $r$ , that result from dividing  $p$  by 5. Thus if  $p = 7$ , the circuit will give  $q = 1$  and  $r = 2$ .

Determine a Boolean expression for  $Q$  and hence show how the whole module may be formed using a 3-bit adder and appropriate gates. [5]

- (b) *Figure 4.2* shows a circuit that combines the “DIV” module of part (a) with a 4-bit register and an 8-bit shift register whose outputs shift in the direction  $Y0 \rightarrow Y1 \rightarrow \dots \rightarrow Y7$ . If  $p_n$  and  $y_n$  represents the values of  $p$  and  $y$  after the  $n^{\text{th}}$  clock pulse, give algebraic expressions for  $p_{n+1}$  and  $y_{n+1}$  in terms of  $p_n$  and  $y_n$  for each of the four cases [6]

- (i)  $p_n < 5$  and  $y_n < 128$
- (ii)  $p_n \geq 5$  and  $y_n < 128$
- (iii)  $p_n < 5$  and  $y_n \geq 128$
- (iv)  $p_n \geq 5$  and  $y_n \geq 128$ .

- (c) If  $p_0 = 0$  and  $y_0 = 215_{10} = 11010111_2$ , determine the values of  $p_n$  and  $y_n$  for  $n = 1, \dots, 8$ . [6]

- (d) Given that  $p_0 = 0$ , explain the relationship of  $p_8$  and  $y_8$  to the number  $y_0$ . Determine the maximum possible value of  $y_8$  and say what value of  $y_0$  will result in it. [3]

 


Figure 4.1

 


Figure 4.2

5. Figure 5.1 shows two 1-bit full adder modules, labelled  $\Sigma E$  and  $\Sigma O$ , which can be cascaded to form an  $n$ -bit adder with the two modules used respectively for the even and odd numbered bit positions. Thus a  $\Sigma E$  module is used for bit 0, the least significant bit. The propagation delays, in gate delays, of the two modules are

$\Sigma E$	$S$	$!CO$	$\Sigma O$	$S$	$CO$
$P, Q$	3	1	$P, Q$	5	2
$CI$	3	1	$!CI$	4	1

(a) If  $n$  modules are cascaded to form an  $n$ -bit adder as described above, calculate for both even and odd  $n$  the worst-case delays from any input to (i) any  $S$  output and (ii) any  $CO$  or  $!CO$  output. [5]

(b) In Figure 5.2 the two  $n$ -bit adders have the same  $P$  and  $Q$  inputs but their  $CI$  inputs are fixed at 0 and 1 respectively. Using a multiplexer, the input signal  $CIN$  is used to select between the outputs of the adders.

- (i) Show that the combined circuit acts as a single  $n$ -bit adder.
- (ii) Design the circuitry for the part of the multiplexer that generates the  $CO_{OUT}$  output.
- (iii) Using the propagation delays from part (a) above and assuming that  $n$  is even, calculate the four propagation delays for the circuit from each of  $CIN$  and  $P_0$  to each of  $CO_{OUT}$  and  $S_{n-1}$ . [9]

(c) If we denote by  $A_n$  and  $B_n$  the  $n$ -bit adders of part (a) and of Figure 5.2 respectively, determine the worst-case propagation delay from any  $P$  input to the  $S_{63}$  output for each of the 64-bit adders using (i) a single  $A_{64}$  adder and (ii) an  $A_{32}$  adder followed by a  $B_{32}$  adder. [6]

 


Figure 5.1

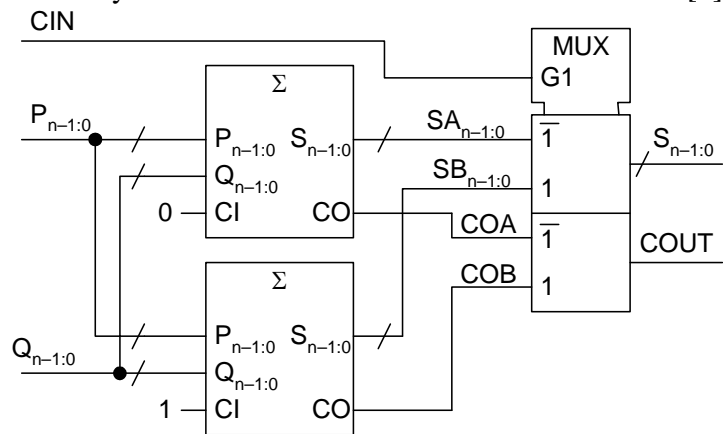



Figure 5.2

1. (a)  $x = \text{round}(V / 0.2) = \text{round}(-52.25) = -52 = 11001100$  [3]
- (b) The voltage  $W$  must be the lower threshold of the corresponding input interval and is therefore  $w = 0.2x - 0.1$ . The sequence is as follows: [11]

Clock	Step	X	X (binary)	W
0	128	0	0000 0000	-0.1
1	64	-64	1100 0000	-12.9
2	32	-32	1110 0000	-6.5
3	16	-48	1101 0000	-9.7
4	8	-56	1100 1000	-11.3
5	4	-52	1100 1100	-10.5
6	2	-50	1100 1110	-10.1
7	1	-51	1100 1101	-10.3
8	0.5	-52	1100 1100	-10.5


- (c) If we assume that X7:0 is set to 0 before the conversion starts, then we don't have to wait for the 100 ns the first time around. The minimum conversion time is therefore  $50 + 60 + 7 \times 160 = 1.23 \mu\text{s}$ . [3]
- (d)  $C = \frac{I \times \Delta t}{\Delta V} = \frac{2 \mu\text{A} \times (1.23 - 0.05) \mu\text{s}}{0.1\text{V}} = 23.6 \text{ pF}$  [3]

2. (a) The state diagram is:

 

Inputs: A,B  
Default: X=Y=0 [8]

(b) The timing diagram is:

 

[6]

(c) These are all straightforward except for D2 for which we need a Karnaugh map and find the two groups of 8 shaded below:

D2		A,B				
		00	01	11	10	
Q2:0	0	0	0	1	1	← A! $Q_0$
	1	0	0	0		
	3		0	0	0	
	2	0		1	1	
	6	0		1	1	
	7	1	1	1	1	← $Q_2 \cdot Q_0$
	5	1	1	1		
	4	0	0		1	


$D_2 = Q_2 \cdot Q_0 + A \cdot !Q_0$

$D_1 = A$   
 $X = !Q_2 \cdot Q_1 \cdot !Q_0$


$D_0 = B$   
 $Y = Q_2 \cdot !Q_1 \cdot !Q_0$

[6]

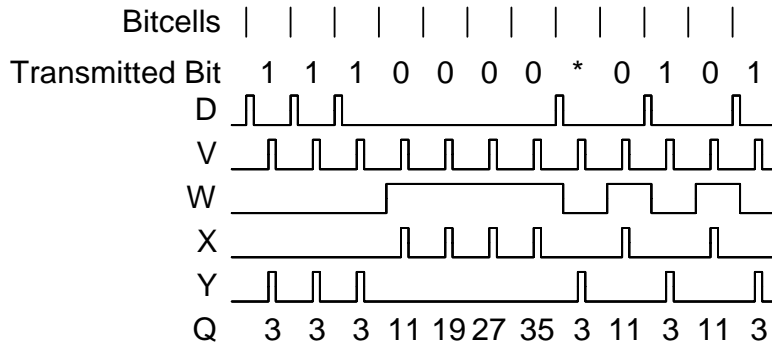3. (a) Because of the AND-gate, pulses on X or Y can only occur when  $Q_{2:0} = 011_2$  which means that that  $Q_{5:0} = 3 + 8k$  for some integer  $k$ . The falling edges of W occur when the counter resets to zero which is immediately at the end of the input pulses. Pulses on V occur midway between the input pulses. In the timing diagram below, Q is the value of  $Q_{5:0}$ . [10]




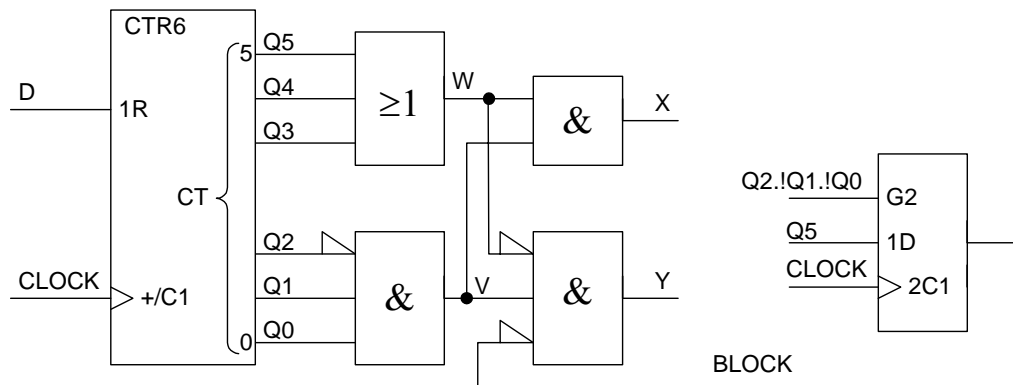- (b) We need to remember that we have had four consecutive zeros and then suppress the next pulse. The easiest way to do this is to use a flipflop with a clock enable input to remember the value of  $Q_5$  at the last pulse: [10]





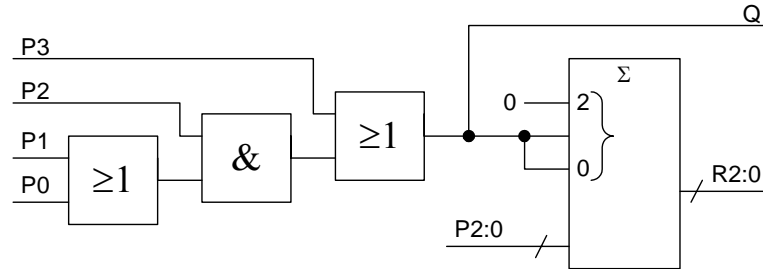4. (a)  $Q = (p \geq 5) = P3 + P2 \cdot (P1 + P0)$  and whenever  $Q=1$ , we need to subtract 5 (= add 3 modulo 8) from  $P$  to give  $R$ . hence:



[5]

- (b)  $y_{n+1} = 2y_n + q_n - 256(y_n \geq 128) = 2y_n + (p_n \geq 5) - 256(y_n \geq 128)$  and  
 $p_{n+1} = 2r_n + (y_n \geq 128) = 2p_n - 10(p_n \geq 5) + (y_n \geq 128)$

Hence we get:

- (i)  $p < 5, y < 128$        $y_{n+1} = 2y_n$  and  $p_{n+1} = 2p_n$   
 (ii)  $p \geq 5, y < 128$        $y_{n+1} = 2y_n + 1$  and  $p_{n+1} = 2p_n - 10$   
 (iii)  $p < 5, y \geq 128$        $y_{n+1} = 2y_n - 256$  and  $p_{n+1} = 2p_n + 1$   
 (iv)  $p \geq 5, y \geq 128$        $y_{n+1} = 2y_n - 255$  and  $p_{n+1} = 2p_n - 9$       [6]

- (c) Using the above expressions, we can generate the following table:      [6]

clock	$y$	$y$ (binary)	$p$	$q$	$r$	$d$
0	215	1101 0111	0	0	0	1
1	174	1010 1110	1	0	1	3
2	92	0101 1100	3	0	3	6
3	184	1011 1000	6	1	1	3
4	113	0111 0001	3	0	3	6
5	226	1110 0010	6	1	1	3
6	197	1100 0101	3	0	3	7
7	138	1000 1010	7	1	2	5
8	21	0001 0101	5	1	0	0

- (d) The numbers  $y_8$  and  $p_8$  are the quotient and remainder after dividing  $y_0$  by 10. The maximum possible value of  $y_0$  is 255 which will result in  $y_8 = 25$  and  $p_8 = 5$ . This is therefore the maximum value of  $y_8$ .      [3]

5. (a) We get one delay from each stage except the last which has more:

[5]


	S	CO!/CO
n even	n+3	n
n odd	n+2	n

(b) (i) If CIN=0 then the outputs come from the top adder which has CI=0. Similarly for CIN=1.

[2]

(ii) This is a standard multiplexer:

[3]

 

(iii) The multiplexer adds 2 onto the delays from P but reduces the delay from CIN to only 3 (independent of n).

[4]

	S	COUT
CIN	3	3
P0	n+5	n+2

(c) (i)  $P0 \rightarrow S63 = 67$

[2]

(ii)  $\max(P0 \rightarrow C31 \rightarrow S63, P32 \rightarrow S63)$   
 $= \max(32+3, 32+5) = \max(35, 37) = 37$

[4]