

# Home Lab 2 Explained


## Electronic Circuits

Peter Cheung  
Department of Electrical & Electronic Engineering  
Imperial College London

URL: [www.ee.ic.ac.uk/pcheung/teaching/DE1\\_EE/](http://www.ee.ic.ac.uk/pcheung/teaching/DE1_EE/)  
E-mail: [p.cheung@imperial.ac.uk](mailto:p.cheung@imperial.ac.uk)



# Experimental Setup

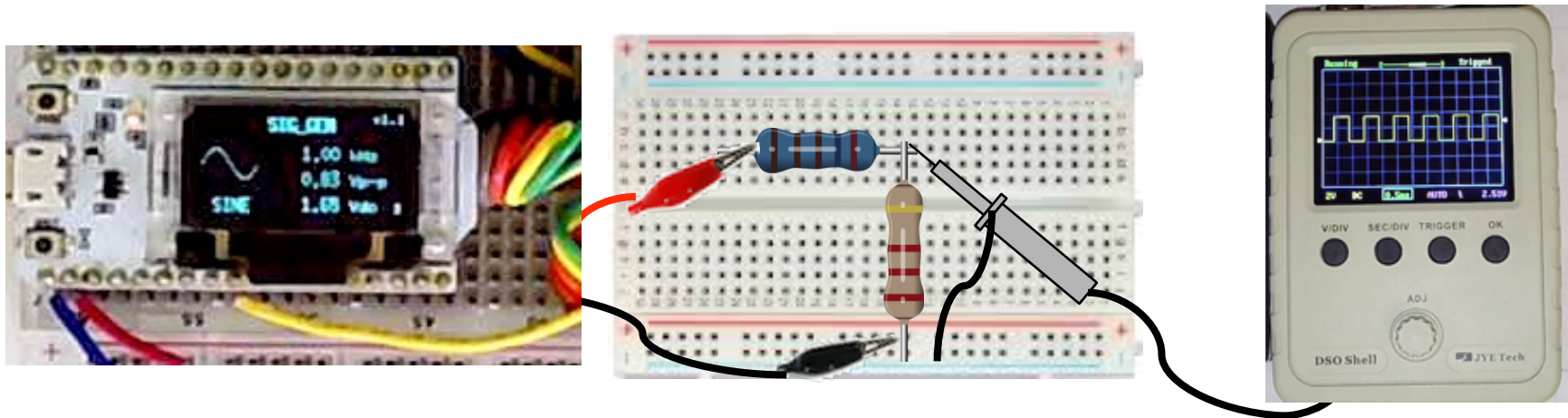

- ◆ You will be using the function generator to produce a digital waveform or a sine wave as the voltage source at different frequencies to drive your circuits.
- ◆ You will build your circuits on the breadboard.
- ◆ You will measure the voltages on your circuits using the scope or using a multimeter.
- ◆ You may want to use male end of ribbon cable to loosen contacts before inserting a component or a hookup wire.

# Task 1: Calibrating the DC voltage source


---

- ◆ Analogue signals: DC, SINE, Exponential, NOISY
- ◆ Digital signals: CLOCK, PWM, UARTModern digital circuits use lower voltages. We will be using digital circuits operating at 3.3v level.
- ◆ In Task 1, you calibrate the DC source by finding out the measured voltage vs the voltage settings:

Voltage Setting	3.0V	2.5V	2.0V	1.5V	1.0V	0.5V
Measured voltage	2.86					
Error in % FS	-4%					

Measured voltage	3.0V	2.5V	2.0V	1.5V	1.0V	0.5V
Voltage Setting	3.18					


# Task 2: Source resistance

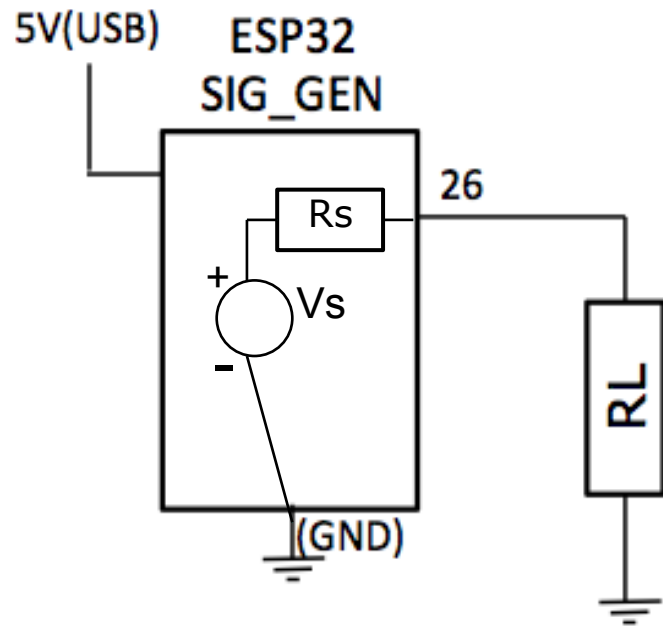

<u>Vs</u> (measured)	V setting	10k	1k	100	68
3.0	3.18				1.93
2.0	2.09				1.7
1.0	1.02				1.0


<u>Vs</u>	<u>V<sub>measured</sub></u>	<u>I<sub>out</sub></u>	<u>Rs</u> ( $\Omega$ )
3.0	1.93	28.4mA	37.7
2.0			
1.0			

# Task 3: Voltage Divider Circuit

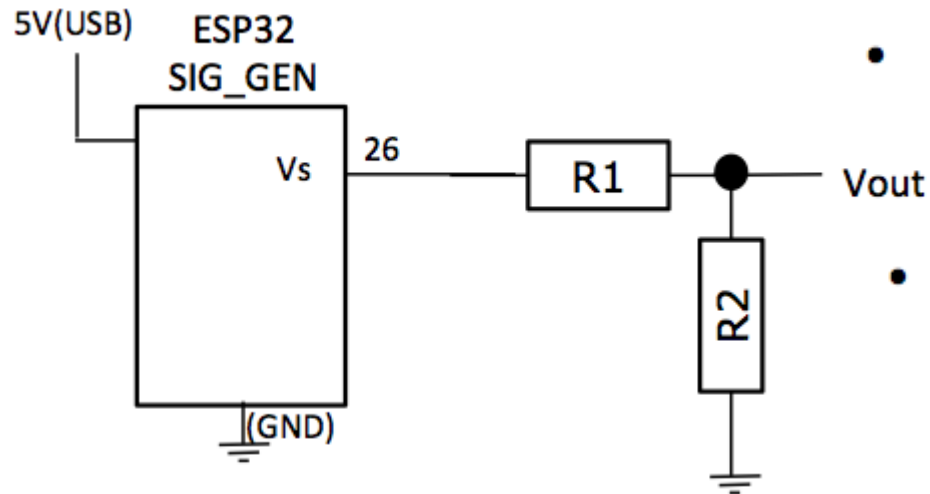


- Set  $V_s$  to 3V. With  $R_1 = R_2 = 10k$ , predict  $V_{out}$ , and confirm with measurement.
  - Substitute  $R_2$  with a 20k resistor. What do you expect  $V_{out}$  to be? Confirm with measurement.
- 
- Now apply a sine wave at 1kHz, and the maximum pk-pk voltage from SIG\_GEN and measure  $V_{out}$ . Confirm that the voltage divider works for both dc and ac signals.

# Task 4: Thevenin Equivalent Circuit

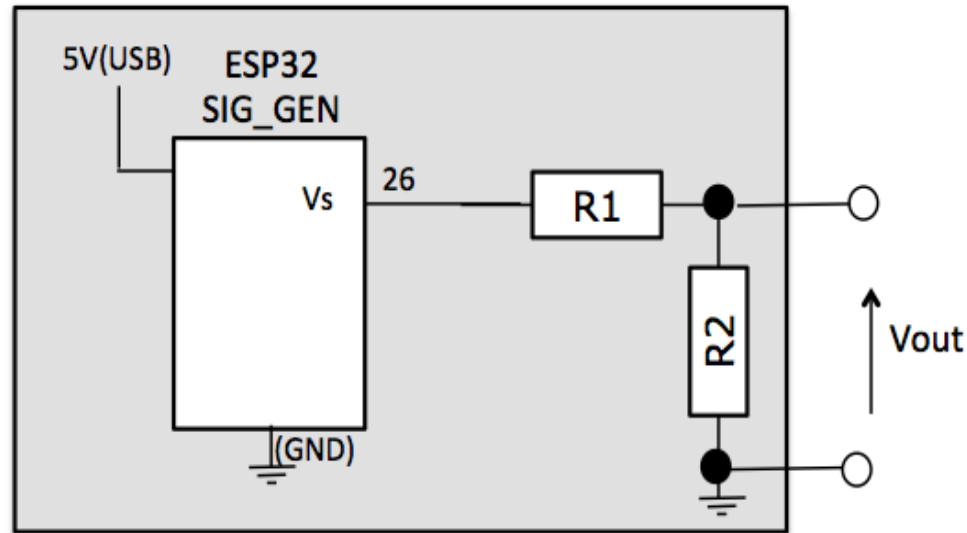

- For the circuit shown here, assume that  $R_1 = 10k$ ,  $R_2 = 20k$ . Derive the Thevenin equivalent network for the circuit inside the grey box. (See below).
- Set  $V_s = 2V$ . Confirm your prediction by measuring the  $V_{th}$  as the open-circuit voltage, and work out the value of  $R_{th}$  by measuring the short-circuit current. (Note: you can measure


# Task 5: Complex Resistor Network

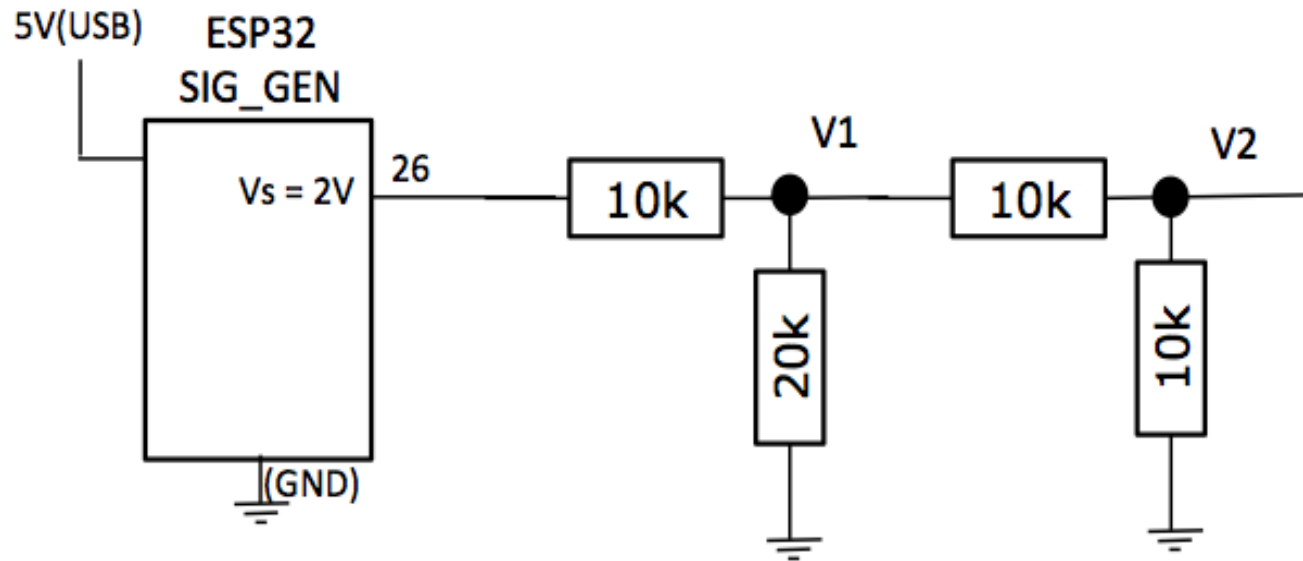

- With  $V_s = 2V$ , measure the value of V1 and V2. Verify this with your calculation to make that this is as you expected.
- The network is the basic for DAC, and is known as a R-2R ladder network. How would you add to this circuit so that a third voltage V3 make sure that this circuit has a third stage and continues the same voltage dividing patent? This would be a good topic for discussion among your team.

# Task 6: RC circuits & Exponential signal


---

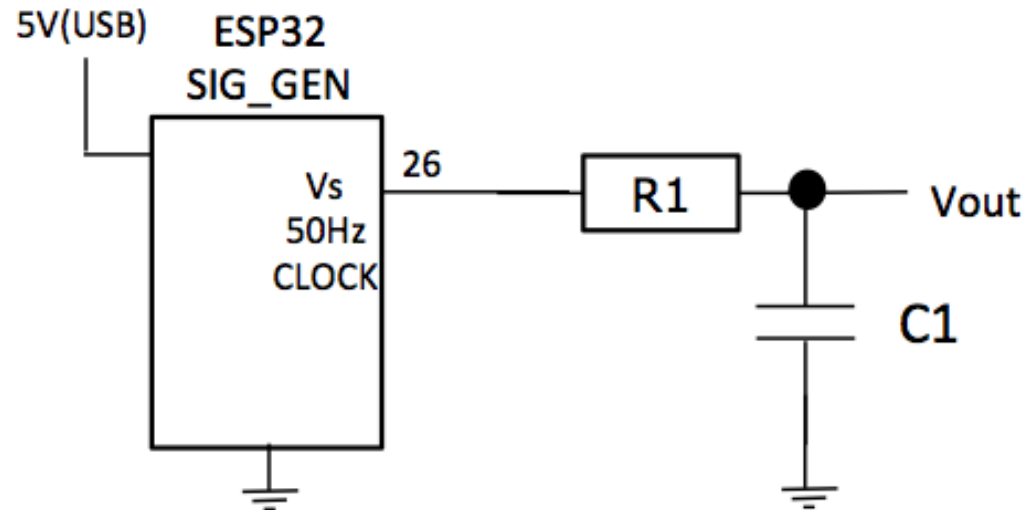


- Construct the following circuit using  $R1 = 10k$  and  $C1 = 0.01\mu F$ . Use SIG\_GEN to generate a 50Hz CLOCK signal. Measure Vout using the scope. Explain the measured waveform. What is the time constant of this RC network, both in theory and in measurement? You must measure the time-constant both for Vs going from low to high (rising step signal), and from high to low (falling step signal).
- Change  $R1 = 1k$  and  $C1 = 0.1\mu F$ , and repeat your measurement. What conclusion can you draw from this?



# Task 7: RC circuits – lowpass filter

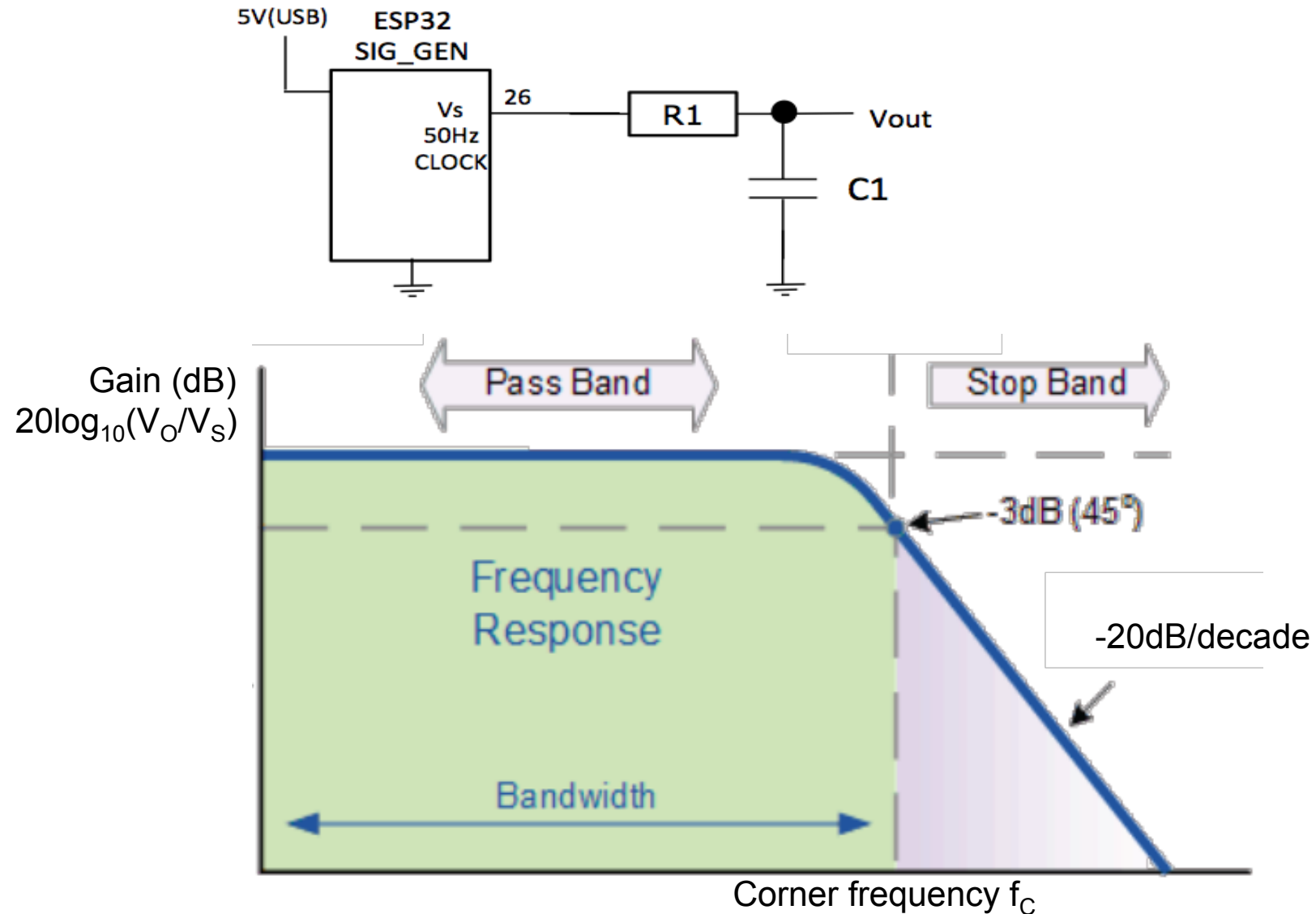


# Task 8: PWM signal & lowpass filter

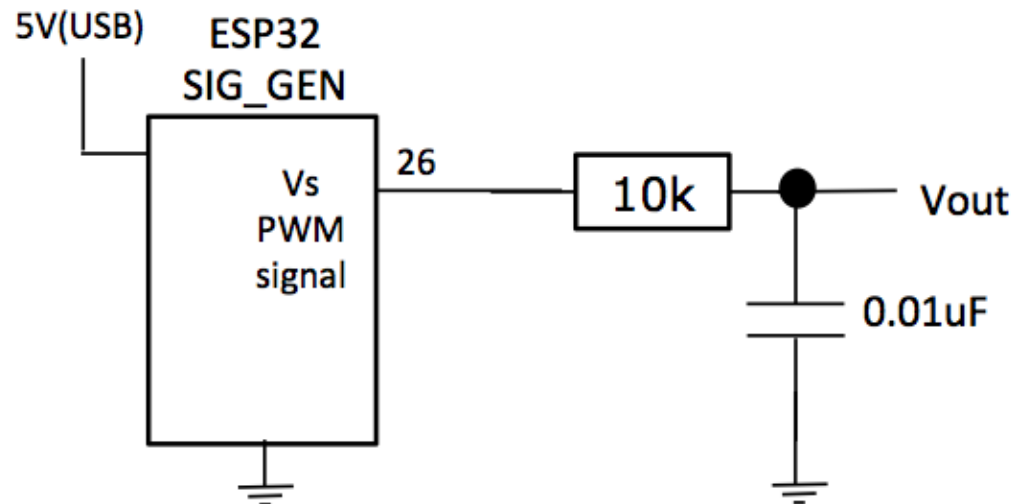


- Select PWM signal at 1kHz and duty cycle of 50% on SIG\_GEN, and measure the output of the RC circuit with  $R1 = 10k$ , and  $C1 = 0.01\mu F$ .
- Increase the frequency to 10kHz and then 100kHz. Explain your observation of the output voltage.
- Using 100kHz PWM signal, adjust the duty cycle from 0% to 100% in steps of 10. Use the multimeter to measure the output voltage. Plot the curve  $V_{out}$  (dc) vs Duty Cycle. Explain the results.

# Task 9: PWM & LED brightness

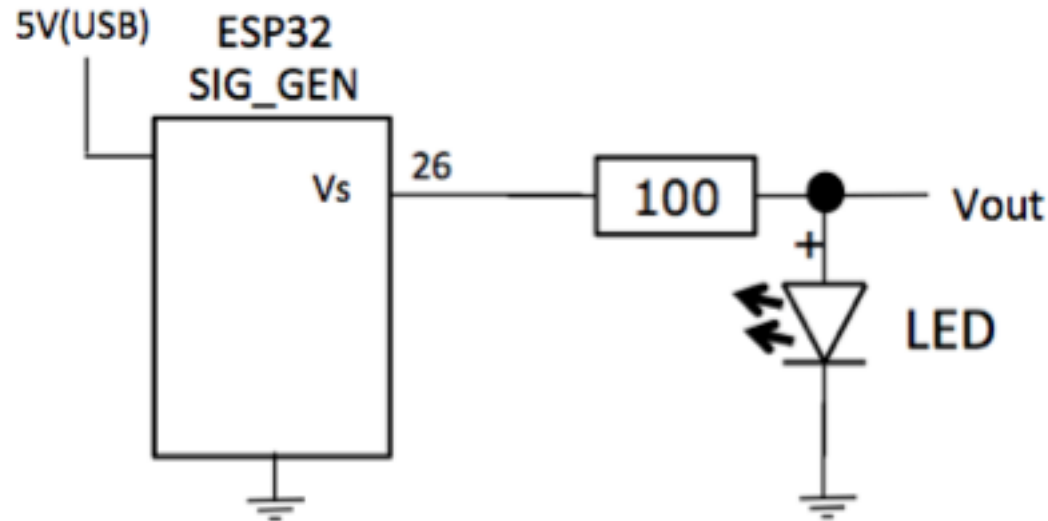

- Set SIG\_GEN to provide a DC voltage between 0 to 3.3V. Measure  $V_{out}$  with a multimeter and determine the minimum voltage and current that the LED is lit up.
- Now drive the LED with a PWM signal at, say 10kHz and observe the output light intensity when the duty cycle is changed from 0% to 100%.
- Change the PWM signal frequency over the frequency range of 20Hz to (say) 20kHz and comment on your observation.
- We see the light intensity varied because the brightness is the result of some lowpass filtering (smoothing) effect. However, we did not use a RC circuit. What is the lowpass filter of the system?

# Task 10: CR circuit & DC blocking

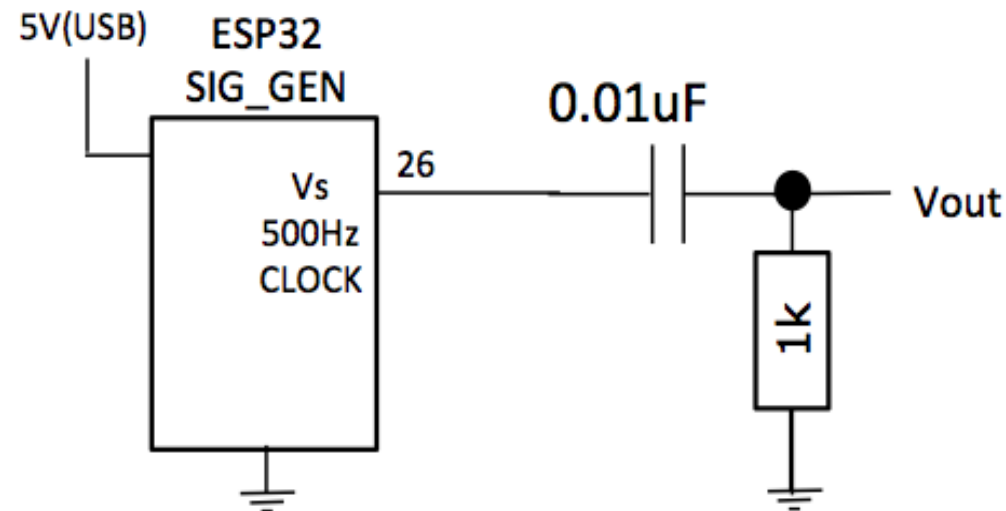

- Apply to this circuit a clock signal at 500Hz. Measure  $V_{out}$  using the scope and comment on the results.
- Note that the wave form you measure is identical no matter whether you set the scope to DC or AC mode. Why? (The sliding switch to select scope measure mode is on the top of the instrument.)
- Change the frequency to 30kHz. Observe and comment on the results.