

Topic 2


Current, Voltage and Power

Prof Peter Cheung
Dyson School of Design Engineering
Imperial College London

URL: www.ee.ic.ac.uk/pcheung/teaching/DE1_EE/
E-mail: p.cheung@imperial.ac.uk




What will you learn on this module?

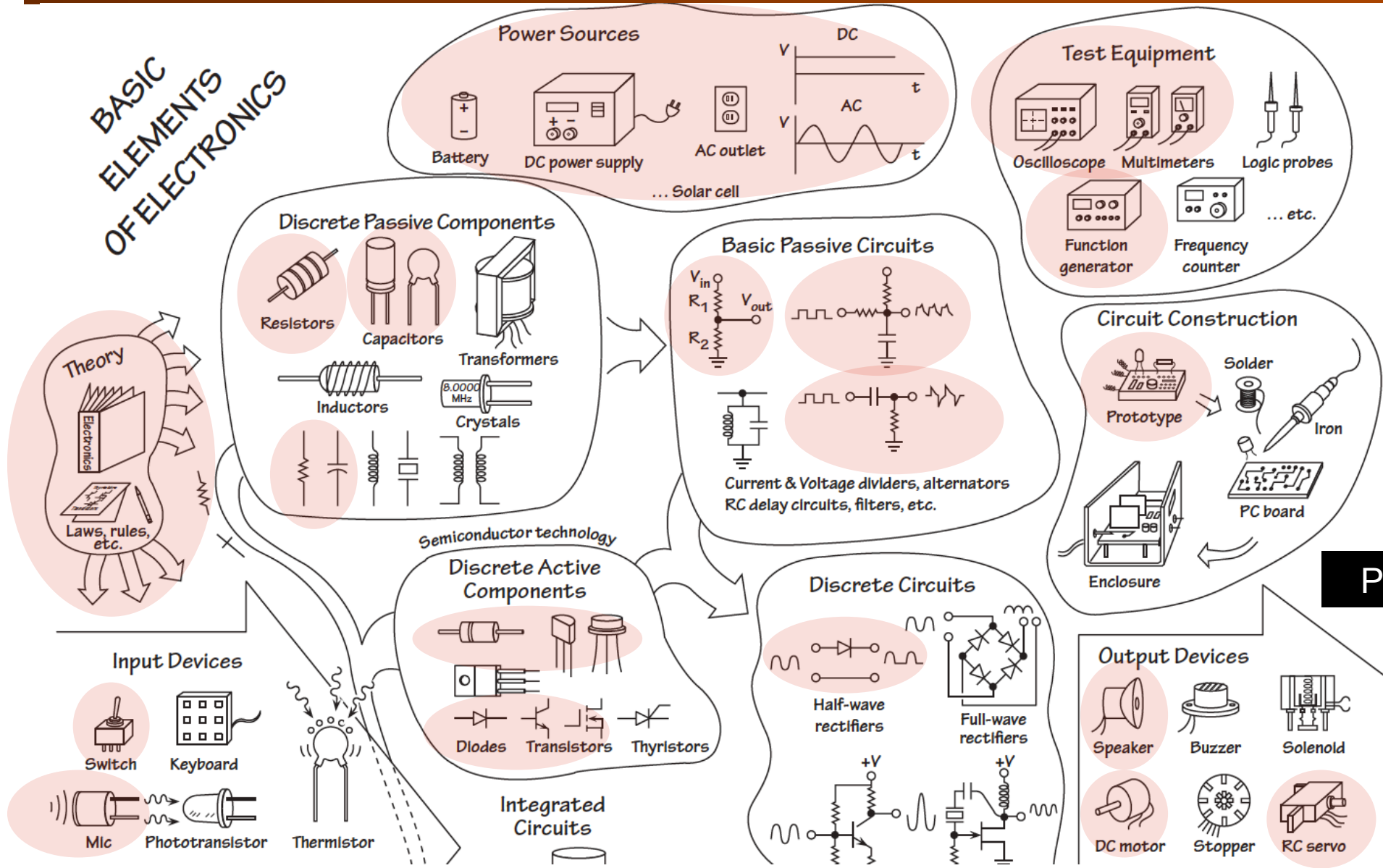

P2


What will you learn on this module?

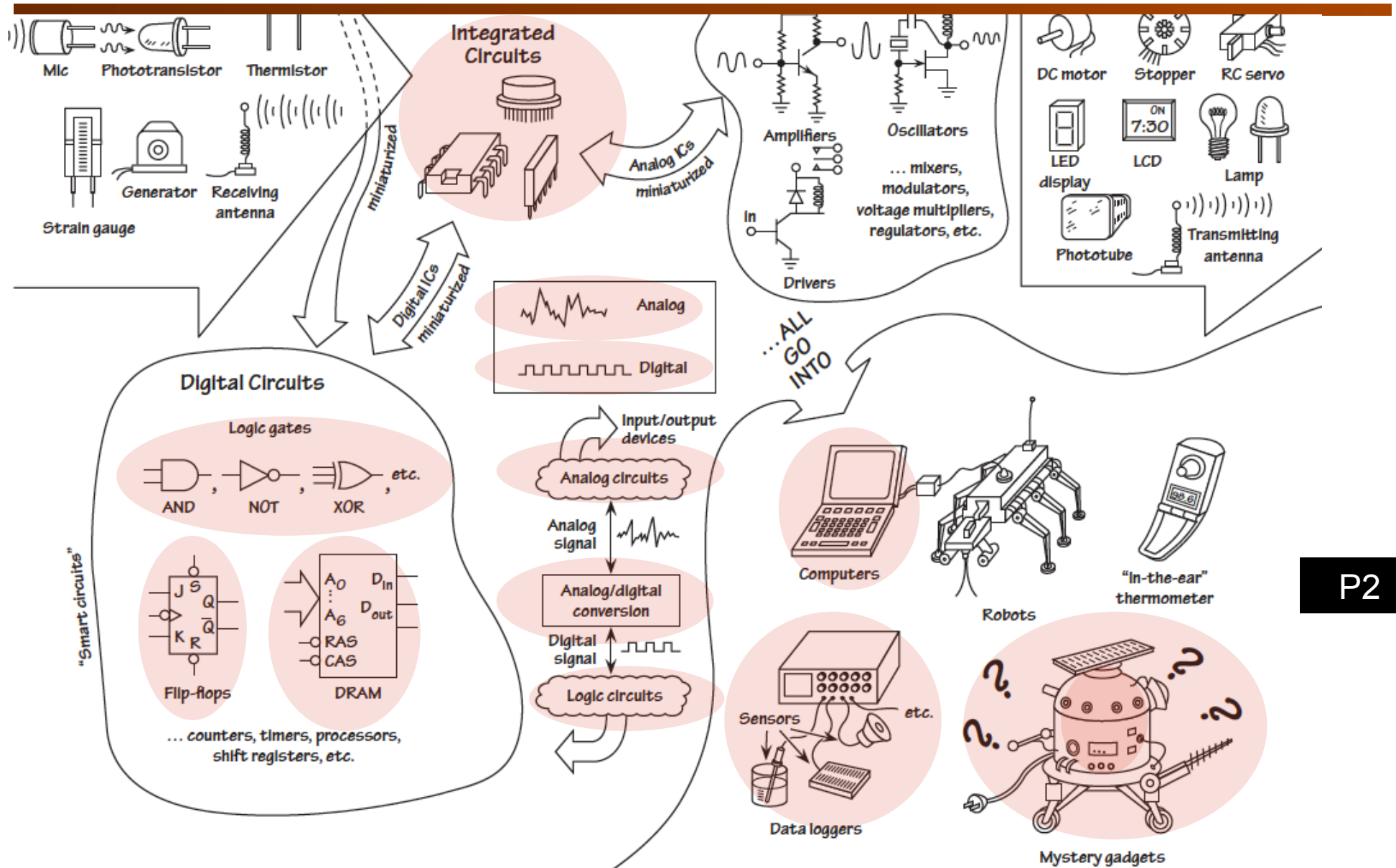


P2

What are electrical circuits?

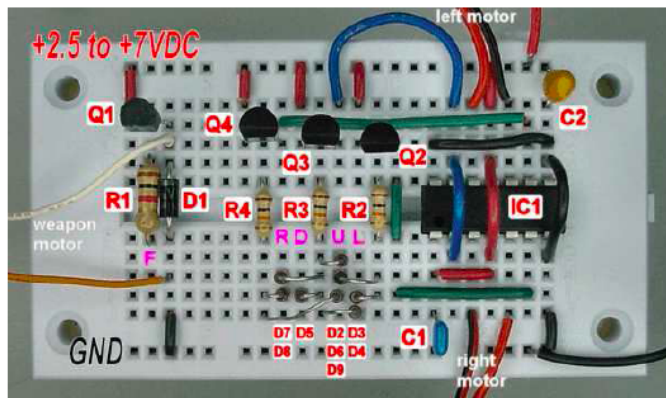
- ◆ A **circuit** consists of electrical or electronic components interconnected with metal wires.
- ◆ Every electrical or electronic device is a circuit.



Breadboard

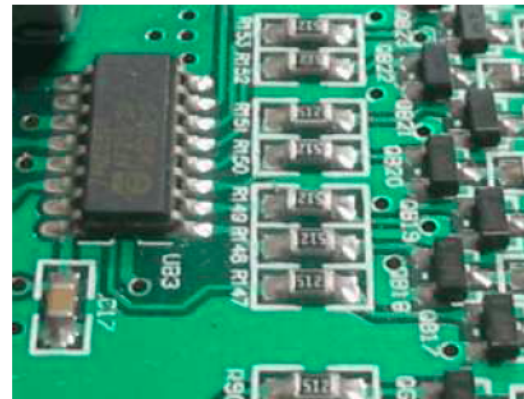

Printed

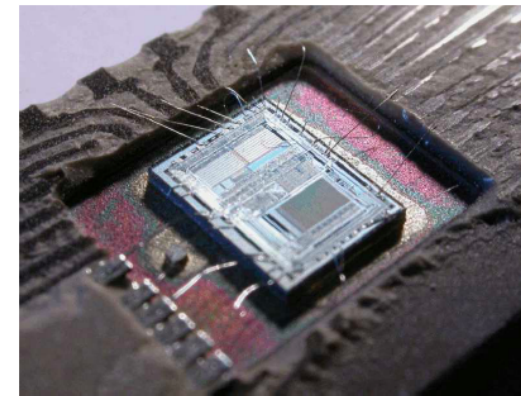


Integrated

- ◆ The function of the circuit is determined by which components are used and how they are interconnected: the physical positioning of the components usually has hardly any effect.


Circuit Diagrams

A **circuit diagram** shows the way in which the components are connected.

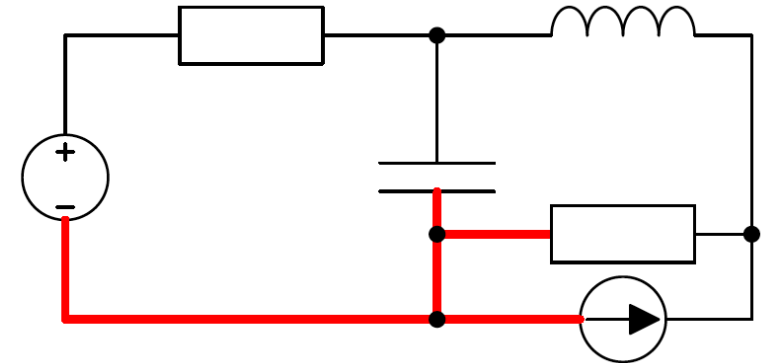- ◆ Each component has a special symbol
- ◆ The interconnecting wires are shown as lines



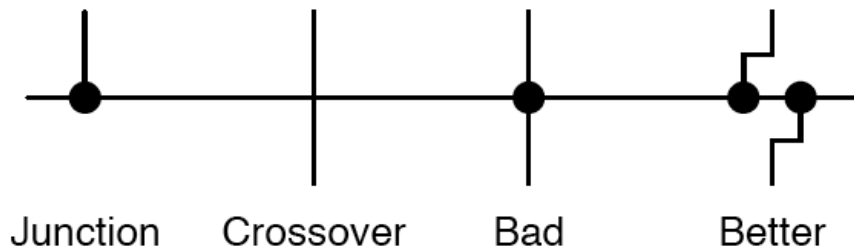A **node** in a circuit is all the points that are connected together via the interconnecting wires. One of the four nodes in the diagram is coloured red.
Assumption: Interconnecting wires have zero resistance so everywhere along a node has the same voltage.



Indicate three meeting wires with a • and crossovers without one.

Avoid having four meeting wires in case the • disappears; stagger the wires instead.

Electrical charge

- ◆ **Charge** is an electrical property possessed by some atomic particles.
- ◆ Charge is measured in Coulombs (abbreviated C).
- ◆ An electron has a charge $-1.6 \times 10^{-19}\text{C}$, a proton $+1.6 \times 10^{-19}\text{C}$.
- ◆ Unlike charges attract; like charges repel.
- ◆ The force is **fantastically** huge:

Two people 384,000 km apart
Each with 1% extra electrons
Force = 2×10^{-8} N
= 360,000 × their weight




- ◆ **Consequence:** Charge never accumulates in a conductor: everywhere in a conducting path stays electrically neutral at all times.

Electrical Current

- ◆ **Current** is the flow of charged particles past a measurement boundary.
- ◆ Using an ammeter, we measure current in Ampères (usually abbreviated to Amps or A): $1 \text{ A} = 1 \text{ C/s}$.
- ◆ **Analogy**: the flow of water in a pipe or river is measured in litres per second.
- ◆ The arrow in a circuit diagram indicates the direction we choose to measure the current:

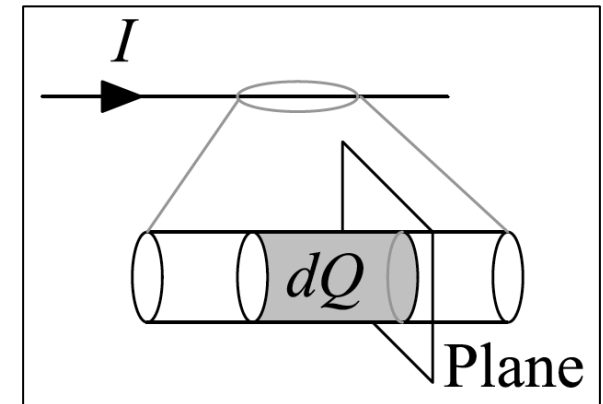$I = +1 \text{ A} \Rightarrow 1 \text{ C}$ of +ve charge passes each point every second in the direction of the arrow (or else 1 C of -ve charge in the opposite direction)




$I = -1 \text{ A} \Rightarrow 1 \text{ C}$ of +ve charge in the direction **opposite** to the arrow.

- ◆ Average electron velocity is surprisingly slow (e.g. 1 mm/s) but (like a water pipe) the signal travels much faster.
- ◆ In metals the charge carriers (electrons) are actually -ve: **in this course you should ignore this always.**

Potential Energy

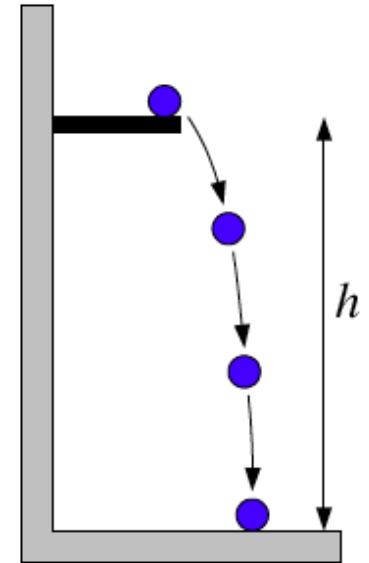- ◆ When a ball falls from a shelf, it loses **potential energy** of mg , or, equivalently, gh per kg .
- ◆ The potential energy per kg of any point on a mountain range is equal to gh where h is measured relative to an equipotential reference surface (e.g. the surface of a lake).



The potential energy difference between any two points is the energy needed to move 1 kg from one point to the other.

The potential energy difference **does not depend on the route** taken between the points.


The potential energy difference **does not depend on your choice of reference** surface (e.g. lake surface or sea level).



Voltage

- ◆ The **electrical potential difference** (or **voltage difference**) between any two nodes in a circuit is the energy per coulomb needed to move a small +ve charge from one node to the the other.
- ◆ We usually pick one of the nodes as a reference and define the voltage at a node to be the voltage difference between that node and the reference.

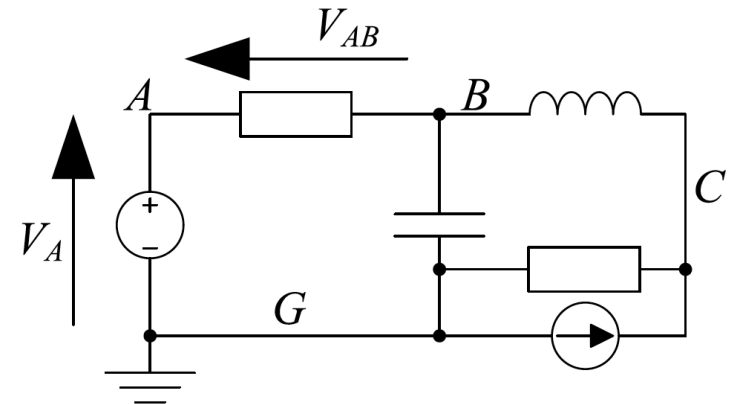The four nodes are labelled: A , B , C , G .
We have chosen G as the reference node;
indicated by the “ground” symbol.





- ◆ The potential difference between A and the ground reference, G , is written V_A and is also called “the voltage at A ”.
- ◆ The potential difference between A and B is written as V_{AB} and shown as an arrow pointing towards A . This is the energy per coulomb in going from B to A and satisfies $V_{AB} = V_A - V_B$. (**Different from vectors**)
- ◆ Easy algebra shows that $V_{AB} = -V_{BA}$ and that $V_{AC} = V_{AB} + V_{BC}$.

P9-12



Resistors – the link between current and voltage

- ◆ A **resistor** is made from a thin strip of metal film deposited onto an insulating ceramic base.
- ◆ The **characteristic** of a component is a graph showing how the voltage and current are related. We always choose the current and voltage arrows in opposite directions.
- ◆ For a resistor, $I \propto V$ and $\frac{V}{I} = R$ its **resistance** which is measured in Ohms (Ω). **This is Ohm's Law**. Sometimes it is more convenient to work in terms of the **conductance**, $G = \frac{1}{R} = \frac{I}{V}$ measured in Siemens (S).
- ◆ The graph shows the characteristic of a 12.5Ω resistor. The gradient of the graph equals the conductance $G = 80 \text{ mS}$. **Alternative zigzag symbol.**

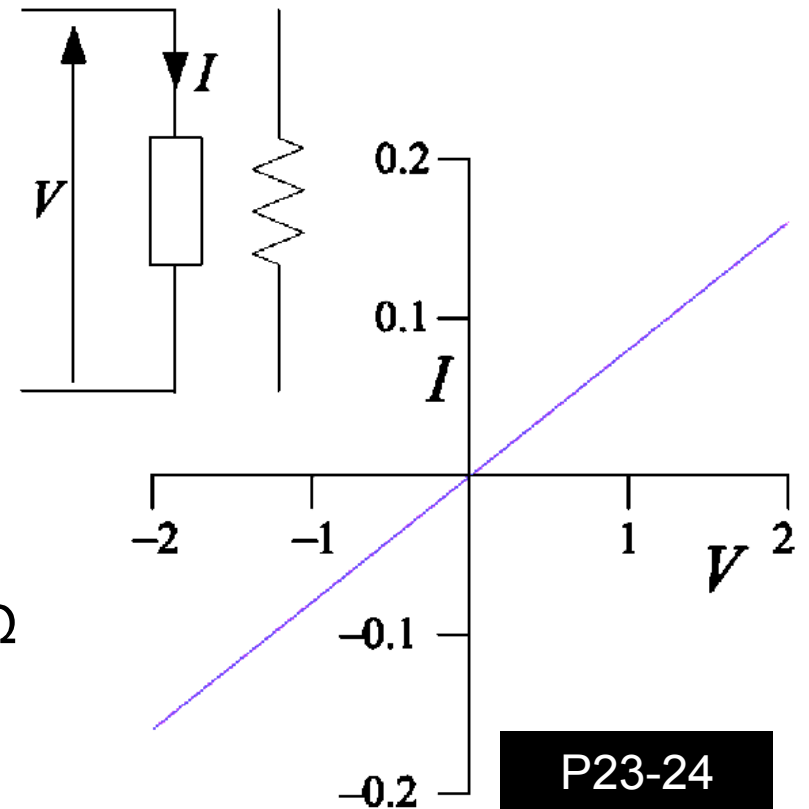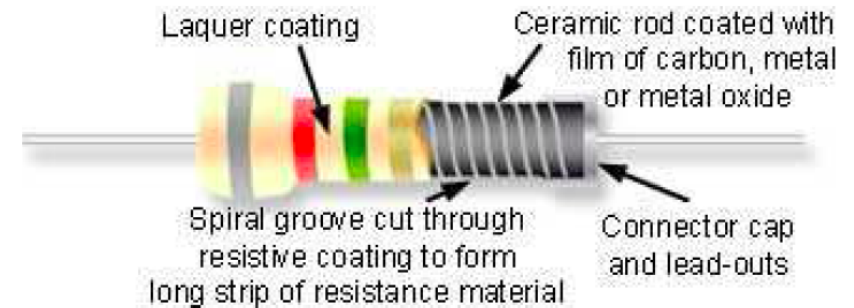

Cause and Effect

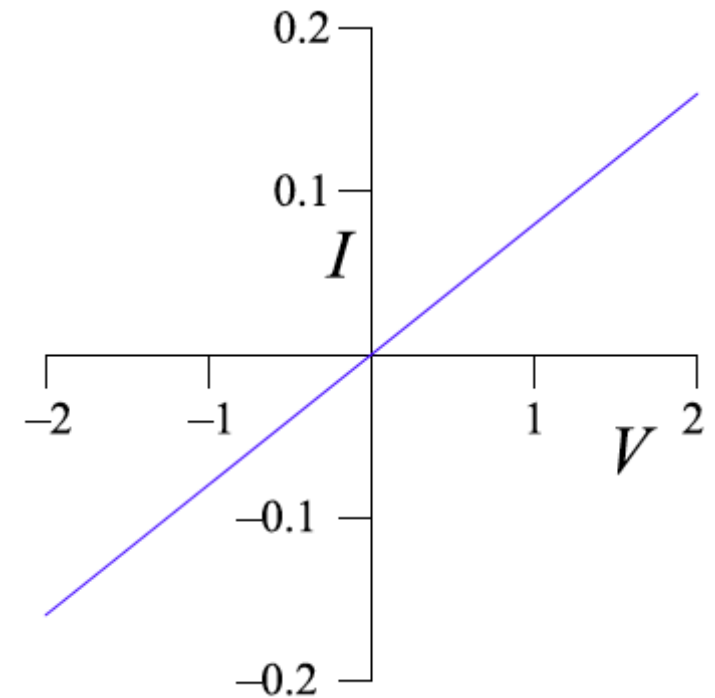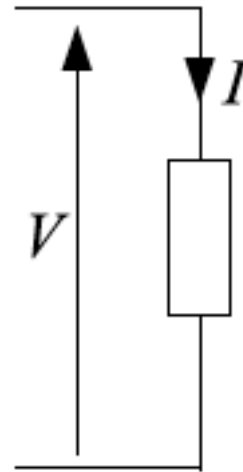Ohm's law relates the voltage drop across a resistor to the current flowing in it.






- ◆ If the voltage, V , is fixed elsewhere in the circuit, it is convenient to think that V **causes** the current I to flow.
- ◆ If the current, I , is fixed elsewhere in the circuit, it is more convenient to think that V is **caused by** the current I flowing through the resistor.
- ◆ Neither statement is “more true” than the other. It is perhaps truer to say that I and V are **constrained to satisfy** $V = I \times R$.

Resistor Power Dissipation

- ◆ Gravitational potential energy, mgh , lost by a falling object is transformed into kinetic energy or heat.

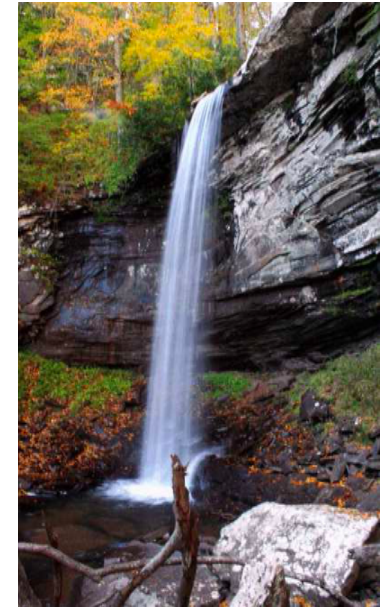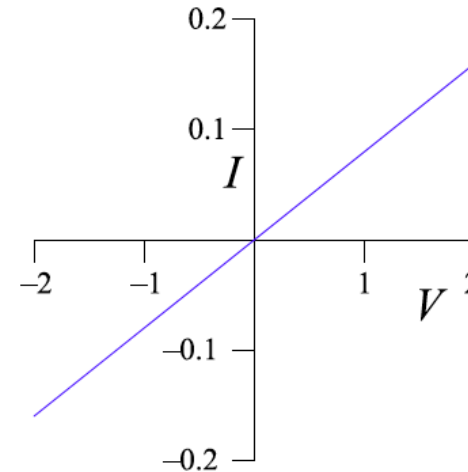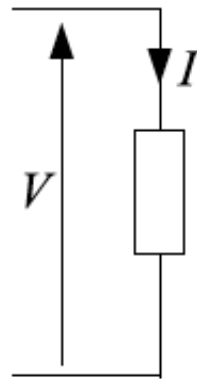Current in a resistor always flows from a high voltage (more positive) to a low voltage (more negative).




- ◆ When current flows through a resistor, the electrical potential energy that is lost is transformed into heat.
- ◆ The power dissipated as heat in a resistor is equal to $V \times I$ Watts (W). 1 Watt equals one Joule of energy per second. Since V and I always have the same sign (see graph) the **power dissipation is always positive**.
- ◆ **Any component:** $P = V I$ gives the power absorbed by any component.
- ◆ **For a resistor only** $\frac{V}{I} = R \Rightarrow P = VI = \frac{V^2}{R} = I^2 R$.

P31-33


Voltage and Current Sources

- ◆ Energy in an electrical circuit is supplied by voltage and current sources

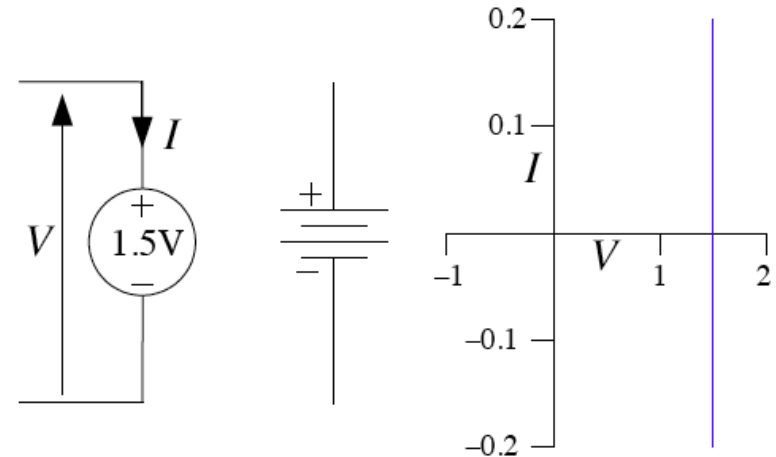An **ideal voltage source** maintains the same value of V for all currents. Its characteristic is a vertical line with infinite gradient. There are two common symbols:



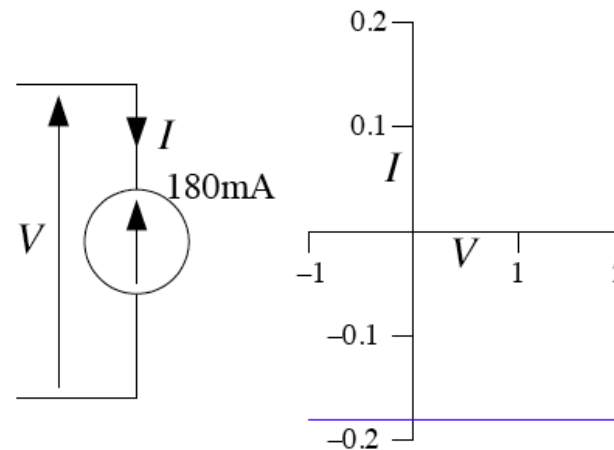An **ideal current source** maintains the same value of I for all voltages. Its characteristic is a horizontal line with zero gradient. Notice that I is negative.



- ◆ If the source is **supplying** electrical energy to a circuit, then $VI < 0$.
- ◆ However, when a rechargeable battery is charging, $VI > 0$.

P31-33


Power Conservation

- ◆ In any circuit some circuit elements will be supplying energy and others absorbing it. At all times, the power absorbed by all the elements will sum to zero.

- ◆ The circuit has two nodes whose potential difference is 10 V.

- ◆ Ohm's Law: $I = \frac{V}{R} = 0.01 \text{ A}$

- ◆ **Power absorbed by resistor:**

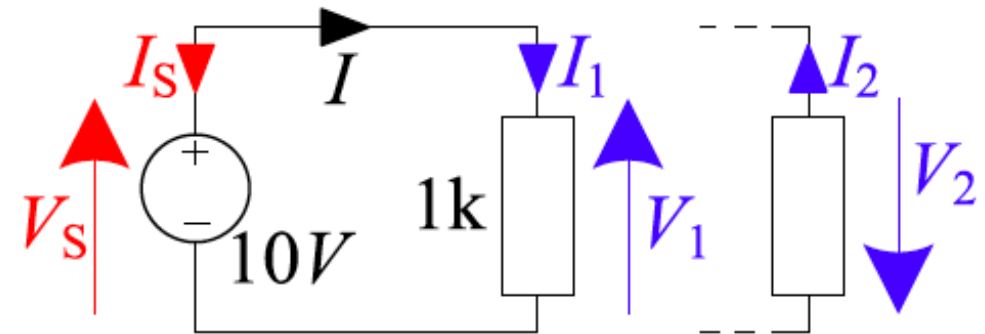

$$P_R = V_1 \times I_1 = (+10) \times (+0.01) = +0.1 \text{ W}$$

- For Ohm's law or power dissipation, V and I can be measured either way round but **must** be in opposite directions.

$$P_R = V_2 \times I_2 = (-10) \times (-0.01) = +0.1 \text{ W}$$

- ◆ **Power absorbed by voltage source:**

$$P_S = V_S \times I_S = (+10) \times (-0.01) = -0.1 \text{ W}$$

- ◆ **Total power absorbed by circuit elements:**

$$P_S + P_R = 0$$

Summary

- ❑ Circuits and Nodes
- ❑ Charge, Current and Voltage
- ❑ Resistors, Voltage Source and Current Sources
- ❑ Power Dissipation and Power Conservation