

Topic 3

Resistors & Resistor Circuits


Prof Peter Y K Cheung
Dyson School of Design Engineering

URL: www.ee.ic.ac.uk/pcheung/teaching/DE1_EE/
E-mail: p.cheung@imperial.ac.uk



Resistor parameters and identification

- ◆ Resistors are usually colour coded with their values and other characteristics as shown here.
- ◆ They also come in different tolerances (e.g. $\pm 0.1\%$ to $\pm 10\%$).
- ◆ Other important parameters are:
 - Power rating (in Watts)
 - Temperature coefficient in parts per million (ppm) per degree C
 - Stability over time (also in ppm)
 - Inductance (don't worry about this for now)
- ◆ Resistors can be made of different materials: carbon composite (most common), enamel, ceramic etc.

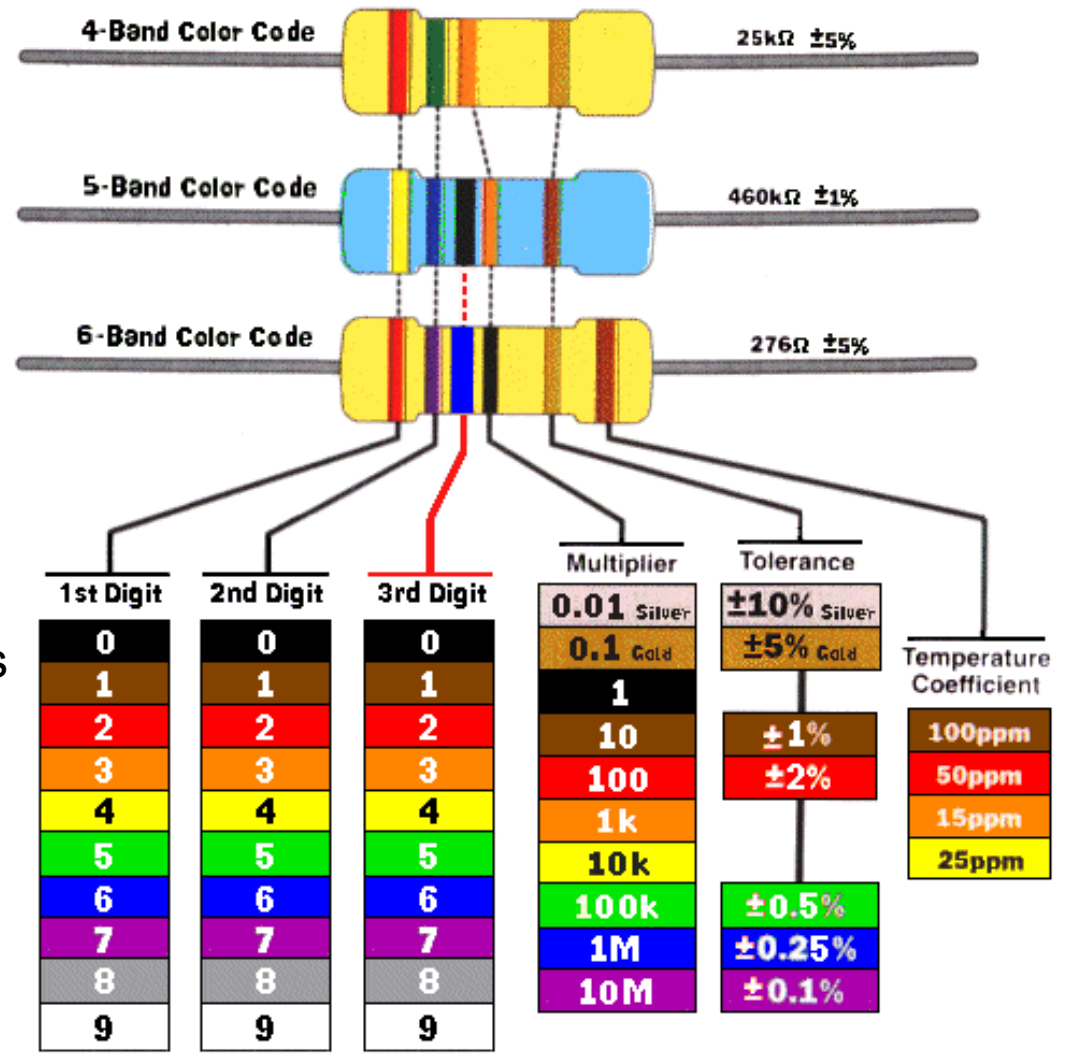

Resistor – Preferred values

- ◆ In theory, resistor values is a continuous quantity with infinite different values.
- ◆ In reality, resistor as a component exists within some tolerance (say, $\pm 5\%$ is common)
- ◆ Therefore there is NO reason to provide more than selected number of different resistor values for a given tolerance.
- ◆ The standard “preferred values” for resistors are given in this table for $\pm 5\%$ (most common), $\pm 10\%$ and $\pm 20\%$, respectively designated as the E24, E12, E6 series.
- ◆ For example, if you need a $31.3\text{k}\Omega$ resistor with tolerance of $\pm 10\%$, you could use a $30\text{k}\Omega$ E24 resistor ($\pm 5\%$) instead and still stay within the allowable tolerance.
- ◆ Therefore, when computing solutions resistor values for electronic circuits, it is silly to use precision with many digits.

E6 (20%)	E12 (10%)	E24 (5%)
10	10	10
		11
	12	12
15	15	15
		16
	18	18
22	22	22
		24
	27	27
33	33	33
		36
	39	39
47	47	47
		51
	56	56
68	68	68
		75
	82	82
		91

Units and Multipliers

Quantity	Letter	Unit	Symbol
Charge	Q	Coulomb	C
Conductance	G	Siemens	S
Current	I	Amp	A
Energy	W	Joule	J
Potential	V	Volt	V
Power	P	Watt	W
Resistance	R	Ohm	Ω


Value	Prefix	Symbol
10^{-3}	milli	m
10^{-6}	micro	μ
10^{-9}	nano	n
10^{-12}	pico	p
10^{-15}	femto	f

Value	Prefix	Symbol
10^3	kilo	k
10^6	mega	M
10^9	giga	G
10^{12}	tera	T
10^{15}	peta	P

Series and Parallel


Series: Components that are connected in a chain so that the same current flows through each one are said to be *in series*.

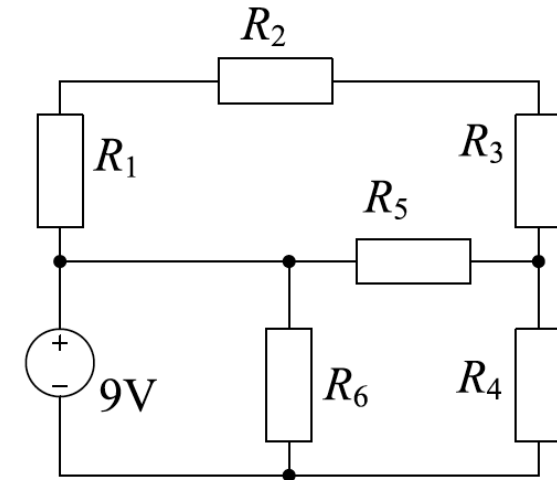- ◆ R_1 , R_2 , R_3 are in series and the **same current** always flows through each.
- ◆ Within the chain, each internal node connects to only two branches.
- ◆ R_3 and R_4 are **not** in series and do not necessarily have the same current.



Parallel: Components that are connected to the same pair of nodes are said to be in parallel .

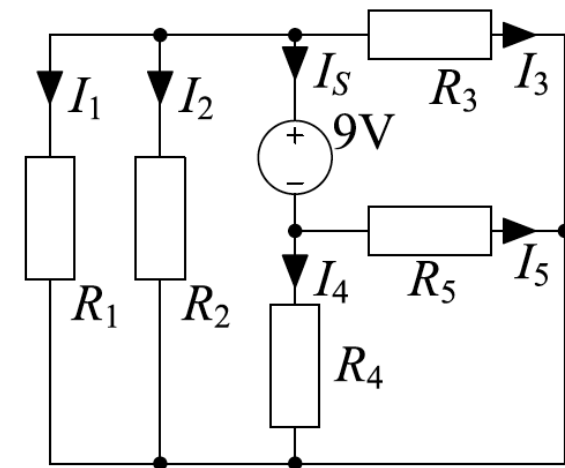- ◆ R_1 , R_2 , R_3 are in parallel and the **same voltage** is across each resistor (even though R_3 is not close to the others).
- ◆ R_4 and R_5 are also in parallel.




P52-53

Series Resistors: Voltage Divider

$$\begin{aligned} V_x &= V_1 + V_2 + V_3 \\ &= I R_1 + I R_2 + I R_3 \\ &= I(R_1 + R_2 + R_3) \end{aligned}$$
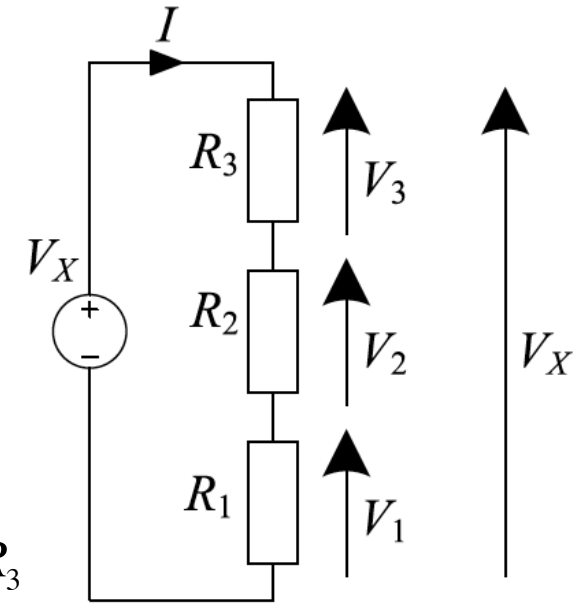
$$\begin{aligned} \frac{V_1}{V_x} &= \frac{I R_1}{I(R_1 + R_2 + R_3)} \\ &= \frac{R_1}{R_1 + R_2 + R_3} = \frac{R_1}{R_T} \end{aligned}$$




Where R_T is the total resistance of the chain $R_T = R_1 + R_2 + R_3$

V_X is divided into $V_1 : V_2 : V_3$ in the proportions $R_1 : R_2 : R_3$

Approximate Voltage Divider:

$$\text{If } I_Y = 0, \text{ then } V_Y = \frac{R_A}{R_A + R_B} V_X.$$
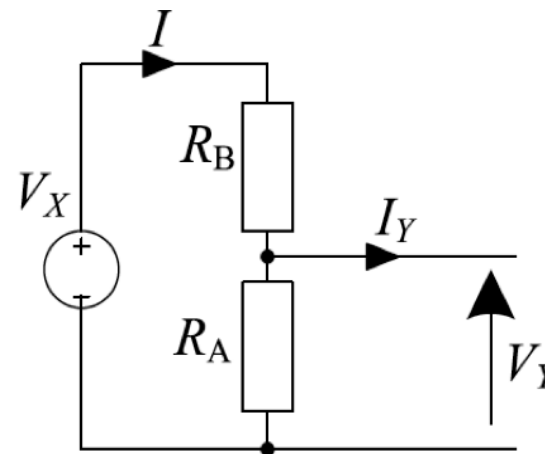
$$\text{If } I_Y \ll I, \text{ then } V_Y \approx \frac{R_A}{R_A + R_B} V_X.$$



P56-57


Parallel Resistors: Current Divider

- ◆ Parallel resistors all share the same V .

$$I_1 = \frac{V}{R_1} = V G_1 \quad \text{where} \quad G_1 = \frac{1}{R_1} \quad \text{is the } \textit{conductance} \text{ of } R_1.$$

$$\begin{aligned} I_x &= I_1 + I_2 + I_3 \\ &= VG_1 + VG_2 + VG_3 \\ &= V(G_1 + G_2 + G_3) \end{aligned}$$
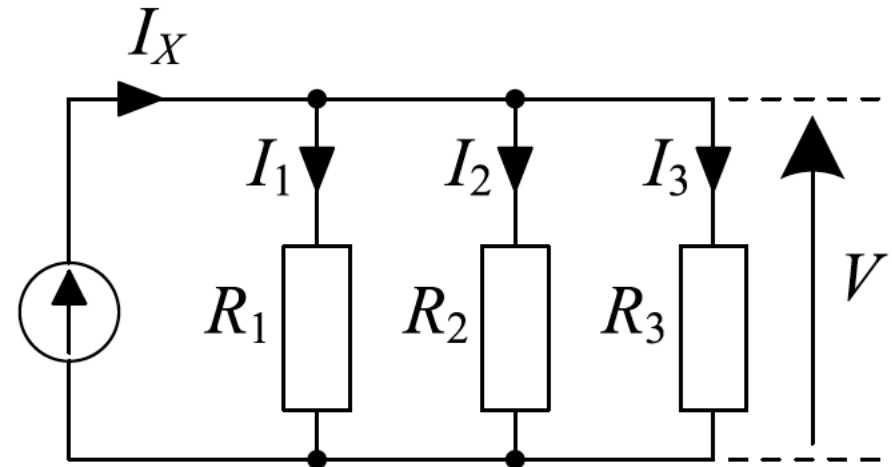
$$\frac{I_1}{I_x} = \frac{VG_1}{V(G_1 + G_2 + G_3)} = \frac{G_1}{G_1 + G_2 + G_3} = \frac{G_1}{G_P}$$



where $G_P = G_1 + G_2 + G_3$ is the total conductance of the parallel resistors.

I_x is divided into $I_1 : I_2 : I_3$ in the proportions $G_1 : G_2 : G_3$.

Equivalent Resistance: Series



- ◆ We know that

$$V = V_1 + V_2 + V_3 = I (R_1 + R_2 + R_3) = I R_T$$

- ◆ So we can replace the three resistors by a single *equivalent resistor* of value R_T without affecting the relationship between V and I .

- ◆ Replacing series resistors by their equivalent resistor will not affect any of the voltages or currents in the rest of the circuit.

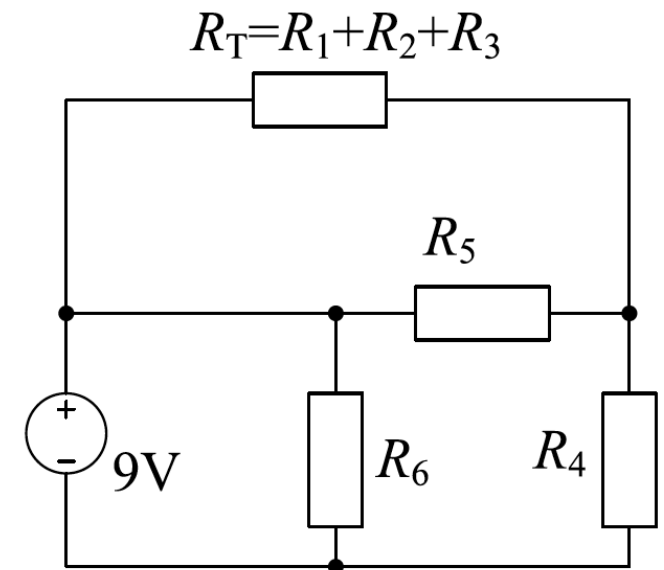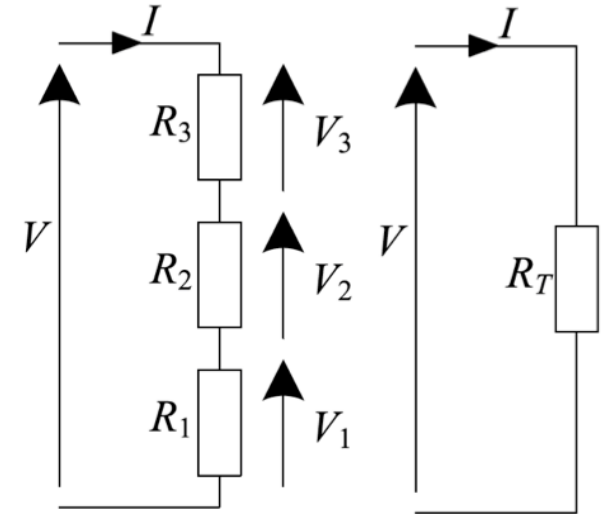- ◆ However the individual voltages V_1 , V_2 and V_3 are no longer accessible.




Equivalent Resistance: Parallel

- ◆ Similarly we know that

$$I = I_1 + I_2 + I_3 = V (G_1 + G_2 + G_3) = V G_P$$

- ◆ So $V = I R_P$ where $R_P = \frac{1}{G_F} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$

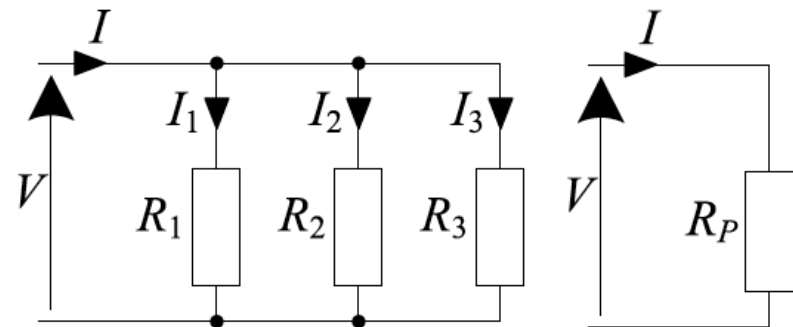
- ◆ We can use a single *equivalent resistor* of resistance R_P without affecting the relationship between V and I .



- ◆ Replacing parallel resistors by their equivalent resistor will not affect any of the voltages or currents in the rest of the circuit.

- ◆ R_4 and R_5 are also in parallel.

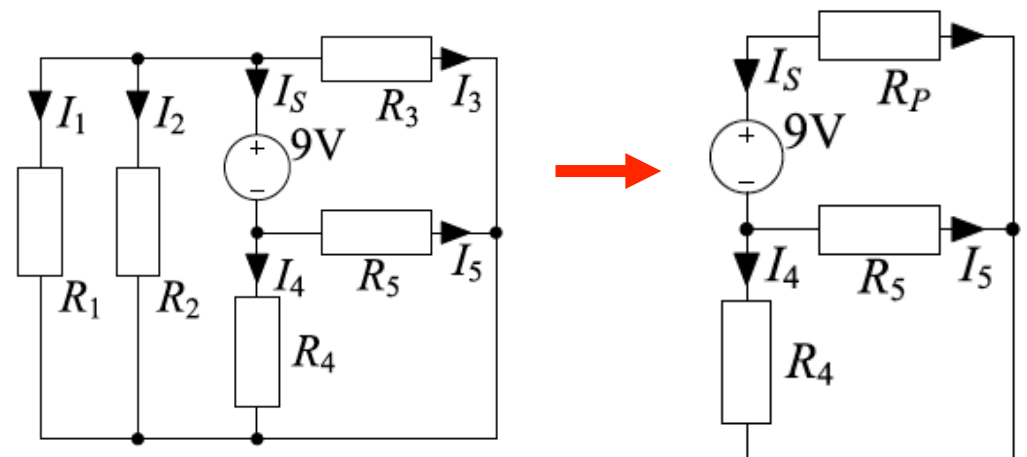- ◆ Much simpler - although none of the original currents I_1, \dots, I_3 are now implicitly specified.



Equivalent Resistance: Parallel Formulae

- ◆ For parallel resistors $G_P = G_1 + G_2 + G_3$

or equivalently $R_P = R_1 \parallel R_2 \parallel R_3 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$

- ◆ These formulae work for any number of resistors.

- ◆ For the special case of two parallel resistors

$$R_P = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} \quad (\text{"product over sum"})$$

- ◆ If one resistor is a multiple of the other

Suppose $R_2 = kR_1$, then

$$R_P = \frac{R_1 R_2}{R_1 + R_2} = \frac{kR_1^2}{(k+1)R_1} = \frac{k}{k+1} R_1 = \left(1 - \frac{1}{k+1}\right) R_1$$

- ◆ Example: $1 \text{ k}\Omega \parallel 99 \text{ k}\Omega = \frac{99}{100} \text{ k}\Omega = \left(1 - \frac{1}{100}\right) \text{ k}\Omega$

- ◆ **Important:** The equivalent resistance of parallel resistors is always less than any of them.

Simplifying Resistor Networks

- ◆ Many resistor circuits can be simplified by alternately combining series and parallel resistors.





Series: $2\text{ k}\Omega + 1\text{ k}\Omega = 3\text{ k}\Omega$

Parallel: $3\text{ k}\Omega \parallel 7\text{ k}\Omega = 2.1\text{ k}\Omega$

Parallel: $2\text{ k}\Omega \parallel 3\text{ k}\Omega = 1.2\text{ k}\Omega$

Series: $2.1\text{ k}\Omega + 1.2\text{ k}\Omega = 3.3\text{ k}\Omega$

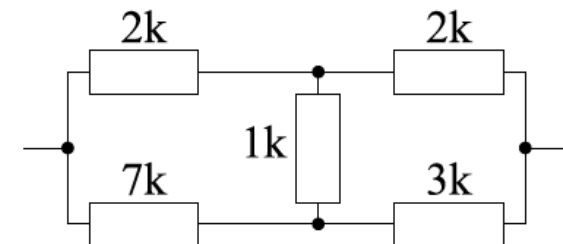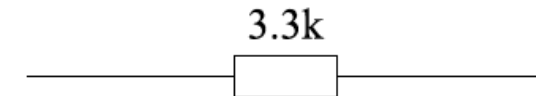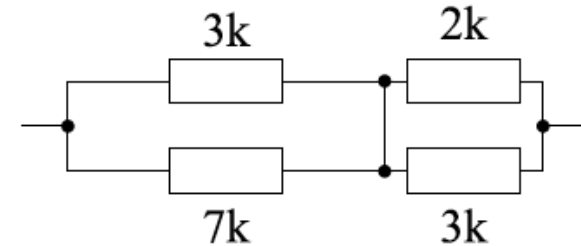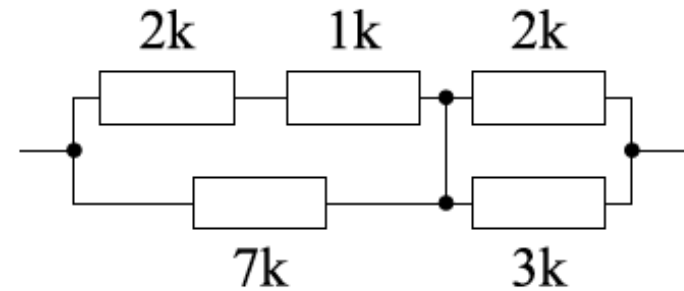
- ◆ Sadly this method does not always work: there are no series or parallel resistors here.



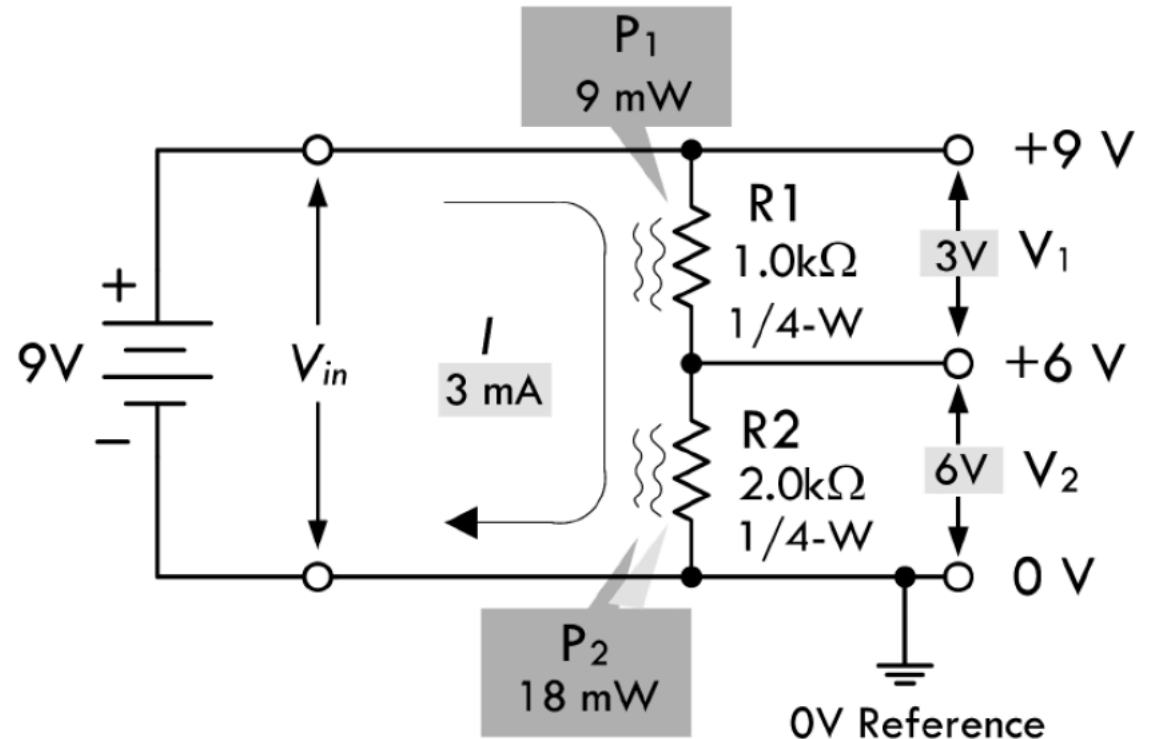Example of a voltage divider

- ◆ Using two resistors R1 and R2, connected to a voltage source 9V, we can produce any voltage between 0V and the battery source voltage of 9V


- ◆ In this example, R1 and R2 are connected in series. The total resistance is $3\text{k}\Omega$
- ◆ The current I through the two resistors is therefore $9\text{V}/3\text{k} = 3\text{mA}$.
- ◆ Therefore the voltage across R2 is: $V_2 = I \times R_2 = 6\text{V}$
- ◆ The voltage across R1 is 3V



- ◆ This is called a voltage divider because R1 and R2 effectively divide the 9V into two parts!

Non-ideal Voltage Source

- ◆ An ideal battery has a characteristic that is vertical: battery voltage does not vary with current.
- ◆ Normally a battery is supplying energy so V and I have opposite signs, so $I \leq 0$.
- ◆ An real battery has a characteristic that has a slight positive slope: battery voltage decreases as the (negative) current increases.
- ◆ Model this by including a small resistor in series. $V = V_B + IR_B$.
- ◆ The equivalent resistance for a battery increases at low temperatures.

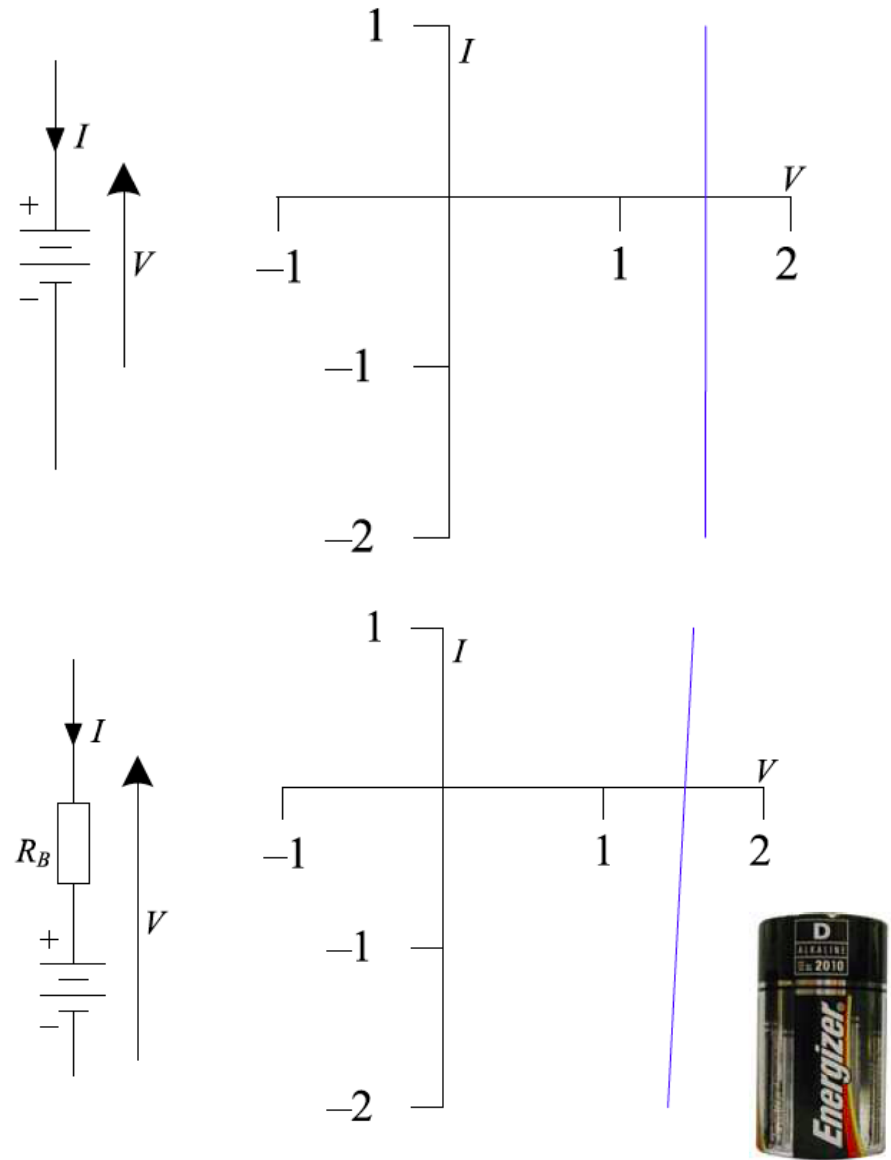

Summary

- ❑ Identify resistor values
- ❑ Series and Parallel components
- ❑ Voltage and Current Dividers
- ❑ Simplifying Resistor Networks
- ❑ Battery Internal Resistance