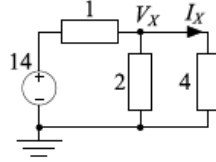


Design Engineering – EA1.3 Electronics


Problem Sheet 2 (Topics 5 - 7)

Key: [A] = easy [E] = hard


1. [B] Calculate V_X and I_X in the following circuit using (a) nodal analysis and (b) simplifying the circuit by combining parallel resistors.



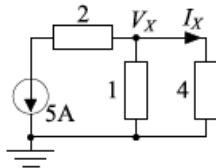
2. [B] Calculate V_X and I_X in the following circuit using (a) nodal analysis and (b) simplifying the circuit by combining parallel resistors.



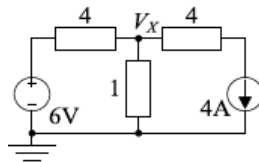
3. [C] Calculate V_X in the following circuit using (a) nodal analysis and (b) superposition.



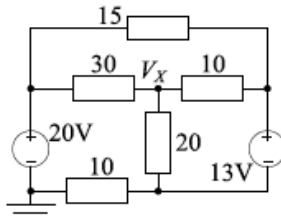
4. [C] Calculate V_X in the following circuit.



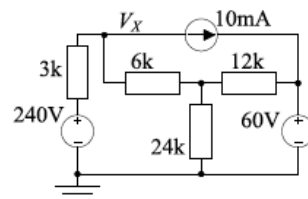
5. [C] Calculate V_X in the following circuit.



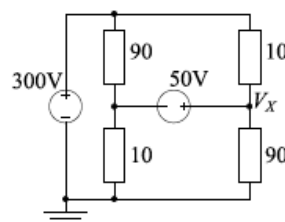
6. [C] Calculate V_X in the following circuit.



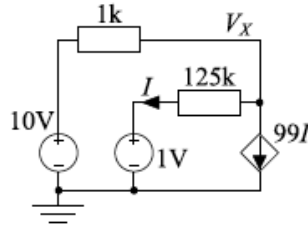
7. [C] Calculate V_x in the following circuit. The value of the dependent current source is 99 times the current flowing through the 1V voltage source.



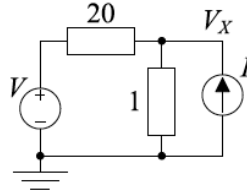
8. [C] In the following circuit calculate V_x in terms of V and I using (a) nodal analysis and (b) superposition.



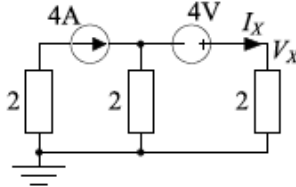
9. [C] Calculate V_x and I_x in the following circuit using (a) nodal analysis and (b) superposition.



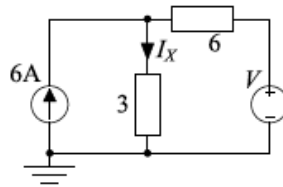
10. [C] Determine an expression for I_x in terms of V in the following circuit. Determine the value of V that will make $I_x = 0$.



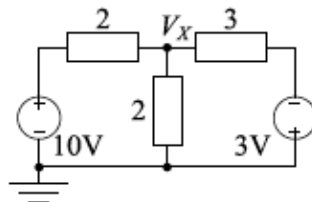
11. [C] Calculate V_x in the following circuit using (a) nodal analysis and (b) superposition.



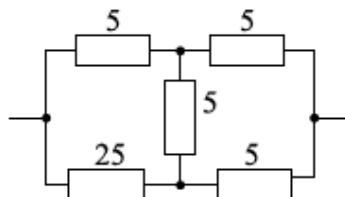12. [C] Find the equivalent resistance of the network shown below.



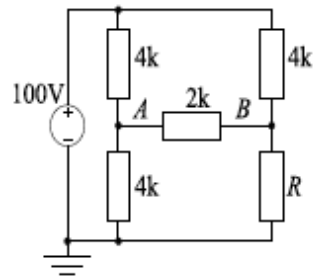13. [D] Prove that if $V_{AB} = 0$, then $R = 4 \text{ k}$ in the following circuit. The circuit is used to detect small changes in R from its nominal value of 4 k . Find an expression for V_{AB} as a function of R . If changes in V_{AB} of 10 mV can be detected, what is the smallest detectable change in R .



14. [D] Calculate V_x in the following circuit. You can either use nodal analysis directly or else simplify the circuit a little to reduce the number of nodes.

