

Design Engineering – DE1.3 Electronics 1


Solutions to Problem Sheet 3 (Topics 7 - 8)

Note: In many of the solutions below I have written the voltage at node X as the variable X instead of V_X in order to save writing so many subscripts.

1. (a) The Thévenin equivalent voltage equals the open circuit voltage is 4 V (from potential divider). To obtain the Thévenin resistance, we set the voltage source to 0 (making it a short circuit) and find the resistance of the network to be $1||4 = 0.8\Omega$.
- (b) The open-circuit voltage is -8V (since the 2 A current flows anticlockwise). To obtain the Thévenin resistance, we set the current source to zero (zero current implies an open circuit), so the resultant network has a resistance of 4 Ω .
2. KCL at node A gives $\frac{A-5}{1} + \frac{A}{4} - I = 0$ from which $5A - 20 - 4I = 0$ which we can rearrange to give $A = 4 + 0.8I = V_{Th} + R_{Th}I$. We can also rearrange to give $I = -5 + \frac{1}{0.8}A = -I_{Nor} + \frac{1}{R_{Nor}}A$.

3. (a) [Method 1 - circuit manipulation] To calculate the Thévenin equivalent, we want to determine the open-circuit voltage and the Thévenin resistance. To determine the open-circuit voltage, we assume that $I = 0$ and calculate V_{AB} . Since $I = 0$, we can combine the 1 Ω and 6 Ω resistors to give 7 Ω and then combine this with the 6 Ω resistor in parallel to give $\frac{42}{13}\Omega$. We now have a potential divider so the voltage at point X is $63 \times \frac{42/13}{3+42/13} = \frac{98}{3}$. This is then divided by the 1 Ω and 6 Ω resistors to give an open-circuit voltage of $\frac{98}{3} \times \frac{6}{7} = 28$ V. The Thévenin resistance can be found by short-circuiting the voltage source to give 3 Ω in parallel with 6 Ω which equals 2 Ω . This is then in series with 1 Ω (to give 3 Ω) and finally in parallel with 6 Ω to give 2 Ω .

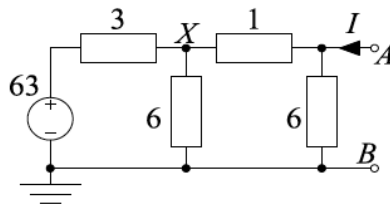- (b) [Method 2 - Nodal Analysis]. We can do KCL at node X (see diagram below) to get $\frac{X-63}{3} + \frac{X}{6} + \frac{X-A}{1} = 0$ which simplifies to $9X - 6A = 126$ or $3X - 2A = 42$. We now do KCL at A but include an additional input current I as shown in the diagram. This gives $\frac{A-X}{1} + \frac{A}{6} - I = 0$ from which $7A - 6X = 6I$. Substituting for $6X = 4A + 84$ gives $3A = 84 + 6I$ or $A = 28 + 2I$. This gives the Thévenin voltage as 28 and the Thévenin/Norton resistance as 2 Ω . Hence the Norton current is 14 A.



4. (a) KCL @ X gives $\frac{X-14}{1} + \frac{X}{4} + \frac{X}{2} = 0$ from which $7X = 56 \Rightarrow X = 8 \Rightarrow I = \frac{X}{2} = 4$ mA.
- (b) Finding the Thévenin equivalent of the left three components: we consider the two resistors as a potential divider to give $V_{Th} = 14 \times \frac{4}{5} = 11.2$ V. Setting the source to zero (short circuit) gives $R_{Th} = 1||4 = 800\Omega$. Hence $I = \frac{V_{Th}}{R_{Th}+2000} = \frac{11.2}{2.8} = 4$ mA.

5. From question 4 the left three components have a Thévenin equivalent: $V_{Th} = 11.2$ V and $R_{Th} = 800\Omega$. It follows that the maximum power will be dissipated in R when $R = R_{Th} = 800\Omega$ (see notes page 5-8). Since the voltage across R will then be $\frac{1}{2}V_{Th}$ the power dissipation will be $\frac{1}{4R_{Th}}V_{Th}^2 = 39.2$ mW.


6.

Setting the voltage source to zero gives us the first diagram. Combining $40 \parallel (60 + 100) = 32$ so $X = -0.1 \times 32 = -3.2$ V. it follows (potential divider) that $A = -3.2 \times \frac{100}{160} = -2$ V.

Now setting the current source to zero gives the second diagram and we have a potential divider giving $V_{AB} = 6 \times \frac{100}{100+60+40} = 3$ V.


Superposition now gives us $V_{AB} = V_{Th} = -2 + 3 = 1$ V.

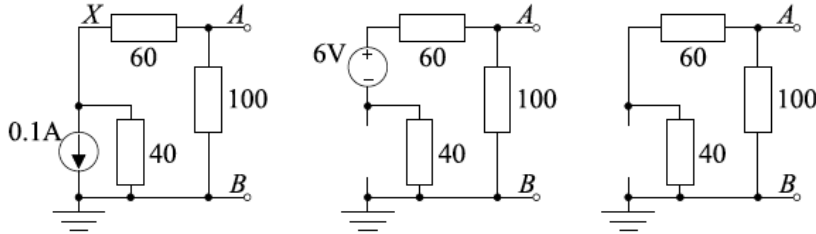To find R_{Th} we set both sources to zero and find the resultant resistance of $100 \parallel (60+40) = 100 \parallel 100 = 50 \Omega$.



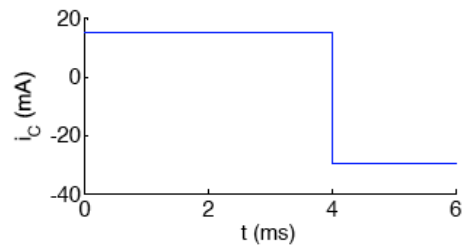7.

$i = C \frac{dv}{dt}$. $\frac{dv}{dt}$ is 3000 V/s for the first 4ms and -6000 V/s for the next 2ms. So $i = +15$ or -30 mA.



8.

When x changes from low to high, y will change from high to low. The maximum current is 2 mA so $\frac{dy}{dt} = -\frac{i}{C} = -50$ MV/s. So the time to fall from 5 V to 1.5 V is $\frac{3.5}{50} \times 10^{-6} = 70$ ns.