

ELEC50001 – Circuits and Systems

2020 - 2021

Answer ALL questions.

There are THREE questions on the paper.

Question ONE counts for 50% of the marks, other questions 25% each


Time allowed: 2 hours

SOLUTIONS

1. (a) This question tests student's ability to read datasheet of an op-amp, and to demonstrate their understanding of the implications of the various parameter and thus what to expect from the performance of the op-amp.

(i) The relevant parameter are those related to step response:

Step Response						
Slew Rate	SR	—	2.3	—	V/μs	G = +1 V/V
Settling Time (0.01%)	t _{settle}	—	4.5	—	μs	G = +1 V/V, 3.8V step

 

The most important part is the slew rate limitation. The typical settling time specification is for 3.8V step in datasheet and is less important for this case.

[4]

Frequency Response						
Gain Bandwidth Product	GBWP	—	2.8	—	MHz	

(ii)

The gain-bandwidth product of this op-amp is 2.8MHz. Therefore the gain for a sinewave at 2.8MHz is -3dB. The DC remains the same at 1.5V, but the peak-to-peak amplitude is reduced to $1/\sqrt{2}$ or 0.71V. Hence the signal at Vout is a sinewave at 2.8MHz between 1.15V and 1.85V.

[3]

(iii)

Input Current and Impedance					
Input Bias Current	I _B	—	1	—	pA
Industrial Temperature	I _B	—	20	60	pA
Extended Temperature	I _B	—	450	5000	pA
Input Offset Current	I _{OS}	—	±1	—	pA
Common Mode Input Impedance	Z _{CM}	—	10 ¹³ 6	—	Ω pF
Differential Input Impedance	Z _{DIFF}	—	10 ¹³ 3	—	Ω pF

Input impedance is so high that we can use, say 100k resistors for R3 and R4 to establish a 2.5V dc offset at +ve input of the op-amp. The lower break frequency is:

$$f_{lower} = \frac{1}{2\pi(R3||R4)C1} \ll 10Hz \quad (\text{say, } = 1Hz)$$

Therefore C1 = 3.2μF.

Assuming impedance of C2 << R1, then the gain of the amplifier is $1+R2/R1 = 10$. Therefore $R2/R1 = 9$. If R2 = 180k, then R1 = 20k.

Again assuming the corner frequency for R1 and C2 is 1Hz as before, C2 = 5*3.2μF = 6μF.

[5]

(b) This question tests student's knowledge about address decoding (normally applied to memory circuits, but here is a slight twist using IP addresses instead). At a simpler level, it also tests student's ability to convert between decimal and hexadecimal code.

(i) This is like decoding 32-bit memory address where only the top 14-bits need to be decoded. The bottom 18-bits are don't cares. This is because

192 is 8'hC0 and 168 is 8'hA8 and 171 is 8'hAC. Therefore the address range for decoding is:

1100 0000 1010 1000 0000 0000 0000 0000 to

1100 0000 1010 1011 1111 1111 1111 1111

Therefore the 14-bit to decode is: **11 00 00 00 10 10 10** or 14'h302A.

Hence

$$Y = IP[31] \& IP[30] \& \sim IP[29] \& \sim IP[28] \& \\ \sim IP[27] \& \sim IP[26] \& \sim IP[25] \& \sim IP[24] \& \\ IP[23] \& \sim IP[22] \& IP[21] \& \sim IP[20] \& \\ IP[19] \& \sim IP[18]$$

[4]

(ii) Two possible implementations:

Straight forward, lots of typing version:

```
1 module ip_detect(ip, match);
2   input [31:0] ip; // 32-bit IP address
3   output      match; // high if address is between 192.168.x.x and 192.171.x.x
4
5   assign match = ip[31]&ip[30]&~ip[29]&~ip[28] & ~ip[27]&~ip[26]&~ip[25]&~ip[24]
6               & ip[23]&~ip[22]&ip[21]&~ip[20] & ip[18]&~ip[18];
7 endmodule
```

Smart version:

```
1 module ip_detect(ip, match);
2   input [31:0] ip; // 32-bit IP address
3   output      match; // high if address is between 192.168.x.x and 192.171.x.x
4
5   assign match = ip[31:18] ==14'h302A;
6 endmodule
```

[4]


- (c) This question tests student's ability to write a simple Verilog HDL code.. The answer is not unique and here is a possible solution.

[8]

```
1  module updn (tick, up, value);
2
3     input        tick;        // clock signalinput
4     input        up;          // high to count up
5     output [6:0] value;
6
7     reg [6:0]    value;
8
9     initial value = 7'b0;
10
11    always @ (posedge tick)
12        if (up == 1'b1) begin
13            if (value!=7'd100)
14                value <= value + 1'b1;
15            end
16        else begin
17            if (value!=7'd0)
18                value <= value - 1'b1;
19            end
20    endmodule
```

(d) This question tests student's understanding of timing constraints in digital circuit.

(i) The timing diagram is:

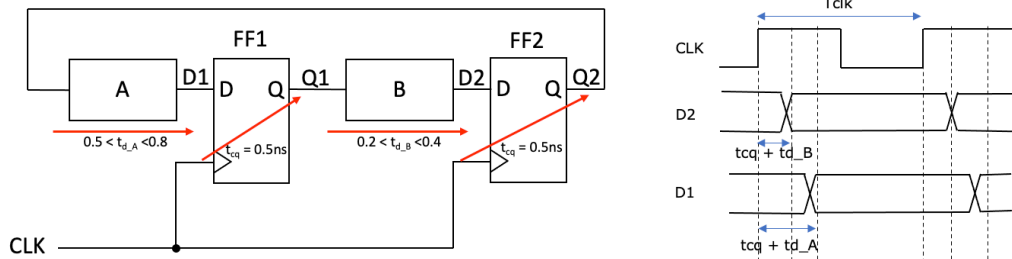

Ignore any hold time violation, the critical path is from Q2 to D1. This gives:

$$T_{CLK} \geq t_{cq(\max)} + t_{d_A(\max)} + t_s$$

Therefore,

$$T_{CLK} \geq 1.8ns, \quad f_{CLK} \leq 555.5MHz$$

[4]


(ii) Hold-time violation occurs when signal changes too soon after the active clock edge. In this case, we need to use the minimum timing constraints.

For FF2, $t_{cq(\min)} + t_{d_B(\min)} \geq t_h$. But $0.5 + 0.2 = 0.7ns \leq t_h$ which is $0.9ns$. Therefore there is hold-time violation.

For FF1, $t_{cq(\min)} + t_{d_A(\min)} = 0.5 + 0.4 \geq t_h$, which is $0.9ns$. So no hold-time violation.

[4]

(iii) Here is the new timing diagram:

 

Setup-time requirement is same as before excepted that clock is now divided into high and low period.

For FF1:

$$T_{CLK_l} \geq t_{cq(\max)} + t_{d_A(\max)} + t_s \geq 1.8ns$$

For FF2:

$$T_{CLK_h} \geq t_{cq(\max)} + t_{d_B(\max)} + t_s \geq 1.4ns$$


Since the clock is symmetrical, clock period is $2 * \max(T_{CLK_l}, T_{CLK_h})$, or $f_{CLK} \leq 277.8MHz$.

As can be seen in the timing diagram, hold-time is never violated.

[4]


(e) This question tests student's ability to reverse engineer the code to hardware, and the idea of PWM.

(i)

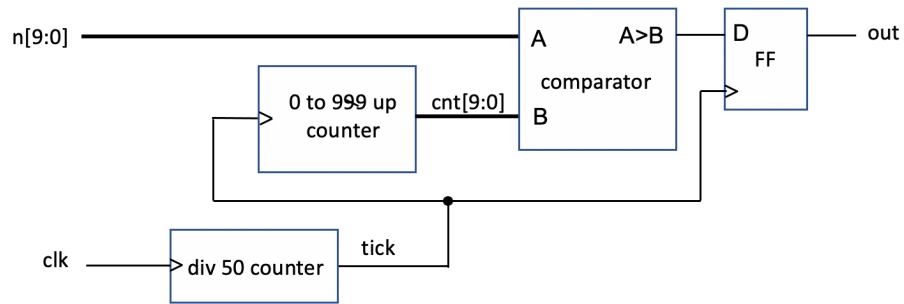

[5]

(ii)

 

[5]

2. This question tests student's understanding of how FSM is implemented on FPGA hardware, the FPGA internal circuits, Mealy FSM, one-hot encoding and how to specify a FSM in Verilog HDL.

(a)

S1, S0	NS1, NS2 / Q	
	P=0	P=1
0 0	0 1/0	0 1/0
0 1	1 0/1	1 1/0
1 0	1 1/1	0 0/0
1 1	0 0/0	1 0/1

(b) A3 is always 0:

[5]

P	S1	S0	S1'	S0'
A2	A1	A0	Y1	Y0
0	0	0	0	1
0	0	1	1	0
0	1	0	1	1
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	0	0	0
1	1	1	1	0

(c) LE2 is LUT only with D-FF bypassed.. The LUT content (A3 is again 0) is:

[7]

P	S1	S0	Q
A2	A1	A0	
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

[5]

(d)

```
1  module FSM (clk, p, q);
2      input  clk, p;
3      output reg  q;
4
5      parameter S_0 = 4'b0001;
6      parameter S_1 = 4'b0010;
7      parameter S_2 = 4'b0100;
8      parameter S_3 = 4'b1000;
9
10     parameter NSTATE = 4;
11     reg [NSTATE - 1:0] state;
12     initial state = S_0;
13
14     //-----state machine transition-----//
15     always @ (posedge clk)
16     case (state)
17     S_0: state <= S_1;
18     S_1: if (p == 1'b1) state <= S_3;
19         else state <= S_2;
20     S_2: if (p == 1'b1) state <= S_0;
21         else state <= S_3;
22     S_3: if (p == 1'b1) state <= S_2;
23         else state <= S_0;
24     default: state <= S_0;
25     endcase
26
27     // ----- state machine output -----//
28     always @ (*)
29     case (state)
30     S_0: assign q = 1'b0;
31     S_1: assign q = ~p;
32     S_2: assign q = -p;
33     S_3: assign q = p;
34     default: assign q = 1'b0;
35     endcase
36 endmodule
```

[5]

3. This question tests student's understanding of R-2R ladder network, and then apply the same principle to a completely new circuit (that is actually not that useful but interesting).

(a) Bookwork.

Every node "sees" a resistance of R, made up of 2 branch resistors 2R, splitting the current equally. Therefore

$$I_3 = V_{REF}/4R \quad I_2 = V_{REF}/8R \quad I_1 = V_{REF}/16R \quad I_0 = V_{REF}/32R$$

$$V_3 = V_{REF}/2 \quad V_2 = V_{REF}/4 \quad V_1 = V_{REF}/8 \quad V_0 = V_{REF}/16$$

[5]

(b) This part is quite tricky. With this network, all branch current split into 1/3 on the right branch and 2/3 on the downward branch. Further, every node now "sees" a resistance of $R \parallel 2R = 2/3 R$. Starting from I_0 and work up the ladder. The right branch resistor is connect to either GND or virtual earth. Therefore we get:

Hence: $V_{REF}/R = (81/8)I_0 \Rightarrow I_0 = (8/81) V_{REF}/R$.


$$I_1 = (4/27) V_{REF}/R, \quad I_2 = (2/9) V_{REF}/R, \quad I_3 = (1/3) V_{REF}/R.$$

$$V_0 = (16/71)V_{REF}, \quad V_1 = (8/27)V_{REF}, \quad V_2 = (4/9)V_{REF}, \quad V_3 = (2/3)V_{REF}$$

[10]

(c) The right terminal of all 2R resistors are connected either to GND or virtual GND of the inverting op-amp, which sum the current that flow into the negative input of the op-amp. The SPDT switch steers the current, hence minimizing the current swings and eliminate the problem of changing current quickly. The op-amp acts as a current summer that add the branch current where the digital control signal is 1.

[5]

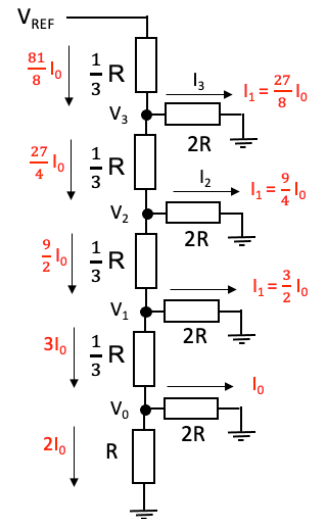

(d) $V_{OUT} = -2R(I_3 + I_1) = -2V_{REF}(1/3 + 4/27) = - (26/27)V_{REF} = -4.81V$.

[5]