

# **ELEC50001 – Circuits and Systems**

**2021 - 2022**

Answer ALL questions.

There are THREE questions on the paper.

Question ONE counts for 50% of the marks, other questions 25% each

Time allowed: 2 hours

**Information for Candidates:**


The following notation is used in this paper:

1. Unless explicitly indicated otherwise, digital circuits are drawn with their inputs on the left and their outputs on the right.
2. Within a circuit, signals with the same name are connected together even if no connection is shown explicitly.
3. The notation  $X[2:0]$  denotes the three-bit number  $X_2$ ,  $X_1$  and  $X_0$ . The least significant bit of a binary number is always designated bit 0.


1. (a) Part of the datasheet for AD823, a dual operational amplifier integrated circuit, is provided as a separate document for your convenience.

Based on the information available, answer the following questions with appropriate justifications.

- (i) *Figure 1.1(a)* shows half of the AD823 connected as an amplifier. Sketch the output signal  $V_{OUT}$  if the input signal  $V_{IN}$  is a sinewave at 3.2MHz with an amplitude of 0.1V and a DC offset of 0.2V. State any assumptions made. [4]
- (ii) Sketch the output signal  $V_{OUT}$  if the input signal  $V_{IN}$  is a symmetrical digital clock signal at a frequency of 1MHz with low and high logic levels at 0V and 0.3V. [3]
- (iii) *Figure 1.1(b)* shows the AD823 connected as audio amplifier for input signal in the frequency range of 20Hz to 20kHz driving a 32Ω headphone. [5]
- What is the gain of the amplifier at the specified frequency range?
  - What is the DC operating voltage at nodes A, B and C?
  - What value would you choose for the value of R in *Figure 1.1(b)* and why?
  - What is a suitable value of the output capacitor  $C_{OUT}$  and why?

 

*Figure 1.1(a)*

 

*Figure 1.1(b)*

(b) A 16-bit microprocessor system has 32k byte of RAM, 8k byte of ROM and two I/O devices each occupy 4 bytes of the memory address space. The microprocessor has a 16-bit address bus A[15:0]. The starting addresses of the RAM, ROM and I/O devices are shown in *Figure 1.2*.

(i) What is the address range of each of the devices? [4]

(ii) Design in the form of Boolean equations the chip select signals RAM\_CS, ROM\_CS, IO1\_CS and IO2\_CS. You may assume that the chip select signals are low-active in all cases. [4]


(iii) Implement in Verilog this address decoder module. [2]

Device	Starting Address (in Hex)
RAM	0000
ROM	A000
I/O 1	FE00
I/O 2	FF00

*Figure 1.2*

(c) *Figure 1.3* shows a circuit with two D flip-flops FF1 and FF2 with setup and hold times of 2 ns and 1 ns respectively, and a clock-to-Q output delay of 1 ns. The clock signal CLK has a 1:1 mark-space ratio. The signal path has two combinational circuits, LUT\_1 and LUT\_2, each having a propagation delay between 1 ns and 5 ns. The clock path is driven by non-inverting clock buffer, which has a propagation delay between 2 ns and 10 ns.

- (i) Derive the inequalities for the setup time constraints for this circuit. [4]
- (ii) Hence derive the maximum frequency of the signal CLK for reliable operation of this circuit. [2]
- (iii) How would you modify the circuit to increase the maximum operating clock frequency? What is the new maximum frequency? [4]

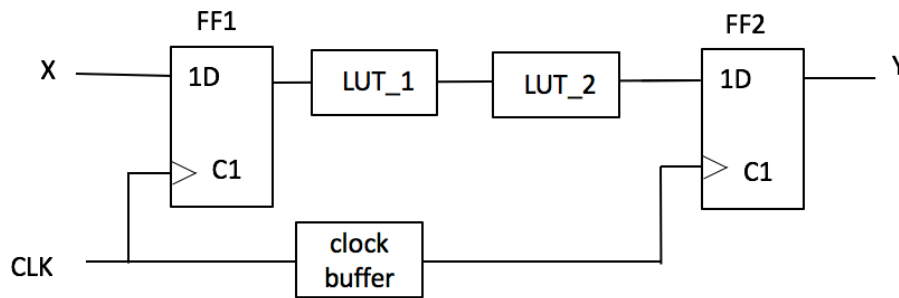

*Figure 1.3*


(d) You are required to convert a 10-bit digital number to an analogue voltage over the voltage range of 0 to 3.3V with a Digital-to-Analogue Converter (DAC).

(i) What is the resolution of the analogue output?

[2]

(ii) *Figure 1.4* shows the circuit of a 4-bit DAC using R-2R ladder architecture, four electronic switches and a current summing operational amplifier. Derive the value  $I_o$  flowing through the bottom  $2R$  resistor (in terms of  $R$ ). Hence or otherwise, derive the value of  $I_{in}$ , the input current from the voltage reference  $V_{ref}$ . What is the output voltage  $V_{out}$  of the DAC with the switch setting as shown in *Figure 1.4*?

[6]

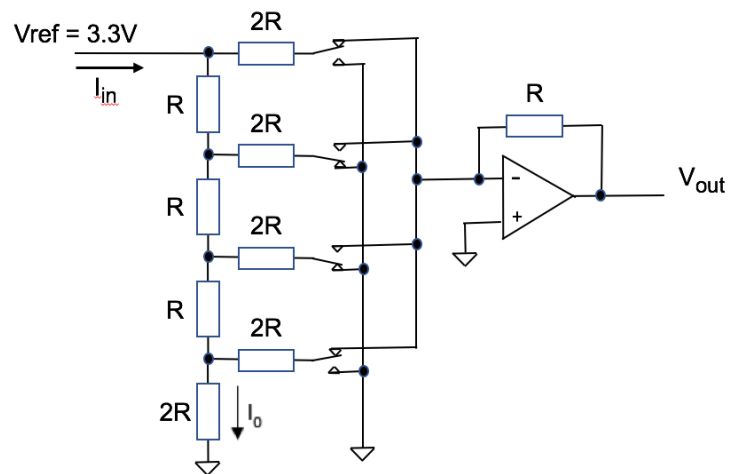

*Figure 1.4*

- (e) A circuit with a 4-bit unsigned input  $X[3:0]$  and a 4-bit unsigned output  $Y[3:0]$  is required to perform a decoding function as described by the following pseudo-code:

```
if X < 5
    Y = X
else if X < 12
    Y = X + 3
else
    Y = X - 2
```

- (i) Design this decoder circuit in Verilog HDL with the interface declarations shown in *Figure 1.5* using the CASE statement. [8]

- (ii) If the decoder is implemented using Intel's MAX-10 FPGA, estimate the number of Logic Elements (LEs) required. [2]

```
module decoder (X, Y);
    input  [3:0] X;
    output [3:0] Y;
```

*Figure 1.5*

2. (a) *Figure 2.1* shows an integrator circuit implemented using a dual supply operational amplifier. Derive from first principle the relationship between  $V_{OUT}$  and  $V_{IN}$ , and hence shows that the transfer function of this circuit is:


$$K(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{1}{RC} \times \frac{1}{s} \quad [5]$$

- (b) *Figure 2.2* shows a summing integrator with two input voltages  $X$  and  $Y$ . Shows that the relationship between the output  $V_1$  and the inputs  $X$  and  $Y$  is given by the following:


$$V_1(s) = -\frac{1}{\frac{1}{2} + 10RCs} (X(s) + Y(s)) \quad [10]$$

- (c) *Figure 2.3* shows a filter circuit combining the circuits from (a) and (b) above and feedback. Show that the transfer function of this circuit is that of a second-order low pass filter of the form:


$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{1000}{s^2 + 5s + 1000} \quad [10]$$

 

*Figure 2.1*

 

*Figure 2.2*

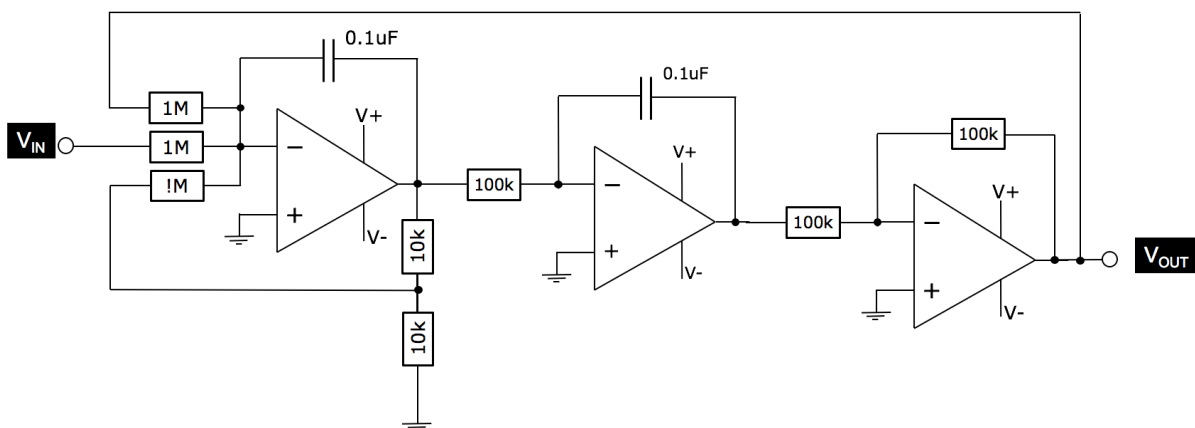

*Figure 2.3*



3. *Figure 3.1* shows the top-level schematic of the serial peripheral interface SPI used to interface between the MAX10 FPGA board and a digital to analogue converter.

a) Specify in Verilog HDL the divide-by-50 clock circuit that produces the 1MHz internal symmetrical clock signal `clk_1MHz` (i.e. 1:1 mark-space ratio) from the 50MHz system clock.


[5]

b) *Figure 3.2* shows the state diagram of the “load detector” FSM circuit. Specify in Verilog HDL the code segment that implements this FSM.


[10]

c) *Figure 3.3* shows the code segment of the 16-bit data shift register circuit in Verilog HDL. Draw the digital circuit that is expected to be synthesized, using only D flip-flops, multiplexers and basic logic gates.

[10]

 

*Figure 3.1*

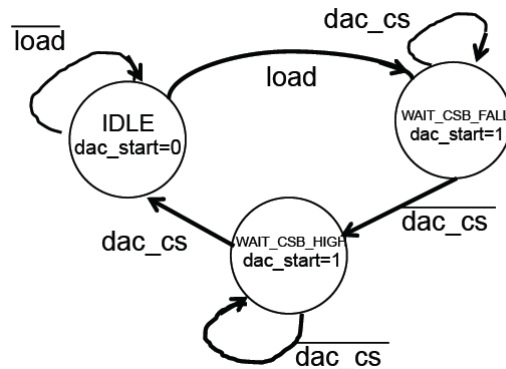

*Figure 3.2*

```

input [9:0] data_in; // input data to DAC
wire [9:0] data_in;
reg      dac_cs, dac_ld;
wire     dac_sck, dac_sdi;

parameter BUF=1'b1;      // 0:no buffer, 1:Vref buffered
parameter GA_N=1'b0;     // 0:gain = 2x, 1:gain = 1x
parameter SHDN_N=1'b1;  // 0:power down, 1:dac active

wire [3:0] cmd = {1'b0,BUF,GA_N,SHDN_N}; // wire to VDD or GND

// shift register for output data
reg [15:0] shift_reg;
initial begin
    shift_reg = 16'b0;
end

always @(posedge clk_1MHz)
    if((dac_start==1'b1)&&(dac_cs==1'b1)) // parallel load data to shift reg
        shift_reg <= {cmd,data_in,2'b00};
    else // .. else start shifting
        shift_reg <= {shift_reg[14:0],1'b0};

// Assign outputs to drive SPI interface to DAC
assign dac_sck = !clk_1MHz&!dac_cs;
assign dac_sdi = shift_reg[15];

```

*Figure 3.3*



# Dual, 16 MHz, Rail-to-Rail FET Input Amplifier

Data Sheet

AD823

## FEATURES

### Single-supply operation

- Output swings rail-to-rail
- Input voltage range extends below ground
- Single-supply capability from 3 V to 36 V

### High load drive

- Capacitive load drive of 500 pF,  $G = +1$
- Output current of 15 mA, 0.5 V from supplies

### Excellent ac performance on 2.6 mA/amplifier

- 3 dB bandwidth of 16 MHz,  $G = +1$
- 350 ns settling time to 0.01% (2 V step)
- Slew rate of 22 V/ $\mu$ s

### Good dc performance

- 800  $\mu$ V maximum input offset voltage
- 2  $\mu$ V/ $^{\circ}$ C offset voltage drift
- 25 pA maximum input bias current

### Low distortion: -108 dBc worst harmonic @ 20 kHz

### Low noise: 16 nV/ $\sqrt{\text{Hz}}$ @ 10 kHz

### No phase inversion with inputs to the supply rails

## APPLICATIONS

### Battery-powered precision instrumentation

### Photodiode preamps

### Active filters

### 12-bit to 16-bit data acquisition systems

### Medical instrumentation

## GENERAL DESCRIPTION

The AD823 is a dual precision, 16 MHz, JFET input op amp that can operate from a single supply of 3.0 V to 36 V or from dual supplies of  $\pm 1.5$  V to  $\pm 18$  V. It has true single-supply capability with an input voltage range extending below ground in single-supply mode. Output voltage swing extends to within 50 mV of each rail for  $I_{OUT} \leq 100 \mu\text{A}$ , providing outstanding output dynamic range.

An offset voltage of 800  $\mu\text{V}$  maximum, an offset voltage drift of 2  $\mu\text{V}/^{\circ}\text{C}$ , input bias currents below 25 pA, and low input voltage noise provide dc precision with source impedances up to a Gigaohm. It provides 16 MHz, -3 dB bandwidth, -108 dB THD @ 20 kHz, and a 22 V/ $\mu$ s slew rate with a low supply current of 2.6 mA per amplifier. The AD823 drives up to 500 pF of direct capacitive load as a follower and provides an output current of 15 mA, 0.5 V from the supply rails. This allows the amplifier to handle a wide range of load conditions.

## CONNECTION DIAGRAM

 
 
 


Figure 1. 8-Lead PDIP and SOIC

Figure 2. Output Swing,  $+V_S = +3$  V,  $G = +1$ Figure 3. Small Signal Bandwidth,  $G = +1$ 

This combination of ac and dc performance, plus the outstanding load drive capability, results in an exceptionally versatile amplifier for applications such as A/D drivers, high speed active filters, and other low voltage, high dynamic range systems.

The AD823 is available over the industrial temperature range of  $-40^{\circ}\text{C}$  to  $+85^{\circ}\text{C}$  and is offered in both 8-lead PDIP and 8-lead SOIC packages.

### Rev. E

Information furnished by Analog Devices is believed to be accurate and reliable. However, no responsibility is assumed by Analog Devices for its use, nor for any infringements of patents or other rights of third parties that may result from its use. Specifications subject to change without notice. No license is granted by implication or otherwise under any patent or patent rights of Analog Devices. Trademarks and registered trademarks are the property of their respective owners.

One Technology Way, P.O. Box 9106, Norwood, MA 02062-9106, U.S.A.  
Tel: 781.329.4700 [www.analog.com](http://www.analog.com)  
Fax: 781.461.3113 ©1995–2011 Analog Devices, Inc. All rights reserved.

At  $T_A = 25^\circ\text{C}$ ,  $+V_S = +3.3\text{ V}$ ,  $R_L = 2\text{ k}\Omega$  to  $1.65\text{ V}$ , unless otherwise noted.

Table 2.

Parameter	Conditions	Min	Typ	Max	Unit
<b>DYNAMIC PERFORMANCE</b>					
-3 dB Bandwidth, $V_O \leq 0.2\text{ V p-p}$	$G = +1$	12	15		MHz
Full Power Response	$V_O = 2\text{ V p-p}$		3.2		MHz
Slew Rate	$G = -1, V_O = 2\text{ V Step}$	13	20		V/ $\mu\text{s}$
Settling Time					
to 0.1%	$G = -1, V_O = 2\text{ V Step}$		250		ns
to 0.01%	$G = -1, V_O = 2\text{ V Step}$		300		ns
<b>NOISE/DISTORTION PERFORMANCE</b>					
Input Voltage Noise	$f = 10\text{ kHz}$		16		nV/ $\sqrt{\text{Hz}}$
Input Current Noise	$f = 1\text{ kHz}$		1		fA/ $\sqrt{\text{Hz}}$
Harmonic Distortion	$R_L = 100\ \Omega, V_O = 2\text{ V p-p}, f = 20\text{ kHz}$		-93		dBc
Crosstalk					
$f = 1\text{ kHz}$	$R_L = 5\text{ k}\Omega$		-105		dB
$f = 1\text{ MHz}$	$R_L = 5\text{ k}\Omega$		-63		dB
<b>DC PERFORMANCE</b>					
Initial Offset			0.2	1.5	mV
Maximum Offset Over temperature			0.5	2.5	mV
Offset Drift			2		$\mu\text{V}/^\circ\text{C}$
Input Bias Current	$V_{CM} = 0\text{ V to }2\text{ V}$		3	25	pA
at $T_{MAX}$	$V_{CM} = 0\text{ V to }2\text{ V}$		0.5	5	nA
Input Offset Current			2	20	pA
at $T_{MAX}$			0.5		nA
Open-Loop Gain	$V_O = 0.2\text{ V to }2\text{ V}, R_L = 2\text{ k}\Omega$	15	30		V/mV
$T_{MIN}$ to $T_{MAX}$		12			V/mV
<b>INPUT CHARACTERISTICS</b>					
Input Common-Mode Voltage Range		-0.2 to +1	-0.2 to +1.8		V
Input Resistance			$10^{13}$		$\Omega$
Input Capacitance			1.8		pF
Common-Mode Rejection Ratio	$V_{CM} = 0\text{ V to }1\text{ V}$	54	70		dB
<b>OUTPUT CHARACTERISTICS</b>					
Output Voltage Swing					
$I_L = \pm 100\ \mu\text{A}$			0.025 to 3.275		V
$I_L = \pm 2\text{ mA}$			0.08 to 3.22		V
$I_L = \pm 10\text{ mA}$			0.25 to 3.05		V
Output Current	$V_{OUT} = 0.5\text{ V to }2.5\text{ V}$		15		mA
Short-Circuit Current	Sourcing to $1.5\text{ V}$		40		mA
	Sinking to $1.5\text{ V}$		30		mA
Capacitive Load Drive	$G = +1$		500		pF
<b>POWER SUPPLY</b>					
Operating Range		3		36	V
Quiescent Current	$T_{MIN}$ to $T_{MAX}$ , total		5.0	5.7	mA
Power Supply Rejection Ratio	$V_S = 3.3\text{ V to }15\text{ V}, T_{MIN}$ to $T_{MAX}$	70	80		dB

 


Figure 11. Open-Loop Gain vs. Load Resistance

 


Figure 14. Open-Loop Gain vs. Temperature

 


Figure 12. Open-Loop Gain vs. Output Voltage,  $V_S = \pm 2.5 V$

 


Figure 15. Open-Loop Gain and Phase Margin vs. Frequency

 


Figure 13. Total Harmonic Distortion vs. Frequency

 


Figure 16. Input Voltage Noise vs. Frequency