

**Lecture 14**  
**(Supplementary)**


**spi2dac.v Explained**

Peter Cheung  
Department of Electrical & Electronic Engineering  
Imperial College London

URL: [www.ee.imperial.ac.uk/pcheung/teaching/E2\\_CAS/](http://www.ee.imperial.ac.uk/pcheung/teaching/E2_CAS/)  
E-mail: [p.cheung@imperial.ac.uk](mailto:p.cheung@imperial.ac.uk)
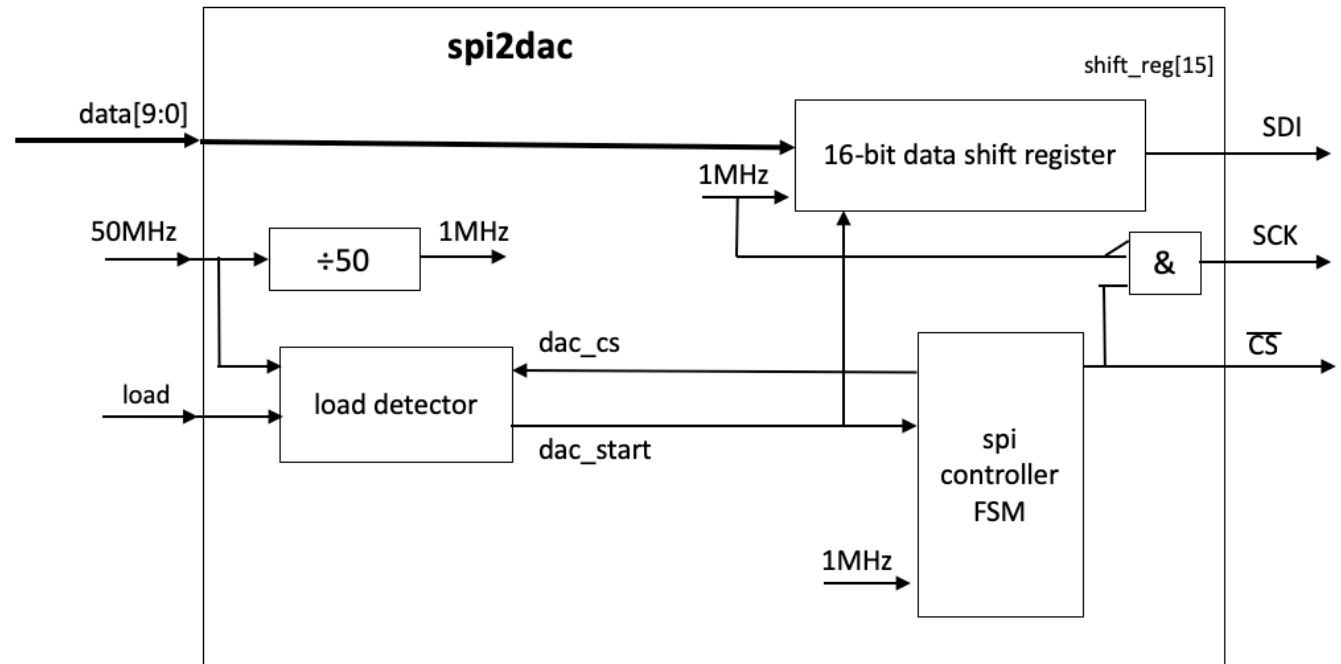
# Spi2dac.v design overview

- ◆ The components inside spi2dac are:
  1. Clock divider
  2. Load detector to detect load pulse
  3. FSM to control the spi interface
  4. Parallel to serial shift register to shift OUT the command and data to the DAC
  5. Various gates e.g. inverters and AND gates



- ◆ Note that the Verilog code is designed to match the block diagram shown here
- ◆ It consists of TWO state machines, a counter and a shift register


# The 1MHz clock generator

```
parameter BUF=1'b1; // 0:no buffer, 1:vref buffered
parameter GA_N=1'b1; // 0:gain = 2x, 1:gain = 1x
parameter SHDN_N=1'b1; // 0:power down, 1:dac active
wire [3:0] cmd = {1'b0,BUF,GA_N,SHDN_N}; // wire to VDD or GND
```


```
// --- internal 1MHz symmetrical clock generator ---
reg clk_1MHz; // 1MHz clock derived from 50MHz
reg [4:0] ctr; // internal counter

parameter TC = 5'd24; // Terminal count - change if needed
initial begin
    clk_1MHz = 0; // don't need to reset - don't care if
    ctr = 5'b0; // ... Initialise when FPGA is configured
end

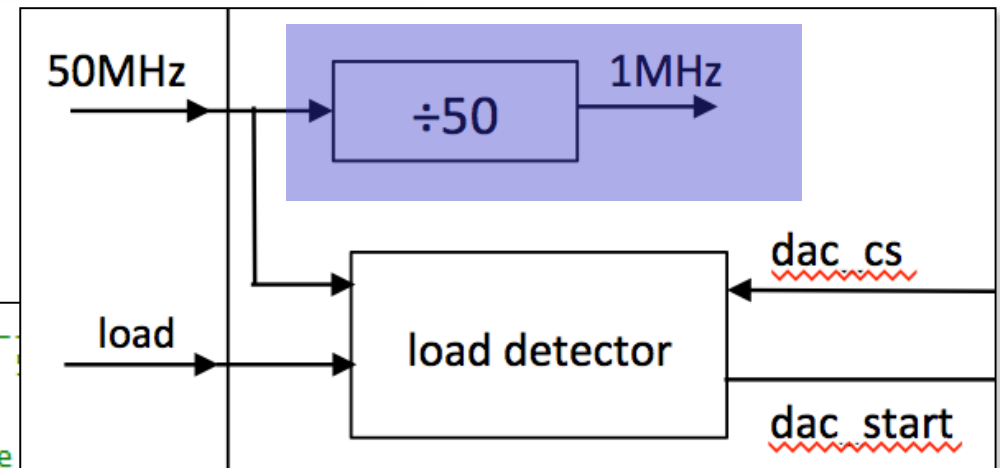always @ (posedge sysclk)
    if (ctr==0) begin
        ctr <= TC;
        clk_1MHz <= ~clk_1MHz; // toggle the output clock for symmetry
    end
    else
        ctr <= ctr - 1'b1;
// ---- end internal 1MHz symmetrical clock generator ----
```



# The load pulse detector

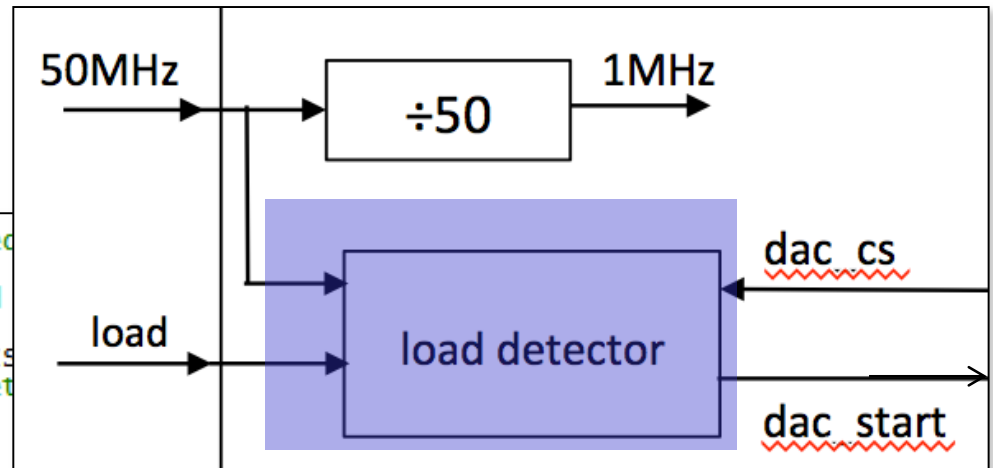


```
// ---- FSM to detect rising edge of load and falling edge
// .... sr_state set on posedge of load
// .... sr_state reset when dac_cs goes high at the end of conversion
reg [1:0] sr_state;
parameter IDLE = 2'b00, WAIT_CSB_FALL = 2'b01, WAIT_CSB_HIGH = 2'b10;
reg dac_start; // set if a DAC write is detected

initial begin
    sr_state = IDLE;
    dac_start = 1'b0; // set while sending data to DAC
end

always @ (posedge sysclk) // state transition
    case (sr_state)
        IDLE: if (load==1'b1) sr_state <= WAIT_CSB_FALL;
        WAIT_CSB_FALL: if (dac_cs==1'b0) sr_state <= WAIT_CSB_HIGH;
        WAIT_CSB_HIGH: if (dac_cs==1'b1) sr_state <= IDLE;
        default: sr_state <= IDLE;
    endcase

always @ (*)
    case (sr_state)
        IDLE: dac_start = 1'b0;
        WAIT_CSB_FALL: dac_start = 1'b1;
        WAIT_CSB_HIGH: dac_start = 1'b0;
        default: dac_start = 1'b0;
    endcase

 //----- End circuit to detect start and end of conversion state machine
```



# The SPI Controller FSM



```

//----- spi controller FSM
// .... with 17 states (idle, and S1-S16)
// .... for the 16 cycles each sending 1-bit to dac)
reg [4:0] state;

initial begin
    state = 5'b0; dac_cs = 1'b1;
end

always @(posedge clk_1MHz) // FSM state transition
    case (state)
        5'd0: if (dac_start == 1'b1) // waiting to start
            state <= state + 1'b1;
        else
            state <= 5'b0;
        5'd17: state <= 5'd0; // go back to idle state
        default: state <= state + 1'b1; // default go to next state
    endcase

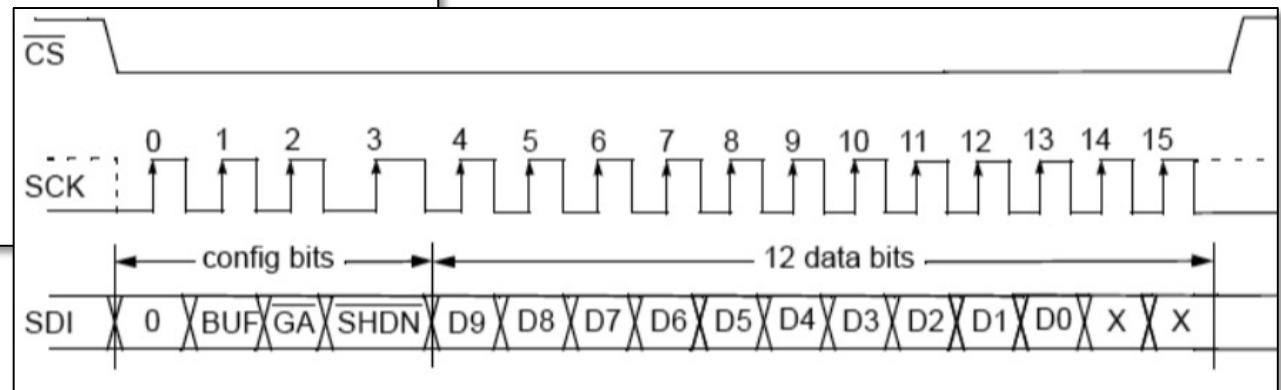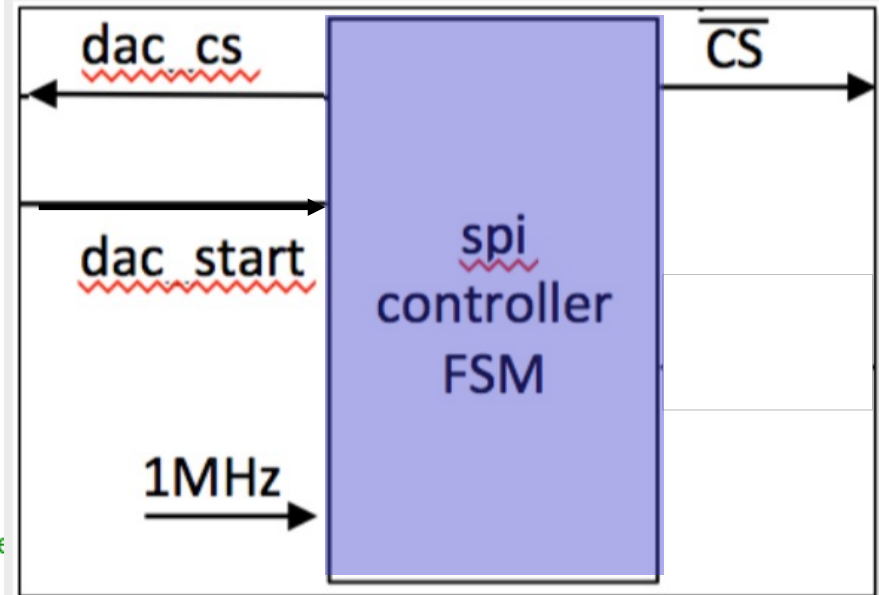always @ (*) begin // FSM output
    dac_cs = 1'b0;
    case (state)
        5'd0: dac_cs = 1'b1;
        5'd17: dac_cs = 1'b1;
        default: dac_cs = 1'b0;
    endcase
end //always
// ----- END of spi controller FSM
    
```



# The data shift register

```

parameter BUF=1'b1; // 0:no buffer, 1:vref buffered
parameter GA_N=1'b1; // 0:gain = 2x, 1:gain = 1x
parameter SHDN_N=1'b1; // 0:power down, 1:dac active

wire [3:0] cmd = {1'b0,BUF,GA_N,SHDN_N}; // wire to VDD or GND
    
```

```

// shift register for output data
reg [15:0] shift_reg;
initial begin
    shift_reg = 16'b0;
end

always @(posedge clk_1MHz)
    if((dac_start==1'b1)&&(dac_cs==1'b1)) //
        shift_reg <= {cmd,data_in,2'b00}; //
    else //
        shift_reg <= {shift_reg[14:0],1'b0};

// Assign outputs to drive SPI interface to DAC
assign dac_sck = !clk_1MHz&!dac_cs;
assign dac_sdi = shift_reg[15];
    
```

