## Lecture 4

# **Understanding op-amp models**

Prof Peter YK Cheung Imperial College London

URL: www.ee.ic.ac.uk/pcheung/teaching/EE2\_CAS/ E-mail: p.cheung@imperial.ac.uk

PYKC 15 Oct 2024

## What is SPICE Simulator?

- Simulation Program with Integrated Circuit Emphasis
  - > Developed by Larry Nagel at Berkeley in 1970's (under Prof Don Pederson).
  - Many commercial and freeware versions available.
  - Most significant CAD tool that drove the advancements in microelectronics.
- Linear Technology SPICE (LTspice)
  - Developed by Mike Engelhardt in early 2000s when he worked for Linear Technology (later bought by Analog Devices).
  - Added schematic capture and results plotting.
  - > Engelhardt now has his own company marketing Qspice not free.
- Input to SPICE is a SPICE netlist multiple lines of text that describe:
  - Components and voltage/current sources in a circuit.
  - > How the components and sources are connected to each other.
  - Model of components.
  - Type of analysis to be performed by the simulator

### **Example of a Spice netlist**



PYKC 15 Oct 2024

### **SPICE Cheat Sheet**

Letter	Component
R	Resistor
С	Capacitor
L	Inductor
V	independent voltage source
	Independent current source
М	MOSFET
D	Diode
Q	Bipolar transistor
Х	Subcircuit
E	Voltage-controlled voltage source
G	voltage-controlled current source

Letter	Unit	Multiplier		
T, t	tera	10 E+12		
G,g	giga	10 E+9		
MEG, meg	mega	10 E+6		
K, k	kilo	10 E+3		
M, m	milli	10 E-3		
U, u	micro	10 E-6		
N, n	nano	10 E=9		
Р, р	pico	10 E-12		

Directive	Action				
.op	DC operating point analysis				
.ac	Small signal AC analysis				
.tran	Transient analysis				
.backanno	Annotate current back to ports				
.include	Include another file				
.lib	Include a library				
.end	End of netlist				
.ends	End of subcircuit				
.ic	Set initial condition				

* Netlist for Lab1Task2					
R3 VG 0 200k					
R2 V1 N002 200k					
C1 N001 0 0.1µ					
XU1 VG N002 N001 0 V1 MCP6001					
V2 N001 0 5					
V1 VG 0 SINE(1 0.5 10K)					
.tran 1m					
.lib /Volumes/External					
SSD/Dropbox/_My Documents/MCP6001.mod					
.backanno					
.end					

PYKC 15 Oct 2024

## Model input stage of MCP6001

Differential Input Impedance	Z <sub>DIFF</sub>	—	10 <sup>13</sup>   3	—	Ω  pF
Input Offset Voltage	V <sub>OS</sub>	-4.5	_	+4.5	mV



G1 0 int\_gain offset in- 0.00628

#### Model gain vs frequency & slew rate of MCP6001



... G1 0 int\_gain offset in- 0.00628 R2 int\_gain 0 63.7Meg C2 int\_gain 0 1n

✤ Assume compensation capacitor C2 is 1nF

AC Response							
Gain Bandwidth Product		GBWF	>	1.0		MHz	
Phase Margin		PM	_	90		0	G = +1 V/V
Slew Rate		SR	_	0.6	_	V/µs	
DC Open-Loop Gain (Large Signal)	A <sub>OL</sub>		88	112	-	dB	[

### Model open-loop gain vs frequency of MCP6001



- Therefore  $R_2 = 63.7 \times 10^6 \Omega$
- Calculate gm for G1:

 $gm \times R_2 = A_{OL}$ , hence  $gm = \frac{400,000}{63.7} \times 10^{-6} = 0.00628$ 

#### **Model Slew rate limit**



Model the slew rate limit of 0.6V/us:

$$SR = max \frac{dV_{c2}}{dt} = max(current of G1)/C2,$$
 therefore  $max(current) = SR \times C_2 = 0.6mA$ 

G1 0 int\_gain value={limit(0.00628\*V(offset,in-),0.6m, -0.6m)}
R2 int\_gain 0 63.7Meg
C2 int\_gain 0 1n

### Model the output stage of MCP6001



\* output stage - current limit to +/- 20mA, ROUT = 300 ohm

G2 0 out value={limit(V(int_gain, 0)/300, 20m	$, -20m) \}$
R3 out 0 300	
* output voltage limited to V+ and V-	
D1 int_gain V+ Dlimit	
D2 V- int_gain Dlimit	
.model Dlimit D(Ron=0.0001 Roff=100G Vfwd=0)	

#### The complete model of MCP6001



### What specifications are NOT modelled?

- Common mode input impedances
- Common mode rejection ratio
- Power supply rejection ratio
- Common mode input voltage clipping
- Temperature effect on input bias current and offset voltage
- Noise characteristics of the op-amp
- Quiescent current of the op-amp

## **Power supply bypass (decoupling) capacitor**



- Wire connection from power supply to op-amp power pin is an inductor.
- Inductor has high impedance at high frequency.
- Current draw through op-amp causes current fluctuation in inductor can feedback to the op-amp.
- Resulting in op-amp prone to oscillation at high frequency or output overshoot.
- Add ceramic or tantalum capacitor close to op-amp supply pin to bypass (or decouple) any such high frequency fluctuations.