Lecture 6

Active Filters

Prof Peter YK Cheung Imperial College London

URL: www.ee.ic.ac.uk/pcheung/teaching/EE2_CAS/ E-mail: p.cheung@imperial.ac.uk

PYKC 22 Oct 2024

Transfer Function of 1st order LP Filter



Transfer function defined as:

$$H(s) = \frac{Y(s)}{X(s)} = \frac{R + 1/sC}{4R + 1/sC} = \frac{1 + sRC}{1 + 4sRC}.$$

Frequency response is calculated as

$$H(s)|_{s=j\omega} = \frac{Y(j\omega)}{X(j\omega)} = \frac{1+j\omega RC}{1+4j\omega RC}.$$

- Easier to perform algebra manipulation than using $j\omega$.
- Provides better intuitions on system behaviour.
- This simple filter is first-order low-pass with 1 pole and 1 zero.
- The break frequency occurs when real and imaginary parts are equal in numerator (zero freq) and denominator (pole freq).

• More general if use **complex frequency s** to represent the quantity
$$j\omega$$
.

- Covered in Signals and Systems module this term, and Control Systems next term.
- Express impedance of capacitor as $\frac{1}{sC}$ instead of $\frac{1}{j\omega C}$.
 - Capture both steady state (ac) and transient behaviour.



1st order Active Filter



2nd order Active Lowpass Filter



Sallen-Key Filter Topology



- Invented by R.P. Sallen and E.L. Key in 1955 using valves as active devices (!)
- ✤ Z1 to Z4 are arbitrary impedance from resistors, capacitors or inductors.
- Assume amplifier gain is 1 (can be generalised to K), $V_Y = V_{out}$.
- Apply KCL to V_X yields:

$$\frac{V_{in} - V_x}{Z_1} + \frac{V_{out} - V_x}{Z_3} + \frac{V_{out} - V_x}{Z_4} = 0$$

• Apply KCL at V_Y yields:

$$V_x = V_{out} + \frac{Z_2}{Z_4} V_{out} = V_{out} (1 + \frac{Z_2}{Z_4})$$

Combining the two gives a general transfer function equation:

$$\frac{V_{out}}{V_{in}} = \frac{Z_3 Z_4}{Z_1 Z_2 + Z_3 (Z_1 + Z_2) + Z_3 Z_4}$$

2nd order Sallen-Key Lowpass Filter



$$\frac{V_{out}}{V_{in}} = \frac{Z_3 Z_4}{Z_1 Z_2 + Z_3 (Z_1 + Z_2) + Z_3 Z_4}$$

$$Z_1 = R_1, Z_2 = R_2$$

 $Z_3 = 1/sC_1, Z_4 = 1/sC_2$

• Using the transfer function equation H(s) from previous slice:

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{\frac{1}{s^2 C_1 C_2}}{R_1 R_2 + \frac{1}{s C_1} (R_1 + R_2) + \frac{1}{s^2 C_1 C_2}}$$

✤ Rearrange and put this in a standard form for a 2nd order lowpass system:

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + C_2(R_1 + R_2) s + C_1 C_2 R_1 R_2 s^2}$$

Significance of ω_0 and Q (1)



$$Z_1 = R_1, Z_2 = R_2$$

 $Z_3 = 1/sC_1, Z_4 = 1/sC_2$

✤ Put this into the standard form of a 2nd order lowpass filter is:

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{1}{\omega_0 Q} s + \frac{1}{\omega_0^2} s^2} = \frac{1}{1 + C_2(R_1 + R_2) s + C_1 C_2 R_1 R_2 s^2}$$

$$Q \text{ is the quality factor}$$

$$\zeta \text{ is the damping ratio}$$

$$Q = \frac{1}{2\zeta}$$

$$\frac{2\zeta}{\omega_0} = \frac{1}{\omega_0 Q}$$

$$\frac{1}{\omega_0^2}$$

$$\frac{1}{\omega_0^2}$$

$$f_c = \frac{\omega_0}{2\pi} = \frac{1}{2\pi \sqrt{C_1 C_2 R_1 R_2}} \text{ in Hz}$$

$$f_c = \frac{\omega_0}{2\pi} = \frac{1}{2\pi \sqrt{C_1 C_2 R_1 R_2}} \text{ Hz}$$

$$* \text{ The refore, the cutoff frequency is: } f_c = \frac{\omega_0}{2\pi} = \frac{1}{2\pi \sqrt{C_1 C_2 R_1 R_2}} \text{ Hz}$$

Significance of ω_0 and Q (2)

Rewrite the transfer function as:

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{1}{1 + \frac{1}{\omega_0 Q}s + \frac{1}{\omega_0^2}s^2} = \frac{\omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \qquad f_0 = \frac{\omega_0}{2\pi}$$



A simple Sallen-Key filter (from Lab 2)



• Simplify by making
$$R_1 = R_2 = R = 18k\Omega$$
, and $C_1 = C_2 = C = 3.3nF$.

• The cutoff frequency is:
$$f_c = \frac{1}{2\pi\sqrt{R_1R_2C_1C_2}} = \frac{1}{2\pi RC} = 2.7$$
kHz and

•
$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{C_2 (R_1 + R_2)} = \frac{RC}{(C \times 2R)} = \frac{1}{2}$$

• This is NOT a Butterworth filter because Q is not 0.707 or
$$\frac{1}{\sqrt{2}}$$
.

Sallen-Key filter with gain = K





✤ Keep same R and C values, fix Q by changing gain of op-amp K

- Left as an exercise to proof: $H(s) = \frac{V_{out}(s)}{V_{in}(s)} = K \times \frac{1}{1 + (3 - K)RC \ s + R^2C^2 \ s^2}$
- Therefore, cutoff frequency f_c is same as before: $f_c = \frac{1}{2\pi\omega_0} = \frac{1}{2\pi RC}$.

• And,
$$Q = \frac{1}{\omega_0} \times \frac{1}{(3-K)RC} = \frac{1}{3-K}$$

Therefore, to get a Butterworth filter with this topology, Q = 0.707, and

✤
$$K = 3 - \frac{1}{0} = 1.586.$$

*

General Procedure: Butterworth LP filter

- 1. Determine the required cutoff frequency f_c .
- 2. Calculate R and C product with: $RC = \frac{1}{2\pi f_c}$.
- 3. Pick a suitable value of C >> input capacitance of op-amp (say in nF range).
- 4. Calculate value of R to give the required cutoff frequency.
- 5. Determine order of filter depending on required attenuation rate. Filter attenuation rate is 20 x n dB/decade, for an nth order filter.
- 6. Round n to the nearest high even number. You will need n/2 Salley-Key filter stages.
- 7. Use the table below to design gain of each stage of the filter. For example, for a 4th order Butterworth filter, we need two Sallen-Key stages with gain of 1.152 followed by 2.235.
- 8. Choose resistors for op-amps feedback paths to provides specified gain values.



ORDER n	Gain values K
2	1.586
4	1.152, 2.235
6	1.068, 1.586, 2.483
8	1.038, 1.337, 1.889, 2.610

Other Sallen-Key filter circuits





Using different values for R1 and R2



Solve the two equations for R1 and R2 values.