

Lecture 6

SystemVerilog HDL

Peter Cheung
Imperial College London

URL: www.ee.imperial.ac.uk/pcheung/teaching/EE2_CAS/
E-mail: p.cheung@imperial.ac.uk

Lecture Objectives

- ◆ By the end of this lecture, you should understand:
 - The basic structure of a module specified in Verilog HDL
 - Commonly used syntax of Verilog HDL
 - Continuous vs Procedural Assignments
 - **always** block in Verilog and sensitivity list
 - Nets vs variables
 - The use of arithmetic and logic operations in Verilog
 - The danger of **incomplete specification**
 - How to specify **clocked circuits**
 - Differences between **blocking** and **nonblocking** assignments

Schematic vs HDL

Schematic

- ✓ Good for multiple data flow
- ✓ Give overview picture
- ✓ Relate directly to hardware
- ✓ Don't need good programming skills
- ✓ High information density
- ✓ Easy back annotations
- ✓ Useful for mixed analogue/digital

- ✗ Not good for algorithms
- ✗ Not good for datapaths
- ✗ Poor interface to optimiser
- ✗ Poor interface to synthesis software
- ✗ Difficult to reuse
- ✗ Difficult to parameterise

HDL

- ✓ Flexible & parameterisable
- ✓ Excellent input to optimisation & synthesis
- ✓ Direct mapping to algorithms
- ✓ Excellent for datapaths
- ✓ Easy to handle electronically (only needing a text editor)

- ✗ Serial representation
- ✗ May not show overall picture
- ✗ Need good programming skills
- ✗ Divorce from physical hardware

SystemVerilog HDL

- ◆ Similar to C language to describe/specify hardware
- ◆ Description can be at different levels:
 - **Behavioural level**
 - **Register-Transfer Level (RTL)**
 - **Gate Level**
- ◆ Not only a specification language, also with associated **simulation environment**
- ◆ Easier to learn and “lighter weight” than its competition: VHDL
- ◆ Very popular with chip designers

- ◆ For this lecture, we will:
 - Learn through examples and practical exercises
 - Use examples: e.g. 2-to-1 multiplexer and 7 segment decoder

HDL to Gates

❖ Simulation

- Inputs applied to circuit
- Outputs checked for correctness
- Millions of dollars saved by debugging in simulation instead of hardware

❖ Synthesis

- Transforms HDL code into a netlist describing the hardware (i.e., a list of gates and the wires connecting them)

❖ Physical design

- Placement, routing, chip layout, – not considered in this module

IMPORTANT:


When using an HDL, think of the **hardware** the HDL should produce, then write the appropriate idiom that implies that hardware.

Beware of treating HDL like software and coding without thinking of the hardware.

System Verilog: Module Declaration

❖ Two types of Modules:

 - **Behavioral:** describe what a module does
- **Structural:** describe how it is built from simpler modules



```
1  module example(input  logic a, b, c,  
2  |              |              |      output logic y);  
3  |              |              |      // module body goes here  
4  endmodule
```


❖ module/endmodule: required to begin/end module

❖ example: name of the module


System Verilog: Behavioural Description

```
module example(input logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```

synthesis

 

simulation

 

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

System Verilog: Syntax

❖ Case sensitive

- e.g.: reset and Reset are not the same signal.

❖ No names that start with numbers

- e.g.: 2mux is an invalid name

❖ Whitespace ignored

❖ Comments:

- `//` single line comment
- `/*` multiline
- `comment */`

System Verilog: Structural Description

Behavioural

```
module and3(input logic a, b, c,  
           output logic y);  
    assign y = a & b & c;  
endmodule
```


```
module inv(input logic a,  
          output logic y);  
    assign y = ~a;  
endmodule
```

Structural

```
module nand3(input logic a, b, c  
            output logic y);  
    logic n1; // internal signal  
  
    and3 andgate(a, b, c, n1); // instance of and3  
    inv inverter(n1, y); // instance of inv  
endmodule
```

System Verilog: Bitwise Operators


```
module gates(input logic [3:0] a, b,  
            output logic [3:0] y1, y2, y3, y4, y5);  
    /* Five different two-input logic  
       gates acting on 4 bit busses */  
    assign y1 = a & b;    // AND  
    assign y2 = a | b;    // OR  
    assign y3 = a ^ b;    // XOR  
    assign y4 = ~(a & b); // NAND  
    assign y5 = ~(a | b); // NOR  
endmodule
```

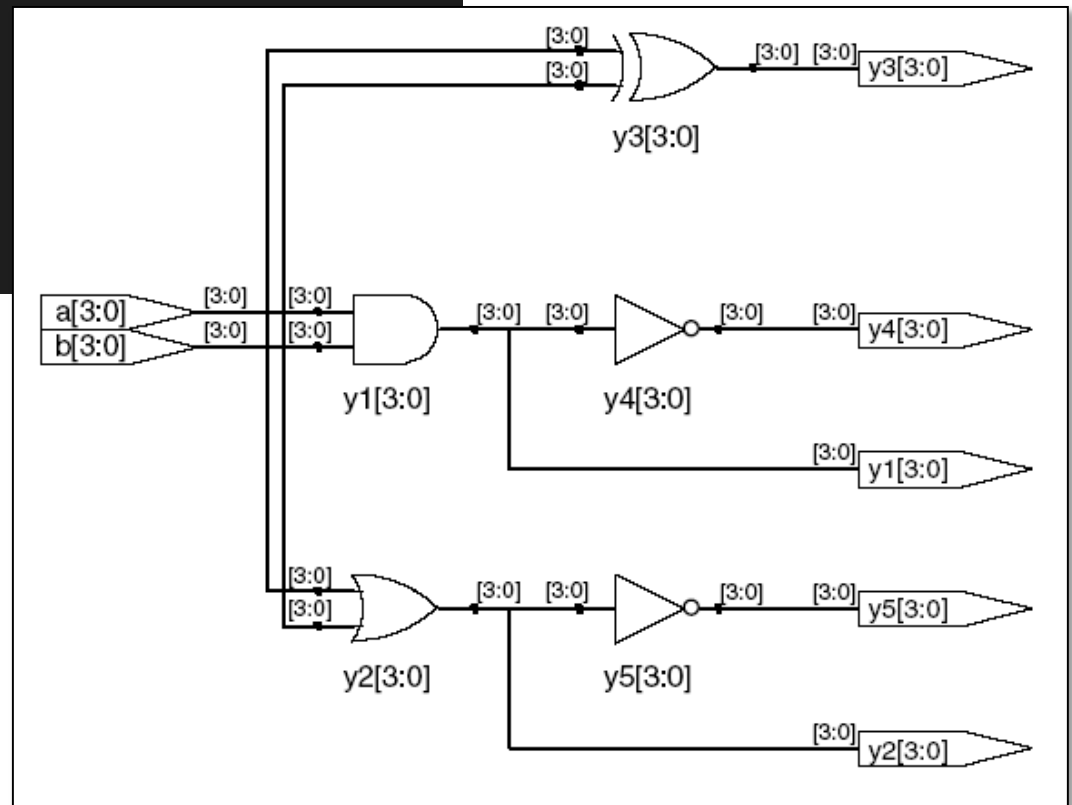

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

SystemVerilog: Reduction Operators

 
```
module and8(input logic [7:0] a,  
           output logic y);  
  assign y = &a;  
  // &a is much easier to write than  
  // assign y = a[7] & a[6] & a[5] & a[4] &  
  //           a[3] & a[2] & a[1] & a[0];  
endmodule
```



Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

System Verilog: Conditional Assignment

 
```
module mux2(input logic [3:0] d0, d1,  
            input logic      s,  
            output logic [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```



Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

System Verilog: Internal Signals

```
module fulladder(input logic a, b, cin,  
                output logic s, cout);  
    logic p, g; // internal nodes  
  
    assign p = a ^ b;  
    assign g = a & b;  
  
    assign s = p ^ cin;  
    assign cout = g | (p & cin);  
endmodule
```

 

Based on: "Digital Design and Computer Architecture (RISC-V Edition)" by Sarah Harris and David Harris (H&H),

System Verilog: Precedence of operators

Highest

~	NOT
*, /, %	mult, div, mod
+, -	add, sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
?:	ternary operator

Lowest

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

System Verilog: Number Format

Format: N'Bvalue

N = number of bits, **B** = base

N'B is optional but recommended (default is decimal)

Number	# Bits	Base	Decimal Equivalent	Stored
3'b101	3	binary	5	101
'b11	unsized	binary	3	00...0011
8'b11	8	binary	3	00000011
8'b1010_1011	8	binary	171	10101011
3'd6	3	decimal	6	110
6'o42	6	octal	34	100010
8'hAB	8	hexadecimal	171	10101011
42	Unsize	decimal	42	00...0101010

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

System Verilog: Bit Manipulations (1)

```
assign y = {a[2:1], {3{b[0]}}, a[0], 6'b100_010};
```


❖ If y is a 12-bit signal, the above statement produces:

```
y = a[2] a[1] b[0] b[0] b[0] a[0] 1 0 0 0 1 0
```

❖ Underscores (`_`) are used for formatting only to make it easier to read. **System Verilog ignores them.**

System Verilog: Bit Manipulations (2)

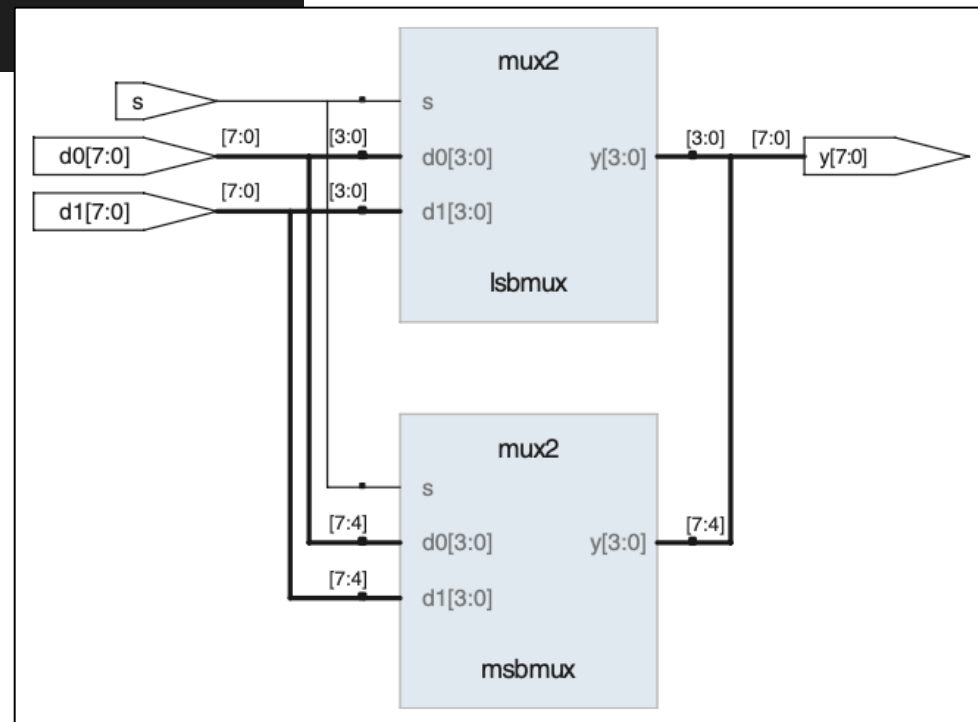
```
module mux2_8(input logic [7:0] d0, d1,  
             input logic      s,  
             output logic [7:0] y);  
  
    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);  
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);  
endmodule
```



Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

System Verilog: Floating Output Z
 
```
module tristate(input logic [3:0] a,  
               input logic      en,  
               output tri  [3:0] y);  
    assign y = en ? a : 4'bz;  
endmodule
```




❖ Note that Verilator does not handle floating output Z

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

System Verilog: Delays

```
module example(input logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} = ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

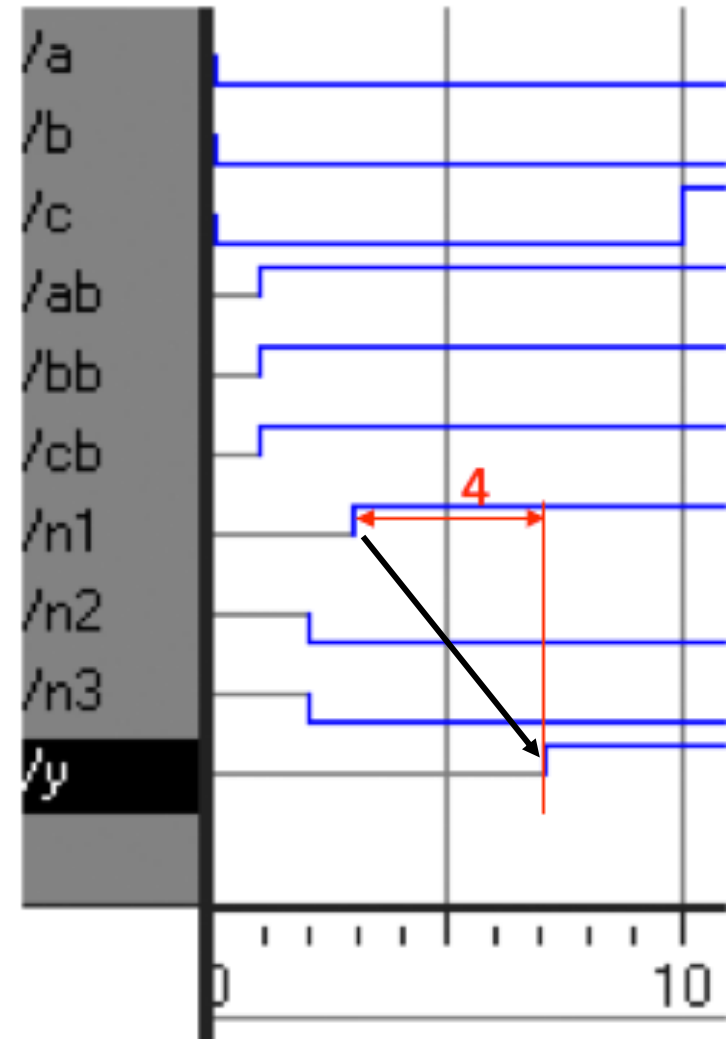- ❖ Delays are for simulation only! They do not determine the delay of your hardware.
- ❖ **Verilator simulator ignores delays** – it is cycle accurate without timing.



Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

System Verilog: Sequential Logic


- ❖ System Verilog uses **idioms** (or special keywords or groups of words) to describe latches, flip-flops and FSMs
- ❖ Other coding styles may simulate correctly but produce incorrect hardware
- ❖ GENERAL STRUCTURE:

```
always @(sensitivity list)  
    statement;
```

- ❖ Whenever the event in **sensitivity list** occurs, **statement** is executed

System Verilog: D Flip-Flop
 
```
module flop(input logic clk,  
           input logic [3:0] d,  
           output logic [3:0] q);  
  
    always_ff @(posedge clk)  
        q <= d;           // pronounced "q gets d"  
  
endmodule
```



Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

System Verilog: Resettable D Flip-Flop

Asynchronous reset


```
module flopr(input logic clk,
            input logic reset,
            input logic [3:0] d,
            output logic [3:0] q);

// asynchronous reset
always_ff @(posedge clk, posedge reset)
    if (reset) q <= 4'b0;
    else q <= d;
endmodule
```

Synchronous reset

```
module flopr(input logic clk,
            input logic reset,
            input logic [3:0] d,
            output logic [3:0] q);

 // synchronous reset
always_ff @(posedge clk)
    if (reset) q <= 4'b0;
    else q <= d;
endmodule
```



Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),


Combinational Logic using always

```
// combinational logic using an always statement
module gates(input logic [3:0] a, b,
             output logic [3:0] y1, y2, y3, y4, y5);
    always_comb // need begin/end because there is
    begin      // more than one statement in always
        y1 = a & b; // AND
        y2 = a | b; // OR
        y3 = a ^ b; // XOR
        y4 = ~(a & b); // NAND
        y5 = ~(a | b); // NOR
    end
endmodule
```

This hardware could be described with **assign statements using fewer lines** of code, so it's better to use **assign** statements in this case.

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

Putting everything together – 7 seg decoder

 

In3 : in2

out6	00	01	11	10
00	1	0	1	0
01	1	0	0	0
11	0	1	0	0
10	0	0	0	0

In1 : in0

in[3..0]	out[6:0]	Digit	in[3..0]	out[6:0]	Digit
0000	1000000	0	1000	0000000	8
0001	1111001	1	1001	0010000	9
0010	0100100	2	1010	0001000	A
0011	0110000	3	1011	0000011	b
0100	0011001	4	1100	1000110	C
0101	0010010	5	1101	0100001	d
0110	0000010	6	1110	0000110	E
0111	1111000	7	1111	0001110	F

$$\text{out6} = \text{/in3*in2*in1} + \text{in3*in2*in1*in0} + \text{/in3*in2*in1*in0}$$

$$\text{out5} = \text{/in3*in2*in0} + \text{/in3*in2*in1} + \text{/in3*in1*in0} + \text{in3*in2*in1*in0}$$

$$\text{out4} = \text{/in3*in0} + \text{/in3*in2*in1} + \text{in3*in2*in1*in0}$$

$$\text{out3} = \text{/in3*in2*in1*in0} + \text{/in3*in2*in1*in0} + \text{in2*in1*in0} + \text{/in2*in1*in0}$$


$$\text{out2} = \text{/in3*in2*in1*in0} + \text{in3*in2*in0} + \text{in3*in2*in1}$$

$$\text{out1} = \text{in3*in2*in0} + \text{/in3*in2*in1*in0} + \text{in3*in1*in0} + \text{in2*in1*in0}$$

$$\text{out0} = \text{/in3*in2*in1*in0} + \text{/in3*in2*in1*in0} + \text{in3*in2*in1*in0} + \text{in3*in2*in1*in0}$$


Method 1: Schematic Entry Implementation

$$\begin{aligned} \text{out6} &= /in3*/in2*/in1 + in3*in2*/in1*/in0 + /in3*in2*in1*in0 \\ \text{out5} &= /in3*/in2*in0 + /in3*/in2*in1 + /in3*in1*in0 + in3*in2*/in1*in0 \\ \text{out4} &= /in3*in0 + /in3*in2*/in1 + in3*/in2*/in1*in0 \\ \text{out3} &= /in3*in2*/in1*/in0 + /in3*/in2*/in1*in0 + in2*in1*in0 + /in2*in1*/in0 \\ \text{out2} &= /in3*/in2*in1*/in0 + in3*in2*/in0 + in3*in2*in1 \\ \text{out1} &= in3*in2*/in0 + /in3*in2*/in1*in0 + in3*in1*in0 + in2*in1*/in0 \\ \text{out0} &= /in3*/in2*/in1*in0 + /in3*in2*/in1*/in0 + in3*in2*/in1*in0 + in3*/in2*in1*in0 \end{aligned}$$

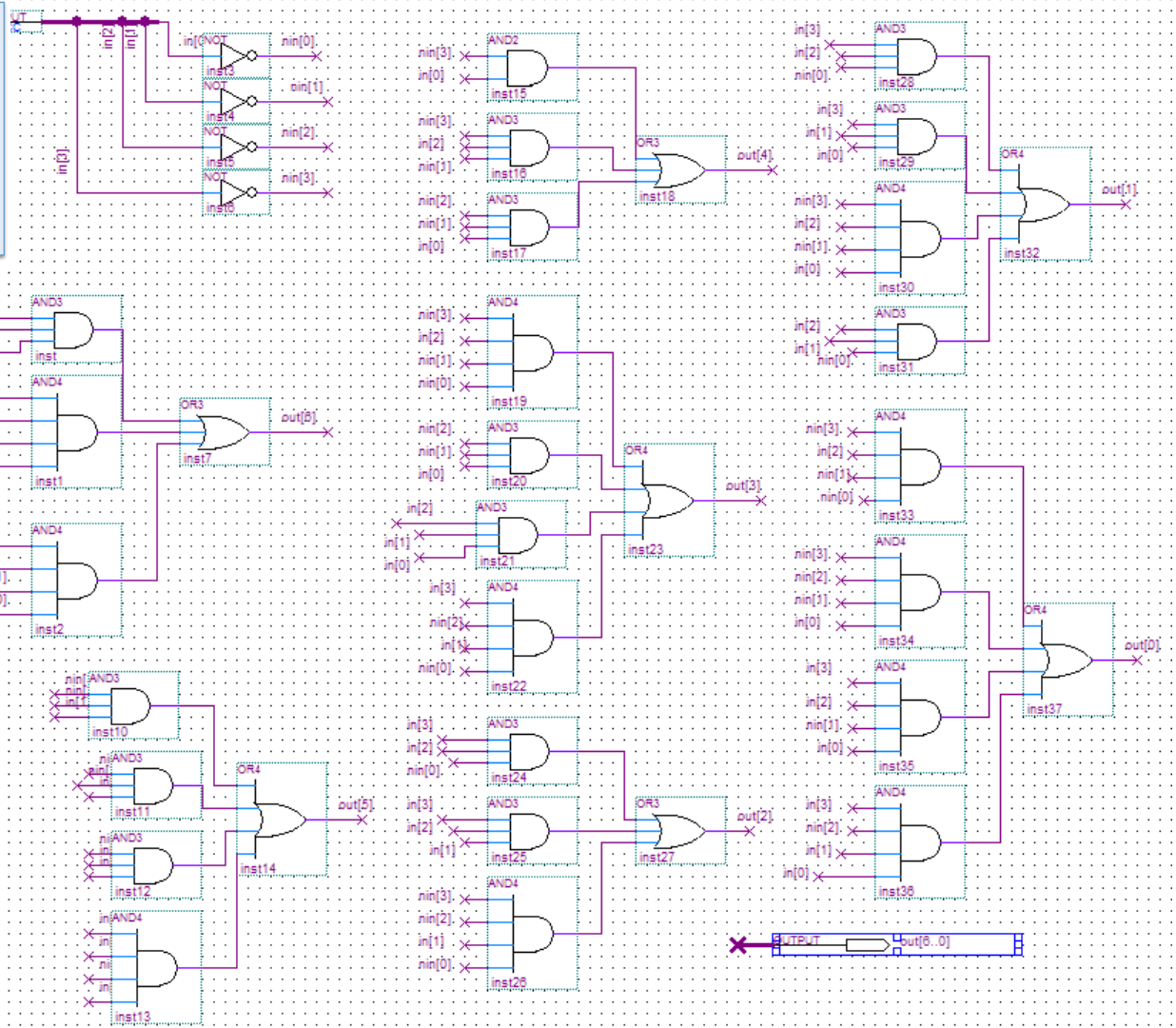

TEDIOUS!!!!

Method 2: Use primitive gates in Verilog

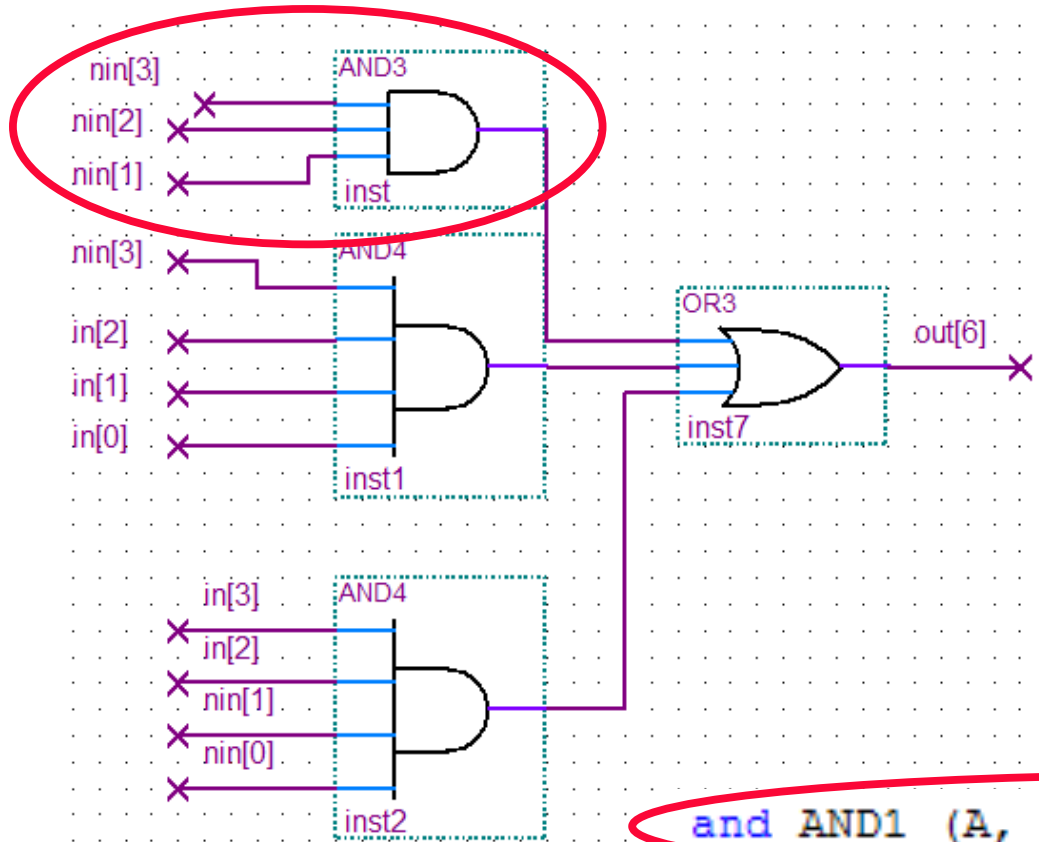


Equally TEDIOUS!!!!

Direct mapping of gates to primitives

```
and AND1 (A, nin[3], nin[2], nin[1]);  
and AND2 (B, nin[3], in[2], in[1], in[0]);  
and AND3 (C, in[3], in[2], nin[1], nin[0]);  
or OR1 (out[6], A, B, C);
```

Method 3: Use continuous assignment in Verilog
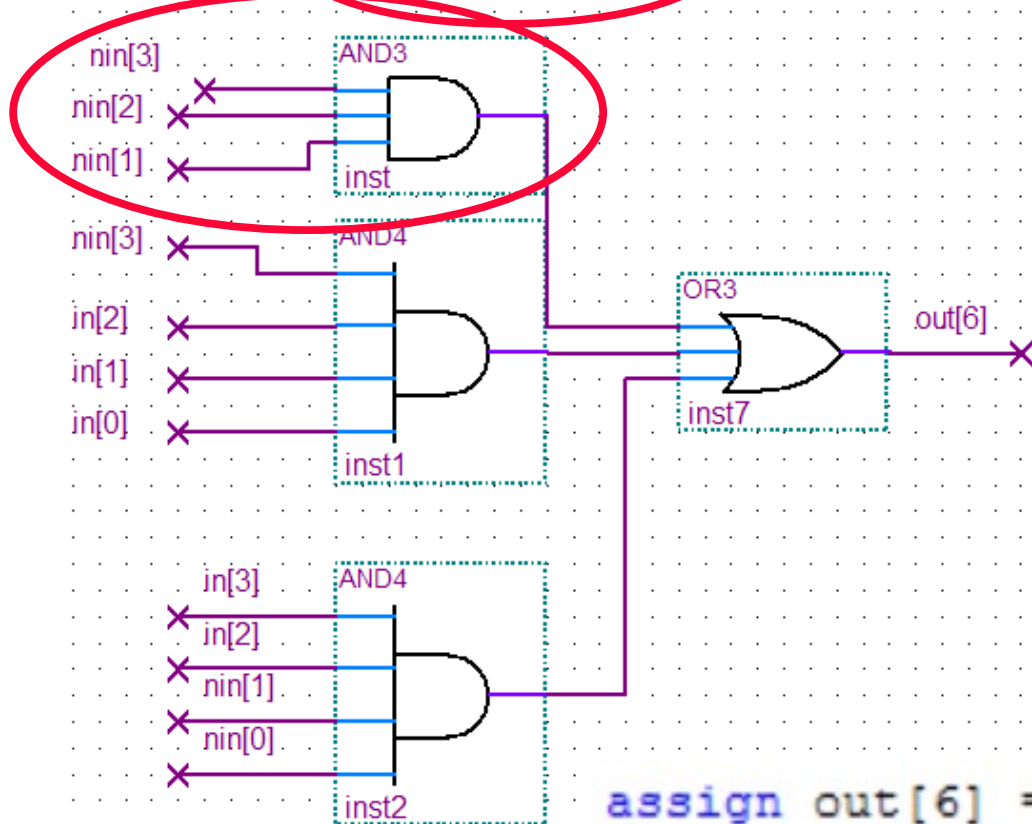
$$\text{out6} = \sim \text{in3} \cdot \sim \text{in2} \cdot \sim \text{in1} + \text{in3} \cdot \text{in2} \cdot \sim \text{in1} \cdot \sim \text{in0} + \sim \text{in3} \cdot \text{in2} \cdot \text{in1} \cdot \text{in0}$$



Much Better?

Direct mapping of Boolean equation using continuous assignment..

```
assign out[6] =  $\sim$ in[3] &  $\sim$ in[2] &  $\sim$ in[1] |
in[3] & in[2] &  $\sim$ in[1] &  $\sim$ in[0] |
 $\sim$ in[3] & in[2] & in[1] & in[0];
```

Hexto7seg.v (in Verilog)

module & endmodule
sandwich the content of
this hardware module

good header helps
documenting your code

specify interface to this
module as viewed from
outside

specify a 7-bit output bus,
out[6] ... out[0]

declaration of
input and output
ports

assign used to specify
combinational circuit

```
//-----  
// Module name: hex_to_7seg  
// Function: convert 4-bit hex value to drive 7 segment display  
//           output is low active  
// Creator: Peter Cheung  
// Version: 1.0  
// Date: 22 Oct 2011  
//-----  
  
module hex_to_7seg (out,in);  
  
    output [6:0] out; // low-active output to drive 7 segment display  
    input [3:0] in; // 4-bit binary input of a hexademical number  
  
    assign out[6] = ~in[3]&~in[2]&~in[1] | in[3]&in[2]&~in[1]&~in[0] |  
                  ~in[3]&in[2]&in[1]&in[0];  
    assign out[5] = ~in[3]&~in[2]&in[0] | ~in[3]&~in[2]&in[1] |  
                  ~in[3]&in[1]&in[0] | in[3]&in[2]&~in[1]&in[0];  
    assign out[4] = ~in[3]&in[0] | ~in[3]&in[2]&~in[1] | in[3]&~in[2]&~in[1]&in[0];  
    assign out[3] = ~in[3]&in[2]&~in[1]&~in[0] | ~in[3]&~in[2]&~in[1]&in[0] |  
                  in[2]&in[1]&in[0] | ~in[2]&in[1]&~in[0];  
    assign out[2] = ~in[3]&~in[2]&in[1]&~in[0] | in[3]&in[2]&~in[0] |  
                  in[3]&in[2]&in[1];  
    assign out[1] = in[3]&in[2]&~in[0] | ~in[3]&in[2]&~in[1]&in[0] |  
                  in[3]&in[1]&in[0] | in[2]&in[1]&~in[0];  
    assign out[0] = ~in[3]&~in[2]&~in[1]&in[0] | ~in[3]&in[2]&~in[1]&~in[0] |  
                  in[3]&in[2]&~in[1]&in[0] | in[3]&~in[2]&in[1]&in[0];  
  
endmodule
```

Method 4: Power of behavioural abstraction


```
module hexto7seg (
    output logic [6:0] out, // low-active
    input logic [3:0] in // 4-bit binary
);
    always_comb
        case (in)
            4'h0: out = 7'b1000000;
            4'h1: out = 7'b1111001; // -- 0 --
            4'h2: out = 7'b0100100; // |
            4'h3: out = 7'b0110000; // 5
            4'h4: out = 7'b0011001; // |
            4'h5: out = 7'b0010010; // -- 6 --
            4'h6: out = 7'b0000010; // |
            4'h7: out = 7'b1111000; // 4
            4'h8: out = 7'b0000000; // |
            4'h9: out = 7'b0011000; // -- 3 --
            4'ha: out = 7'b0001000;
            4'hb: out = 7'b0000011;
            4'hc: out = 7'b1000110;
            4'hd: out = 7'b0100001;
            4'he: out = 7'b0000110;
            4'hf: out = 7'b0001110;
            default: out = 7'b0000000; // def
        endcase
endmodule
```

BEAUTIFUL !!!

- Direct mapping of truth table to case statement
- Close to specification, not implementation

in[3..0]	out[6:0]	Digit
0000	1000000	0
0001	1111001	1
0010	0100100	2
0011	0110000	3
0100	0011001	4
0101	0010010	5
0110	0000010	6
0111	1111000	7
1000	0000000	8
1001	0010000	9
1010	0001000	A
1011	0000011	b
1100	1000110	C
1101	0100001	d
1110	0000110	E
1111	0001110	F

From SystemVerilog code to FPGA hardware

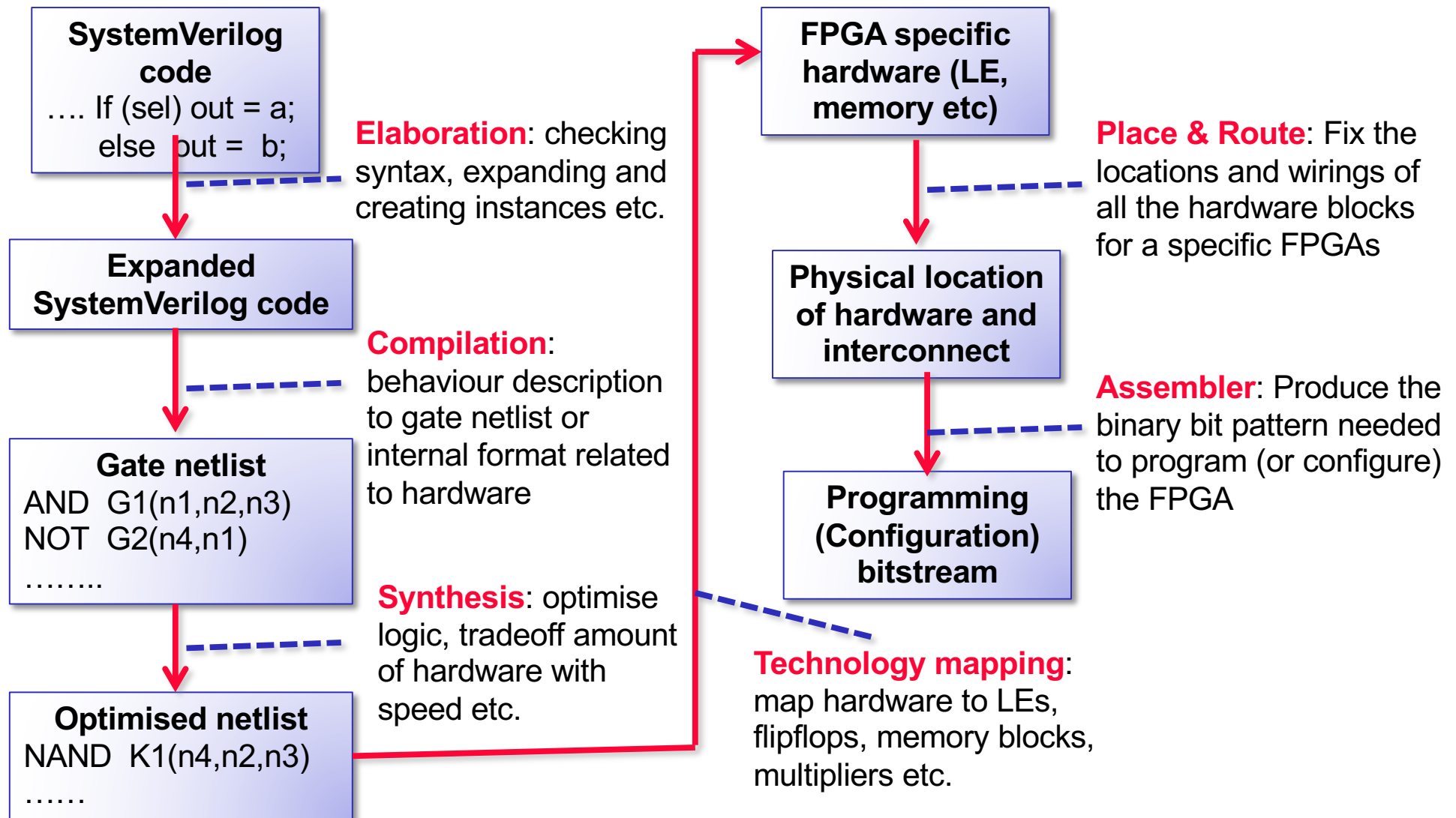

Power of SystemVerilog: Integer Arithmetic

- ◆ Arithmetic operations make computation easy:


```
module add32 (  
    input  logic [31:0]  a,  
    input  logic [31:0]  b,  
    output logic [31:0]  sum  
);  
    assign sum = a + b;  
endmodule
```

- ◆ Here is a 32-bit adder with carry-in and carry-out:

```
module add32_carry (  
    input  logic [31:0]  a,  
    input  logic [31:0]  b,  
    input  logic         cin,  
    output logic [31:0]  sum,  
    output logic         cout  
);  
    assign {cout, sum} = a + b + cin;  
endmodule
```

A larger example – 32-bit ALU in Verilog

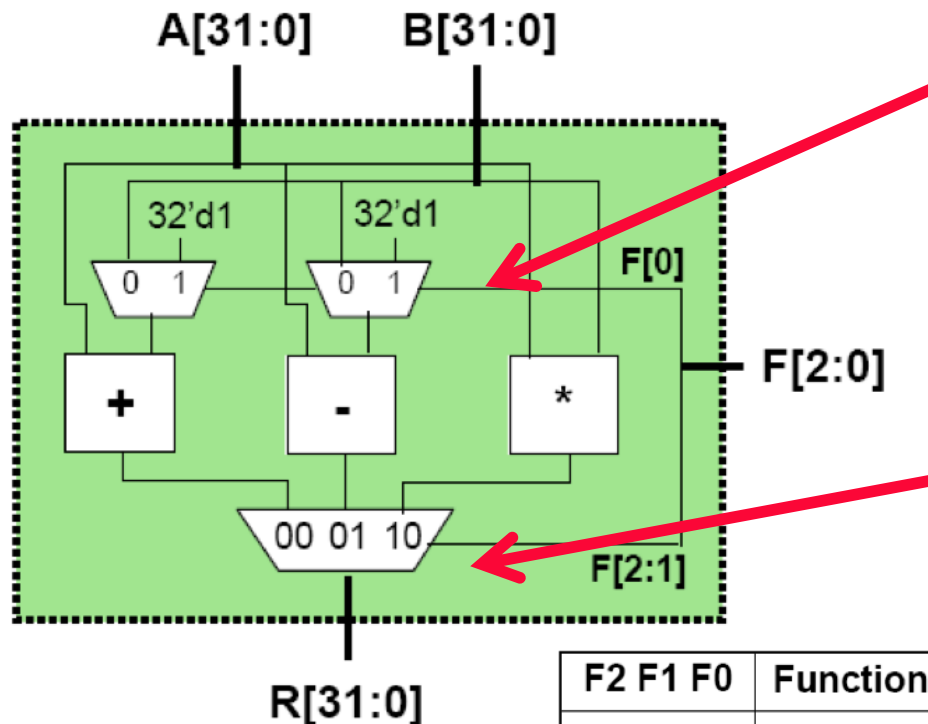- Here is an 32-bit ALU with 5 simple instructions:



F2	F1	F0	Function
0	0	0	A + B
0	0	1	A + 1
0	1	0	A - B
0	1	1	A - 1
1	0	X	A * B

```


module mux2to1 (
    input  logic [31:0]    i0,
    input  logic [31:0]    i1,
    input  logic          sel,
    output logic [31:0]    out
);
    assign out = sel ? i1 : i0;
endmodule
    
```

```

module mux3to1 (
    input  logic [31:0]    i0,
    input  logic [31:0]    i1,
    input  logic [31:0]    i2,
    input  logic [1:0]    sel,
    output logic [31:0]    out
);
    always_comb
        case (sel)
            2'b00: out = i0;
            2'b01: out = i1;
            2'b10: out = i2;
            default: out = 32'bx;
        endcase
endmodule
    
```


The arithmetic modules

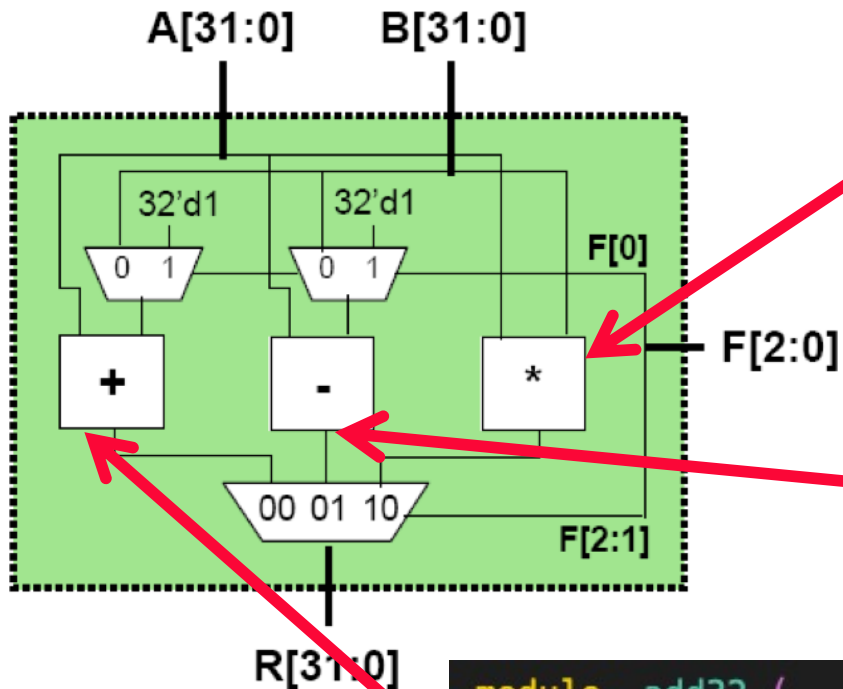- Here is an 32-bit ALU with 5 simple instructions:



```

module mul16 (
    input  logic [15:0]    i0,
    input  logic [15:0]    i1,
    output logic [31:0]    prod
);
    assign prod = i0 * i1;
endmodule
    
```

```

module sub32 (
    input  logic [31:0]    i0,
    input  logic [31:0]    i1,
    output logic [31:0]    diff
);
    assign diff = i0 - i1;
endmodule
    
```

```

module add32 (
    input  logic [31:0]    i0,
    input  logic [31:0]    i1,
    output logic [31:0]    sum
);
    assign sum = i0 + i1;
endmodule
    
```

Top-level module – putting them together

- Given submodules:

```
module mux2to1 (i0, i1, sel, out);  
module mux3to1 (i0, i1, i2, sel, out);  
module add32 (i0, i1, sum);  
module sub32 (i0, i1, diff);  
module mul16 (i0, i1, prod);
```

```
module alu (  
    input logic [31:0] a,  
    input logic [31:0] b,  
    input logic [2:0] f,  
    output logic [31:0] r  
);  
    logic [32:0] addmux_out, submux_out;  
    logic [32:0] add_out, sub_out, mul_out;  
  
    mux2to1 adder_mux (b, 32'd1, f[0], addmux_out);  
    mux2to1 sub_mux (b, 32'd1, f[0], submux_out);  
    add32 our_adder (a, addmux_out, add_out);  
    sub32 out_sub (a, submux_out, sub_out);  
    mul16 our_mult (a[15:0], b[15:0], mul_out);  
    mux3to1 output_mux (add_out, sub_out, mul_out, f[2:1], r);  
endmodule
```

