

Lecture 10

Analogue-to-Digital Conversion

Peter Cheung
Department of Electrical & Electronic Engineering
Imperial College London

URL: www.ee.imperial.ac.uk/pcheung/teaching/E2_CAS/
E-mail: p.cheung@imperial.ac.uk


Lecture Objectives

- ◆ Understand the relationship between the continuous input signal to an Analog-to-Digital converter and its discrete output
- ◆ Understand the source and magnitude of quantisation noise
- ◆ Understand how a flash converter works
- ◆ Understand the principles behind a successive approximation converter
- ◆ Understand how a successive approximation converter can be implemented using a state machine
- ◆ Understand the need for using a sample/hold circuit with a successive approximation converter

References:

- “Data Converter Architectures” in Data Conversion Handbook by Analog Devices

Analogue to Digital Conversion

 

- ◆ Converters with only +ve input voltages are called **unibipolar** converters and usually round ($V_{IN} \div 1\text{LSB}$) to the **nearest** integer.

$$X = \text{round}\left(\frac{V_{IN}}{1 \text{ LSB}}\right)$$

- ◆ Example:


- If $1 \text{ LSB} = 0.5 \text{ V}$, then $V_{IN} = 2.8 \text{ V}$ will be converted to:

$$X = \text{round}\left(\frac{2.8}{0.5}\right) = \text{round}(5.6) = 6$$

Analog to digital conversion **destroys information**: we convert a range of input voltages to a single digital value.

Sampling

 - ◆ To process a continuous signal in a computer or other digital system, you must first sample it:



Time Quantisation

- ◆ Samples taken (almost always) at regular intervals: sample frequency of f_{samp} .
- ◆ This causes *aliasing*: A frequency of f is indistinguishable from frequencies $k f_{\text{samp}} \pm f$ for all integers k .
- ◆ No information lost if signal contains only frequencies below $\frac{1}{2}f_{\text{samp}}$. This is the *Nyquist limit*.


Amplitude Quantisation

- ◆ Amplitude of each sample can only take one of a finite number of different values.
- ◆ This adds quantisation noise: an irreversible corruption of the signal.
- ◆ For low amplitude signals it also adds distortion. This can be eliminated by adding dither before sampling.

Quantisation Noise

- ◆ V_{OUT} is restricted to discrete levels so cannot follow V_{IN} exactly. The error, $V_{OUT} - V_{IN}$ is the quantisation noise and has an amplitude of $\pm \frac{1}{2}$ LSB.
- ◆ If all error values are equally likely, the RMS value of the quantisation noise is:
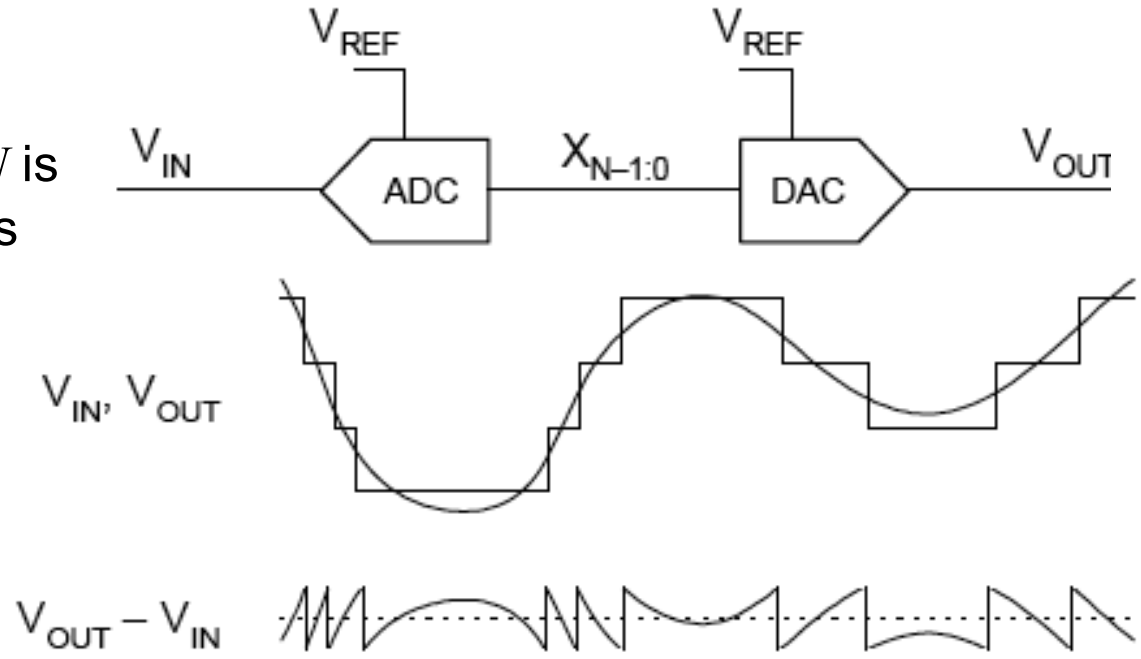
$$\sqrt{\int_{-\frac{1}{2}}^{+\frac{1}{2}} x^2 dx} = \frac{1}{\sqrt{12}} = 0.3 \text{ LSB}$$




Signal-to-Noise Ratio (SNR) for an n-bit converter

- ◆ Ratio of the maximum sine wave level to the noise level:
 - Maximum sine wave has an amplitude of $\pm 2^{n-1}$ which equals an RMS value of $0.71 \times 2^{n-1} = 0.35 \times 2^n$.
 - SNR is:


$$20 \log_{10} \left(\frac{0.35 \times 2^n}{0.3} \right) = 20 \log_{10} (1.2 \times 2^n) = 1.8 + 6n \text{ dB}$$

Threshold Voltages

 


- ◆ Each value of X corresponds to a range of values of V_{IN} .
- ◆ The voltage at which V_{IN} switches from one value of X to the next is called a **threshold voltage**.
- ◆ The task of an A/D converter is to discover which of the voltage ranges V_{IN} belongs to. To do this, the converter must compare V_{IN} with the threshold voltages.
- ◆ The threshold voltages corresponding to X are at $(X \pm \frac{1}{2})$ LSB


Flash A/D Converter

 

 - ◆ For an n -bit converter we have $2^n - 1$ **threshold voltages**
- ◆ Use $2^n - 1$ comparators:
- ◆ Resistor chain used to generate threshold voltages
- ◆ Priority encoder logic must determine the highest G_n input that equals 1.
- ◆ 12-bit converter needs 4095 comparators on a single chip!
- ◆ This example shows a unipolar converter




A Naïve ADC using a counter

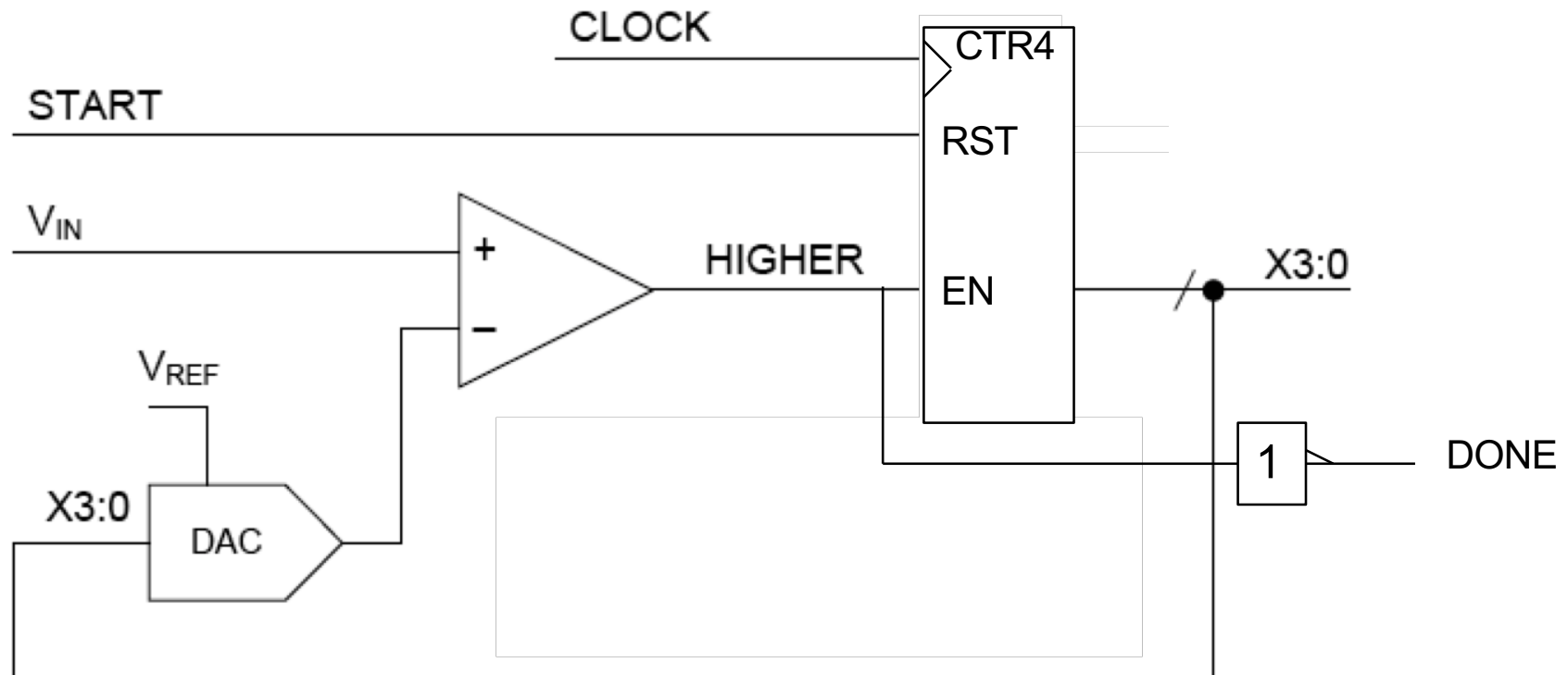


- ◆ Here is a simple ADC using a DAC, a comparator and a binary up counter.

Successive Approximation ADC (1)

 


- ◆ First guess: set MSB to 1
- ◆ Set test voltage to 4V
- ◆ Is input $\geq 4V$?
- ◆ If input $\geq 4V$, X = 1???, keep MSB
else X = 0???, clear MSB

Successive Approximation ADC (2)

 


- ◆ Second guess: set next bit to 1 ($X = 0100$)
- ◆ Set test voltage to 2V
- ◆ Is input $\geq 2V$?
- ◆ **If input $\geq 2V$, $X = 01??$, keep bit as 1**
else $X = 00??$, clear bit to 0

Successive Approximation ADC (3)

 


- ◆ Third guess: set next bit to 1 ($X = 0110$)
- ◆ Set test voltage to 3V
- ◆ Is input $\geq 3V$?
- ◆ If input $\geq 3V$, $X = 011?$, keep bit as 1
else $X = 010?$, clear bit to 0

Successive Approximation ADC (4)

 

- ◆ Fourth guess: set next bit to 1 ($X = 0101$)
- ◆ Set test voltage to 2.5V
- ◆ Is input $\geq 2.5V$?
- ◆ **If input $\geq 2.5V$, $X = 0101$, keep bit as 1**
else $X = 0100$, clear bit to 0
- ◆ Make successive guesses and use a comparator to tell whether your guess is too high or too low.
- ◆ Each guess determines one bit of the answer and cuts the number of remaining possibilities in half.



Successive Approximation ADC (5)

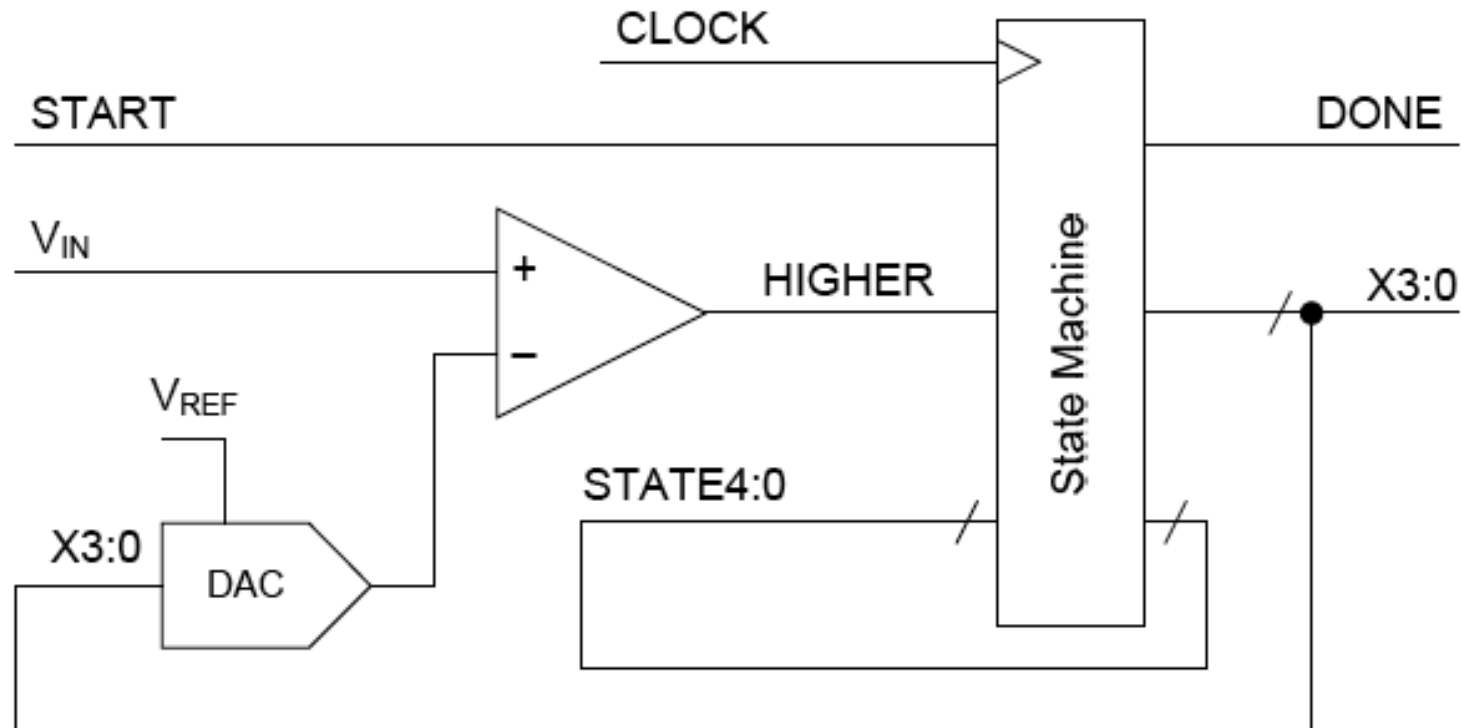


- ◆ Use a DAC to generate the threshold voltages and a state machine to create the sequence of guesses
- ◆ A DAC input of n generates the threshold between $n-1$ and n which equals $(n-\frac{1}{2}) \times 1 \text{ LSB}$

A/D conversion with sample/hold

  - ◆ Input switch is opened during the conversion so V_{ADC} remains constant (HOLD).
- ◆ Choice of C is a compromise:
 - Big C keeps constant voltage despite leakage currents since $dV/dt = I_{leakage}/C$
 - Small C allows faster acquisition time for any given input current since $dV/dt = I_{in}/C$.



Sample/Hold Circuit

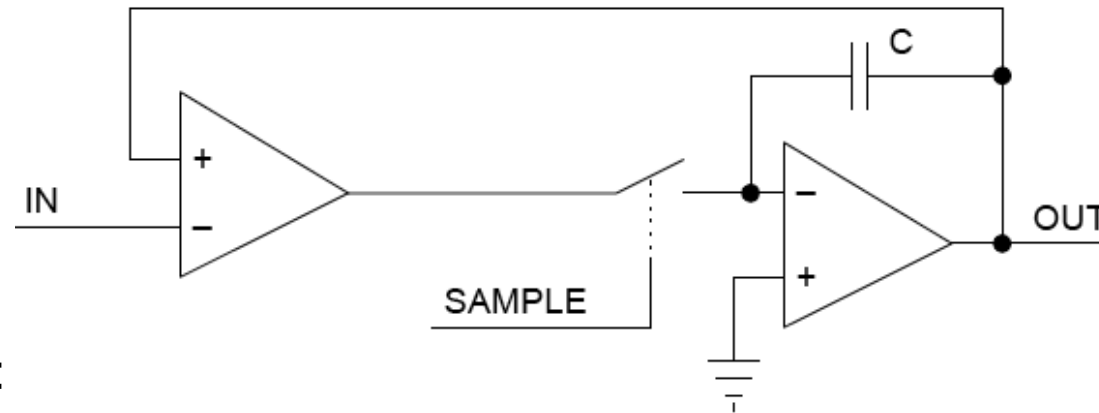



- ◆ When switch is open:
 - Leakage currents through open switch and op-amp input will cause output voltage to drift up or down.
 - Choose capacitor large enough that this drift amounts to less than 0.5 LSB during the time for a conversion
 - Converters with high resolution or long conversion times need larger capacitors
- ◆ When switch closes:
 - Charge rate of capacitor is limited by the maximum op-amp output current. This determines the **acquisition time**: to acquire the signal to within $\frac{1}{2}$ LSB. It is typically of the same order as the conversion time.
- ◆ Value of C is a compromise: big C gives slow acquisition, small C gives too much drift.

ADC used in Lab

- ◆ **Microchip MCP3201** 12-bit ADC
- ◆ Uses **successive approximation** architecture
- ◆ Serial Peripheral Interface (SPI)

Features

 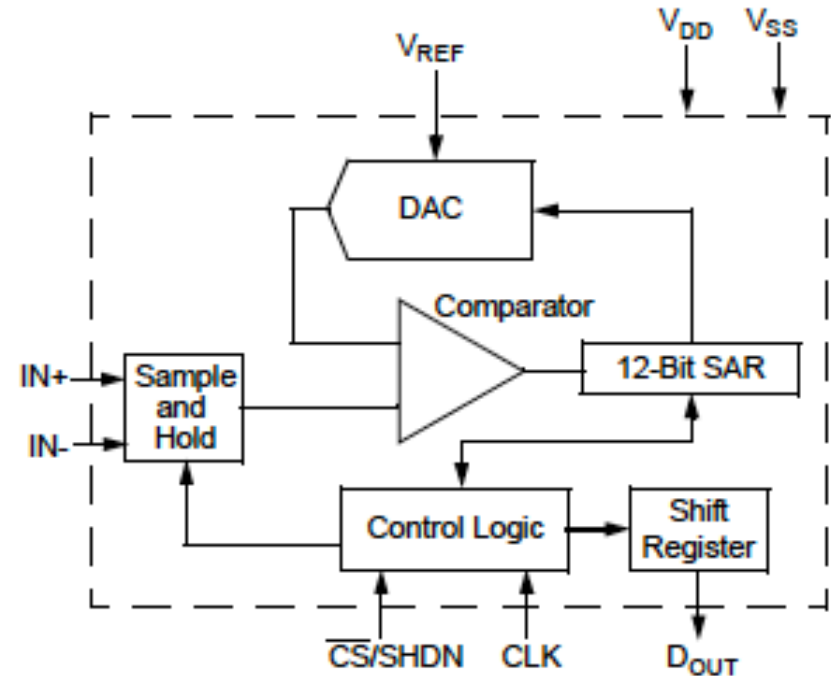- 12-Bit Resolution
- ± 1 LSB max DNL
- ± 1 LSB max INL (MCP3201-B)
- ± 2 LSB max INL (MCP3201-C)
- On-chip Sample and Hold
- SPI Serial Interface (modes 0,0 and 1,1)
- Single Supply Operation: 2.7V - 5.5V
- 100 ksp/s Maximum Sampling Rate at $V_{DD} = 5V$
- 50 ksp/s Maximum Sampling Rate at $V_{DD} = 2.7V$



Other types of Converter

Sampling ADC

- ◆ Many A/D converters include a sample/hold within them: these are *sampling* A/D converters.

Oversampling DAC and ADC

- ◆ *Oversampling* converters (also known as sigma-delta $\Sigma\Delta$ or delta-sigma $\Delta\Sigma$ converters) sample the input signal many times for each output sample. By combining digital averaging with an error feedback circuit they can obtain up to 20 bits of precision without requiring a high accuracy resistor network (hence cheaper). A typical oversampling ratio is 128X, i.e. the input is sampled at 6.4MHz to give output samples at 50 kHz. Most CD players use an oversampling DAC.