

Lecture 3

The Anatomy of an Op-Amp

Prof Peter YK Cheung
Imperial College London

URL: www.ee.ic.ac.uk/pcheung/teaching/EE2_CAS/
E-mail: p.cheung@imperial.ac.uk

What you should know already?

Imperial College
London

EE1 Analogue Electronics

C-E Amplifier Revisited Quiescent Analysis

- KVL on input side

$$V_{BIAS} = I_B R_B +$$

and $V_{BE} \approx 0.7$ V, $I_E =$

$$\Rightarrow I_E \approx \frac{V_E}{R_E}$$

- As before:

$$V_E = I_E R_E$$

Imperial College
London

EE1 Analogue Electronics

BJT Current Mirror

INPUT SIDE



- For transistors identical apart from


$$I \approx I_{REF}$$

where we have used $I_S \propto A$, and

Imperial College
London

EE1 Analogue Electronics

The Differential Pair – large signal



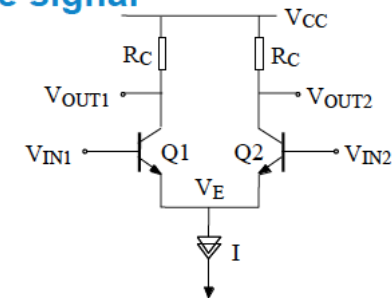


- If transistors are matched, then:

$$I_{C1} = \frac{I}{1 + \exp(-V_D/V_T)} \quad I_{C2} = \frac{I}{1 + \exp(V_D/V_T)}$$

$V_D = (V_{IN1} - V_{IN2})$ is the DIFFERENTIAL INPUT VOLTAGE

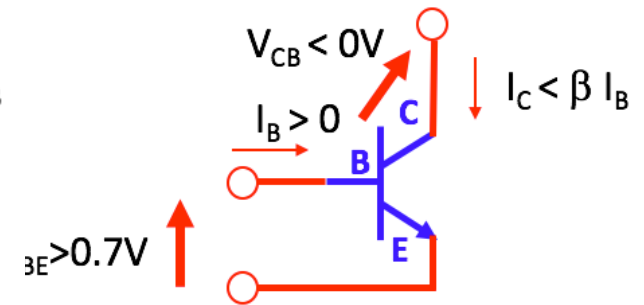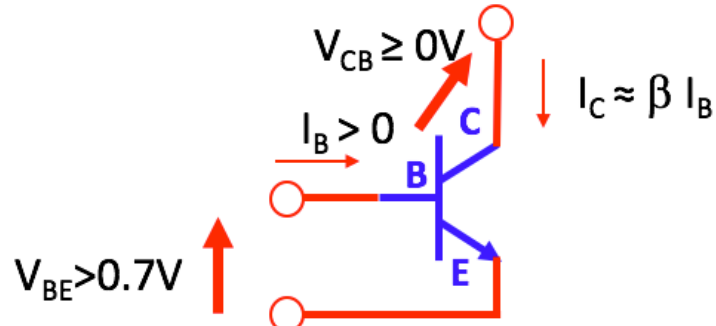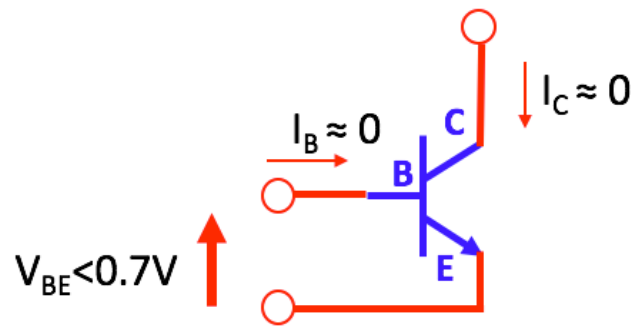Rules of thumb – Bipolar Junction Transistor (BJT)




- ❖ $V_{BE} < 0.7V$
- ❖ Transistor OFF
- ❖ Near zero I_B and I_C (except leakage)
- ❖ Good for digital circuits

- ❖ $V_{BE} \geq 0.7V$
- ❖ BC junction diode reverse biased
- ❖ Transistor in linear/active region
- ❖ $I_C \approx \beta I_B$ applies
- ❖ Good for analogue circuits

- ❖ $V_{BE} \geq 0.7V$
- ❖ BC junction diode NOT reverse biased
- ❖ Transistor in saturation region
- ❖ $I_C < \beta I_B$
- ❖ Good for digital circuits


NPN Transistor in Linear Region

Common-emitter amp (Class A)

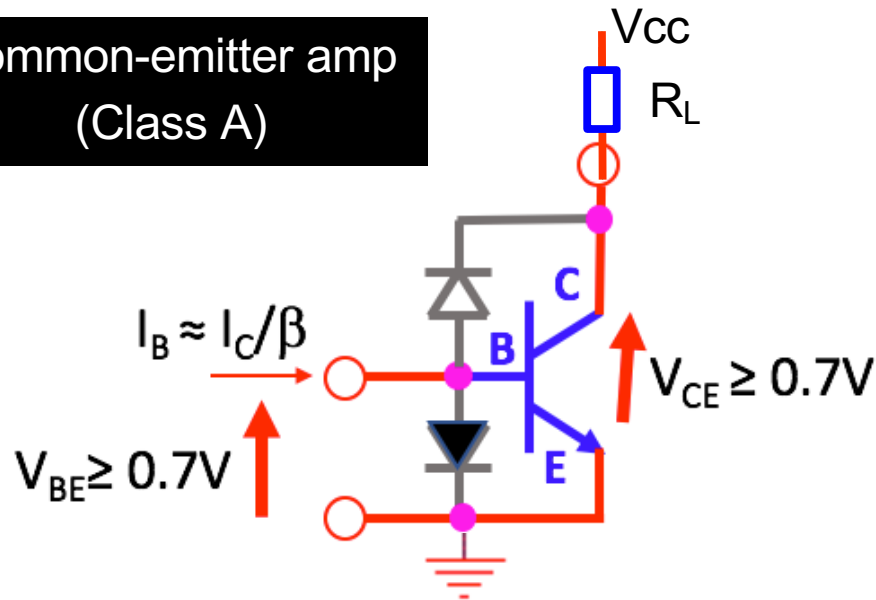


- ❖ BE junction diode forward biased (ON)
- ❖ BC junction diode reverse biased (OFF)
- ❖ I_C is often determined by **DC bias circuit**
- ❖ I_B then fixed by β
- ❖ V_{CE} can take on any value between 0.3V and V_{CC}

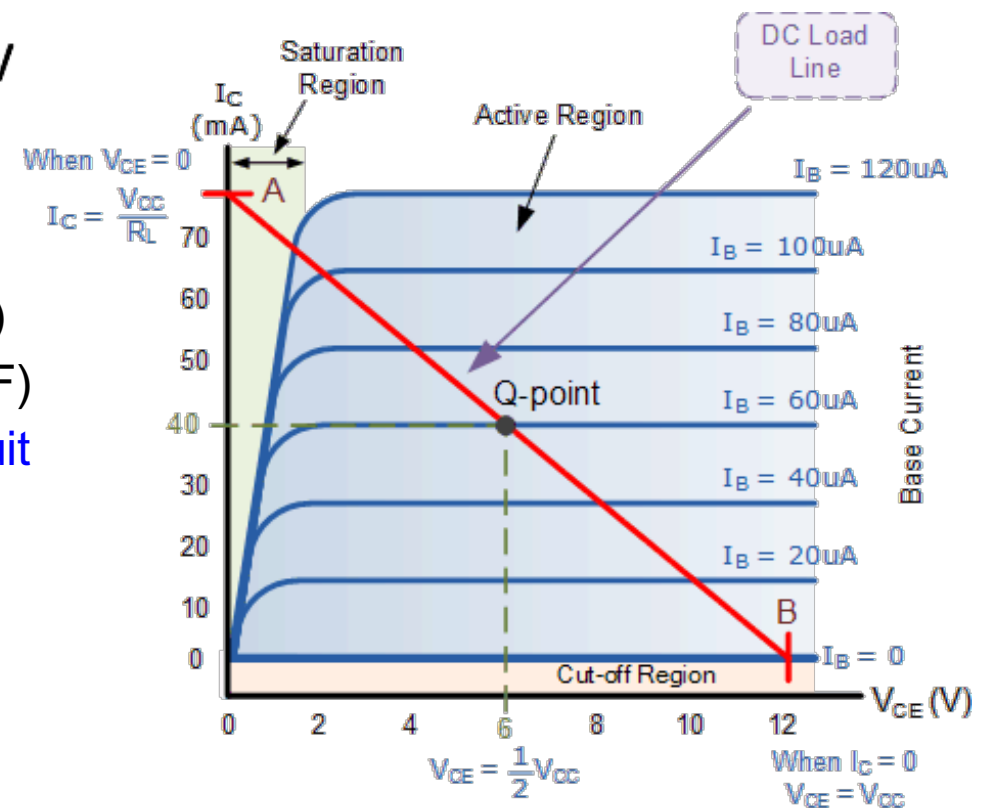- ❖ Quiescent (DC) condition – **biasing**
- ❖ Ensures transistor in **linear region**
- ❖ **Operating condition** determined by I_C
- ❖ Use large signal model



Small signal behaviour of NPN transistor

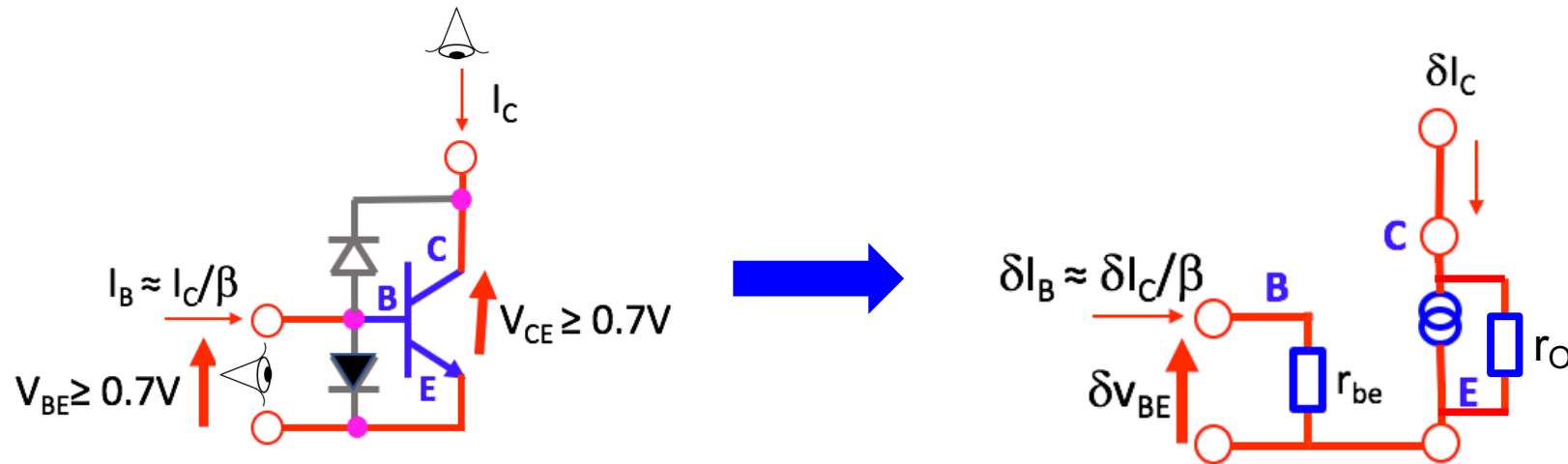

- ❖ Quiescent I_C determine operating point
- ❖ Small signal model – 2 resistors r_{be} and r_o , and a current source


- ❖ $\delta i_B = \delta v_{BE} / r_{BE}$
- ❖ $\delta i_C = g_m \delta v_{BE}$
- ❖ $\delta i_E = \delta i_B + \delta i_C$

- ❖ r_o large - can be omitted


- ❖ current gain: $\beta = \delta i_C / \delta i_B$
- ❖ transconductance: $g_m = \delta i_C / \delta v_{BE} = I_C / V_T$
- ❖ Input resistance: $r_{be} = \delta v_{BE} / \delta i_B = \beta V_T / I_C$

Inside a typical op-amp

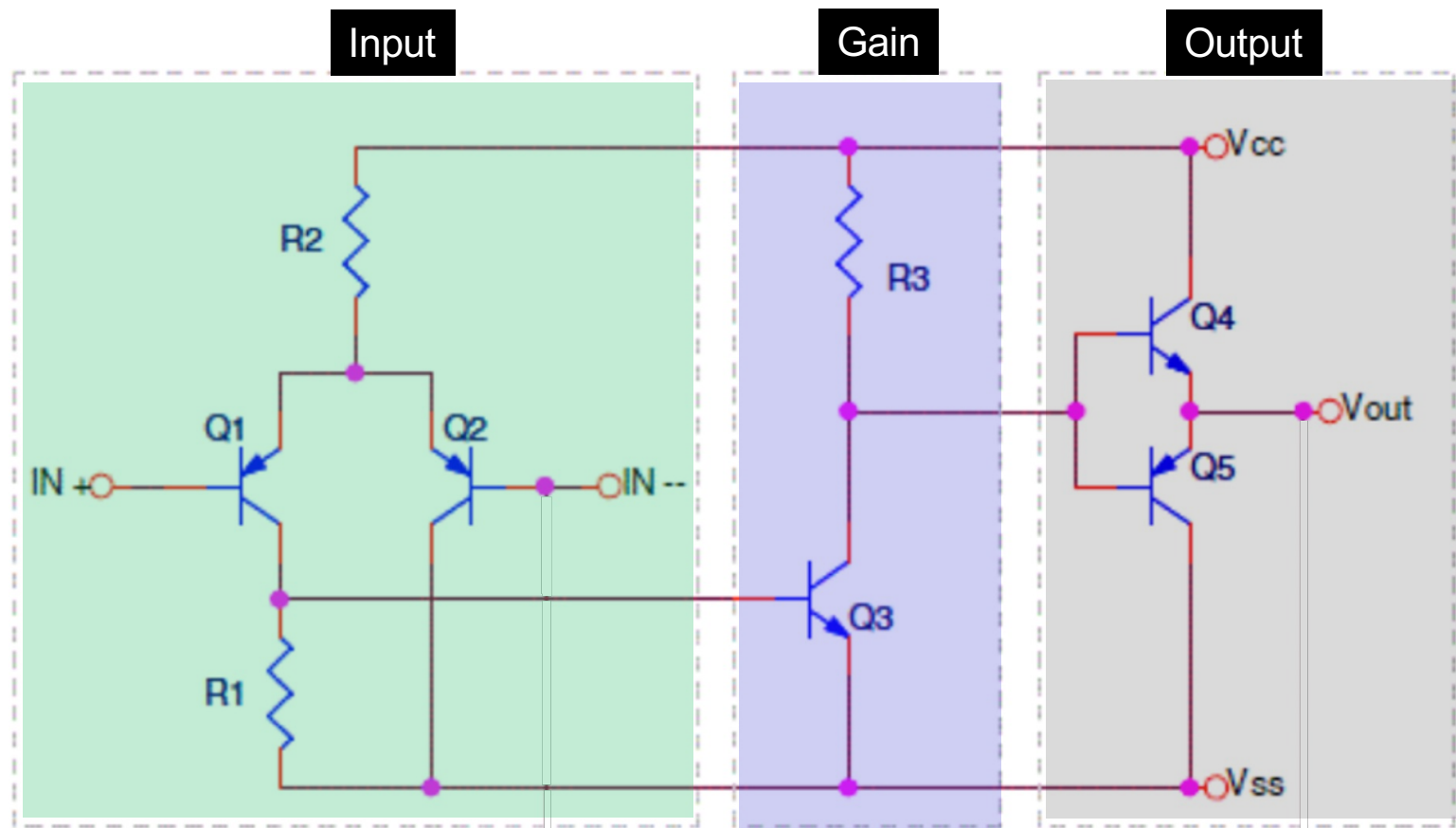- ❖ Three stages architecture:
 1. **Differential input stage** – long-tail pair (Yr 1 Circuits part 2, adc_9, slides 8-14)
 2. **Voltage gain stage** – common emitter amp (adc_6, slides 3-7)
 3. **Output drive stage** – push-pull circuit



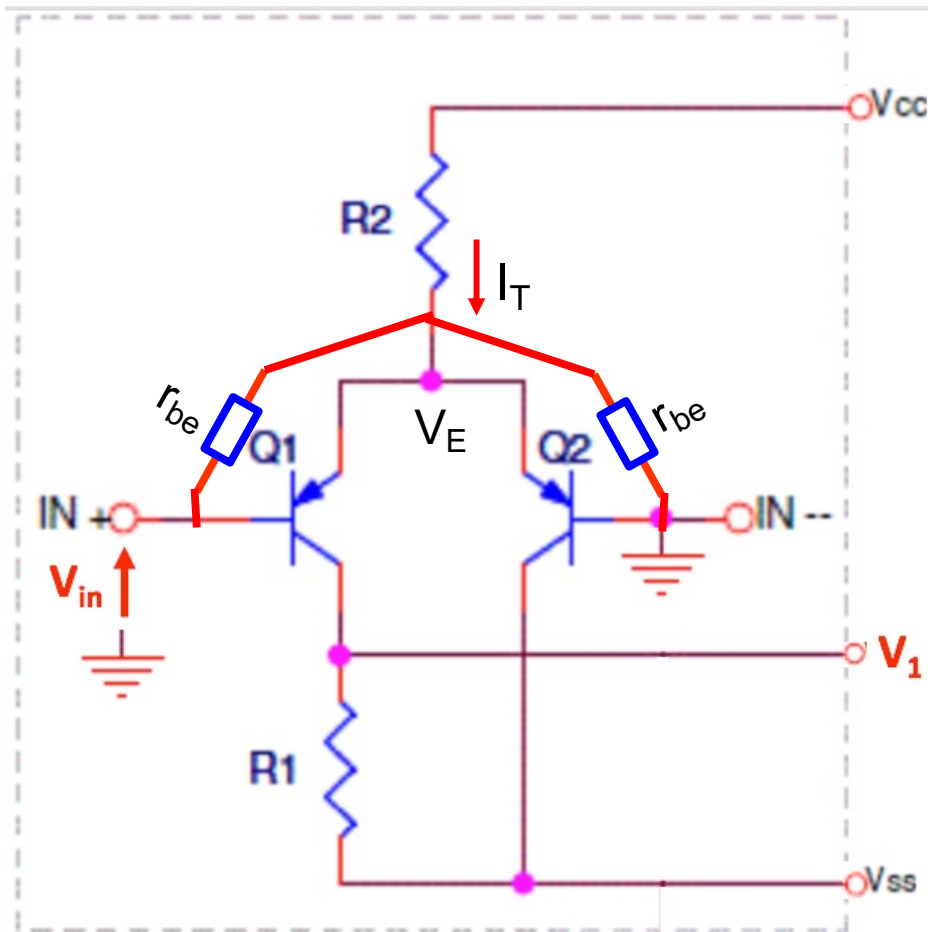Differential Input Stage – differential gain



$$A_{V_{diff}} = \delta v_1 / \delta v_{in} = -\frac{1}{2} g_m * R_1$$


Consider $V_{in} = 0$, IN - is grounded

- ❖ $V_E \approx 0.7V$
- ❖ $I_T \approx (V_{CC} - 0.7) / R_2$
- ❖ $I_1 \approx I_2 \approx \frac{1}{2} I_T \approx \frac{1}{2} (V_{CC} - 0.7) / R_2$
- ❖ $V_1 = R_1 * I_{C1} + V_{SS}$

Apply small input signal δV_{in}

- ❖ $\delta v_E \approx \frac{1}{2} \delta v_{in}$
- ❖ $\delta i_T \approx \frac{1}{2} \delta v_{in} / R_2 \approx 0$
- ❖ $\delta i_1 \approx -\delta i_2 = -g_m * \frac{1}{2} \delta v_{in}$
- ❖ $\delta v_1 = R_1 * \delta i_1 = -R_1 * g_m * \frac{1}{2} \delta v_{in}$

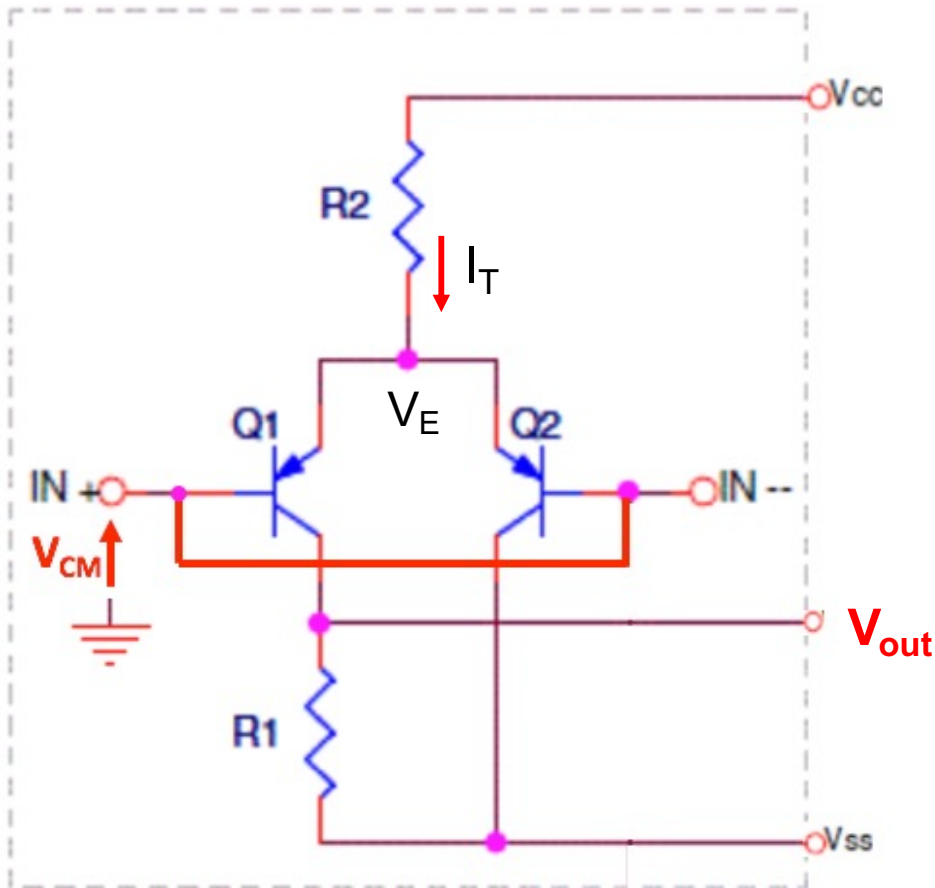Differential Input Stage – common mode gain




Apply v_{CM} to both inputs

- ❖ $\delta v_E \approx v_{CM}$
- ❖ $\delta i_T \approx -\delta v_E / R_2 = -v_{CM} / R_2$
- ❖ $\delta i_{C1} \approx \delta i_{C2} = \frac{1}{2} \delta i_T = -\frac{1}{2} v_{CM} / R_2$
- ❖ $\delta v_{out} \approx -R_1 / 2R_2 * v_{CM}$


$$A_{V_{cm}} = \delta v_{out} / v_{CM} = -R_1 / 2R_2$$

Small Signal Gain stage

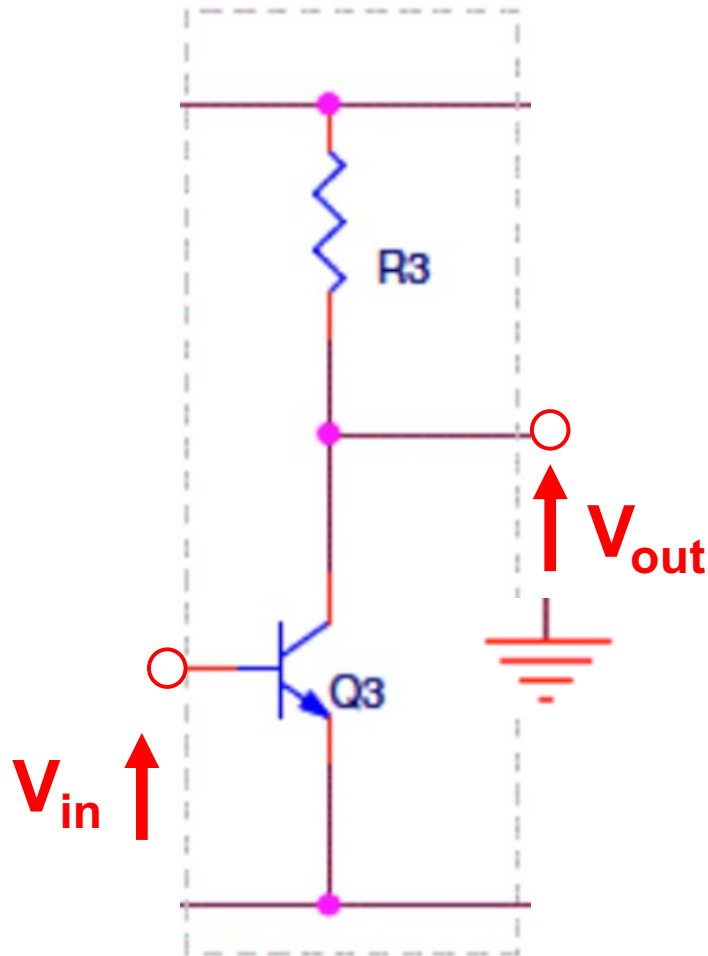

- ❖ Common Emitter amplifier (Yr 1st ADC part 2 Lecture 6, S7)
- ❖ $\delta v_{out} = -g_m \delta v_{in} * R_3$
- ❖ $A_V = \delta v_{out} / \delta v_{in} = -g_m R_3$
- ❖ Increase g_m and R_3
- ❖ Most of the voltage gain produced by this stage

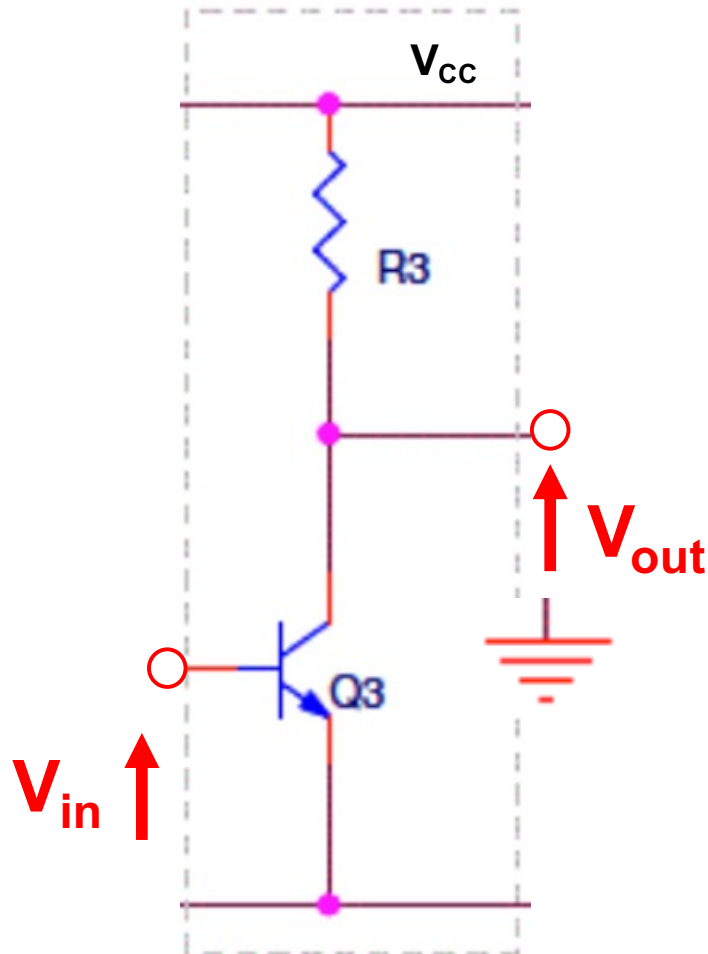
Gain stage is not suitable to drive output load



- ❖ Common-emitter amplifier is also called a **Class A amplifier** (name does not matter)
- ❖ R3 is the load (e.g. speaker)
- ❖ Transistor Q3 works throughout the entire cycle of a sine signal (360°)
- ❖ Very poor power efficiency:

$$\text{efficiency } \eta = \frac{\text{power to load } R_3}{\text{Power from supply}} < 25\%$$

Efficiency of a class A amplifier

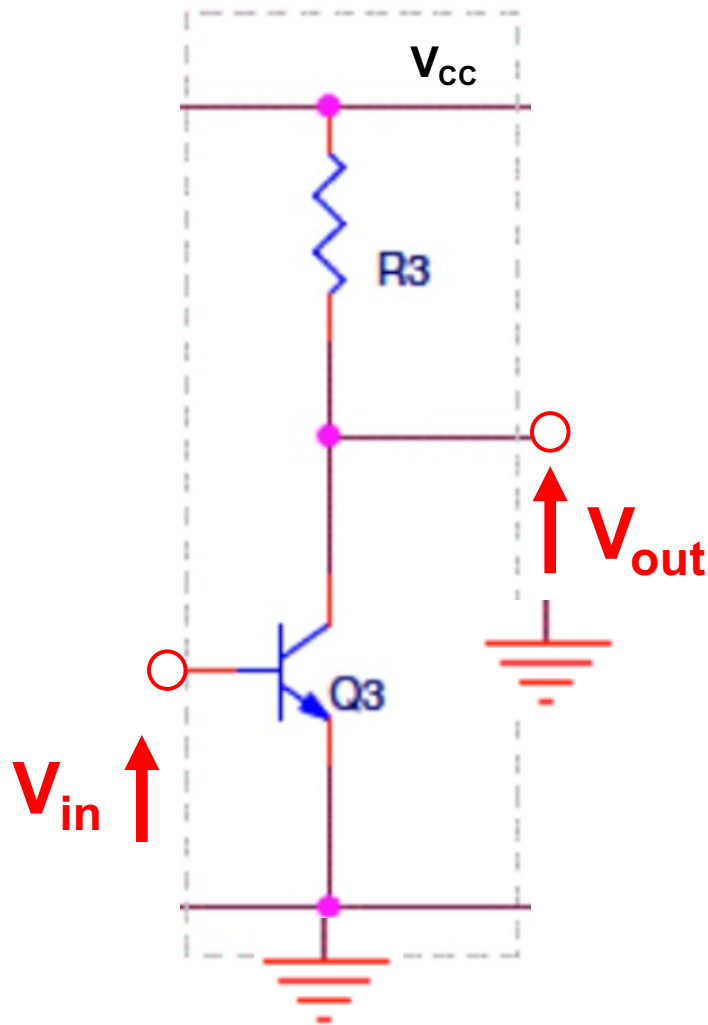

- ❖ Assume V_{out} at quiescent (i.e. no input) is biased to be at $V_{CC}/2$
- ❖ Quiescent collector current $I_{CQ} = (V_{CC}/2) * R3$
- ❖ Average power drawn from supply voltage is:

$$P_i(dc) = V_{CC} I_{CQ} = \frac{V_{CC}^2}{2 * R3}$$

- ❖ AC power delivered to load R3 is:

$$P_o(ac) = \frac{V_{out}(rms)^2}{R3}$$


- ❖ P_o is maximum when $V_{out(pk-pk)} = V_{CC}$, i.e. maximum output voltage swing

- ❖ Or $V_{out}(rms) = V_{CC}/2\sqrt{2}$

- ❖ Therefore $\max P_o(ac) = \frac{V_{CC}^2}{8R3}$


- ❖ Hence $\max \eta = \frac{\text{maximum } P_o(ac)}{P_i(dc)} = \frac{V_{CC}^2/8R3}{V_{CC}^2/2R3} = \frac{1}{4}$

Output Stage

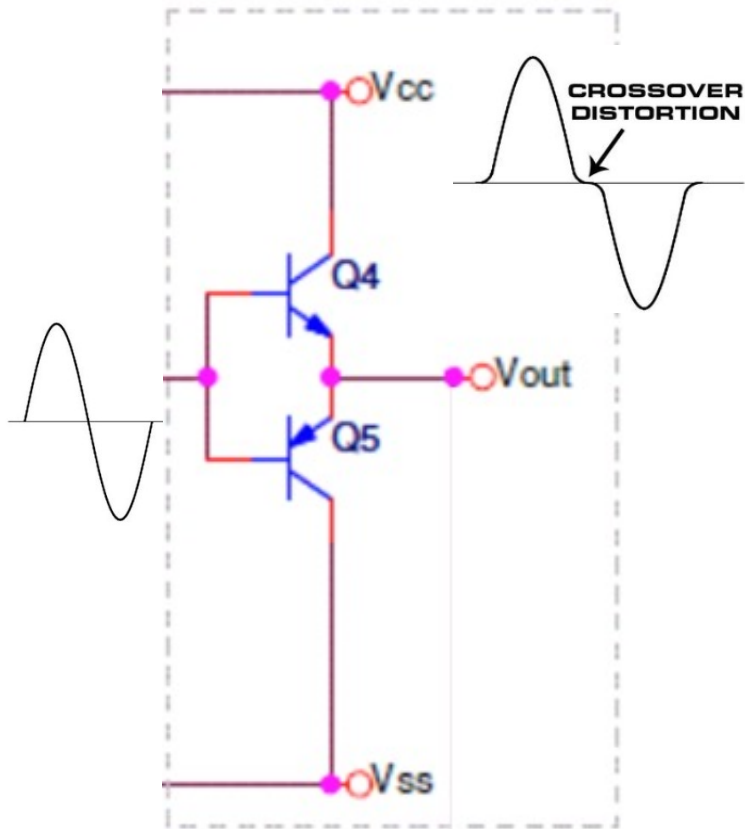

- ❖ Yr 1st ADC part 2 Lecture 6, S3-5
- ❖ Q4 is emitter follower (Common-Emitter) for sourcing current to Vout (PUSH)
- ❖ Q5 is another emitter follower for sinking current from Vout (PULL)
- ❖ This is known as a PUSH-PULL or class B amplifier circuit
- ❖ $\delta V_{out} \approx \delta V_{in}$, i.e. its gain is 1
- ❖ Each transistor only operate for half cycle or 180° of a sinewave signal
- ❖ Further, Q4 and Q5 requires $V_{BE} > 0.7V$ to start conducting, therefore this amplifier has distortion.

Push-pull (Class B) amplifier efficiency

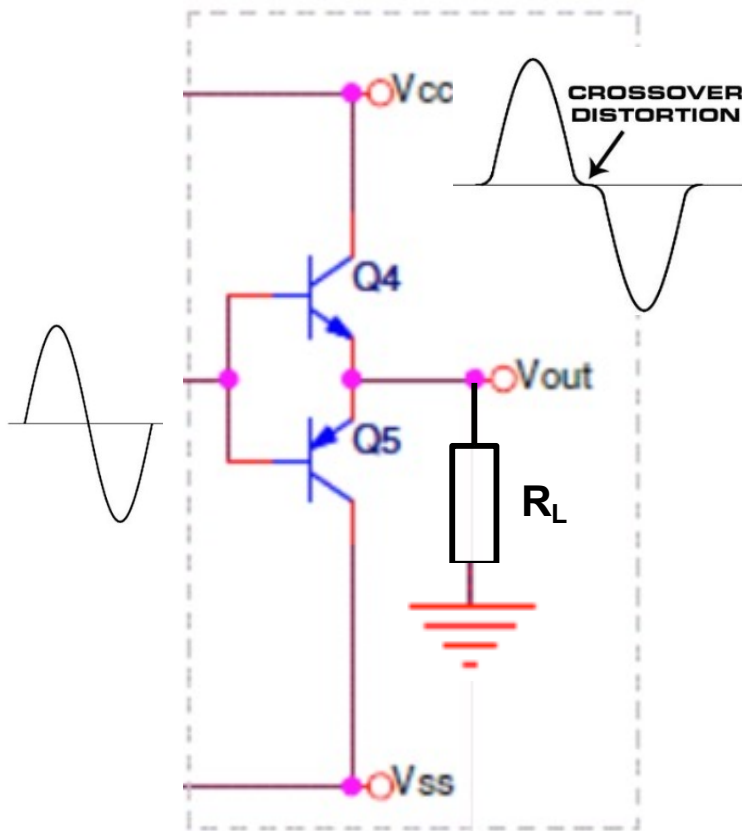

- ❖ Assume $V_{ss} = -V_{cc}$ for simplicity, output swing is $\pm V_{pk}$ and $V_{pk} = V_{cc}$.

- ❖ Q4 and Q5 conduct only for half cycle, hence

$$\text{DC supply power } P_i(dc) = V_{CC} I_{DC}$$

- ❖ Average current is that of a full-wave rectified signal: $I_{DC} = \frac{2}{\pi} I_{pk}$ where I_{pk} is the peak output current.

- ❖ Hence $I_{DC} = \frac{2}{\pi} \left(\frac{V_{pk}}{R_L} \right)$, and $P_i(dc) = \frac{2}{\pi} \left(\frac{V_{CC}^2}{R_L} \right)$

- ❖ Output AC power is (from before)


$$P_o(ac) = \frac{V_{out(pk-pk)}^2}{8R_L} = \frac{(2V_{pk})^2}{8R_L} = \frac{V_{CC}^2}{2R_L}$$

- ❖ Hence $\eta = \frac{P_o(ac)}{P_i(dc)} = \frac{V_{CC}^2/2R_L}{\frac{2}{\pi} \left(\frac{V_{CC}^2}{R_L} \right)} = \frac{\pi}{4} = 78.5\%$

Driving 8Ω speaker with LM386

LM386 Low Voltage Audio Power Amplifier



Amplifier with Gain = 20 Minimum Parts

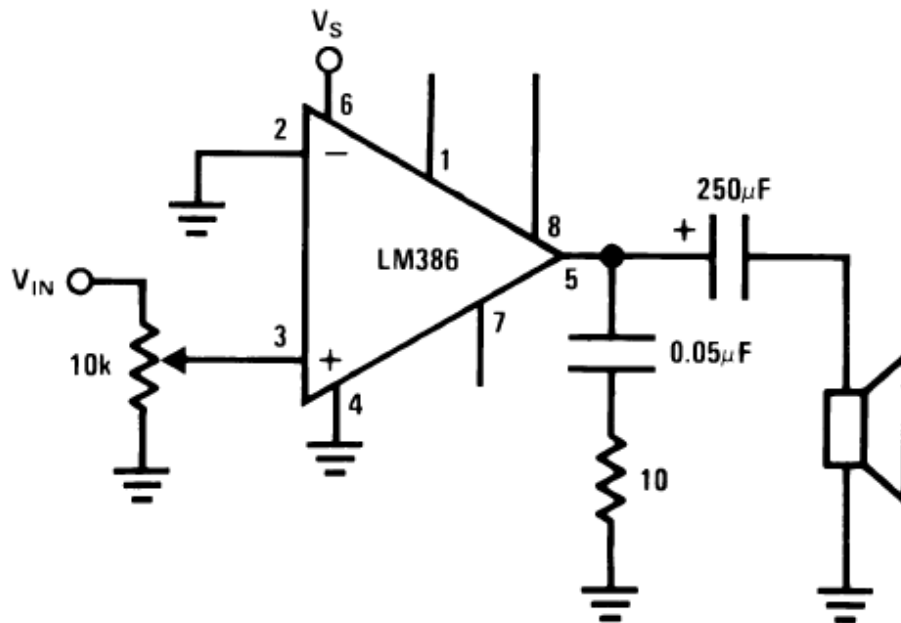

Features

- Battery operation
- Minimum external parts
- Wide supply voltage range: 4V–12V or 5V–18V
- Low quiescent current drain: 4mA
- Voltage gains from 20 to 200
- Ground referenced input
- Self-centering output quiescent voltage
- Low distortion: 0.2% ($A_V = 20$, $V_S = 6V$, $R_L = 8\Omega$, $P_O = 125mW$, $f = 1kHz$)
- Available in 8 pin MSOP package

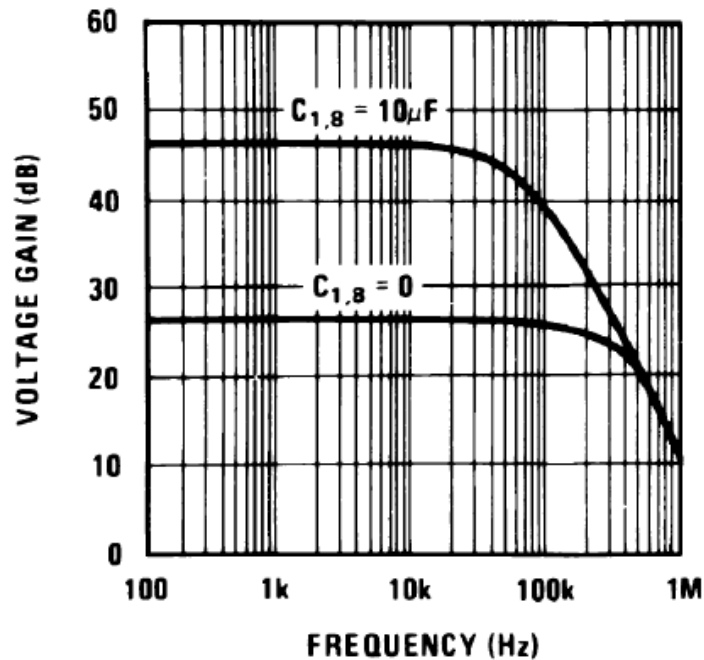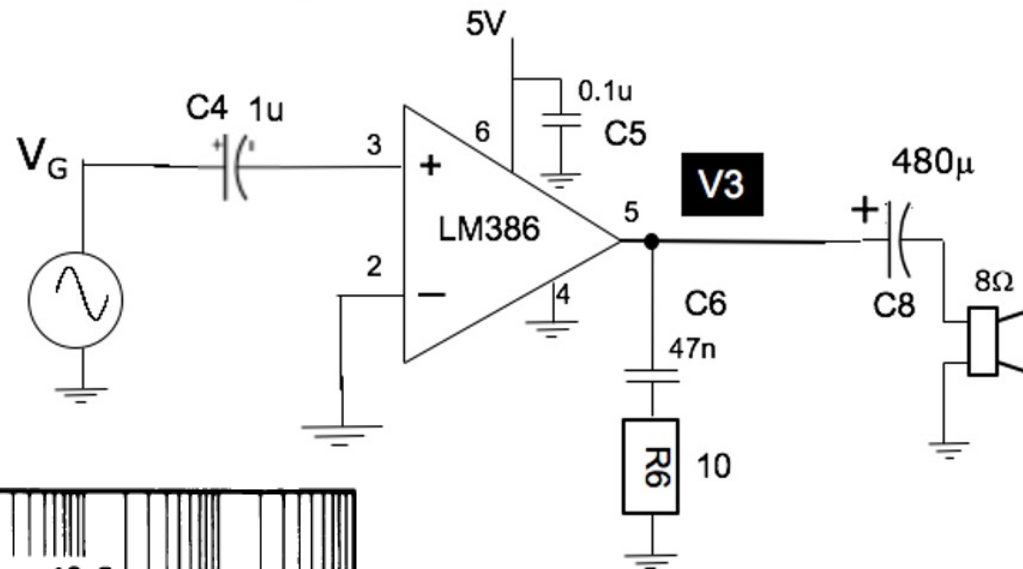LM386 as a practical x20 amplifier (Lab 1)



- ❖ LM386 provides x20 gain
- ❖ Drives 8 ohm speaker
- ❖ C4 and C8 – blocking DC
- ❖ C6, R6, compensate for series inductance in 8 ohm speaker