

Lecture 8

Digital-to-Analogue Conversion

Peter Cheung
Imperial College London

URL: www.ee.imperial.ac.uk/pcheung/teaching/EE2_CAS/
E-mail: p.cheung@imperial.ac.uk


Lecture Objectives

- ◆ Understand **pulse-width modulated** (PWM) DAC
- ◆ Understand how a **weighted-resister DAC** can be used to convert numbers with binary or non-binary bit weightings
- ◆ Understand the meaning of the terms used to **specify DAC accuracy**
- ◆ Understand **resistor string based DAC** architecture
- ◆ Understand how an **R-2R ladder** can be used to convert both unsigned and signed binary numbers
- ◆ Understand **multiplying DAC**


References:

- “Data Converter Architectures” in Data Conversion Handbook by Analog Devices

Analogue Pulse-width Modulated (PWM)

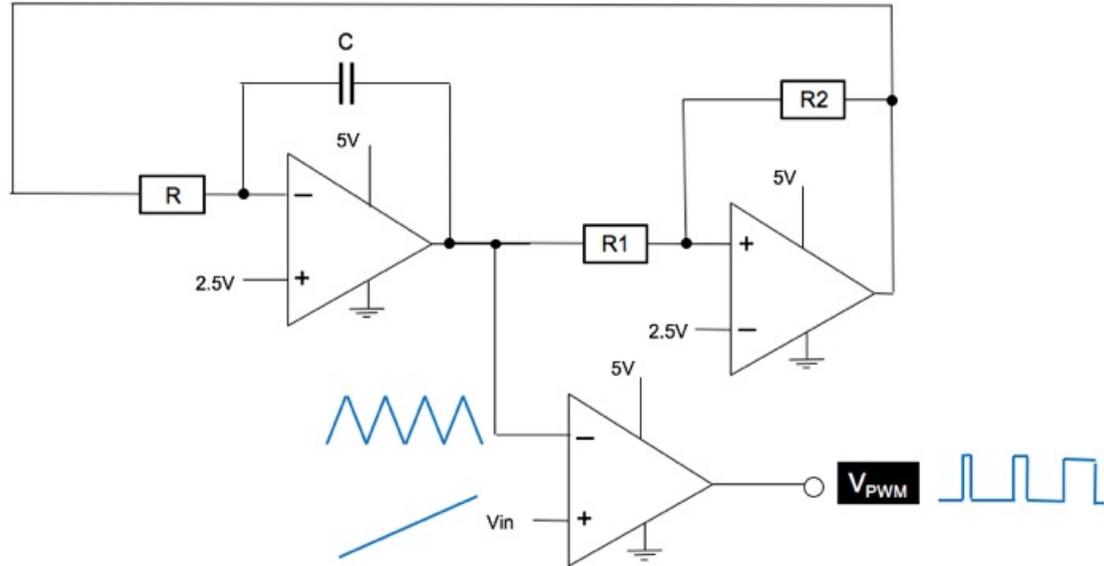


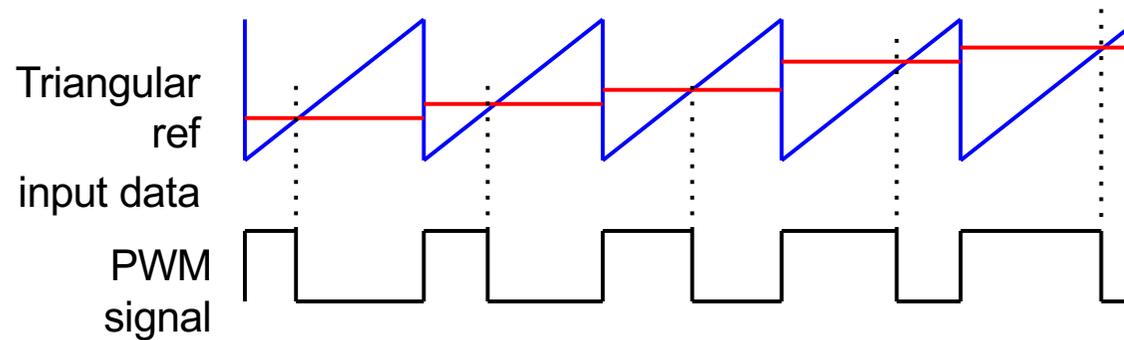- Simple idea: PWM signal is generated by comparing a triangular reference signal with the input data value




Digital Pulse-width Modulated (PWM) as DAC

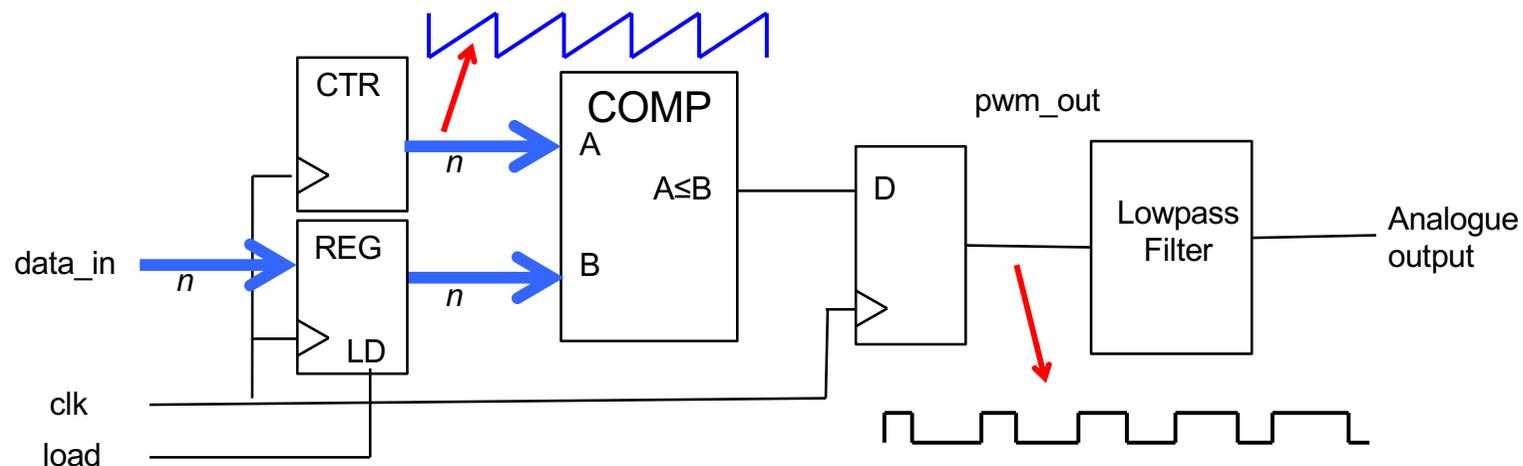- ◆ Sawtooth value generated by a wrap-around counter
- ◆ Load pulse latches **data_in** and stores it in register
- ◆ When input value is reached by counter, comparator output changes state (H to L)
- ◆ Lowpass filter provides analogue output voltage proportional to the duty cycle of PWM signal



PWM DAC in SystemVerilog

```
module pwm # (parameter WIDTH = 10)(
    input logic clk, // system clock
    input logic [WIDTH-1:0] data_in, // input data for conversion (limited to 10-bit)
    input logic load, // high pulse to load new data
    input logic [WIDTH-1:0] max, // maximum value of data_in
    output logic pwm_out // PWM output
);
    logic [WIDTH-1:0] d; // internal register
    logic [WIDTH-1:0] count; // internal 10-bit counter
```

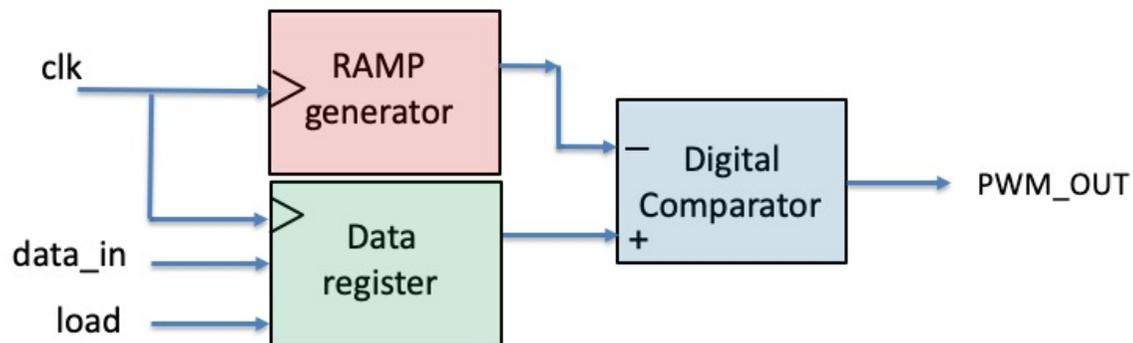

```
always_ff @ (posedge clk)
    if (load == 1'b1) d <= data_in;


initial count = {WIDTH{1'b0}};

always_ff @ (posedge clk) begin
    if (count == max)
        count <= {WIDTH{1'b0}};
    else
        count <= count + 1'b1;

    if (count >= d)
        pwm_out <= 1'b0;
    else
        pwm_out <= 1'b1;
end
```

Simple DAC

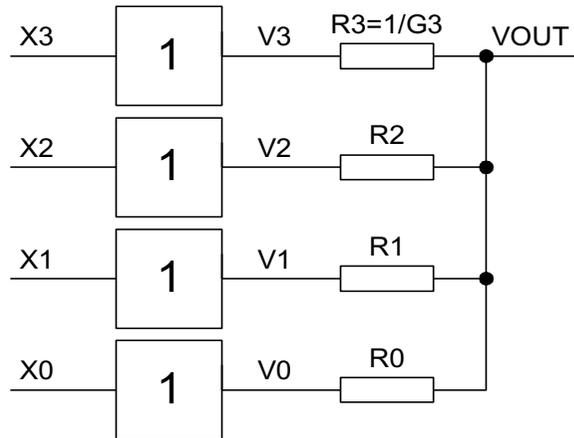- ◆ A DAC converts a binary number into a voltage proportional to its value:




$$(V_3 - V_{OUT})G_3 + \dots + (V_0 - V_{OUT})G_0 = 0$$

$$V_{OUT} = \frac{V_3G_3 + V_2G_2 + V_1G_1 + V_0G_0}{G_3 + G_2 + G_1 + G_0}$$

$$R_{Thevenin} = \frac{1}{G_3 + G_2 + G_1 + G_0}$$

- ◆ Hence V_{OUT} is a weighted sum of V_3, \dots, V_0 with weights proportional to the conductances G_3, \dots, G_0 .
 - If X3:0 is a binary number we want conductances in the ratio 8:4:2:1.
 - Very fast: gate slew rate > 3 V/ns.
 - We can scale the resistors to give any output impedance we want.
- ◆ You do not have to use a binary weighting
 - By using other conductance ratios we can choose arbitrary output voltages for up to five of the sixteen possible values of X3:0. May need additional resistors from VOUT to the power supplies.

Improved DAC with Output Op-Amp

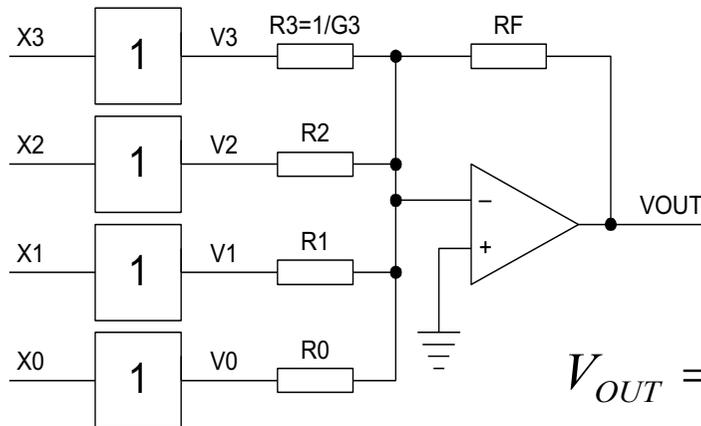

$$V_{OUT} = \frac{-R_F}{R_{Thévenin}} \times V_{Thévenin} = -R_F (V_3 G_3 + V_2 G_2 + V_1 G_1 + V_0 G_0)$$


◆ Adding an op-amp:

- The voltage at the junction of all the resistors (the **virtue earth** node) is now held constant by the feedback
 - Hence current drawn from V_3 is independent of the other voltages V_2, \dots, V_0
 - Hence any gate non-linearity has no effect \Rightarrow more accurate
- Lower output impedance
- Much slower: op-amp slew rate $\approx 1 \text{ V}/\mu\text{s}$


◆ Hard to make accurate resistors covering a wide range of values in an integrated circuit

- Weighted-resistor DAC is no good for converters with many bits

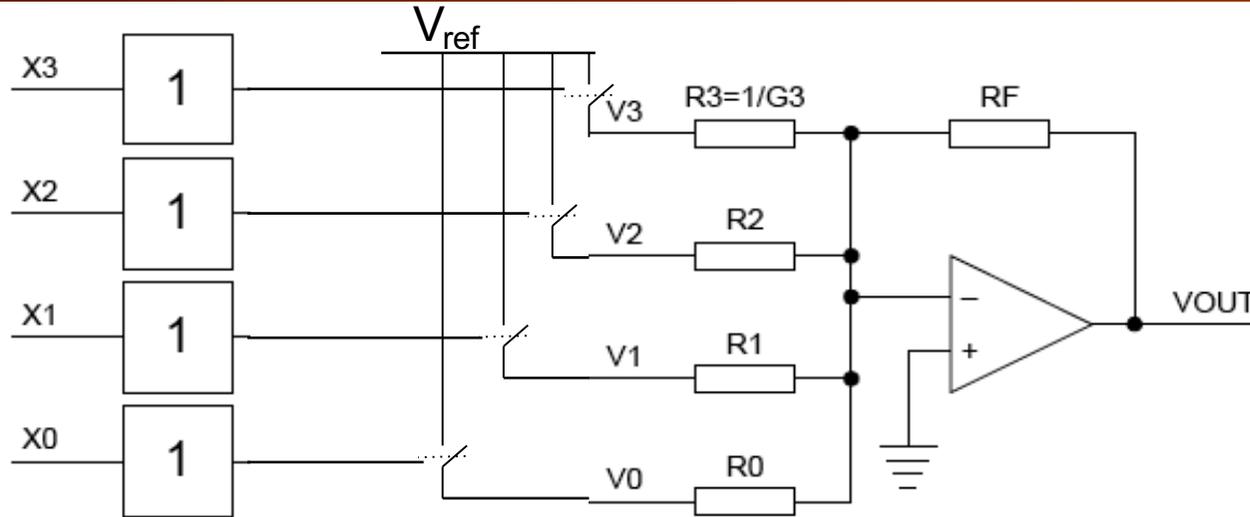
Further Improvement with reference voltage source



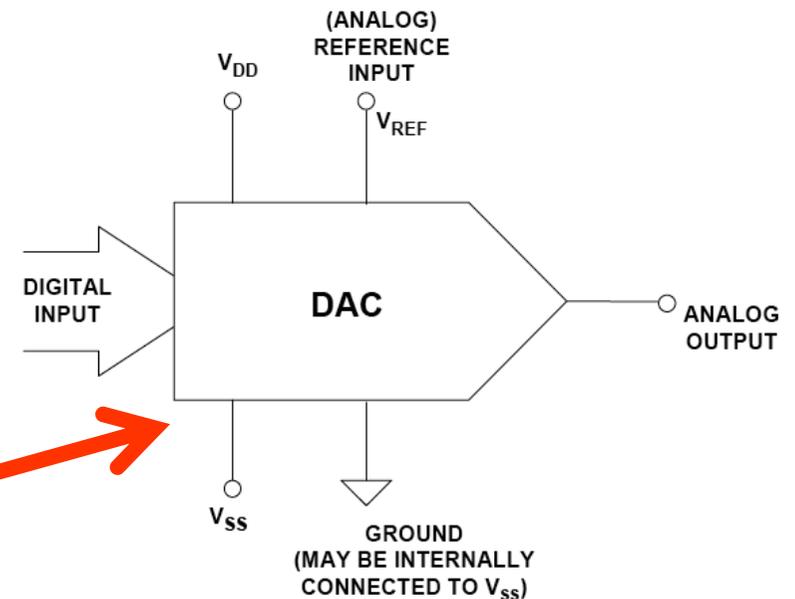- ◆ Use digital signal to control analogue switches
- ◆ Switching V_{ref} on/off the resistor network
- ◆ Clear separation between digital control and analogue voltages – much better accuracies
- ◆ General DAC block diagram:



DAC Specification Jargon

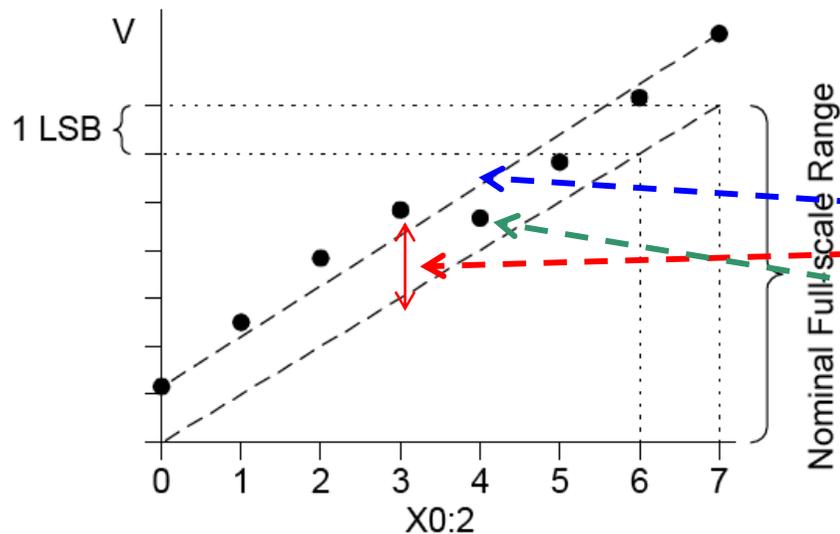

Accuracy=1.8@X=3 Linearity=-0.7@X=4
 Non-monotonic@3→4 Diff Linearity=-1.2@ 3→4
 (all in units of LSB)

◆ Resolution

- 1 LSB = ΔV when $X \rightarrow X+1$
= Full-scale range $\div (2^N - 1)$

◆ Accuracy

- Worst deviation from nominal line

◆ Linearity

- Worst deviation from line joining end points

◆ Differential Linearity

- Worst error in ΔV when $X \rightarrow X+1$
- measures smoothness


◆ Monotonic

- At least ΔV always has the correct sign

◆ Settling time


- Time taken to reach the final value to within some tolerance, e.g. $\pm \frac{1}{2}$ LSB

Thermometer DAC using Resistor String

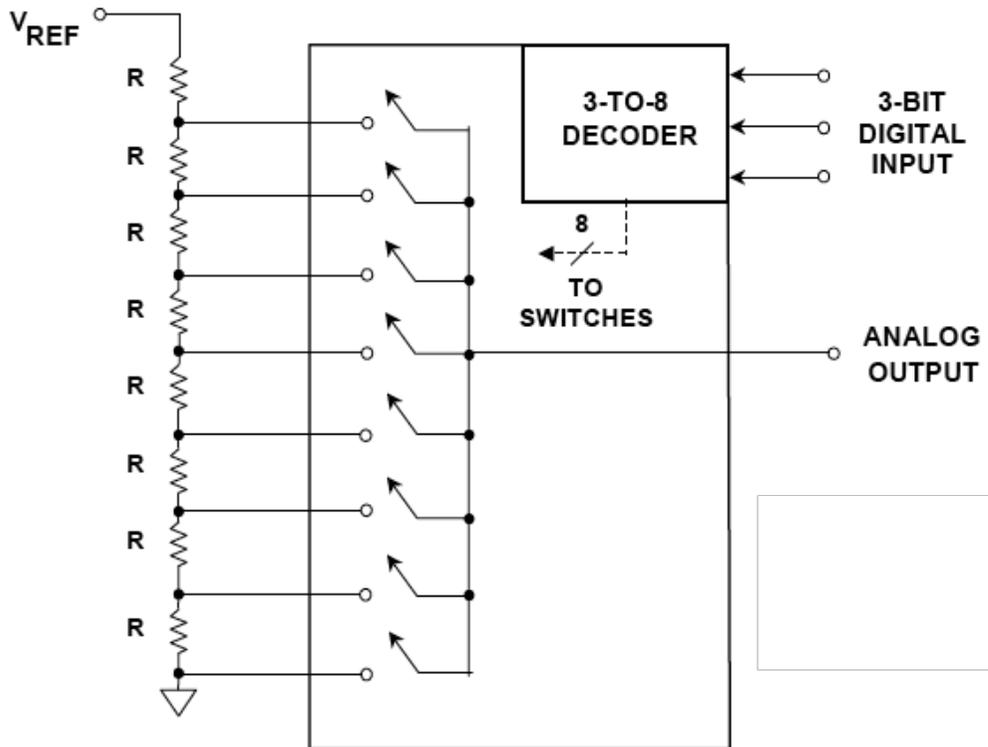

- ✓ Simple
- ✓ Inherently monotonic
- ✓ Needs only IDENTICAL resistors, good differential linearity
- ✓ Only two switches operate during a transition, low output glitch and fast settling
- ✓ Low power
- ✓ Widely use with modern technology with small feature sizes
- ✗ Large number of resistors
- ✗ Useful for low to medium resolution DAC
- ✗ Large resistance – resulting in higher noise

Resistor String DAC with Op-Amp output


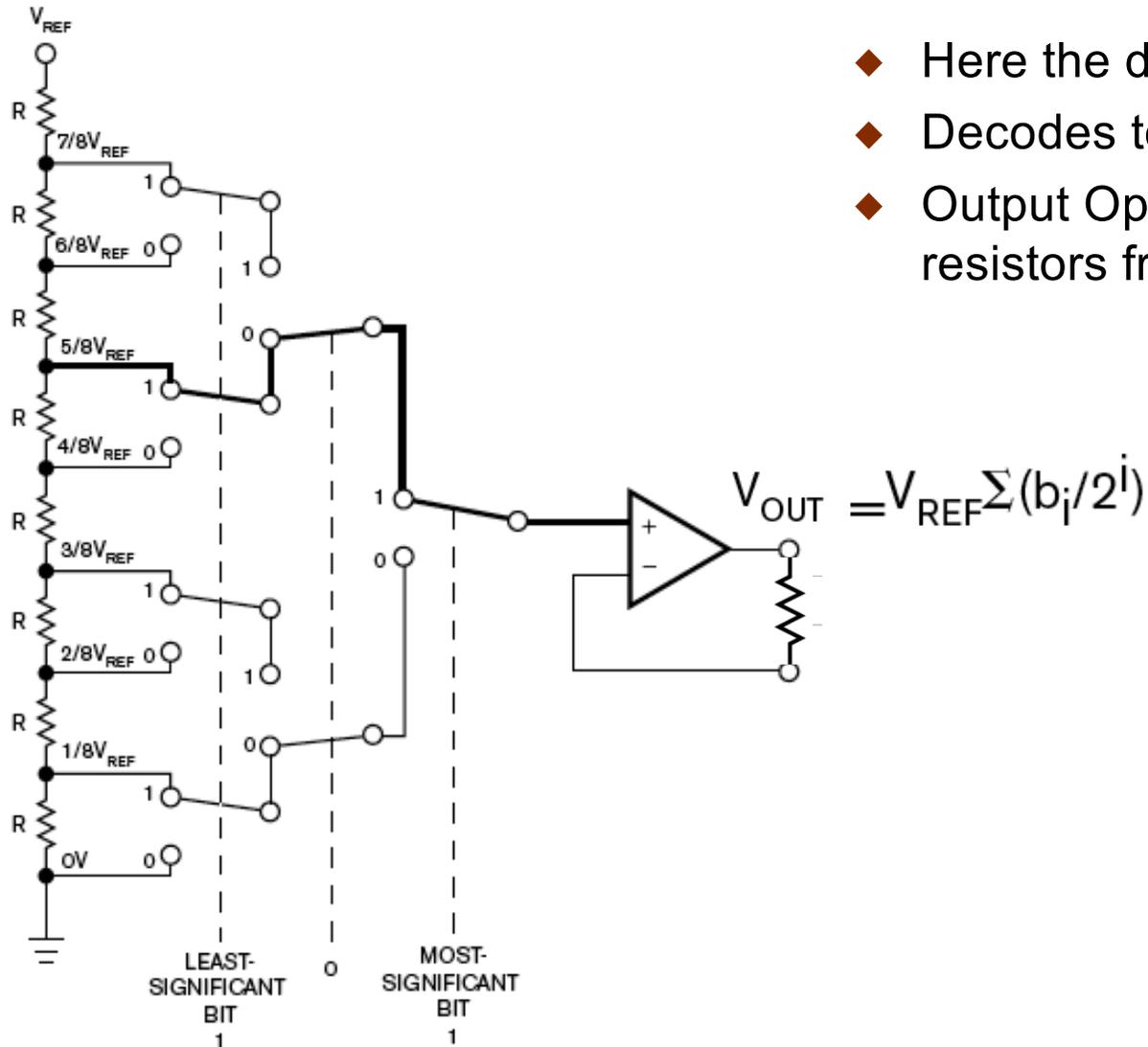


- ◆ Here the digital code is 3'b101
- ◆ Decodes to $5/8 V_{REF}$
- ◆ Output Op-amp isolate internal resistors from output load

DAC using R-2R Ladder

We want to generate currents $I_0, 2I_0, 4I_0, \dots$

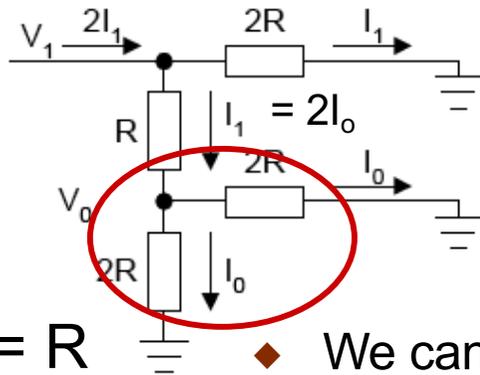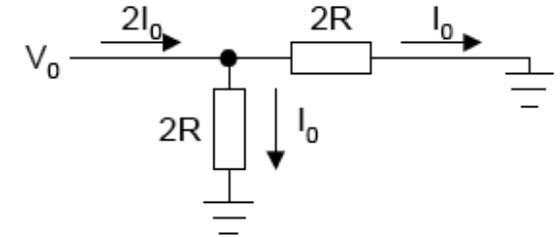- ◆ Two $2R$ resistors in parallel means that the $2I_0$ current will split equally and equivalent resistance R




- ◆ The Thévenin resistances of the two branches at V_1 both equal $2R$ so the current into this node will split evenly
 - We already know that the current into node V_0 is $2I_0$, so it follows that $I_1=2I_0$

= R

- ◆ We can repeat this process indefinitely and, using only two resistor values, can generate a whole series of currents where $I_n=2^n I_0$
 - From the voltage drop across the horizontal resistors, we see that $V_n = 2RI_n = 2^{n+1}RI_0$
 - For an N -bit ladder the input voltage is therefore
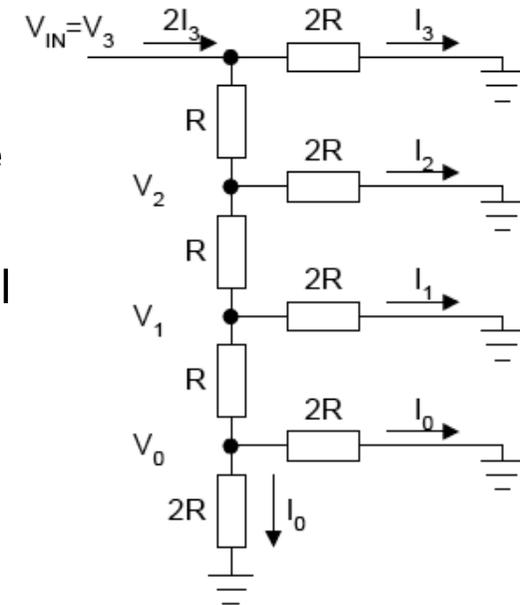
$$V_{in} = 2^N RI_0 \Rightarrow I_0 = 2^{-N} V_{in} / R$$



Current-Switched DAC

- ◆ Total current into summing junction is $X_{3:0} \times I_0$

- Hence $V_{out} = X_{3:0} \times V_{in} / 16R \times -R_f$

- ◆ We switch currents rather than voltages so that all nodes in the circuit remain at a constant voltage

- ⇒ no need to charge/discharge node capacitances


- ⇒ faster

- ◆ Use CMOS transmission gates as switches: adjust ladder resistors to account for switch resistance

- Each 2-way switch needs four transistors

- ◆ As required by R/2R ladder, all the switch output terminals are at 0 V.

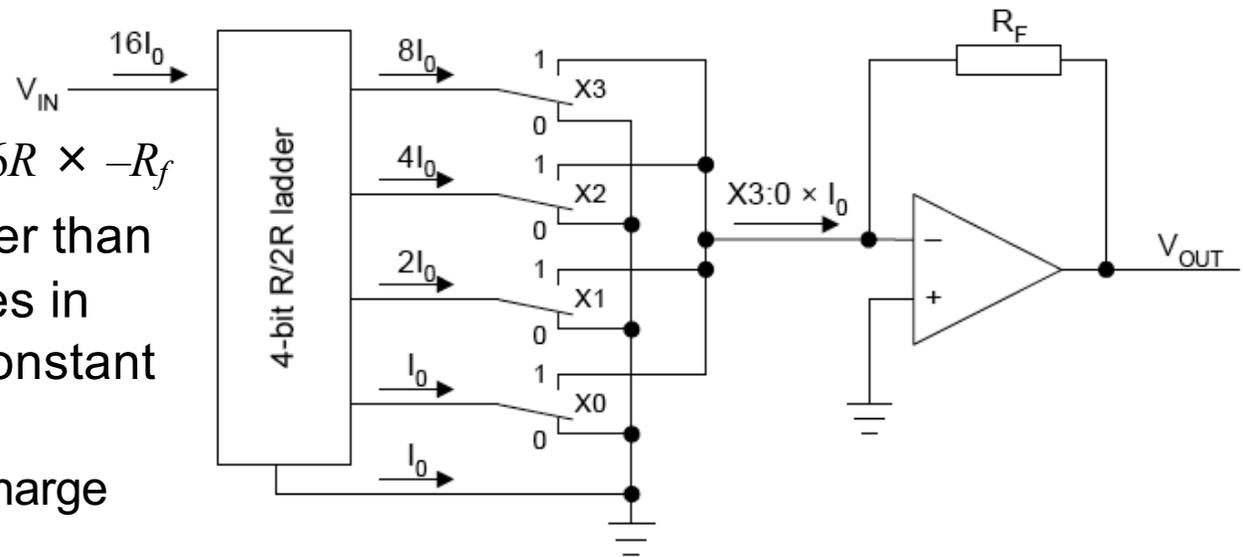- ladder outputs are always connected either to ground or to a virtual earth




Programmable Attenuator (Amplifier)

- ◆ The output of the DAC is proportional to the **product** of an analog voltage (V_{in}) and a digital number ($X_{3:0}$)

$$V_{out} = X_{3:0} \times V_{in} / 16R \times -R_f$$

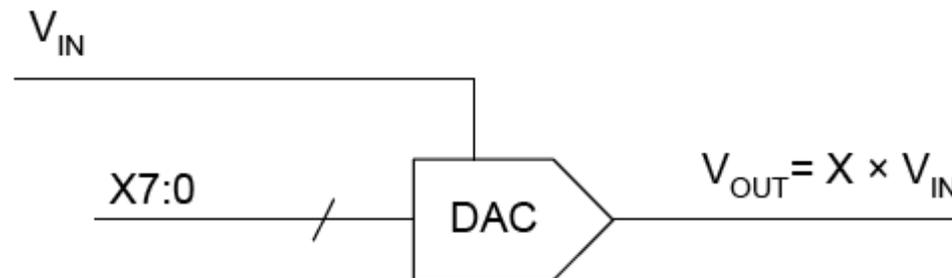
- ◆ It is called a **multiplying** DAC
- ◆ Can be used as a digital attenuator:



- ◆ Here the digital number $X_{7:0}$ controls the gain of the circuit


The MCP4921 DAC (used in Lab)

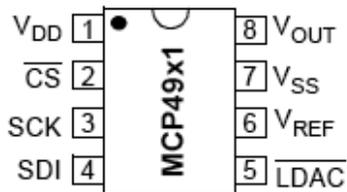- ◆ Microchip MCP4921 12-bit DAC
- ◆ Uses **resistor string** architecture (earlier lecture)
- ◆ Serial Peripheral Interface (SPI)




- Rail-to-Rail Output
- SPI Interface with 20 MHz Clock Support
- Simultaneous Latching of the DAC Output with LDAC Pin
- Fast Settling Time of 4.5 μ s
- Selectable Unity or 2x Gain Output
- External Voltage Reference Input
- External Multiplier Mode

Symbol	Description
V_{DD}	Supply Voltage Input (2.7V to 5.5V)
\overline{CS}	Chip Select Input
SCK	Serial Clock Input
SDI	Serial Data Input
\overline{LDAC}	DAC Output Synchronization Input. This pin is used to transfer the input register (DAC settings) to the output register (V_{OUT})
V_{REF}	Voltage Reference Input
V_{SS}	Ground reference point for all circuitry on the device
V_{OUT}	DAC Analog Output

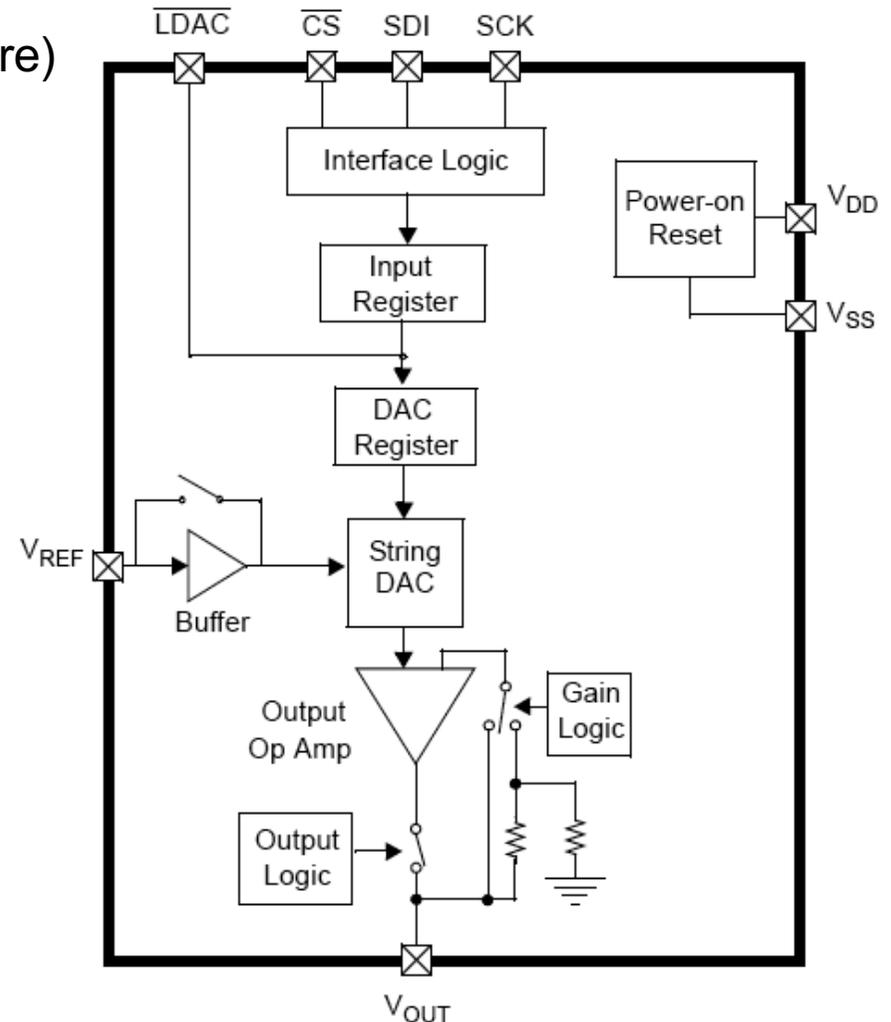


Serial Peripheral Interface for DAC (SPI)


- | | | | |
|--------|---|----------|--|
| bit 15 | 0 = Write to DAC register
1 = Ignore this command | bit 12 | SHDN : Output Shutdown Control bit
1 = Active mode operation. V _{OUT} is available.
0 = Shutdown the device. |
| bit 14 | BUF : V _{REF} Input Buffer Control bit
1 = Buffered
0 = Unbuffered | bit 11-0 | D11:D0 : DAC Input Data bits. Bit x is ignored. |
| bit 13 | GA : Output Gain Selection bit
1 = 1X (V _{OUT} = V _{REF} * D/4096)
0 = 2X (V _{OUT} = 2 * V _{REF} * D/4096) | bit 11-2 | D9:D0 : DAC input data bit |
- V_{REF} = 3.3V**
- V_{out} = V_{REF} * (D[9:0]/1024)**

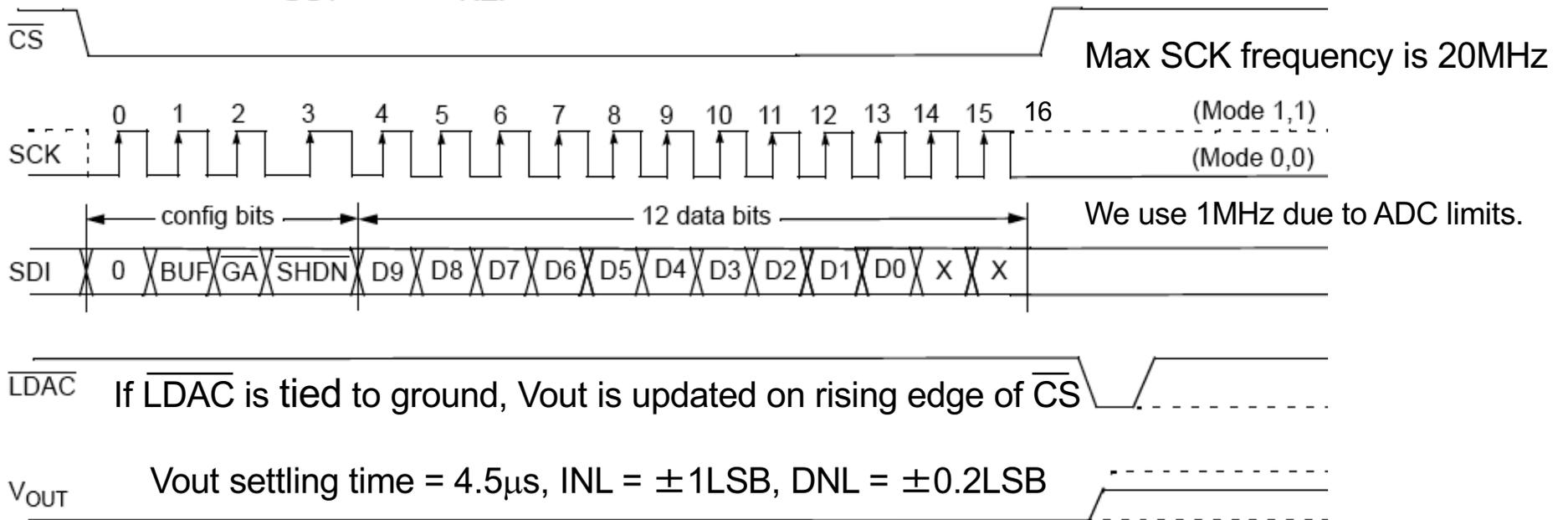


Interfacing the FPGA to the DAC

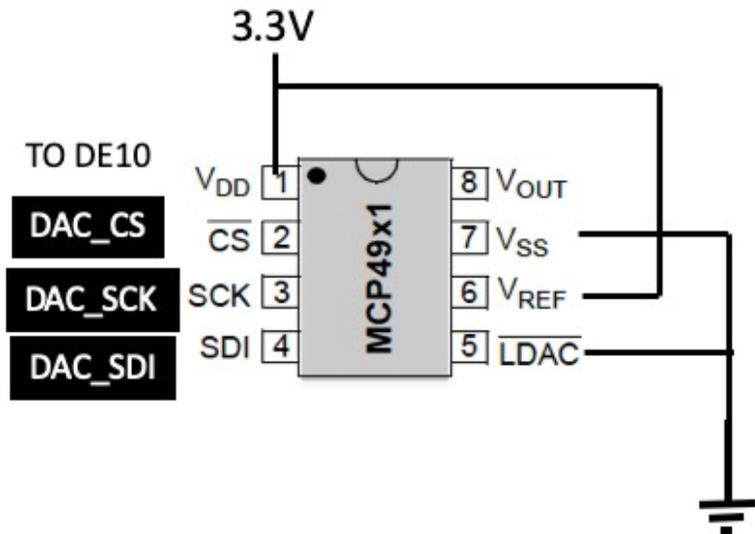


Symbol	Description
V _{DD}	Supply Voltage Input (2.7V to 5.5V)
$\overline{\text{CS}}$	Chip Select Input
SCK	Serial Clock Input
SDI	Serial Data Input
$\overline{\text{LDAC}}$	DAC Output Synchronization Input. This pin is used to transfer the input register (DAC settings) to the output register (V _{OUT})
V _{REF}	Voltage Reference Input
V _{SS}	Ground reference point for all circuitry on the device
V _{OUT}	DAC Analog Output

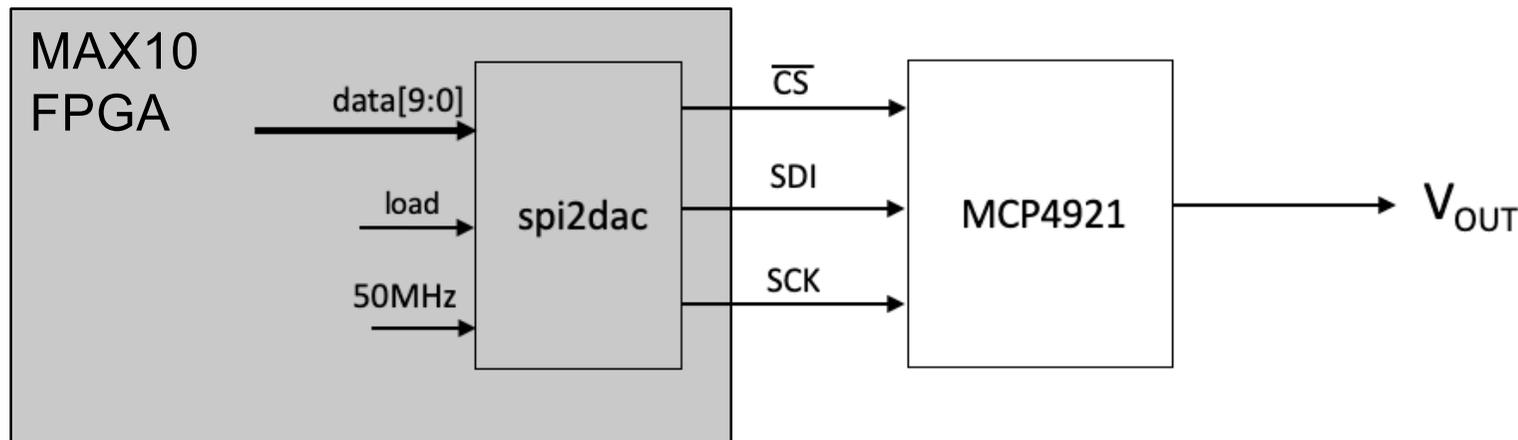

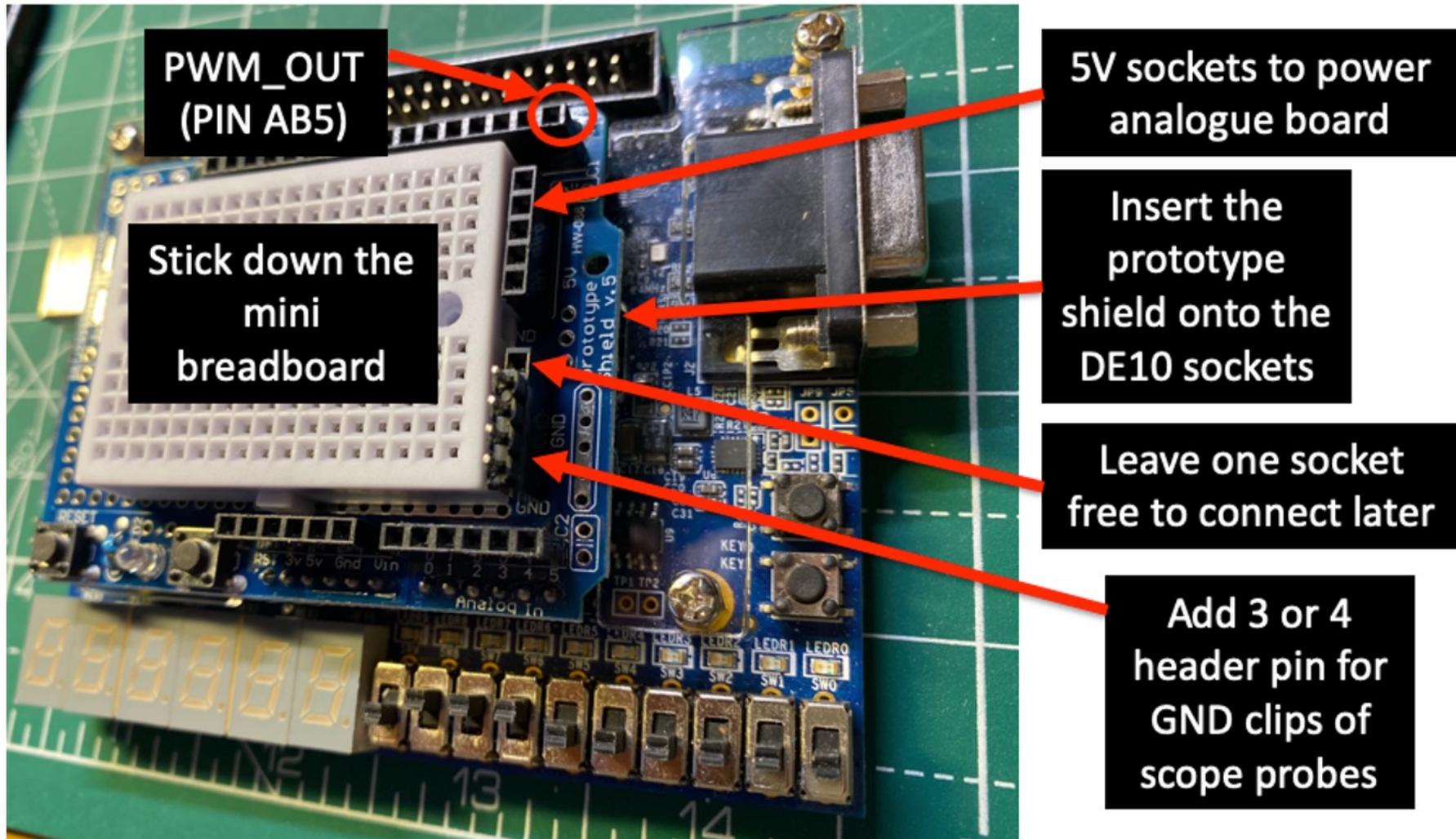Lab 5 – DAC conversion – Prototype Shield



Lab 5 Task 1 PWM as a DAC converter

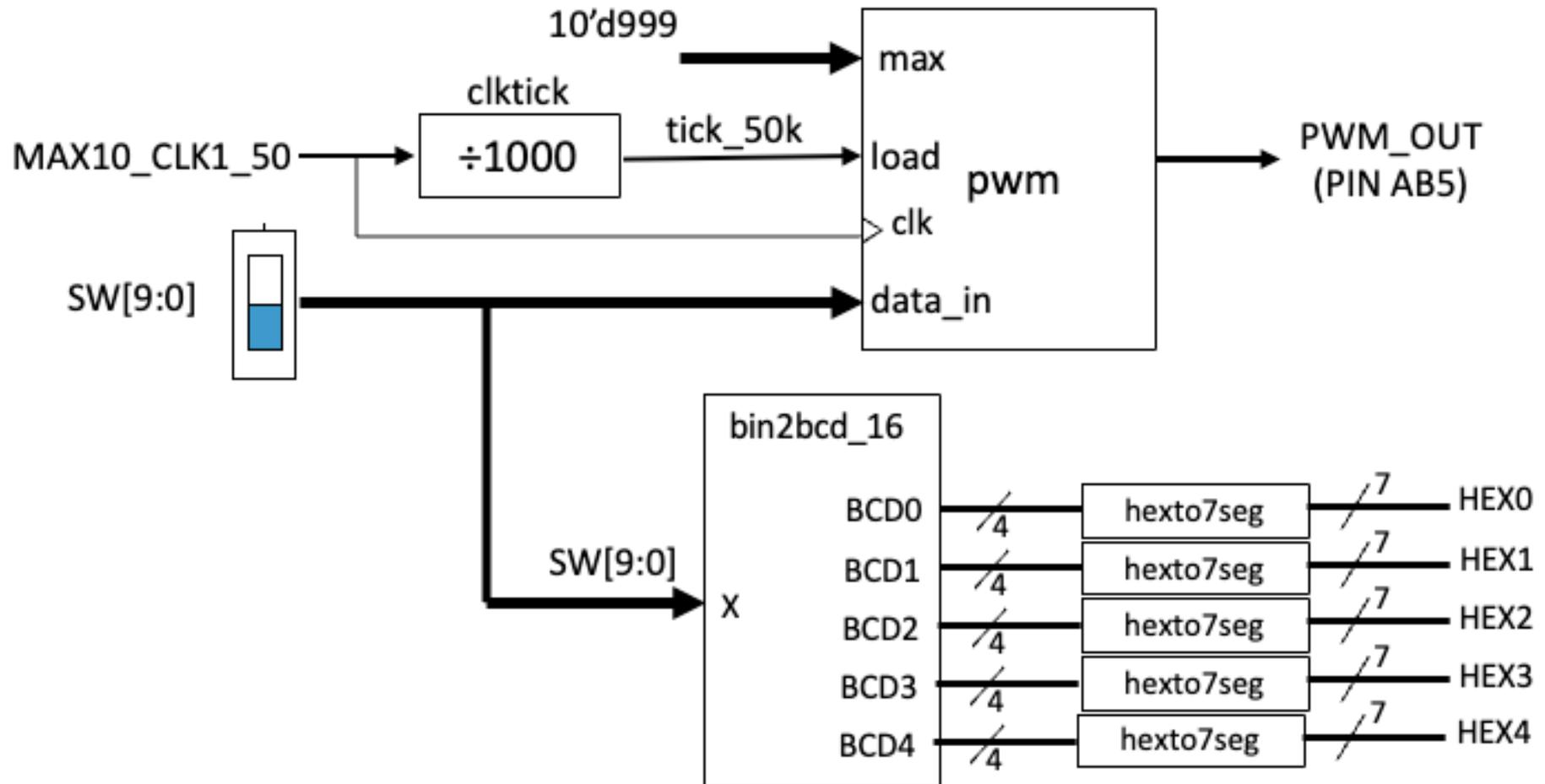

Lab 5 Task 2 Using the MCP4921 chip

