

ELEC50001 EE2 Circuits and Systems


Problem Sheet 4

(Counters and Shift Registers – Lecture 7)

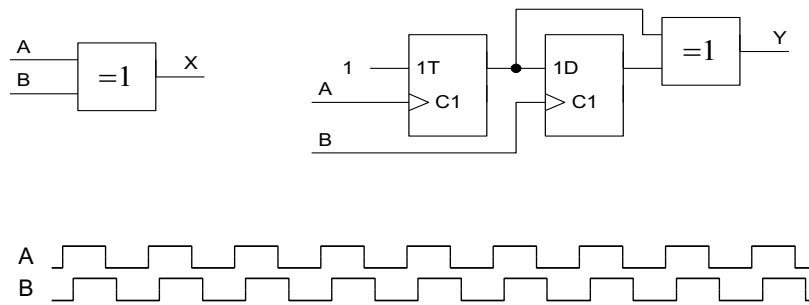
(Question ratings: A=Easy, ..., E=Hard. All students should do questions rated A, B or C as a minimum)

1B. Q2:0 is the output of a 3-bit binary counter whose input is a constant frequency squarewave, CLOCK. Give a Boolean expression for Z in terms of Q2:0 such that Z is high whenever Q2:0 has the value 6. Draw a timing diagram showing the waveforms of CLOCK and Z and the value of Q2:0 during each clock cycle. Indicate on your diagram where glitches might occur in Z.


2C. The diagram shows two *phase-detector* circuits. Inputs A and B are symmetrical squarewaves with the same frequency but differing phases. Complete the timing diagram by showing the waveforms of X and Y for the case when B lags A by 45°. If logical 0 and 1 correspond to 0 V and 5 V respectively, sketch graphs showing how the DC components (i.e. average values) of X and Y vary with the phase difference.



 
3B. The signal X forms the input to a shift register that is clocked by CLOCK↑. As shown in the timing diagram, the signal Z gives one pulse when X goes high and two pulses when it returns low. If the successive outputs from the shift register are A, B, C, ... derive a Boolean expression for Z.



 4B. Complete the timing diagram by drawing the waveform of P and Q. Explain why only one of these signals is certain to be glitch-free. If the GO pulse occurs at a random time with respect to the CLOCK, determine the average time delay in CLOCK periods between the GO↑ edge and the Q↑ edge. Implement this circuit in Verilog.



 - 5C. The diagram shows an AND gate, a 4-bit register and an adder connected together to form a counter. List the values taken by the P input of the adder for all possible values of Q3:0. Draw a state diagram showing the sequence of values taken by Q3:0 on successive CLOCK pulses.



- 6C. Modify the above circuit so that it follows the count sequence 1, 2, 3, ..., 9, 10, 1, 2, 3, Draw a state diagram for your revised circuit. Implement this circuit in Verilog.
- 7B. In lecture 5 slide 17, a 4-bit linear feedback shift register (LFSR) is implemented with the primitive polynomial $1 + X^3 + X^4$. An alternative primitive polynomial that also gives a maximal cycle length of 15 with a 4-bit LFSR is: $1 + X + X^4$ as shown in the notes for that slide. Derive the sequence resulted in this alternative polynomial. Implement this in Verilog.
- 8B. Design a maximal length 7-bit LFSR in Verilog.
- 9C. The DE10-Lite board has a 50MHz system clock available. Design a clock divider circuit that produces a 20 ns pulse every 1 microsecond in schematic form and in Verilog form.