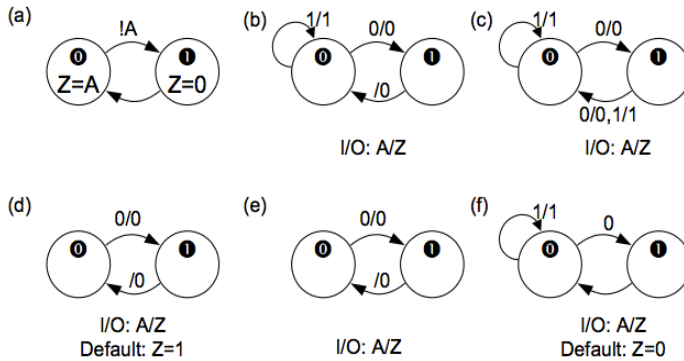


**Problem Sheet 6**


(Finite State Machines – Lecture 9)

 (Question ratings: A=Easy, ..., E=Hard. All students should do questions rated A, B or C as a minimum)

1B. Say which of the following state diagrams denote the same state machine as version (a). Where an arrow is marked 0/1, for example, it means when A=0, the output Z will be 1 and the transition will be taken at the next CLOCK rising edge.




2C. The state diagram and input waveforms of a state machine are shown below. All input and state transitions occur shortly after the clock rising edge. Complete the timing diagram by indicating the value of the state during each clock cycle and by drawing the waveform of X. The initial state is 0 as shown.



3B. A synchronous state machine has its state represented by the 2-bit number S1:0 and has a single input signal DIR. The current state is stored in a D-type register whose input NS1:0 is defined by:  $NS1 = S0 \oplus DIR$  and  $NS0 = S1 \oplus DIR$ . Draw the state diagram for the state machine.

 4C. Draw the state diagram for a state machine whose output goes high when the input is high for four or more clock cycles. As shown in the timing diagram, the output should go high during the fourth clock cycle and remain high so long as the input does. Input and state transitions occur shortly after the clock rising edge.



5D. Draw the state diagram for a state machine whose output goes high during the clock cycle following the reception of the input sequence 1011010. The trigger sequences can overlap as in the example below. Indicate the sequence of states followed by your design for the input sequence given below.

