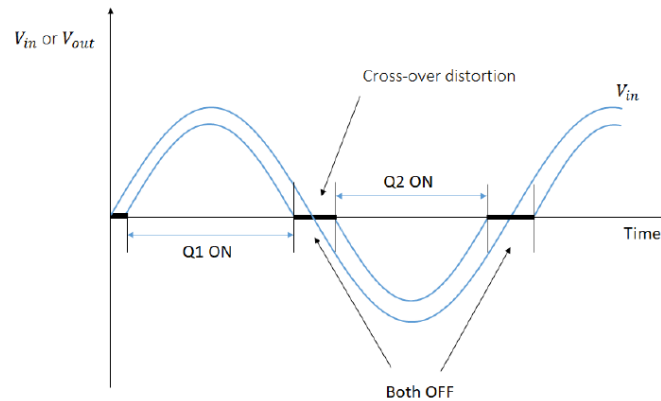



ELEC50001 EE2 Circuits and Systems

Problem Sheet 2 Solutions (Operation Amplifier Applications – Lectures 3 – 4)

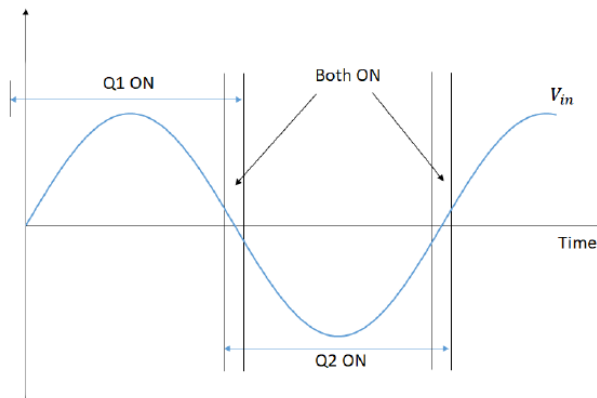1. The circuit here is also covered in Year 1 ADC Lecture 11. Q1 and Q2 need 0.7V in the base-emitter to make them conduct and act as emitter follower for Load. So Q1a circuit waveform will look like this. (Although I discourage anyone to just remember names, this output circuit architecture is known as a Class B output.)



Adding Q1 and Q2 provides the necessary bias voltages V_{BE} for Q3 and Q4 in the circuit in Figure Q1b. R3 and R4 are small (typically 10 ohms) and they improve the linearity of the amplifier. The waveform at V_{out} will look something like this. There is not cross-over distortion. This is also known as a class AB output.



2. We first need to determine what determines the biasing of this transistor and hence the quiescent base current. V_{BE} is 0.7V, therefore R_B determines I_{BQ} .

$$I_{BQ} = \frac{V_{CC} - 0.7}{R_B} = 19.3mA$$

Therefore $I_{CQ} = \beta I_B = 25 * 19.3mA = 0.48A$

$$V_{CEQ} = V_{CC} - I_C R_C = 20 - 0.48 * 20 = 10.4V$$

Note that the supply current is a sinusoidal wave centred around I_{CQ} .

Therefore supply input power is:

$$P_i(dc) = V_{CC} I_{CQ} = 20 * 0.48 = 9.6W$$

Given that input (ac) signal has a peak current of 10mA in the question, we can calculate the peak collector current:

$$I_C(pk) = \beta I_B(pk) = 250mA (pk)$$

Therefore ac power to load (R_C) is:

$$P_o(ac) = I_C^2(rms) R_C = \frac{I_C^2(pk)}{2} R_C = \frac{0.25^2}{2} * 20 = 0.625W$$

Hence the amplifier's power efficiency is only:

$$\eta = \frac{P_o(ac)}{P_i(dc)} = \frac{0.625}{9.6} * 100\% = 6.5\%$$

 


Figure Q2

3. We solve this problem in a similar way to that of Q2 except that the input power is calculated with current that is NOT the same as the quiescent current due to the push-pull action of Q1 and Q2. Instead we have to calculate the average current for the full-wave rectified current as explained in the notes.

The peak input signal voltage is:

$$V_i(pk) = \sqrt{2} V_i(rms) = \sqrt{2} * 12 = 17V.$$

Assuming that the voltage gain is 1. Therefore $V_L(pk) = 17V$

$$\text{Hence } P_o(ac) = \frac{V_L^2(pk)}{2R_L} = \frac{17^2}{2 \times 4} = 36.125W$$

The peak load current is:

$$I_L(pk) = \frac{V_L(pk)}{R_L} = \frac{17}{4} = 4.25A$$

Therefore the average (dc) current draw from supply rails is:

$$I_{dc} = \frac{2}{\pi} I_L(pk) = 2 \times \frac{4.25}{\pi} = 2.71A$$

Hence power from supply is

$$P_i(dc) = V_{CC} I_{dc} = 25 \times 2.71 = 67.75W$$

The power dissipated by each of the output transistors Q1 and Q2 is the same. It is:

$$P_Q = \frac{P_i - P_o}{2} = \frac{67.75 - 36.125}{2} = 15.8W$$

The amplifier efficiency is $\eta = \frac{P_o}{P_i} \times 100\% = \frac{36.125}{67.75} \times 100\% = 53.3\%$

This is much better than the efficiency found in Q2!

 


Figure Q2

4. $Z = [R2/(R1+R2)] * Y = X' / K$ (due to the negative feedback)

Therefore $X' = [R2/(R1+R2)] * K * Y$

$Y = A_1 (X - X')$

Therefore $Y = A_1 X - A_1 * K * [R2/(R1+R2)] * Y$

$Y\{1 + A_1 K * [R2/(R1+R2)]\} = A_1 X$

Closed-loop gain $= \frac{Y}{X} = \frac{1}{\left(\frac{1}{A_1} + \frac{KR2}{R1+R2}\right)}$

Check: Assume $A_1 = \text{infinite}$, $K = 1$, Gain = $1 + R1/R2$ - correct for conventional non-inverting amplifier.

 


Figure Q4

5. Circuit for Q5a: Comparator output switch over state when V_+ reaches V_{REF} . Apply KCL at V_+ node: $(V_{IN} - V_{REF})/R1 = (V_{REF} - V_{OUT})/R2 \Rightarrow V_{IN} = (1+R1/R2) V_{REF} - (R1/R2) * V_{OUT}$

For positive going V_{IN} , $V_{OUT} = 0$. Therefore $V_{th_H} = V_{REF} (1 + R1/R2)$.

For negative going V_{IN} , $V_{OUT} = 5$. Therefore $V_{th_L} = V_{REF} (1+R1/R2) - 5 * R1/R2$

Circuit for Q5b: Apply KCL at node V_+ : $V_{IN} = V_{REF}[R2/(R1+R2)] + V_{OUT}[R1/(R1+R2)]$.

For positive going V_{IN} , $V_{OUT} = 5$. Therefore $V_{th_H} = V_{REF}[R2/(R1+R2)] + 5 * [R1/(R1+R2)]$.

For negative going V_{IN} , $V_{OUT} = 0$. Therefore $V_{th_L} = V_{REF} R2/(R1+R2)$

 


Figure Q5a

 


Figure Q5b

6. Since $R_1 = 180k$ and $R_2 = 200k$, from Q5, $V_{th_H} = 4.75V$ and $V_{th_L} = 0.25V$. Therefore the triangular signal peak-to-peak is $4.5V$.

For the integrator, the integration current $i_c = \pm(V_{sq} - 2.5)/R$, ($R = 10k$).

Therefore $\Delta V_c / \Delta t = i_c / C = 2.5 / RC$. $\Delta V_c = 4.5V$. Therefore $\Delta t = RC \cdot 4.5 / 2.5 = 18\mu s$. Therefore the oscillation frequency is $1 / (2 \cdot 18) \text{ MHz} = 27.8 \text{ kHz}$.

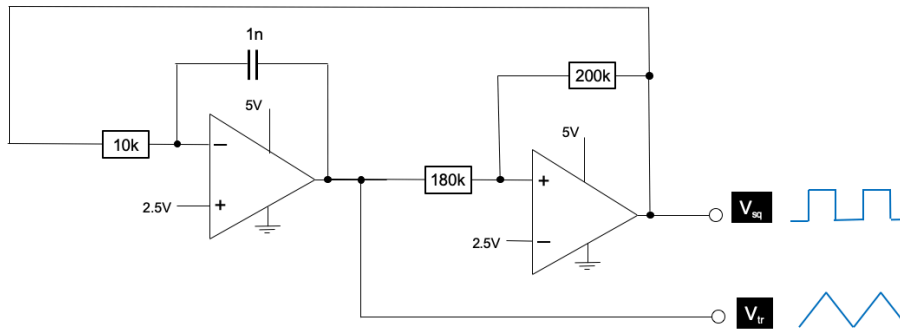


Figure Q6

$$7. \frac{V_{out}(s)}{V_{in}(s)} = \frac{1/R_1R_2C_1C_2}{s^2 + s\left(\frac{1}{R_2C_1} + \frac{1}{R_1C_1}\right) + \frac{1}{R_1C_1R_2C_2}}$$

For Butterworth filter, the cut-off frequency is $f_c = \frac{1}{2\pi\sqrt{R_1R_2C_1C_2}}$

Since $C_1 = C_2 = 10\text{nF}$, $R_1 = R_2 = 1.59\text{k ohm}$.

 


Figure Q7

8. The triangular signal from Q5 goes from 0.25V to 4.75V. The range is 4.5V. Therefore:

$$V_{pwm(average)} = (V_{in} - 0.25) * (5/4.5) \text{ for } 0.25 \leq V_{in} \leq 4.75.$$

Check: When $V_{in} = 0.25\text{V}$, $V_{pwm(average)} = 0\text{V}$ (or 0% duty cycle).

When $V_{in} = 4.75\text{V}$, $V_{pwm(average)} = 5\text{V}$ (or 100% duty cycle).

 


Figure Q8