

Lecture 7

Microarchitecture of a simplified RISC-V

Peter Cheung
Imperial College London

URL: www.ee.imperial.ac.uk/pcheung/teaching/EE2_CAS/
E-mail: p.cheung@imperial.ac.uk


What is microarchitecture?

- **Microarchitecture:** how to implement an architecture in hardware
- Processor:
 - **Datapath:** functional blocks
 - **Control:** control signals

Based on: “*Digital Design and Computer Architecture (RISC-V Edition)*”
by Sarah Harris and David Harris (H&H),

RISC-V State Elements

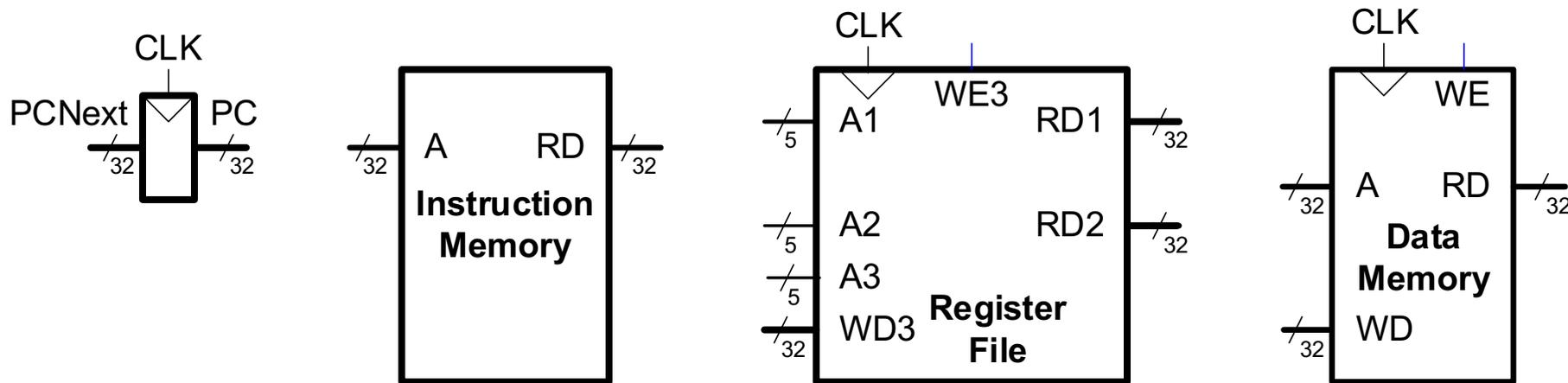- **State elements:** determines everything about a processor:
 - **Architectural state:**
 - 32 registers
 - Program Counter (PC)
 - Memory



Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),


Example Program

- Design datapath
- View example program executing

Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	imm _{11:0} 1111111111100	rs1 f3 rd op 01001 010 00110 0000011 FFC4A303
0x1004	sw x6, 8(x9)	S	imm _{11:5} rs2 0000000 00110	rs1 f3 imm _{4:0} op 01001 010 01000 0100011 0064A423
0x1008	or x4, x5, x6	R	funct7 rs2 0000000 00110	rs1 f3 rd op 00101 110 00100 0110011 0062E233
0x100C	beq x4, x4, L7	B	imm _{12,10:5} rs2 1111111 00100	rs1 f3 imm _{4:1,11} op 00100 000 10101 1100011 FE420AE3


I-Type

```
lw x6, -4(x9)
lw rd, imm(rs1)
```

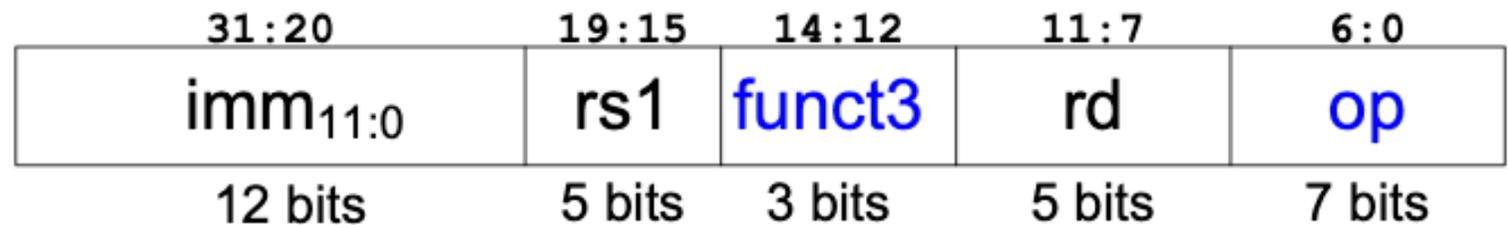

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),


Step 1: Instruction Fetch

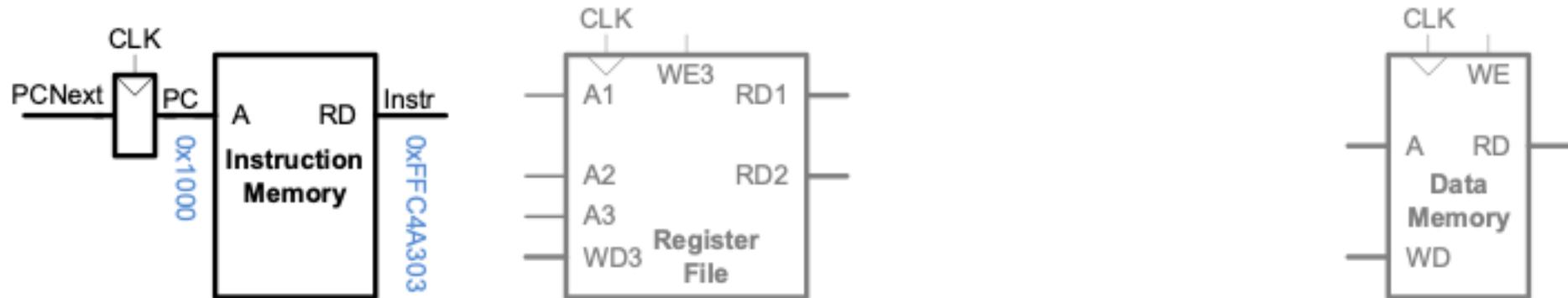

Address	Instruction	Type	Fields	Machine Language										
0x1000	L7: lw x6, -4(x9)	I	<table border="1"> <thead> <tr> <th>imm_{11:0}</th> <th>rs1</th> <th>f3</th> <th>rd</th> <th>op</th> </tr> </thead> <tbody> <tr> <td>111111111100</td> <td>01001</td> <td>010</td> <td>00110</td> <td>0000011</td> </tr> </tbody> </table>	imm _{11:0}	rs1	f3	rd	op	111111111100	01001	010	00110	0000011	FFC4A303
imm _{11:0}	rs1	f3	rd	op										
111111111100	01001	010	00110	0000011										

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),


Step 2: Read Source Operand (rs1)

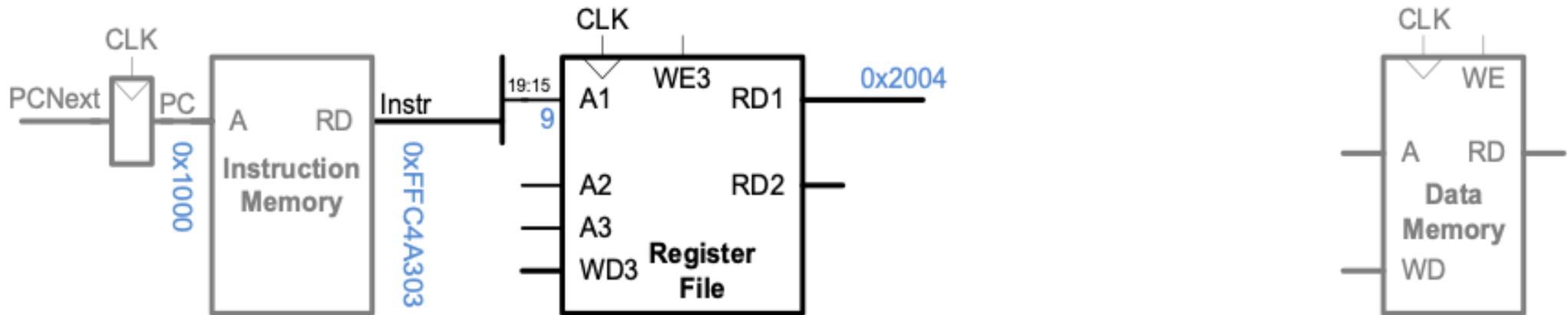

Address	Instruction	Type	Fields				Machine Language	
			$imm_{11:0}$	rs1	f3	rd	op	
0x1000	L7: lw x6, -4(x9)	I	111111111100	01001	010	00110	0000011	FFC4A303

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),


Step 3: Extend the immediate constant

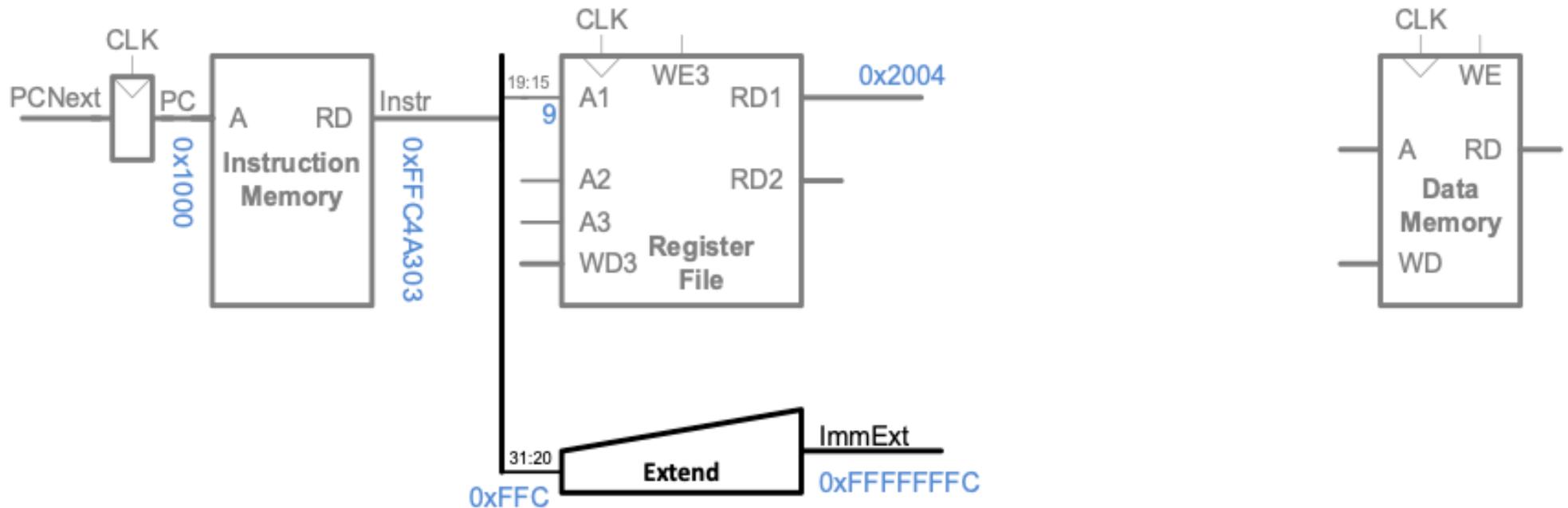

Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	$imm_{11:0}$ 111111111100 rs1 f3 rd op 01001 010 00110 0000011	FFC4A303

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
 by Sarah Harris and David Harris (H&H),


Step 4: Calculate memory address

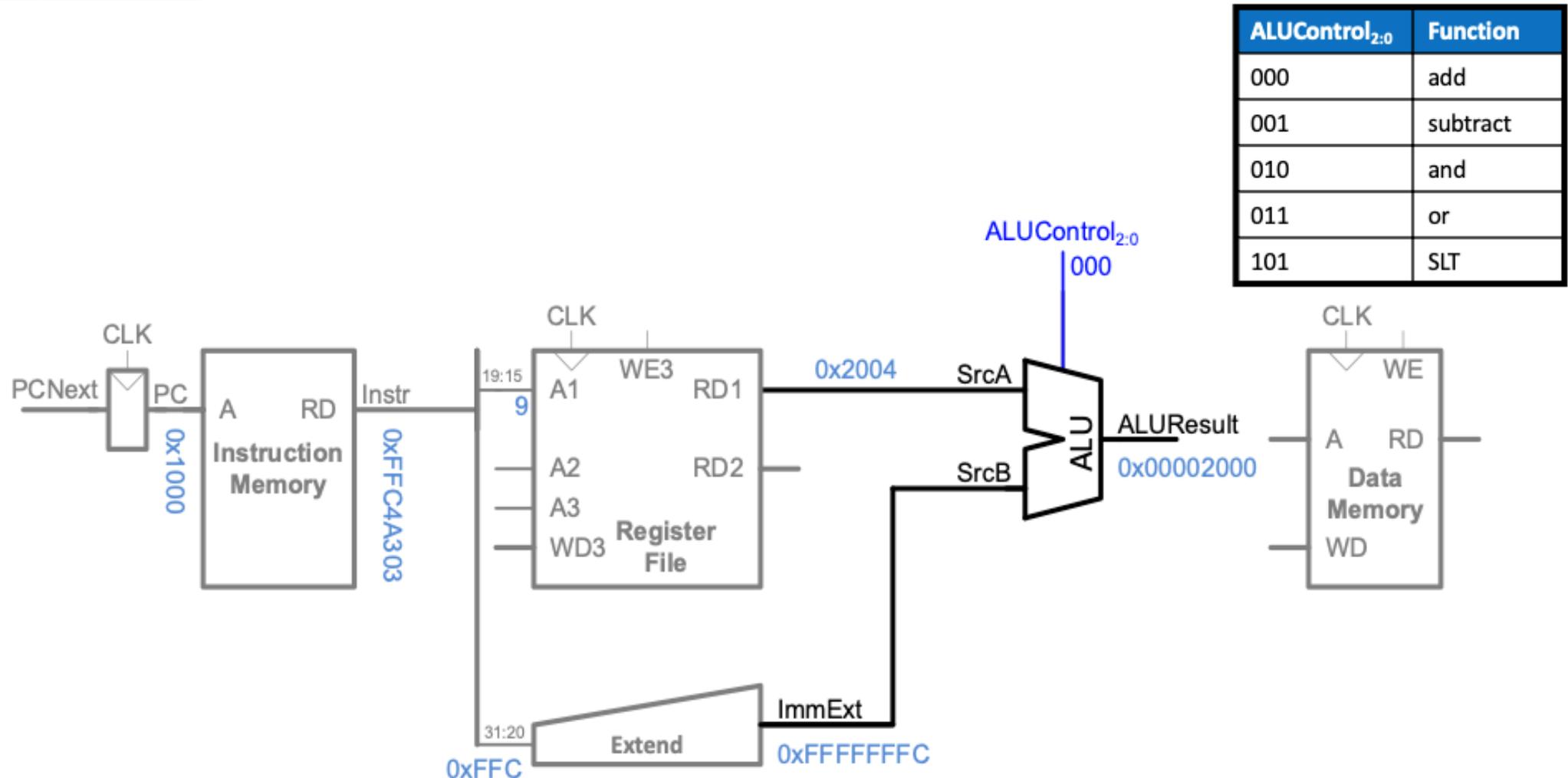

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	imm _{11:0} 111111111100 rs1 01001 f3 010 rd 00110 op 0000011	FFC4A303

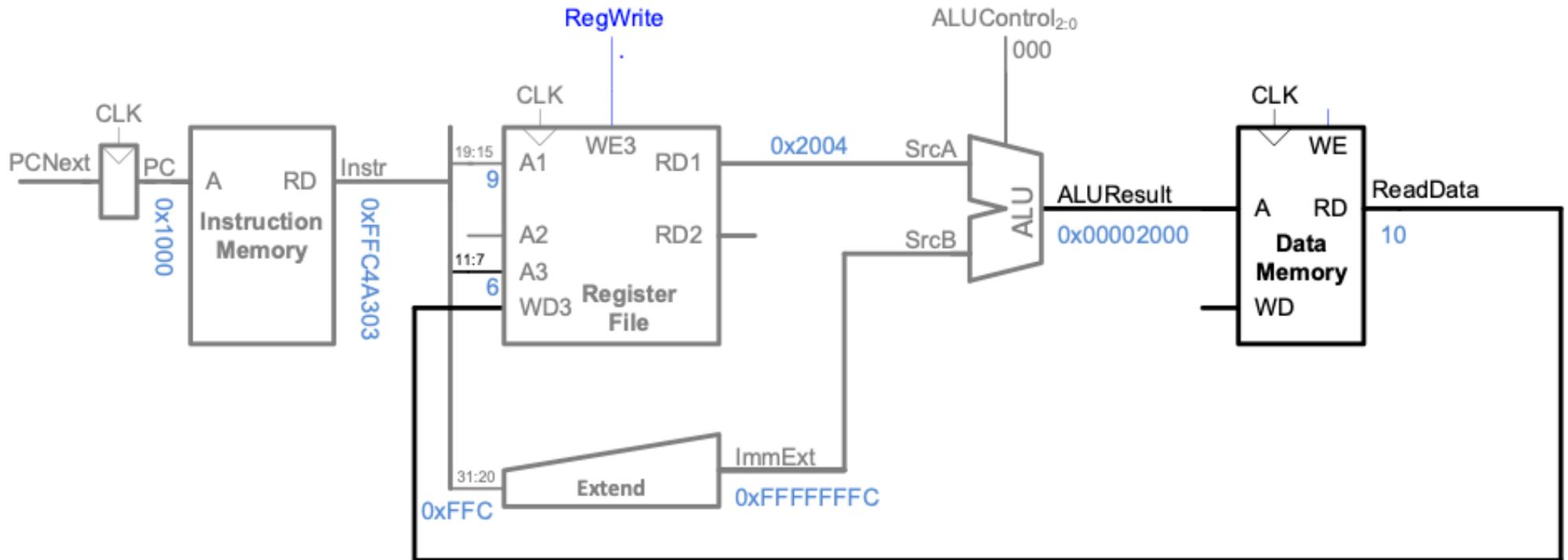
Step 5: Read data from memory & write to Reg



Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	$imm_{11:0}$ 111111111100 rs1 f3 rd op	FFC4A303

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
 by Sarah Harris and David Harris (H&H),

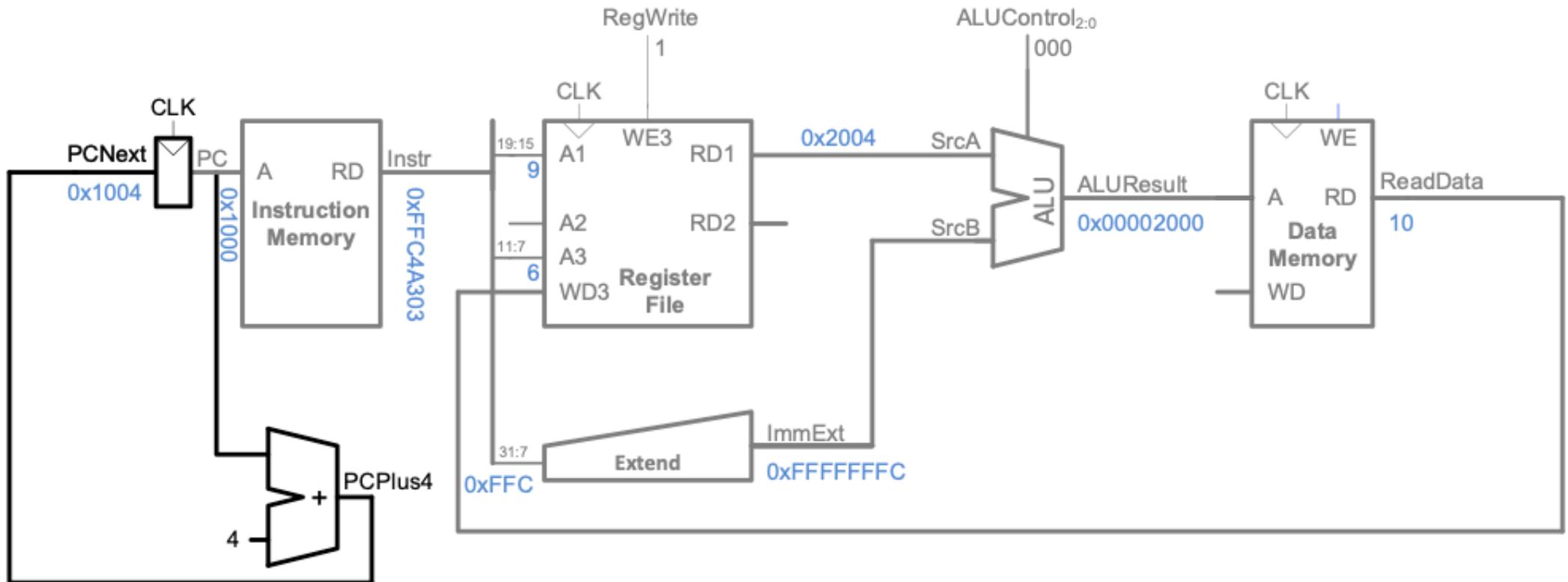Step 6: Determine address of next instruction




Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	$imm_{11:0}$ 111111111100 rs1 f3 rd op	FFC4A303

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
 by Sarah Harris and David Harris (H&H),

Implementation of the "sw" instruction

- **Immediate:** now in {instr[31:25], instr[11:7]}
- **Add control signals:** ImmSrc, MemWrite

Address	Instruction	Type	Fields					Machine Language
			imm _{11:5}	rs2	rs1	f3	imm _{4:0}	op
0x1004	sw x6, 8(x9)	S	0000000	00110	01001	010	01000	0100011
								0064A423

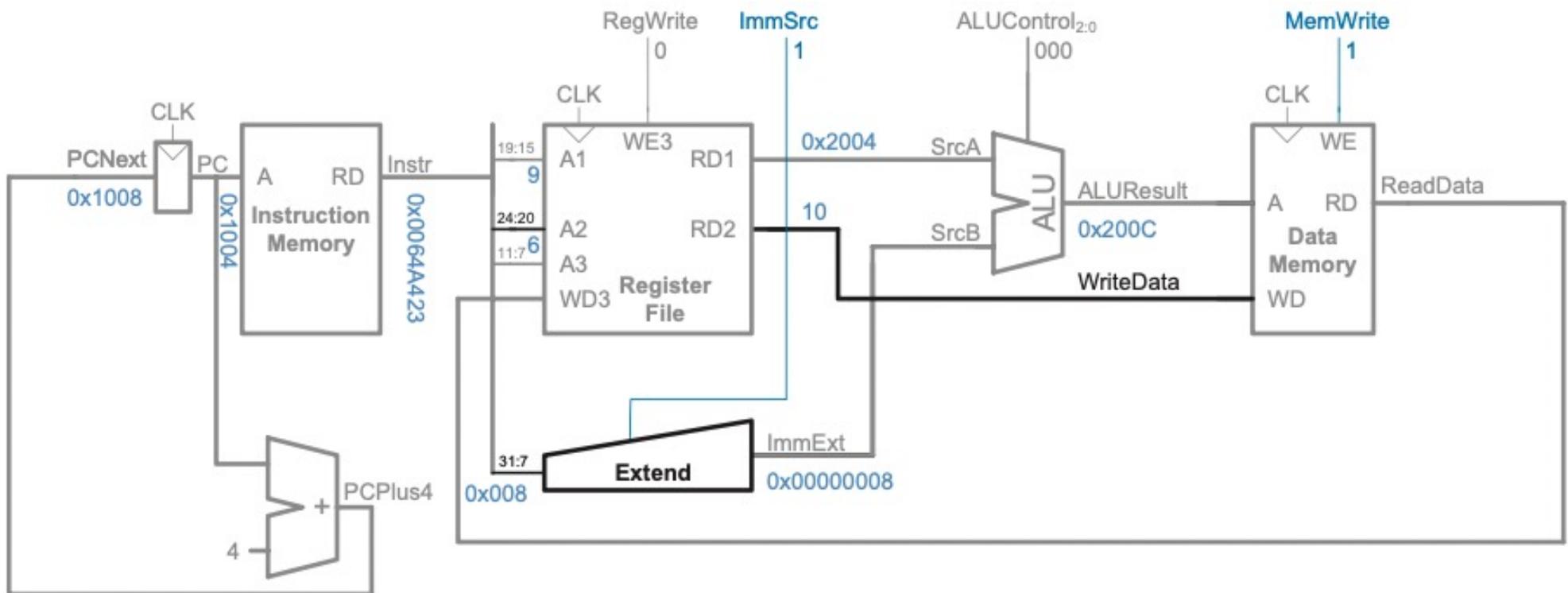


Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

Implementation of the "sw" instruction

- **Immediate:** now in {instr[31:25], instr[11:7]}
- **Add control signals:** ImmSrc, MemWrite

Address	Instruction	Type	Fields						Machine Language
			imm _{11:5}	rs2	rs1	f3	imm _{4:0}	op	
0x1004	sw x6, 8(x9)	S	0000000	00110	01001	010	01000	0100011	0064A423

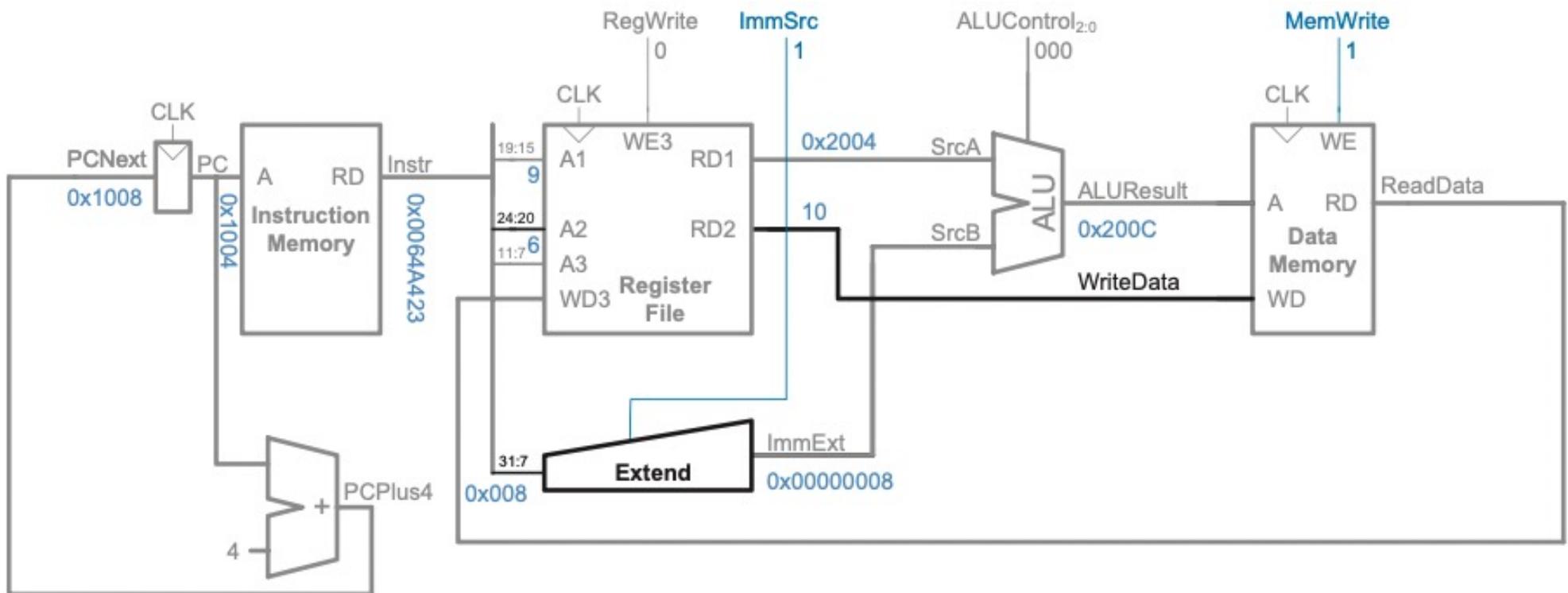

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

Immediate offset for I-type and S-type are different

Instruction Formats	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
Immediate	imm[11:0]											rs1			funct3			rd				opcode										
Store	imm[11:5]						rs2					rs1			funct3			imm[4:0]				opcode										


ImmSrc	ImmExt	Instruction Type
0	{{20{instr[31]}}, instr[31:20] }	I-Type
1	{{20{instr[31]}}, instr[31:25], instr[11:7] }	S-Type

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

Implementation of the "or" instruction

- Read from **rs1** and **rs2** (instead of **imm**)
- Write **ALUResult** to **rd**

Address	Instruction	Type	Fields					Machine Language	
			funct7	rs2	rs1	f3	rd	op	
0x1008	or x4, x5, x6	R	0000000	00110	00101	110	00100	0110011	0062E233

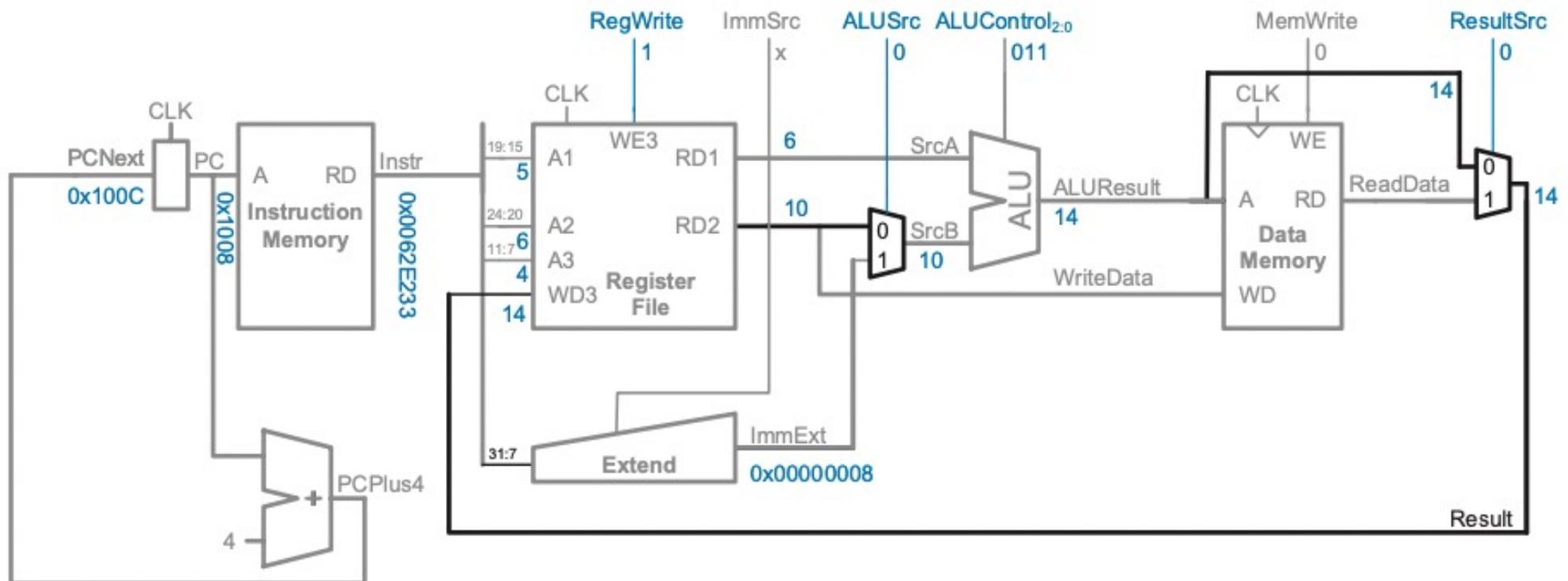


Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

Implementation of the "beq" instruction

Calculate **target address**: $PCTarget = PC + imm$


Address	Instruction	Type	Fields					Machine Language	
			$imm_{12,10:5}$	$rs2$	$rs1$	$f3$	$imm_{4:1,11}$	op	
0x100C	beq x4, x4, L7	B	11111111	00100	00100	000	10101	1100011	FE420AE3

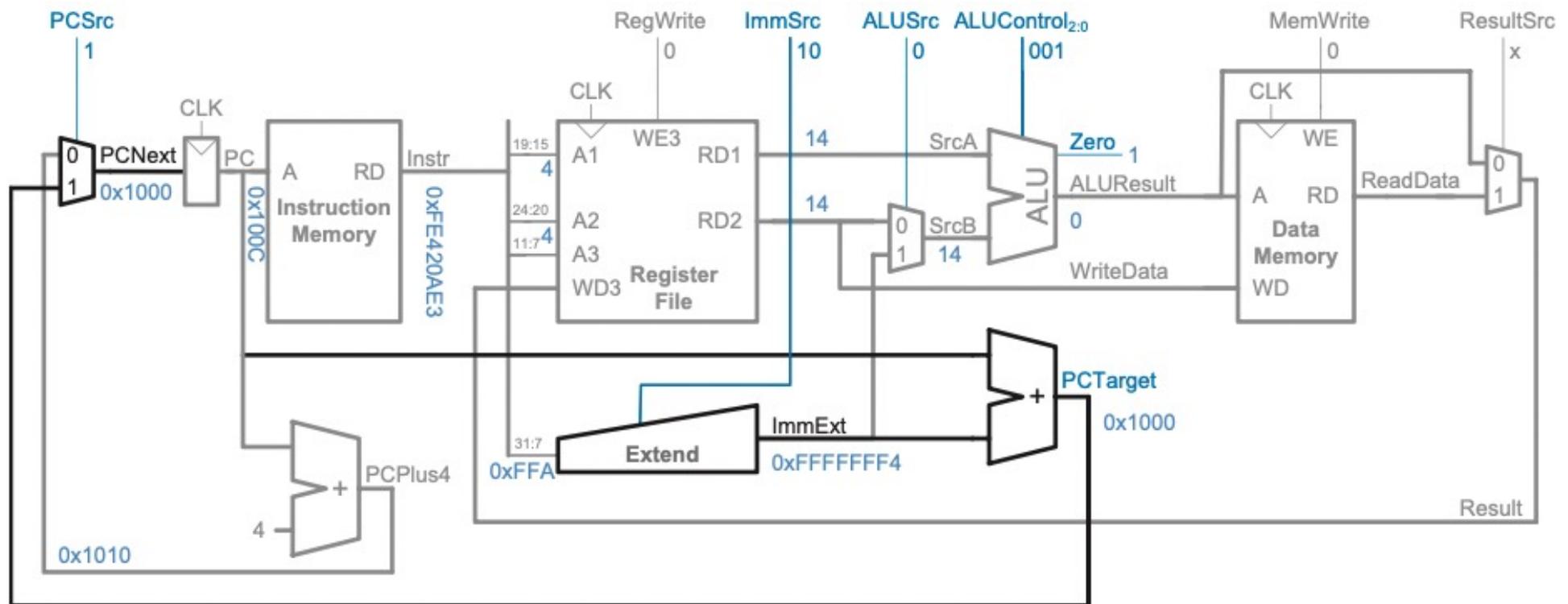


Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

Two different views of the Control Unit

High-Level View

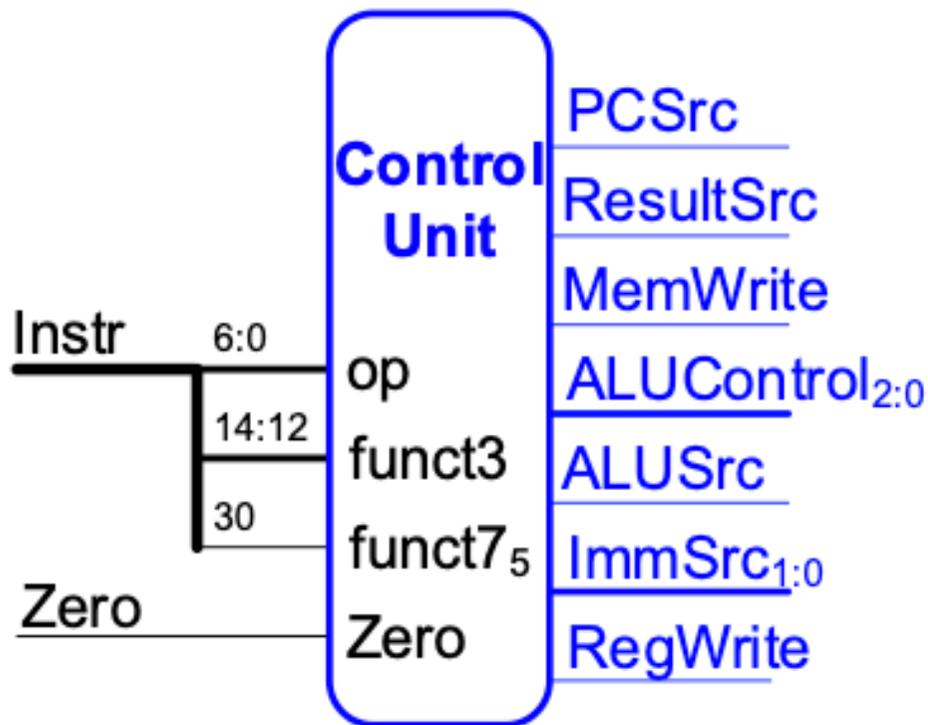


Low-Level View

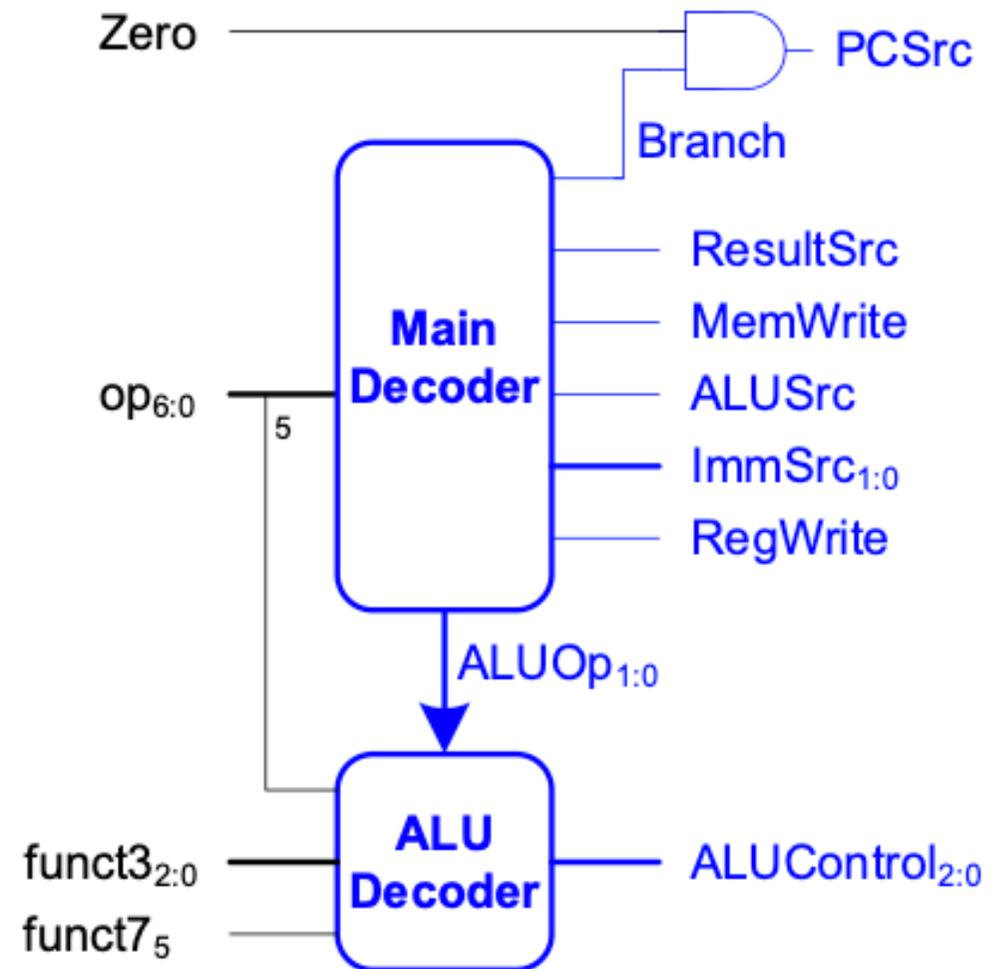

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),


Main decoder

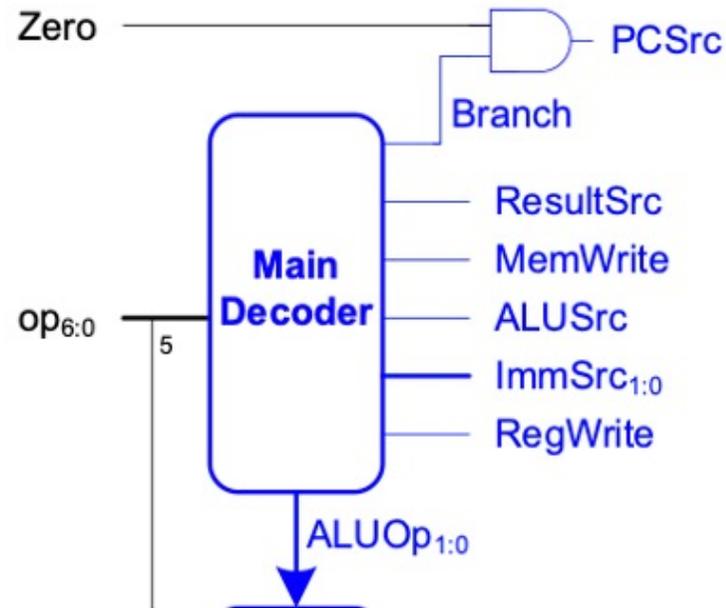

Instruction	Op	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
lw	0000011	1	00	1	0	1	0	00
sw	0100011	0	01	1	1	x	0	00
R-type	0110011	1	xx	0	0	0	0	10
beq	1100011	0	10	0	0	x	1	01

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

ALU Decoder

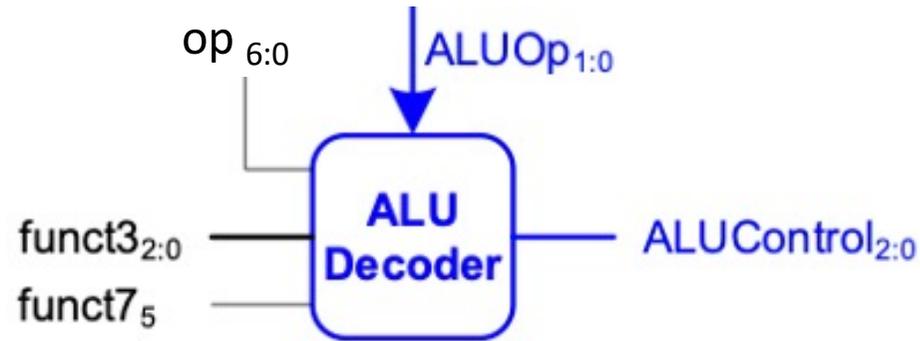


ALUOp	funct3	{ op_5 , $funct7_5$ }	ALUControl	Instruction
00	x	x	000 (add)	lw, sw
01	x	x	001 (subtract)	beq
10	000	00, 01, 10	000 (add)	add
	000	11	001 (subtract)	sub
	010	x	101 (set less than)	slt
	110	x	011 (or)	or
	111	x	010 (and)	and

Based on: "Digital Design and Computer Architecture (RISC-V Edition)"
by Sarah Harris and David Harris (H&H),

Example – Control for `x5`, `x6`, `x7`

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
51	R-type	1	XX	0	0	0	0	010

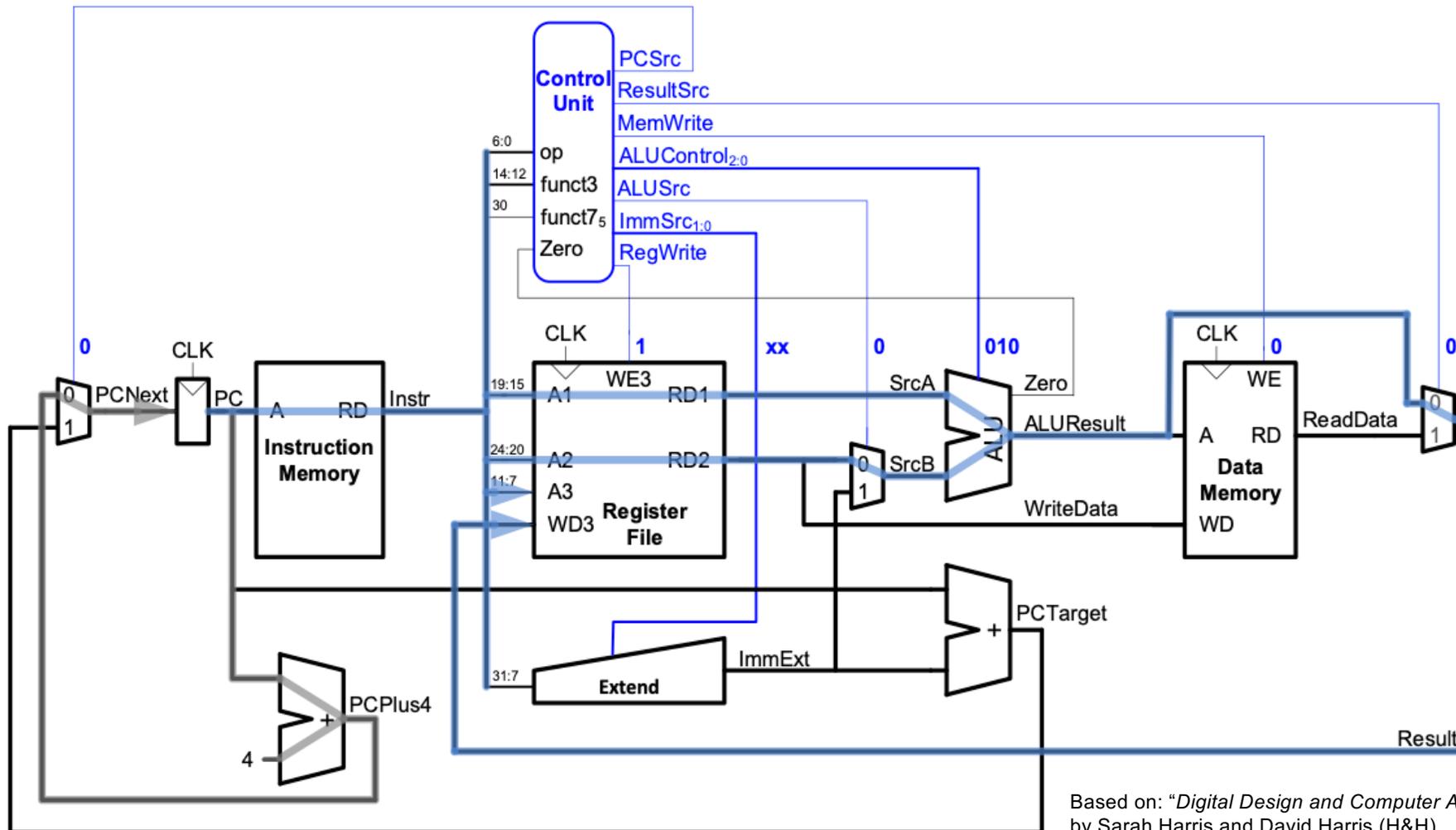

Based on: "Digital Design and Computer Architecture (RISC-V Edition)" by Sarah Harris and David Harris (H&H),

Lab 4 – A Very Basic RISC-V CPU

- Start working as a Team – 2 pairs allocated by me
- **Lab objectives:**
 1. To get to know your teammates.
 2. To establish a Github Repo for your team where everyone's contribute towards.
 3. To learn about TWO RISC-V instructions in great details.
 4. To design a simple CPU that executes these two instructions.
 5. To use execute a short program using only these two instructions. The program implements the binary counter in Lab 1, but in software.
 6. Stretched goal – to implement a third instruction accessing data memory. With this, implement the sinewave generator in software.

Lab 4 – Program to execute

```
1 main:
2     addi    t1, zero, 0xff      # load t1 with 255
3     addi    a0, zero, 0x0      # a0 is used for output
4 mloop:
5     addi    a1, zero, 0x0      # a1 is the counter, init to 0
6 iloop:
7     addi    a0, a1, 0          # load a0 with a1
8     addi    a1, a1, 1          # increment a1
9     bne     a1, t1, iloop      # if a1 = 255, branch to iloop
10    bne     t1, zero, mloop     # else always branch to mloop
```

Online RISC-V Assembler:

<https://riscvasm.lucasteske.dev>

Hex Dump	
	0ff00313
	00000513
	00000593
	00058513
	00158593
	fe659ce3
	fe0318e3

Lab 4 – Pseudoinstruction is easier to read

```
1 main:
2     addi    t1, zero, 0xff
3     addi    a0, zero, 0x0
4 mloop:
5     addi    a1, zero, 0x0
6 iloop:
7     addi    a0, a1, 0
8     addi    a1, a1, 1
9     bne     a1, t1, iloop
10    bne     t1, zero, mloop
```

```
0000000000000000
:
0:    0ff00313      li    t1,255
4:    00000513      li    a0,0

0000000000000008 :
8:    00000593      li    a1,0

000000000000000c :
c:    00058513      mv    a0,a1
10:   00158593      addi  a1,a1,1
14:   fe659ce3      bne   a1,t1,c
18:   fe0318e3      bnez  t1,8
```

Lab 4 – Overall block diagram

