

## Clocked circuits, Shift Registers & BCD converter

Peter Cheung  
Department of Electrical & Electronic Engineering  
Imperial College London



Course webpage: [www.ee.ic.ac.uk/pcheung/teaching/MSc\\_Experiment/](http://www.ee.ic.ac.uk/pcheung/teaching/MSc_Experiment/)  
E-mail: [p.cheung@imperial.ac.uk](mailto:p.cheung@imperial.ac.uk)

I hope you have completed Part 1 of the Experiment. This lecture leads you to Part 2 of the experiment and hopefully helps you with your progress to Part 2. It covers a number of topics:

1. How do we specify clocked (i.e. sequential) circuits in Verilog?
2. How do we specify a flexible counter?
3. How to specify and use shift registers?
4. How to specify linear-feedback shift registers as a pseudo random binary sequence generator?
5. How to convert binary (or hexadecimal) numbers to binary coded decimal (BCD) numbers?

## Power of Verilog: Integer Arithmetic

- ♦ Arithmetic operations make computation easy:

```
module add32(a, b, sum);  
    input[31:0] a,b;  
    output[31:0] sum;  
    assign sum = a + b;  
endmodule
```

- ♦ Here is a 32-bit adder with carry-in and carry-out:

```
module add32_carry(a, b, cin, sum, cout);  
    input[31:0] a,b;  
    input cin;  
    output[31:0] sum;  
    output cout;  
    assign {cout, sum} = a + b + cin;  
endmodule
```

Verilog is very much like C. However, the declaration of **a**, **b** and **sum** in the **module add32** specifies the data width (i.e. number of bits in each signal **a**, **b** or **sum**). This is often known as a “**vector**” or a “**bus**”. Here the data width is 32-bit, and it is ranging from bit 31 down to bit 0 (e.g. **sum[31:0]**).

You can refer to individual bits using the index value. For example, the least-significant bit (LSB) of **sum** is **sum[0]** and the most-significant bit (MSB) is **sum[31]**. **sum[7:0]** refers to the least-significant byte of **sum**.

The ‘+’ operator can be used for signals of any width. Here a 32-bit add operation is specified. **sum** is also 32-bit in width. However, if **a** and **b** are 32-bit wide, the sum result could be 33-bit (including the carry out). Therefore this operation could result in a wrong answer due to **overflow** into the carry bit. The 33th bit is truncated. The second example **module add32\_carry** shows the same adder but with carry input and carry output. Note the LHS of the **assign** statement. The **{cout, sum}** is a **concatenation** operator – the contents inside the brackets **{ }** are concatenated together, with **cout** is assigned the MSB of the 33th bit of the result, and the remaining bits are formed by **sum[31:0]**.

## Different types of Boolean Operators

- ♦ **Bitwise operators:** perform bit-sliced operations on vectors bit by bit
  - $\sim(4'b0101) = \{\sim 0, \sim 1, \sim 0, \sim 1\} = 4'b1010$
  - $4'b0101 \& 4'b0011 = 4'b0001$
- ♦ **Logical operators:** return true or false (1-bit) results
  - $!(4'b0101) = \sim 1 = 1'b0$
- ♦ **Reduction operators:** act on each bit of a SINGLE input vector
  - $\&(4'b0101) = 0 \& 1 \& 0 \& 1 = 1'b0$

Bitwise		Logical		Reduction	
$\sim a$	NOT	$!a$	NOT	$\&a$	AND
$a \& b$	AND	$a \&\& b$	AND	$\sim\&$	NAND
$a   b$	OR	$a    b$	OR	$ $	OR
$a \wedge b$	XOR			$\sim $	NOR
$a \sim\wedge b$	XNOR			$\wedge$	XOR

Note distinction between  $\sim a$  and  $!a$

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 3

There are three different types of Boolean operators:

**Bitwise operators** perform what you would expect as if there are parallel gates used for each bit of the operands. Therefore  $a\&b$  means that each bit from  $a$  and  $b$  is passed through an AND-gate.

**Logical operators** only result in 0 or 1 (i.e. 1-bit result). In this example  $!a$  (not  $a$ ) where  $a = 0101$ , will result in first,  $a$  being evaluated as a logical value (i.e. logical '1' or true). Therefore the result  $\sim a$  is logical 0 (or false).

**Reduction operators** is applied to a single operand (and sometimes known as unary operators). It performs the operation one-bit at a time to the operand.

## Incomplete specification: adds unwanted latch circuit

if out is not assigned during any pass through the always block, then the previous value must be retained!


```

module maybe_mux_3to1(a, b, c,
                      sel, out);
    input [1:0] sel;
    input a,b,c;
    output out;
    reg out;

    always @(a or b or c or sel)
    begin
        case (sel)
            2'b00: out = a;
            2'b01: out = b;
            2'b10: out = c;
        endcase
    end
endmodule

```

Synthesized Circuit

 

- ♦ When  $sel = 2'b11$ ,  $G = 0$ , therefore the latch stores the previous output value as required by Verilog in this situation.

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 4

The consequence of this is an unexpected extra latch being added to the hardware. In order to cope with the unspecified condition of  $sel = 2'b11$ , the output of the MUX is fed to be latch.

Noted that a latch is **level-triggered**; a flipflop is **edge-triggered**. A latch has the property that when the gate input  $G$  is high,  $Q = D$  (i.e. it is **transparent**: input goes straight to output). If  $G$  is low, the latch become **opaque**, meaning that it retains the previous value.

The green shaded latch in the diagram and the controlling NAND gate are the unintended consequences of this incompletely specified 3-to-1 multiplexer.

## Always avoid incomplete specification

- ♦ Solution 1: Precede all conditionals with a default assignment for all signals:
- ♦ Solution 2: Fully specify all branches of if-else construct, or include a default statement in case construct:

```

always @(a or b or c or sel)
begin
    out = 1'bx;
    case (sel)
        2'b00: out = a;
        2'b01: out = b;
        2'b10: out = c;
    endcase
end
endmodule

always @(a or b or c or sel)
begin
    case (sel)
        2'b00: out = a;
        2'b01: out = b;
        2'b10: out = c;
        default: out = 1'bx;
    endcase
end
endmodule

```

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 5

There are two solutions to avoid the unintended latch being added.



**Solution 1** is to put outside the **case** statement a “**default**” value for out. Here **1'bx** (i.e. ‘x’) means **undefined**.

**Solution 2** is better: inside the **case** statement block, always add the **default** line. This will catch ALL the unspecified cases and avoid the introduction of the spurious unintended latches.

Lesson: always include a default assignment in any **case** statement to capture unintended incomplete specification.

## How to specify a sequential circuit?

- ♦ Edge-triggered flipflop is specified with: **always @ (posedge clk):**

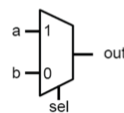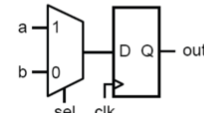Combinational cct	Sequential cct
<pre> module combinational(a, b, sel,                     out);     input a, b;     input sel;     output out;     reg out;     always @ (a or b or sel)     begin         if (sel) out = a;         else out = b;     end endmodule </pre>	<pre> module sequential(a, b, sel,                  clk, out);     input a, b;     input sel, clk;     output out;     reg out;     always @ (posedge clk)     begin         if (sel) out &lt;= a;         else out &lt;= b;     end endmodule </pre>
	

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 6

We have previously seen the 2-to-1 MUX being specified as combinational circuit in Verilog using the **always** construct with the **sensitivity list**.

The right hand diagram shows how a clocked **sequential circuit** is being specified using **always** block, but with a **sensitivity list** that includes the keyword **posedge** (or **negedge**). Note that the clocking signal **clk** is an arbitrary name – you could call it “**fred**” or anything else!


The **sensitivity list** NO LONGER contains the input signals **a**, **b** or **sel**. Instead the hardware is specified to be sensitive the positive edge of **clk**. When this happens, the output changes according to the specification inside the **always** block. Two assignments (“**=**” and “**<=**”) are shown here. I will explain the difference between these later.

## Synchronous clear in D-flipflop

- ♦ **posedge** and **negedge** makes an always block sequential and edge-triggered
- ♦ Sensitivity list in a sequential **always** block determines what circuit is synthesized

D flipflop with **synchronous** clear
 
```
module dff_sync_clear(d, clearb,
clock, q);
input d, clearb, clock;
output q;
reg q;
always @ (posedge clock)
begin
    if (!clearb) q <= 1'b0;
    else q <= d;
end
endmodule
```



+ve edge on clock triggers action in always block

- ♦ Beware of **race condition** if you have two or more always blocks – they execute in parallel!

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 7

Therefore in Verilog, you specify flipflops using **always block** in conjunction with the keyword **posedge** or **negedge**.

Here is a specification for a D-flipflop with synchronous clear which is low active (i.e. clear the FF when **clearb** is low).

You may have more than one **always** block in a module. But if this is the case, beware that the two **always** blocks will **execute in parallel**. Therefore they must NOT specify the same output, otherwise a **race condition** exists and the result is unpredictable.

## Blocking vs Non-blocking Assignments

- ♦ Verilog has two different types of assignments: **blocking** & **nonblocking**.
- ♦ Blocking assignments **=** are executed in the order they appear, therefore they are done one after another. Therefore the first statement "blocks" the second until it is done, hence it is called blocking assignments.

```
a = b;
b = a;
// both a & b = b
```

**blocking**

```
always @ (a or b or c)
begin
    x = a | b;
    y = a ^ b ^ c;
    z = b & ~c;
end
```

**blocking**

1. Evaluate  $a | b$ , assign result to  $x$

2. Evaluate  $a \wedge b \wedge c$ , assign result to  $y$

3. Evaluate  $b \& \sim c$ , assign result to  $z$

- ♦ Non-blocking assignments **<=** are executed in parallel. Therefore an earlier statement does not block the later statement. Note the subtle effect this has within **always** block:

```
a <= b;
b <= a;
// swap a and b
```

**Non-blocking**

```
always @ (a or b or c)
begin
    x <= a | b;
    y <= a ^ b ^ c;
    z <= b & ~c;
end
```

**Non-blocking**

1. Evaluate  $a | b$  but defer assignment of  $x$

2. Evaluate  $a \wedge b \wedge c$  but defer assignment of  $y$

3. Evaluate  $b \& \sim c$  but defer assignment of  $z$

4. Assign  $x$ ,  $y$ , and  $z$  with their new values

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 8

In Verilog '**=**' is known as **blocking assignment**. They are **executed in the order** they appear within the Verilog simulation environment. So the first '**=**' assignment blocks the second one. This is very much like what happens in C codes.

In the top left example, both **a** and **b** eventually have the value **b**.

In the top right example, each statement is evaluated in turn and assignment is performed immediately at the end of the statement.


**Non-block assignment** is '**<=**', and statements with this assignments are **executed in parallel** (i.e. order do not matter).

In the bottom left example, **a** and **b** are **swapped** over because you can view that the two assignments happen at the same time.

In the bottom right example, three evaluations are made, and the assignment to  $x$ ,  $y$  and  $z$  happens at the same time on exiting from the **always** block.
 
## Be careful to use the correct assignment

- Here are two versions of a 3-stage shift register consisting of 3 flipflops using blocking and nonblocking assignments.
- Will they give the same results?



```
module blocking(in, clk, out);
    input in, clk;
    output out;
    reg q1, q2, out;
    always @ (posedge clk)
    begin
        q1 = in;
        q2 = q1;
        out = q2;
    end
endmodule
```

```
module nonblocking(in, clk, out);
    input in, clk;
    output out;
    reg q1, q2, out;
    always @ (posedge clk)
    begin
        q1 <= in;
        q2 <= q1;
        out <= q2;
    end
endmodule
```

Understanding the difference between '=' and '<=' is important. Suppose we want to specify a three-stage shift register (i.e. three D-FF in series as shown in the schematic).

Here are two possible specification. Which one do you think will create the correct circuit and which one is wrong?



## Use NONBLOCKING assignment for sequential logic

```
always @ (posedge clk)
begin
    q1 = in;
    q2 = q1;
    out = q2;
end
```

```
always @ (posedge clk)
begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
end
```

- At each rising clock edge:  
 $q1 = in$ ,  
then  $q2 = q1 = in$ ,  
then,  $out = q2 = q1 = in$ .  
Therefore  $out = in$ , which is NOT the intention.

  - At each rising clock edge,  $q1$ ,  $q2$  and  $out$  simultaneously receive the old values of  $in$ ,  $q1$ ,  $q2$  respectively.




The left hand specification is **wrong**. Since the three assignments are performed in sequence,  $out = q2 = q1 = in$ . Therefore the resultant circuit is ONE D-flipflop. The right hand side is **correct**.  $q1$ ,  $q2$  and  $out$  are updated simultaneously on exit from the **always** block. Therefore their "original" values MUST be retained. Hence this will result in three D-flipflops being synthesised (i.e. created).

In general, you should always use '<=' inside an **always** block to specify your circuit.
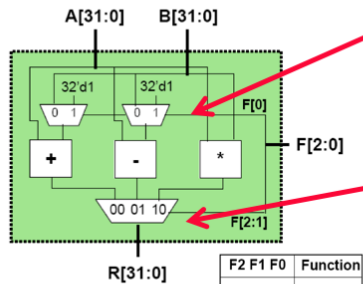
## A larger example – 32-bit ALU in Verilog

- Here is an 32-bit ALU with 5 simple instructions:



F2	F1	F0	Function
0	0	0	A + B
0	0	1	A + 1
0	1	0	A - B
0	1	1	A - 1
1	0	X	A * B

### 2-to-1 MUX

```
module mux32two(i0,i1,sel,out);
input [31:0] i0,i1;
input sel;
output [31:0] out;

assign out = sel ? i1 : i0;

endmodule
```

### 3-to-1 MUX

```
module mux32three(i0,i1,i2,sel,out);
input [31:0] i0,i1,i2;
input [1:0] sel;
output [31:0] out;
reg [31:0] out;

always @ (i0 or i1 or i2 or sel)
begin
case (sel)
2'b00: out = i0;
2'b01: out = i1;
2'b10: out = i2;
default: out = 32'bx;
endcase
end
endmodule
```

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design


Lecture 2 Slide 11

Now let us put all you have learned together in specifying (or designing) a 32-bit ALU in Verilog.

There are five operators in this ALU. We assume that there are three arithmetic blocks, and three multiplexers (two 2-to-1 MUX and one 3-to-1 MUX).
 
## The arithmetic modules

- Here is an 32-bit ALU with 5 simple instructions:



```
module mul16(i0,i1,prod);
input [15:0] i0,i1;
output [31:0] prod;

// this is a magnitude multiplier
// signed arithmetic later
assign prod = i0 * i1;

endmodule
```

```
module sub32(i0,i1,diff);
input [31:0] i0,i1;
output [31:0] diff;

assign diff = i0 - i1;

endmodule
```

```
module add32(i0,i1,sum);
input [31:0] i0,i1;
output [31:0] sum;

assign sum = i0 + i1;

endmodule
```

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 12

Each hardware block is defined as a Verilog module. So we have the following modules:

**mux32two** – a 32-bit multiplexer that has TWO inputs


**mux32three** – a 32-bit multiplexer that has THREE inputs

**mul16** – a 16-by-16 binary multiplier that produces a 32-bit product

**add32** – a 32-bit binary adder

**sub32** – a 32-bit binary subtractor
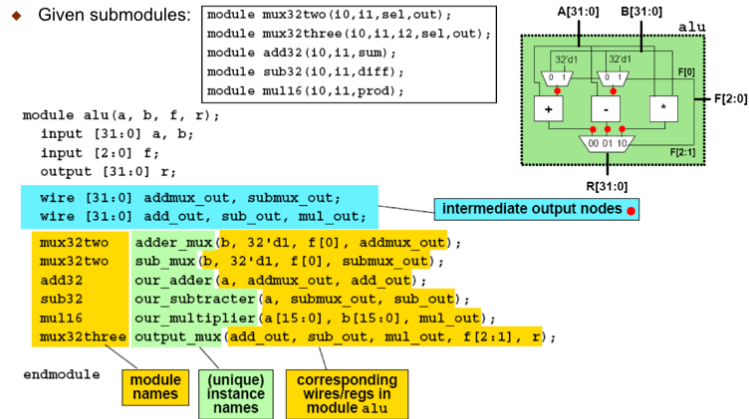
## Top-level module – putting them together



PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 13


Now let us put all these together.

Note that **mxu32two** is being used twice and therefore this is **instantiated** two times with two different **instance names**: **adder\_mux** and **sub\_mux**.

**Connections** between modules are implicit through the use of **signal names**. For example, the 16-bit inputs to the multiplier are taken from the lower 16-bits of **a** and **b** inputs (i.e. **a[15:0]** and **b[15:0]**).
 
## A Flexible Timer – clktick.v

- ◆ Instead of having a counter that count events, we often want a counter to provide a measure of **time**. We call this a timer.
- ◆ Here is a useful **timer** component that use a clock reference, and produces a pulse lasting for one cycle pulse every N+1 clock cycles.
- ◆ If "enable" is low (not enabled), the clkln pulses will be ignored.



```

module clktick (
    clkln, // Clock input to the design
    enable, // enable clk divider
    N, // Clock division factor is N+1
    tick // pulse_out goes high for one cycle (n+1) clock cycles
);
// End of port list

parameter N_BIT = 16;
//-----Input Ports-----
input clkln;
input enable;
input [N_BIT-1:0] N;
//-----Output Ports-----
output tick;
    
```

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 14

Counters are good in counting events (e.g. clock cycles). We can also use counters to provide some form of time measurement.

Here is a useful component which I can a clock tick circuit. We are not interested in the actual count value. What is needed, however, is that the circuit generates a single clock pulse (i.e. lasting for one clock period) for every N+1 rising edge of the clock input signal **clkln**.


We also add an enable signal, which must be set to '1' in order to enable the internal counting circuit.

Shown below is the module interface for this circuit in Verilog.

Note that the **parameter** keyword is used to define the number of bits of the internal counter (or the count value N). This makes the module easily adaptable to different size of counter.
 
## clktick.v explained

- ♦ "count" is an internal N\_BIT counter.
- ♦ We use this as a down (instead of up) counter.
- ♦ The counter value goes from N to 0, hence there are N+1 clock cycles for each tick pulse.



```
//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
reg [N_BIT-1:0] count;
reg tick;

initial tick = 1'b0;

//----- Main Body of the module -----

always @ (posedge clkln)
if (enable == 1'b1)
if (count == 0) begin
tick <= 1'b1;
count <= N;
end
else begin
tick <= 1'b0;
count <= count - 1'b1;
end

endmodule // End of Module clktick
```

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 15


The actual Verilog specification for this module is shown here.

There has to be an internal counter **count** whose output is NOT visible external to this module. This is created with the **reg [N\_BIT-1:0] count;** statement. The output **tick** has to be declared as **reg** here because its value is updated inside the always block.

Also note that instead of adding '1' on each positive edge of the clock, this design uses a **down** counter. The counter counts from N to 0 (hence N+1 clock cycles). When that happens, it is reset to N and the tick output is high for the next clock cycle.
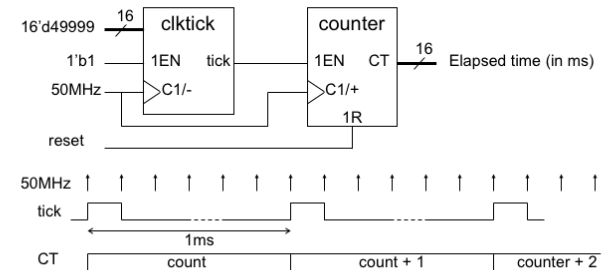
## Cascading counters

- ♦ By connecting **clktick** module in series with a counter module, we can produce a counter that counts the number of millisecond elapsed as shown below.



PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 16

Using this style of designing a clock tick circuit allows us to easily connect multiple counters in series as shown here.

The **clktick** module is producing a pulse on the **tick** output every 50,000 cycles of the 50MHz clock. Therefore **tick** goes high for 20 microsecond once every 1 msec (or 1KHz).

The **clktick** module is sometimes called a **prescaler** circuit. It prescale the input clock signal (50MHz) in order for the second counter to count at a lower frequency (i.e. 1KHz).


The second counter is now counting the number of millisecond that has been elapsed since the last time reset 1R goes high.

The design of this circuit is left as a tutorial problem for you to do.


 
## A clock divider

- ◆ Another useful module is a clock divider circuit.
- ◆ This produces a symmetrical clock output, dividing the input clock frequency by a factor of  $2^{*(K+1)}$ .



```

module clkdiv (
    clkdiv, // Clock input signal to be divided
    enable, // enable clk divider when high
    K, // Clock frequency divider is 2*(K+1)
    clkout // symmetric clock output Fout = Fin / 2*(K+1)
);
    //-----Input Ports-----
    input clkdiv;
    input enable;
    input [K_BIT-1:0] K;

    //-----Output Ports-----
    output clkout;

```


PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 17

Here is yet another useful form of a counter. I call this a clock divider. Unlike the **clktick** module, which produces a one cycle tick signal every  $N+1$  cycle of the clock, this produces a symmetric clock output **clkout** at a frequency that is  $2^{*(K+1)}$  lower than the input clock frequency. Shown here is the module interface in Verilog. Again we have used the **parameter** statement to make this design ease of modification for different internal counter size.

## clkdiv.v explained

 

```

//-----Output Ports Data Type-----
// Output port can be a storage element (reg) or a wire
reg [K_BIT-1:0] count;
reg clkout;

initial clkout = 1'b0;

//----- Main Body of the module -----

always @ (posedge clkdiv)
    if (enable == 1'b1)
        if (count == 10'b0) begin
            clkout <= ~clkout; // toggle the clock output signal
            count <= K; // shift right one bit
        end
        else
            count <= count - 1'b1;

endmodule // End of Module clkdiv

```


PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 18

The Verilog specification is similar to that for **clktick**. This also has an internal counter that counts from  $K$  to  $0$ , then the output **clkout** is toggled whenever the count value reaches  $0$ .
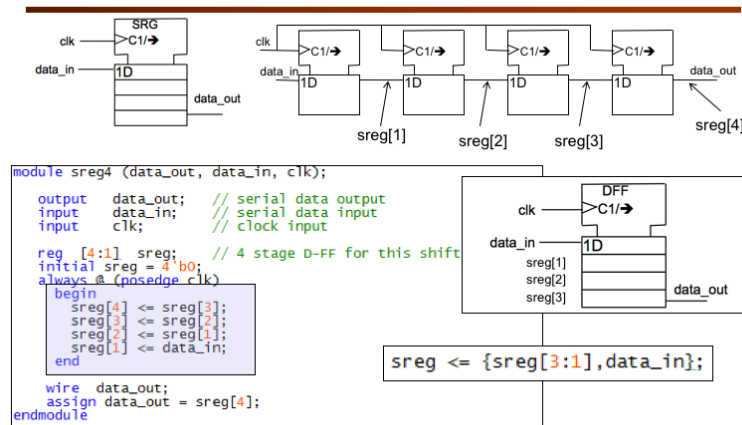
## Shift Register specification in Verilog



PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 19


To specify a shift register in Verilog, use the code shown here (in blue box). We use `<=` assignment to make sure that **sreg[4:1]** are updated only at the end of the always block.

On the right is a short-hand version of the four assignment statements:

```
sreg <= {sreg[3:1], data_in}
```

This way of specifying the input to the assignment is powerful. We use the concatenation operation `{ .... }` to make up four bits from **sreg[3:0]** and **data\_in** (with **data\_in** being the LSB) and assign it to **sreg[4:1]**.

## Linear Feedback Shift Register (LFSR)

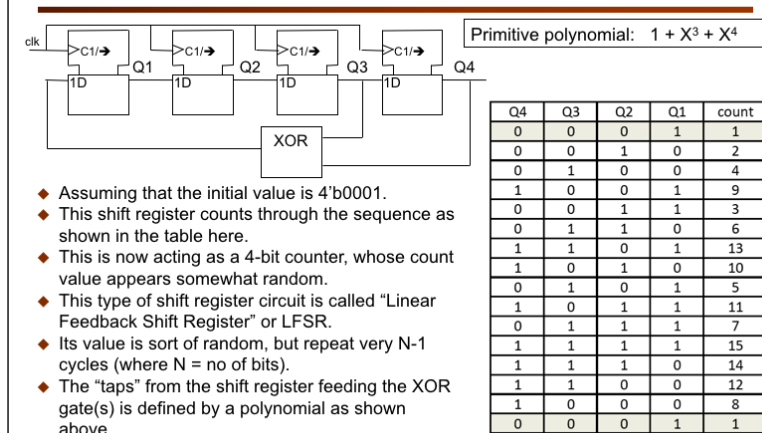

- Assuming that the initial value is 4'b0001.
- This shift register counts through the sequence as shown in the table here.
- This is now acting as a 4-bit counter, whose count value appears somewhat random.
- This type of shift register circuit is called "Linear Feedback Shift Register" or LFSR.
- Its value is sort of random, but repeat very N-1 cycles (where N = no of bits).
- The "taps" from the shift register feeding the XOR gate(s) is defined by a polynomial as shown above.

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 20

We can also make a shift register count in binary, but in an interesting sequence. Consider the above circuit with an initial state of the shift register set to 4'b0001. The sequence that this circuit goes through is shown in the table here. It is NOT counting binary. Instead it is counting in a sequence that is sort of **random**. This is often called a pseudo random binary sequence (or counter). The shift register connect this way is also known as a "Linear Feedback Shift Register" or LFSR. There is a whole area of mathematics devoted to this type of computation, known as "finite fields" which we will not consider on this course. The circuit shown below is effectively implementing a sequence defined by a polynomial shown:  $1 + X^3 + X^4$ . The term "1" specifies the input to the left-most D-FF. This signal is derived as an XOR function (which is the finite field '+' ) of two signals "tapped" from stage 3 (i.e.  $X^3$ ) and stage 4 (i.e.  $X^4$ ) of the shift register.


For a m stage LFSR, where m is an integer, one could always find a polynomial (i.e. tap configuration) that will provide maximal length. This means that the sequence will only repeat after  $2^m - 1$  cycles. Such a polynomial is known as a "primitive polynomial".

m		m	
3	$1 + X + X^3$	14	$1 + X + X^6 + X^{10} + X^{14}$
4	$1 + X + X^4$	15	$1 + X + X^{15}$
5	$1 + X^2 + X^5$	16	$1 + X + X^3 + X^{12} + X^{16}$
6	$1 + X + X^6$	17	$1 + X^3 + X^{17}$
7	$1 + X^3 + X^7$	18	$1 + X^7 + X^{18}$
8	$1 + X^2 + X^3 + X^4 + X^8$	19	$1 + X + X^2 + X^5 + X^{19}$
9	$1 + X^4 + X^9$	20	$1 + X^3 + X^{20}$
10	$1 + X^3 + X^{10}$	21	$1 + X^2 + X^{21}$
11	$1 + X^2 + X^{11}$	22	$1 + X + X^{22}$
12	$1 + X + X^4 + X^6 + X^{12}$	23	$1 + X^5 + X^{23}$
13	$1 + X + X^3 + X^4 + X^{13}$	24	$1 + X + X^2 + X^5 + X^{24}$

The table here shows some of the popular primitive polynomials for different value of m.

Since the output of such a counter is pseudorandom, it is a commonly used circuit to produce random binary sequence for different applications.

### lsfr4.v

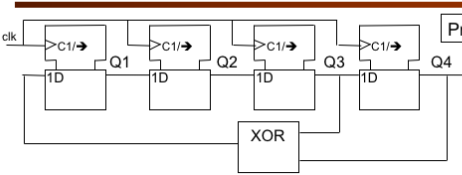

Primitive polynomial:  $1 + X^3 + X^4$


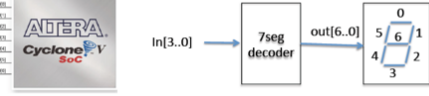
```

module lfsr4 (data_out, clk);
    output [4:1] data_out; // four bit random output
    input clk; // clock input
    reg [4:1] sreg; // 4 stage D-FF for this shift register
    initial sreg = 4'b1;
    always @ (posedge clk)
        sreg <= {sreg[3:1], sreg[4] ^ sreg[3]};
    assign data_out = sreg;
endmodule
    
```

PYKC 19 Oct 2017
MSc Lab – Mastering Digital Design
Lecture 2 Slide 21

Here is the Verilog specification for a 4-bit LFSR.

### Displaying a binary number as decimal

- ◆ As the part 1 of the Lab Experiment VERI, you will be implementing the 7 segment decoder we designed in the last lecture. This will show every four binary bits as a hexadecimal digit on the display.
- ◆ Hex numbers are difficult to interpret. Often we would like to see the binary value displayed as decimal. For that we need to design a combinational circuit to convert from binary to binary-coded decimal. For example, the value 8'hff or 8'b11111111 is converted to 8'd255 in decimal.

PYKC 19 Oct 2017
MSc Lab – Mastering Digital Design
Lecture 2 Slide 22


We now take another example of a relative complex combinational circuit, and see how we can specify our design in Verilog.

The goal is to design a circuit that converts an 8-bit binary number into three x 4-bit binary coded decimal values (i.e. 12 bit).

There is a well-known algorithm called “**shift-and-add-3**” algorithm to do this conversion. For example, if we take 8-bit hexadecimal number 8'hff (i.e. all 1’s), it has two hex digits. Once converted to binary coded decimal (BCD) it becomes 255 (3 BCD digits).
 
## Shift and Add 3 algorithm [1] – shifting operation

- Let us consider converting hexadecimal number 8'h7c (which is decimal 8'd124)
- Shift the 8-bit binary number left by 1 bit = multiply number by 2
- Shifting the number left 8 times = multiply number by  $2^8$
- Now truncate the number by dropping the bottom 8 bits = divide number by  $2^8$
- So far we have done nothing to the number – it has the same value
- The idea is that, as we shift the number left into the BCD digit "bins", we make the necessary conversion to the hex number so that it conforms to the BCD rule (i.e. falls within 0 to 9, instead of 0 to 15)



PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 23


Before we examine this algorithm in detail, let us consider the arithmetic operation of shifting left by one bit. This is the same as a  $\times 2$  operation.

If we do it 8 times, then we have multiplied the original number by 256 or  $2^8$ .

Now if you ignore the bottom 8-bit through a truncation process, you effectively divide the number by 256. In other words, we get back to the original number in binary (or in hexadecimal).
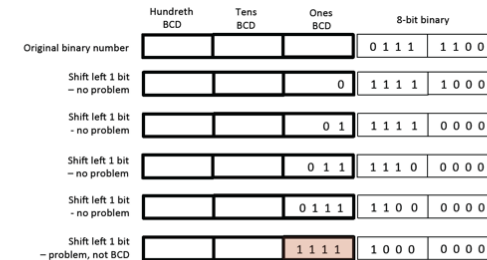
## Shift and Add 3 algorithm [2] – shift left with problem

- If we take the original 8-bit binary number and shift this three times into the BCD digit positions. After 3 shifts we are still OK, because the **ones digit** has a value of 3 (which is OK as a BCD digit).
- If we shift again (4<sup>th</sup> time), the digit now has a value of 7. This is still OK. However, no matter what the next bit is, another shift will make this digit illegal (either as hexadecimal "e" or "f", both not BCD).
- In our case, this will be a "f"!



PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 24

Our conversion algorithm works by shift the number left 8 times, but each time make an adjustment (or correction) if it is NOT a valid BCD digit.

Let us consider this example. We can shift the number four times left, and it will give a valid BCD digit of 7.

However, if we shift left again, then 7 becomes hex F, which is NOT valid. Therefore the algorithm demands that 3 is added to 7 (7 is larger or equal to 5) before we do the shift.

### Shift and Add 3 algorithm [3] – shift and adjust

- So on the fourth shift, we detect that the value is  $>$  or  $= 5$ , then we adjust this number by adding 3 before the next shift.
- In that way, after the shift, we move a 1 into the tens BCD digit as shown here.

	Hundreth BCD	Tens BCD	Ones BCD	8-bit binary
Original binary number				0 1 1 1 1 1 0 0
Shift left 1 bit - no problem			0	1 1 1 1 1 0 0 0
Shift left 1 bit - no problem			0 1	1 1 1 1 0 0 0 0
Shift left 1 bit - no problem			0 1 1	1 1 1 0 0 0 0 0
Shift left 1 bit - no problem			0 1 1 1	1 1 0 0 0 0 0 0
Perform adjustment Before shifting by adding 3			1 0 1 0	1 0 0 0 0 0 0 0
We perform adjustment (if $\geq 5$ , add 3) before shift			1 0 1 0 1	1 1 0 0 0 0 0 0

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 25

The rationale of this algorithm is the following. If the number is 5 or larger, after shift left, we will get 10 or larger, which cannot fit into a BCD digit. Therefore if the number 5 (or larger) we add 3 to it (after shifting is adding 6), which measure we carry forward a 1 to the next BCD digit.

### Shift and Add 3 algorithm [4] – full conversion

- In summary, the basic idea is to shift the binary number left, one bit at a time, into locations reserved for the BCD results.
- Let us take the example of the binary number 8'h7C. This is being shifted into a 12-bit/3 digital BCD result of 12'd124 as shown below.

	Hundreth BCD	Tens BCD	Ones BCD	8-bit binary
Original binary number				0 1 1 1 1 1 0 0
Shift left three times no adjust			0 1 1	1 1 1 0 0
Shift left Ones = 7, $\geq 5$			0 1 1 1	1 1 0 0
Add 3			1 0 1 0	1 1 0 0
Shift left Ones = 5			1 0 1 0 1	1 0 0
Add 3			1 1 0 0 0	1 0 0
Shift left 2 times Tens = 6, $\geq 5$			1 1 0 0 0 1 0	0
Add 3			1 0 0 1 0 0 1 0	0
Shift left BCD value is correct	1	0 0 1 0	0 1 0 0	

PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 26

To recap: the basic idea is to shift the binary number left, one bit at a time, into locations reserved for the BCD results. Let us take the example of the binary number 8'h7C. This is being shifted into a 12-bit/3 digital BCD result as shown above.


After 8 shift operations, the three BCD digits contain respectively: hundredth digit = 4'b0001, tens digit = 4'b0010 and ones digit = 4'b0100, thus representing the BCD value of 124.

The key idea behind the algorithm can be understood as follow (see the diagram in the slide):

- Each time the number is shifted left, it is multiplied by 2 as it is shifted to the BCD locations;
- The values in the BCD digits are the same as as binary if its value is 9 or lower. However if it is 10 or above it is not correct because for BCD, this should carry over to the next digit. A correction must be made by adding 6 to this digit value.
- The easiest way to do this is to detect if the value in the BCD digit locations are 5 or above BEFORE the shift (i.e. X2). If it is  $\geq 5$ , then add 3 to the value (i.e. adjust by +6 after the shift).
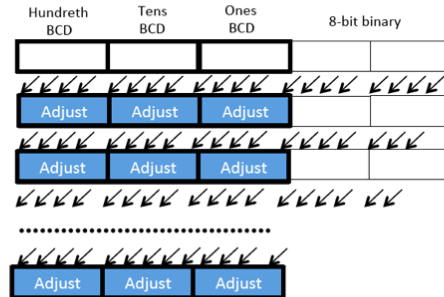
## Hardware implementation (1) – binary to BCD

- ◆ The hardware to perform binary to BCD conversion is shown below.
- ◆ Shifting is easy – just wiring all signals one position to the left.
- ◆ For each of the BCD locations, we need an “adjust” module which perform the follow operation: if the value is  $\geq 5$ , then add 3.



PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 27

In order to understand how to we may implement this converter in hardware, you have to understand that shifting in hardware is easy. You just need to connect signals with one bit shift to the left. It DOES NOT need any gates, just wires!

Now we also need to do the adjust module, which simply performs the operation:


**if (in  $\geq 5$ ) out = in + 3    else    out = in**

The easiest way to implement such a module is to use a **case statement**. This is set as a tutorial problem in Problem Sheet 1.
 
## Hardware implementation (2) – array of gates

- ◆ Here is the full array of logic gates to do the conversion.
- ◆ After 8 shift and adjustment on the way, the result should be three BCD digits.
- ◆ Each ADJUST block perform the following operation:

if (input  $\geq 5$ )  
    output = input + 3  
else  
    output = input



PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 28


The entire full array is shown here. The shade module is the adjust module (which we call: **add3\_ge5**).

As I said in the last slide, the easiest way to implement (specify) **add3\_ge5** is using a case statement.

The BLUE signal path traces what happens to the least significant bit of the original number.
 
### Hardware implementation (3) – propagate 0 to simplify

- ◆ If we now propagate forward all the 0s, we can eliminate all ADJUST modules except those in RED.
- ◆ All the others are just wires from input to output because the input values are GUARANTEED to be smaller than 5.



PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design


Lecture 2 Slide 29

The full array is more complicated than need be. If we propagate the '0's forward in the array of gates, you will find those marked with 'X' will always have its input less than 5. In which, **output = input** in these modules. THIS IS JUST A SET OF FOUR WIRES.

The only remaining **add3\_ge5** modules are those shaped in orange.
 
### Putting things together

- ◆ Once you have specified the **adjust module (A<sub>n</sub>)** in Verilog, you can wire up the entire converter as shown here:



PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 30

After simplification, here are ALL the remaining **add3\_ge5** modules for the 8-bit binary to BCD conversion (bin2bcd8). I have labeled the input ports to **add3\_ge3** **wn[3:0]** and the output parts **an[3:0]** where n is 1 to 7.

## Binary to BCD conversion in Verilog

- Here is the Verilog code to perform the 8-bit binary to BCD conversion:


```
module bin2bcd8 (b, BCD_0, BCD_1, BCD_2);
    input [7:0] b; // binary input number
    output [3:0] BCD_0, BCD_1, BCD_2; // BCD digit LSD to MSD

    wire [3:0] w1,w2,w3,w4,w5,w6,w7;
    wire [3:0] a1,a2,a3,a4,a5,a6,a7;

    // Instantiate a tree of add3-if-greater than or equal to 5 cells
    // ... input is w_n, and output is a_n
    add3_ge5 A1 (w1,a1);
    add3_ge5 A2 (w2,a2);
    add3_ge5 A3 (w3,a3);
    add3_ge5 A4 (w4,a4);
    add3_ge5 A5 (w5,a5);
    add3_ge5 A6 (w6,a6);
    add3_ge5 A7 (w7,a7);

    // wire the tree of add3 modules together
    assign w1 = {1'b0, b[7:5]}; // w1 is the input port to module An
    assign w2 = {a1[2:0], b[4]};
    assign w3 = {a2[2:0], b[3]};
    assign w4 = {1'b0, a1[3], a2[3], a3[3]};
    assign w5 = {a3[2:0], b[2]};
    assign w6 = {a4[2:0], a5[3]};
    assign w7 = {a5[2:0], b[1]};

     // connect up to four BCD digit outputs
    assign BCD_0 = {a7[2:0], b[0]};
    assign BCD_1 = {a6[2:0], a7[3]};
    assign BCD_2 = {2'b0, a4[3], a6[3]};
endmodule
```



PYKC 19 Oct 2017

MSc Lab – Mastering Digital Design

Lecture 2 Slide 31

Assuming that we have designed a module “**add3\_ge5**” to perform the adjustment as required, the converter can be implemented in Verilog by simply “WIRING UP” the various modules together.

The interconnections are specified in the wire statements.

The next block is instantiating 7 **add3\_ge5** modules.

The next block of code is to wire the modules together.

Finally the last statements are to connect up the signals from the modules to the output ports.