

## Lecture 5: More Gates and their Applications

Professor Peter Cheung  
Department of EEE, Imperial College London


(Floyd 3.6, 6.8-6.10)  
(Tocci 3.13-3.15, 4.6-4.8, 9.6-9.8)

## Points Addressed in this Lecture



- Exclusive-OR & Exclusive NOR gates
- Usefulness of Logic Gates (as functions)
- Parity Circuits using XOR gates
- Multiplexer and Demultiplexer circuits
- Alternative logic symbols – IEEE Standard
 
## Exclusive-OR

Exclusive-OR (XOR) produces a HIGH output whenever the two inputs are at opposite levels.




XOR gate symbols

 
 



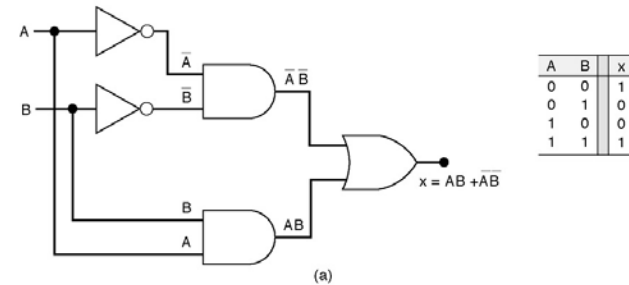
## Exclusive-XNOR

Exclusive-NOR (XNOR) produces a HIGH output whenever the two inputs are at the same level.





XNOR gate symbols

 
 


  

  XNOR gate may be used to simplify circuit implementation.




### Parity Generator and Checker

 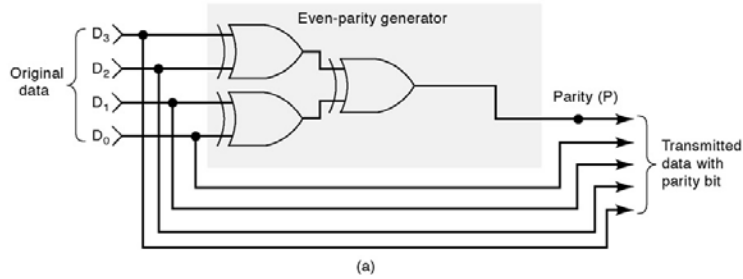

 
### Enable/Disable Circuits

AND gate function act as enable/disable circuits:-



 
## Enable/Disable Circuits cont.

Design a logic circuit that will allow a signal to pass to the output only when control inputs B and C are both HIGH; otherwise, the output will stay LOW.




 Design a logic circuit that will allow a signal to pass to the output only when one, but not both, of the control inputs are HIGH; otherwise, the output will stay HIGH.



 
## Merging & Inversion Circuits


OR gate performs signal merging function:-



 XOR gate performs selectable inversion function:-




## Multiplexers (Data Selectors)

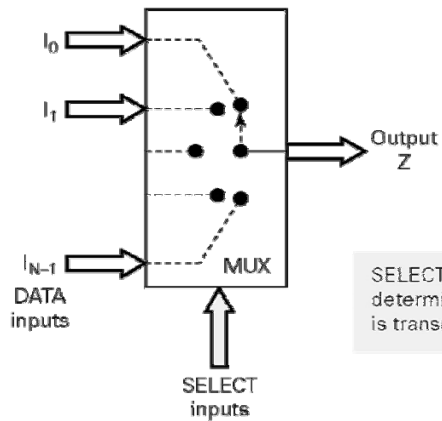

SELECT input code determines which input is transmitted to output Z.

## Multiplexers cont.

 


$$Z = I_0 \cdot \bar{S} + I_1 \cdot S$$


S	Output
0	$Z = I_0$
1	$Z = I_1$

Two-input multiplexer.

### Multiplexers cont.

 


Four-input multiplexer.

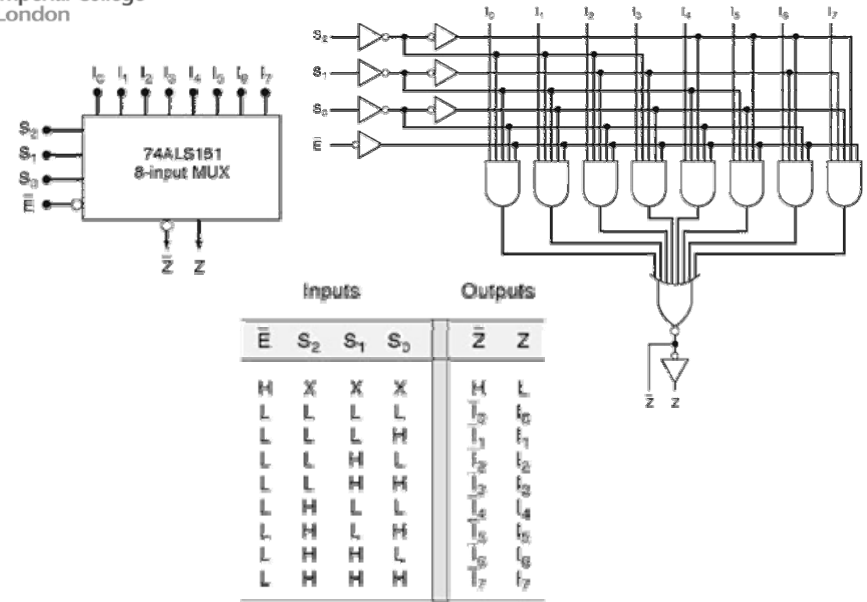
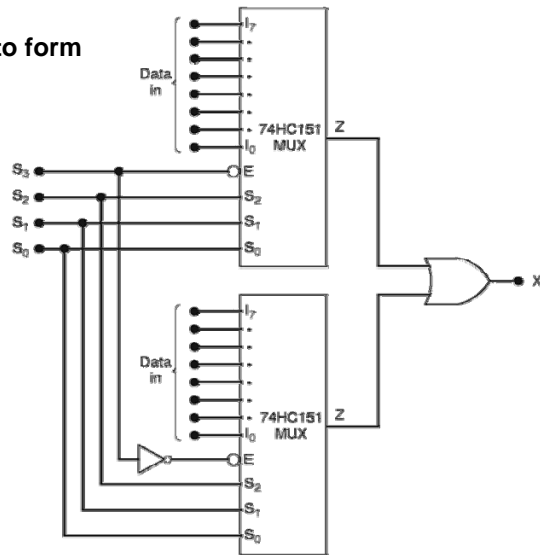
### Multiplexers cont.

two 74HC151s combined to form  
a 16-input multiplexer.




### Mux used to Implement Logic Function


$$f = \overline{A}BC + A\overline{B}C + ABC$$

$$f = \sum(3,4,7)$$

A	B	C	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


### Another example

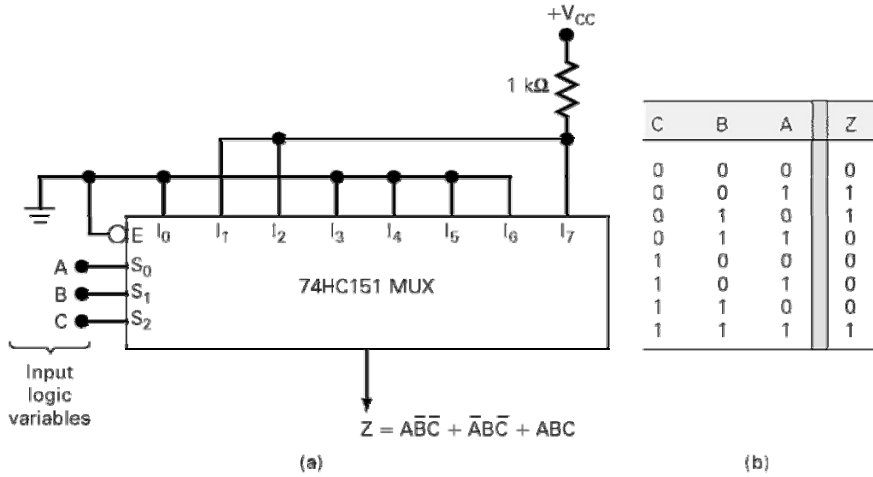

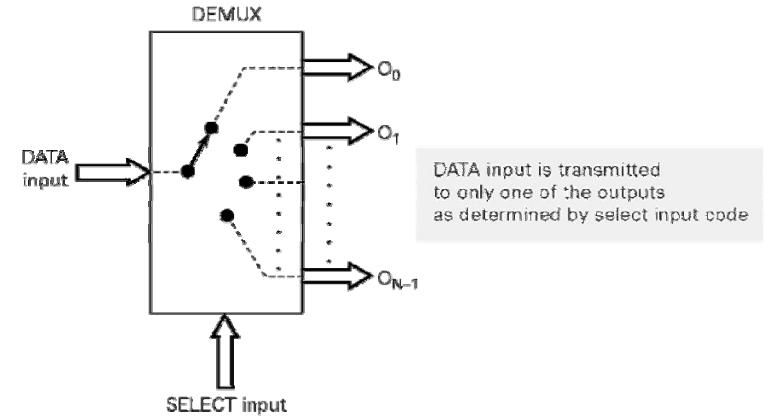
### Demultiplexers (Data Distributors)

A DEMUX takes a single input and distributes it over several outputs.




### Demultiplexers

#### • 2-line-to 4-line demux


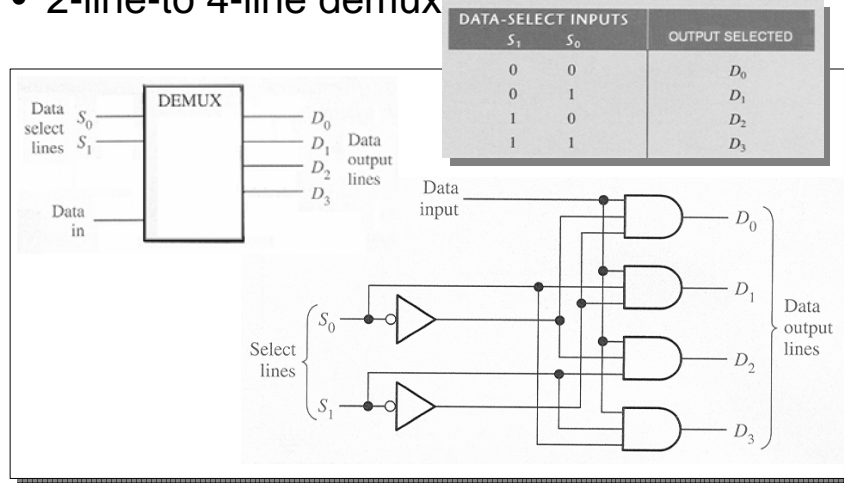

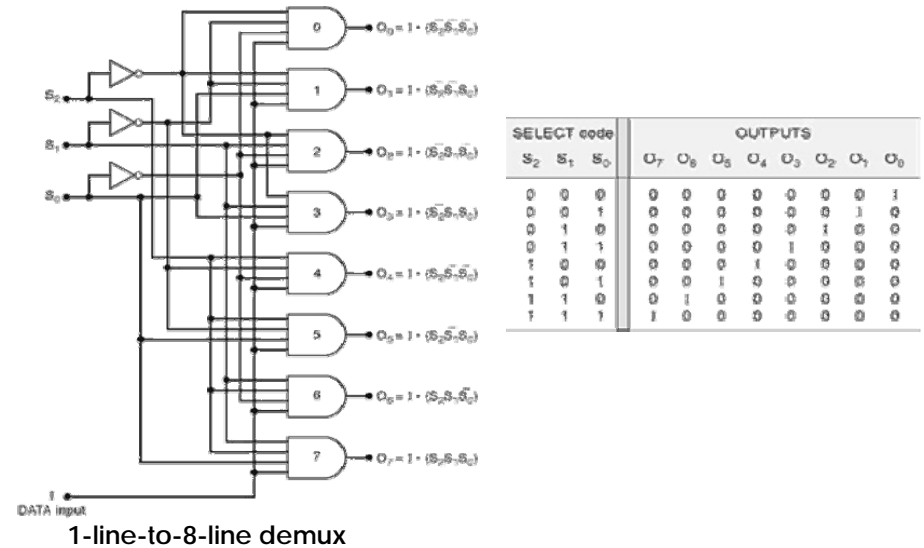
### Demultiplexers (Data Distributors) cont.


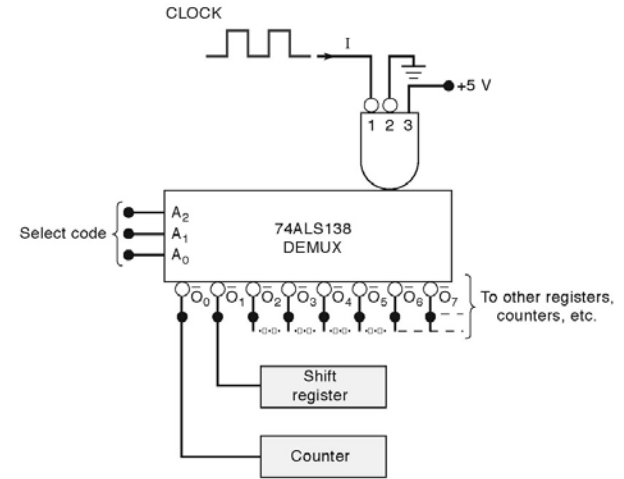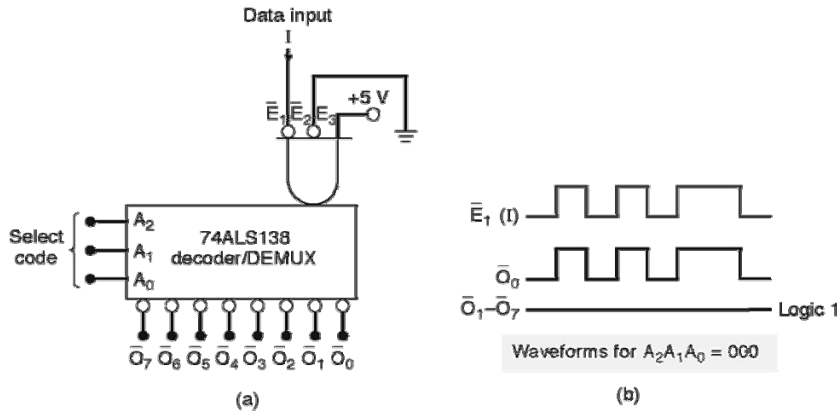
### Demultiplexers (Data Distributors) cont.


The 74ALS138 demultiplexer with  $E_1$  used as the data input. (b) Typical waveforms for a select code of  $A_2 A_1 A_0 = 000$  show that  $O_0$  is identical to the data input I on  $E_1$ .



A clock demultiplexer transmits the clock signal to a destination determined by the select code inputs.
 
### Alternative Symbols for Gates


- The symbols presented so far are International Standards of ANSI and IEEE
- Other (older) symbols are still widely used



- inputs are on the left, outputs on the right
- qualifying symbol top centre:

1	<b>Straight through (buffer)</b>		
&	<b>AND</b>	≥1	<b>OR</b>
=1	<b>XOR</b>	Σ	<b>Adder</b>
P	<b>Multiplier</b>	MUX	<b>Multiplexer</b>

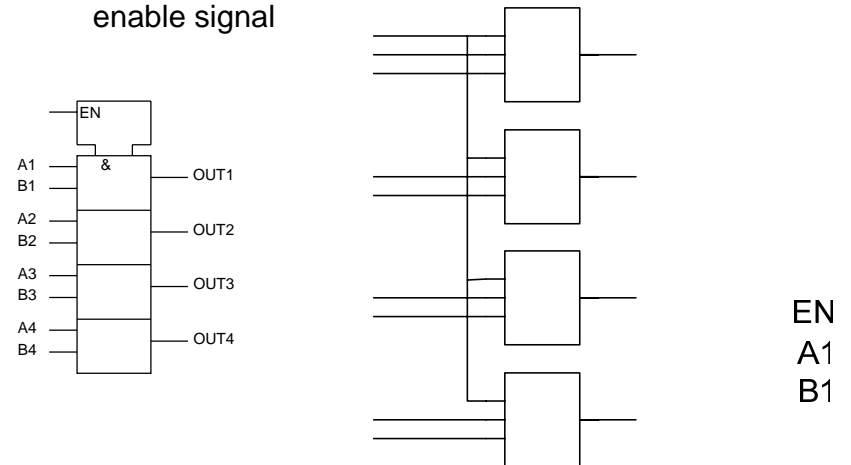- identical elements can be grouped as an array with common control signals
- Here is a 4 identical AND gates sharing a single enable signal




• Other Dependencies

Label	Name	On assertion ...	On de-assertion ...
EN	Enable	permits action	prevents action
G	AND (Gate)	permits action	forces output low
V	OR	forces output high	permits action
N	NOT (Invert)	Inverts output	No effect
S	Set	forces output high	No effect
R	Reset	forces output low	No effect

Numbered Dependencies

 
- Data inputs and outputs can be uniquely numbered
- Control input dependency labels can be followed by a number
  - indicates which inputs or outputs they affect
  - E.g.



- An array of buffers with
  - inputs (1) are ANDed with the ENABLE signal
  - outputs (2) are inverted if INV is asserted (active low)

Active High and Active Low Inputs

 - Consider a device with an additional "enable" input



- The chip is enabled if the Enable input is "asserted".
- What does asserted mean?
  - If the input is labelled EN, asserted means set Enable to 1
    - Active High
  - If the input is labelled  $\overline{EN}$ , asserted means set Enable to 0
    - Active Low

IEEE Standard symbol for 4-input MUX

