

Lecture 10: Sequential Circuits

Digital Electronics I

Digital Electronics I, Slide 10.1

Points Addressed in this Lecture

- ◆ Properties of synchronous and asynchronous sequential circuits
- ◆ Overview of flip-flops and latches

Digital Electronics I, Slide 10.2

Properties of Sequential Circuits

- ◆ So far we have seen Combinational Logic
 - the output(s) depends only on the current values of the input variables
- ◆ Here we will look at Sequential Logic circuits
 - the output(s) can depend on present and also past values of the input and the output variables
- ◆ Sequential circuits exist in one of a defined number of states at any one time
 - they move "sequentially" through a defined sequence of transitions from one state to the next
- ◆ The output variables are used to describe the state of a sequential circuit either directly or by deriving state variables from them

Digital Electronics I, Slide 10.3

Synchronous and Asynchronous Sequential Logic

- ◆ Synchronous
 - the timing of all state transitions is controlled by a common clock
 - changes in all variables occur simultaneously
- ◆ Asynchronous
 - state transitions occur independently of any clock and normally dependent on the timing of transitions in the input variables
 - changes in more than one output do not necessarily occur simultaneously
- ◆ Clock
 - A clock signal is a square wave of fixed frequency
 - Often, transitions will occur on one of the edges of clock pulses
 - i.e. the rising edge or the falling edge

Digital Electronics I, Slide 10.4

Truth Tables

- Just as for combinational circuits, sequential circuits can be described using truth tables
- In sequential circuits, truth tables include the idea of transitions in time

A	B	Q+
0	0	Q
0	1	0
1	0	1
1	1	X

Notes

- Q is the output before a change in inputs
- Q+ is the output after a change in inputs
- X is don't care

- For synchronous circuits Q+ is the value of Q at the next clock pulse

Flip-Flops

- Flip-flops are the fundamental element of sequential circuits

- bistable
- (gates are the fundamental element for combinational circuits)

- Flip-flops are essentially 1-bit storage devices

- outputs can be set to store either 0 or 1 depending on the inputs
- even when the inputs are de-asserted, the outputs retain their prescribed value

- Flip-flops have (normally) 2 complimentary outputs


- Q and \bar{Q}

- Three main types of flip-flop

- R-S J-K D-type

R-S Flip-Flop

Symbols

 

Operation

- Asserting S sets Q to 1 and \bar{Q} to 0
- Asserting R resets Q to 0 and \bar{Q} to 1
- In the asynchronous flip-flop the outputs change immediately following the changes in the inputs
- In the synchronous flip-flop the outputs change on the next clock pulse after the changes in the inputs

Truth Table

S	R	Q+
0	0	Q ***
0	1	0
1	0	1
1	1	X


- the "memory" in this device can be seen in the truth table row marked ***

- i.e. when S=R=0, the output holds onto its value

- in a synchronous flip-flop the Q output changes on the next clock


- the input condition S=R=1 produces an undefined output X
- this combination of inputs would normally be avoided in a design

Construction of a Bistable Circuit

 

J-K Flip-Flop

◆ Symbol

 

◆ Operation

- The J-K flip-flop is a synchronous device
- Inputting J=1 and K=0 sets Q to 1 and Q-bar to 0 after the next clock pulse
- Inputting J=0 and K=1 resets Q to 0 and Q-bar to 1 after the next clock pulse
- Additional S and R inputs are sometimes included to permit asynchronous set and reset of the outputs respectively. These signals override the J and K inputs.

◆ Truth Table




J	K	Q+
0	0	Q
0	1	0
1	0	1
1	1	Q-bar

◆ Notes

- the first 3 lines of the truth table are the same as for R-S flip-flop
- all input combinations have defined outputs
- Q+ indicates the value of Q after the next clock pulse
- inputting J=K=1 causes the output to toggle on each clock pulse
 - you might call this a Toggle flip-flop

D Flip-Flop

◆ Symbol

 

Operation

- The D-type flip-flop is a synchronous device
- It has one data input and a clock.
- On the rising edge of the clock the data on D goes to the output Q



◆ Truth Table



D	Q+
0	0
1	1


◆ Notes

- Probably the simplest flip-flop and very widely used

Transparent Latch

- A latch is a device which “latches” data for use at a future time.
- The D-type flip-flop can do this - so can a transparent latch

◆ Symbol

 

◆ Truth Table

ENABLE	Q+
0	Q
1	DATA

◆ Operation



- When ENABLE goes to 0, Q is "latched" (held at its current value)
- When ENABLE is 1, Q is the same as DATA

Transparent Latch Implementation

- ◆ Tocci page 205

Edge-Triggering

- ◆ Synchronous flip-flops change state on the edge of a clock pulse




◆ Positive edge triggered:

- changes state on the 0 to 1 transition of the clock



◆ Negative edge triggered:

 - changes state on the 1 to 0 transition of the clock



- ◆ D-types are positive edge triggered
- ◆ J-Ks are negative edge triggered
 - need to check on the data sheet for a particular device
- ◆ For internal design of flip-flops see:
 - section 4.3 of Wilkinson and
 - (The internal design of flip-flops is non-examinable material in this course)