

Lecture 10: More on Flip-flops

Professor Peter Cheung
Department of EEE, Imperial College London

Points Addressed in this Lecture


- Introduction to Moore model and Mealy model state diagrams
- State diagrams and state tables of flip-flops
- Timing parameters of flip-flops

State Diagrams

- There are two ways to draw state diagrams:
 - **Moore** model and **Mealy** model
 - we will look first at the Moore model using the Reset-Set (RS) flip-flop as an example
- A Moore model state diagram shows
 - a circle for each of the various "states" a circuit can be in
 - "states" refers to the logic levels around the circuit
 - labels in the circles to show the state number and the associated output for that state
 - an arrow for each possible transition between states
 - labels on the arrows to show the required conditions to transit between states

State Diagram of RS Flip-Flop

 - The circuit must be in either state 1 or state 2.



- In state 1
 - Q output = 0
 - an input of S=1, R=0 causes a transition to state 2
 - any other input leaves the circuit in state 1
 - (an input of S=R=1 is not allowed for RS flip-flops)
- In state 2
 - Q output = 1
 - an input of S=0, R=1 causes a transition to state 1
 - any other input leaves the circuit in state 2

State Table of RS-Flip-Flop

- A state table is a tabular form of the state diagram
 - one row for each possible state
- Shows the next state which will be entered for all possible combinations of inputs
- The ordering of the inputs is same as for Karnaugh map

- Example

Present State	Next state inputs: SR			
	00	01	11	10
1	1	1	X	2
2	2	1	X	2

- The circuits is in state 2; the inputs are S=1, R=0. What is the next state?
 - state 2

Assigned State Table of RS-Flip-Flop

- Differs from a State Table by showing the associated outputs not the state numbers
- Example

Present Output	Next output inputs: SR			
	00	01	11	10
0	0	0	X	1
1	1	0	X	1

- The output of the circuits is 1; the inputs are S=1, R=0. What is the next output?
 - 1

Boolean Expression from Assigned State Table

- We continue the example of the RS flip-flop and call the "next output" Q+
- The assigned state table defines the logical relationship between the inputs (S and R) and Q+
 - a Boolean relationship
- Hence we can re-draw the assigned state table as a Karnaugh map

Q\SR	00	01	11	10
0	0	0	X	1
1	1	0	X	1

Q \ SR	00	01	11	10
0	0	0	X	1
1	1	0	X	1

- The Boolean expression is then obtained by grouping terms as usual

$$Q^+ = Q\bar{R} + S$$

$$\bar{Q}^+ = \bar{Q}\bar{S} + R$$


- Such equations are called **characteristic equations**

Implementation from Characteristic Equations

- The flip-flop can be implemented using gates
- It is common to re-write using NAND gates only

$$Q^+ = \overline{\overline{Q\bar{R}} \cdot \bar{S}}$$

 
$$\bar{Q}^+ = \overline{\overline{\bar{Q}\bar{S}} \cdot R}$$



Asynchronous RS Flip-flop

JK State Implementation

- Moore Model State Diagram

 

- Assigned State Table

Present Output	Next output inputs: JK			
	00	01	11	10
0	0	0	1	1
1	1	0	0	1

- Characteristic Equation


$$Q^+ = J\bar{Q} + \bar{K}Q = \overline{\overline{J\bar{Q}} \cdot \overline{\bar{K}Q}}$$

- when J=1, K=0 then $Q^+ = \bar{Q} + Q = 1$
- when J=0, K=1 then $Q^+ = 0$
- when J=1, K=1, then $Q^+ = \bar{Q}$ (toggle)

- Note that the JK is not normally implemented directly from this equation
- A master-slave configuration is used instead

D-type Implementation

- Moore Model State Diagram

 

- Assigned State Table


Characteristic Equation

Present Output	Next output	
	0	1
0	0	1
1	0	1

$$Q^+ = D$$


Mealy Model State Diagrams

 - Similar principles to Moore model but different labelling
- State circles are labelled only with state numbers
- Outputs are written next to inputs on the arrows
- E.g. JK Flip-flop




Timing Parameters of Flip-flops

 - For correct operation of flip-flops
 - data inputs must not change either just before or just after clock pulses
- If data changes near the clock the flip-flop might enter a metastable state
 - neither 0 nor 1
- The amount of time before and after the clock pulse in which data transitions are not allowed are called:
 - setup and hold times
 - defined by the manufacturer



Cascaded Flip-flops

 - Hold time of a flip-flop is always less than the propagation delay between CLOCK and Q
- Rising edge of CLOCK causes the data at A to go to B and data at B to go to C in example below



- What data does C end up with?
 - B doesn't change immediately because of the propagation delay
 - The input to the second flip-flop is value of B just before the CLOCK rising edge i.e. B->C; A->B
- Hence
 - This circuit shifts the data one position to the right on each clock pulse