

Lecture 11: Circuits using Flip-flops

Professor Peter Cheung
Department of EEE, Imperial College London

(Floyd 7.4, 8.1, 9.1)
(Tocci 5.17-18, 7.1, 7.19-20)


Points Addressed in this Lecture

- Registers and shift registers
- Synchronous and asynchronous counters


Registers

- A register is a digital electronic device capable of storing several bits of data
 - Normally made from D-type flip-flops with asynchronous RESET inputs
 - Operates on the bits of the data word in parallel (parallel in / parallel out)
- Operation
 - Data on each data input is stored in the flip-flop on the rising edge of CLOCK
 - The data can be read from the Q outputs
 - New data can be reloaded by re-CLOCKing the register
 - The register can be cleared (zeroed) by asserting the CLEAR inputs

3-bit Parallel in/Parallel out

 


- Symbol

 

Shift Registers

 
- Application Examples
 - Multiplication and division by integer power of 2
 - Conversion of data between parallel formats and bit-serial formats
- Construction
 - Like ordinary registers but with Q outputs connected to D inputs of the following flip-flop
 - E.g.: 3-bit shift register




- Operation
 - On the rising edge of the clock, each bit moves right by one flip-flop
 - All the flip-flops can be asynchronously reset
 - Parallel data can be asynchronously loaded into flip-flops using the P signals
 - The data at the output of each flip-flop can be read from the Q signals hence
 - bits can be input serially at Din and output serially from Q2 with a delay of 3 clocks
 - bits can be input serially at Din and output in parallel from Q2:0 after 3 clocks

Divide by 2 Circuit

 - Consider a D-type flip-flop with \bar{Q} connected to D



 
- D is always the inverse of Q hence Q will always toggle on a rising clock edge



- The frequency of Q is half the frequency of CLOCK

Binary Counters


- Example: 3-bit counter

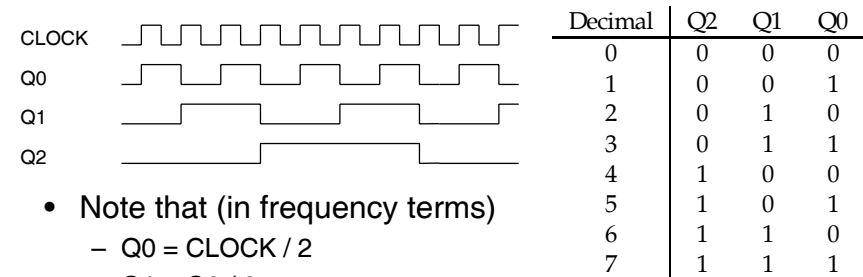

- Note that (in frequency terms)
 - $Q0 = \text{CLOCK} / 2$
 - $Q1 = Q0 / 2$
 - $Q2 = Q1 / 2$

Asynchronous Binary Counter

 - Asynchronous counters are made from flip-flops
 - NOT all clocked with the same clock
 - sometimes called ripple counters
 - can be implemented using divide by 2 circuits
 - e.g. 3 bit counter



Notes

- called asynchronous because the C1 inputs of the flip-flops are not all driven by the same (CLOCK) signal
- each output depends on a change in the previous flip-flops output
- sometimes called a ripple counter because the data "ripples" from the output of one flip-flop to the input of the next
- can also be implemented in JK

Limitations


- Consider the change from count 3 to count 4
 - CLOCK goes from low to high
 - Q0 goes from high to low
 - Q1 goes from high to low
 - Q2 goes from low to high
- The "CLOCK-TO-Q" delay of a typical flip-flop is about 30 ns
 - Hence total time needed is about 90 ns.
 - Hence max CLOCK frequency is = 11.1 MHz
- The time needed for such transitions increases with the number of bits in the counter

Synchronous Binary Counters

- All flip-flops clocked with the same signal
 - hence all outputs change simultaneously
- the sequence of the count is controlled by combinational logic
 - sometimes called the state sequence
 - note that synchronous binary counters use both sequential and combinational elements

Example: 3-bit up-counter

- State Diagram

 


- From the state diagram we can construct a state transition table (let the variables be A (MSB), B and C)

Current State			Next State		
A	B	C	A+	B+	C+
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Implementation

 - Use a register of flip-flops + Logical combinations of state variables
- E.g. For D-type Flip-flops



- The design task is to find a combinational circuit for ?
 - It should give the D inputs from the Q outputs such that, on the next clock, the correct counting sequence is followed
 - Other flip-flops can be used, e.g. J-K.