 







## Delays

- A shift register can be used as a delay element
  - Each Q output lags behind the D input by successive numbers of clock periods



- Synchronous Delay
  - The input signal DIN is aligned with the clock
  - The outputs Q0, Q1, Q2 will be delayed by 1,2 and 3 CLOCK periods respectively
- Asynchronous Delay
  - The input signal DIN is NOT aligned with the clock
  - The Q0 output will be delayed by up to 1 clock period
  - Q1 and Q2 will be delayed by further whole clock periods


## Timing Diagram of Shift Register

 

**Note:** These timing diagrams do not show the CLOCK-to-Q delays of the flip-flops. In practice, changes in output will follow slightly later than the rising edge of the CLOCK
 
## Ring Counter

- A ring counter is made from a shift register with the output of the last bit fed to the input of the first bit



• Transition Table

– The above can be summarised in the following table

Q3	DIN	Q0:3	(Q0:3)+
0	0	n	2n
0	1	n	2n+1
1	0	n	2n-16
1	1	n	2n-15

- Now reconnect the feedback from Q3 to DIN
- the operation of the ring counter follows the top and bottom lines of the table only

## Serial Adder

• Bit-serial data


- Normally when we think of binary numbers represented in digital electronic hardware, we think of parallel data
  - one connection per bit
  - all bits processed together
- In bit-serial data, the bits making up a binary number are processed one bit at a time
  - takes longer but
  - simplifies the hardware

Eg.

- to add two 8-bit numbers in parallel requires 8 full adders
- to add two 8-bit numbers bit-serially requires only 1 full adder and some registers
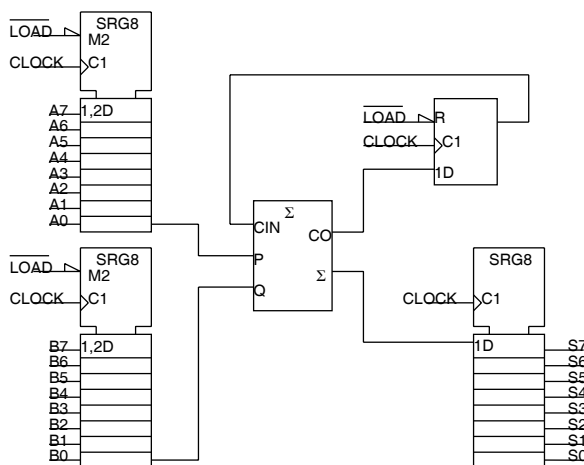
### Circuit Diagram for Bit-serial Adder



- The 2 numbers to be added (A0:7 and B0:7) are stored in shift registers.
- The bits of A and B are presented to a 1-bit adder one bit at a time starting with the LSB.
- The flip-flop stores the carry from the previous summation and is initialised to 0, ie. CIN=0 for the addition of the LSBs
- After 8 clock periods the result is stored in the output shift register S0:7.



## Schmitt Trigger


- Slowly changing input transitions may cause oscillations on the output of digital devices

– EG: inverter

  


- Schmitt Trigger circuits produce “clean” outputs

 - this is achieved by having different thresholds for low-to-high and high-to-low transitions.
- known as hysteresis



 
## FSM Example – Vending Machine

- Step 1: Define the problem
  - Accepts 10p and 20p coins
  - Delivers a can of drink costing 30p
  - Provide change where appropriate




- Assumptions:
  - One coin at a time
  - Generate pulse p10 or p20 lasting for one clock cycle when coin inserted
  - vend = 1 for one clock period to deliver a coke
  - change = 1 for one clock period to return a 10p coin

## Step 2: Draw State Diagram

 


- FSM remains in S0 until there is a p20 or p10 input
- S1 represents 10p credit
- S2 represent 20p credit
- S3 represent 40p credit

## Step 3: Reduce state diagram

 

- Two states are said to be **equivalent** if they have
  - identical next states
  - Identical outputs
- Therefore  $S3 \equiv S2$

## Step 4: Ensure no undefined states

 

### Step 5: Draw State Transition Table

		Inputs p20: p10			
		00	01	11	10
Current State	S0p	S0p,00	S10p,00	xx,xx	S20p,00
	S10p	S10p,00	S20p,00	xx,xx	S0p,10
	S20p	S20p,00	S0p,10	xx,xx	S0p,11
	Sbad	S0p,00	S0p,00	xx,xx	S0p,00

Next State

Outputs vend: change

### Step 6: Assign binary value to states


S0p = 00  
S10p = 01  
S20p = 11  
Sbad = 10

		Inputs p20: p10			
		00	01	11	10
Current State	S0p	00,00	01,00	xx,xx	11,00
	S10p	01,00	11,00	xx,xx	00,10
	S20p	11,00	00,10	xx,xx	00,11
	Sbad	00,00	00,00	xx,xx	00,00

Next State n1: n0

Outputs vend: change

### Step 7: Hardware design

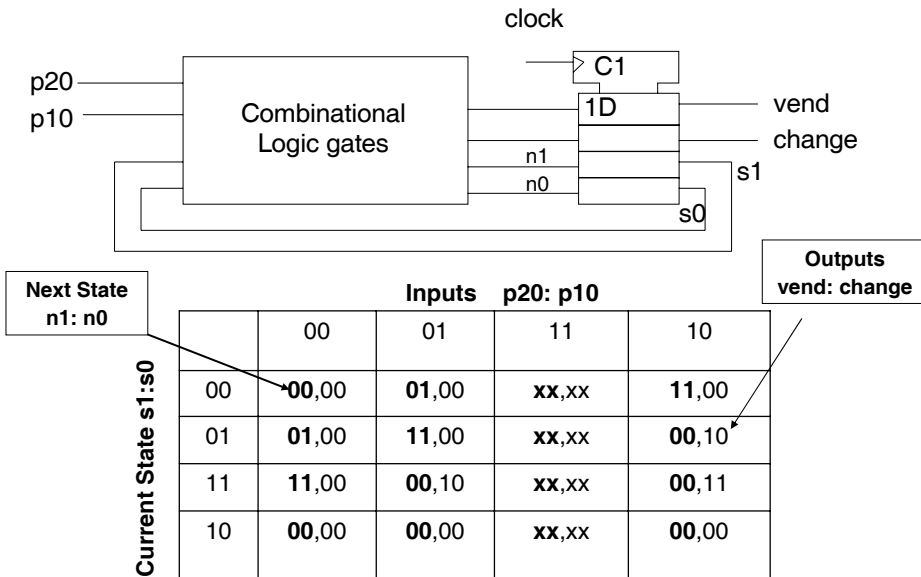

### Step 8: Draw Karnaugh Map for each output variable

		Inputs p20: p10				
		n1	00	01	11	10
Current State s1:s0	00	0	0	x	1	
	01	0	1	x	0	
	11	1	0	x	0	
	10	0	0	x	0	

		Inputs p20: p10				
		n0	00	01	11	10
Current State s1:s0	00	0	1	x	1	
	01	1	1	x	0	
	11	1	0	x	0	
	10	0	0	x	0	

$$n1 = s1 s0 \overline{p20} \overline{p10} + s1 s0 p10 + s1 s0 p20$$

$$n0 = s0 \overline{p20} \overline{p10} + s1 p10 + n1 n0 p20$$

Inputs p20: p10

Current State s1:s0	vend	00	01	11	10
00	0	0	x	0	
01	0	0	x	1	
11	0	1	x	1	
10	0	0	x	0	

$$vend = s1 s0 p10 + s0 p20$$

Inputs p20: p10

Current State s1:s0	change	00	01	11	10
00	0	0	x	0	
01	0	0	x	0	
11	0	0	x	1	
10	0	0	x	0	

$$change = s1 \bar{s0} p20$$