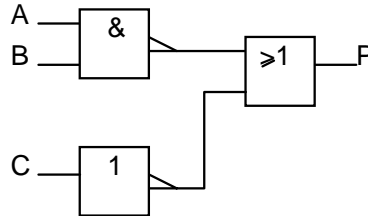


# Digital Electronics

## Tutorial Sheet 6

---

1.\*\* Show that the following circuit is equivalent to a single gate.




2.\* Give two ways of showing inversion at the output of gates.

3.\*\* Given a two input multiplexer, write down its truth table and hence use it to implement a) an AND gate and b) an OR gate.

4.\*\*\* For a multiplexer with control inputs A and B, derive the required data inputs to implement (i) the carry function of a full adder (ii)  $f = (A + B)(\bar{A} + \bar{C})$ .

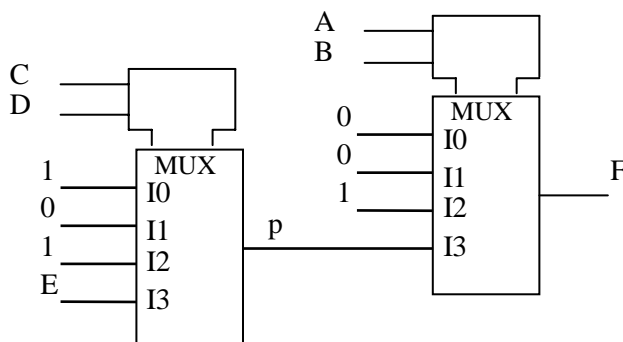5.\*\*\* What is the logic function of the MUX circuit below?



6.\*\* Redesign the parity generator and checker circuit given in the Lecture to operate using odd parity.

7.\*\* Determine the input conditions needed to produce  $x=1$  for the circuit below.

